

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L

## Application note

**Authors:** Peter B. Green, Kali Naraharisetti, Weidong Fan, Isabel Alvarez

## About this document

### Scope and purpose

The purpose of this document is to provide a comprehensive functional description and guide to using the DEMO\_100W\_24VDC\_FB single-stage PFC Flyback power supply evaluation board based on the IRS2982S and IR1161L controllers. It describes the operation and covers technical aspects essential to the design process, including calculation of external component values, MOSFET selection and PCB layout optimization, as well as additional protection circuitry that may be added if needed. Test results and waveforms are also included.

### Intended audience

Power supply design engineers, applications engineers, students.

## Table of contents

|  |           |
|--|-----------|
| <b>About this document</b> .....                             | <b>1</b>  |
| <b>Table of contents</b> .....                               | <b>1</b>  |
| <b>1 Introduction</b> .....                                  | <b>3</b>  |
| <b>2 Evaluation board specifications</b> .....               | <b>4</b>  |
| <b>3 Schematics</b> .....                                    | <b>5</b>  |
| <b>4 IRS2982S functional overview</b> .....                  | <b>8</b>  |
| <b>5 Flyback converter</b> .....                             | <b>9</b>  |
| 5.1 Flyback converter types .....                            | 9         |
| <b>6 IR1161L functional overview</b> .....                   | <b>10</b> |
| <b>7 Design calculations</b> .....                           | <b>12</b> |
| 7.1 Voltage feedback and loop compensation.....              | 14        |
| 7.2 Output capacitor calculation.....                        | 18        |
| 7.3 MOT resistor calculation for IR1161L.....                | 18        |
| <b>8 Protection features</b> .....                           | <b>19</b> |
| 8.1 Brown-out protection .....                               | 19        |
| 8.2 Overload and short-circuit protection .....              | 20        |
| <b>9 Bill of Materials (BOM)</b> .....                       | <b>21</b> |
| <b>10 PCB layout</b> .....                                   | <b>24</b> |
| 10.1 PCB layout guidelines for system optimization .....     | 25        |
| <b>11 Flyback transformer specifications</b> .....           | <b>26</b> |
| <b>12 Test results</b> .....                                 | <b>27</b> |
| 12.1 Operation under different line and load conditions..... | 27        |
| 12.2 Power factor and input current harmonics (iTHD) .....   | 31        |

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L

---



## Introduction


|           |   |           |
|-----------|---|-----------|
| 12.1      | Operating waveforms.....                                    | 35        |
| 12.2      | Thermal performance under normal operating conditions ..... | 44        |
| 12.3      | Conducted EMI .....   | 46        |
| <b>13</b> | <b>Conclusion .....</b>                                     | <b>48</b> |
|           | <b>References.....</b>                                      | <b>49</b> |
|           | <b>Revision history.....</b>                                | <b>50</b> |

## Introduction


### 1 Introduction

The IRS2982S is a versatile SMPS controller IC primarily intended for power supply and LED drivers in the 5 to 100 W power range suitable for buck, buck-boost and Flyback converters operating in Critical Conduction Mode (CrCM) and Discontinuous Conduction Mode (DCM) at light loads. Flyback converters will be covered in this application note, focusing on an isolated voltage-regulated design with Power Factor Correction (PFC). All of the control and protection required for the converter is integrated in the IRS2982S as well as a HV start-up cell to enable rapid start-up at switch-on over a wide line input voltage range. The IRS2982S is also able to provide PFC in a single-stage Flyback converter able to meet class D line current harmonic limits of the EN 61000-3-2 standard.

A 100 W isolated constant voltage-regulated PFC Flyback evaluation board based on the IRS2982S controller is described in detail in this application note and detailed test results are presented.

 

**Figure 1** DEMO\_100W\_24VDC\_FB single-stage PFC Flyback converter demo board (top view)

 

**Figure 2** DEMO\_100W\_24VDC\_FB single-stage PFC Flyback converter demo board (bottom view)

## 2 Evaluation board specifications

### Input and output at normal operation

- AC input voltage 90 to 265 V<sub>RMS</sub> (55 to 65 Hz)
- Output voltage 24 V
- Output current 4.2 A
- Maximum output continuous power 100 W
- PF greater than 0.9 at maximum load, 90 V AC to 265 V AC input voltage
- Total Harmonic Distortion (iTHD) less than 20 percent at maximum load, to 265 V<sub>RMS</sub> input voltage
- Start-up time to reach the secondary nominal output voltage during full-load condition at 120 and 230 V<sub>RMS</sub> input voltage less than 2 s

### Protection features

- Output Over-Voltage Protection (OVP) at V<sub>OUT</sub> less than or equal to 25 V
- Over-Current Protection (OCP) at 5.5 A
- Short-Circuit Protection (SCP)
- Brown-out protection, shut-down at 60 to 65 V<sub>RMS</sub>, start-up at 85 to 90 V<sub>RMS</sub> AC input voltages

### No-load operation

- Burst mode during no-load condition
- Maximum power loss during no-load condition is 1.6 W at 120 and 230 V<sub>RMS</sub> input voltage

### Maximum component temperature

In an ambient temperature of 30°C, the maximum allowed component temperatures are as follows:

- Resistors less than 100°C
- Ceramic capacitors, film capacitors and electrolytic capacitors less than 100°C
- Flyback transformer less than 100°C
- MOSFET transistors and diodes less than 100°C
- ICs less than 100°C

### Dimensions of evaluation board

Maximum width 6.5 inches (165.3 mm), maximum length 3.72 inches (94.5 mm)

### **WARNING!**

The board should be tested only by qualified engineers and technicians.







# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Schematics

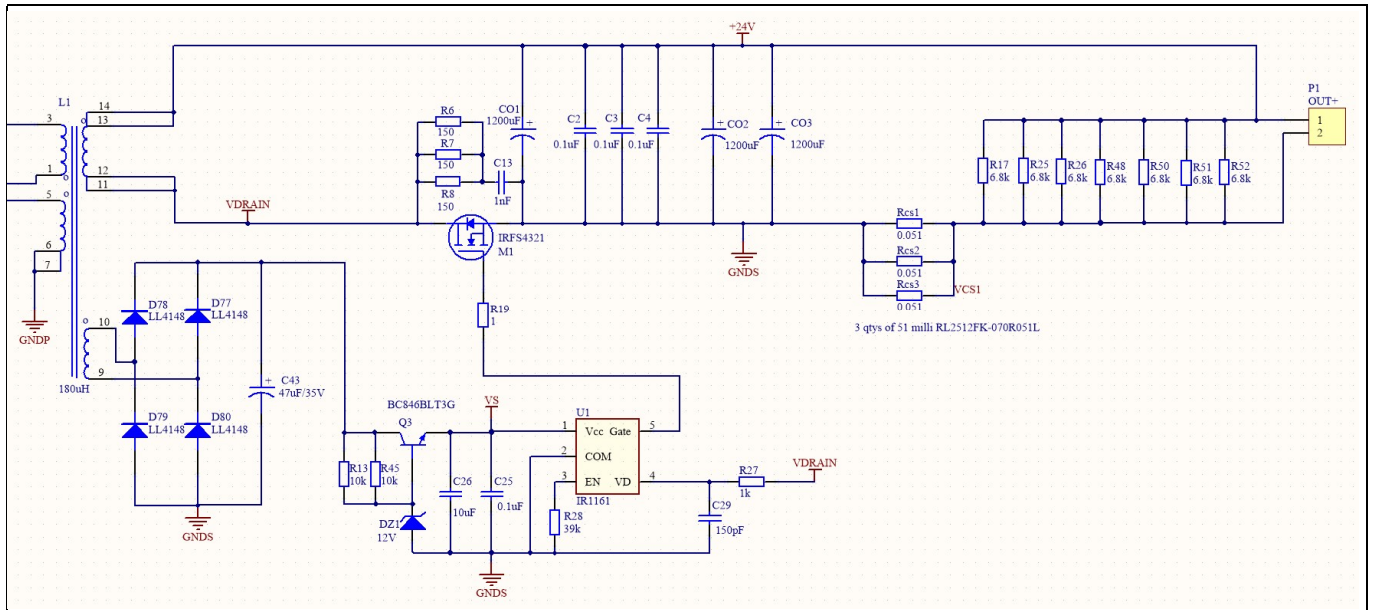

**Figure 5** Secondary side of PFC Flyback

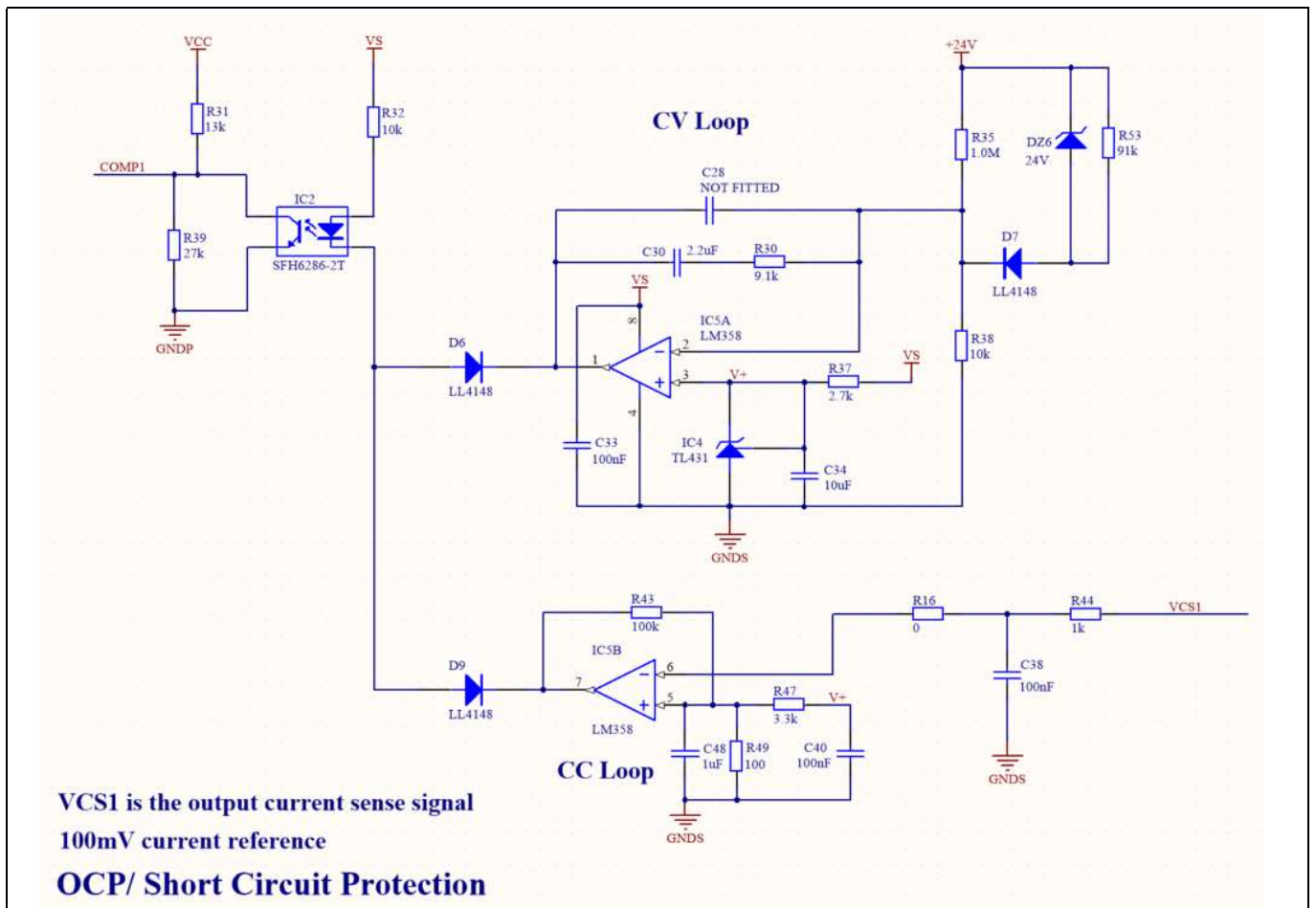

**Figure 6** Voltage feedback amplifier and over-current protection

Schematics

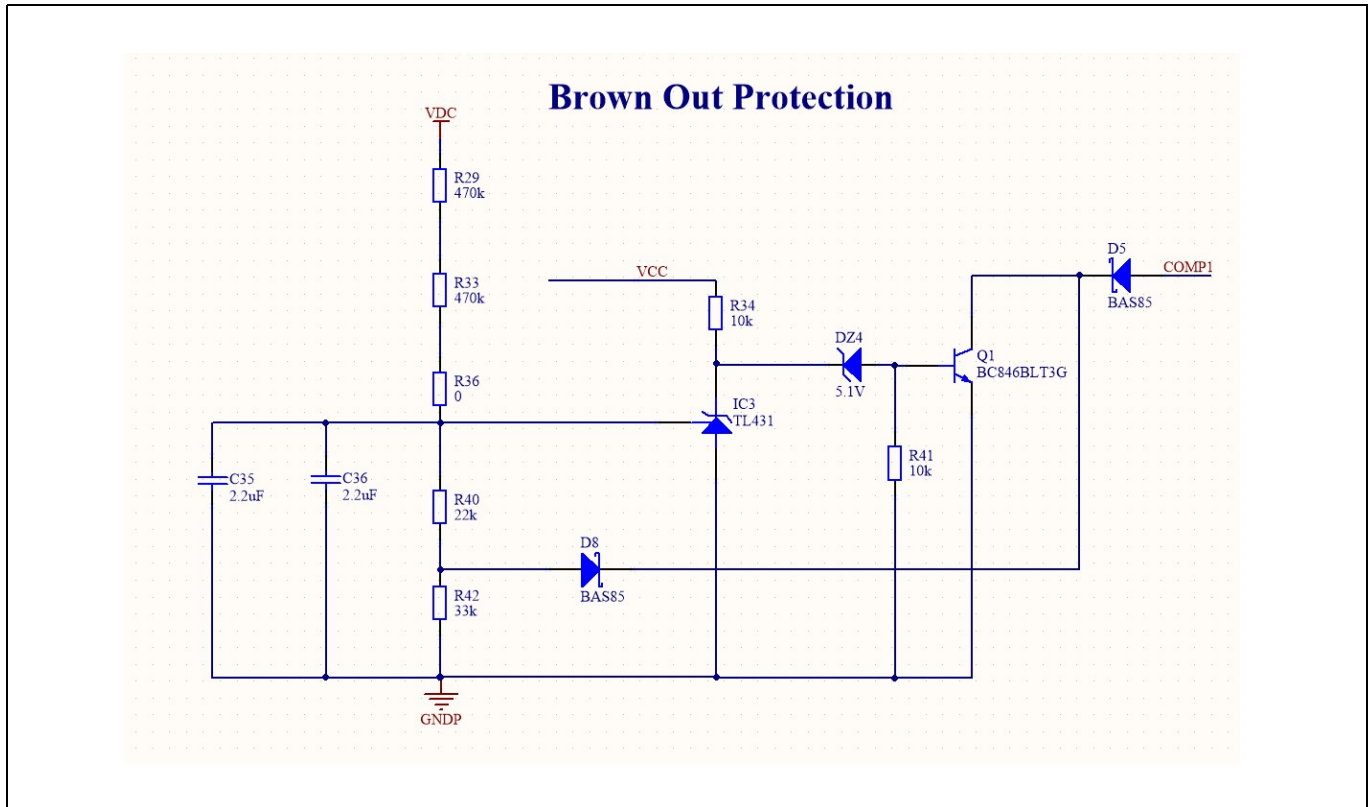


Figure 7 Brown-out protection

### 4 IRS2982S functional overview

The IRS2982S is comprised of the following functional blocks:

1. *HV start-up cell*

The IC internal functional blocks remain disabled in low-power mode until  $V_{CC}$  first rises above the  $V_{CCUV+}$  Under Voltage Lockout (UVLO) threshold, continuing to operate while  $V_{CC}$  remains above  $V_{CCUV-}$ .  $V_{CC}$  is initially supplied through the integrated HV start-up cell, which supplies a controlled current from the HV input provided a voltage greater than  $V_{HVS_{MIN}}$  is present. The current supplied is limited to  $I_{HV\_CHARGE}$ , reducing to less than  $I_{HVS\_OFF}$  when  $V_{CC}$  reaches the cut-off threshold  $V_{HVS\_OFF1}$ . The HV start-up cell switches over from start-up mode to support mode after the feedback input at FB has exceeded  $V_{REG}$  for the first time. In this mode the cut-off threshold becomes  $V_{HVS\_OFF2}$ . During steady-state operation under all line-load conditions  $V_{CC}$  is supplied through an auxiliary winding on the Flyback transformer with  $V_{CC}$  high enough so that the HV start-up cell does not supply current. If the auxiliary supply were unable to maintain  $V_{CC}$ , the HV start-up cell operating in support mode would supply current to assist.


2. *PWM controller*

The SMPS control section operates in voltage mode where the gate drive output on-time is proportional to the error amplifier output voltage appearing at the compensation output COMP. An external capacitor  $C_{COMP}$  (shown in Figure 8) connected to 0 V (ground) acts with the trans-conductance characteristic of the error amplifier to provide loop compensation and stability. Minimum on-time is reached when  $V_{COMP}$  falls to  $V_{COMPOFF}$ , below which the gate drive is disabled. Under very light-load conditions  $V_{COMP}$  transitions above and below  $V_{COMPOFF}$  to produce burst-mode operation. Off-time is determined by the demagnetization signal received at the ZX input, which is derived from the auxiliary transformer winding that supplies  $V_{CC}$  through a resistor divider. Internal logic limits the minimum off-time to  $t_{OFFMIN}$ , therefore the system transitions from CrCM to Discontinuous Conduction Mode (DCM) at light loads. If the ZX input signal fails to provide triggering the next cycle will start automatically after a restart period of  $t_{WD}$ .

3. *Protection*

The IRS2982S includes cycle-by-cycle primary OCP, which causes the gate drive to switch off if the voltage detected at the CS exceeds the threshold  $V_{CSTH}$ . This prevents the possibility of transformer saturation at low-line under heavy load, but does not protect against output over-load or short-circuit.

OVP is also provided through the ZX input, which provides a voltage proportional to the output voltage. This disables the gate-drive output and pulls the COMP voltage below the  $V_{COMPOFF}$  threshold. The error amplifier then starts to charge  $C_{COMP}$  until the gate drive starts up again at minimum on-time. Under an open-circuit output condition the OVP causes the converter to operate in burst mode, preventing the output voltage from rising too high. The IRS2982S uses an SO-8 package, as shown below:

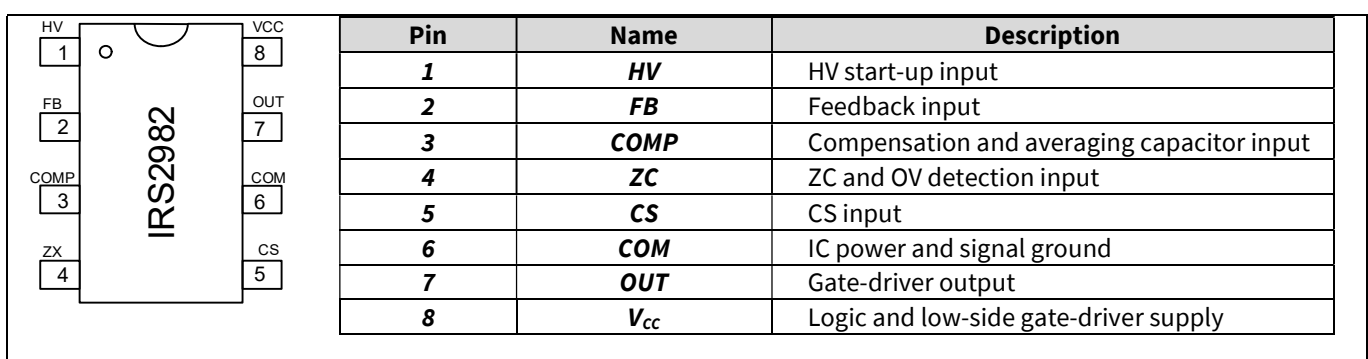

**Figure 8** IRS2982S pin assignments



### 5 Flyback converter

#### 5.1 Flyback converter types

There are several configurations of Flyback converter that may be used with the IRS2982S depending on the application. These can be classified according to isolation and regulation requirements as follows:


1. Isolated or non-isolated

2. Current or voltage regulation

In the case of voltage regulation current limiting is needed for protection against over-load or short-circuit, and in the case of current regulation OVP is necessary for an open circuit.

The IRS2982S can operate in any of the four combinations of (1) and (2). Extremely accurate current or voltage regulation is achieved in non-isolated converters since direct feedback to the FB input is possible. Isolation is however required in the majority of Flyback converters, therefore for isolated constant voltage and/or regulation as used in this design, an opto-isolator is needed. Primary side regulation from the auxiliary transformer winding as shown in the figure below is unable to produce sufficient accuracy due to the leakage inductance, which causes ringing oscillations that result in poor tracking between the rectified DC output voltage and the rectified auxiliary winding voltage. . From reference [4], it can be seen that very low leakage inductance is needed for primary side regulation to achieve reasonably accuracy and it would probably be impossible to meet isolation requirements in such a transformer design

The basic circuit below shows the main elements of the IRS2982S-based PFC Flyback converter. This single stage converter is able to provide a regulated output voltage over a wide range of line and load with sufficient accuracy for the many applications.

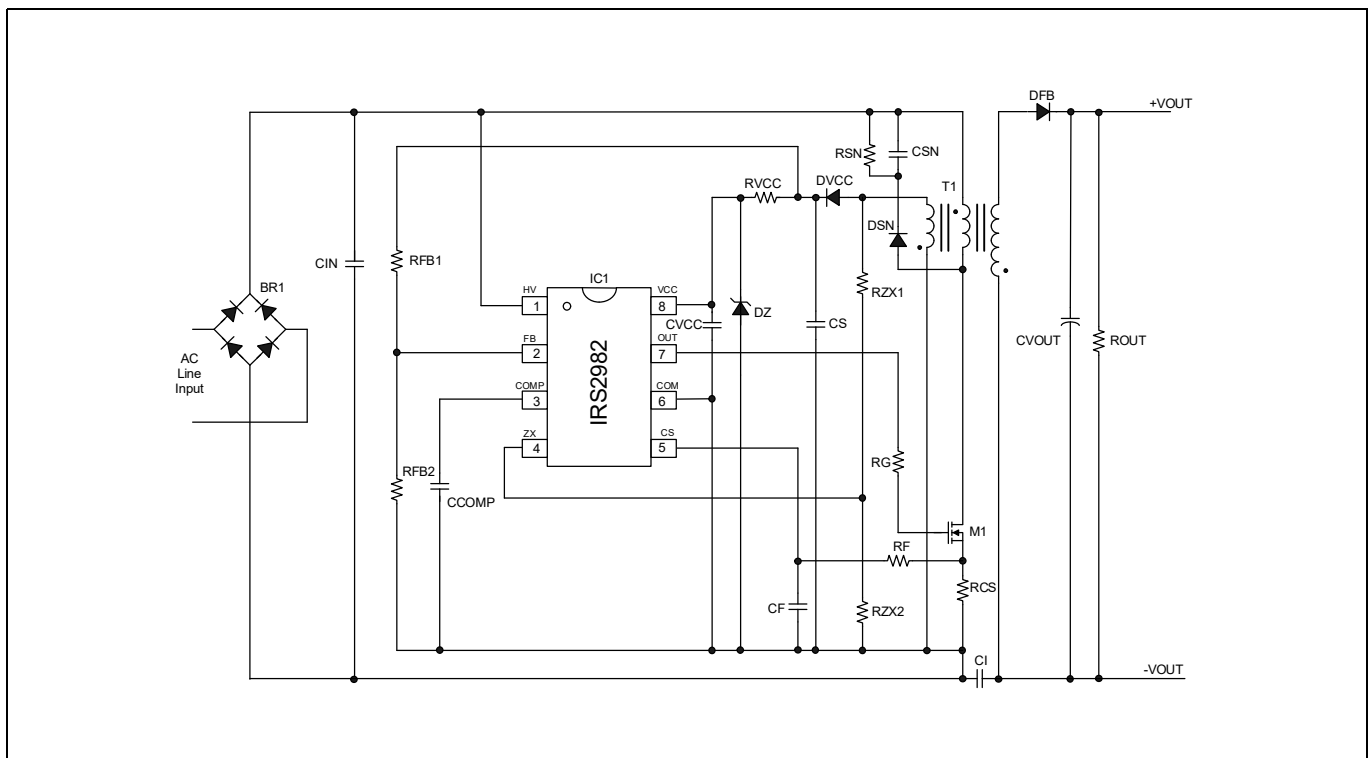

**Figure 9 Isolated voltage primary side regulated Flyback converter based on the IRS2982S**

### 6 IR1161L functional overview

The IR1161L smart secondary-side controller drives an N-channel power MOSFET used as a synchronous rectifier (SR) in isolated Flyback converters operating in DCM or quasi resonant (QR) mode, also known as CrCM, transition or Boundary Mode (BCM). A pair of IR1161L controllers and MOSFETs may be also be used as a dual SR in resonant half-bridge converters.


The IR1161L precisely controls switching on and off of the synchronous MOSFET thereby bypassing its body diode during the secondary conduction phase and emulating the rectifying action of a diode rectifier while eliminating the majority of conduction losses. The MOSFET drain to source voltage is sensed at millivolt levels to determine the polarity of the drain current switching the gate on and off in close proximity to the zero current transition. The HV input structure allows the IR1161L to withstand up to 200 V from direct connection to the drain.

Internal blanking, reverse current protection circuit and double-pulse suppression provide safe and reliable operation. The IR1161L-based smart SR offers significant efficiency improvement in DCM Flyback converters over the full load range so that replacing a Schottky diode output rectifier with the IR1161L and a correctly selected high-performance MOSFET provides significantly lower power dissipation. PCB space savings due to the IR1161L’s small SOT23-5 package are further aided by reduced MOSFET heat dissipation.

The IR1161L is able to operate from a wide  $V_{CC}$  supply voltage ranging from 4.75 to 20 V, making it possible to supply it from the output in a 5 V system and eliminating the need for an auxiliary winding. A logic-level MOSFET is required for low output voltage applications.

A built-in arming and triggering mechanism is included to allow correct switching on and off of the SR MOSFET under all system conditions, making it superior to a basic self-driven SR scheme or earlier generations of SR controller.

IR1161L is available in a 5-pin SOT-23 package. The pin-out is shown below:

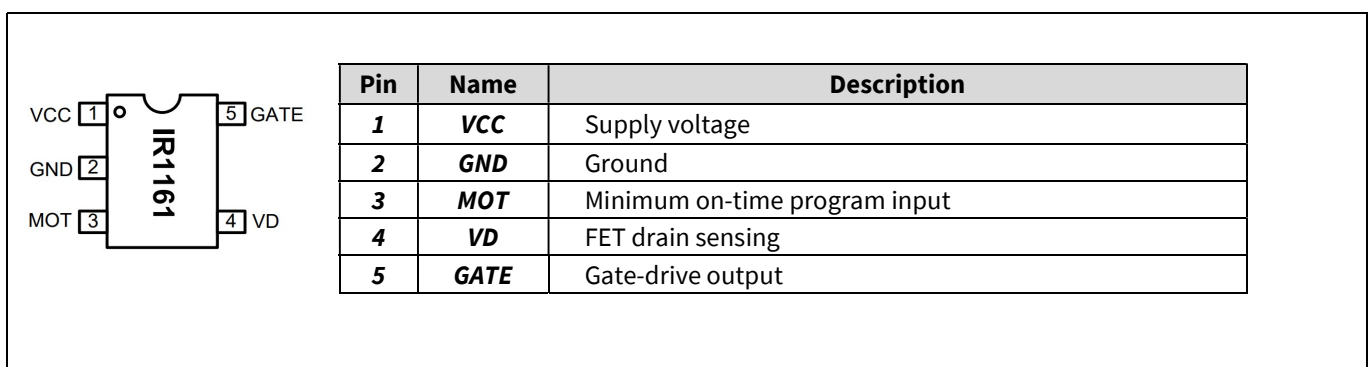


**Figure 10 IR1161L pin assignments**

Referring to the diagram below, T1 is the conduction phase of the primary switch during which energy is being stored in the Flyback transformer. The T2 phase begins when the primary switch is turned off and the energy stored in the magnetic field starts to be delivered to load through the output rectifier circuit. At this point the conduction phase of the SR MOSFET is initiated, and current starts flowing through the body diode, generating a negative  $V_{DS}$  voltage. The body diode has a much higher voltage drop than the turn-on threshold  $V_{TH1}$ , causing the IR1161L to drive the gate of the SR MOSFET on to bypass it. When the MOSFET is turned on the instantaneous sensed voltage reduces to  $I \cdot R_{DS(on)}$ . This voltage level, being much lower than the body diode

## IR1161L functional overview

forward voltage drop, is sensitive to parasitic ringing generated by the transformer leakage inductance and MOSFET output capacitance. To avoid mis-triggering and resulting premature gate turn-off, a blanking period (MOT) is used that disables  $V_{TH1}$  triggering for a minimum period of time set by an external resistor.

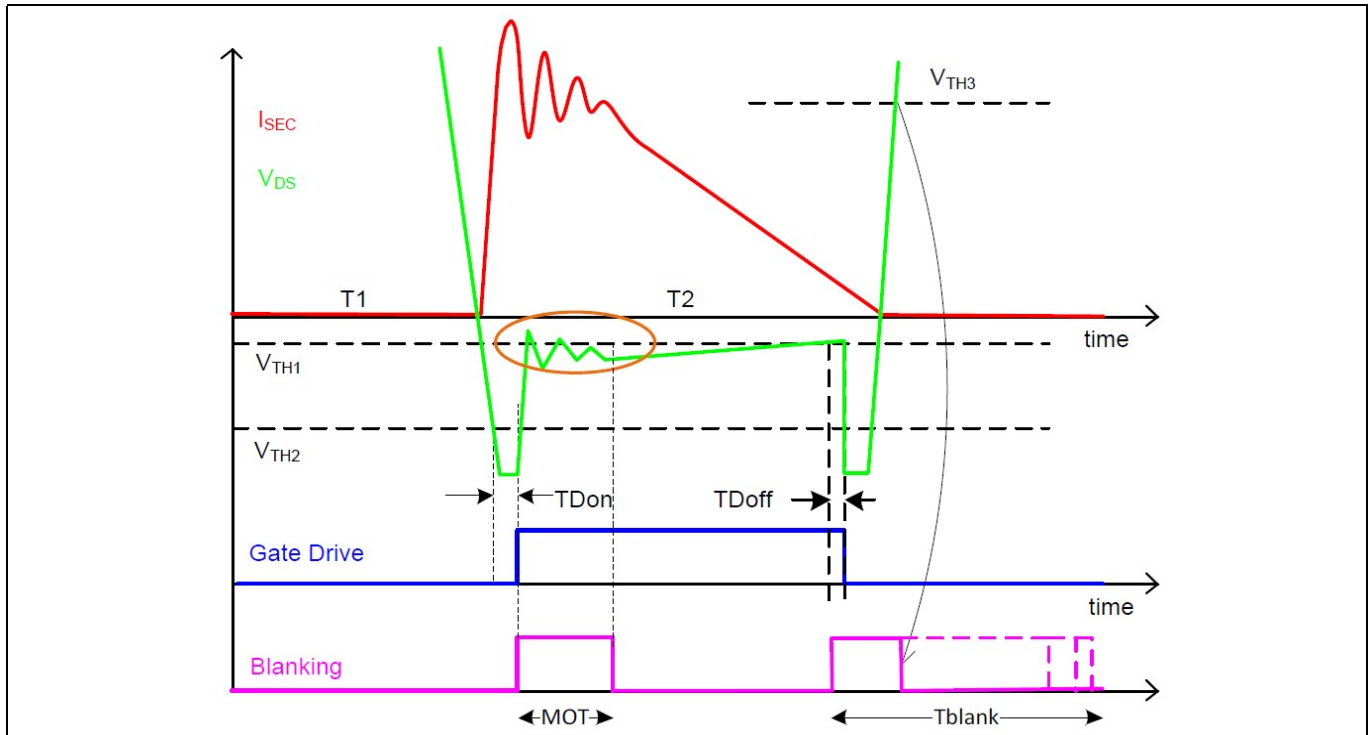

**Figure 11** Secondary SR waveforms of DCM/CrCM Flyback

At the end of each switching cycle the secondary current reduces to zero and the  $V_{DS}$  voltage crosses the turn-off threshold  $V_{TH1}$ . The IR1161L then turns the gate off and current will again start flowing through the body diode, causing the  $V_{DS}$  voltage to make a sharp negative transition. Depending on the amount of residual current,  $V_{DS}$  may once again exceed the turn-on threshold  $V_{TH2}$ . For this reason re-triggering is disabled after the gate drive has been switched off until the controller has re-armed. The re-arming sequence requires  $V_{DS}$  to cross the  $V_{TH3}$  threshold and remain above it for a period denoted as  $t_{BRST}$ . If this does not occur, the gate drive will remain low for a period of  $t_{BLANK}$ , after which time re-arming will occur automatically.

To achieve high system efficiency and low standby loss at the same time, the IR1161L incorporates a programmable minimum on-time. This feature offers flexibility in various applications at different switching frequencies. The MOT function determines the shut-down point at light load. During normal operation, the designer sets the minimum on-time to be shorter than the secondary conduction period. At progressively lighter loads, the conduction period reduces until it eventually becomes shorter than the MOT. If the IR1161L detects no voltage drop signifying no SR drain current the MOT protection function causes the gate drive to remain off for the next cycle. MOT protection operates whether or not the SR gate drive is active or whether conduction is through the body diode. In this way the IR1161L does not drive the gate at light loads and therefore consumes minimal power, improving system efficiency.

## 7 Design calculations

The principle of operation for the single-stage PFC Flyback converter is that it uses an unsmoothed DC bus voltage with only a small high-frequency capacitor to maintain a full wave-rectified voltage profile. The converter operates in CrCM under normal operating conditions with the on-time remaining effectively constant over the period of the AC-line cycle. This results in an approximately sinusoidal average input current with minimal phase shift and distortion. The output current or voltage is regulated by controlling the on-time using a FB loop that responds to line and load changes.

One of the principal advantages of operating a power supply in CrCM is that the power stage appears as a first-order system and is therefore easier to stabilize. Please see reference [5], which goes into detail about the modeling of the Flyback power stage and compensating it using type-II error amplifier compensation. The second advantage of using CrCM is that there is no reverse recovery ( $t_{rr}$ ) loss in the output diode since the primary switch is turned on when the output diode current reaches zero. This being the case, the selection of the output diode is quite straightforward, as super-fast recovery time is not required. The third advantage is that if the MOSFET is turned on in the drain voltage valley the capacitive switching loss due to  $C_{oss}$  is reduced significantly [7]. On the other hand the drawbacks of CrCM are that the operating frequency varies in relation to the input and output conditions. The frequency increases during light-load conditions, which can increase switching losses. In order to limit switching frequency the IRS2982 incorporates a minimum off-time of 3  $\mu$ s, which limits the maximum switching frequency, thereby limiting the switching losses. At full load the frequency is at minimum. During this period conduction losses dominate over switching losses. CrCM operation involves high peak and RMS currents compared to CCM operation. During low-line and full-load conditions the switching frequency can decrease enough to enter the audible range if the primary inductance value is too high.

The advantages such as ease of design, simple compensation and low switching losses increase the overall efficiency of the converter. The advantages of CrCM operation outweigh the disadvantages.

The evaluation board described here is designed to provide a constant output voltage of +24 V, as shown in Figure 3. It consists of a Flyback converter designed for PFC with low AC-line iTHD. The MOSFET used is an IPP80R360P7 800 V rated CoolMOS™ device with 360 m $\Omega$  on-resistance and 30 nC gate charge in a TO-220 package. This device is able to withstand HV ringing at switch-off with minimal added snubber components and has low conduction and switching losses as well low gate-drive current. The CoolMOS™ P7 series offers high performance though optimizing key parameters ( $C_{oss}$ ,  $E_{oss}$ ,  $Q_g$ ,  $C_{iss}$  and  $V_{GS(th)}$ , etc.), integrating a Zener diode for ESD protection and other measures. This product family fully addresses design needs, ease of use and price/performance ratio, delivering best-in-class performance. The 700 V and 800 V CoolMOS™ P7 series have been designed for Flyback converters and could also be used in PFC topologies.

A synchronous MOSFET is used on the secondary side for achieving lower loss and high efficiency compared to using a rectifying diode. The synchronous MOSFET is a IPB073N15N5. This is a 150 V D<sup>2</sup>PAK device with 7.3 m $\Omega$  on-resistance and 49 nC gate charge being driven by the IR1161L. If a diode is used on the secondary side instead of a MOSFET the losses would be quite high at full load current of 4.2A and it would be necessary to use a heatsink.

The parameters of the primary and secondary MOSFETs contribute to the overall high efficiency of the converter. The design of the transformer is critical. Reducing the core losses and the winding losses play an important role in the converter efficiency. The Flyback transformer (more accurately described as a coupled inductor) consists of four windings; the primary for energy storage during the on-time, the secondary for energy transfer to the output during the off-time and the auxiliary, which supplies  $V_{CC}$  to the IRS2982 and provides the required de-magnetization and voltage FB signals. The second auxiliary winding is on the secondary side to supply the IR1161L and also plays an important role in feedback loop, which will be described later.

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Design calculations

The IRS2982S (IC1)  $V_{CC}$  supply is derived from the transformer auxiliary winding through D4 initially charging C19 and then C23 through an NPN transistor, parallel combination of R9, R19 and a series diode D4 with DZ2 to clamp the voltage to protect IC1 from over-voltage. The FB pin of the IC is grounded since secondary-side regulation is being used to provide a stable 24 V output. The zero crossing of the transformer secondary current is detected using an auxiliary winding on the primary side. At the input AC line zero crossing the auxiliary voltage is not high enough to trigger the zero crossing (ZX) so the ZX voltage may remain below 1.54 V, which results in no gate pulses. This causes little reduction in the THD. On this demo board a Zener diode of 3.9 V is used at the ZX pin to allow continuous switching through the line zero crossing by eliminating the functionality of OVP using this ZX pin. This is not a concern on this demo board since secondary-side voltage regulation also takes care of the over-voltage. Under a no-load condition the voltage remains constant at around 24 V.

Switching-cycle peak current limiting is set by parallel shunt resistors R20 to R24, which give a combined resistance of 200 m $\Omega$ , setting the peak current to 6 A according to the threshold  $V_{CSTH}$  of 1.2 V. This limits the inrush current during start-up and also protects against damage under over-load or short-circuit conditions. At the input AC-line after the fuse an NTC thermistor of 5  $\Omega$  is also used to reduce the inrush current. The NTC resistor starts with a higher resistance when cold and reduces its resistance when the temperature of the NTC increases. The evaluation board is not designed to withstand a sustained output over-load or short-circuit.

**Table 1 PFC Flyback converter specifications**

|                             |  |
|-----------------------------|--|
| AC input voltage            | 90 to 265 $V_{RMS}$  |
| Input line frequency        | 47 to 63 Hz  |
| Nominal DC output voltage   | 24 V   |
| Maximum output power        | 100 W  |
| Power factor                | 0.99 at 120 $V_{RMS}$ /100 W<br>0.99 at 230 $V_{RMS}$ /100 W |
| Start-up time               | 1.5 s  |
| Minimum switching frequency | 60 kHz   |
| OVP                         | 24.5 V   |

The maximum peak current at low-line and full load, assuming  $D_{MAX}$  is 0.58, is calculated as:

$$L = \frac{V_{acmin}^2 \cdot \eta \cdot D_{max}^2}{2 \cdot P_{out} \cdot f_{min}} \quad [H] \quad [1]$$

$$\frac{85^2 \cdot 0.9 \cdot 0.58^2}{2 \cdot 100.8 \cdot 60000} = 180.8 \mu H$$

The peak inductor current is then calculated from:

$$I_{pk} = \frac{\sqrt{2} \cdot V_{acmin} \cdot D_{max}}{L_p \cdot f_{min}} \quad [A] \quad [2]$$



## Design calculations

$$\frac{\sqrt{2} \cdot 85 \cdot 0.58}{181 \cdot 60000} = 6.426 \text{ A}$$

The CS resistor ( $R_{CS}$ ) is then calculated:

$$R_{CS} = \frac{V_{CS(th)}}{I_{Trip}} \quad [\Omega] \quad [3]$$

$$I_{Trip} = 1.1 \cdot I_{PK} = 7.068$$

$$R_{CS} = \frac{1.26 \text{ V}}{7.068} = 0.18 \Omega$$

In this case a parallel combination with a combined resistance of  $0.2 \Omega$  has been used.

## 7.1 Voltage feedback and loop compensation

The input-to-output DC transfer characteristic for the Flyback converter is given by:

$$\frac{V_{out}}{V_{in}} = \frac{N_s}{N_p} \cdot \frac{D}{1-D} \quad [4]$$

The voltage mode Flyback converter operating in DCM or CrCM/BCM has a basic error amplifier output-to-converter output voltage small-signal transfer characteristic with a single pole formed by the output capacitor and load resistance and a zero formed by the output capacitor ESR:

$$F(s) = \frac{V_{OUT}(s)}{V_{COMP}(s)} \approx \frac{V_{OUT}}{V_{COMP}} \cdot \frac{1 + \frac{s}{\omega_{zo}}}{1 + \frac{s}{\omega_{po}}} \quad [5]$$

Where,

$$\omega_{po} = \frac{2}{R_{LOAD} \cdot C_{OUT}}, \quad R_{LOAD} = \frac{V_{OUT}}{I_{OUT}} \quad \text{and} \quad \omega_{zo} = \frac{1}{R_{ESR} \cdot C_{OUT}}$$

The ESR zero occurs at a relatively high frequency and does not come into play in PFC Flyback converters since these have a much slower loop speed than converters operating from DC, which are required to compensate rapidly for step changes in line or load.

The plant transfer function may therefore be simplified to:

$$F(s) = \frac{V_{OUT}(s)}{V_{COMP}(s)} \approx \frac{V_{OUT}}{V_{COMP}} \cdot \frac{1}{1 + \frac{s}{\omega_{po}}} = \frac{V_{OUT}}{V_{COMP}} \cdot \frac{1}{1 + \left( \frac{s R_{LOAD} \cdot C_{OUT}}{2} \right)} \quad [6]$$

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Design calculations

While the pole can be easily calculated at each specific load, the relationship between  $V_{OUT}$  and  $V_{COMP}$  is non-linear and depends on several system parameters, making it necessary to evaluate it at each operating point at which the small-signal stability analysis is to be done.

For the Flyback converter operating in DCM the plant transfer characteristic is as follows:

$$\frac{V_{OUT}(s)}{d(s)} = \frac{V_{IN(RMS)}}{\sqrt{k}} \cdot \frac{1}{1 + \left( \frac{s \cdot R_{LOAD} \cdot C_{OUT}}{2} \right)} \quad [7]$$

Where,

$$k = \frac{2 \cdot L_S}{R_{LOAD} \cdot T_S} = \frac{2 \cdot \frac{N_S}{N_P} \cdot L_P}{R_{LOAD} \cdot (T_{ON} + T_{OFF})} \quad [8]$$

Duty cycle depends on the input and output voltages and the transformer turns ratio. It varies during the line cycle, so for convenience the duty-cycle operating point is evaluated at a 45-degree phase angle where the instantaneous voltage is equal to the RMS voltage:

$$D = \frac{1}{1 + \left( \frac{V_{IN(RMS)}}{V_{OUT} + V_F} \right) \cdot \left( \frac{N_S}{N_P} \right)} \quad [9]$$


$T_{ON}$  is constant and can be evaluated according to:

$$T_{ON} = \frac{L_P \cdot P_{OUT}}{\eta \cdot V_{IN(RMS)}^2 \cdot D} = \frac{L_P \cdot V_{OUT}^2}{\eta \cdot V_{IN(RMS)}^2 \cdot R_{LOAD} \cdot D} \quad [10]$$

$T_{OFF}$  varies with the full wave-rectified bus voltage :

$$T_{OFF} = \frac{\left( \frac{N_S}{N_P} \right) \cdot V_{IN(RMS)} \cdot T_{ON}}{V_{OUT} + V_F} \quad [11]$$

From equations (4) through (10) the small-signal duty cycle to output voltage transfer function can be evaluated at the operating point. The relationship between  $V_{COMP}$  and the  $T_{ON}$  for the IRS2982 is shown below:

 

**Figure 12** On-time as a function of  $V_{COMP}$

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Design calculations

The relationship is non-linear, defined by the polynomial equation by curve fitting:

$$T_{ON} \approx 0.0178 \cdot V_{COMP}^6 - 0.3463 \cdot V_{COMP}^5 + 2.6845 \cdot V_{COMP}^4 - 10.426 \cdot V_{COMP}^3 + 21.192 \cdot V_{COMP}^2 - 20.642 \cdot V_{COMP} + 7.5426 \quad [12]$$

The derivative of this equation provides the small-signal relationship at any operating point up to an on-time of approximately 20  $\mu$ s:

$$\frac{\delta T_{ON}}{\delta V_{COMP}} \approx 0.1068 \cdot V_{COMP}^5 - 1.7315 \cdot V_{COMP}^4 + 10.738 \cdot V_{COMP}^3 - 31.278 \cdot V_{COMP}^2 + 42.384 \cdot V_{COMP} - 20.642 \quad [13]$$

Since

$$d = \frac{T_{ON}}{T_{ON} + T_{OFF}} \quad [14]$$

therefore,

$$\delta d = \frac{\delta T_{ON}}{T_{ON} + T_{OFF}} \quad [15]$$

Then

$$\frac{\delta d}{\delta V_{COMP}} \approx \frac{(0.1068 \cdot V_{COMP}^5 - 1.7315 \cdot V_{COMP}^4 + 10.738 \cdot V_{COMP}^3 - 31.278 \cdot V_{COMP}^2 + 42.384 \cdot V_{COMP} - 20.642)}{T_{ON} + T_{OFF}} \quad [16]$$

$V_{COMP}$  can be determined by extrapolating from Figure 7 according to the on-time operating point.

$$\frac{V_{OUT}(s)}{V_{COMP}(s)} = \frac{\delta d}{\delta V_{COMP}} \cdot \frac{V_{IN(RMS)}}{\sqrt{k}} \cdot \frac{1}{1 + \left(\frac{s \cdot R_{LOAD} \cdot C_{OUT}}{2}\right)} \quad [17]$$

By combining all of the above equations, the plant small-signal transfer function can be determined for a given set of conditions. From there the bode plot can be generated for the control to output power conversion stage, which is valid for the specified operating point.

The DEMO\_100W\_24VDC\_FB board includes secondary-side voltage and current feedback loops ORed together through D6 and D9 to provide a current sink for the diode of the opto-isolator IC2. During normal operation only the voltage feedback loop is in operation. The current feedback loop is included for over-load and short-circuit protection only. In both cases accurate temperature stable references are derived from IC4, being divided via R47 and R49 to provide the current feedback reference. The output current is sensed through the parallel shunt resistor combination including RCS1, RCS2 and RCS3.

Stable operation over the range of line and load depends on the correct compensation of the voltage feedback loop, which is constructed around the operational amplifier IC5A. The output voltage is scaled to the 2.5 V reference provided by IC4, through the divider network of R35 and R38. As the output voltage starts to rise above 24 V, the voltage at the divider node of R35 and R38 reaches the 2.5 V threshold and the output of IC5A (pin 1) sinks more current increasing the current through the opto diode. The opto-transistor therefore pulls down on the IRS2982 COMP input to reduce the on-time, which makes the output voltage fall.

The voltage feedback loop transfer function  $G(s)$  is composed of the error amplifier  $E(s)$  and the opto-isolator and COMP pin network  $I(s)$ :

$$G(s) = E(s) \cdot I(s) \quad [18]$$

where

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Design calculations

$$E(s) = \frac{\left(R_{30} - \frac{1}{s \cdot C_{30}}\right)}{\left(s \cdot R_{30} \cdot C_{28} + \frac{C_{28}}{C_3} + 1\right) \cdot R_{35}} \quad [19]$$

and

$$I(s) = \frac{CTR \cdot R_3}{R_{32} \cdot (1 + s \cdot C_2 \cdot R_3)} \quad [20]$$

Where CTR is the current transfer ratio of the opto-isolator.

E(s) is simplified since C28 is not fitted to the board, therefore

$$E(s) = \frac{\left(R_{30} - \frac{1}{s \cdot C_{30}}\right)}{R_3} \quad [21]$$

The combined voltage feedback loop transfer function then takes the form:


$$G(s) = \frac{V_{COMP}(s)}{V_{OUT}(s)} = -CTR \cdot \frac{R_{31}}{R_{32}} \cdot \frac{R_{30}}{R_{35}} \cdot \frac{1 + \frac{s}{\omega_{z0}}}{\left(1 + \frac{s}{\omega_{p1}}\right)} \quad [22]$$

In order for the converter to provide high power factor and low iTHD the voltage loop response must be slow enough for the on-time to remain effectively constant throughout each line frequency half-cycle. Since the AC-line frequency is 50 to 60 Hz the overall gain then needs to roll off at a lower frequency. Since the load variation is wide it is challenging to keep the crossover frequency less than 10 Hz and have a good phase margin.

The equation above shows how the DC gain can be adjusted via R30, R31, R32 and R35. However R35 is fixed as part of the divider and R32 needs to be selected to supply the opto-isolator diode with a current in the milliamp range, therefore adjustment is made with R30 and R31. It can be seen that adjusting these values also moves the pole and zero frequencies so C22 and C30 must be adjusted to position them as needed. It can be seen that C22 needs to be large enough for the pole to exist at around 10 Hz.

Based on the circuit values:  $\omega_{p1} = 77$  rads/s, 12.3 Hz and  $\omega_{z1} = 50$  rads/s, 8 Hz.

These are positioned to provide a large phase margin calculated at around 75 degrees at maximum load, which gets smaller as the load is reduced, reaching 50 degrees at 10 percent load and dropping further at lighter loads. These values are calculated using a MathCAD script that calculates and the closed loop gain and phase. This tool is sufficient to demonstrate that the gain will cross over at the desired frequency close to 10 Hz at full load, dropping to 2 Hz at 10 percent load. It can be seen that the system will remain stable over the load range although the dynamic response will be quite slow. This cannot be avoided in a single-stage PFC Flyback converter.

 

**Figure 13 System gain (left) and phase (right) response at full-load, low-line voltage**

## 7.2 Output capacitor calculation

The selection of the output capacitor is based on low-frequency 120 Hz ripple and the ESR. The output capacitor ( $C_{OUT}$ ) can be a parallel combination of four capacitors to reduce the low-frequency ripple and the ESR.

$$C_{OUT} = \frac{P_{OUT}}{2 \cdot \pi \cdot f_{IN(MIN)} \cdot \Delta_{RIPPLE} \cdot V_{OUT}^2} \quad [F] \quad [23]$$

$$= \frac{100.8}{2 \cdot \pi \cdot 50 \cdot 2 \cdot 24^2} = 279 \mu F$$

$$ESR \leq \frac{V_{RIPPLE}}{I_{SEC(PK)}}$$

$$= \frac{2V}{20A} = 100m\Omega$$

$$I_{SPK} = 2 \cdot \frac{I_{OUT}}{(1 - D_{max})} = \frac{2 \cdot 4.2}{(1 - 0.58)} = 20 A$$

$$I_{SRMS} = I_{SPK} \cdot \sqrt{\frac{1 - D_{max}}{3}} = 20 \cdot \sqrt{\frac{1 - 0.58}{3}} = 7.483 A$$

$$I_{COUT(RMS)} = \sqrt{I_{SRMS}^2 - I_{OUT}^2} = \sqrt{7.483^2 - 4.2^2} = 6.194 A$$

Three capacitors each of value 1200  $\mu F$  (part number: 860040580016) are selected. Each capacitor has 2.8 A ripple current capability at 100 kHz and an ESR equal to 28 m $\Omega$ .

## 7.3 MOT resistor calculation for IR1161L

The MOT is linear in relation to the resistor value  $R_{MOT}$ . The following formula can be used to determine the required value:

$$R_{MOT} = 5.10^{10} \cdot t_{MOT} \quad [24]$$

The value of  $R_{MOT}$  should not be lower than the minimum recommended on the datasheet. On this board a standard value of 39 k $\Omega$  is used at the MOT pin of the IC. This value gives a minimum on-time of 780 ns.



## 8 Protection features

### 8.1 Brown-out protection

The following circuit has been used to implement the brown-out protection of the PFC Flyback converter. The converter stops switching once the input AC voltage falls below 60 to 65  $V_{RMS}$  and turns back on when the input AC voltage rises above 85 to 90  $V_{RMS}$ . When the input to IC3 divided from the rectified input voltage  $V_{DC}$  through the network consisting of R29, R33, R36, R40 and R42 rises above the 2.5 V threshold, the cathode of DZ4 is pulled down to 2.5 V. This causes Q1 to switch off, allowing COMP1 to start and the converter to start up. In this state D8 is blocking and R42 forms part of the divider network. If the AC input voltage falls below 60 to 65  $V_{RMS}$  the input to IC3 falls below 2.5 V and the cathode voltage rises until DZ4 conducts and Q1 is turned on. At this point D8 conducts, pulling down on the node of R40 and R42 thereby adjusting the divider ratio to provide hysteresis requiring a higher AC input and VDC voltage to 2.5 V at the IC3 input required to pull down the cathode and turn off Q1 again.

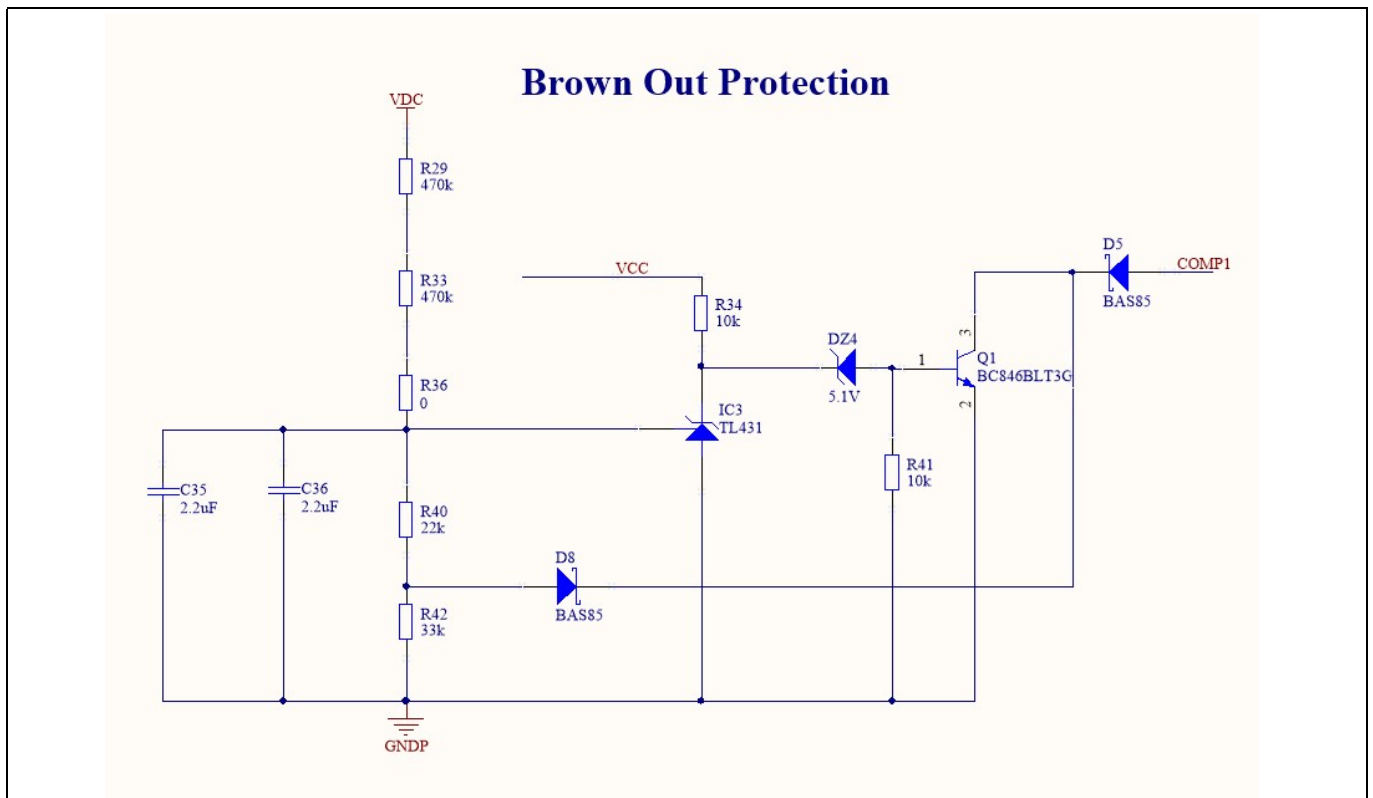


Figure 14 Brown-out protection circuit

Protection features

### 8.2 Overload and short-circuit protection

The over-current protection feature is very important in the flyback converter to prevent high currents occurring under a fault condition, which could result in failure of either the primary or secondary MOSFETs (M2 and M1). The primary cycle by cycle current limit provides some protection to M2 by terminating the gate drive if an excessive current is detected, however this alone is not sufficient to limit the output current and protect the power supply in the event of an overload or short-circuit.

To accomplish this an output current sensing network consisting of parallel resistors; Rcs1, Rcs2 and Rcs3 has been included. The voltage drop proportional to the output current is compared with a reference determined by the resistor divider R47 and R49 connected to the 2.5 V reference of IC4. IC5B is configured as a comparator with hysteresis determined by R43. If the sensed output current exceeds the reference the output transitions from high to low causing conduction through D9 to energize the feedback opto-isolator IC2. This causes the COMP voltage at IC1 to be pulled down rapidly as C22 is discharged, which turns off the gate drive to M2.

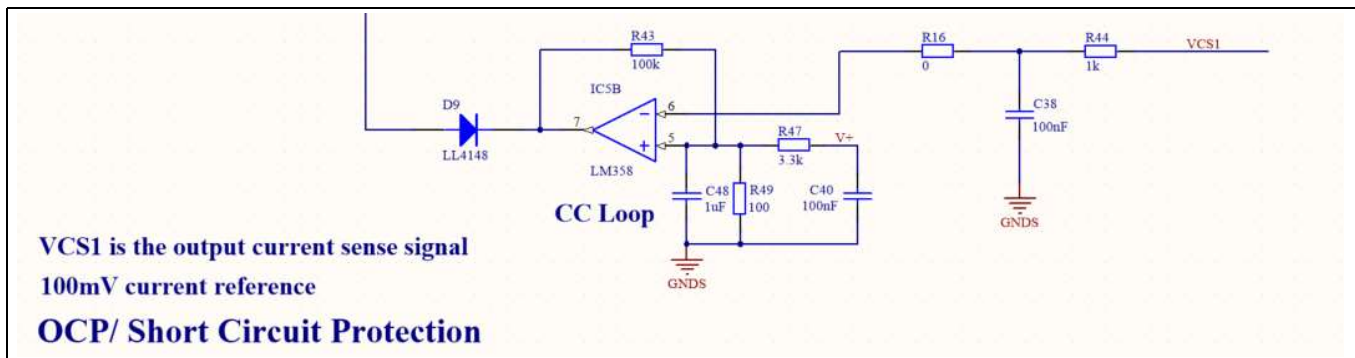


Figure 15 Overload and short-circuit protection circuit

Since the output current has now dropped to zero, the output of IC5B then transitions high shutting off the current through D9 and de-energizing IC2 allowing the system to re-start as C22 charges through R31. If the fault condition at the output remains then as the output current rises above the threshold the same shut down function will occur. This hiccup mode operation will continue indefinitely until the fault condition is removed allowing the power supply to automatically re-start.

## 9 Bill of Materials (BOM)

| Designator                        | Manufacturer                         | Part Number          | Quantity | Value/Rating                    |
|-----------------------------------|--------------------------------------|----------------------|----------|---------------------------------|
| BR1                               | Vishay Semiconductor Diodes Division | GBU4J-E3/51          | 1        | 600 V/4 A/4-SIP/GBU             |
| C2, C3, C4, C25                   | Samsung Electro-Mechanics            | CL10B104KB8NNNL      | 4        | 0.1 $\mu$ F/50 V/X7R/0603       |
| C8, C39                           | Kemet                                | C1210C104KBAC7800    | 2        | 0.1 $\mu$ F/630 V/X7R/1210      |
| C9, C10                           | Würth Electronics Inc.               | 890334023028         | 2        | 0.22 $\mu$ F/310 VAC/Radial/10% |
| C11                               | EPCOS (TDK)                          | B32621A6222K189      | 1        | 2.2 nF/630 V                    |
| C12                               | Kemet                                | C330C222GDG5TA       | 1        | 2.2 nF/1 kV/NP0/Radial          |
| C13                               | Yageo                                | CC1206KRX7RABB102    | 1        | 1 nF/200 V/X7R/1206             |
| C14, C15, C27                     | Panasonic Electronic Components      | ECQ-U3A104MG         | 3        | 0.1 $\mu$ F/300 VAC/20%/Radial  |
| C16, C17, C20, C32, C44, C45, C47 | Vishay, Vishay BC Components         | VY1102M29Y5VQ6TV0    | 7        | 1 nF/500 VAC/Y5V Radial         |
| C18                               | Würth Electronics Inc.               | 885012208058         | 1        | 0.1 $\mu$ F/25 V/X7R/1206       |
| C19                               | Rubycon                              | 50YXG220MEFC10X16    | 1        | 220 $\mu$ F/50 V/20%/Radial     |
| C21                               | TDK Corporation                      | CGA3E2NP01H220J080AA | 1        | 22 pF/50 V/NP0/0603             |
| C22                               | Kemet                                | C1206C105J3RACTU     | 1        | 1 $\mu$ F/25 V/X7R/1206         |
| C23                               | Würth Electronics Inc.               | 860160474016         | 1        | 180 $\mu$ F/25 V/20%            |
| C24                               | Würth Electronics Inc.               | 885012007040         | 1        | 1 nF/25 V/COG/NP0/0805          |
| C26                               | Samsung Electro-Mechanics            | CL31B106KAHNNNE      | 1        | 10 $\mu$ F/25 V/X7R/1206        |
| C28                               |                                      |                      | 1        |                                 |
| C29                               | Yageo                                | CC0603JRNPOYBN151    | 1        | 150 pF/250 V/NP0/0603           |
| C30, C35, C36                     | Yageo                                | CC1206JKX7R8BB225    | 3        | 2.2 $\mu$ F/25 V/X7R/1206       |
| C33, C38, C40                     | AVX                                  | 08053C104JAT2A       | 3        | 0.1 $\mu$ F/25V/0805/5%         |
| C34                               | Kemet                                | C0805C106K8PACTU     | 1        | 10 $\mu$ F/10V/X5R/0805         |
| C48                               | AVX Corporation                      | 08053C105JAT2A       | 1        | 1 $\mu$ F/25 V/X7R/0805         |
| C41, Cx                           | Würth Electronics Inc.               | 890334024005         | 2        | 0.47 $\mu$ F/310 VAC/10%/Radial |
| C42                               | Kemet                                | C0805C471JDRACTU     | 1        | 470 pF/1 kV/ X7R/0805           |
| C43                               | Würth Electronics Inc.               | 860040572002         | 1        | 47 $\mu$ F/35 V/20%             |

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Bill of Materials (BOM)

|  |                                    |                  |    |                                   |
|--|------------------------------------|------------------|----|-----------------------------------|
| CO1, CO2, CO3                              | Wurth Electronics Inc.             | 860040580016     | 3  | 1200 $\mu$ F/35 V                 |
| COMP1, ZX1                                 | Keystone                           | 5004             | 2  | 0.04" dia yellow                  |
| D1   | Diodes Inc                         | RS3K-13-F        | 1  | 800 V/3 A/SMC                     |
| D2, D3, D4, D6, D7, D9, D77, D78, D79, D80 | ON Semiconductor                   | FDLL4148         | 10 | 100 V/0.2 A/MINIMELF              |
| D5, D8                                     | Vishay                             | BAS85-GS08       | 2  | Schottky/30 V/200 mA/SOD80        |
| DZ1  | Nexperia USA Inc.                  | BZV55-C12,115    | 1  | Zener/12 V/500 mW/SOD80C          |
| DZ2  | Nexperia USA Inc.                  | BZV55-C16,115    | 1  | Zener/16V/500mW/SOD80C            |
| DZ3  | Nexperia USA Inc.                  | BZV55-C3V9,115   | 1  | Zener/3.9 V/500 mW/SOD80C         |
| DZ4  | Nexperia USA Inc.                  | BZV55-C5V1,115   | 1  | Zener/5.1 V/500 mW/SOD80C         |
| DZ5  | Micro Commercial Co                | P6KE250A-TP      | 1  | TVS DIODE/214 V/344 V/DO15        |
|  |                                    |                  |    |                                   |
| DZ6  | Nexperia USA Inc.                  | BZV55-C24,115    | 1  | Zener/24V/500mW/SOD80C            |
| IC1  | Infineon                           | IRS2982S         | 1  | SMPS Controller                   |
| IC2  | Vishay Semiconductor Opto Division | SFH6286-2T       | 1  | Opto-isolaror/5.3 kV/TRANS/4-SMD  |
| IC3, IC4                                   | Diodes Inc                         | ZTL431AFTA       | 2  | Voltage Reference/SOT23-3         |
| IC5  | Diodes Inc                         | LM358S-13        | 1  | Operational amplifier/dual        |
| L1   | Wurth Electronik                   | 750317969        | 1  | Flyback                           |
| L2, L4, L5, L7                             | Bourns                             | 2124-V-RC        | 4  | 1 mH/1.3 A                        |
| L3, L6                                     | TDK                                | B82733F2122B1    | 2  | CM choke 39 mH/1.2 A              |
| M1   | Infineon                           | IRFS4321         | 1  | 150 V/60 A/15 m $\Omega$ /D2PAK   |
| M2   | Infineon                           | IPA80R280P7      | 1  | 800 V/17 A/280 m $\Omega$ /TO-220 |
| P1   | Phoenix Contact                    | 1985195          | 1  | 2 Position/3.5mm/Green            |
| P2   | Phoenix Contact                    | 1985205          | 1  | 3 Position/3.5mm/Green            |
| Q1, Q2, Q3                                 | ON Semiconductor                   | BC846BLT3G       | 3  | NPN/65V/0.1A/SOT-23               |
| R1   | Yageo                              | CFR-50JB-52-10K  | 1  | 10 k/0.5 W/5%                     |
| R2, R3                                     | Stackpole Electronics Inc.         | RSF2JT10R0       | 2  | 10/2 W/5%/Axial                   |
| R4, R5, R12                                | Yageo                              | FMP200FRF52-130K | 3  | 130 k/2 W/1%/Axial                |
| R6, R7, R8                                 | Stackpole Electronics Inc.         | CR1206-JW-151ELF | 3  | 150/0.25 W/1206/5%                |
| R9, R11                                    | Yageo                              | RC1206FR-076K2L  | 2  | 6.2 k/0/25 W/1206/1%              |
| R10  | Yageo                              | RC1206FR-0714KL  | 1  | 14 k/0.25 W/1206/1%               |
| R13, R45                                   | Panasonic Electronic Components    | ERJ-8ENF1002V    | 2  | 10 k/0.25 W/1206/1%               |

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L




## Bill of Materials (BOM)

|                                   |                                 |                   |   |                                   |
|-----------------------------------|---------------------------------|-------------------|---|-----------------------------------|
| R14                               | TDK                             | B57153S479M54     | 1 | ICL/4.7 $\Omega$ /3 A/20%/8.5 mm  |
| R15, R19                          | Vishay Dale                     | CRCW12061R00FKEA  | 2 | 1/0.25 W/1206/1%                  |
| R16                               | Stackpole Electronics           | RMCF0805ZTOR00    | 1 | 0/0.125 W/0805                    |
| R17, R25, R26, R48, R50, R51, R52 | Panasonic Electronic Components | ERJ-8GEYJ682V     | 7 | 6.8 k/0.25 W/1206/5%              |
| R18                               | Yageo                           | RC0805FR-07470RL  | 1 | 470/0.125 W/0805/1%               |
| R20, R21, R22, R23, R24, R46      | Vishay Dale                     | CRCW12061R00FKEA  | 6 | 1/0.25 W/1206/1%                  |
| R27, R44                          | TE Connectivity Passive Product | CRG1206F1K0       | 2 | 1 k/0.25 W/1206/1%                |
| R28                               | Stackpole Electronics Inc.      | RMCF0805FT39K0    | 1 | 39 k/0.125 W/0805/1%              |
| R29, R33                          | Yageo                           | RC1206FR-07470KL  | 2 | 470 k/0.25 W/1206/1%              |
| R30                               | Yageo                           | RC0805FR-079K1L   | 1 | 9.1 k/0.125 W/0805/1%             |
| R31                               | Yageo                           | RC1206FR-0713KL   | 1 | 13 k/0.25 W/1206/1%               |
| R34, R41                          | Yageo                           | RC0805FR-0710KL   | 2 | 10 k/0.125 W/0805/1%              |
| R35                               | Stackpole Electronics Inc.      | RMCF1206FT1M00    | 1 | 1 M/0.25 W/1206/1%                |
| R36                               | Stackpole Electronics Inc.      | RMCF1206ZTOR00    | 1 | 0/0.25 W/1206                     |
| R37                               | Stackpole Electronics Inc.      | RMCF0805FT2K70    | 1 | 2.7 k/0.125 W/0805/1%             |
| R47                               | Stackpole Electronics Inc.      | RMCF0805FT3K30    | 1 | 3.3 k/0.125 W/0805/1%             |
| R32, R38                          | Vishay Dale                     | CRCW120610K0FKEAC | 2 | 10 k/0.25 W/1206/1%               |
| R39                               | Yageo                           | RC1206FR-0727KL   | 1 | 27 k/0.25 W/1206/1%               |
| R40                               | Yageo                           | RC0805FR-0722KL   | 1 | 22 k/0.125 W/0805/1%              |
| R42                               | Yageo                           | RC0805FR-0733KL   | 1 | 33 k/0.125 W/0805/1%              |
| R43                               | TE Connectivity Passive Product | CRG0805F100K      | 1 | 100 k/0.125 W/0805/1%             |
| R49                               | Yageo                           | RC0805FR-07100RL  | 1 | 100/0.125 W/0805/1%               |
| R53                               | Stackpole Electronics Inc.      | RMCF1206FT91K0    | 1 | 91 k/0.25 W/1206/1%               |
| Rcs1, Rcs2, Rcs3                  | Yageo                           | RL2512FK-070R051L | 3 | 51 m $\Omega$ /2512/1 W/1%        |
| U1                                | Infineon                        | IR1161L           | 1 | Synchronous Rectifier IC /SOT23-5 |
| VCC1                              | Keystone                        | 5000              | 1 | 0.04" dia red                     |
| VR1                               | EPCOS (TDK)                     | B72214S321K101    | 1 | Varistor/510 V/4.5 kA/DISC/14 mm  |





### 10.1 PCB layout guidelines for system optimization

 

**Figure 18 Complete board layout**

The primary HF current loop on the left side of the board originates from HF capacitor C8 connecting to the Flyback inductor (L1). The other side of the Flyback inductor winding is connected to the drain of the MOSFET (M2) and the CS resistor R20. The other end of the CS resistor is connected to the return of the C8 capacitor. To minimize EMI and also the loop inductance, this HF loop is kept as small as possible.

The secondary-side HF current loop originates from C2, M1 and L1. Therefore, in order to keep the layout as tight as possible, these HF AC loop components are placed close to each other, minimizing the loop area, and this translates to lower EMI. In order to keep the loops as small as possible, it is preferable to use ceramic capacitors C2, C3 and C4 to close the AC loops and keep the return paths small. Aside from EMI considerations it is also extremely important to design the PCB so that IRS2982 and IR1161L ICs are able to operate correctly without suffering from potential interference caused by noise or incorrect grounding. Decoupling capacitors C18 and C25 are located right next to IC1 and U1 with direct connections to the  $V_{CC}$  and COM/0 V pins.

As in all switching power supplies, the signal and power grounds must be kept separate and join together only at the star points or single-point connections, which are at the negative side of the HF capacitor C8 for the primary side and C2 for the secondary side.



# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Flyback transformer specifications

### 11 Flyback transformer specifications

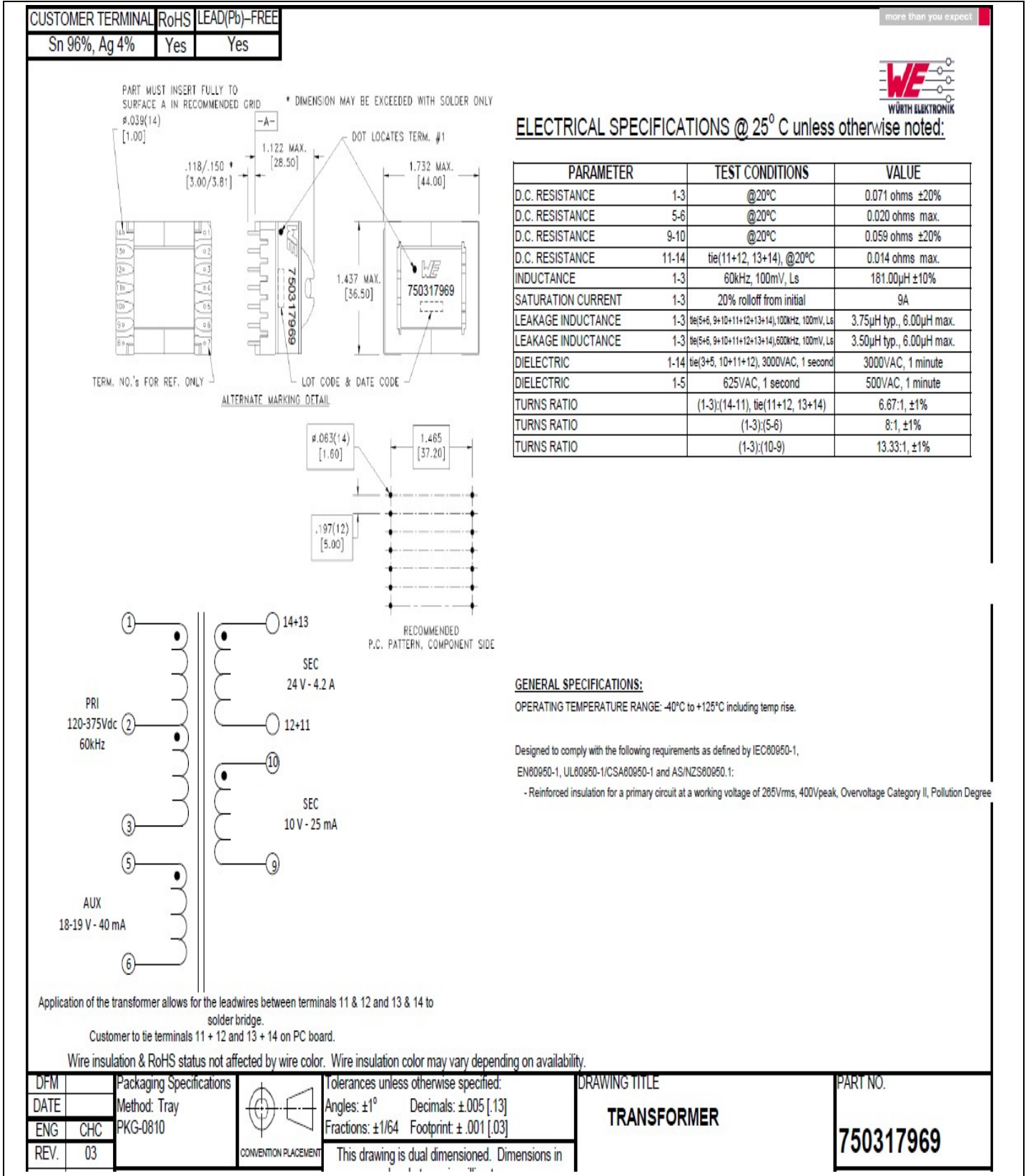


Figure 19 Flyback transformer

Test results

## 12 Test results

### 12.1 Operation under different line and load conditions

**Table 2** Input 120 V AC<sub>(RMS)</sub>

| <b>P<sub>IN</sub></b><br><b>(W)</b> | <b>V<sub>OUT</sub></b><br><b>(V)</b> | <b>I<sub>OUT</sub></b><br><b>(A)</b> | <b>P<sub>OUT</sub></b><br><b>(W)</b> | <b>PF</b> | <b>iTHD</b><br><b>(%)</b> | <b>Efficiency</b><br><b>(%)</b> |
|-------------------------------------|--------------------------------------|--------------------------------------|--------------------------------------|-----------|---------------------------|---------------------------------|
| 1.64                                | 23.95                                | 0                                    | 0.00                                 | 0.25      | ---                       | 0.00%                           |
| 9.45                                | 23.94                                | 0.244                                | 5.84                                 | 0.753     | 23.0%                     | 61.81%                          |
| 15.81                               | 23.93                                | 0.492                                | 11.77                                | 0.876     | 18.9%                     | 74.47%                          |
| 22.92                               | 23.73                                | 0.743                                | 17.63                                | 0.916     | 17.3%                     | 76.93%                          |
| 29.21                               | 23.75                                | 0.991                                | 23.54                                | 0.946     | 16.7%                     | 80.58%                          |
| 35.55                               | 23.82                                | 1.24                                 | 29.54                                | 0.965     | 11.7%                     | 83.09%                          |
| 41.9                                | 23.89                                | 1.48                                 | 35.36                                | 0.973     | 9.1%                      | 84.38%                          |
| 48.39                               | 23.93                                | 1.74                                 | 41.64                                | 0.978     | 9.4%                      | 86.05%                          |
| 55                                  | 23.92                                | 1.987                                | 47.53                                | 0.98      | 8.8%                      | 86.42%                          |
| 61.71                               | 23.91                                | 2.237                                | 53.49                                | 0.985     | 8.1%                      | 86.67%                          |
| 68.41                               | 23.9                                 | 2.485                                | 59.39                                | 0.987     | 7.7%                      | 86.82%                          |
| 75.22                               | 23.88                                | 2.735                                | 65.31                                | 0.989     | 7.3%                      | 86.83%                          |
| 82.09                               | 23.87                                | 2.984                                | 71.23                                | 0.99      | 7.1%                      | 86.77%                          |
| 89.06                               | 23.855                               | 3.235                                | 77.17                                | 0.99      | 7.0%                      | 86.65%                          |
| 95.98                               | 23.84                                | 3.482                                | 83.01                                | 0.99      | 6.9%                      | 86.49%                          |
| 102.98                              | 23.82                                | 3.731                                | 88.87                                | 0.99      | 6.8%                      | 86.30%                          |
| 110.1                               | 23.79                                | 3.982                                | 94.73                                | 0.99      | 6.6%                      | 86.04%                          |
| 117.18                              | 23.78                                | 4.23                                 | 98.47                                | 0.99      | 6.5%                      | 85.84%                          |

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Test results

**Table 3** Input 230 V AC<sub>(RMS)</sub>

| <b>P<sub>IN</sub></b><br><b>(W)</b> | <b>V<sub>OUT</sub></b><br><b>(V)</b> | <b>I<sub>OUT</sub></b><br><b>(A)</b> | <b>P<sub>OUT</sub></b><br><b>(W)</b> | <b>PF</b> | <b>iTHD</b><br><b>(%)</b> | <b>Efficiency</b><br><b>(%)</b> |
|-------------------------------------|--------------------------------------|--------------------------------------|--------------------------------------|-----------|---------------------------|---------------------------------|
| 1.8                                 | 23.9                                 | 0                                    | 0.00                                 | 0.08      | ---                       | 0.00%                           |
| 9.77                                | 23.85                                | 0.244                                | 5.82                                 | 0.35      | ---                       | 59.56%                          |
| 16.96                               | 23.85                                | 0.492                                | 11.73                                | 0.53      | 22.4%                     | 69.19%                          |
| 23.6                                | 23.67                                | 0.742                                | 17.56                                | 0.65      | 19.0%                     | 74.42%                          |
| 30.17                               | 23.63                                | 0.99                                 | 22.80                                | 0.73      | 19.0%                     | 77.54%                          |
| 36.31                               | 23.57                                | 1.241                                | 28.63                                | 0.78      | 17.4%                     | 80.56%                          |
| 42.7                                | 23.42                                | 1.489                                | 34.87                                | 0.83      | 15.4%                     | 81.67%                          |
| 49.23                               | 23.63                                | 1.739                                | 41.09                                | 0.87      | 14.0%                     | 83.47%                          |
| 55.6                                | 23.73                                | 1.988                                | 47.18                                | 0.89      | 13.3%                     | 84.85%                          |
| 62.12                               | 23.76                                | 2.237                                | 53.15                                | 0.91      | 13.0%                     | 85.56%                          |
| 68.45                               | 23.75                                | 2.485                                | 59.02                                | 0.92      | 13.2%                     | 86.22%                          |
| 74.89                               | 23.75                                | 2.735                                | 64.96                                | 0.93      | 13.0%                     | 86.74%                          |
| 81.32                               | 23.75                                | 2.984                                | 70.87                                | 0.94      | 12.7%                     | 87.15%                          |
| 87.83                               | 23.73                                | 3.234                                | 76.74                                | 0.94      | 13.1%                     | 87.38%                          |
| 94.28                               | 23.73                                | 3.482                                | 82.63                                | 0.95      | 13.4%                     | 87.64%                          |
| 100.77                              | 23.72                                | 3.731                                | 88.50                                | 0.952     | 13.7%                     | 87.82%                          |
| 107.39                              | 23.71                                | 3.981                                | 94.39                                | 0.96      | 14.0%                     | 87.89%                          |
| 114                                 | 23.71                                | 4.229                                | 100.27                               | 0.96      | 14.0%                     | 87.96%                          |

Test results

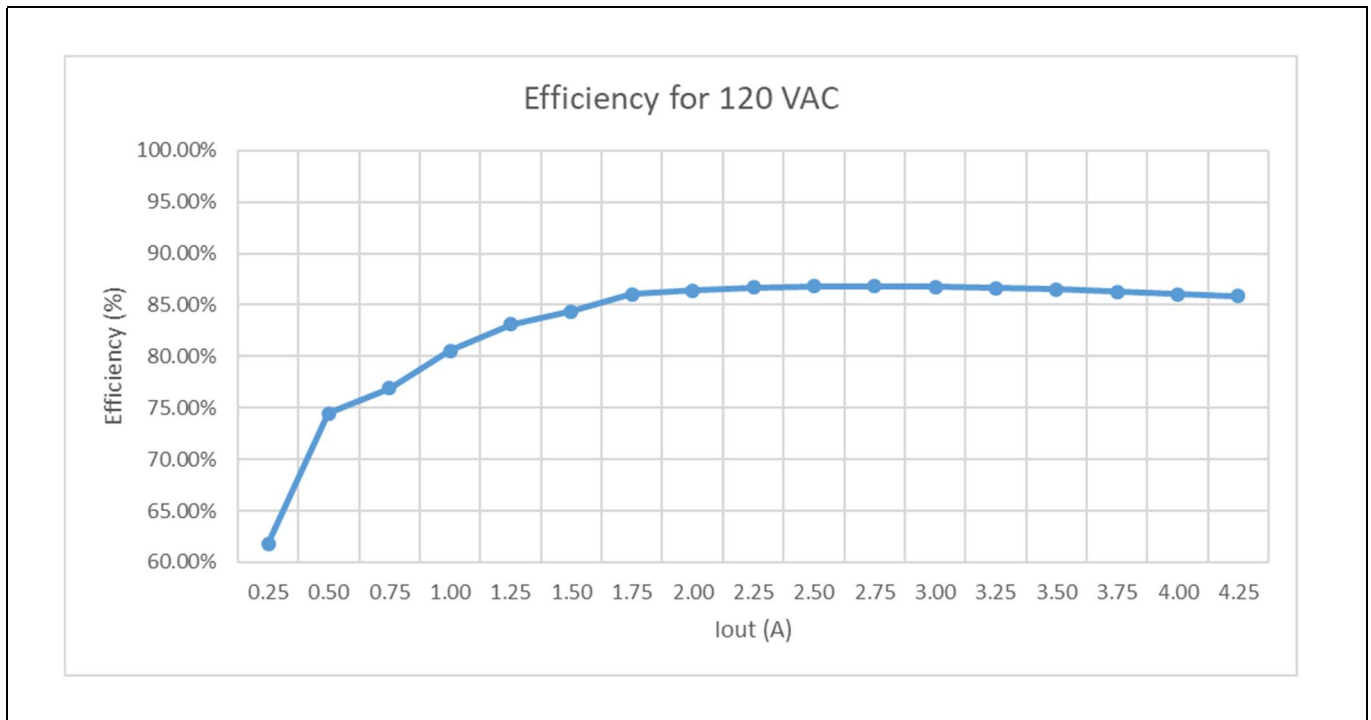


Figure 20 Efficiency at 120 V AC<sub>RMS</sub> input

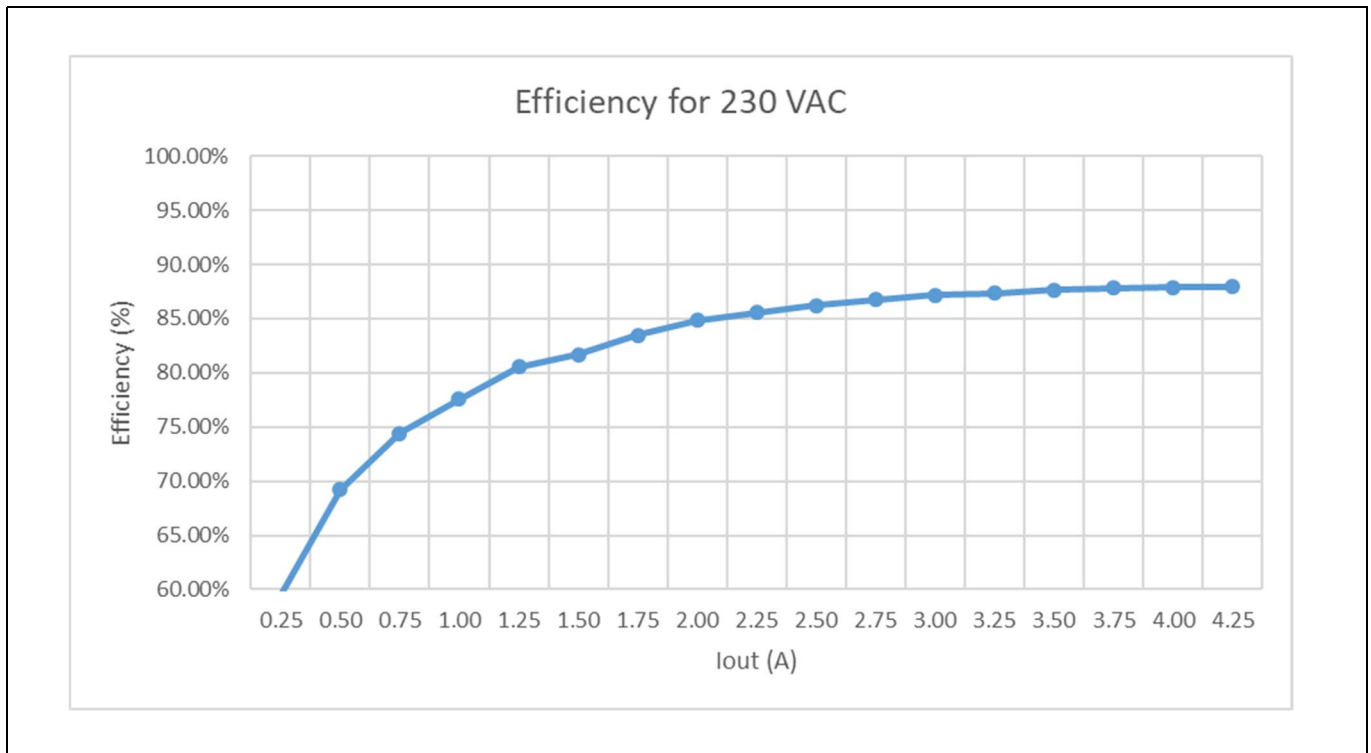


Figure 21 Efficiency at 230 V AC<sub>RMS</sub> input

Test results

 


Figure 22 Load regulation at 120 V AC<sub>RMS</sub> input

 


Figure 23 Load regulation at 230 V AC<sub>RMS</sub> input



Test results

12.2 Power factor and input current harmonics (iTHD)

 


Figure 24 Power factor and iTHD at 120 VAC<sub>RMS</sub> input

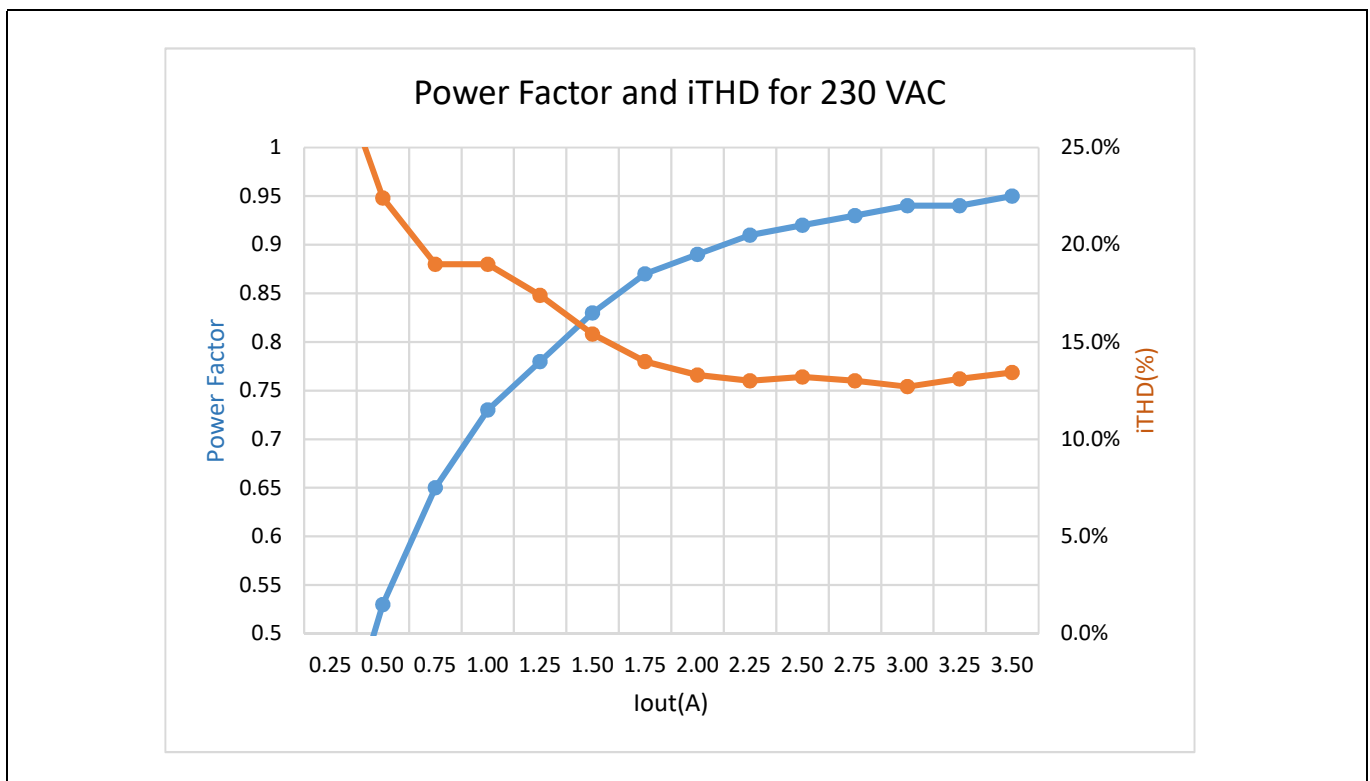


Figure 25 Power factor and iTHD at 230 VAC<sub>RMS</sub> input

## Test results

An international standard, the IEC 1000-3-2 (EN 61000-3-2), defines the rules for the current distortion affecting mains-powered devices. This standard does not discuss the power factor directly but fixes current harmonic limits [4].

**Table 4** EN 61000-3-2 class D limits for system power greater than 75 W

| Requirements | Harmonics limits class D according to EN 61000-3-2 for system power greater than 75 W and less than 600 W |                                   |
|--------------|---|-----------------------------------|
|              | Harmonics order n   | $\text{mA}_{\text{RMS}}/\text{W}$ |
|              | 3   | 3.4                               |
|              | 5   | 1.9                               |
|              | 7   | 1.0                               |
|              | 9   | 0.5                               |
|              | 11  | 0.35                              |
|              | 13  | 0.296                             |
|              | 15 less than or equal to n less than or equal to 39   | $3.85/n$                          |

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Test results

 


Figure 26 Power analyzer read-out at 120 V AC<sub>RMS</sub> input with 4.2 A load

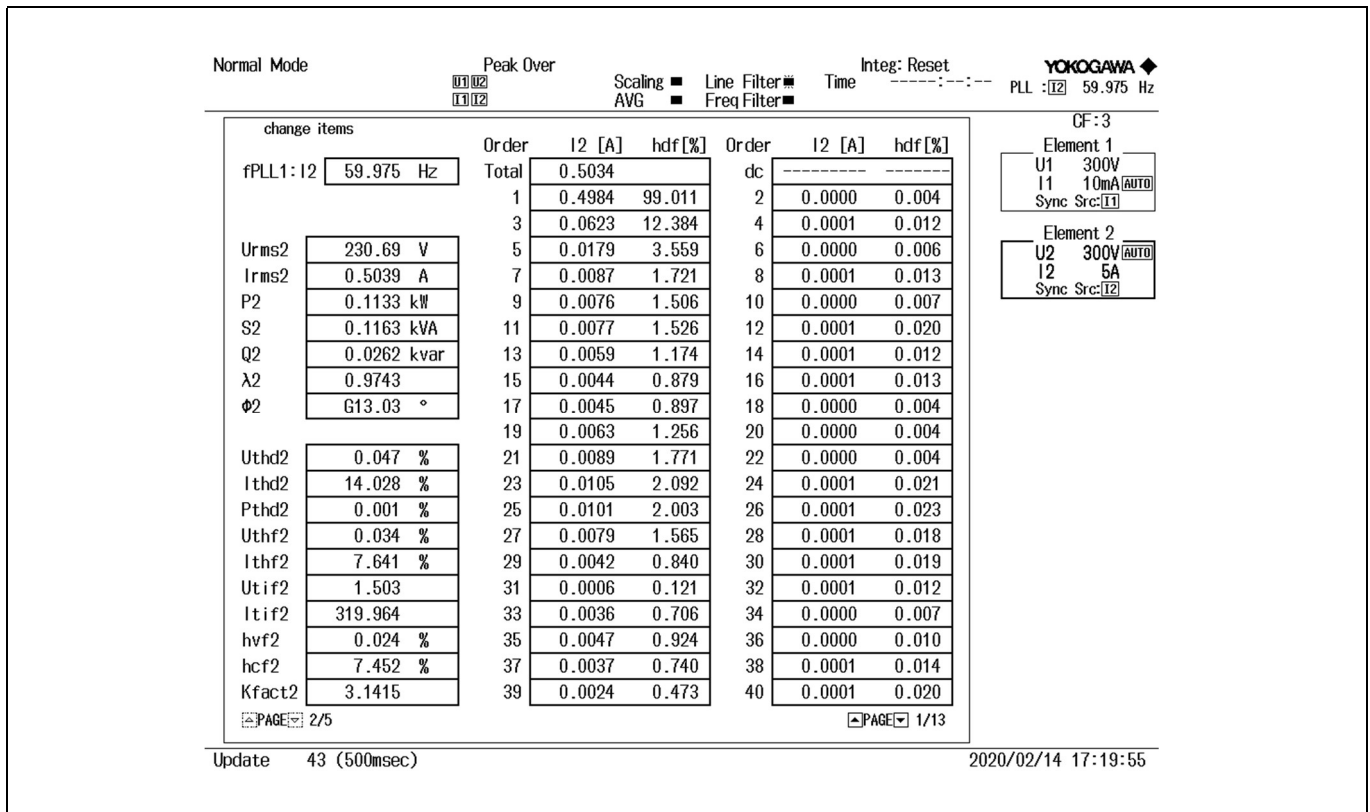


Figure 27 Power analyzer read-out at 230 V AC<sub>RMS</sub> input with 4.2 A load

Test results

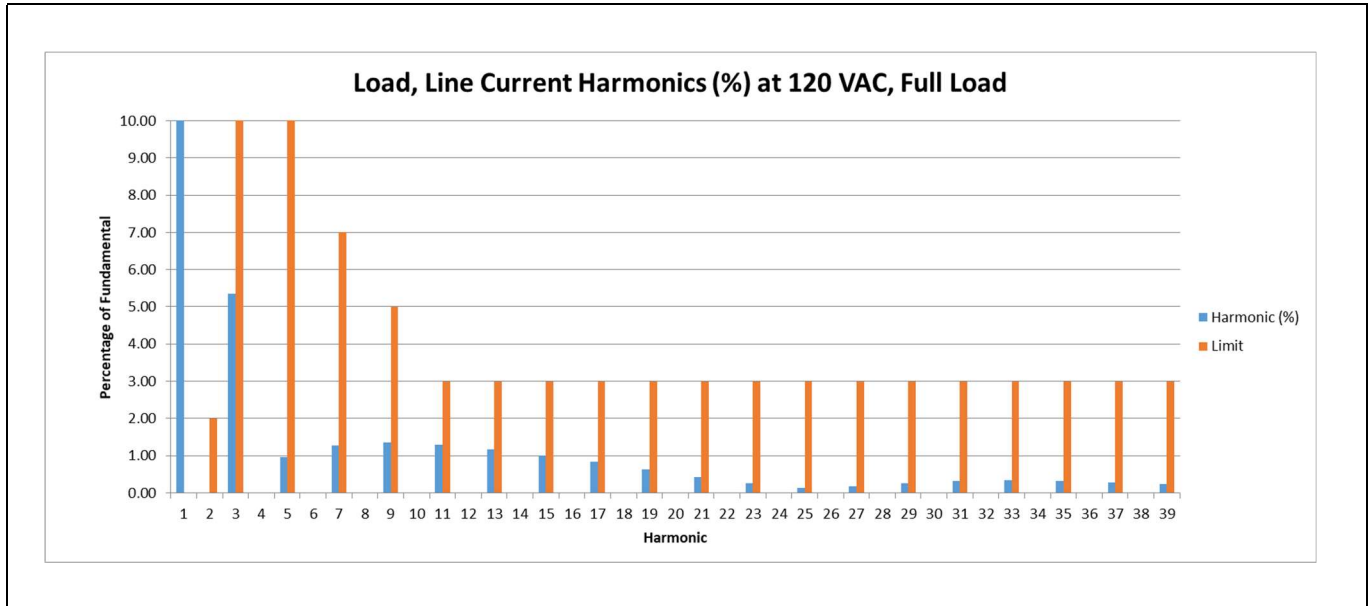


Figure 28 Input current harmonics compared with class D limits at 120 V AC<sub>RMS</sub> input with 4.2 A load

 


Figure 29 Input current harmonics compared with class D limits at 230 V AC<sub>RMS</sub> input with 4.2 A load

It is shown that the input current harmonics at full load are well within the class D limits of standard EN 61000-3-2 at both nominal input voltages.

Test results

12.1 Operating waveforms

 


Figure 30 120 V AC<sub>RMS</sub> steady-state operation at 100 percent load: output voltage  $V_{OUT}$  ripple (red), input current (blue), current sense  $V_{CS}$  (yellow),  $V_{CC}$  (green)



 


Figure 31 120 V AC<sub>RMS</sub> start-up operation at 100 percent load: output voltage  $V_{OUT}$  (red), input current (blue), rectified input voltage (yellow),  $V_{CC}$  (green)

## Test results

 


**Figure 32** 120 V AC<sub>RMS</sub> steady-state operation at 100 percent load: COMP voltage (yellow), Primary MOSFET gate V<sub>GS</sub> (blue), zero crossing voltage V<sub>ZX</sub> (red)

 


**Figure 33** 120 V AC<sub>RMS</sub> line zero crossing: MOSFET gate V<sub>GS</sub> (yellow), zero crossing voltage V<sub>ZX</sub> (blue), Primary MOSFET drain voltage (red), current sense voltage (V<sub>CS</sub>)



## Test results

 

**Figure 34** 120 V AC<sub>RMS</sub> steady-state operation at 100 percent load: drain voltage  $V_{DS}$  (red), Primary MOSFET gate  $V_{GS}$  (yellow), current sense voltage  $V_{CS}$  (green), zero crossing voltage  $V_{Zx}$  (blue)

 


**Figure 35** No-load burst mode operation at 120 V AC<sub>RMS</sub>: COMP voltage (yellow), Primary MOSFET gate voltage  $V_{GS}$  (blue), zero crossing voltage  $V_{Zx}$  (red)




# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Test results

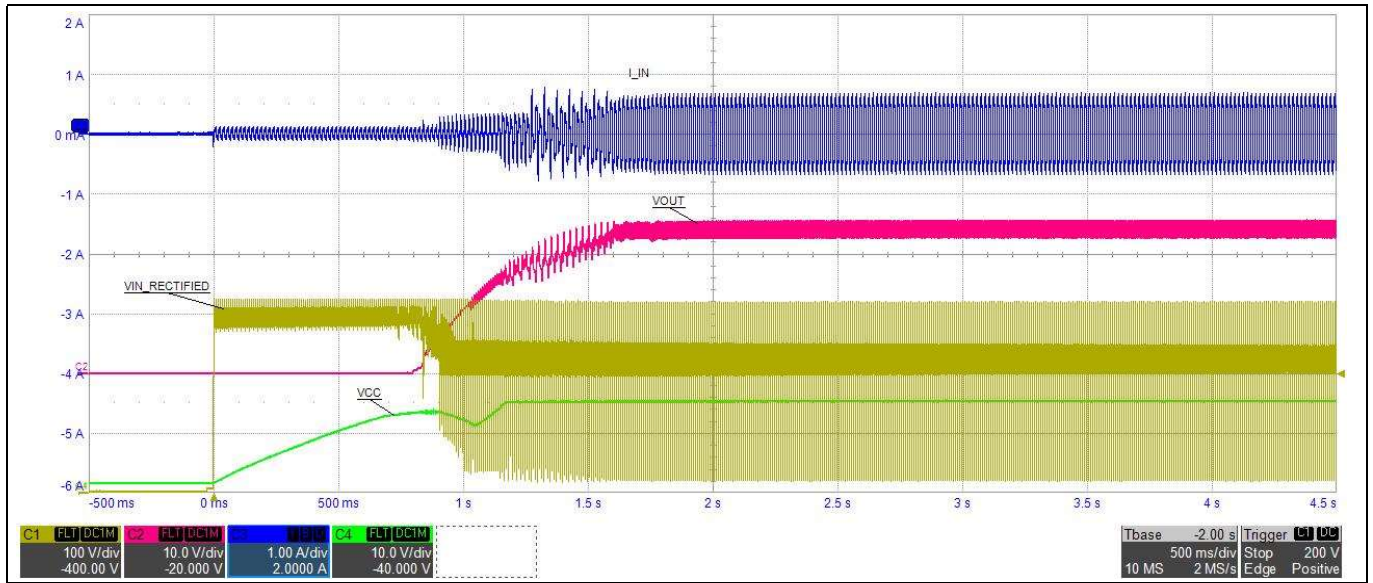

**Figure 36** 230 V AC<sub>RMS</sub> start-up operation at 100 percent load: output voltage  $V_{OUT}$  (red), input current (blue), rectified input voltage (yellow),  $V_{CC}$  (green)

 


**Figure 37** 230 V AC<sub>RMS</sub> steady-state operation at 100 percent load: output voltage  $V_{OUT}$  ripple (red), input current (blue), current sense  $V_{CS}$  (yellow),  $V_{CC}$  (green)


# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Test results

 

**Figure 38** 230 V AC<sub>RMS</sub> steady-state operation at 100 percent load: drain voltage  $V_{DS}$  (red), Primary MOSFET gate  $V_{GS}$  (yellow), current sense voltage  $V_{CS}$  (green), zero crossing voltage  $V_{Zx}$  (blue)

 


**Figure 39** 230 V AC<sub>RMS</sub> steady-state operation at 100 percent load: COMP voltage (yellow), Primary MOSFET gate  $V_{GS}$  (blue), zero crossing voltage  $V_{Zx}$  (red)


# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Test results

 


**Figure 40** 230 V AC<sub>RMS</sub> line zero crossing: MOSFET gate V<sub>GS</sub> (yellow), zero crossing voltage V<sub>Zx</sub> (blue), Primary MOSFET drain voltage (red)

 


**Figure 41** No-load burst mode operation at 230 V AC<sub>RMS</sub>: COMP voltage (yellow), Primary MOSFET gate voltage V<sub>GS</sub> (blue), zero crossing voltage V<sub>Zx</sub> (red)

Test results

 


**Figure 42** 120 V AC<sub>RMS</sub> steady-state operation at 100 percent load: Secondary MOSFET drain voltage  $V_{DS}$  (yellow), MOSFET  $V_{GS}$  (red)

 


**Figure 43** 230 V AC<sub>RMS</sub> steady-state operation at 100 percent load: Secondary MOSFET drain voltage  $V_{DS}$  (yellow), MOSFET  $V_{GS}$  (red)



Test results

 


**Figure 44** Overload from 4.2 A to 5 A  
 Primary MOSFET  $V_{GS}$  (yellow),  $V_{OUT}$  (red),  $I_{OUT}$  (blue), COMP (green)

 


**Figure 45** Overload recovery from 5 A to 4.2 A  
 Primary MOSFET  $V_{GS}$  (yellow),  $V_{OUT}$  (red),  $I_{OUT}$  (blue), COMP (green)

Test results

 

**Figure 46 Output short circuit at 4.2 A**  
**Primary MOSFET  $V_{GS}$  (yellow),  $V_{OUT}$  (red),  $I_{OUT}$  (blue), COMP (green)**

 

**Figure 47 Output short circuit recovery to 4.2 A**  
**Primary MOSFET  $V_{GS}$  (yellow),  $V_{OUT}$  (red),  $I_{OUT}$  (blue), COMP (green)**

Test results

12.2 Thermal performance under normal operating conditions

Thermal images captured under conditions of 120 V AC input, 24 V/4.2 A load (after 1 hour of operation):

 


Figure 48 Top-side thermal image

 


Figure 49 Bottom-side thermal image




# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L




## Test results

Thermal images captured under conditions of 230 V AC<sub>RMS</sub> input, 24 V/4.2 A load (after 1 hour of operation):

 

**Figure 50** Top-side thermal image

 

**Figure 51** Bottom-side thermal image

Test results

12.3 Conducted EMI

 


Figure 52 Conducted emissions at 120 V AC<sub>RMS</sub> with 100 percent load



Figure 53 Conducted emissions at 230 V AC<sub>RMS</sub> with 100 percent load

The limit lines in the above figures represent EN 55022 class B limits for the quasi-peak in red and average in yellow. Frequency sweep measurements are shown in red for quasi-peak and pink for average. The results provided here are from pre-compliance tests only. These were not carried out at a certified test lab. For compliance with the standard the traces must remain below their respective limit lines for both quasi-peak and average measurements, as shown in the table below.

Tests were carried out using a 4.2 A resistive load. EMI emissions are very dependent on the board layout; please refer to section 9.1.

# 100 W single-stage CrCM PFC Flyback converter using the IRS2982S and IR1161L



## Test results

**Table 5 EN 55022 class B limits for conducted EMI**

| <b>CISPR22 class B conducted EMI limits</b>     |                   |                |
|---|-------------------|----------------|
| <b>Frequency emission (MHz)</b>                 | <b>Quasi-peak</b> | <b>Average</b> |
| 0.15 to 0.50                                    | 66 to 56*         | 56 to 46*      |
| 0.50 to 5.00                                    | 56                | 46             |
| 5.00 to 30.0                                    | 60                | 50             |
|   |                   |                |
| <b>FCC part 15 class B conducted EMI limits</b> |                   |                |
| <b>Frequency emission (MHz)</b>                 | <b>Quasi-peak</b> | <b>Average</b> |
| 0.15 to 0.50                                    | 66 to 56*         | 56 to 46*      |
| 0.50 to 5.00                                    | 56                | 46             |
| 5.00 to 30.0                                    | 60                | 50             |
|   |                   |                |

\*Decreases with logarithm of the frequency

### **Note**

Infineon Technologies does not guarantee compliance with any EMI standard.

### 13 Conclusion

The DEMO\_100W\_24VDC\_FB evaluation board demonstrates a low-cost single-stage PFC Flyback power supply design successfully implemented with the IRS2982S.

It has been shown that the IRS2982S operating in CrCM is able to provide a very high power factor with low-line current THD over the input range. The benefits of SR using the IR1161L to improve efficiency and minimize output rectifier losses have also been demonstrated.

Furthermore operation over a wide line and load range can be achieved by moving to DCM operation at light loads using voltage mode control as long as rapid dynamic response is not required. The minimum off-time limit prevents the switching frequency from rising too high thereby limiting MOSFET switching losses. The secondary-side feedback circuit demonstrates a very tight voltage regulation over a wide load and line range. Accuracy of regulation over the output current range remains within +/-2.5 percent of the nominal output over the input line voltage range. It has been demonstrated that to achieve these results the control loop must be designed carefully to accommodate a wide line-load range while also maintaining stability and best possible power factor and iTHD.

The short-circuit and over-load protection functions are implemented. Brown out protection has also been implemented with minimal external components. Both of these functions have been verified.

The start-up time of the power supply over the input voltage range is less than 2 s measured at 120 V AC<sub>RMS</sub> and 230 V AC<sub>RMS</sub> line inputs. The component temperatures on the board remain less than 85°C under all line and load conditions.

Test results show that the design specifications have been met.

## References

- [1] IRS2505LPBF SMPS control IC datasheet, Infineon Technologies
- [2] IRS2982S SMPS control IC datasheet, Infineon Technologies
- [3] IRS2505L  $\mu$ PFC control IC design guide, Peter B. Green and Helen Ding, Infineon Technologies
- [4] Peter B. Green, 55 W Flyback converter design using the IRS2982 controller, [https://www.infineon.com/dgdl/Infineon-ApplicationNote\\_55WFlyback\\_ConverterDesign\\_IRS2982S\\_controller\\_IRXLED04-AN-v01\\_02-EN.pdf?fileId=5546d46253f6505701547c76f7d57264](https://www.infineon.com/dgdl/Infineon-ApplicationNote_55WFlyback_ConverterDesign_IRS2982S_controller_IRXLED04-AN-v01_02-EN.pdf?fileId=5546d46253f6505701547c76f7d57264)
- [5] Using the IRS2982S in a PFC Flyback with opto-isolated feedback, [https://www.infineon.com/dgdl/Infineon-AN\\_201610\\_PL16\\_01-AN-v01\\_00-EN.pdf?fileId=5546d4625a888733015a91a5e0fa622e](https://www.infineon.com/dgdl/Infineon-AN_201610_PL16_01-AN-v01_00-EN.pdf?fileId=5546d4625a888733015a91a5e0fa622e)
- [6] 90 W PFC evaluation board for the IRS2505L. [https://www.infineon.com/dgdl/Infineon-aneval\\_201511\\_pl16\\_012-AN-v02\\_00-EN.pdf?fileId=5546d462533600a40153559ff7761263](https://www.infineon.com/dgdl/Infineon-aneval_201511_pl16_012-AN-v02_00-EN.pdf?fileId=5546d462533600a40153559ff7761263)
- [7] Christophe Basso, Switch-Mode Power Supplies: SPICE Simulations and Practical Designs, second edition

## Conclusion

## Revision history

| Document version | Date of release | Description of changes   |
|------------------|-----------------|--|
| 1.0              | 9/25/2019       | First release  |
| 2.0              | 1/28/2020       | Modified overload and short-circuit protection circuits. Test results updated. More test waveforms added. Minor corrections. |
|                  |                 |  |

**Trademarks**

All referenced product or service names and trademarks are the property of their respective owners.

**Edition 2020-02-20**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2020 Infineon Technologies AG.**

**All Rights Reserved.**

**Do you have a question about this document?**

**Email: [erratum@infineon.com](mailto:erratum@infineon.com)**

**Document reference**

**AN\_1909\_PL88\_1909\_005304**

**IMPORTANT NOTICE**

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology delivery terms and conditions and prices please contact your nearest Infineon Technologies office ([www.infineon.com](http://www.infineon.com)).

**WARNINGS**

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.