Frequency modulation techniques

2011 February



Overview of FM modulation techniques



Modulator type	Short description	Advantages	Disadvantage	Block diagram	Key feature
Switched capacitor	• a chip-internal transistor is switched ON and OFF by the modulating signal. The frequency is pulled (between FSK_low and FSK_high) values due to this additional (switched) capacitor Typical representatives TDK510x and TDK511x family PMA5110 and PMA7105; PMA7106; PMA7107; PMA7110 family	simple, robust, easy to implement works "on the fly", no need to program anything, just apply the power and the modulating and control signal	 the maximum frequency shift is determined mainly by parameters of the crystal (crystal pullability) and careful selection for value of the frequency setting capacitor (C) is required tradeoff between startup time and frequency shift capability (due to inherent nature of crystal resonators) unwanted but low energy transients may appear in spectrum due to capacitor switching 	Modulation signal (applied to FSKDTA pin) Frequency shift setting capacitor Load capacitor for crystal Load capacitor for crystal Swetch FSK ATAL PFD Clock Output	Low cost , simple solutions
With external varactor	the crystal pulling is achieved over a varactor for higher demands of linearity a pair of varactors may be connected into antiparalel group Typical representatives The solution can be applied to the TDK510x; TDK511x and PMA5110 / PMA71xx family	clean, predictable spectrum, very low amount of transients, less sideband noise as by switched capacitor type modulator works "on the fly", no need to program anything, just apply the power and the modulating signal	The maximum frequency shift is determined by: parameters of the crystal used in application (> crystal pullability) and varactor characteristics (i.e. Cmax/Cmin ratio) limitations regarding Cmin / Cmax capacitance variation (of varactor) due to low power supply voltage and limited modulation signal voltage swing	Modulation signal (applied to varactor) RF blocking coil RF rejection capacitor	Low cost
Digital modulator	the digital modulation is achieved by seamlessly changing the division ratio of a Fractional-N type synthesizer between two "end" frequencies Typical representatives TDA5150 transmitter, TDA5340 transceiver	almost unlimited freedom in setting the size and shape of frequency shift vs. time function switchover between FSK and GFSK over software (by reprogramming some of SFR registers) no special crystal pullability requirements, the crystal swings always on same frequency well suited for multichannel systems for identical modulation indexes the occupied bandwidth (OBW) of a GFSK signal is less then of a FSK signal, thus GFSK is more effective in terms of spectrum usage	to avoid (minimize) fractional spurs some rules in choice of the synthesizer's fractional part ratio have to be obeyed Note: this does not limit the system's flexibility in terms of reference clock selection a Host (usually microcontroller) is required to program the chip before transmission can be started Note: this is not a real drawback, as by most practical applications a microcontroller is part of the system. Steering functions and modulation signal (data stream) are derived usually from the uC unit.	XOSC clock division Gauss Divider Ratio Divider FSK / GFSK Filter Mode (FSK: GFSK: ASK) TDA5150; Digital Modulator block	Easy design-in High flexibility, Multiband, multichannel