

Applications for depletion MOSFETs

About this document

Scope and purpose

Depletion MOSFETs, unlike enhancement MOSFETs, are in an on-state even at 0 V of gate-to-source voltage (V_{GS}). This feature makes them suitable for using as a constant current source as well as in other ways. This application note explains how depletion MOSFETs can be used in different applications.

Intended audience

This document is intended for electronic equipment designers.

Table of contents

About this document	1
Table of contents	1
1 What is a depletion MOSFET?	2
2 How to use a depletion MOSFET	3
2.1 Adjusting the drain current	3
2.2 Depletion MOSFET in a start-up circuit	3
2.3 Linear regulators	6
2.3.1 Example	6
2.3.2 Other examples	6
3 Depletion MOSFETs from Infineon	8
Revision history	9

Applications for depletion MOSFETs

What is a depletion MOSFET?

1 What is a depletion MOSFET?

As depletion MOSFETs are in the on-state (i.e. they can conduct current) even when the gate-to-source voltage (V_{GS}) is zero. This can be best shown by comparing the transfer characteristics of enhancement and depletion MOSFETs.

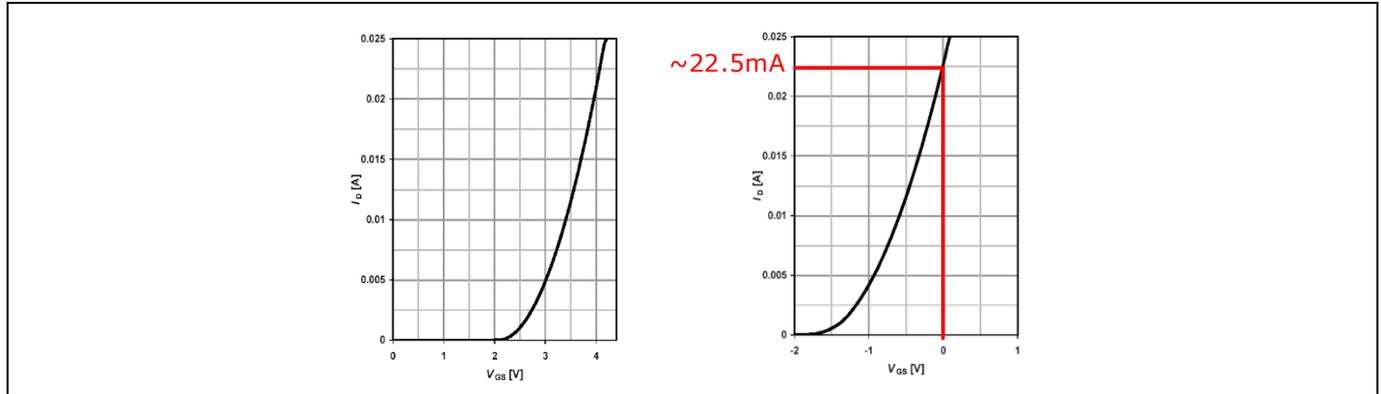


Figure 1 Transfer characteristics of enhancement (BSS127) and depletion (BSS126) MOSFETs

Static characteristics						
Drain-source breakdown voltage	$V_{(BR)DSS}$	$V_{GS} = -5\text{ V}, I_D = 250\ \mu\text{A}$	600	-	-	V
Gate threshold voltage	$V_{GS(th)}$	$V_{DS} = 3\text{ V}, I_D = 8\ \mu\text{A}$	-2.7	-2.0	-1.6	

Figure 2 Screenshot from the datasheet for BSS126

Figure 1 illustrates an example of the transfer characteristics of both devices. For a MOSFET, the gate-to-source voltage (V_{GS}) should be higher than the gate-to-source threshold voltage ($V_{GS(th)}$) in order to conduct current through it. For an N-channel enhancement MOSFET $V_{GS(th)}$ is above 0 V. Therefore, even at V_{GS} of 0 V, a depletion MOSFET can conduct current. To turn off a depletion MOSFET the V_{GS} should be lower than the (negative) $V_{GS(th)}$. This is clearly shown in schematic symbols for both. Figure 3 below shows the schematic symbols for enhancement and depletion MOSFETs respectively.

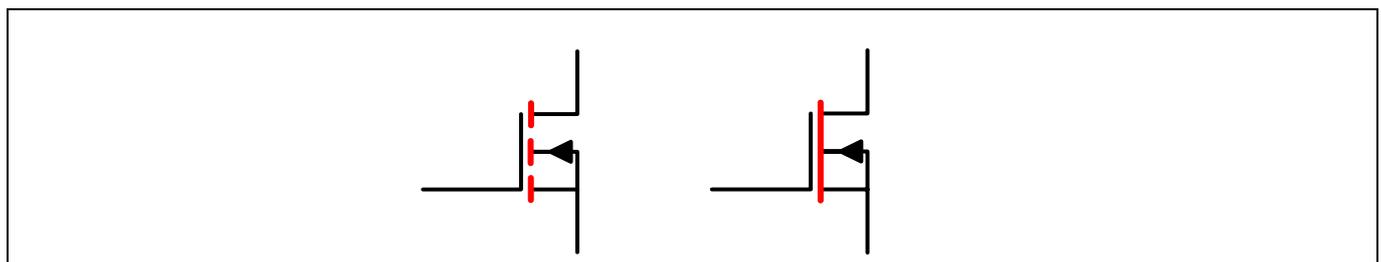


Figure 3 Differences in schematic symbols – enhancement (left) and depletion (right) MOSFET

The symbols for enhancement and depletion MOSFETs show a difference in the second vertical line from the left, marked in red. For the enhancement MOSFET this line is discontinuous. This shows that the MOSFET is switched off with a $V_{GS} = 0\text{ V}$. With a $V_{GS} = 0\text{ V}$ a depletion MOSFET can conduct current, and this is shown by the dashed line.

Applications for depletion MOSFETs

How to use a depletion MOSFET

2 How to use a depletion MOSFET

Shorting gate and source, as shown in Figure 4, results in a load current independent of the applied drain-to-source input voltage. For a BSS126 this current is typically 22.5 mA.

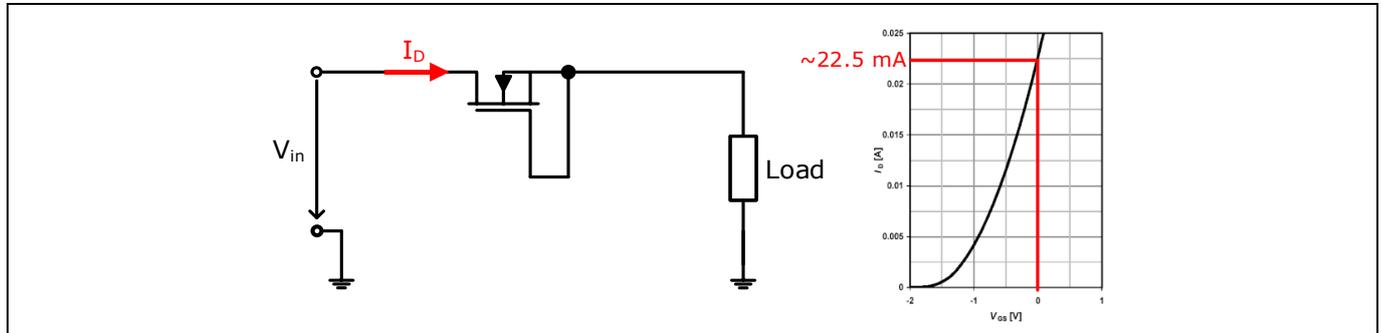


Figure 4 Typical BSS126 drain current with $V_{GS} = 0\text{ V}$

2.1 Adjusting the drain current

If the drain current at $V_{GS} = 0\text{ V}$ is too high a simple source resistor must be added to the circuit.

Figure 5 shows this arrangement. Assuming a drain current of 4 mA the gate-to-source must be -1 V, i.e. the resistor's value is calculated using Ohm's law by $R = 1\text{ V} / 4\text{ mA} \sim 250\ \Omega$.

This is valid for a typical BSS126. In reality the device's tolerances have to be taken into account

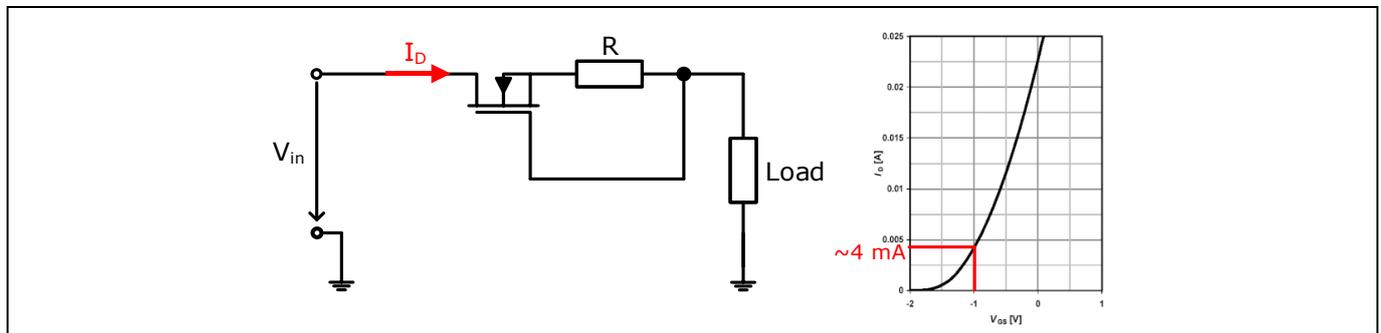


Figure 5 BSS126 with adjusted drain current

2.2 Depletion MOSFET in a start-up circuit

Depletion MOSFETs are widely used in a start-up circuit of auxiliary power supplies.

To power up a PWM IC in a flyback circuit a very common method is shown in Figure 6.

A resistor is connected between the positive rail (for example the rectified mains voltage or a PFC voltage) and the IC's capacitor, C. Typically this capacitor's value is between 10 μF and 100 μF . The start-up time shouldn't be too long.

Applications for depletion MOSFETs

How to use a depletion MOSFET

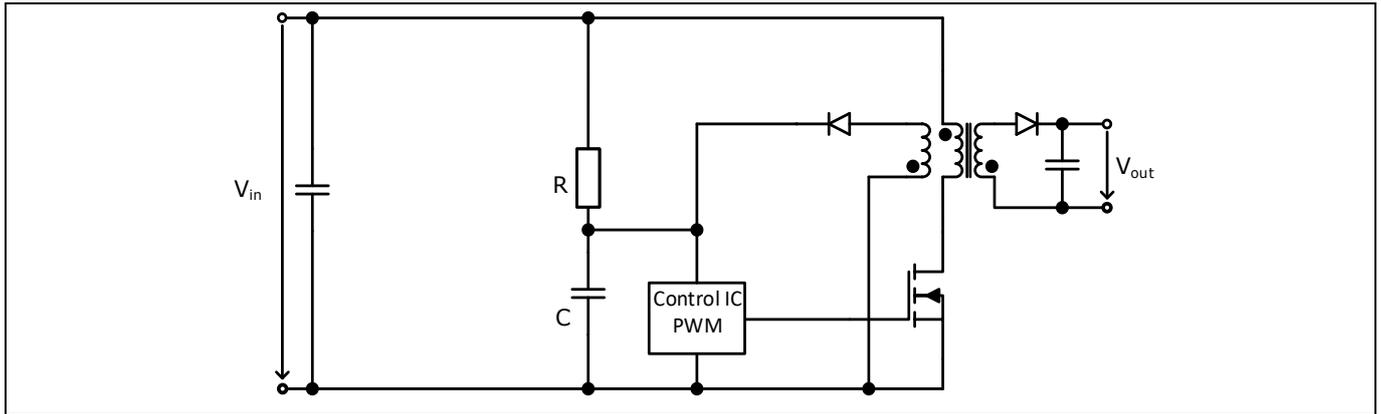


Figure 6 Flyback with control IC and simple resistor start-up circuit

Example: $V_{in} = 400\text{ V}$, $C = 47\text{ }\mu\text{F}$, IC's start-up voltage $V_{ic} = 10\text{ V}$

Assuming the use of SMD resistors the power losses are limited to 0.25 W , i.e. $R \geq (400\text{ V})^2 / 0.25\text{ W} \sim 640\text{ k}\Omega$.

The resulting current is calculated by $T_{start} \sim 400\text{ V} / 640\text{ k}\Omega = 625\text{ }\mu\text{A}$.

The start-up time $T_{start} = C \cdot V / I = 22\text{ }\mu\text{F} \cdot 10\text{ V} / 625\text{ }\mu\text{A} = 0.352\text{ s}$.

If this circuit is used at low-line voltage, e.g. $\sim 110\text{ V}$, the start-up time is increased to $\sim 1\text{ s}$, which in many applications is too long.

Additionally most PWM ICs already sink several hundred μA before they reach the start-up threshold, resulting in an even longer start-up time with this resistor arrangement.

The start-up time can be optimized by decreasing the values of R and/or C.

Decreasing the resistance increases the losses, while decreasing C is sometimes not possible.

A much more elegant solution is the use of a depletion MOSFET, as shown in Figure 7.

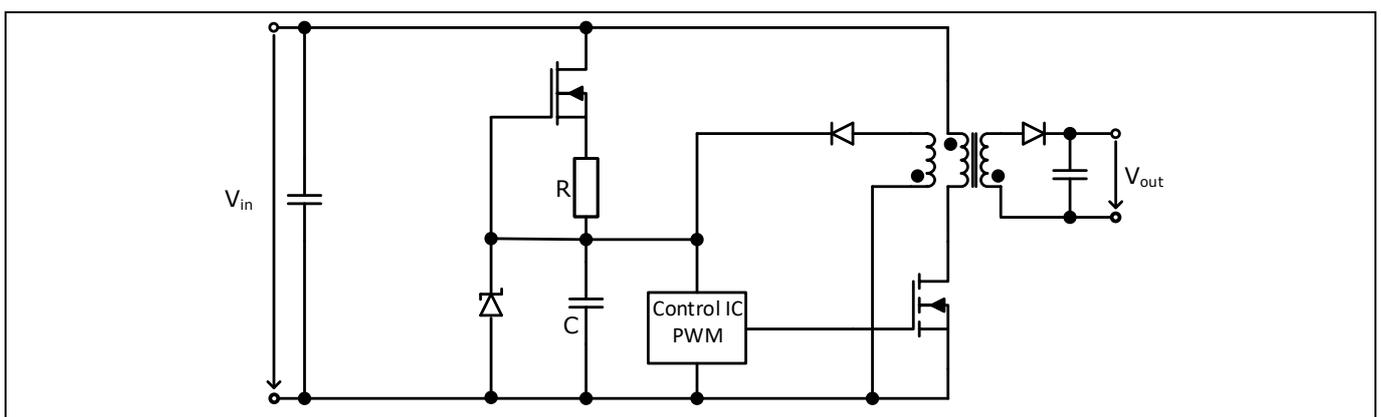


Figure 7 Flyback with control IC with a depletion MOSFET, adjusted drain current

Now the start-up time is independent of the input voltage.

This circuit can be further optimized by adding a few SMD devices – see Figure 8.

Applications for depletion MOSFETs

How to use a depletion MOSFET

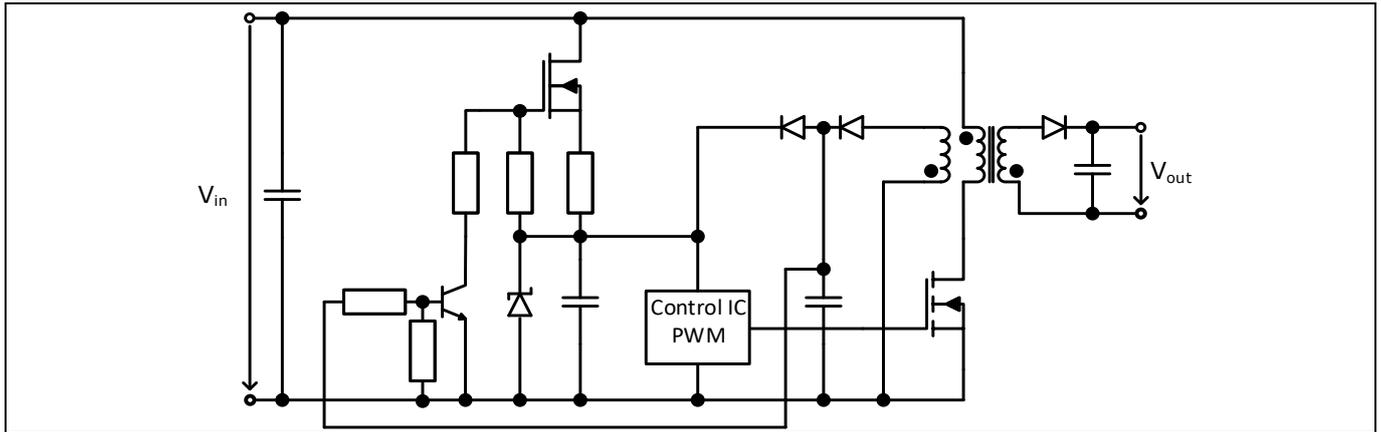


Figure 8 Flyback with control IC with a depletion MOSFET, adjusted drain current and without standby losses

The depletion MOSFET with adjusted drain current powers up the IC. If the voltage delivered by the auxiliary winding is high enough the NPN transistor is triggered, pulling down the gate of the depletion MOSFET below its threshold voltage and switching it completely off.

Example: The depletion MOSFET BSS126 (600 V, 700 Ω, SOT-23) is a good choice. A reasonable start-up time for many applications is 200 ms or shorter. Assuming a PWM IC's standby current of 100 μA and a capacitor's value of 47 μF the start-up current I_D is calculated to:

$$I_D = C \cdot V / t + 100 \mu\text{A} = 22 \mu\text{F} \cdot 10 \text{ V} / 200 \text{ ms} + 100 \mu\text{A} = 1.2 \text{ mA}$$

The depletion MOSFET is switched off shortly after the start-up time of 200 ms so the Z_{thJA} can be used to check if the device is used within its thermal limits.

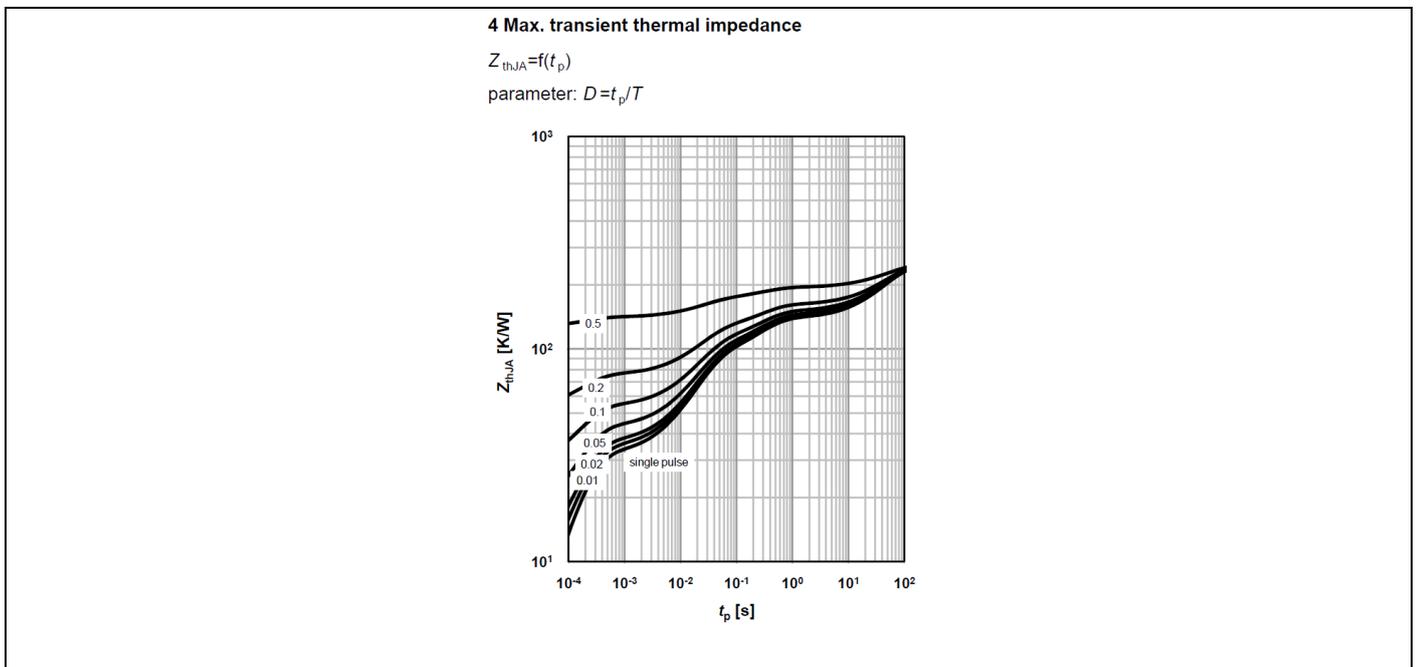


Figure 9 Z_{thJA} diagram – BSS126

For 200 ms the Z_{thJA} is around 120 K/W on a standard PCB. With $V_{in} = 400 \text{ V}$ and an $I_D = 1.2 \text{ mA}$ the losses are $P = 400 \text{ V} \cdot 1.2 \text{ mA} = 480 \text{ mW}$. The temperature rise during the start-up time is now calculated to $\Delta T = 480 \text{ mW} \cdot 120 \text{ K/W} = 57.6 \text{ K}$. A temperature rise of 57.6 K is absolutely acceptable.

Applications for depletion MOSFETs

How to use a depletion MOSFET

2.3 Linear regulators

A depletion MOSFET can also be used as a pass transistor for a linear regulator. Figure 10 shows a linear regulator circuit using a depletion MOSFET plus a Zener diode.

In the circuit, Q_1 acts as a source follower where the source voltage follows the gate voltage (V_G) minus the gate-to-source voltage. V_{GS} increases with increasing drain current. Thus, with a fixed gate voltage, the source voltage will drop with increasing load current. For design purposes, V_{GS} under saturation and cut-off conditions (0 V and $V_{GS(th)}$, respectively) can be used. These values can be readily obtained from the datasheet, and Figure 11 shows the cut-off and saturation conditions of the Infineon BSS169. Bias current for the Zener diode is determined by V_{GS}/R . The Zener diode sets the gate voltage and should be selected to provide a source voltage within the range determined, taking into account the variances of V_{GS} with load.

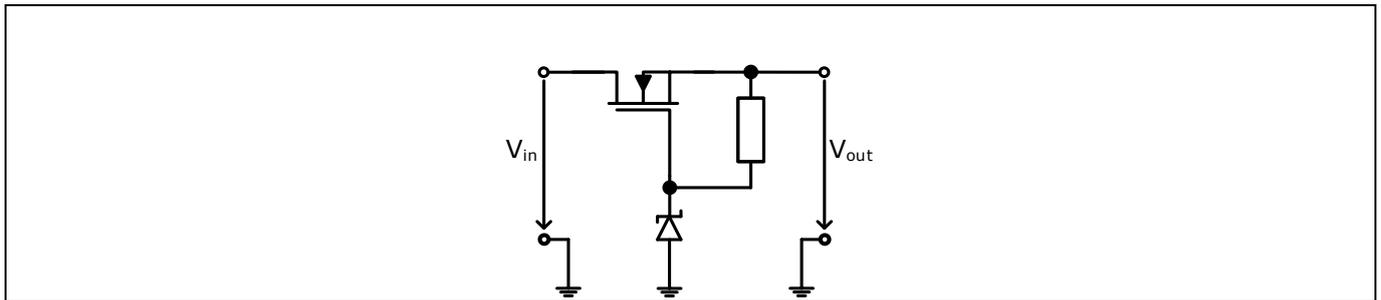


Figure 10 Depletion MOSFET as a linear regulator

The point to be noted here is that the MOSFET's saturation current must be higher than the required load and bias currents, otherwise the device can be stressed or destroyed due to over-current.

Static characteristics						
Drain-source breakdown voltage	$V_{(BR)DSS}$	$V_{GS}=-10\text{ V}, I_D=250\ \mu\text{A}$	100	-	-	V
Gate threshold voltage	$V_{GS(th)}$	$V_{DS}=3\text{ V}, I_D=50\ \mu\text{A}$	-2.9	-2.2	-1.8	

Figure 11 Gate threshold voltage for BSS169

2.3.1 Example

The application above can be explained more clearly with an example. Consider a regulator with 5 V output at 5 mA of output current from 24 V input using Infineon's depletion MOSFET BSS169.

With a 3.3 V Zener diode the output voltage varies due to the MOSFET's $V_{GS(th)}$ spread of 4.7 V to 5.5 V. The resulting power dissipation of the BSS169 is calculated to 0.1 W, which is an acceptable value and well below the specified power limit.

2.3.2 Other examples

A constant current source can be used in many different applications. A few examples are listed below:

- A constant current source is useful to generate a bias current that is independent of the voltage across it. It can be used to charge a capacitor at a constant rate, generating a linear ramp for timing purposes.
- A constant current source can be used as a trickle charger to maintain battery charge state.
- A constant current source can be used as a current limiter when the current is below the limit.

Applications for depletion MOSFETs

How to use a depletion MOSFET

- A constant current source can also be used as a linear LED driver for driving LED strings typically up to 20 mA. Figure 12 shows a linear LED driver circuit using a depletion MOSFET and a series resistor.

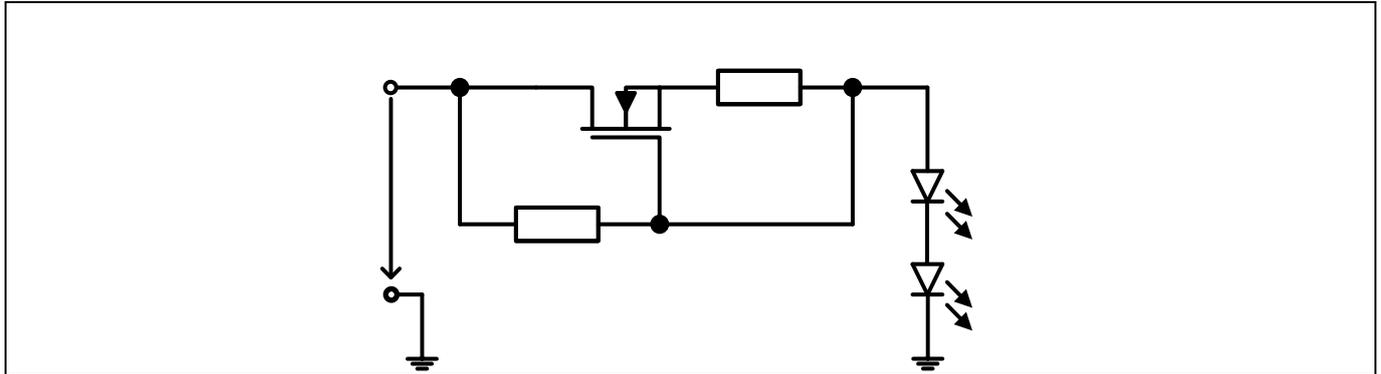


Figure 12 Depletion MOSFET as a linear LED driver

Applications for depletion MOSFETs

Depletion MOSFETs from Infineon

3 Depletion MOSFETs from Infineon

Infineon offers depletion MOSFETs in SOT-223 and SOT-23 packages, with breakdown voltages ranging from 60 V to 600 V. Table 1 shows Infineon's depletion MOSFET portfolio:

Table 1

Part number	Package	BV_{DSS} [V]	$R_{DS(on)}$ [Ω]	$V_{GS(th),max}$ [V]	$V_{GS(th),min}$ [V]	$I_{DSS,min}$ at $V_{GS} = 0$ V [mA]
BSP149	SOT-223	200	1.8	-1	-2.1	140
BSP129	SOT-223	240	6	-1	-2.1	55
BSP179	SOT-223	400	24	-1	-2.1	20
BSP135	SOT-223	600	45	-1	-2.1	20
BSS159N	SOT-23	60	3.5	-2.4	-3.5	130
BSS169	SOT-23	100	6	-1.8	-2.9	90
BSS139	SOT-23	250	14	-1	-2.1	30
BSS126	SOT-23	600	7	-1.6	-2.7	7

For Infineon's depletion MOSFETs $V_{GS(th)}$ is spread across five sorted bands. Each band has a distribution of 0.2 V and is assigned with an identification letter. Limits for each sorted band vary from $V_{GS(th),min}$ to $V_{GS(th),max}$. Figure 13 shows an example of the $V_{GS(th)}$ bands of BSP149.

Threshold voltage $V_{GS(th)}$ sorted in bands ²⁾						
J	$V_{GS(th)}$	$V_{DS}=3$ V, $I_D=8$ μ A	-1.8	-	-1.6	V
K			-1.95	-	-1.75	
L			-2.1	-	-1.9	
M			-2.25	-	-2.05	
N			-2.4	-	-2.2	

Figure 13 Threshold voltage bands

Please note:

A single specific band cannot be ordered separately. However, it can be requested that each reel contains only one band of $V_{GS(th)}$.

Applications for depletion MOSFETs

Revision history

Revision history

Document version	Date of release	Description of changes

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2018-07-20

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2018 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference

AN-1807-PL11-1809-121428

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.