

Application Note No. 031

A Low Noise Amplifier at 1.9 GHz offers +14 dBm
Input Intercept Point

RF & Protection Devices



Never stop thinking

Edition 2007-01-08

**Published by
Infineon Technologies AG
81726 München, Germany**

**© Infineon Technologies AG 2009.
All Rights Reserved.**

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Application Note No. 031

Revision History: 2007-01-08, Rev. 2.0

Previous Version:

Page	Subjects (major changes since last revision)

Trademarks

SIEGET® is a registered trademark of Infineon Technologies AG.

A Low Noise Amplifier at 1.9 GHz offers +14 dBm Input Intercept Point

1 A Low Noise Amplifier at 1.9 GHz offers +14 dBm Input Intercept Point

This application note provides general information, print layout and list of used components, circuit layout and measured data of a low noise amplifier at 1.9 GHz using Infineon SIEGET BFP450. The emphasis has been on high IP_{3in} -values

Data at 1.9 GHz (3 V and 24 mA / R1 = 33, R2 = 5.6 k)

Gain:	11 dB
IP_{3out} :	14 dBm
NF:	1.9 dB
$R_{Lin-out}$	>10 dB

Data at 1.9 GHz (3 V and 15 mA / R1 = 56, R2 = 8.2 k)

Gain:	10.5 dB
IP_{3out} :	10 dBm
NF:	1.8 dB
$R_{Lin-out}$	>10 dB

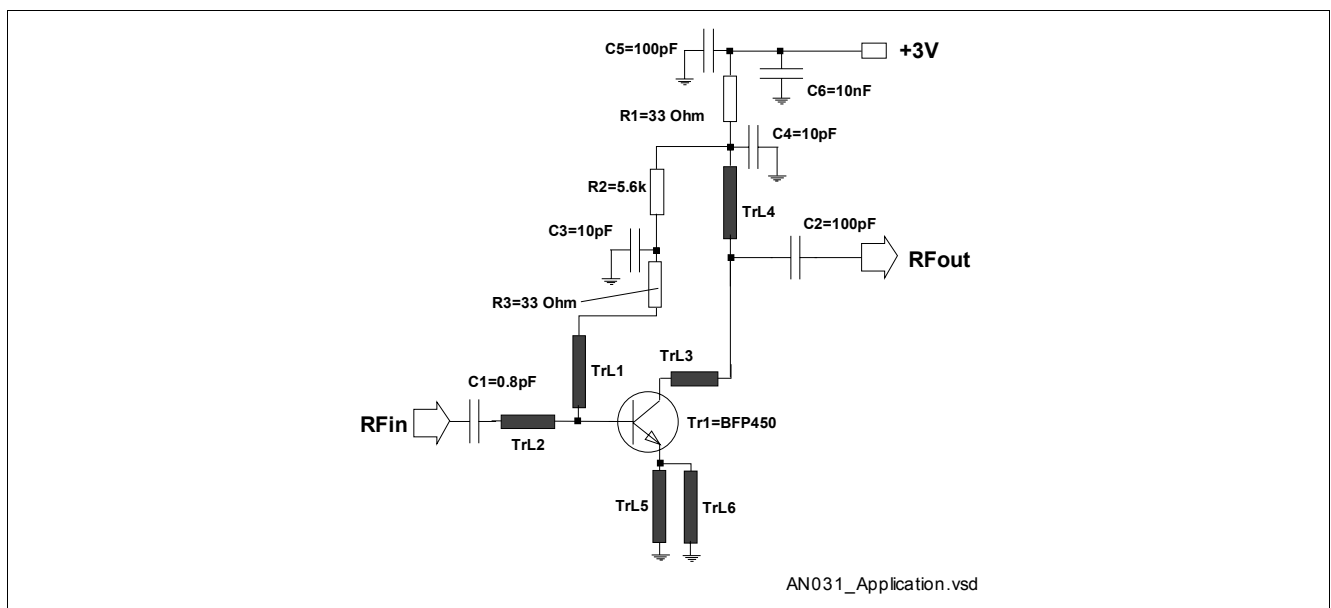


Figure 1 Application

This amplifier at 1.9 GHz has been realized by using microstrip lines for matching purposes. It offers a good compromise between low noise and high IIP_3 values. For optimizing and improving the circuit please observe the following abstract:

- The layout size can be reduced by using chip-inductors instead of the microstrip lines TrL1 and TrL4
- You are able to get a better stabilization behaviour versus temperature and a reduction of current gain distribution problems if you add a Infineon active bias controller BCR400W. This is easily done by replacing collector resistor R1 and by adding two capacitors. For further information please refer to application note No 014. However the resistor R1 and R2 are sufficient in most applications for stabilization purposes.

A Low Noise Amplifier at 1.9 GHz offers +14 dBm Input Intercept Point

- The measured figures include losses of SMA-connectors and the relatively high loss of the microstrip lines on the epoxy-board.
- Resistor R3 is used get higher circuit-stability at low frequencies.

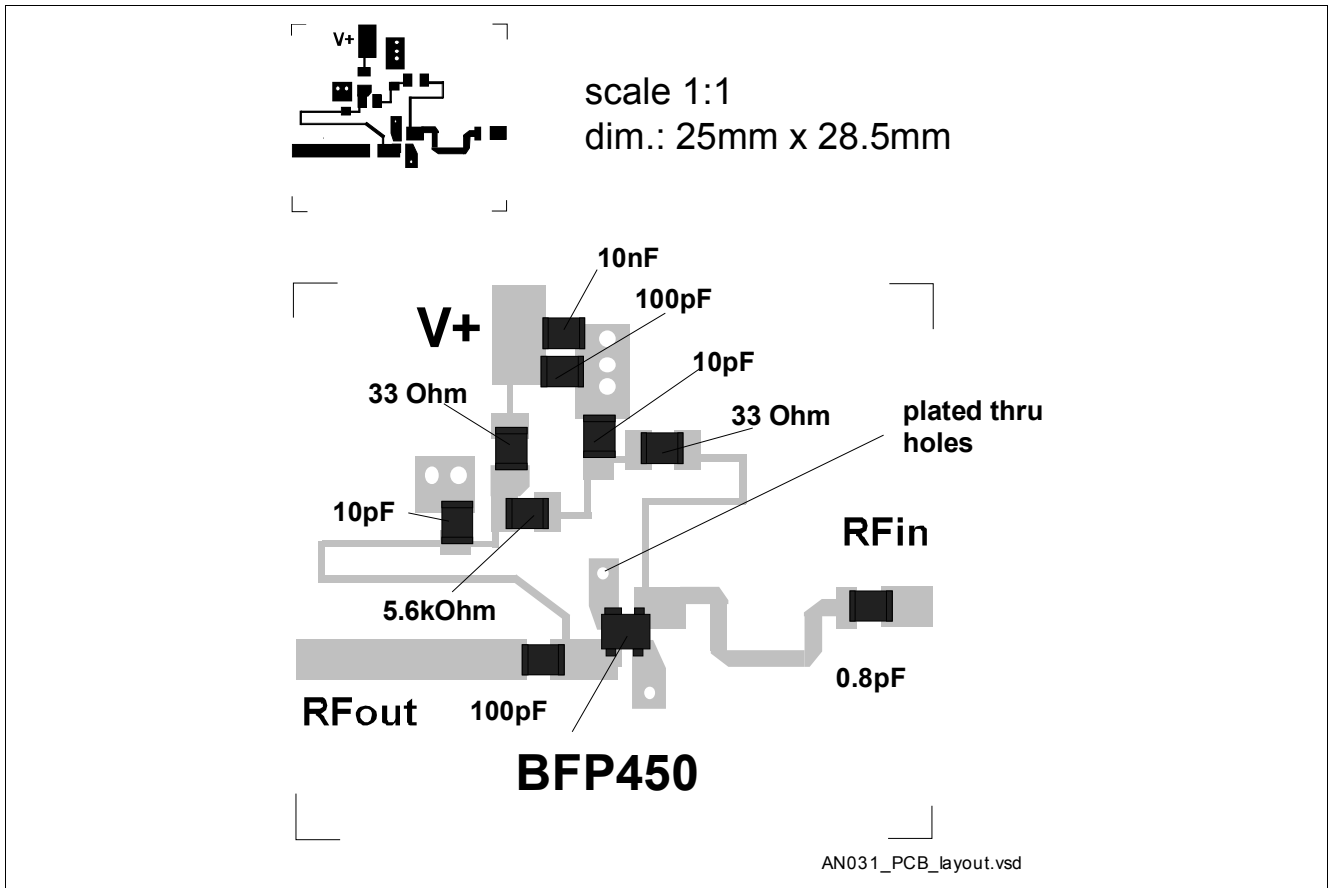


Figure 2 PCB Layout and Component Placement

A Low Noise Amplifier at 1.9 GHz offers +14 dBm Input Intercept Point

Table 1 Component

Component	Value	Unit	Size	Comment
R1	33	Ω	0603/0805	Bias / collector-resistance / $V_{R1} \cong 0.7 \text{ V}$
R2	5.6	$k\Omega$	0603/0805	Bias
R3	33	Ω	0603/0805	To improve AF-stability
C1	0.8	pF	0603/0805	Input match
C2	100	pF	0603/0805	DC-block
C3	10	pF	0603/0805	RF-short
C4	10	pF	0603/0805	RF-short
C5	100	pF	0603/0805	RF-short
C6	10	nF	0603/0805	RF-short
Tr1			SOT343	SIEGET® BFP450
TrL1				Input match, $w = 0.3 \text{ mm}$
TrL2				Input match, $w = 0.8 \text{ mm}$
TrL3				Output match, $w = 1.9 \text{ mm}$
TrL4				Output match, $w = 0.3 \text{ mm}$
TrL5				Emitter inductance, $w = 1.9 \text{ mm}$
TrL6				Emitter inductance, $w = 1.9 \text{ mm}$
Substrate	FR4			$h = 1 \text{ mm}$, $\epsilon_r = 4.5$

A Low Noise Amplifier at 1.9 GHz offers +14 dBm Input Intercept Point

Measured data

$+V = 3 \text{ Vdc}$ / $I = 24 \text{ mA}$ ($R1 = 33 \Omega$, $R2 = 5.6 \text{ k}\Omega$)

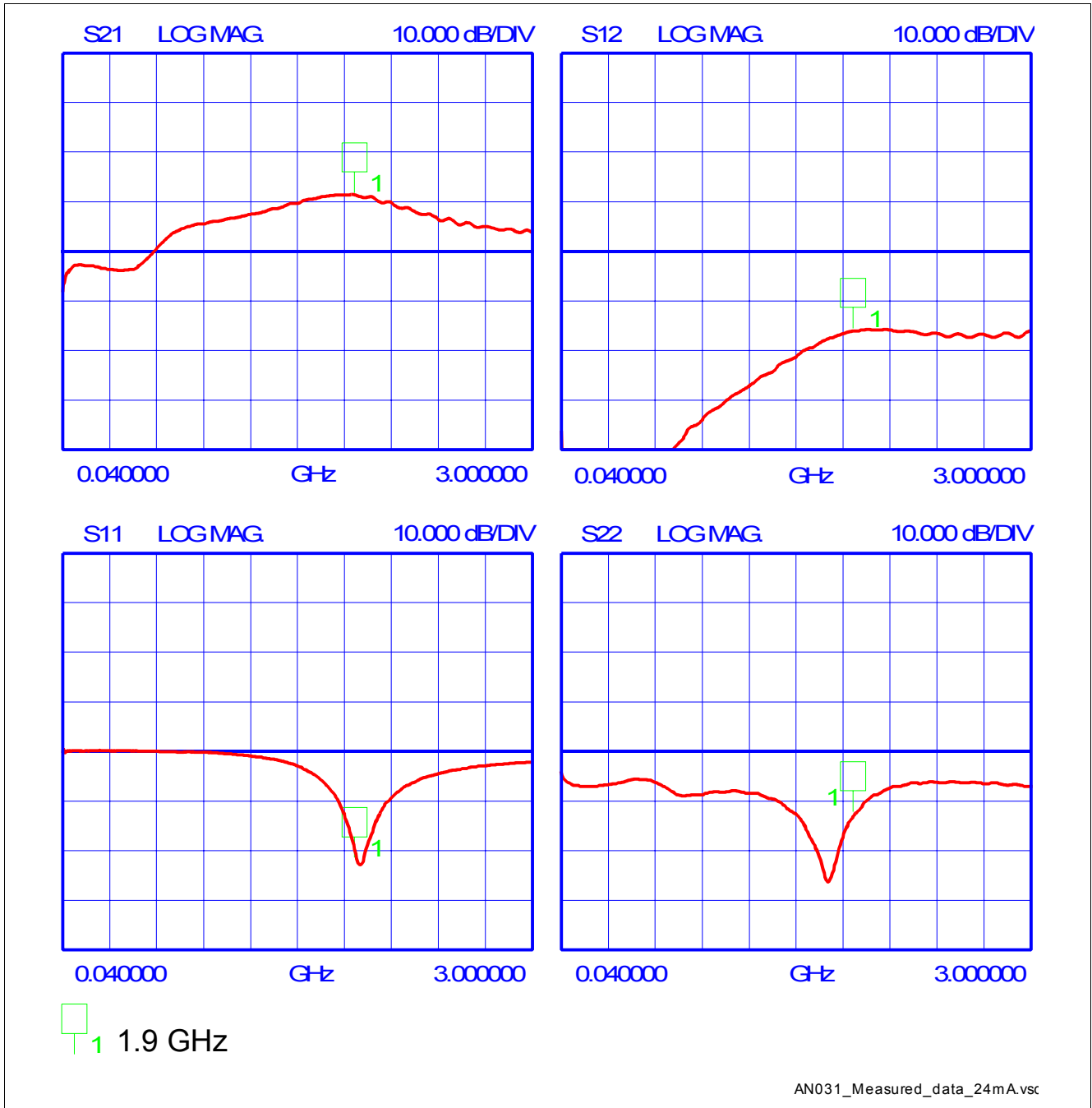


Figure 3 Measured data

A Low Noise Amplifier at 1.9 GHz offers +14 dBm Input Intercept Point

Measured data

$+V = 3 \text{ Vdc}$ / $I = 15 \text{ mA}$ ($R1 = 56 \Omega$, $R2 = 8.2 \text{ k}\Omega$)

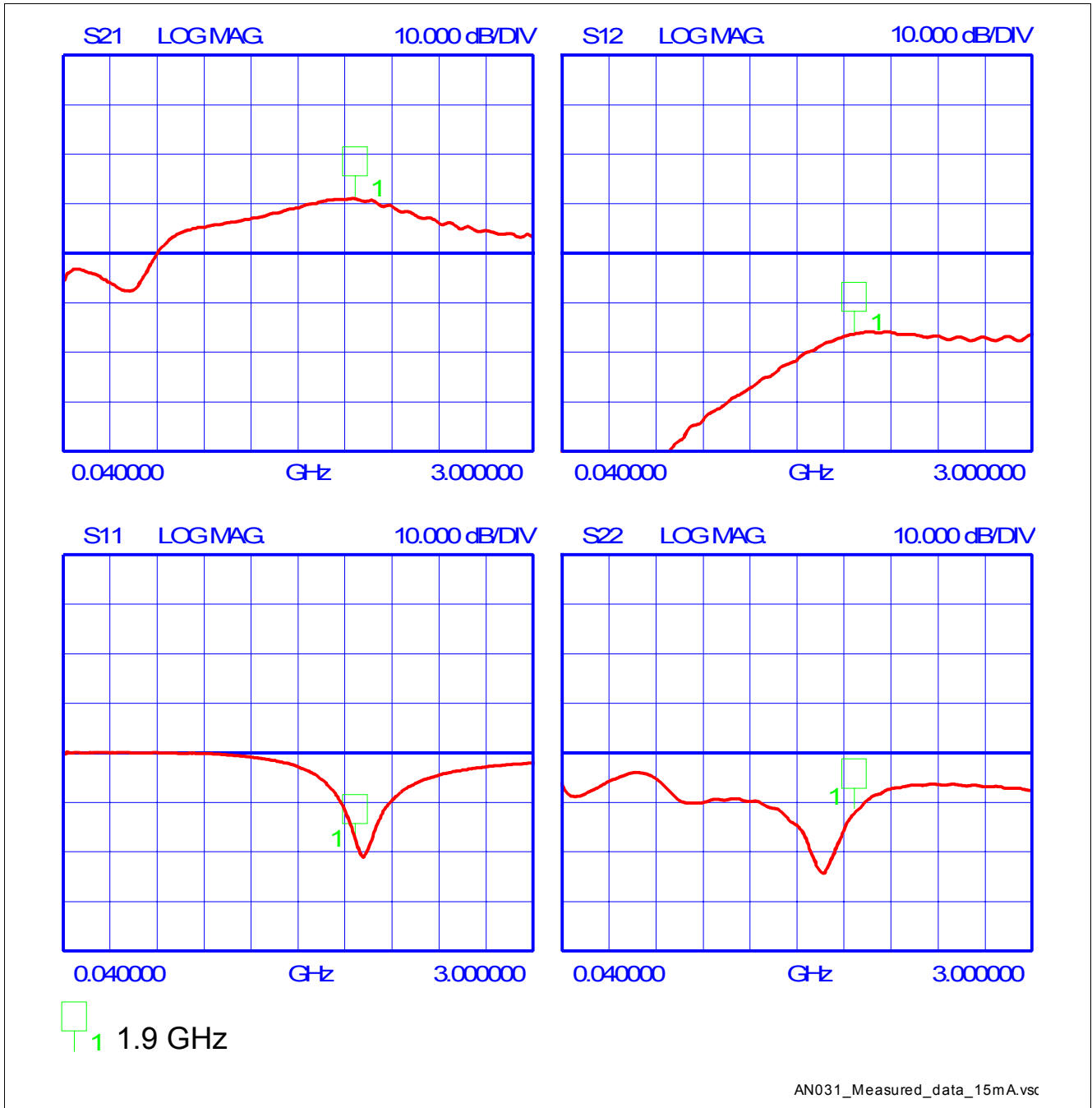


Figure 4 Measured data