

Application Note No. 120

1.8 V Low Noise Amplifier for 1575 MHz GPS
Applications using the SiGe:C BFP740F Transistor

RF & Protection Devices



Never stop thinking

Edition 2007-09-03

**Published by
Infineon Technologies AG
81726 München, Germany**

**© Infineon Technologies AG 2009.
All Rights Reserved.**

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Application Note No. 120

Revision History: 2007-09-03, Rev. 1.2

Previous Version: 2005-08-10, Rev. 1.1

Page	Subjects (major changes since last revision)
All	Document layout change

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

1 1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C BFP740F Transistor

Applications

- 1575.42 MHz GPS

Overview

- BFP740F in TSFP-4 package is evaluated for a GPS LNA application. Note TSFP-4 package is only 1.4 x 1.2 x 0.55 mm high.
Design Goals: Gain = 20 dB min, Noise Figure = 0.8 dB max, Input / Output Return Loss 10 dB or better, current < 10 mA from a 1.8 V power supply
- Printed Circuit Board used is Infineon Part Number 740F-080404 Rev A. Standard FR4 material is used in a three-layer PCB. Please refer to cross-sectional diagram below.
- Low-cost, standard "0402" case-size SMT passive components are used throughout. Please refer to schematic and Bill Of Material. The LNA is unconditionally stable from 5 MHz to 8 GHz.
- Total PCB area used for the single LNA stage is 40 mm². Total Parts count, including the BFP740F transistor, is 11.

Summary of Results

$T = 25\text{ }^{\circ}\text{C}$, Network Analyzer Source Power $\approx -30\text{ dBm}$

Table 1 Summary of Data

Frequency MHz	dB[s11] ²	dB[s21] ²	dB[s12] ²	dB[s22] ²	NF * dB	IIP ₃ dBm	OIP ₃ dBm	IP _{1dB} dBm	OP _{1dB} dBm
1575.42	10.8	19.7	27.1	12.8	0.76	+0.2	+19.9	-17.3	+1.4

PCB loss is not extracted, e.g. reference plane of measurement is at PCB input RF SMA connector. If PCB loss were extracted, noise figure result would improve by 0.1-0.2 dB, e.g. NF result would be lower / better.

PCB Cross - Section Diagram

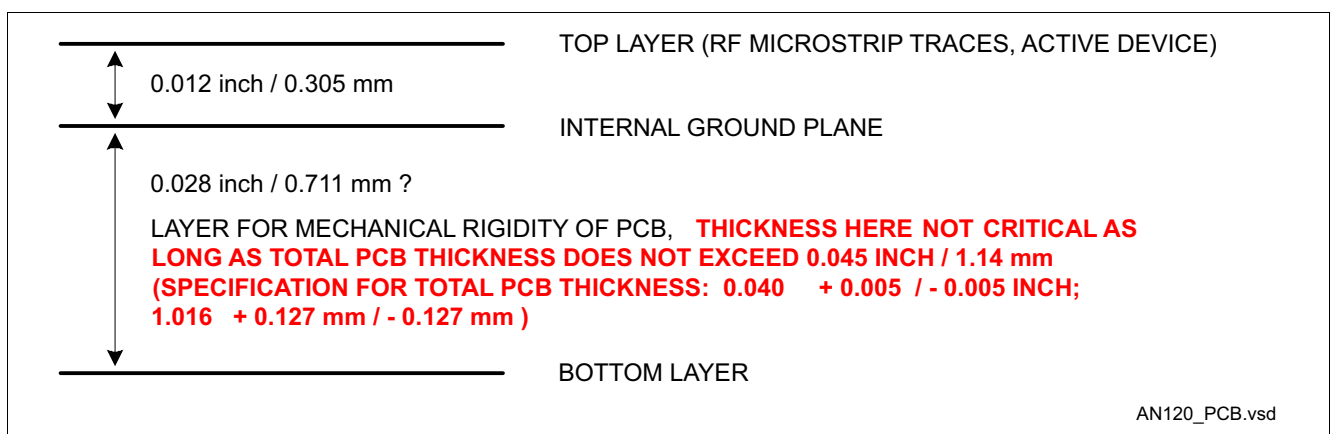


Figure 1 PCB - Cross Sectional Diagram

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

TSFP-4 package details (dimensions in millimeters)

Note maximum package height is 0.59 mm / 0.023 inch

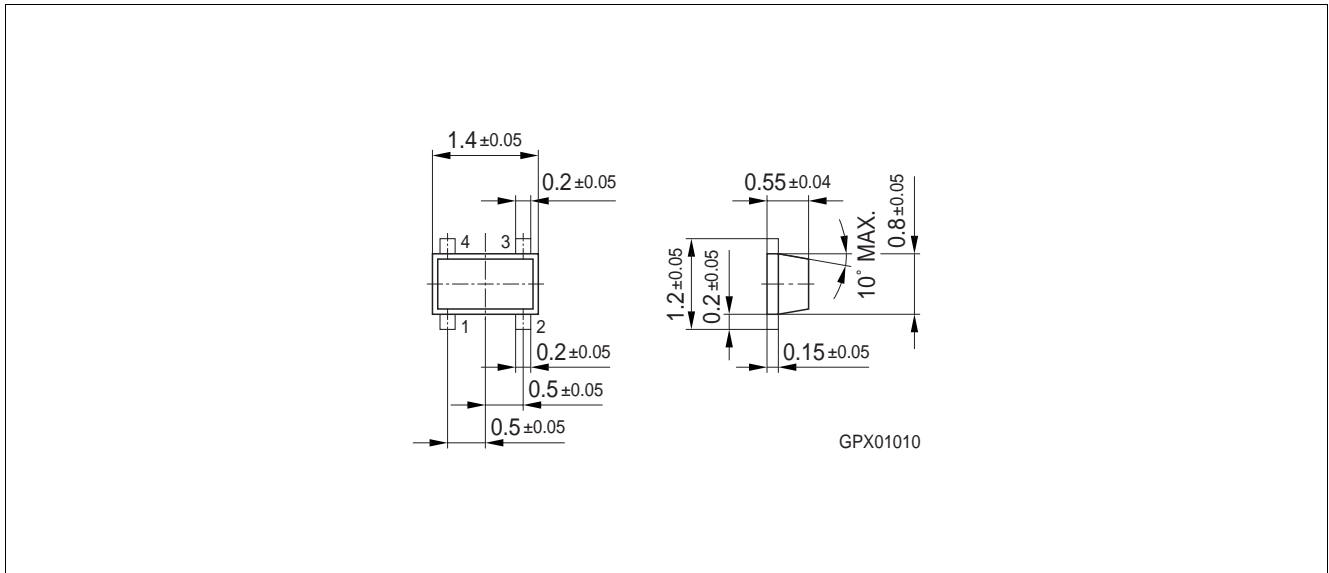


Figure 2 TSFP-4 package details

Recommended Soldering Footprint for TSFP-4 given below (dimensions in millimeters). Device package is to be oriented as shown in above drawing (e.g. orient long package dimension horizontally on this footprint).

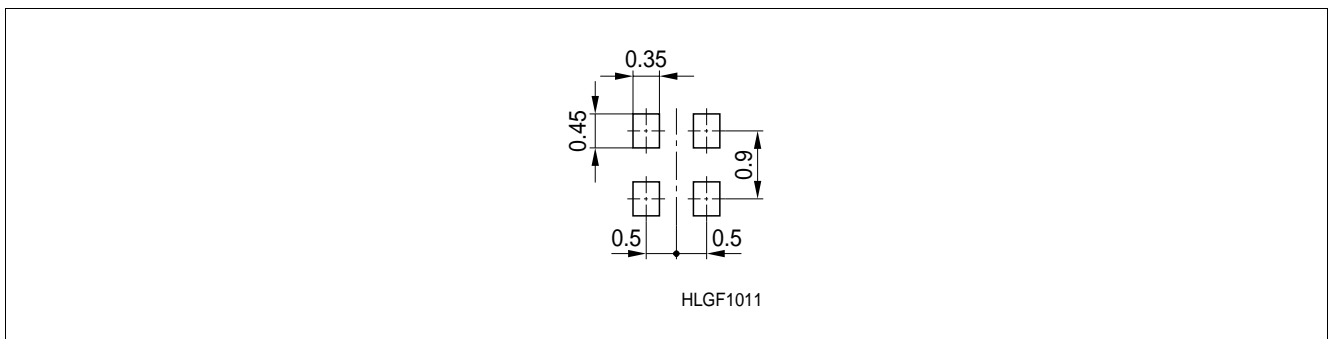


Figure 3 TSFP-4 package - Soldering Footprint

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Bill of Material

Table 2 Bill of Material

Reference Designator	Value	Manufacturer	Case Size	Function
C1	0.1 μ F	Various	0402	DC blocking, input. Also, using cap above self-resonant frequency makes it slightly inductive, slightly improving input match.
C2	2.7 pF	Various	0402	DC block, output. Also influences output and input impedance match.
C3	0.1 μ F	Various	0402	Decoupling, low frequency. Also improves Third-Order Intercept.
C4	3.3 pF	Various	0402	Decoupling at collector; also influence on stability and output match.
C5	0.1 μ F	Various	0402	Low frequency decoupling, slightly improves Third Order Intercept.
L1	9.1 nH	Murata LQP15M series chip inductor	0402	RF choke at input, also influences input impedance match
L2	4.7 nH	Murata LQP15M series chip inductor	0402	RF choke + impedance match at output
R1	10 Ω	Various	0402	Improves low frequency stability e.g. $K > 1$
R2	22 k Ω	Various	0402	Brings bias current / voltage into base of transistor.
R3	30 Ω	Various	0402	Provides some negative feedback for DC bias / DC operating point to compensate for variations in transistor DC current gain, temperature variations, etc.
Q1	-	Infineon Technologies	TSFP-4	BFP740F B7HFe SiGe:C Ultra-Low Noise HBT Transistor
J1, J2	-	Johnson 142-0701-841	-	RF input / output connectors
J3	-	Amp 5 pin header MTA-100 series 640456-5 (standard pin plating) or 641215-5 (gold plated pins)	-	DC connector Pins 1, 5 = Ground Pin 3 = V_{CC} Pins 2, 4 = no connection

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Schematic Diagram for 1575 MHz GPS LNA

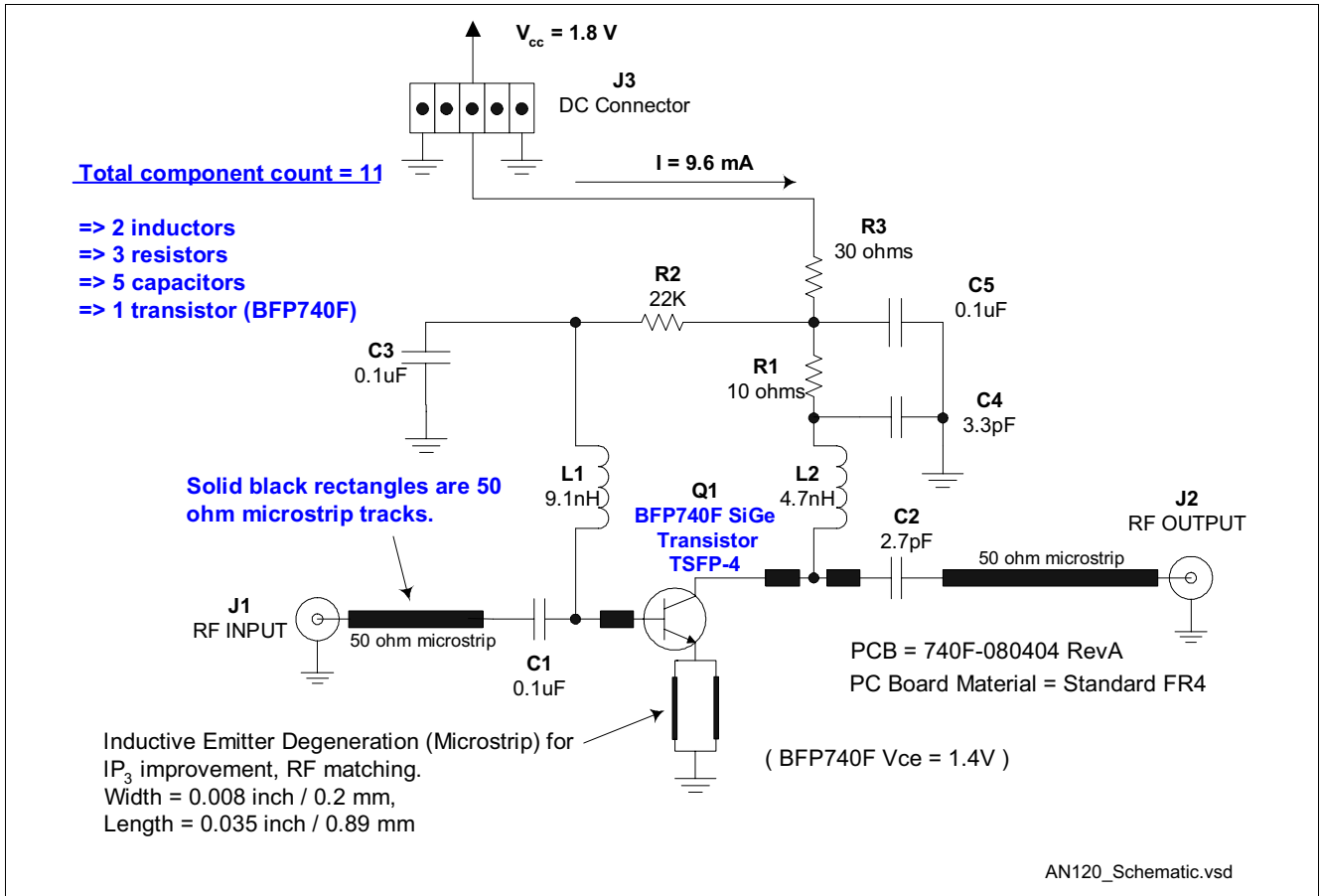


Figure 4 Schematic Diagram

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Noise Figure, Plot, Center of Plot (x-axis) is 1575 MHz.

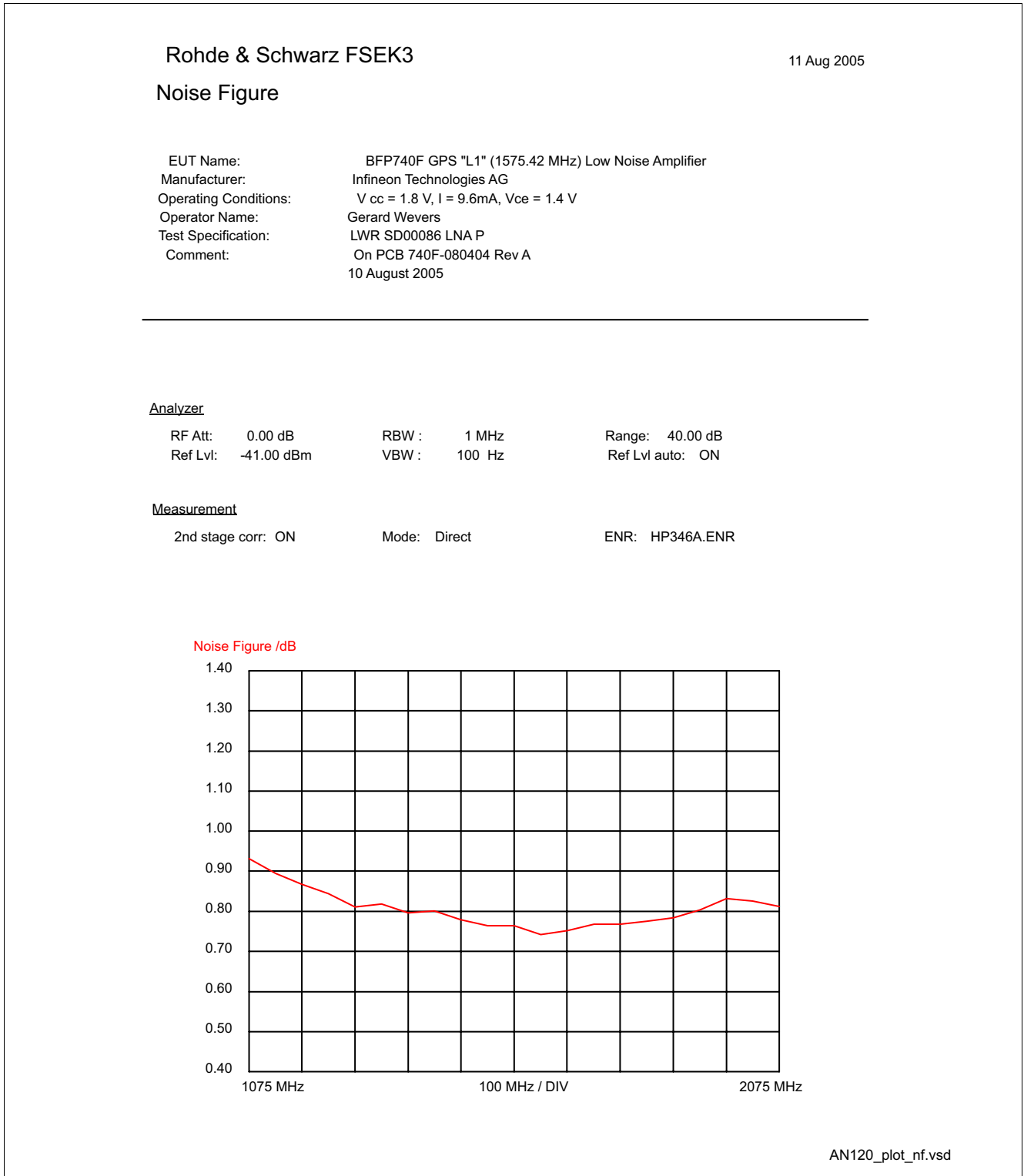


Figure 5 Noise Figure

 1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Noise Figure, Tabular Data

From Rhode & Schwarz FSEK3 + FSEM30 + System Preamplifier

Table 3 Noise Figure

Frequency	Noise Figure
1075 MHz	0.93 dB
1125 MHz	0.89 dB
1175 MHz	0.87 dB
1225 MHz	0.84 dB
1275 MHz	0.81 dB
1325 MHz	0.82 dB
1375 MHz	0.80 dB
1425 MHz	0.80 dB
1475 MHz	0.78 dB
1525 MHz	0.76 dB
1575 MHz	0.76 dB
1625 MHz	0.74 dB
1675 MHz	0.75 dB
1725 MHz	0.77 dB
1775 MHz	0.77 dB
1825 MHz	0.78 dB
1875 MHz	0.78 dB
1925 MHz	0.80 dB
1975 MHz	0.83 dB
2025 MHz	0.83 dB
2075 MHz	0.81 dB

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Scanned Image of PC Board

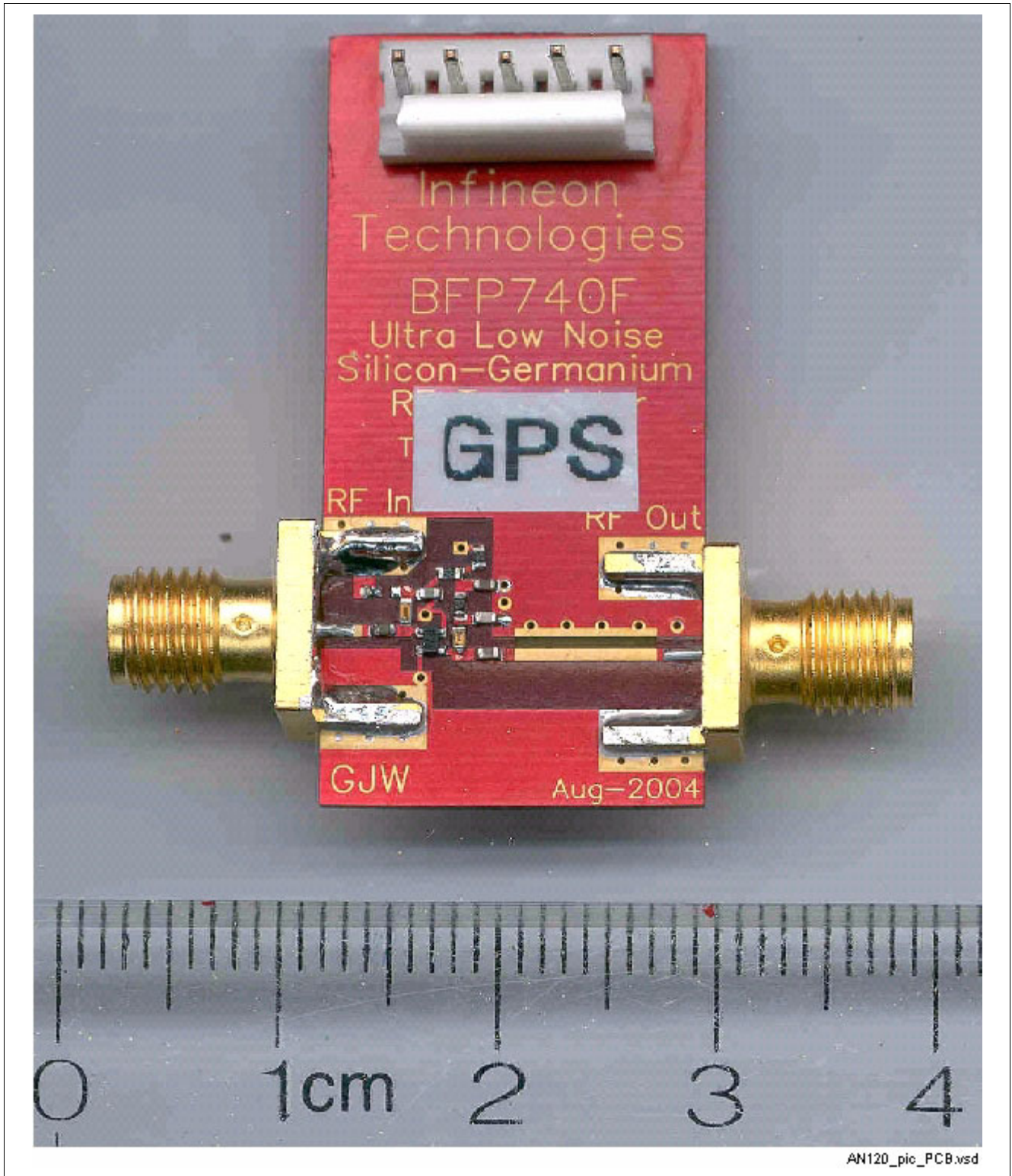


Figure 6 Image of PC Board

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Scanned Image of PC Board, Close-In Shot

Total PCB area used is approximately 40 mm²

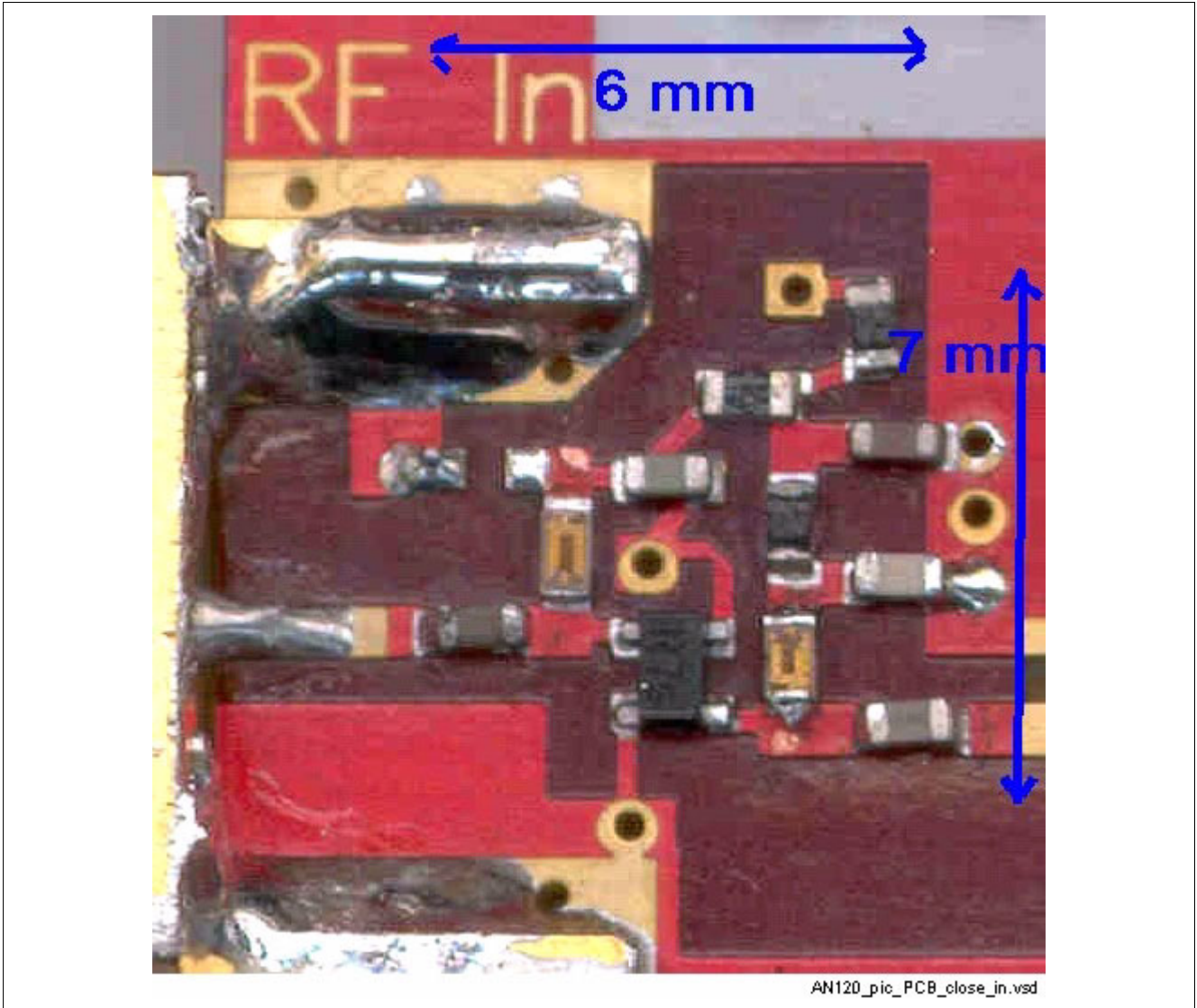


Figure 7 Image of PC Board, Close-In Shot

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Amplifier Stability

$T = 25\text{ }^{\circ}\text{C}$, $V_{CC} = 1.8\text{ V}$, $V_{CE} = 1.4\text{ V}$, $I = 9.6\text{ mA}$

Stability Factor "K" is shown below from "screen shot" taken from Rohde and Schwarz ZVC network analyzer. ZVC Vector Network Analyzer calculates and plots K in real time, from measured S parameters. Note that minimum K value is 0.974 at 1.1 GHz, which is ≈ 1 , for practical purposes; the amplifier is unconditionally stable over 5 MHz to 8 GHz range.

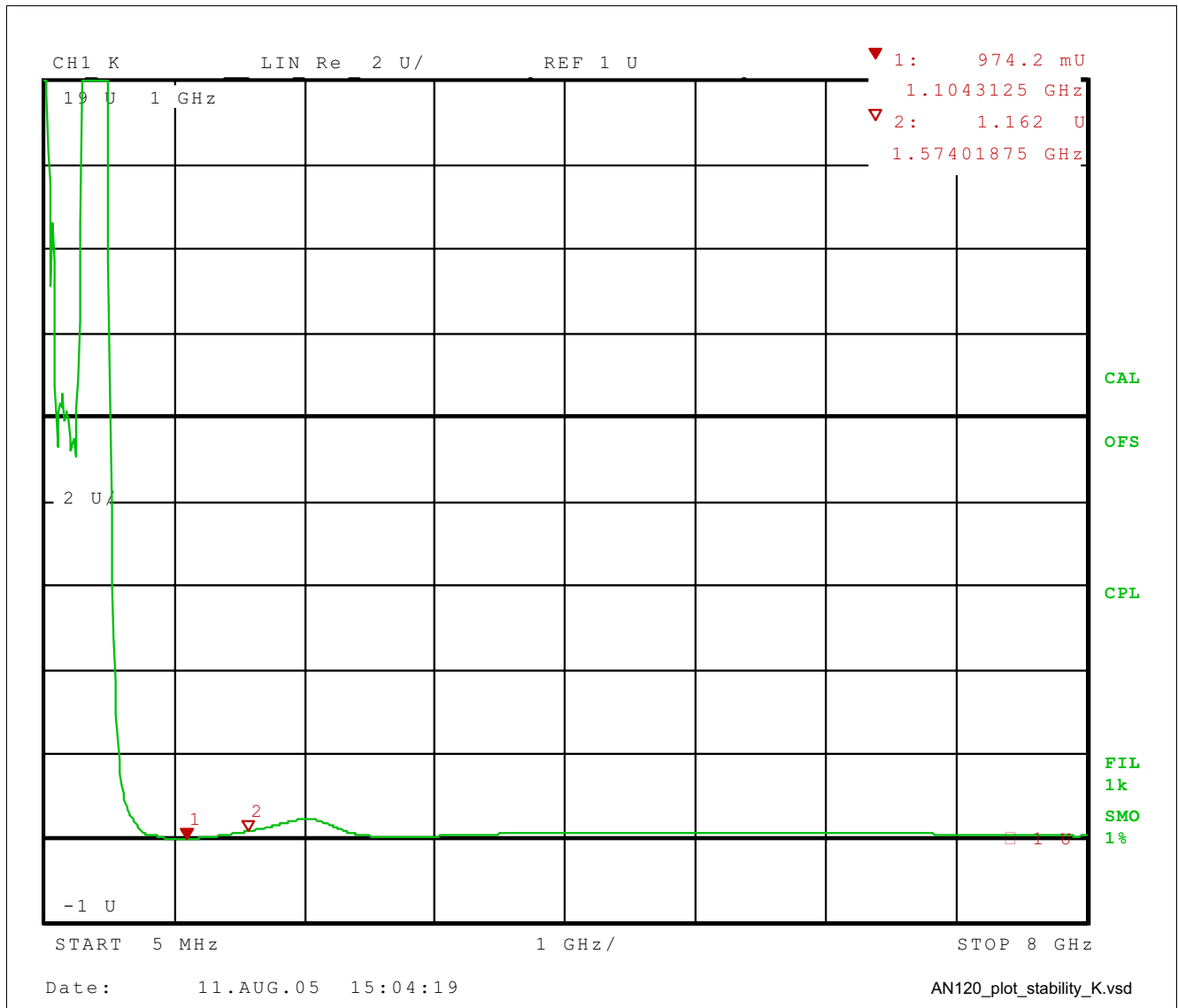


Figure 8 Plot of Stability K(f)

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Gain Compression at 1575 MHz

$T = 25\text{ }^{\circ}\text{C}$, $V_{CC} = 1.8\text{ V}$, $V_{CE} = 1.4\text{ V}$, $I = 9.6\text{ mA}$

Amplifier is checked for 1 dB compression point. An Agilent power meter was used to ensure accurate power levels are measured (as opposed to using Vector Network Analyzer in "Power Sweep" mode).

Output $P_{1dB} \cong +1.4\text{ dBm}$; Input $P_{1dB} = +1.4\text{ dBm} - (\text{Gain} - 1\text{ dB}) = +1.4\text{ dBm} - 18.7\text{ dB} = -17.3\text{ dBm}$

Table 4 Gain Compression (1575 MHz)

P_{OUT} , dBm	Gain, dBm
-10.0	19.7
-9.0	19.7
-8.0	19.7
-7.0	19.6
-6.0	19.6
-5.0	19.6
-4.0	19.6
-3.0	19.5
-2.0	19.4
-1.0	19.3
0.0	19.2
+1.0	18.9
+2.0	18.5
+3.0	17.6

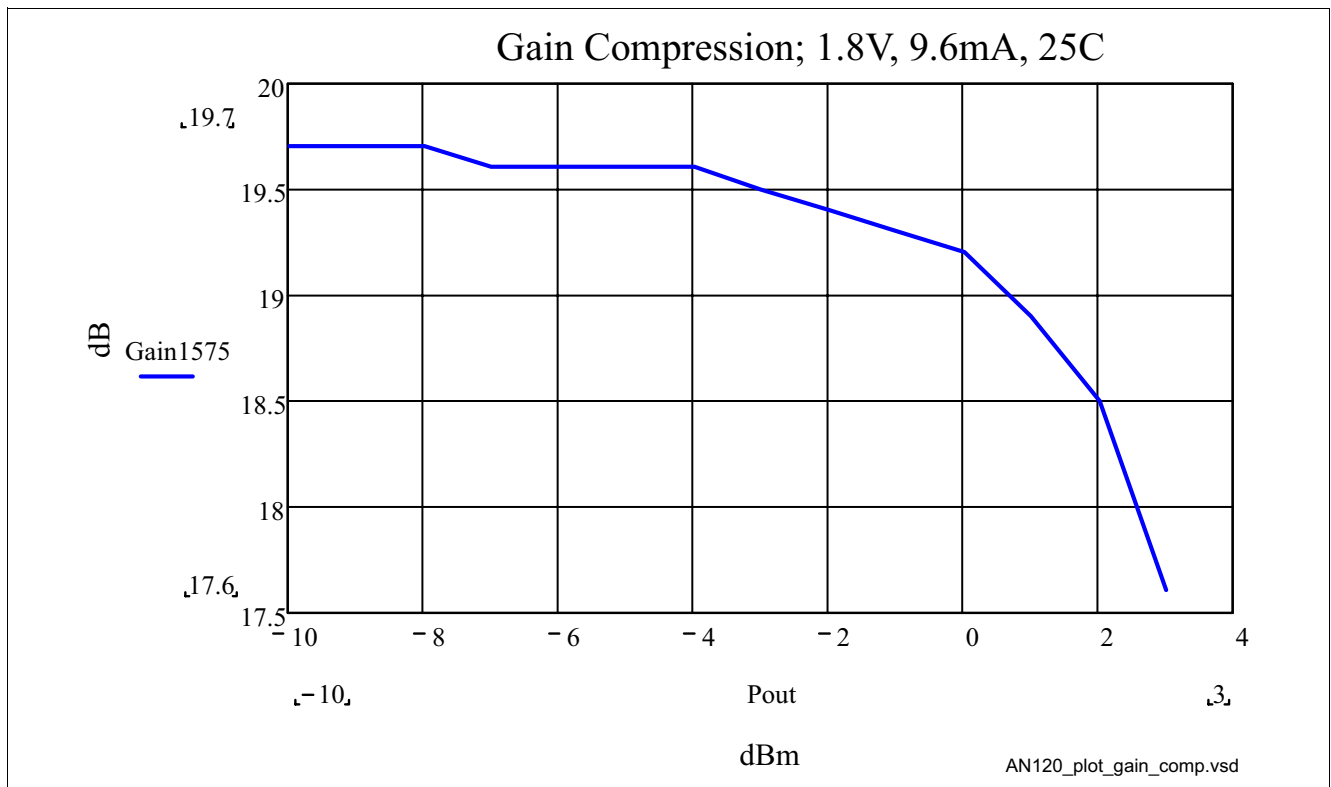


Figure 9 Plot of Gain Compression @ 1575 MHz

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Please Note - all plots are taken from Rhode and Schwarz ZVC Network Analyzer, $T = 25\text{ }^{\circ}\text{C}$, source power $\approx -30\text{ dBm}$

Input Return Loss, Log Mag

5 MHz to 8 GHz Sweep

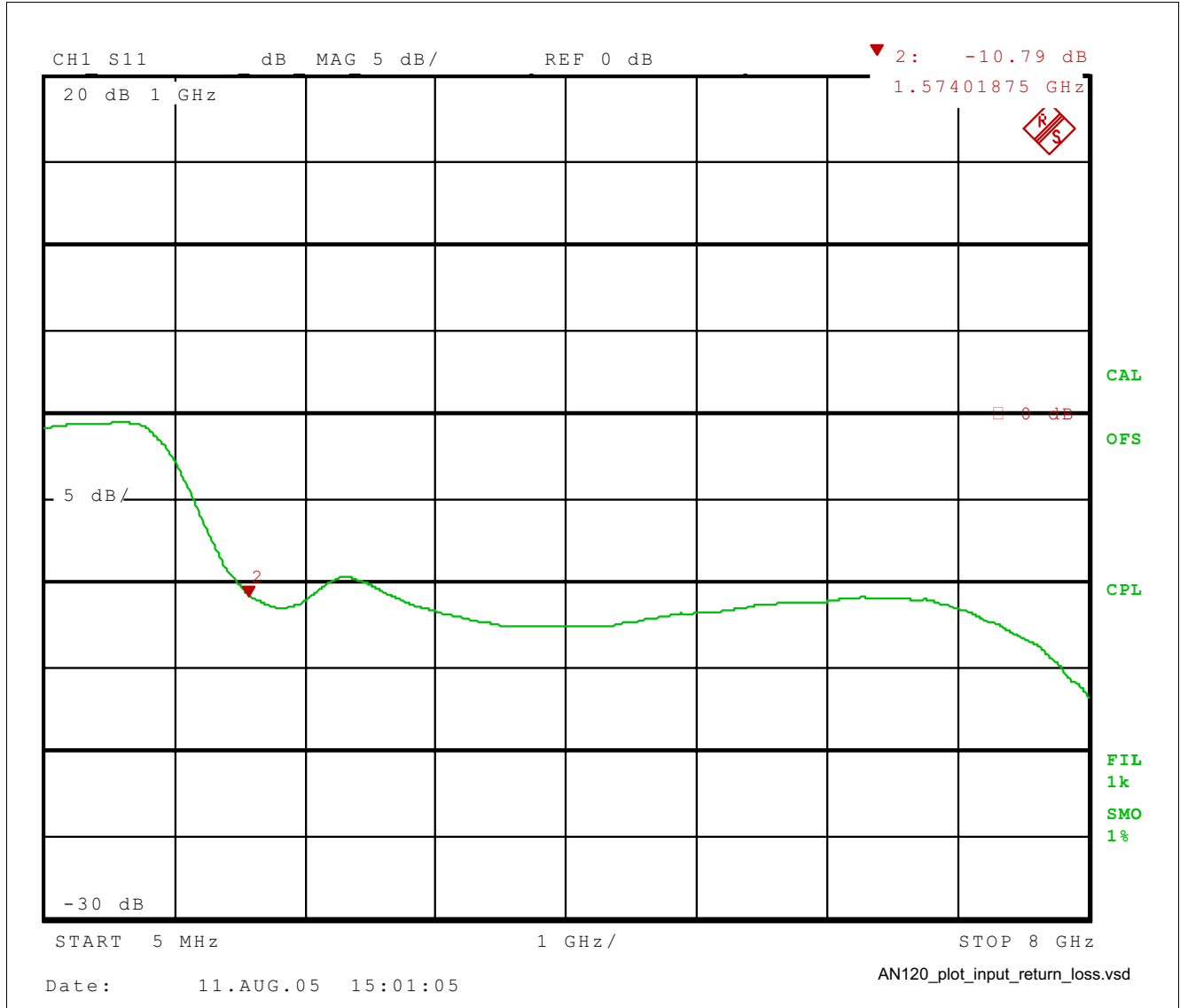


Figure 10 Plot of Input Return Loss

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Input Return Loss, Smith Chart

Reference Plane = Input SMA Connector on PC Board
 5 MHz to 8 GHz Sweep

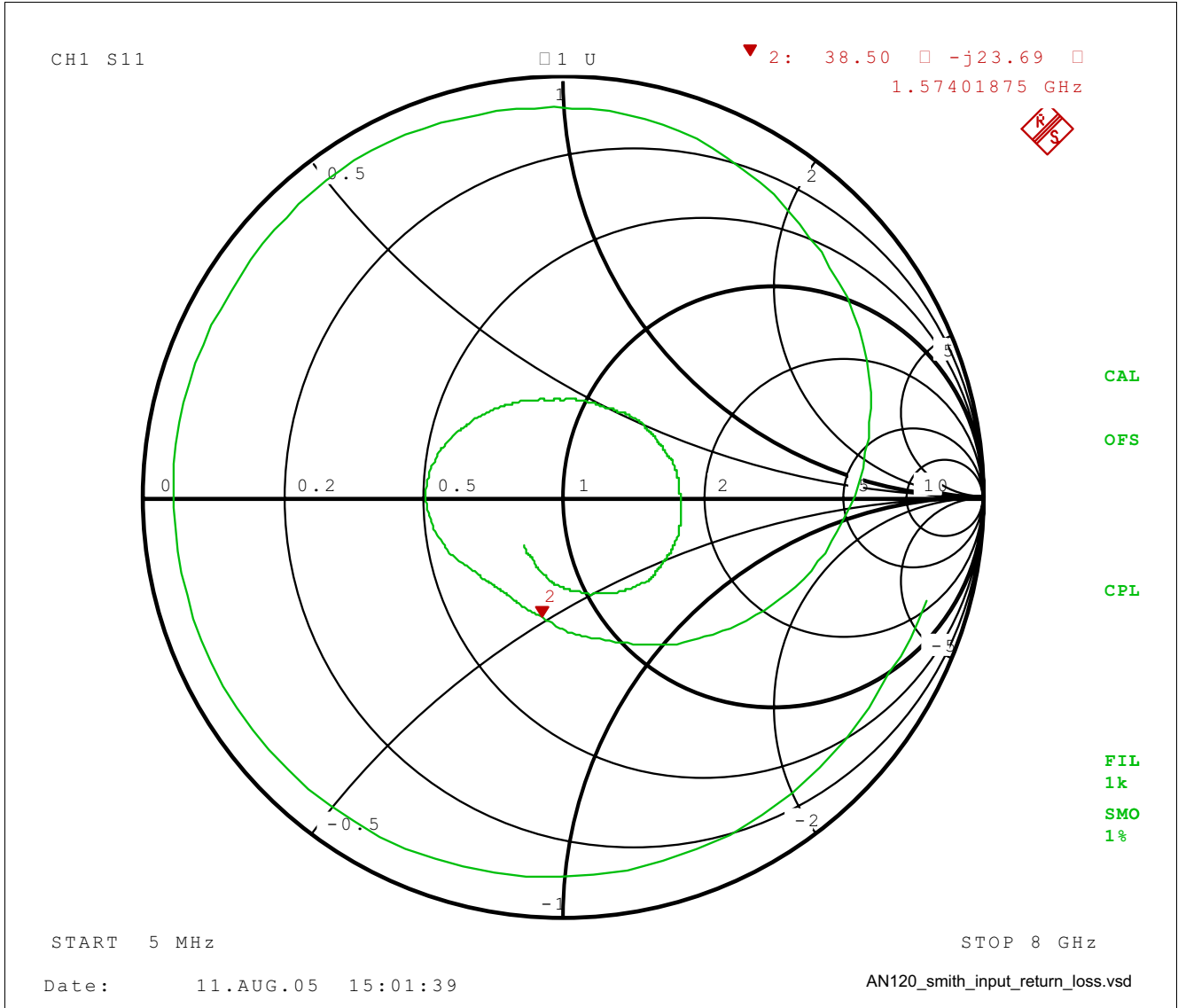


Figure 11 Smith Chart of Input Return Loss

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Forward Gain

5 MHz to 8 GHz Sweep

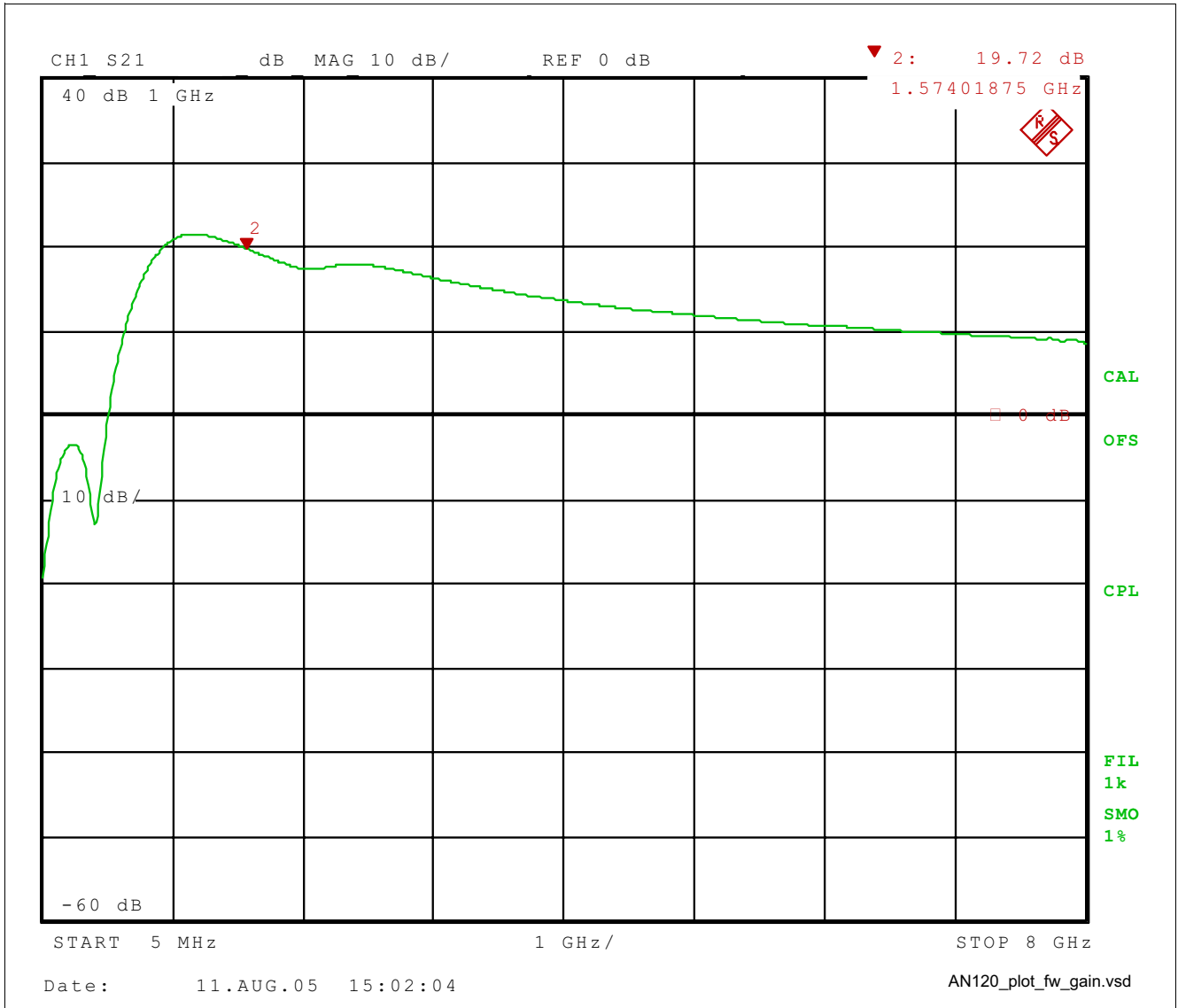


Figure 12 Plot of Forward Gain

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Reverse Isolation

5 MHz to 8 GHz

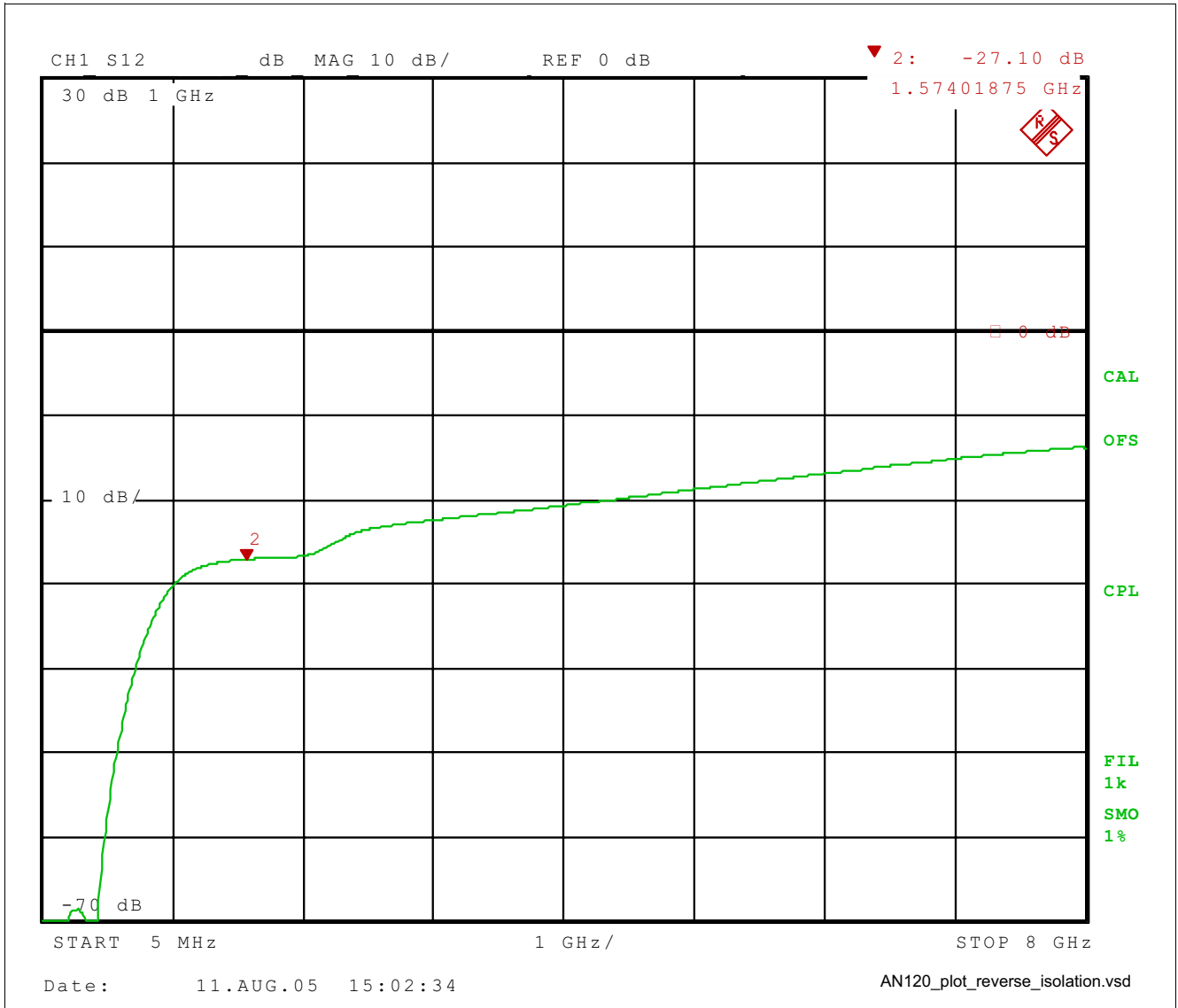


Figure 13 Plot of Reverse Isolation

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Output Return Loss, Log Mag

5 MHz to 8 GHz

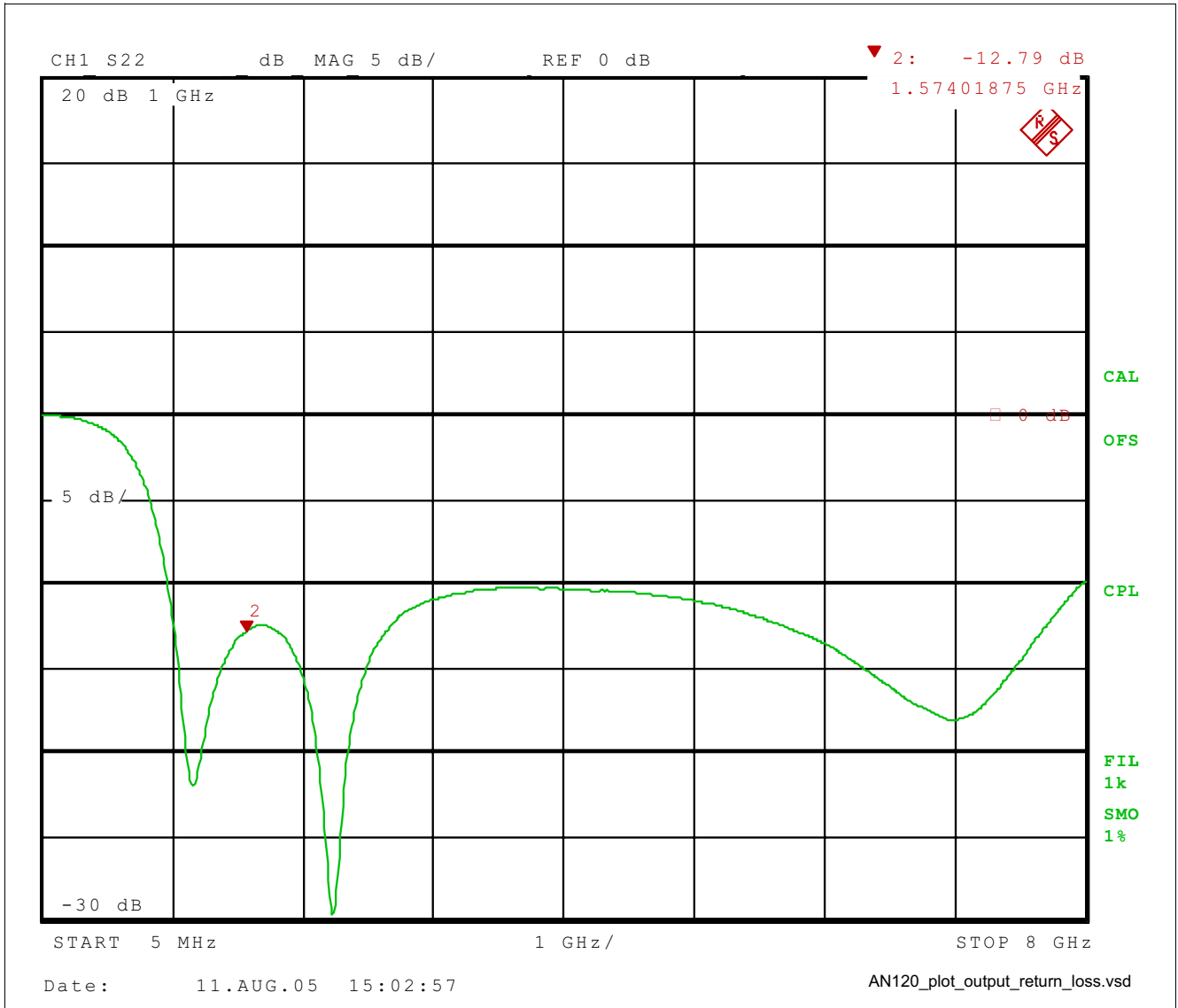


Figure 14 Plot of Output Return Loss

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

Output Return Loss, Smith Chart

Reference Plane = Output SMA Connector on PC Board
5 MHz to 8 GHz Sweep

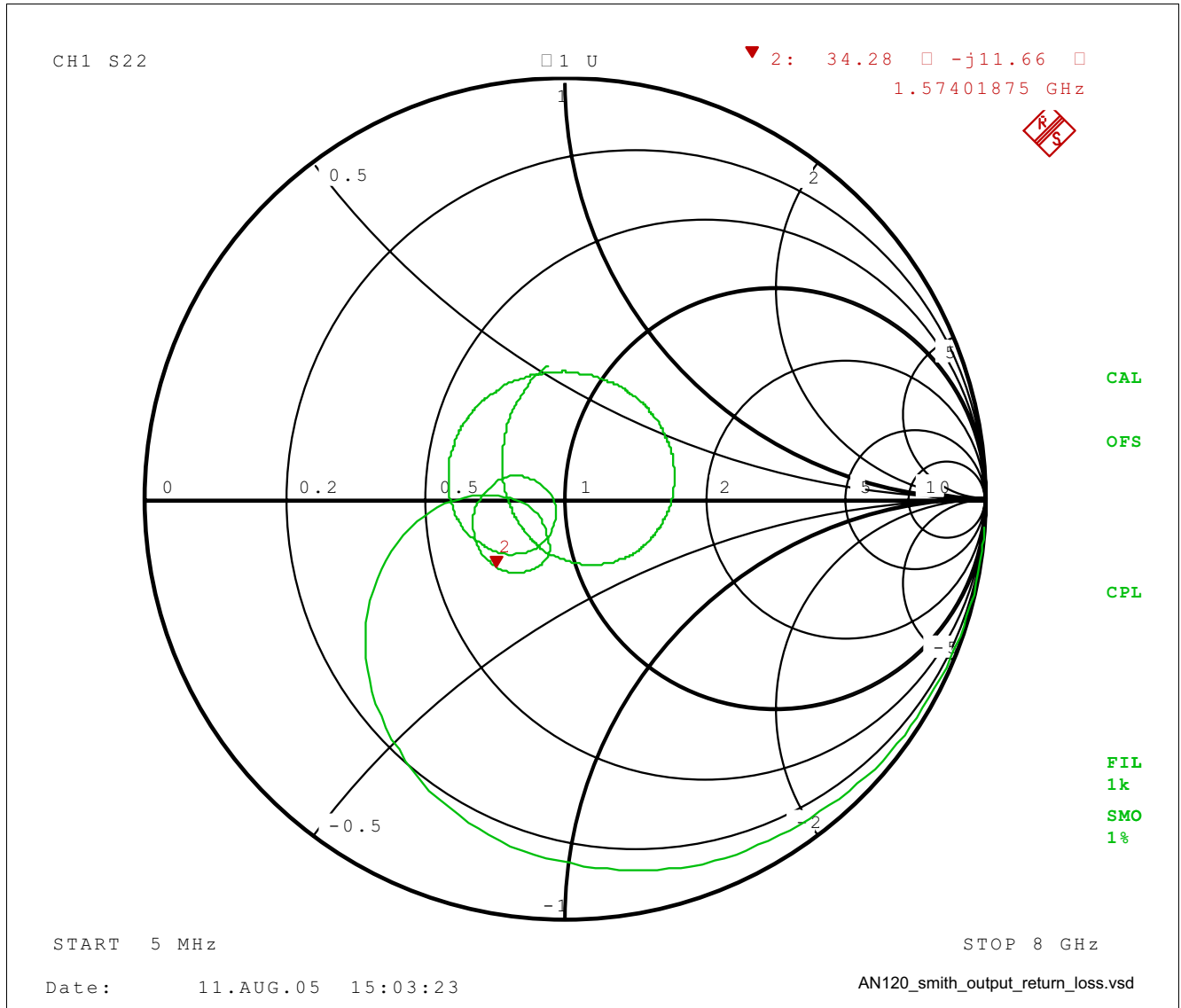


Figure 15 Smith Chart of Output Return Loss

1.8 V Low Noise Amplifier for 1575 MHz GPS Applications using the SiGe:C

LNA Response to Two-Tone Test

Input Stimulus: $f_1 = 1574$ MHz, $f_2 = 1575$ MHz, -25 dBm each tone.

Input $IP_3 = -25 + (50.3/2) = +0.2$ dBm

Output $IP_3 = +0.2$ dBm + 19.7 dB gain = +19.9 dBm

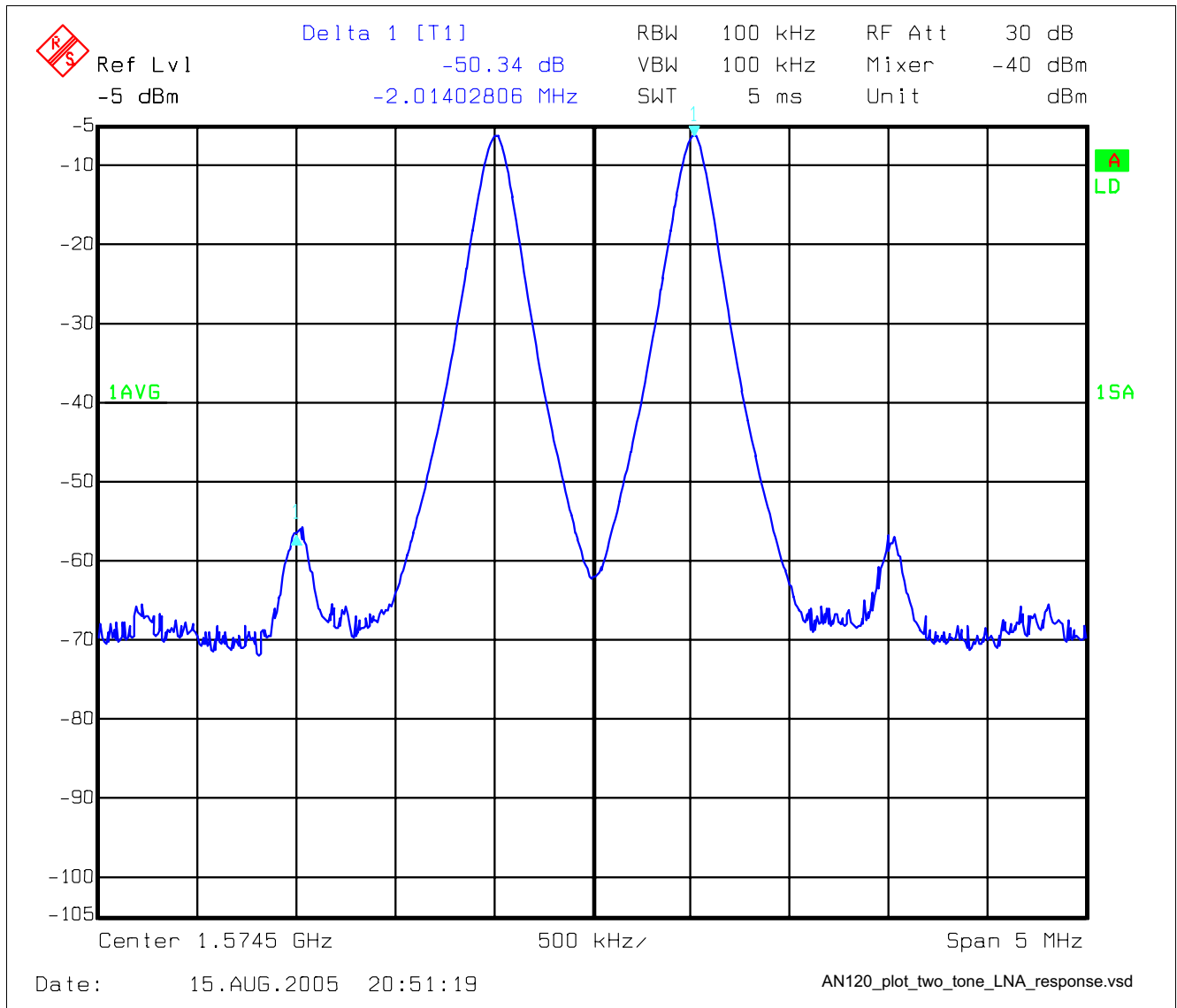


Figure 16 Two-Tone Test, LNA Response (1575 MHz)