

Application Note No. 138

Dual-Band (L1 + L2) GPS Low Noise Amplifier
using the SiGe BFP640 HBT RF Transistor

RF & Protection Devices



Never stop thinking

Edition 2008-01-10

**Published by
Infineon Technologies AG
81726 München, Germany**

**© Infineon Technologies AG 2009.
All Rights Reserved.**

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Application Note No. 138

Revision History: 2008-01-10, Rev. 1.2

Previous Version: 2005-08-09, Rev. 1.1

Page	Subjects (major changes since last revision)
All	Small changes in figure descriptions

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

1 Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF Transistor

Applications

- GPS Low Noise Amplifiers (LNAs) for 3 V systems, where reception of both L1 (1575.42 MHz) and L2 (1227.6 MHz) GPS signals is required.

Overview

The Infineon BFP640 SiGe Heterojunction Bipolar Transistor in SOT343 package is shown in a low-cost LNA circuit suitable for dual band GPS applications operating from a 3 V power supply. PC board is fabricated from standard, low-cost, commercial grade glass-epoxy material ("FR4"). 0402 case-size passive components are used.

Target Specifications

Gain @ 1227.6 MHz => >18 dB; Gain @ 1575.42 MHz => > 17 dB; $OP_{1dB} > +3$ dBm; Noise Figure (NF) < 3 dB; $V_{CC} = 3.0$ Volts, $I < 15$ mA.

Remarks

($T = 25$ °C)

- Amplifier is unconditionally stable from 5 MHz - 8 GHz ($K > 1$). See plot on Page 7
- 19.9 dB gain at 1227.6 MHz, 18.5 dB gain at 1575.42 MHz
- Noise Figure = 1.1 dB for both L1 and L2 frequencies¹⁾
- 9.1 mA current consumption at 3.0 V
- Output P_{1dB} meets target at 1575 MHz, but is slightly low at 1227 MHz. OP_{1dB} can be improved by increasing current; do this by reducing value of resistor R2 (see [Figure 2](#))

Summary of Results

Table 1 Summary of Results, $T = 25$ °C

Frequency (MHz)	dB[s11] ²	dB[s21] ²	dB[s12] ²	dB[s22] ²	NF ¹⁾ dB	IIP_3 dBm	OIP_3 dBm	IP_{1dB} dBm	OP_{1dB} dBm
1227.6	11.3	19.9	27.6	18.9	1.1	---	---	-17.6	+1.3
1575.4	17.2	18.5	25.6	11.3	1.1	+5.7	+24.2	-14.4	+3.1

Cross Sectional Diagram of PC Board

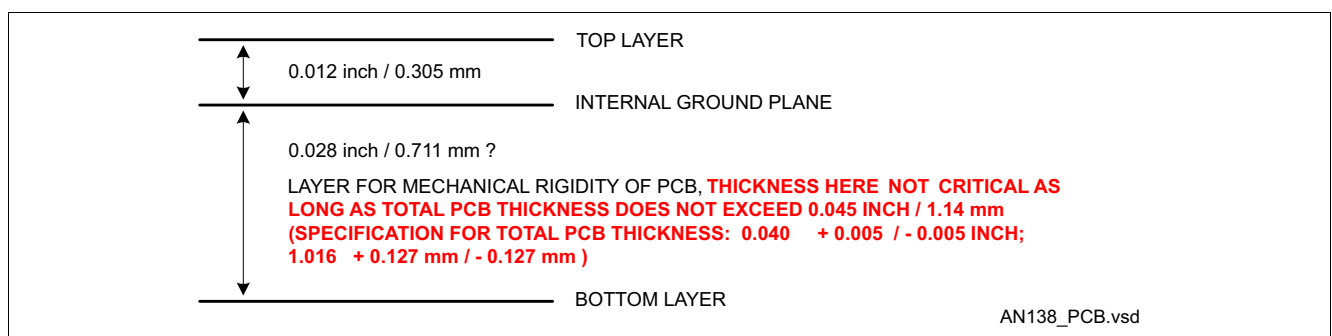


Figure 1 PCB - Cross Sectional Diagram

1) Note that PCB loss is not extracted. If PCB loss were extracted, NF would be 0.1 to 0.2 dB lower

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Schematic Diagram

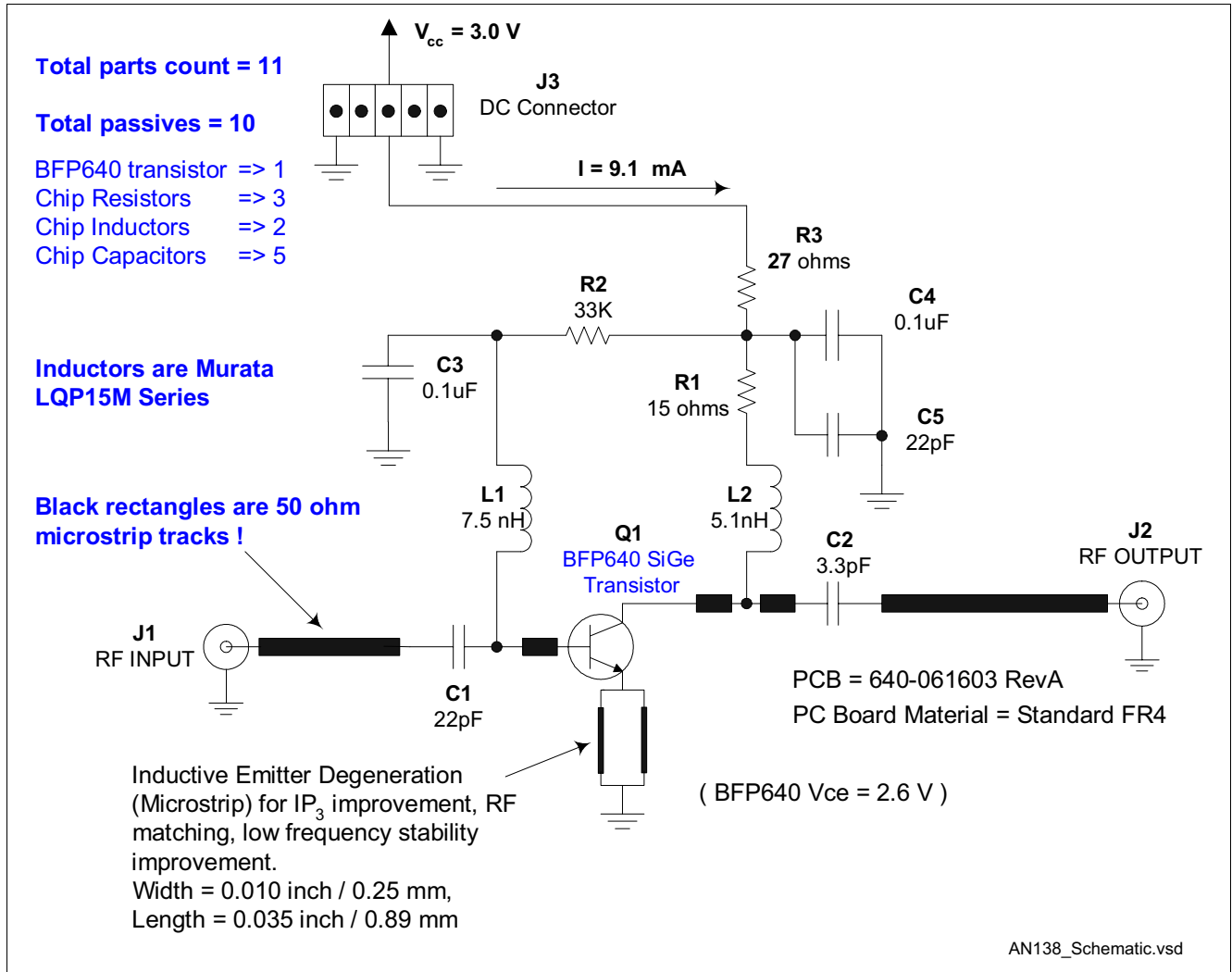


Figure 2 Schematic Diagram

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Noise Figure, Plot, 1100 MHz to 1700 MHz, Center of Plot (x-axis) is 1400 MHz.

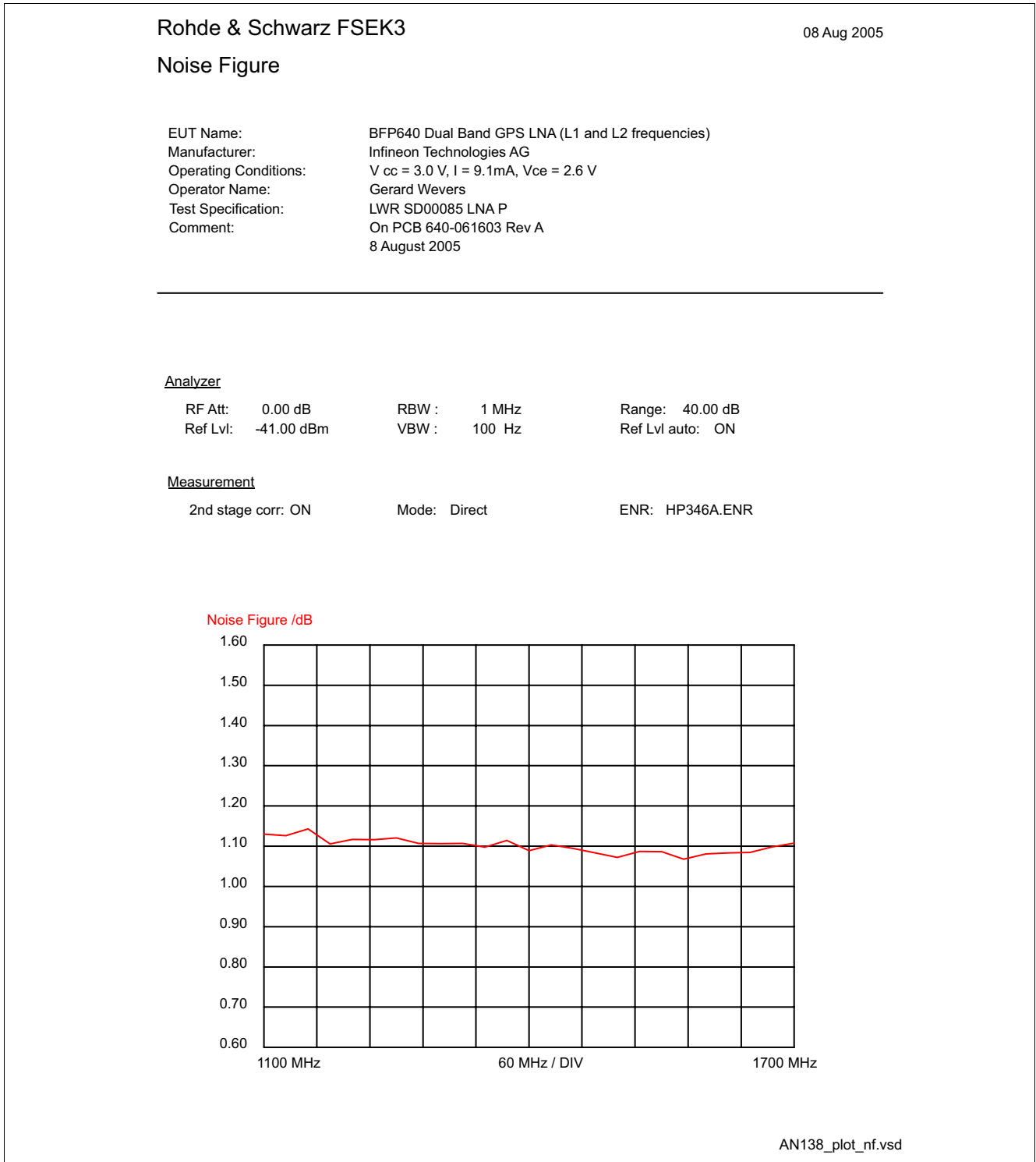


Figure 3 Noise Figure

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Noise Figure, Tabular Data

From Rohde & Schwarz FSEK3 + FSEB30
System Preamplifier = MITEQ SMC-02

Table 2 Noise Figure

Frequency	Noise Figure
1100 MHz	1.13 dB
1125 MHz	1.13 dB
1150 MHz	1.14 dB
1175 MHz	1.11 dB
1200 MHz	1.12 dB
1225 MHz	1.12 dB
1250 MHz	1.12 dB
1275 MHz	1.11 dB
1300 MHz	1.11 dB
1325 MHz	1.11 dB
1350 MHz	1.10 dB
1375 MHz	1.11 dB
1400 MHz	1.09 dB
1425 MHz	1.10 dB
1450 MHz	1.09 dB
1475 MHz	1.08 dB
1500 MHz	1.07 dB
1525 MHz	1.09 dB
1550 MHz	1.09 dB
1575 MHz	1.07 dB
1600 MHz	1.08 dB
1625 MHz	1.08 dB
1650 MHz	1.08 dB
1675 MHz	1.10 dB
1700 MHz	1.11 dB

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Scanned Image of PC Board

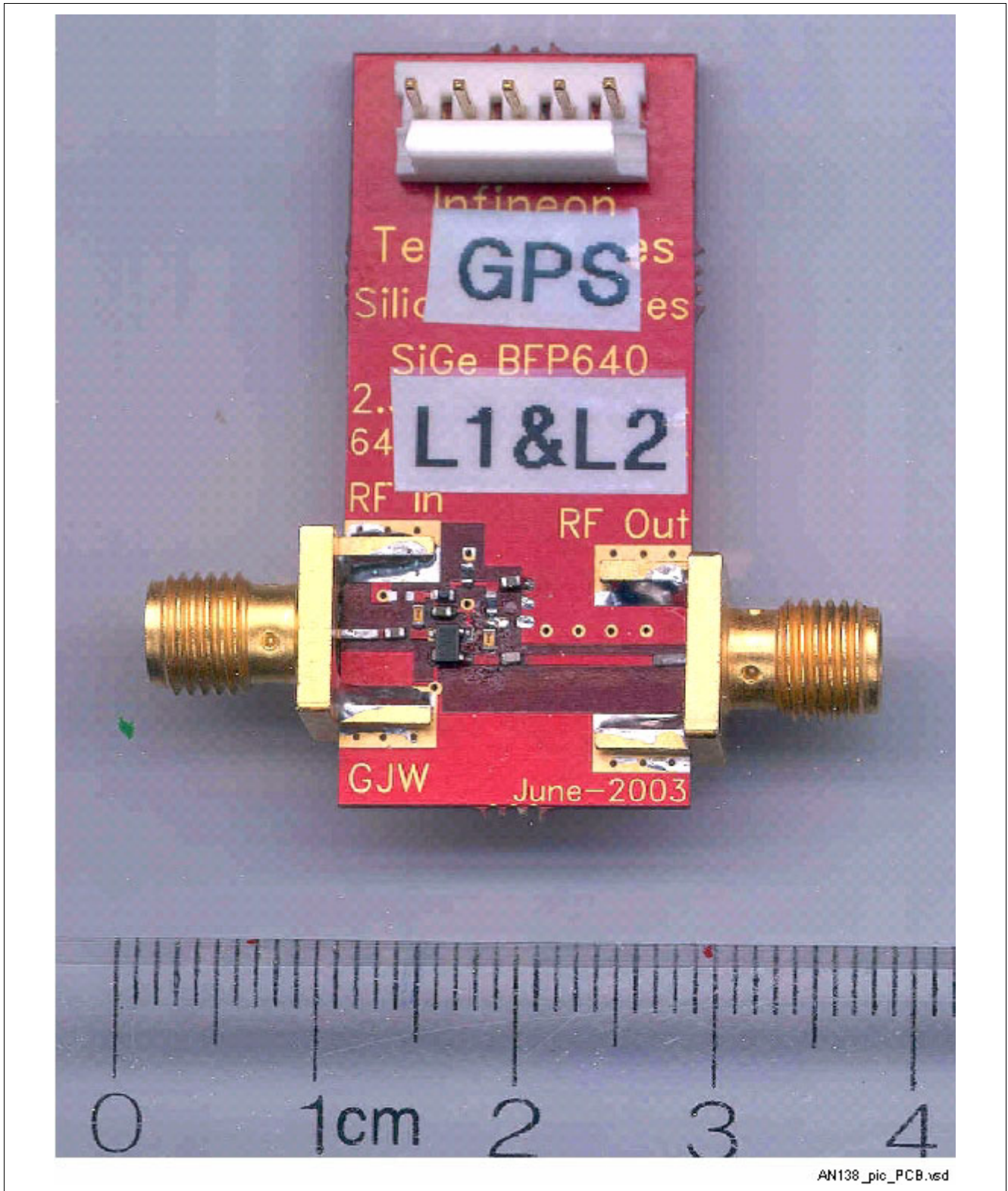


Figure 4 Image of PC Board

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Scanned Image of PC Board, Close-In Shot.

Total PCB area used $\cong 50 \text{ mm}^2$

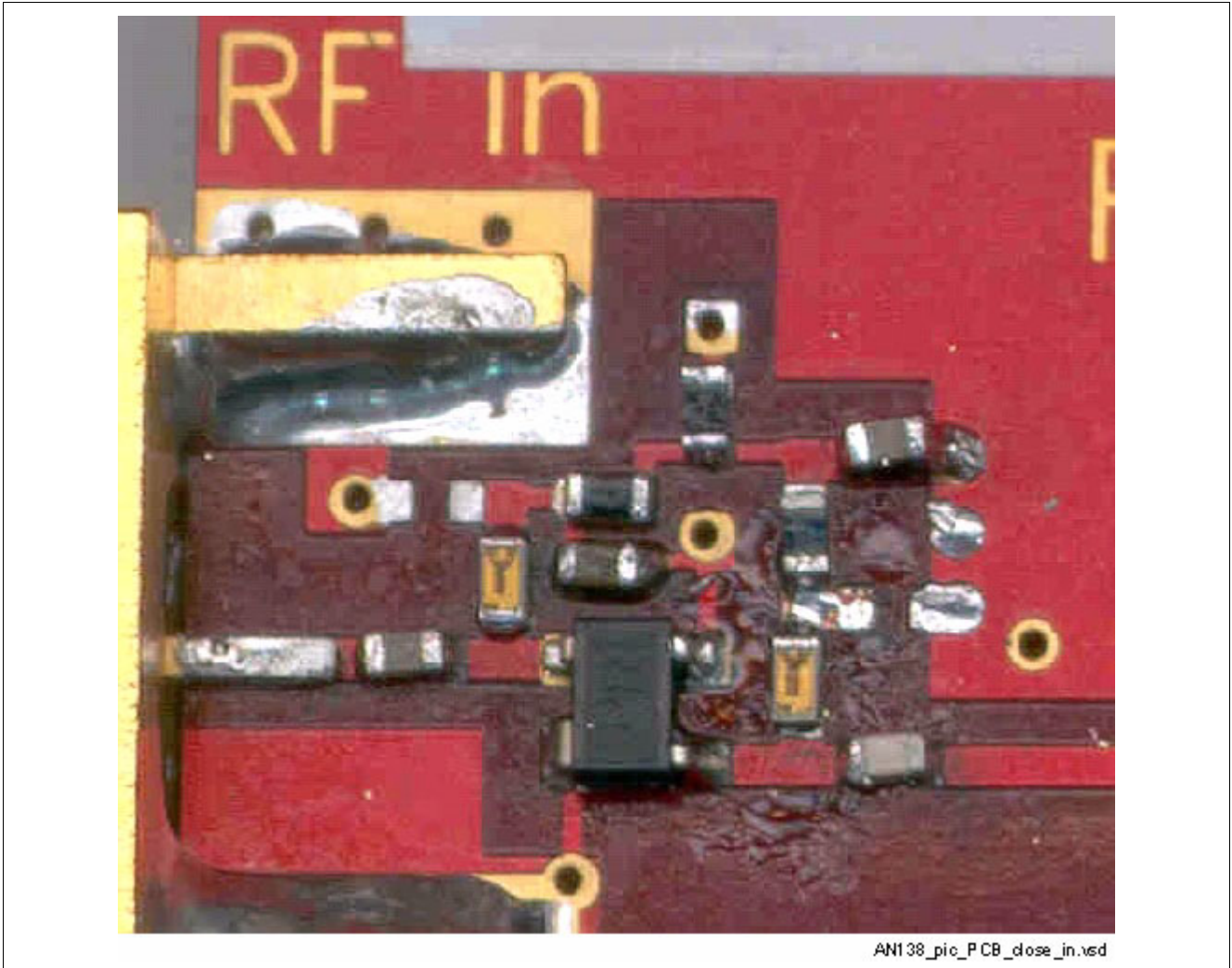


Figure 5 Image of PC Board, Close-In Shot

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Stability

Rohde and Schwarz ZVC Network Analyzer calculates and plots Stability Factor "K" in real time, from 5 MHz to 8 GHz. Note $K > 1$ from 5 MHz to 8 GHz; minimum K value is approximately 1.1 at ≈ 6.6 GHz. Amplifier is Unconditionally Stable over 5 MHz - 8 GHz frequency range.

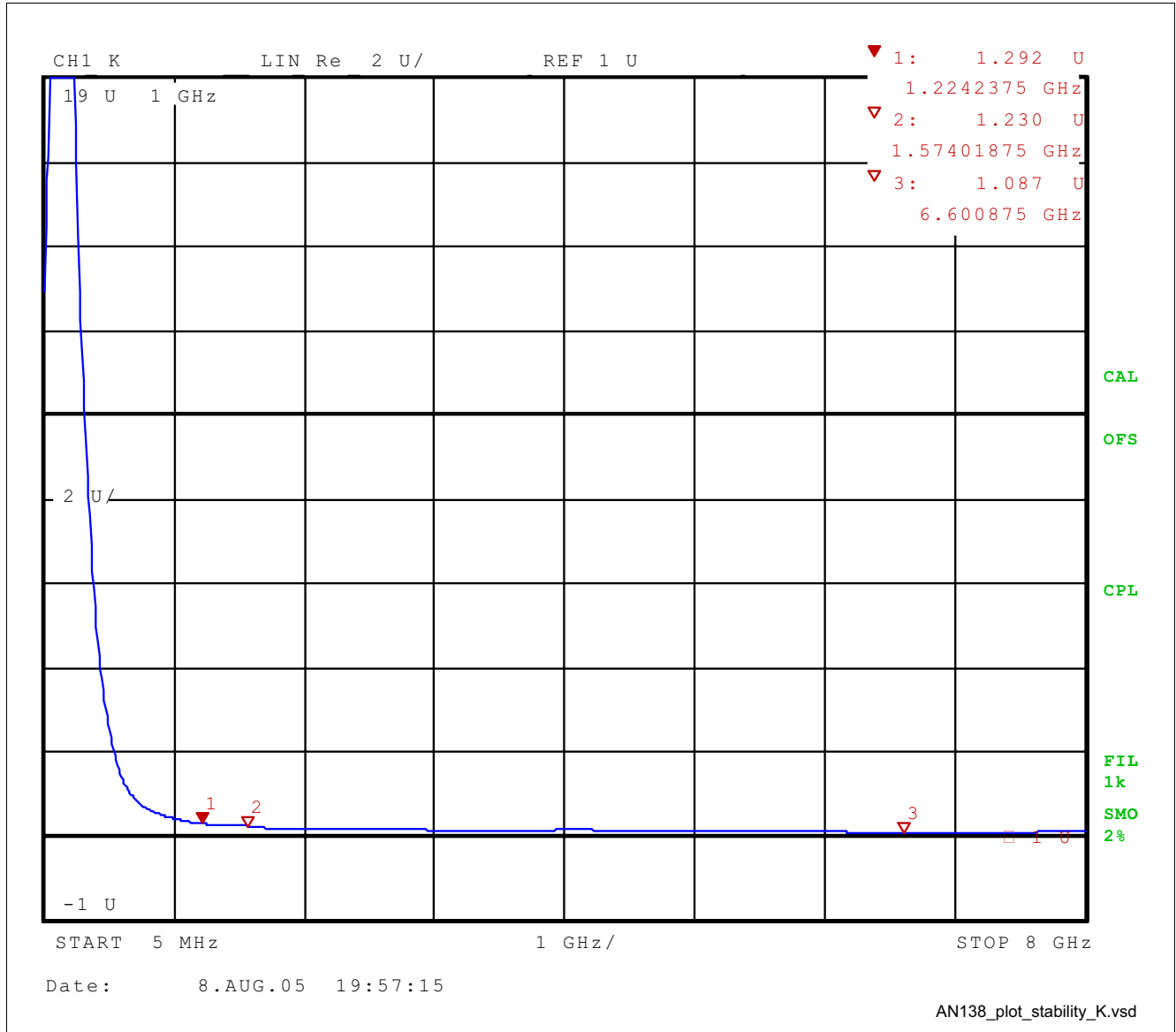


Figure 6 Plot of K(f)

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Gain Compression at 1227 MHz and 1575 MHz

Amplifier is checked for output 1 dB compression point at $V_{CC} = 3\text{ V}$, $I = 9.1\text{ mA}$ (with $V_{CE} = 2.6\text{ V}$). An Agilent power meter was used to ensure accurate power levels are measured (as opposed to using Vector Network Analyzer in "Power Sweep" mode).

1227 MHz:


Output $P_{1dB} \cong +1.3\text{ dBm}$; Input $P_{1dB} = +1.3\text{ dBm} - (\text{Gain} - 1\text{ dB}) = +1.3\text{ dBm} - 18.9\text{ dB} = -17.6\text{ dBm}$

1575 MHz:

Output $P_{1dB} \cong +3.1\text{ dBm}$; Input $P_{1dB} = +3.1\text{ dBm} - (\text{Gain} - 1\text{ dB}) = +1.3\text{ dBm} - 17.5\text{ dB} = -14.4\text{ dBm}$

Table 3 Gain Compression

P_{OUT} , dBm	Gain @ 1227 MHz, dB	Gain @ 1575 MHz, dB
-10.0	19.9	18.5
-9.0	19.9	18.5
-8.0	19.9	18.5
-7.0	19.8	18.5
-6.0	19.8	18.4
-5.0	19.8	18.4
-4.0	19.7	18.4
-3.0	19.7	18.4
-2.0	19.6	18.3
-1.0	19.5	18.3
0.0	19.4	18.2
+1.0	19.1	18.1
+2.0	18.6	17.9
+3.0	17.7	17.5
+4.0	16.3	16.7

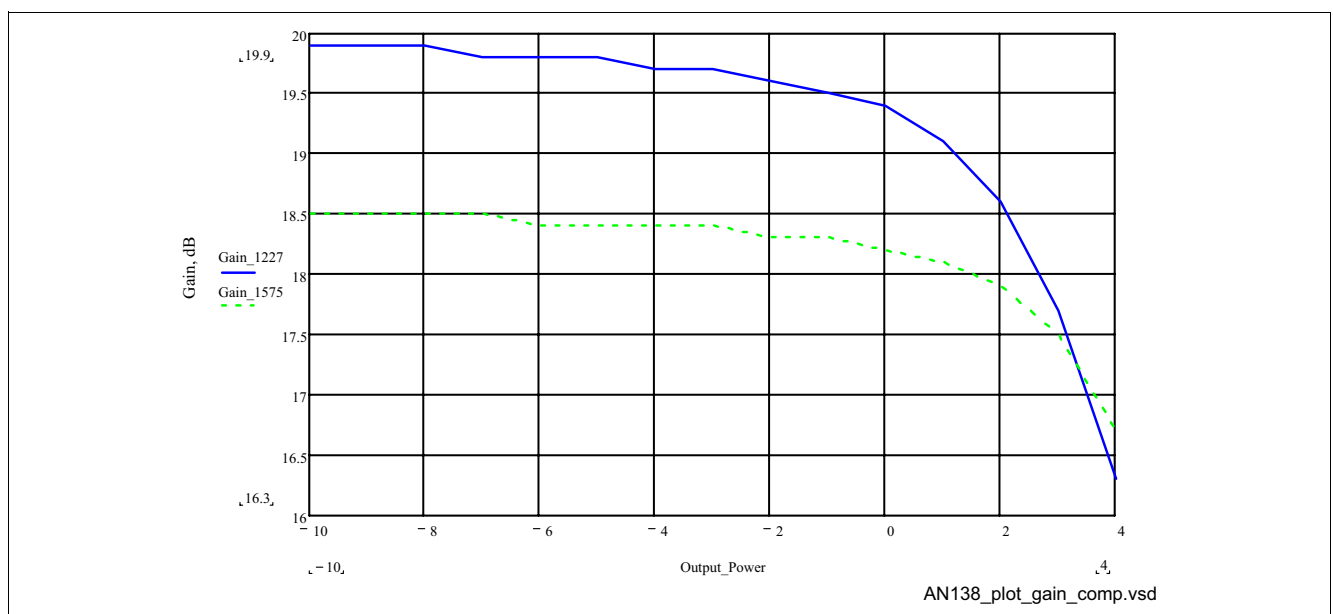
Figure 7 Plot of Gain Compression, Output Power in dB

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Please Note - all plots are taken from Rohde and Schwarz ZVC Network Analyzer, with $T = 25\text{ }^{\circ}\text{C}$, source power $\approx -30\text{ dBm}$

Input Return Loss, Log Mag

5 MHz - 8 GHz Sweep

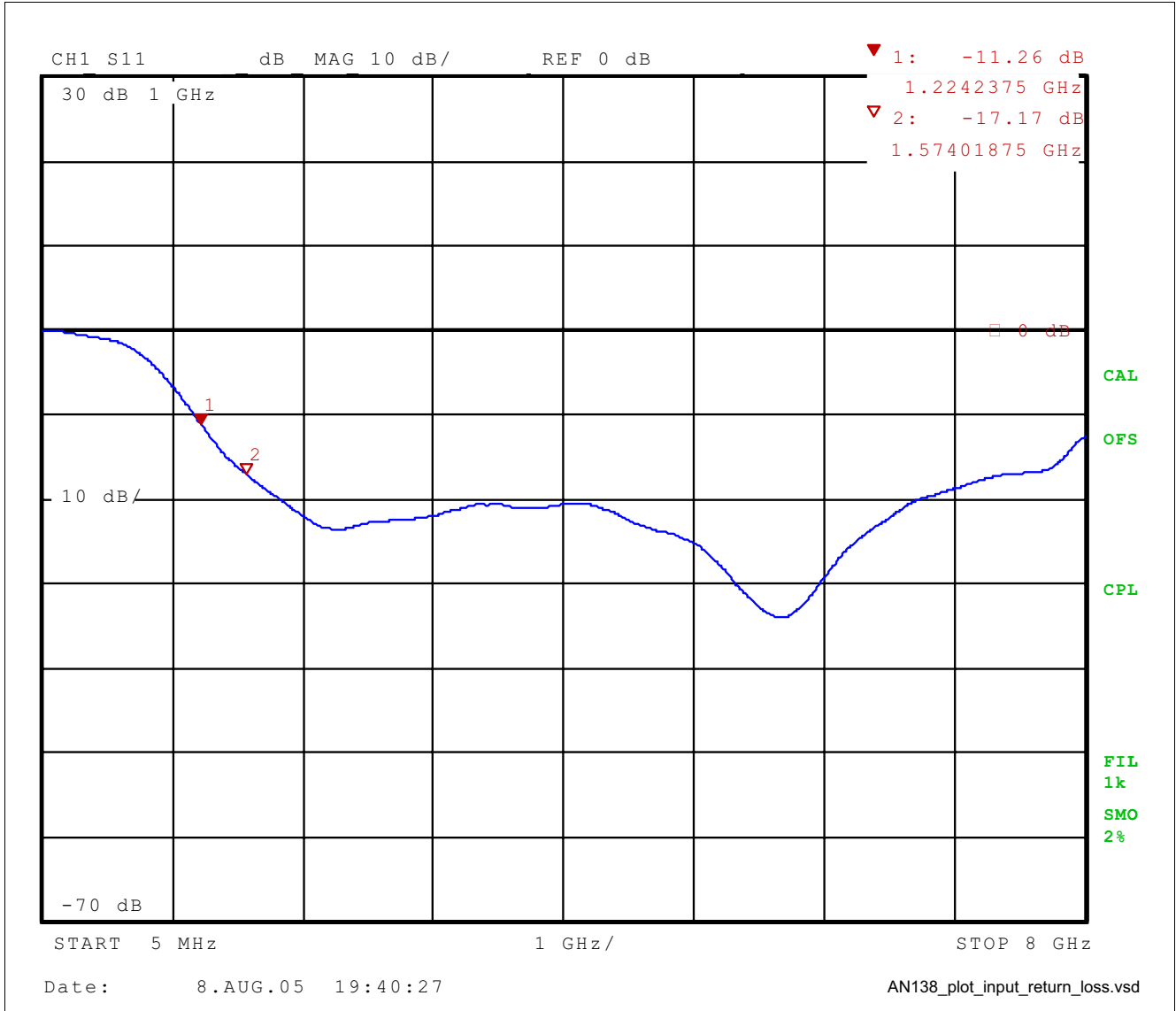


Figure 8 Plot of Input Return Loss

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Input Return Loss, Smith Chart

Reference Plane = Input SMA Connector on PC Board
 5 MHz - 8 GHz Sweep

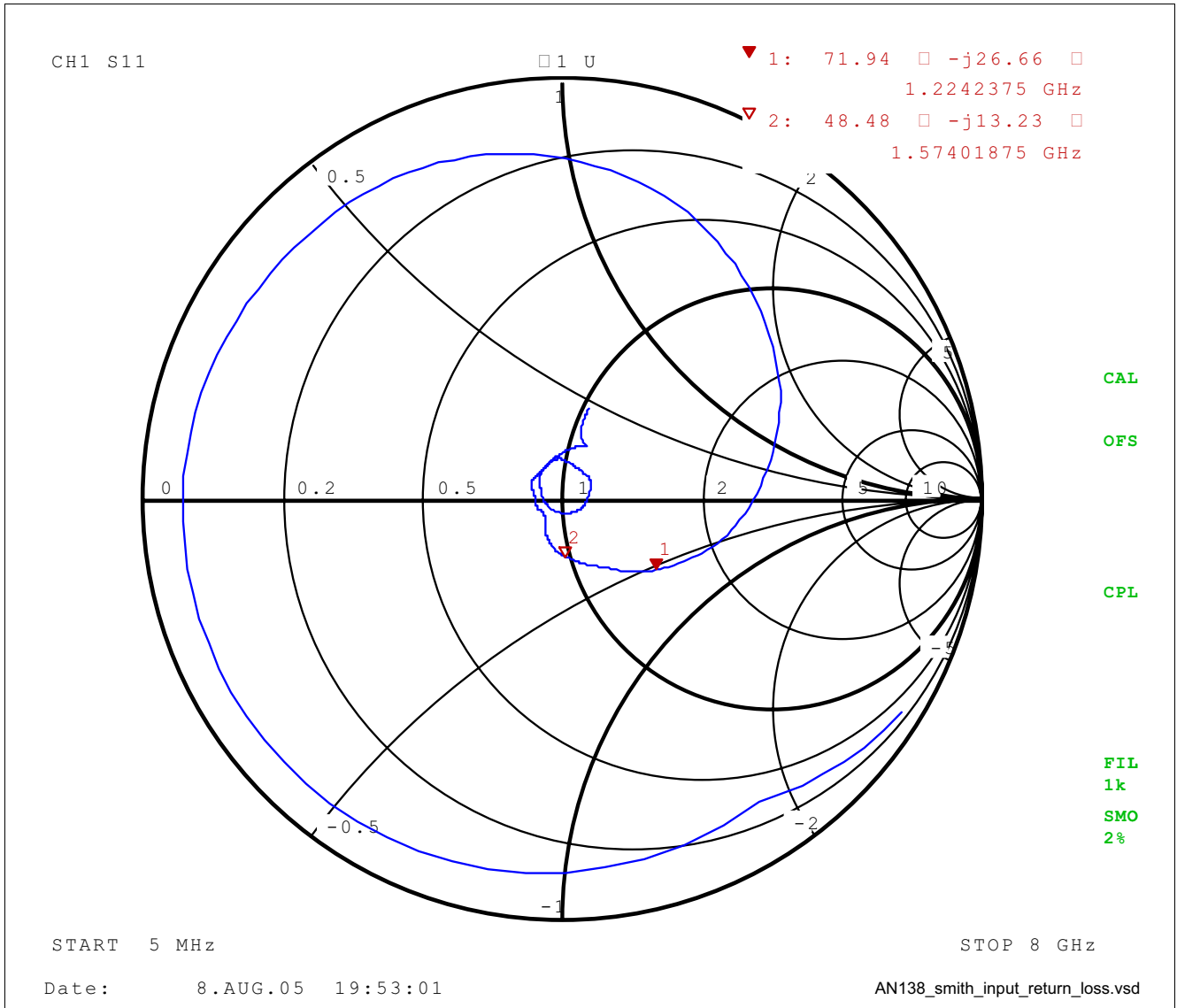


Figure 9 Smith Chart of Input Return Loss

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Forward Gain

5 MHz - 8 GHz Sweep

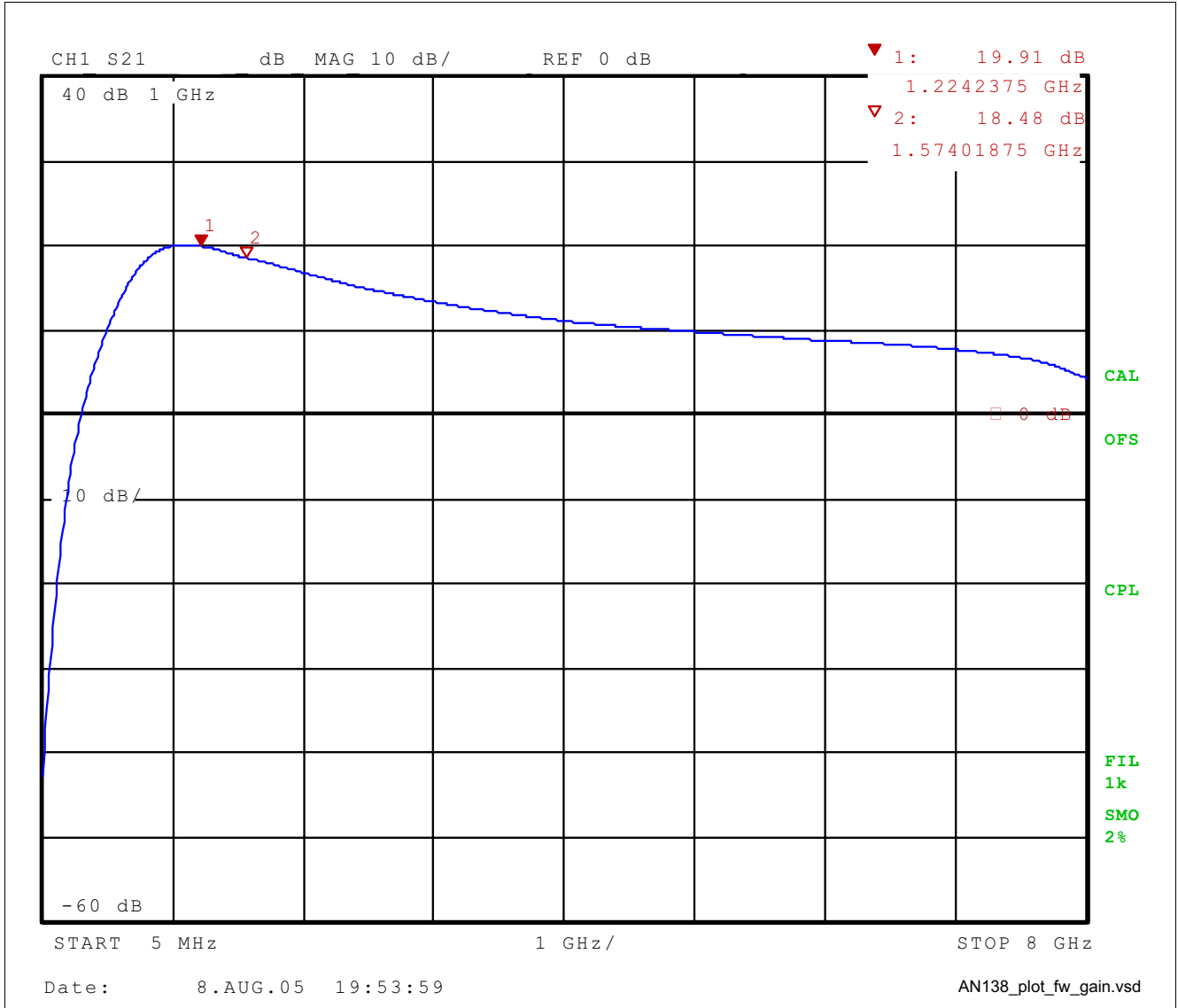


Figure 10 Plot of Forward Gain

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Reverse Isolation

5 MHz - 8 GHz Sweep

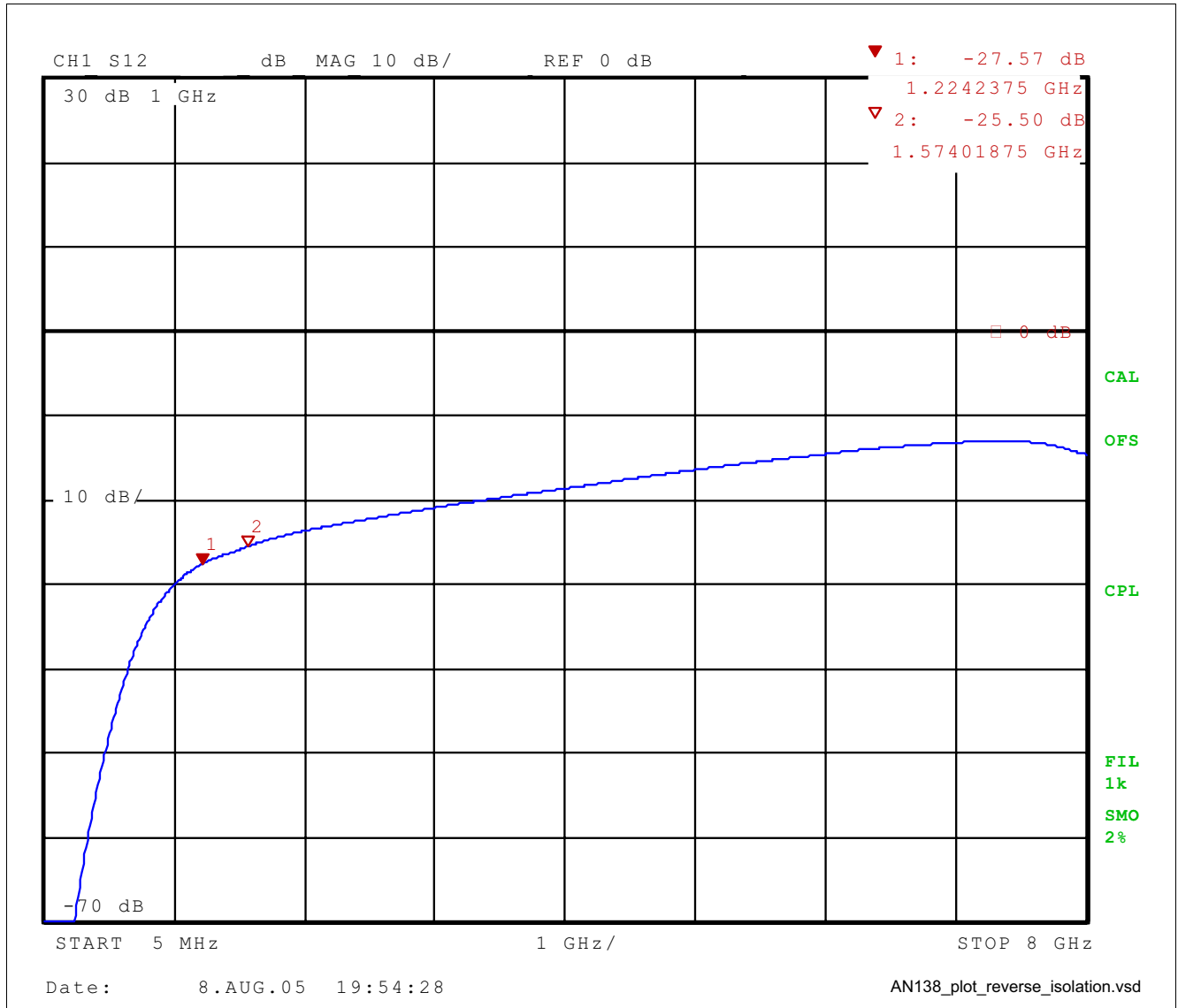


Figure 11 Plot of Reverse Isolation

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Output Return Loss, Log Mag

5 MHz - 8 GHz Sweep

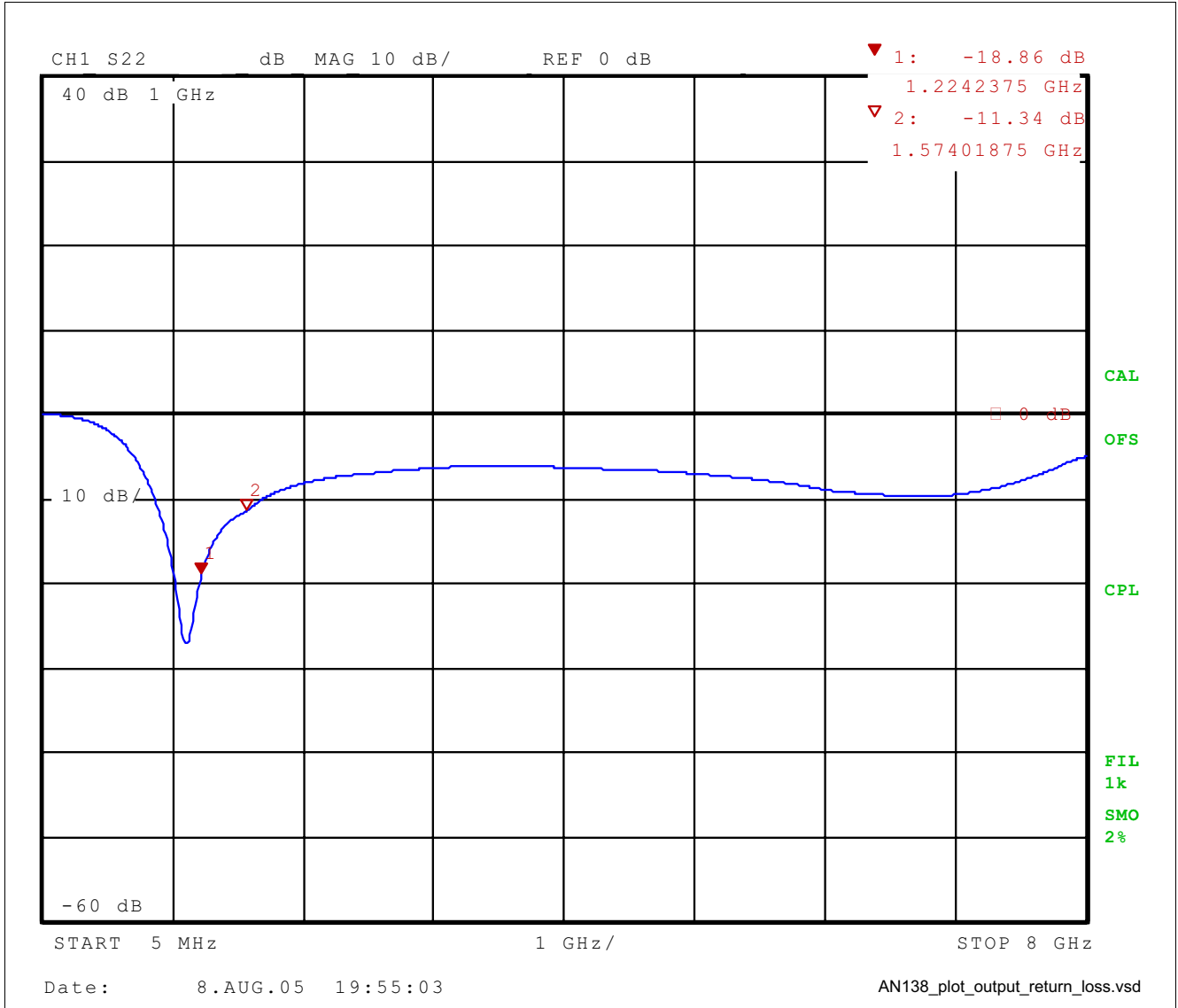


Figure 12 Plot of Output Return Loss

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Output Return Loss, Smith Chart

Reference Plane = Output SMA Connector on PC Board
5 MHz - 8 GHz Sweep

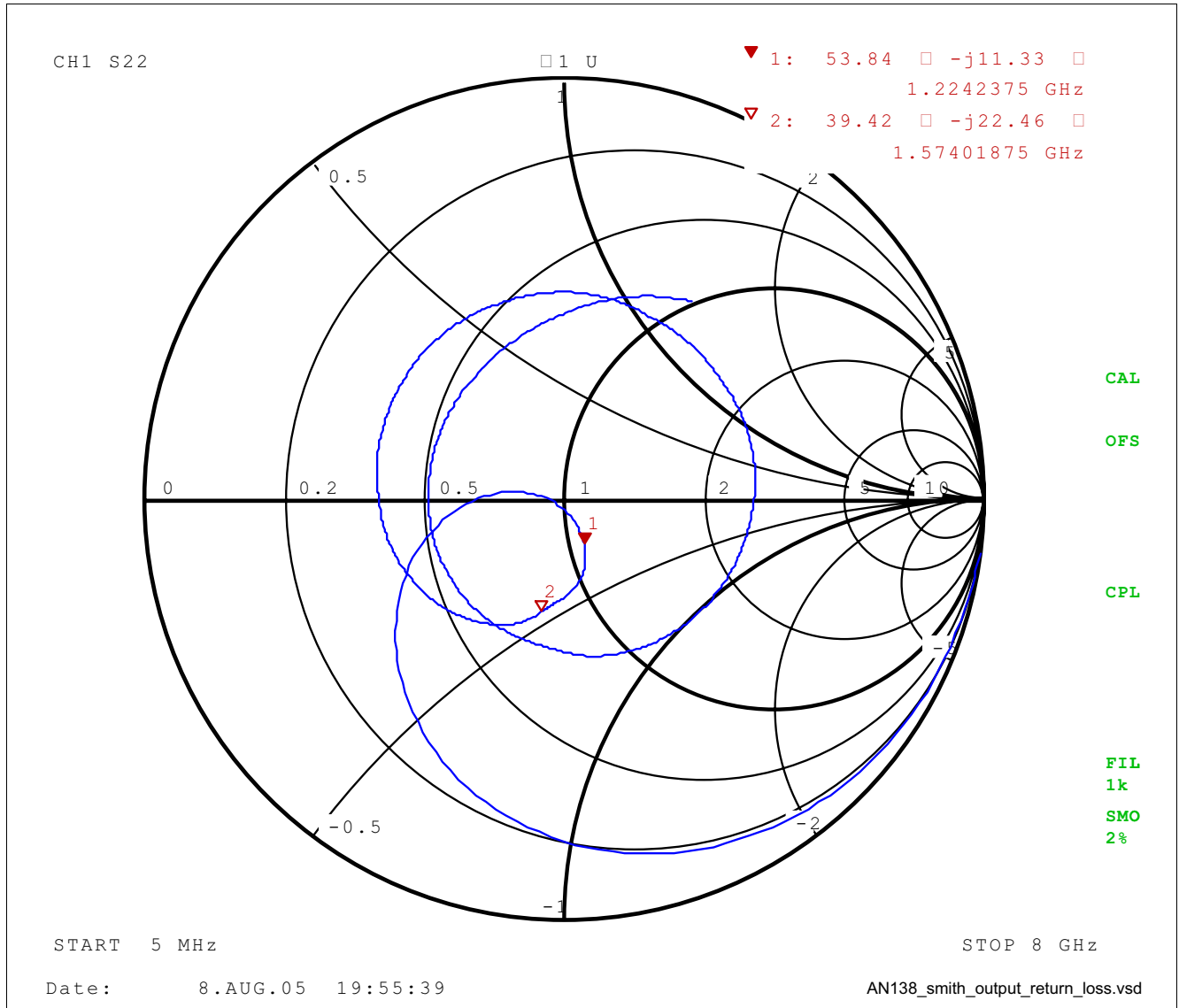


Figure 13 Smith Chart of Output Return Loss

Dual-Band (L1 + L2) GPS Low Noise Amplifier using the SiGe BFP640 HBT RF

Two-Tone Test, 1575 MHz

Input Stimulus for Amplifier Two-Tone Test.

$f_1 = 1575$ MHz, $f_2 = 1576$ MHz, -25 dBm each tone.

LNA response to two-tone test is below (spectrum analyzer screen-shot).

Input $IP_3 = -25 + (61.4 / 2) = +5.7$ dBm. Output $IP_3 = +5.7$ dBm + 18.5 dB gain = +24.2 dBm

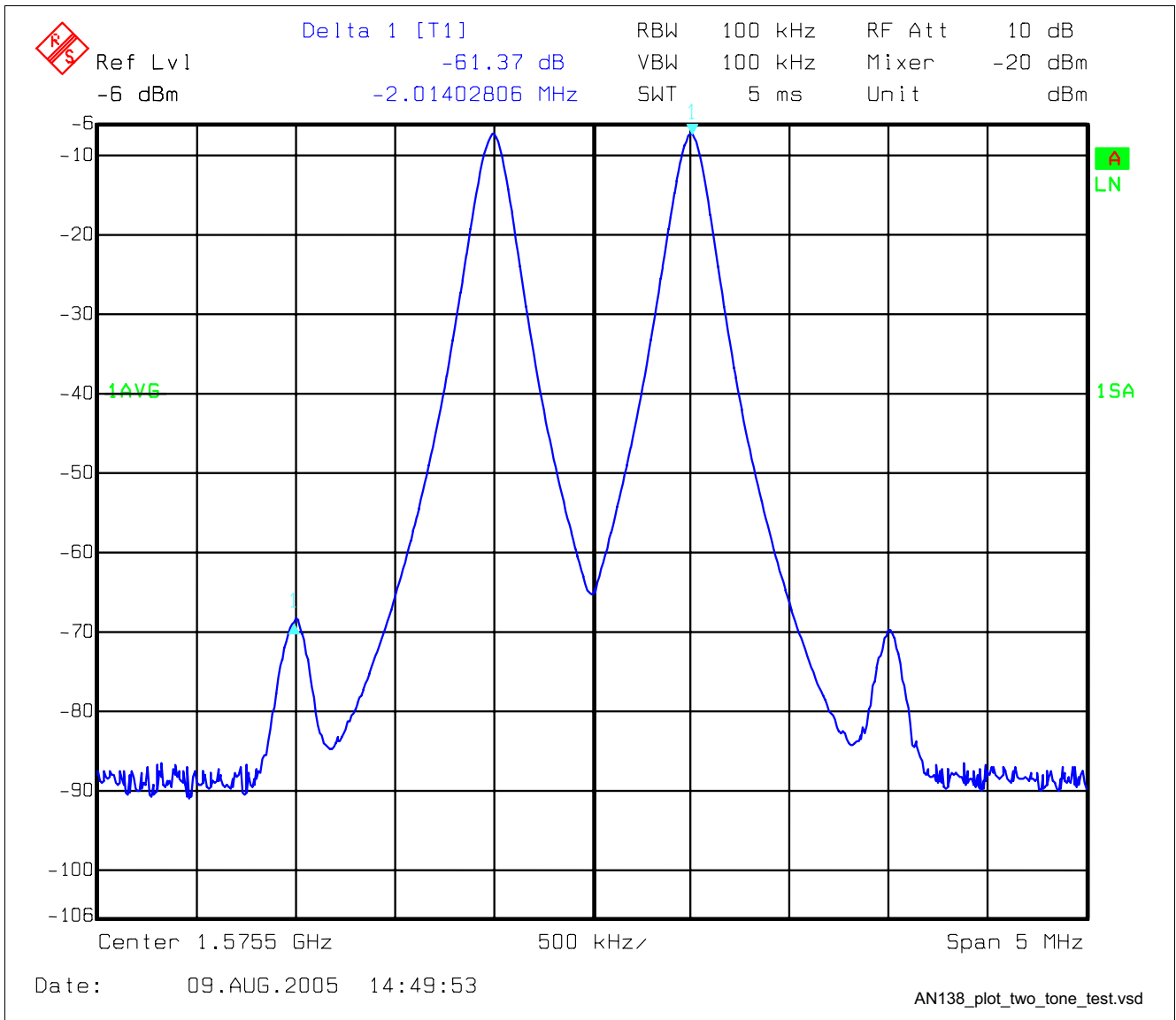


Figure 14 Two-Tone Test, LNA Response @ 1575 MHz