

# Application Note No. 145

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output Stage using the Infineon BFP450 Transistor

RF & Protection Devices



Never stop thinking

**Edition 2008-02-21**

**Published by  
Infineon Technologies AG  
81726 München, Germany**

**© Infineon Technologies AG 2011.  
All Rights Reserved.**

#### **LEGAL DISCLAIMER**

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

#### **Information**

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

#### **Warnings**

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

---

**Application Note No. 145**

**Revision History: 2008-02-21, Rev. 1.2**

**Previous Version: 2005-03-01, Rev. 1.1**

<b>Page</b>	<b>Subjects (major changes since last revision)</b>
All	Small changes in figure descriptions

# 1 Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output Stage using the Infineon BFP450 Transistor

## Overview

BFP450 SIEGET transistor is investigated as an alternative to the BFP650 SiGe Low Noise Transistor for the output stage of an SDARS active antenna LNA. A key parameter is +20 dBm  $P_{1dB}$  capability in the output stage. The PCB used is standard FR4 material & "0402" case sizes components are used. A total of approximately 50 mm<sup>2</sup> of PCB area is required, the total component count, including the BFP450 and all passives, is 13. Net result is: BFP450 provides slightly more available output power than BFP650 at comparable DC operating points; however, BFP450 has less gain and higher noise figure. See table below. Both devices are in SOT343 package with identical pin-outs. Note output power is "voltage limited" = e.g. if bias resistors were changed after power supply voltage was increased, one should be able to hit +20 dBm  $OP_{1dB}$  with less than 100 mA current.

**Table 1 Comparison of BFP650 and BFP450 as SDARS active antenna output stage at 2.33 GHz**


Device	DC Operating Point	Small Signal Gain, dB	Output $P_{1dB}$ , dBm	Noise Figure, dB
BFP450	3 V, 76 mA, $V_{CE} = 2.7$ V	9.8	+18.7	2.7
BFP450	3.7 V, 100 mA, $V_{CE} = 3.2$ V	10.0	+20.5	Not tested
BFP650	3.0 V, 53 mA	14.1	≈ +18.0	1.3

## Summary

- Achieved 9.8 dB gain, 2.7 dB Noise Figure over the 2320 - 2345 MHz band, drawing 76 mA @ 3.0 V, or 100 mA @ 3.7 V. Amplifier is unconditionally stable from 5 MHz to 8 GHz. Output  $P_{1dB} = +18.7$  dBm @ 3 V, 76 mA or +20.5 dBm @ 3.7 V, 100 mA.
- BFP450 seems to show a slight advantage in Output  $P_{1dB}$  as compared to the BFP650. However, gain of BFP450 in same PC board is approx. 4 dB lower, and noise figure of BFP450 is 1.4 dB higher.

## Block Diagram of Application

Typical SDARS Active Antenna LNA  
 2320 - 2332.5 MHz (SIRIUS, 3 Stages)  
 2332.5 - 2345 MHz (XM Radio, 2 Stages)

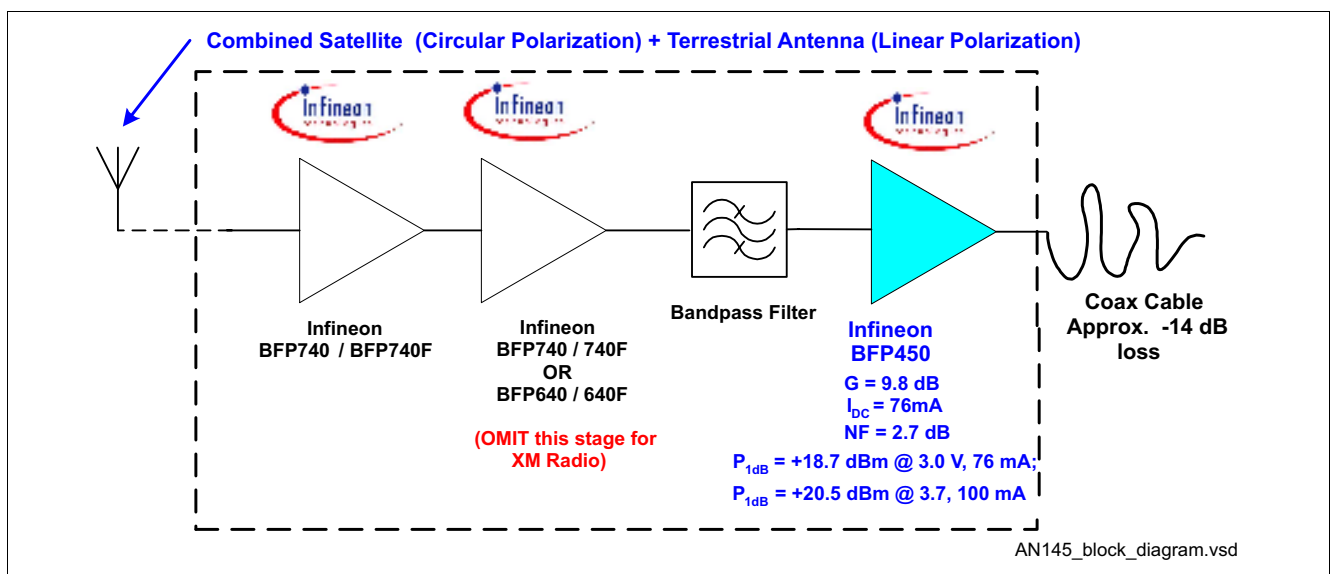

**Figure 1 Block Diagram of Application**

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

PC Board Cross Sectional Diagram

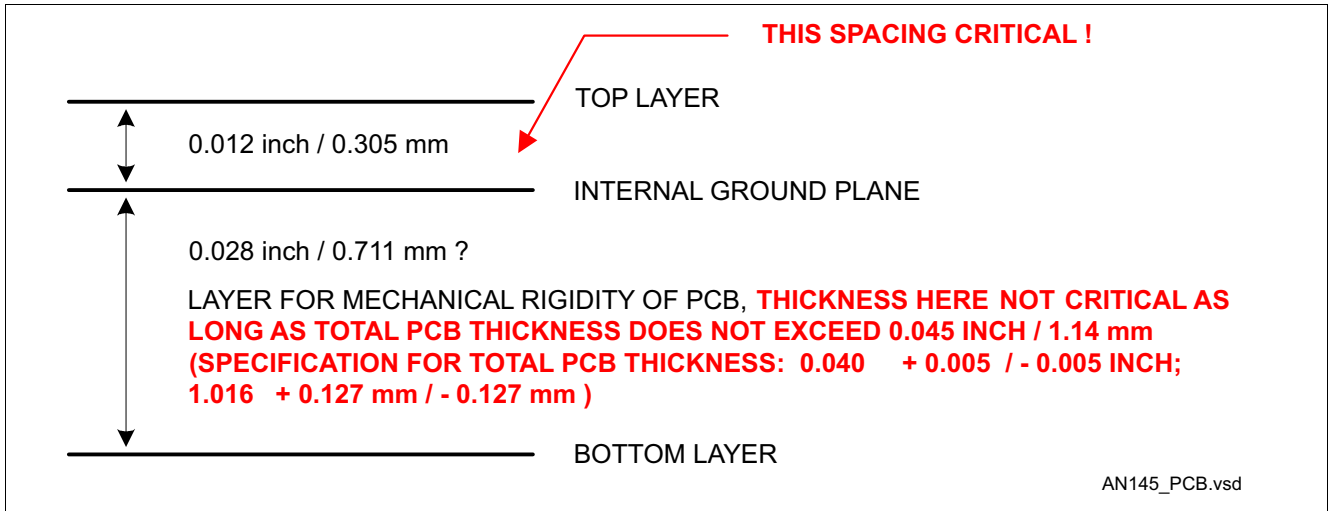


Figure 2 PCB - Cross Sectional Diagram

Schematic Diagram

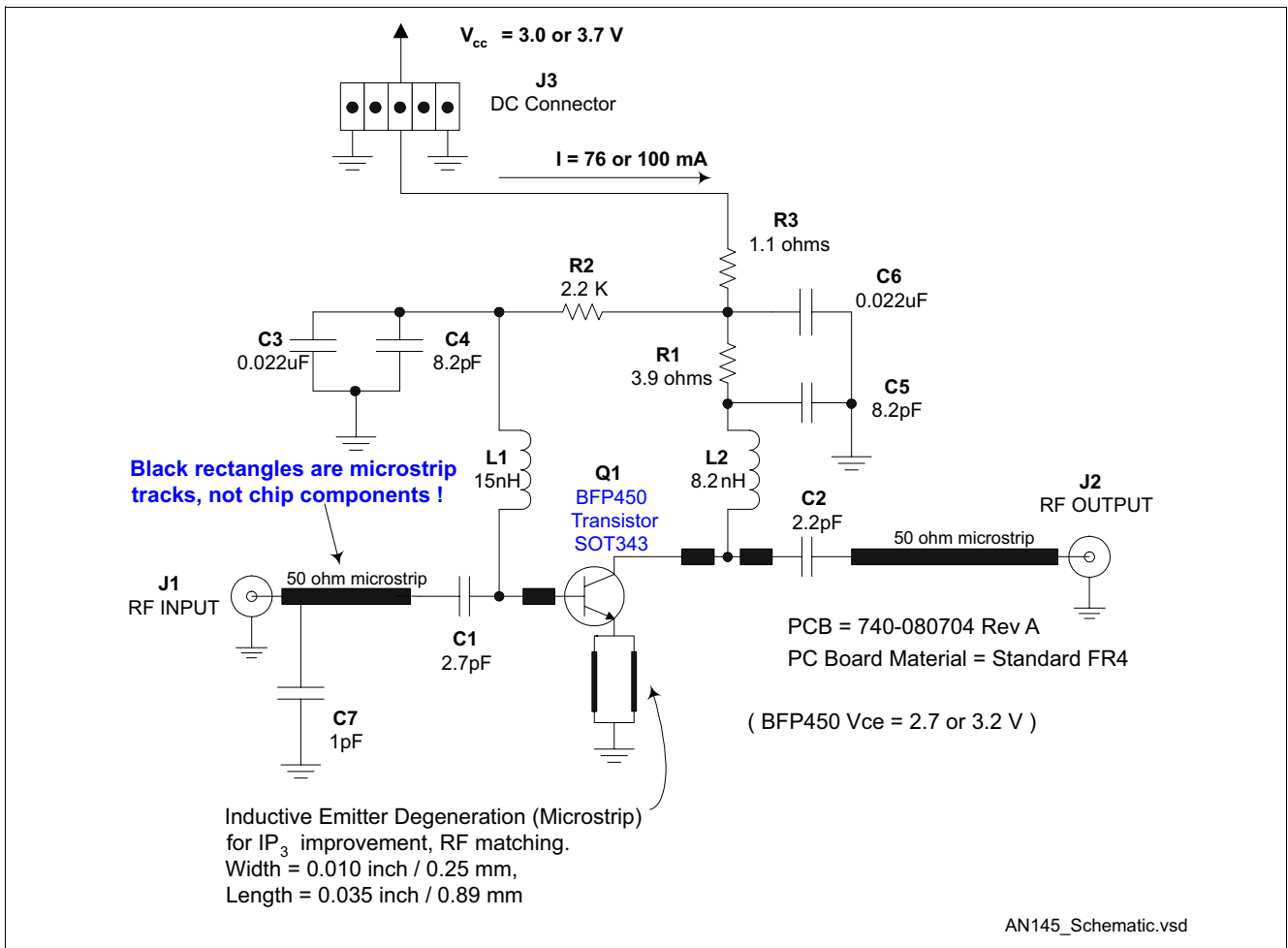


Figure 3 Schematic Diagram

---

**Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output**
**Summary of Data**

$T = 25\text{ }^{\circ}\text{C}$ , Network analyzer source power  $\approx -30\text{ dBm}$

**Table 2 Summary of Results**

Parameter	Result	Comments
Frequency Range	Under 2320 to 2345 MHz	Covers both XM Radio and SIRIUS frequency bands.
DC Current	100 mA @ 3.7 V 76 mA @ 3.0 V	Note power supply voltage is measured directly across PCB supply line and ground, to eliminate voltage drop across wire harness.
Gain	9.8 dB @ 2332.5 MHz	
Noise Figure	2.7 dB @ 2332.5 MHz	These values do not extract PCB losses, etc. resulting from FR4 board and passives used on PCB - these results are at input SMA connector.
Input $P_{1dB}$	+11.7 dBm @ 3.7 V +9.9 dBm @ 3.0 V	Measured @ 2332.5 MHz. See <a href="#">Table 4</a> and <a href="#">Table 5</a> .
Output $P_{1dB}$	+20.5 dBm @ 3.7 V +18.7 dBm @ 3.0 V	See <a href="#">Table 4</a> and <a href="#">Table 5</a> .
Collector Efficiency at 1 dB Compression Point	30.3 % @ 3.7 V 32.5 % @ 3.0 V	Decent results for a Class A amplifier
Input 3 <sup>rd</sup> Order Intercept	+22.9 dBm @ 2332 MHz	<a href="#">Figure 14</a> and <a href="#">Figure 15</a> . Measured at 3.0 V.
Output 3 <sup>rd</sup> Order Intercept	+32.6 dBm @ 2332 MHz	<a href="#">Figure 14</a> and <a href="#">Figure 15</a> . Measured at 3.0 V.
Input Return Loss	9.0 dB @ 2332.5 MHz	
Output Return Loss	9.8 dB @ 2332.5 MHz	
Reverse Isolation	14.6 dB @ 2332.5 MHz	

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

Noise Figure, Plot, 2232.5 MHz to 2432.5 MHz, Center of Plot (x-axis) is 2332.5 MHz.

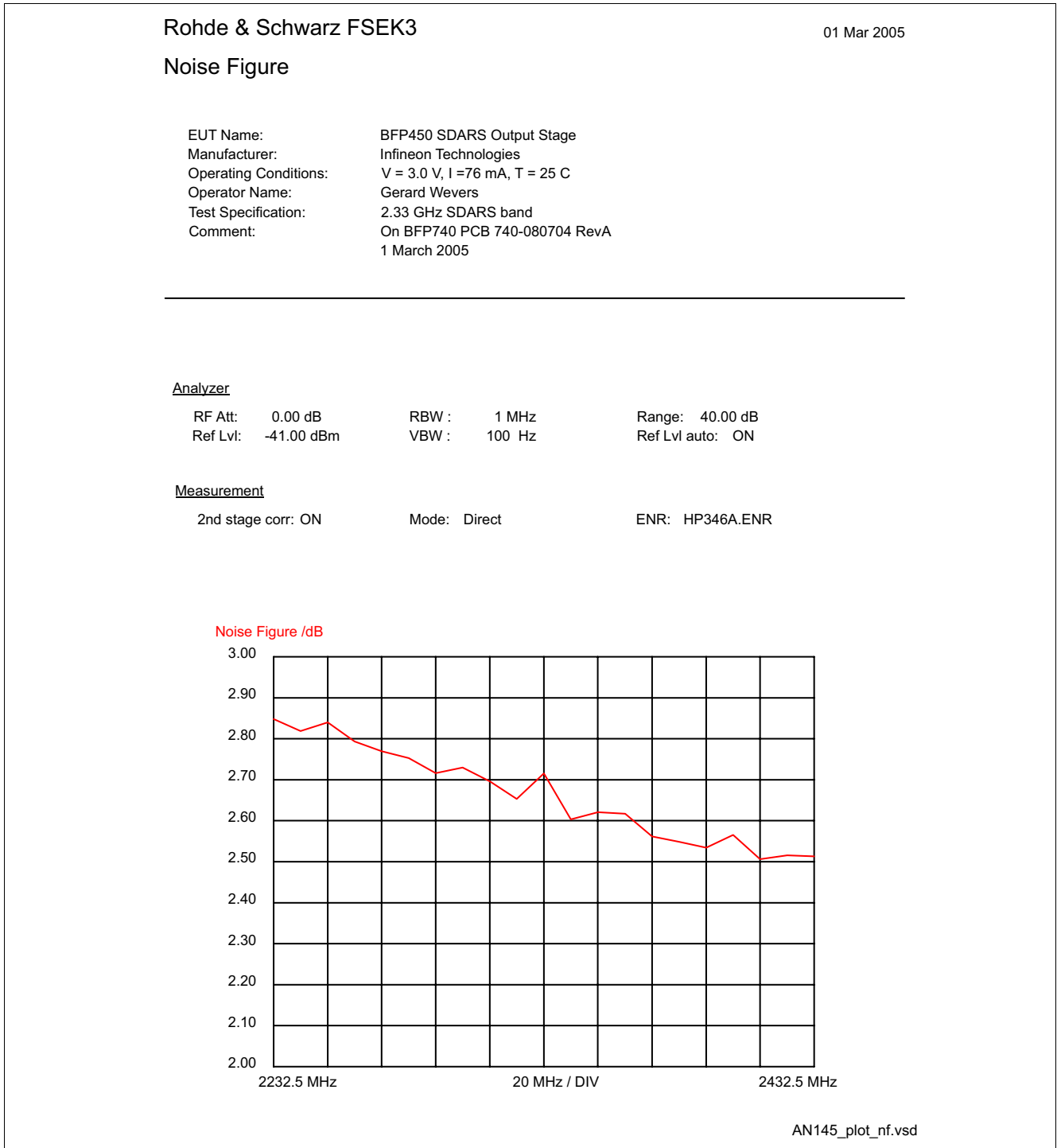


Figure 4 Noise Figure

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**Noise Figure, Tabular Data**

From Rohde & Schwarz FSEK3 + FSEM30  
System Preamplifier = MITEQ SMC-02

**Table 3 Noise Figure**

Frequency	Noise Figure
2232.5 MHz	2.85 dB
2242.5 MHz	2.82 dB
2252.5 MHz	2.84 dB
2262.5 MHz	2.79 dB
2272.5 MHz	2.77 dB
2282.5 MHz	2.75 dB
2292.5 MHz	2.72 dB
2302.5 MHz	2.73 dB
2312.5 MHz	2.70 dB
2322.5 MHz	2.65 dB
2332.5 MHz	2.72 dB
2342.5 MHz	2.60 dB
2352.5 MHz	2.62 dB
2362.5 MHz	2.62 dB
2372.5 MHz	2.56 dB
2382.5 MHz	2.55 dB
2392.5 MHz	2.53 dB
2402.5 MHz	2.57 dB
2412.5 MHz	2.51 dB
2422.5 MHz	2.52 dB
2432.5 MHz	2.51 dB



Scanned Image of PC Board



Figure 5 Image of PC Board

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

Scanned Image of PC Board, Close-In Shot.

Total PCB area used  $\cong$  50 mm<sup>2</sup>.


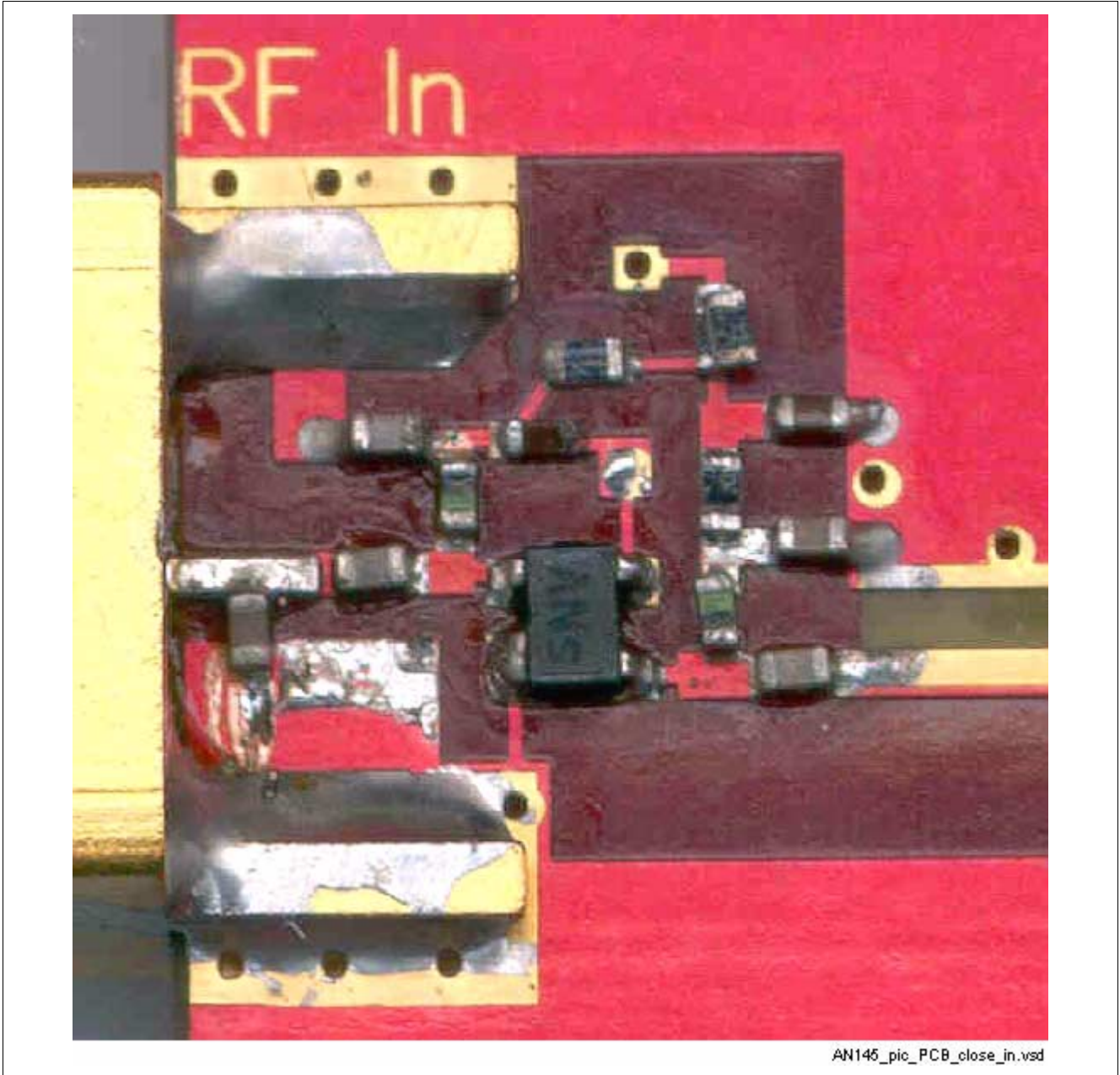


Figure 6 Image of PC Board, Close-In Shot

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**Stability**

Rohde and Schwarz ZVC Network Analyzer calculates and plots Stability Factor "K" in real time. Note minimum K value is approximately 1.04 over the 5 MHz to 8 GHz range. Since inductive emitter degeneration is used, S parameters should be measured up to at least 15 GHz to verify  $K > 1$ ,  $B_1 > 0$  up to 15 GHz.

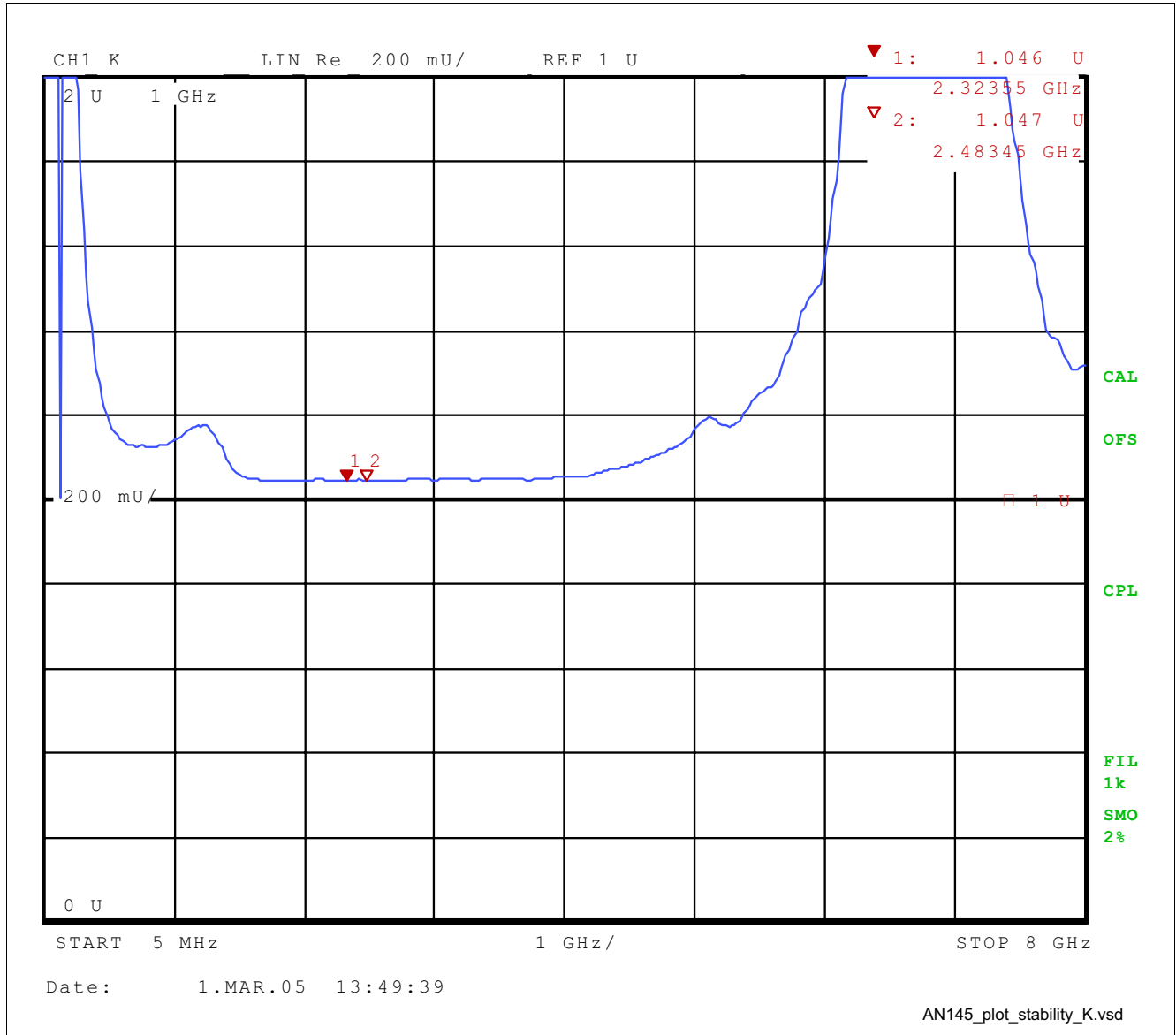

**Figure 7 Plot of K(f)**

## Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**Gain Compression**

Amplifier is checked for 1 dB compression point at  $V_{CC} = 3.0\text{ V}$ ,  $I = 76\text{ mA}$  (with  $V_{CE} = 2.7\text{ V}$ ), and at  $V_{CC} = 3.7\text{ V}$ ,  $I = 100\text{ mA}$  (with  $V_{CE} = 3.2\text{ V}$ ). An Agilent power meter was used to ensure accurate power levels are measured (as opposed to using Vector Network Analyzer in "Power Sweep" mode).

For 3.0 V power supply voltage  $\Rightarrow O_{P1dB} \cong +18.7\text{ dBm}$ , or 74.1 mW

Collector efficiency at this point is  $74.1\text{ mW} / (3\text{ V} \times 76\text{ mA}) = 32.5\%$

For 3.7 V power supply voltage  $\Rightarrow O_{P1dB} \cong +20.5\text{ dBm}$ , or 112.2 mW

Collector efficiency at this point is  $112.2\text{ mW} / (3.7\text{ V} \times 100\text{ mA}) = 30.3\%$

**Table 4 3.0 V, 76 mA**

$P_{IN}$ , dBm	$P_{OUT}$ , dBm	Gain
0	+9.9	9.9
+5.0	+14.8	9.8
+6.0	+15.8	9.8
+7.0	+16.6	9.6
+8.0	+17.5	9.5
+9.0	+18.2	9.2
+10.0	+18.8	8.8
+11.0	+19.2	8.2

**Table 5 3.7 V, 100 mA**


$P_{IN}$ , dBm	$P_{OUT}$ , dBm	Gain
0	+10.1	10.1
+5.0	+15.0	10.0
+6.0	+16.0	10.0
+7.0	+16.9	9.9
+8.0	+17.8	9.8
+9.0	+18.7	9.7
+10.0	+19.5	9.5
+11.0	+20.3	9.3
+12.0	+20.9	8.9

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

Please Note - all plots are taken from ZVC Network Analyzer with amplifier DC bias set to 3.0 V, 76 mA.

**Input Return Loss, Log Mag**

5 MHz - 8 GHz

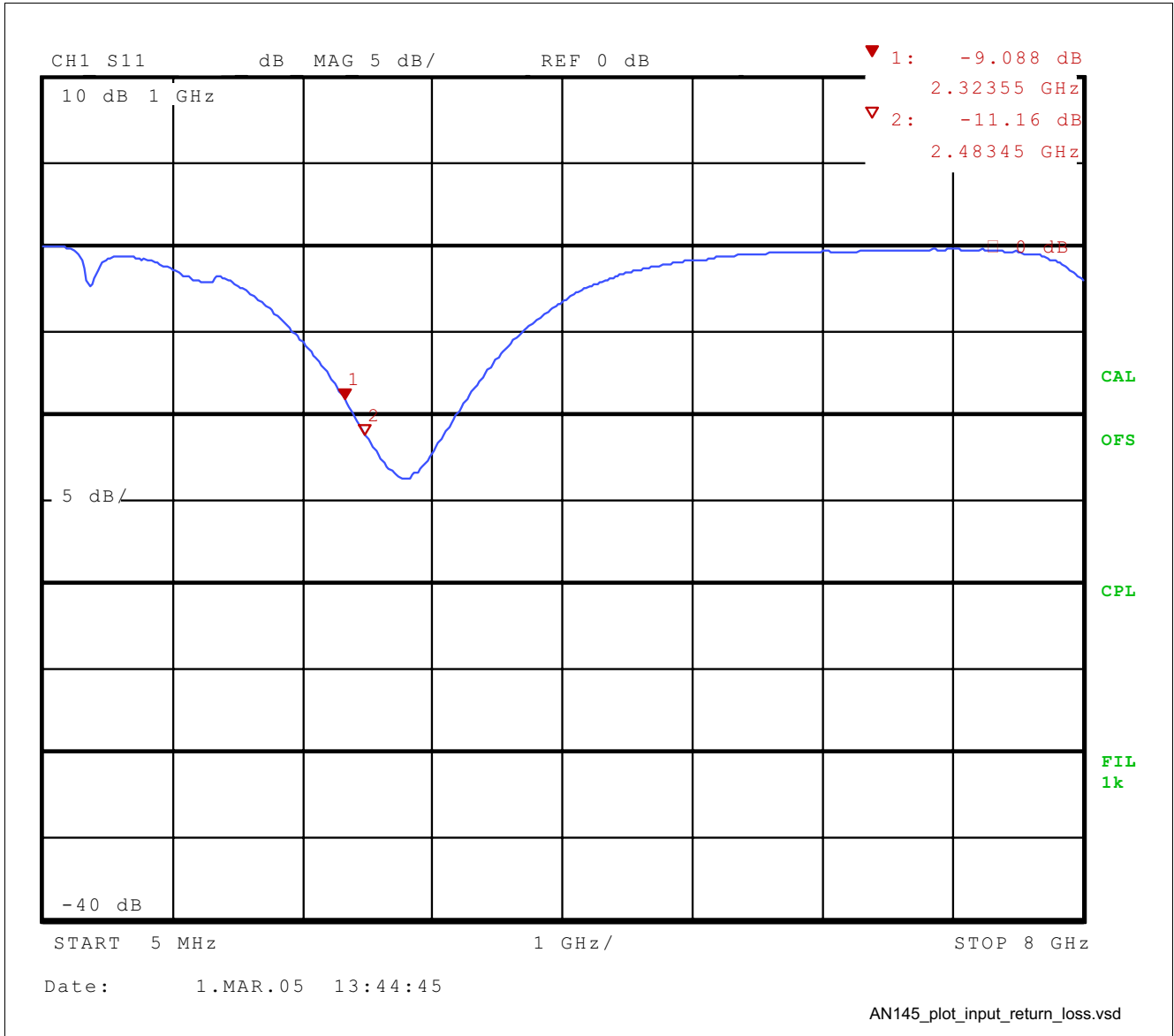


**Figure 8 Plot of Input Return Loss**

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**Input Return Loss, Smith Chart**

Reference Plane = Input SMA Connector on PC Board  
5 MHz - 8 GHz

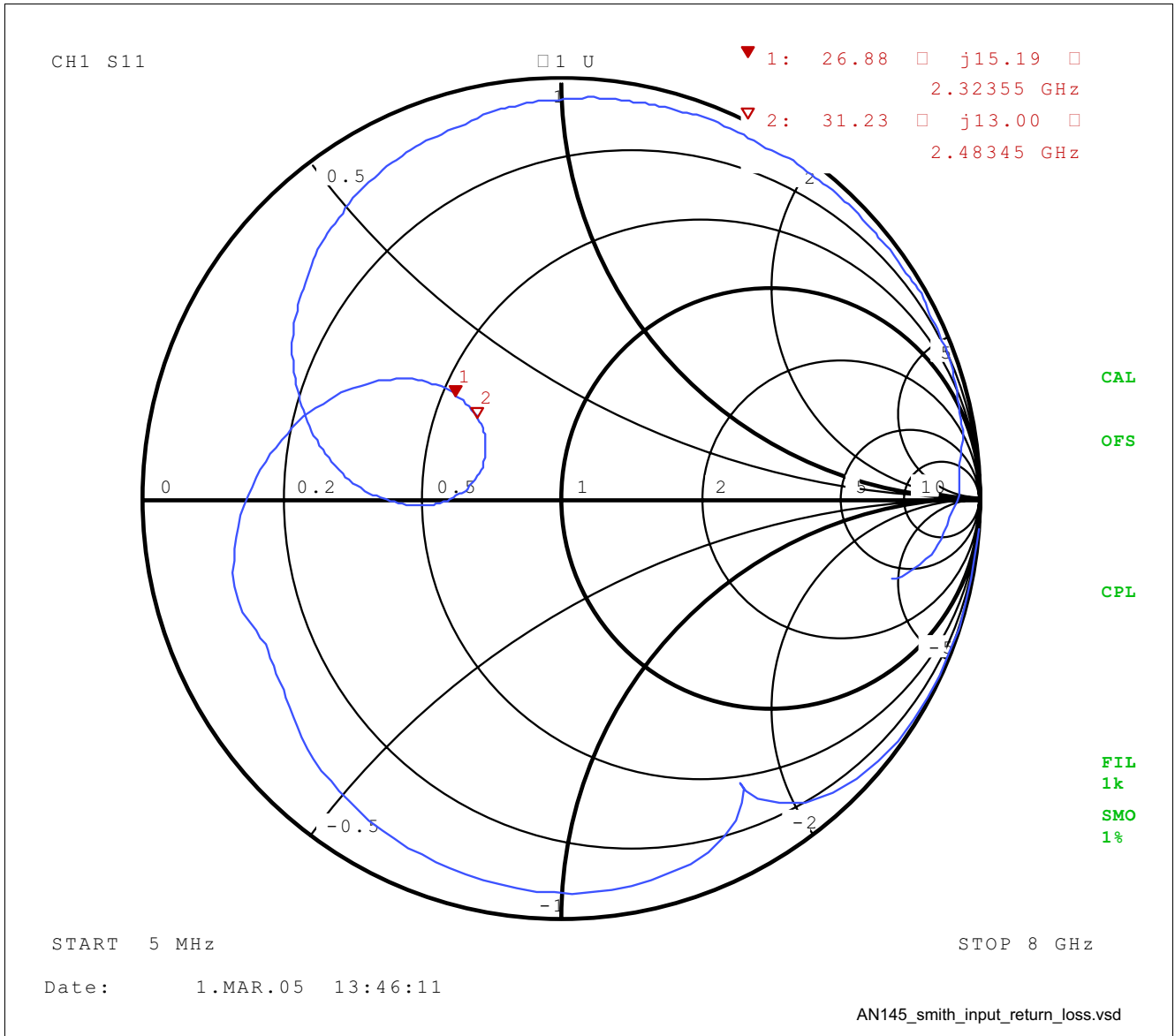

**Figure 9** Smith Chart of Input Return Loss

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

Forward Gain, Wide Sweep

5 MHz - 8 GHz


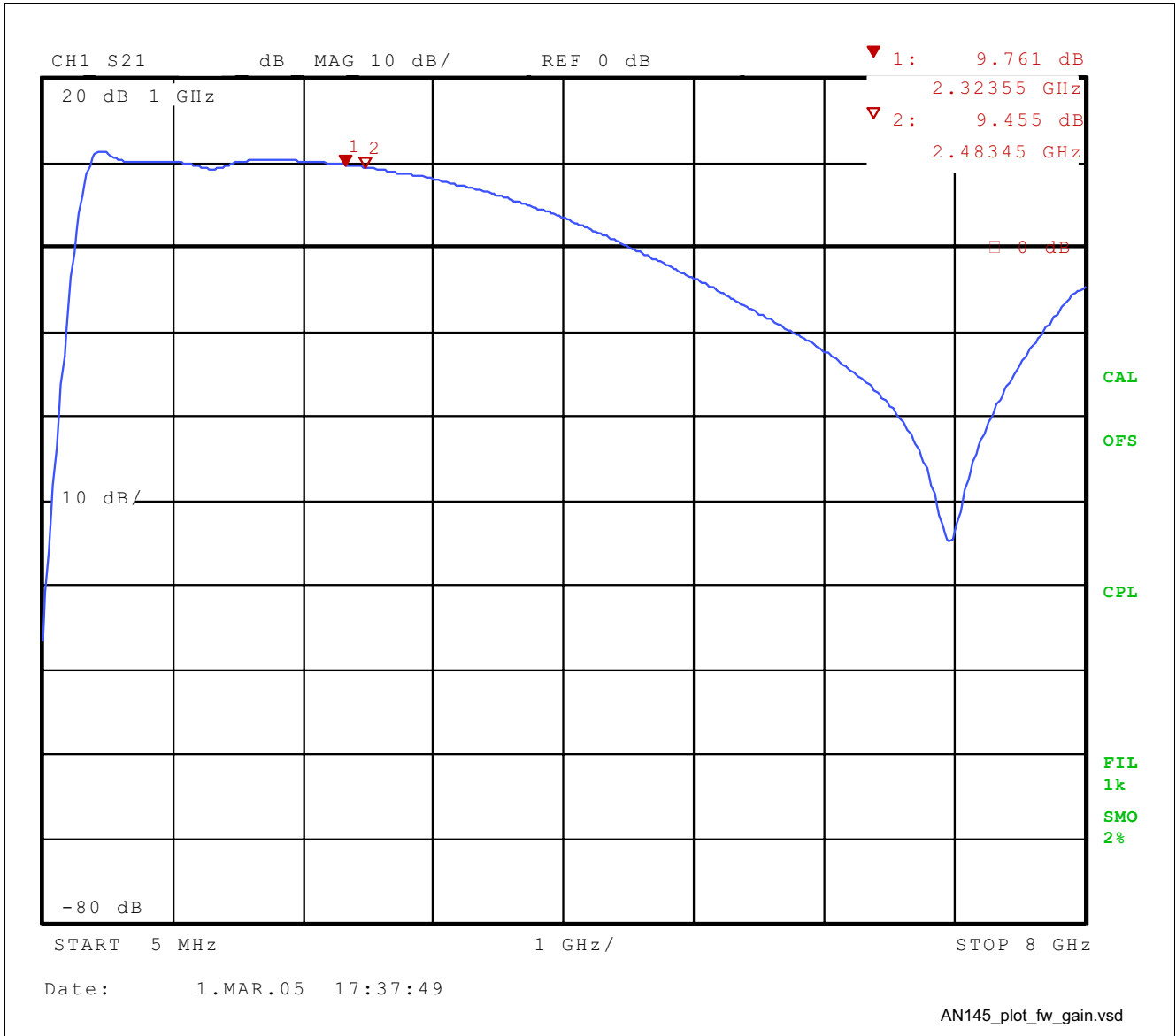


Figure 10 Plot of Forward Gain

**Reverse Isolation**

5 MHz - 8 GHz

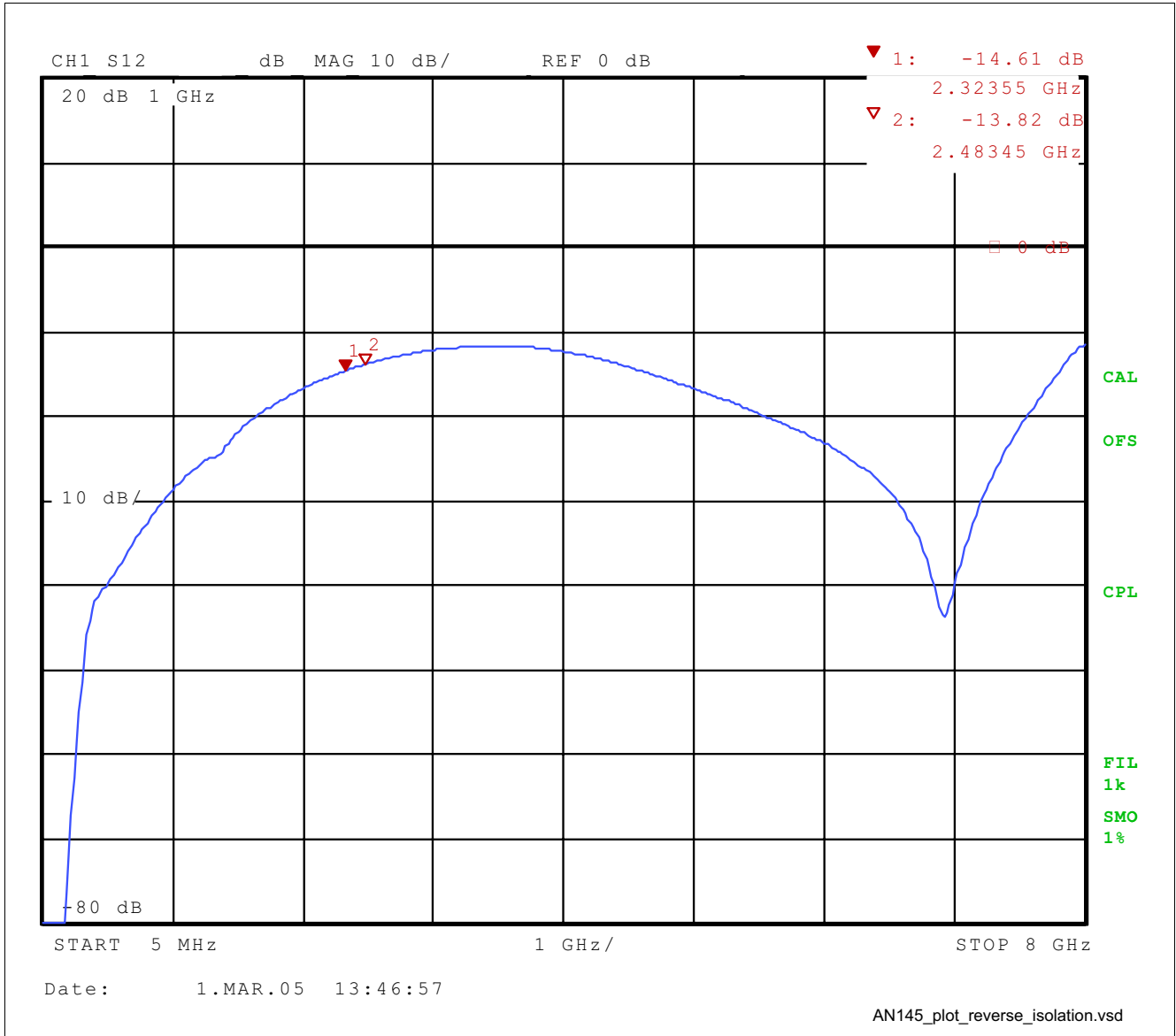

**Figure 11 Plot of Reverse Isolation**



Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

Output Return Loss, Log Mag

5 MHz - 8 GHz


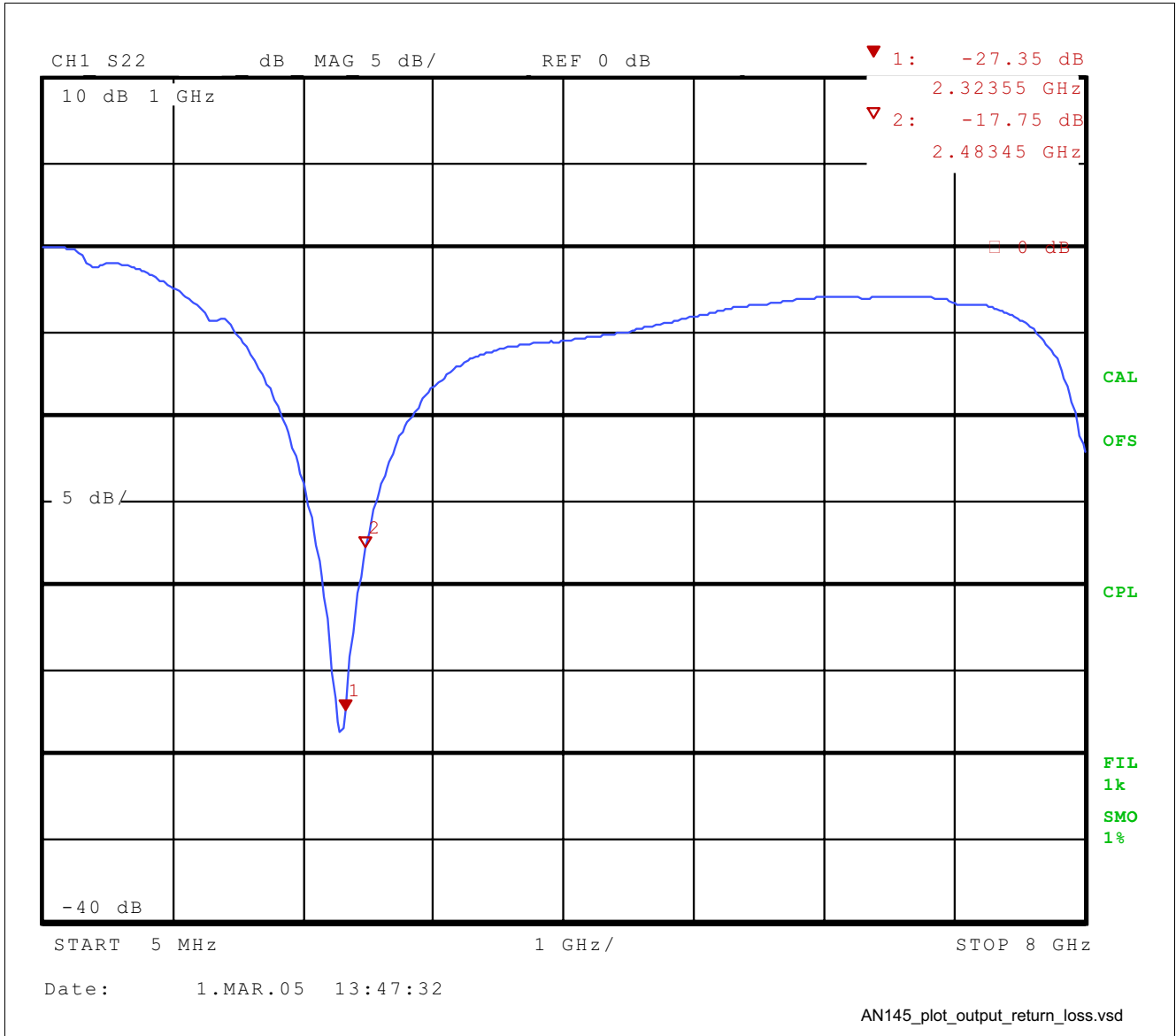


Figure 12 Plot of Output Return Loss

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**Output Return Loss, Smith Chart**

Reference Plane = Output SMA Connector on PC Board  
5 MHz - 8 GHz

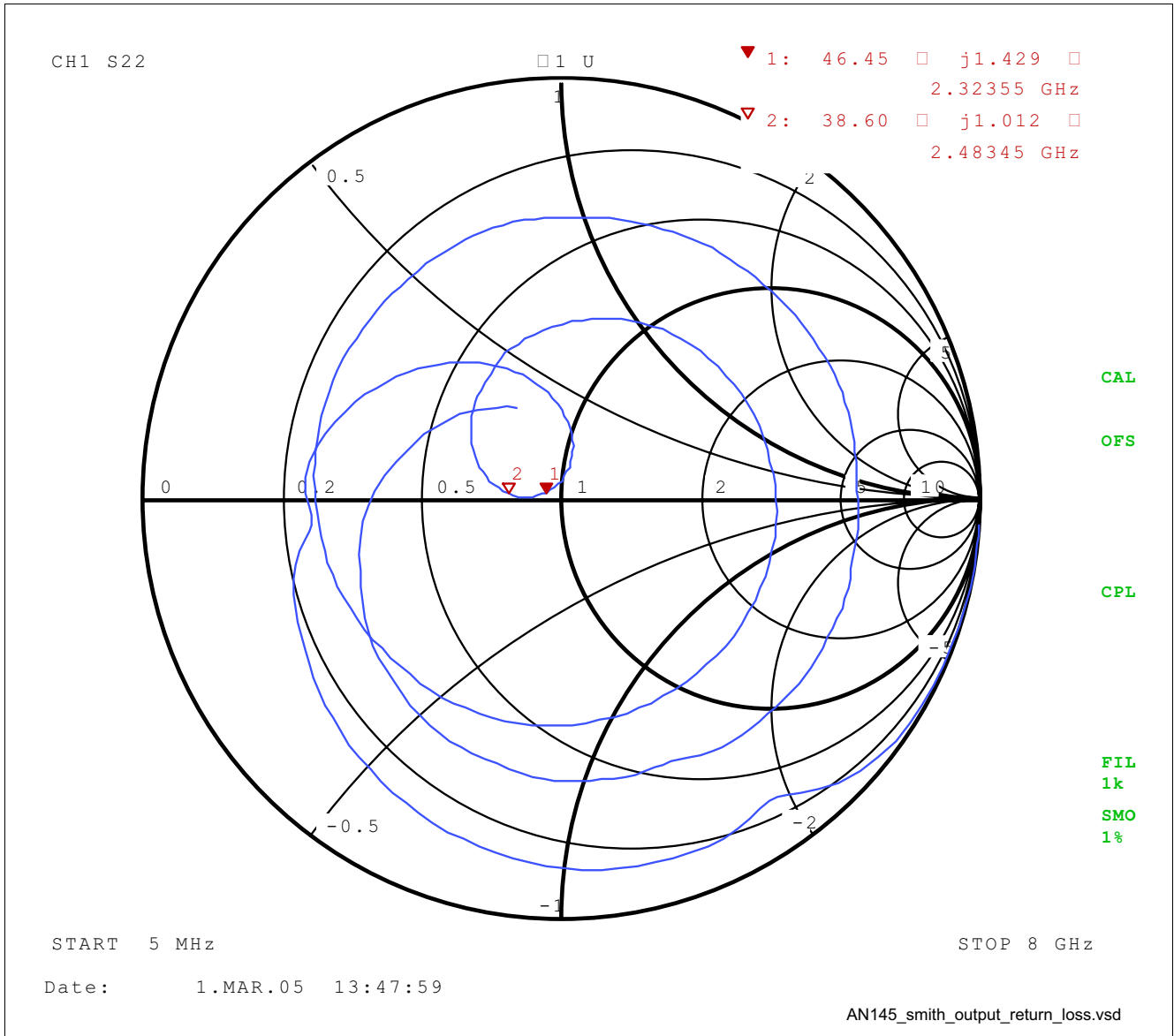


**Figure 13 Smith Chart of Output Return Loss**

Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**Two Tone Test**

Input Stimulus for Amplifier Two-Tone Test:

$f_1 = 2332 \text{ MHz}$ ,  $f_2 = 2333 \text{ MHz}$ ,  $-10 \text{ dBm}$  each tone.

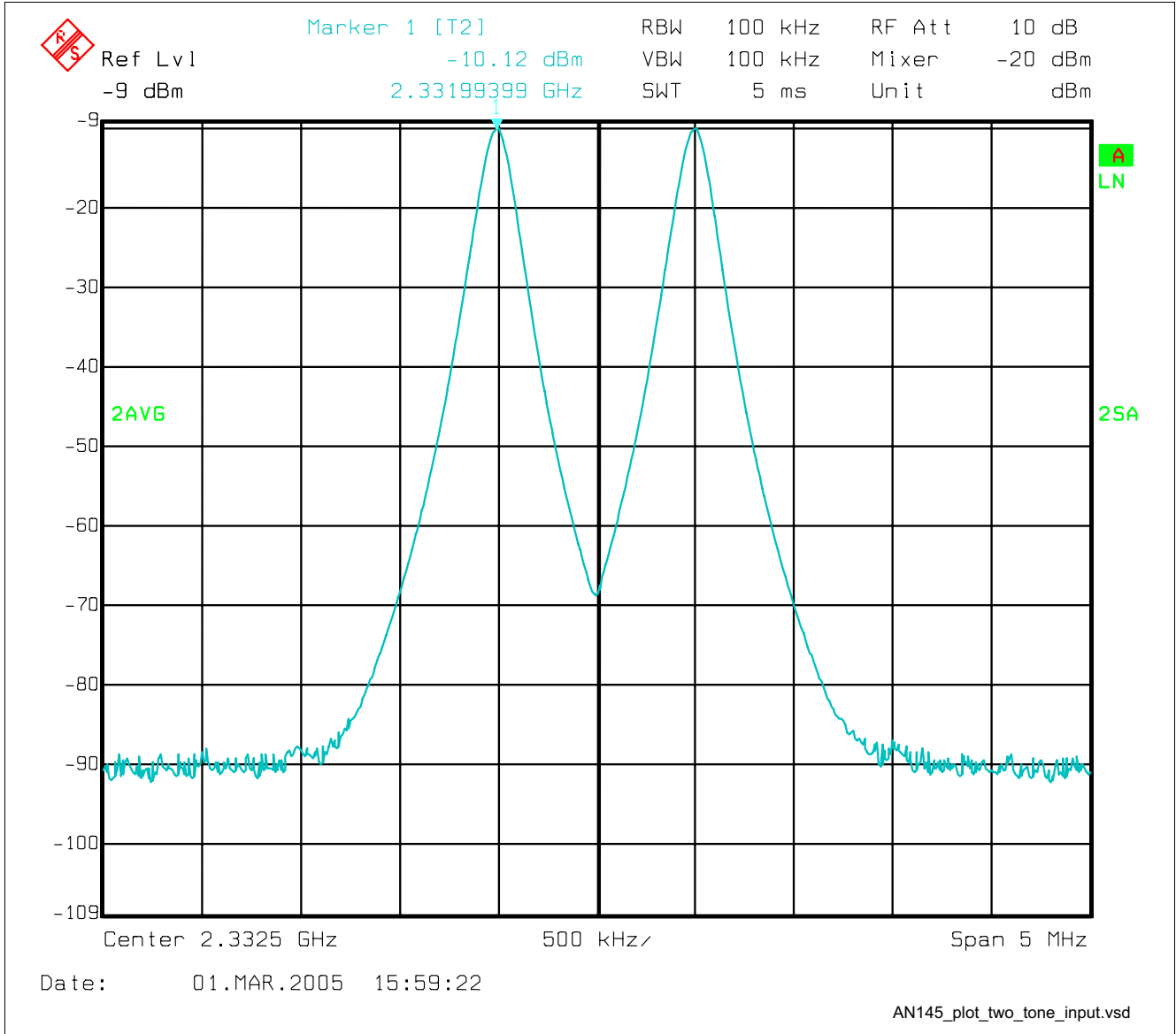

**Figure 14 Two-Tone Test, Input Stimulus**


Low Cost, 3 V, 2.33 GHz Class A SDARS Active Antenna Amplifier Output

**LNA Response to Two Tone Test**

3.0 V, 76 mA for LNA.

Input  $IP_3 = -10 + (65.5 / 2) = +22.8$  dBm

Output  $IP_3 = +22.8$  dBm + 9.8 dB gain = +32.6 dBm

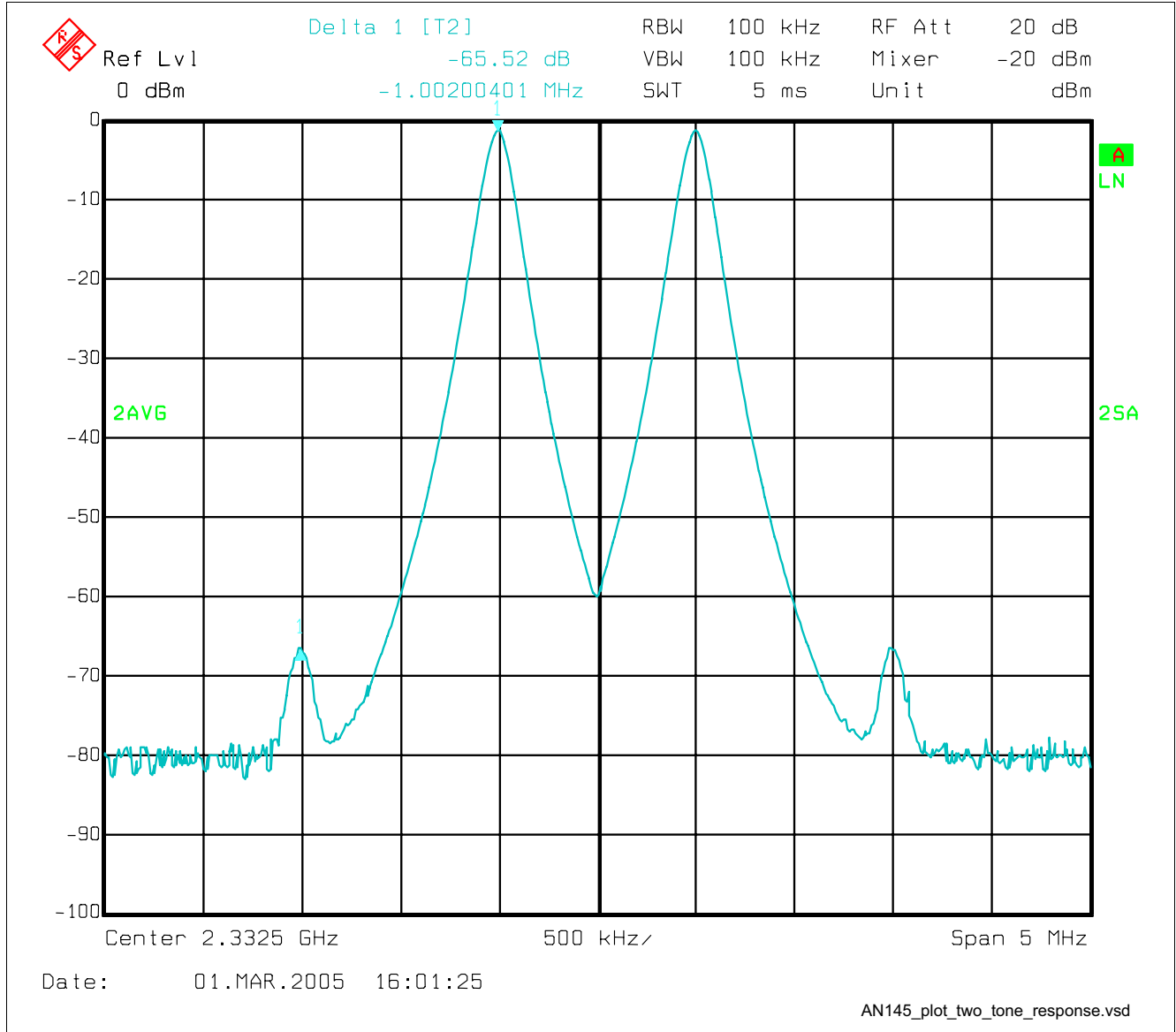

**Figure 15** Two-Tone Test, LNA Response