

# Application Note No. 146

Low Cost 950 - 2150 MHz Direct Broadcast  
Satellite (DBS) Amplifier with the BFP420F RF  
Transistor draws 27 mA from 5 V supply

RF & Protection Devices



Never stop thinking

**Edition 2008-02-21**

**Published by  
Infineon Technologies AG  
81726 München, Germany**

**© Infineon Technologies AG 2009.  
All Rights Reserved.**

#### **LEGAL DISCLAIMER**

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

#### **Information**

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

#### **Warnings**

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

---

**Application Note No. 146**

**Revision History: 2008-02-21, Rev. 1.2**

**Previous Version: 2005-09-19, Rev. 1.1**

<b>Page</b>	<b>Subjects (major changes since last revision)</b>
All	Small changes in figure descriptions

## Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

# 1 Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the BFP420F RF Transistor draws 27 mA from 5 V supply

## Overview

- BFP420F RF Transistor in TSFP-4 package is shown in a low-cost DBS IF Amplifier application. Amplifier uses resistive feedback (R2) to achieve stability and broadband matching. Package is 1.4 x 1.2 x 0.55 mm high.
- No chip coils are used to reduce cost; only resistors and capacitors are needed. "0402" size resistors and capacitors are used; total PCB area needed is 45 mm<sup>2</sup>; total parts count, including the BFP420F transistor, is 9 pieces.
- Printed Circuit Board used is Infineon Part Number 540F-041503 Rev A. Standard FR4 material is used in a two-layer PCB with 0.062 inch / 1.6 mm spacing between RF trace side and ground plane. Please refer to cross-sectional diagram of PCB below.
- The amplifier is unconditionally stable from 5 MHz to 5 GHz; K value dips to 0.88 at 6.5 GHz. See plot of stability factor "K" (Figure 8).

## Summary of Results


$T = 25\text{ }^{\circ}\text{C}$ , Network Analyzer Source Power  $\cong -25\text{ dBm}$ ,  $V_{CC} = 5.0\text{ V}$ ,  $I_C = 27.7\text{ mA}$ ,  $Z_S = Z_L = 50\text{ }\Omega$

**Table 1 Summary of Results**

Frequency MHz	dB [s11] <sup>2</sup>	dB [s21] <sup>2</sup>	dB [s12] <sup>2</sup>	dB [s22] <sup>2</sup>	NF* dB	IIP <sub>3</sub> dBm	OIP <sub>3</sub> dBm	IP <sub>1dB</sub> dBm	OP <sub>1dB</sub> dBm
950	16.7	17.3	23.0	19.7	2.2	---	---	---	---
1450	19.3	14.6	20.8	23.5	2.3	+8.3	+22.9	-4.5	+9.1
2150	17.4	12.0	17.3	19.3	2.5	---	---	---	---

\* PCB loss is not extracted, e.g. reference plane of measurement is at PCB input RF SMA connector. If PCB loss were extracted, noise figure result would improve by 0.1 - 0.2 dB, e.g. NF result would be lower / better.

## PCB Cross - Section Diagram

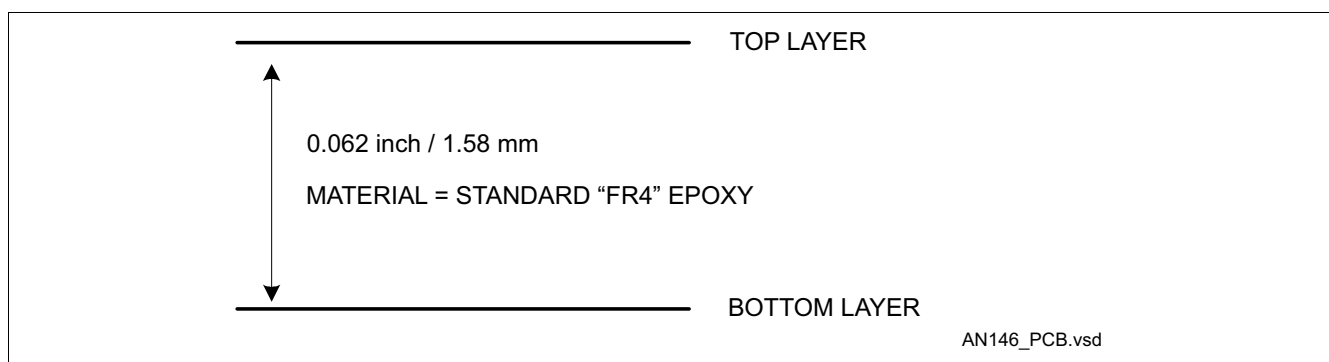

**Figure 1 PCB - Cross Sectional Diagram**

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Schematic Diagram

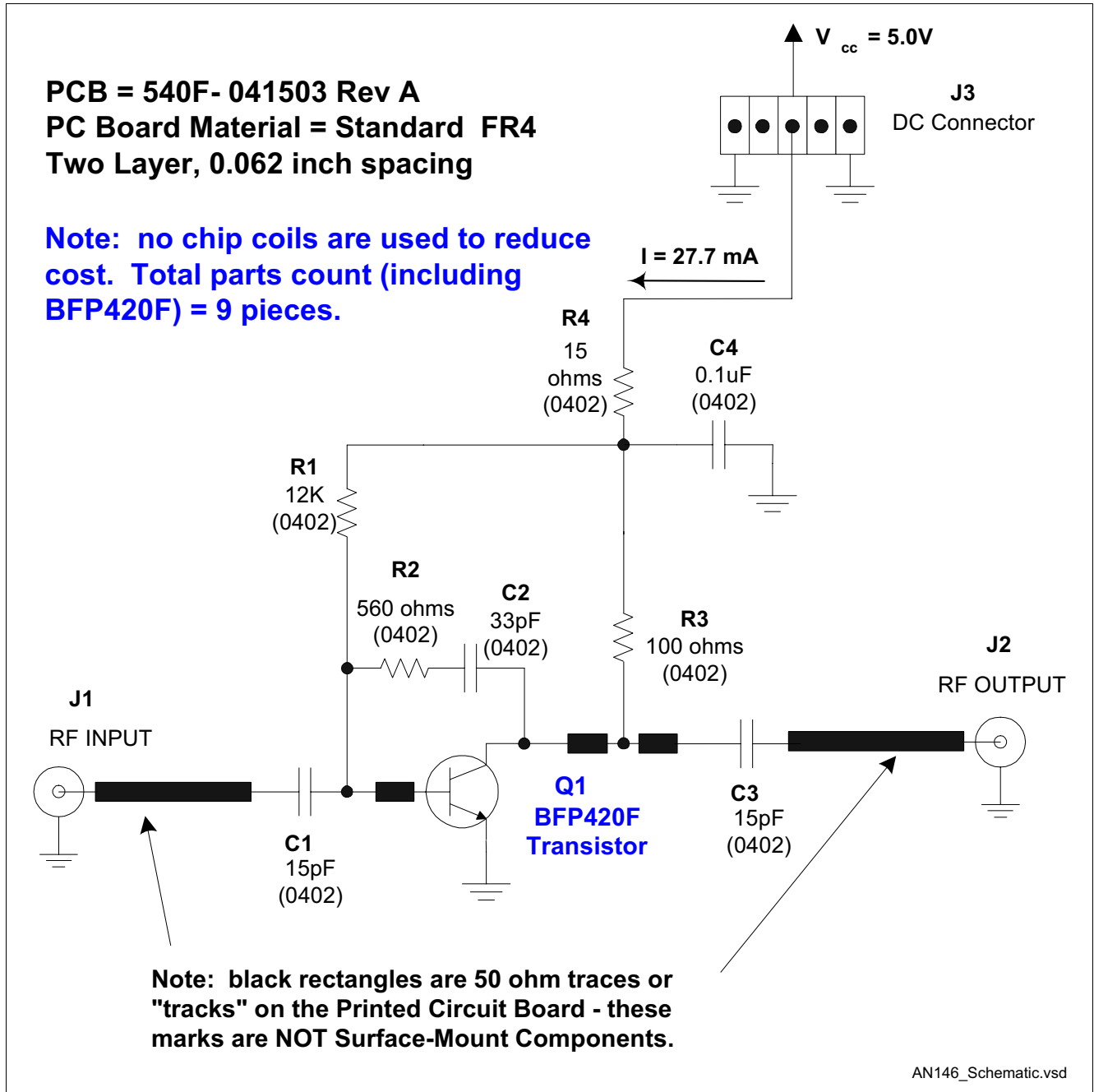


Figure 2 Schematic Diagram

## Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

## Bill of Material


Table 2 Bill of Material

Reference Designator	Value	Manufacturer	Case Size	Function
C1	15 pF	Various	0402	DC blocking, input.
C2	33 pF	Various	0402	DC block, for RF feedback path.
C3	15 pF	Various	0402	DC block, output.
C4	0.1 $\mu$ F	Various	0402	Decoupling
R1	12 k $\Omega$	Various	0402	Sets DC bias current.
R2	560 $\Omega$	Various	0402	RF feedback resistor. Feedback broadens matching and helps stabilize amplifier, at cost of reduced gain.
R3	100 $\Omega$	Various	0402	Brings DC to collector of BFP420F, used instead of a coil. Resistor loads output which degrades gain and output 1 dB compression point, but it improves output match, and is lower cost than a chip coil.
R4	15 $\Omega$	Various	0402	DC bias, provides slight negative feedback for DC operation point; helps stabilize collector current over variations in device DC current gain, over temperature, etc.
Q1	-	Infineon Technologies	TSFP-4	BFP420F B6HF Low Noise RF Transistor
J1, J2	-	Johnson 142-0701-841	-	RF input / output connectors
J3	-	AMP 5 pin header MTA-100 series 640456-5 (standard pin plating) or 641215-5 (gold plated pins)	-	DC connector  Pins 1, 5 = ground Pin 3 = $V_{CC}$ Pins 2, 4 = no connection

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**TSFP-4 Package Details**


(Dimensions in Millimeters). Note maximum package height is 0.59 mm / 0.023 inch.

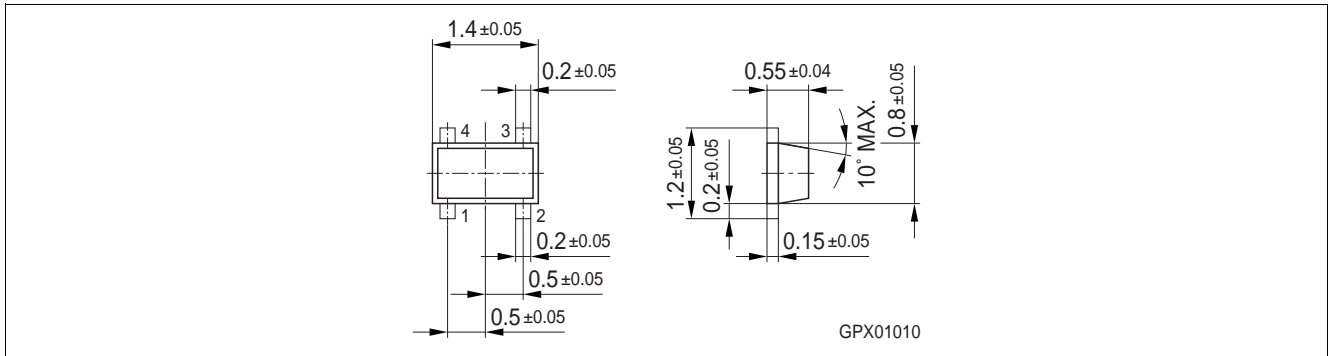

**Figure 3 Package Details of TSFP-4**

**Recommended Soldering Footprint for TSFP-4 (dimensions in millimeters).**

Device package is to be oriented as shown in above drawing (e.g. orient long package dimension horizontally on this footprint).

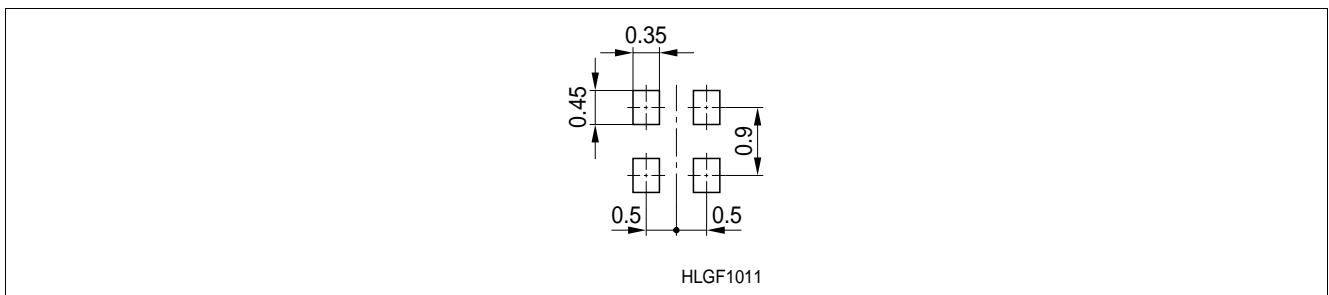

**Figure 4 Package Footprint of TSFP-4**

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Noise Figure, Plot, Center of Plot (x-axis) is 1575 MHz.

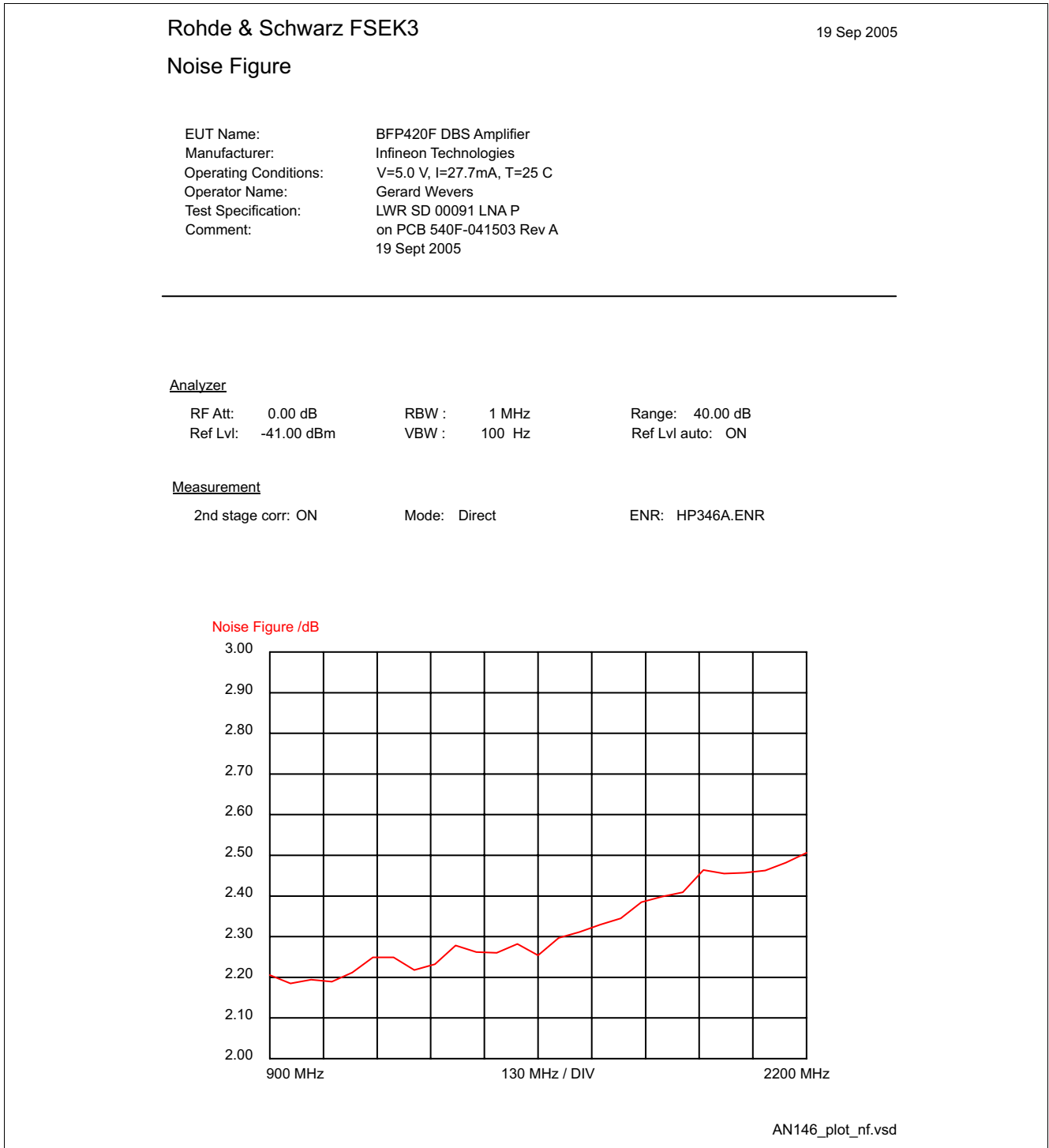


Figure 5 Noise Figure



Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Noise Figure, Tabular Data**

From Rohde & Schwarz FSEK3 + FSEM30 + System Preamplifier  
 System Preamplifier = MITEQ SMC-02

**Table 3 Noise Figure**

Frequency	Noise Figure
900 MHz	2.21 dB
950 MHz	2.18 dB
1000 MHz	2.19 dB
1050 MHz	2.19 dB
1100 MHz	2.21 dB
1150 MHz	2.25 dB
1200 MHz	2.25 dB
1250 MHz	2.22 dB
1300 MHz	2.23 dB
1350 MHz	2.28 dB
1400 MHz	2.26 dB
1450 MHz	2.26 dB
1500 MHz	2.28 dB
1550 MHz	2.25 dB
1600 MHz	2.30 dB
1650 MHz	2.31 dB
1700 MHz	2.33 dB
1750 MHz	2.34 dB
1800 MHz	2.39 dB
1850 MHz	2.40 dB
1900 MHz	2.41 dB
1950 MHz	2.46 dB
2000 MHz	2.45 dB
2050 MHz	2.46 dB
2100 MHz	2.46 dB
2150 MHz	2.48 dB
2200 MHz	2.51 dB

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Scanned Image of PC Board

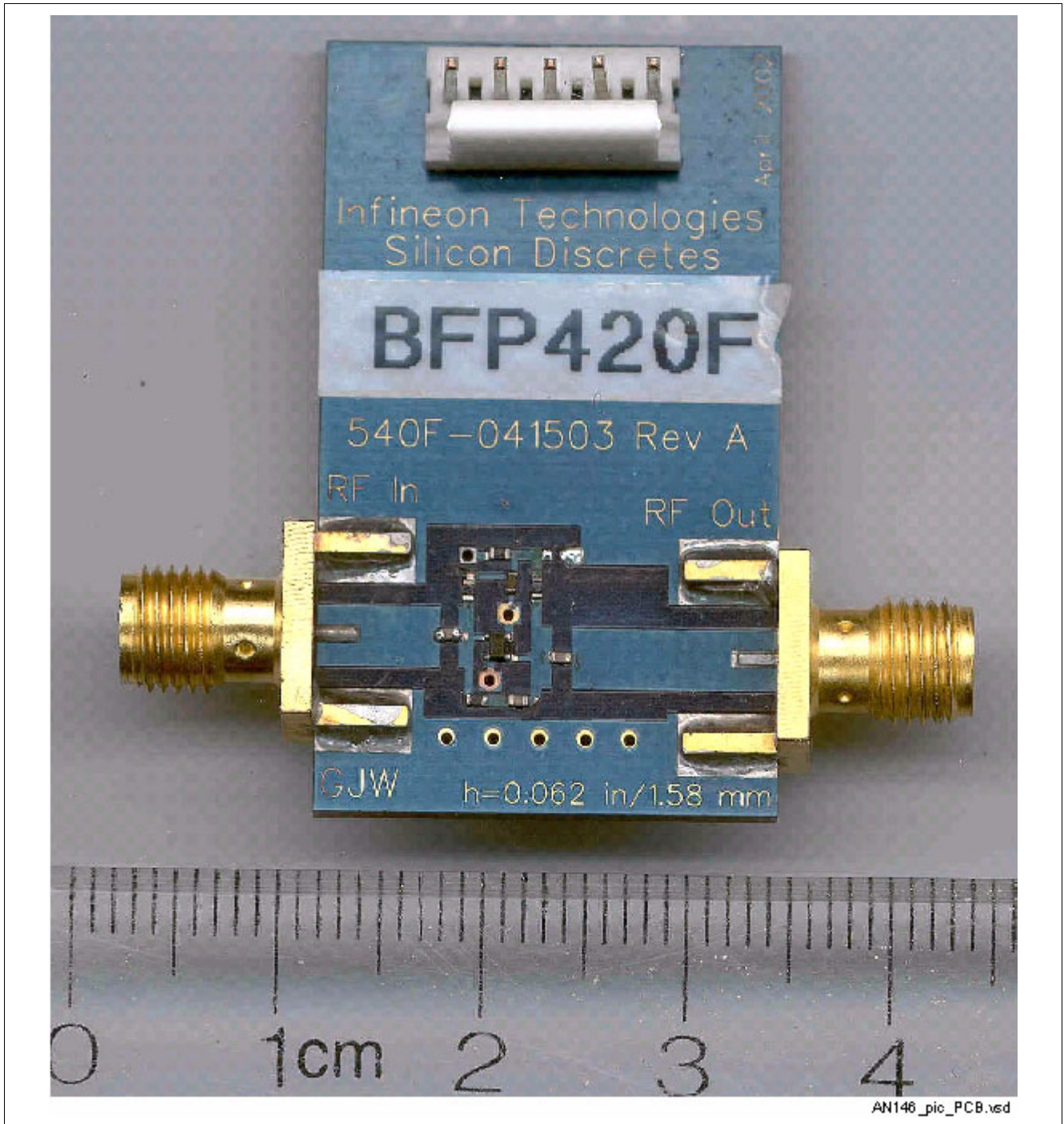


Figure 6 Image of PC Board

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Scanned Image of PC Board, Close-In Shot.

Total PCB area used is approximately 45 mm<sup>2</sup>.

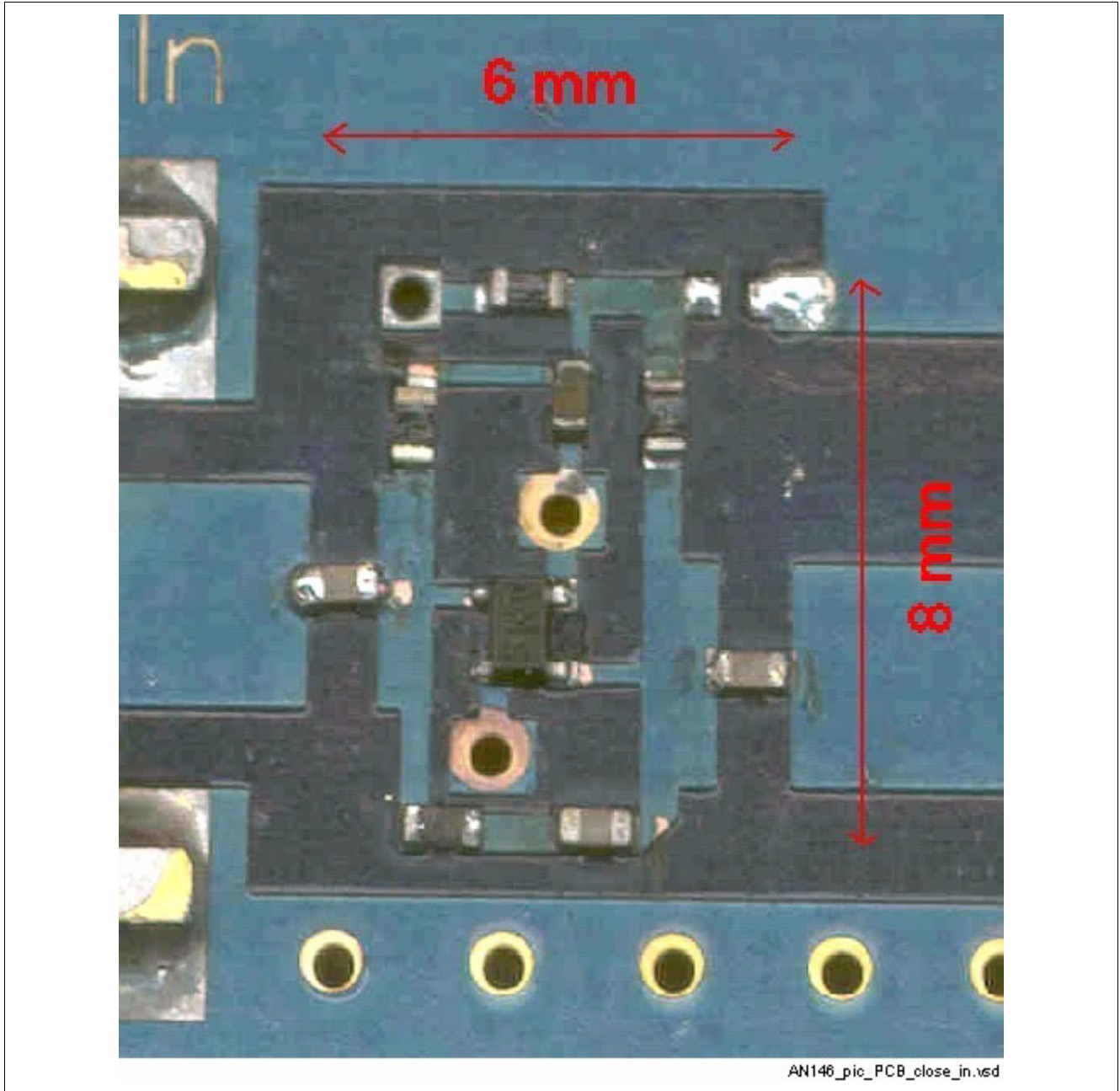



Figure 7 Image of PC Board, Close-In Shot

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Amplifier Stability**

$T = 25\text{ }^{\circ}\text{C}$ ,  $V_{CC} = 1.8\text{ V}$ ,  $V_{CE} = 1.9\text{ V}$ ,  $I = 27.7\text{ mA}$

Stability Factor "K" is shown below from "screen shot" taken from Rohde and Schwarz ZVC network analyzer. ZVC Vector Network Analyzer calculates and plots K in real time, from measured S parameters. Note that  $K > 1$  up to 5 GHz, with minimum K value is 0.89 at 6.5 GHz; the amplifier is unconditionally stable over 5 MHz to 5 GHz range, and conditionally stable for  $5\text{ GHz} < f < 7\text{ GHz}$ .

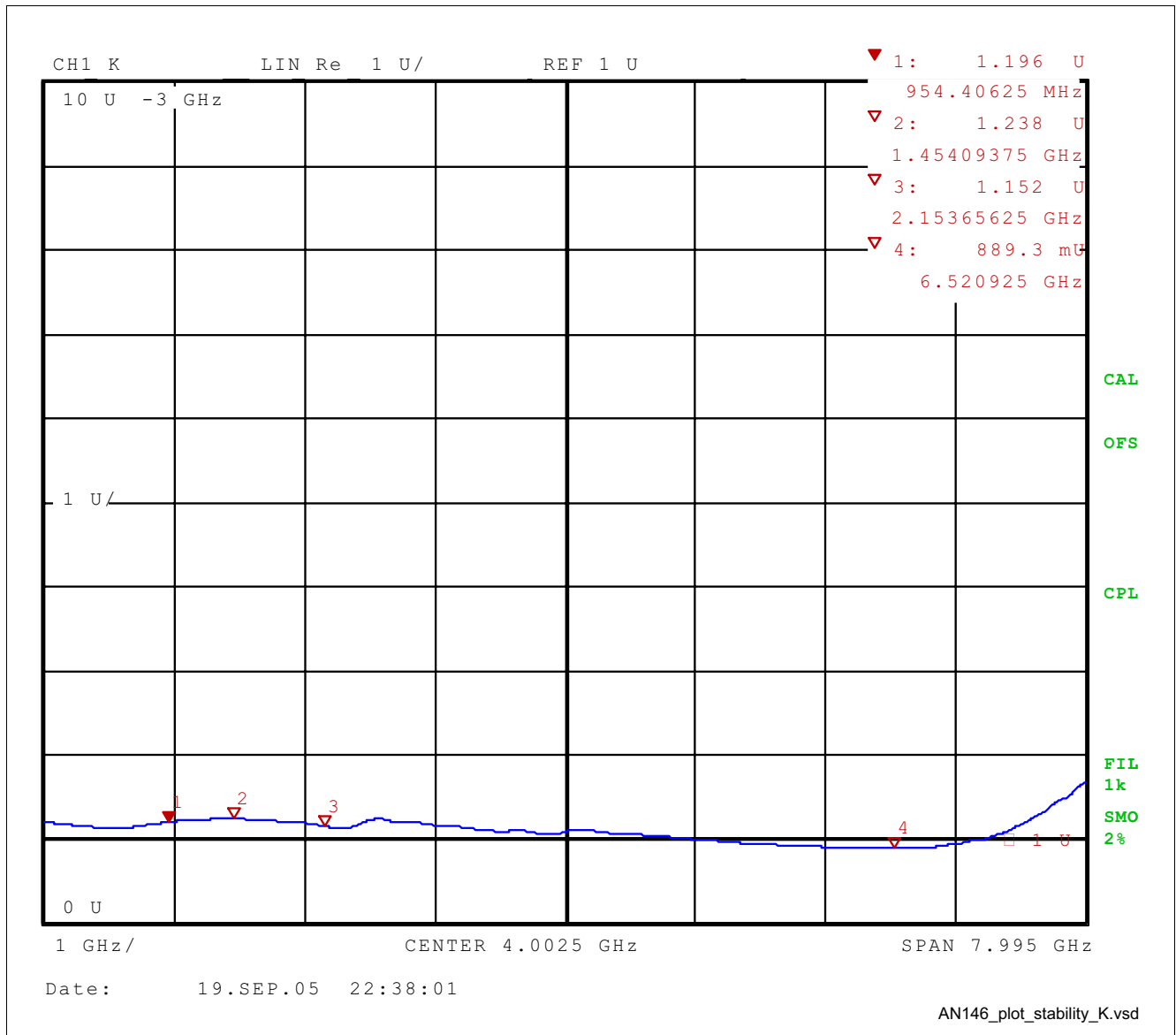

**Figure 8 Plot of K(f)**

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Gain Compression at 1450 MHz**


$T = 25\text{ }^{\circ}\text{C}$ ,  $V_{CC} = 5.0\text{ V}$ ,  $V_{CE} = 1.9\text{ V}$ ,  $I = 27.7\text{ mA}$

Amplifier is checked for 1 dB compression point. An Agilent power meter was used to ensure accurate power levels are measured (as opposed to using Vector Network Analyzer in "Power Sweep" mode).

Output  $P_{1dB} \cong +9.1\text{ dBm}$ ; Input  $P_{1dB} \cong +9.1\text{ dBm} - (\text{Gain} - 1\text{ dB}) = +9.1\text{ dBm} - 13.6\text{ dB} = -4.5\text{ dBm}$

**Table 4 Gain Compression**

$P_{OUT}$ , dBm	Gain, dB
-4.0	14.6
-3.0	14.6
-2.0	14.6
-1.0	14.6
0.0	14.6
+1.0	14.5
+2.0	14.5
+3.0	14.5
+4.0	14.5
+5.0	14.4
+6.0	14.4
+7.0	14.3
+8.0	14.1
+9.0	13.7
+10.0	12.1

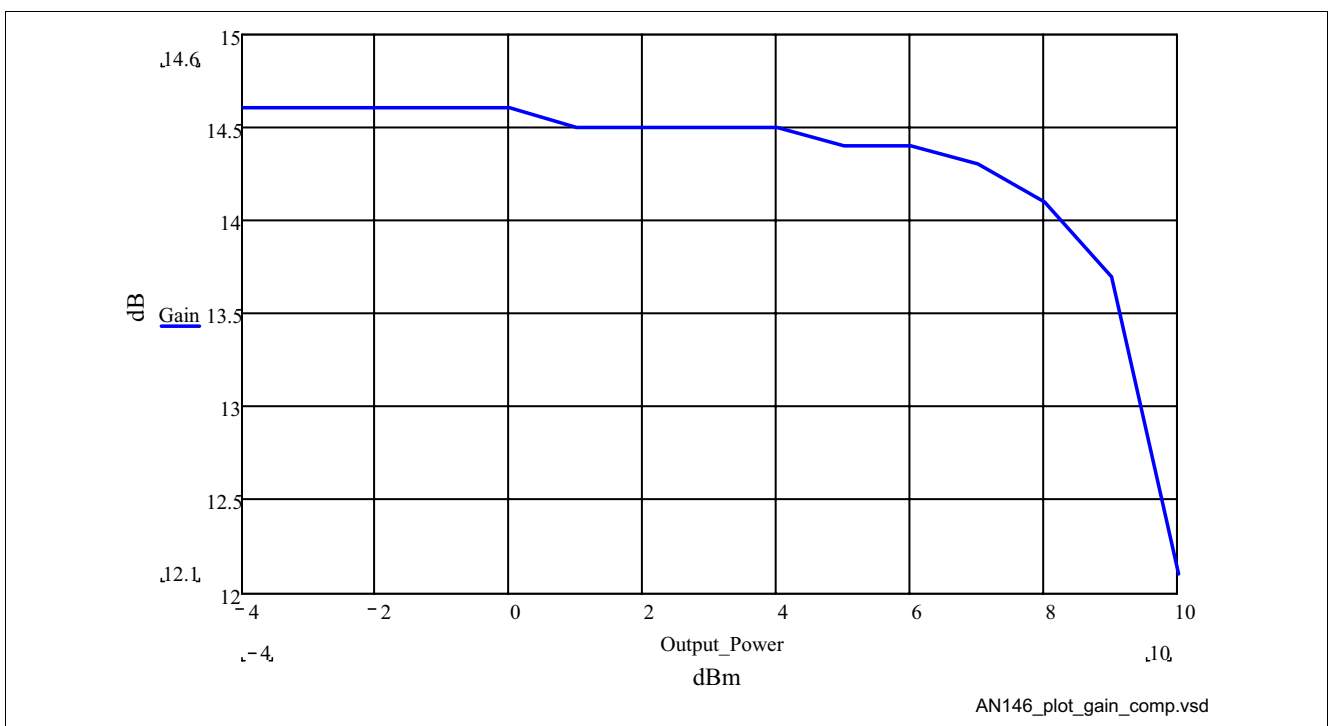


**Figure 9 Plot of BFP420F Gain Compression, 1450 MHz**

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Please Note - all plots are taken from ZVC Network Analyzer,  $T = 25\text{ }^{\circ}\text{C}$ , source power  $\approx -25\text{ dBm}$ .

**Input Return Loss, Log Mag**

5 MHz - 8 GHz Sweep

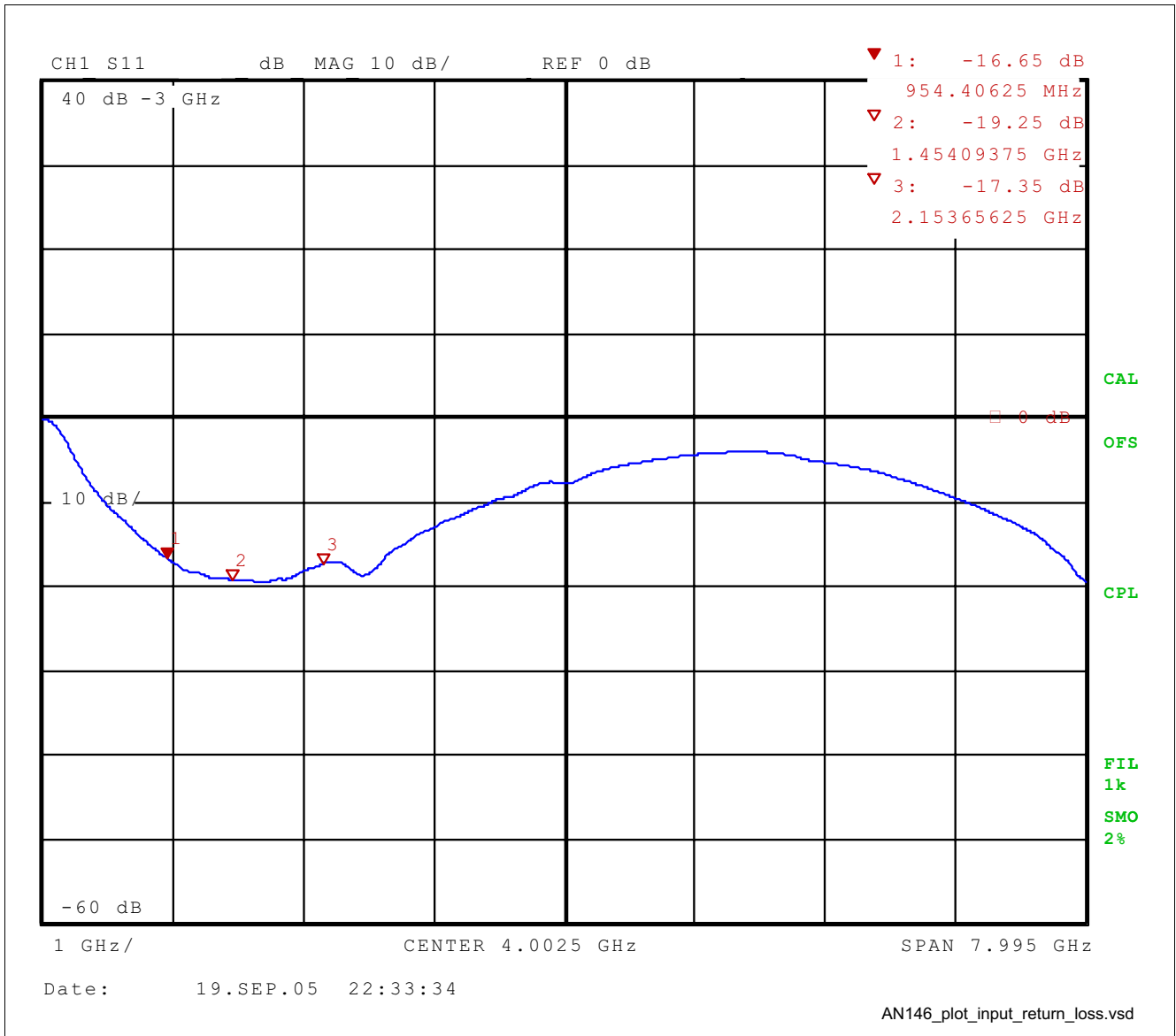


**Figure 10 Plot of Input Return Loss**

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Input Return Loss, Smith Chart**

Reference Plane = Input SMA Connector on PC Board  
 5 MHz - 8 GHz Sweep

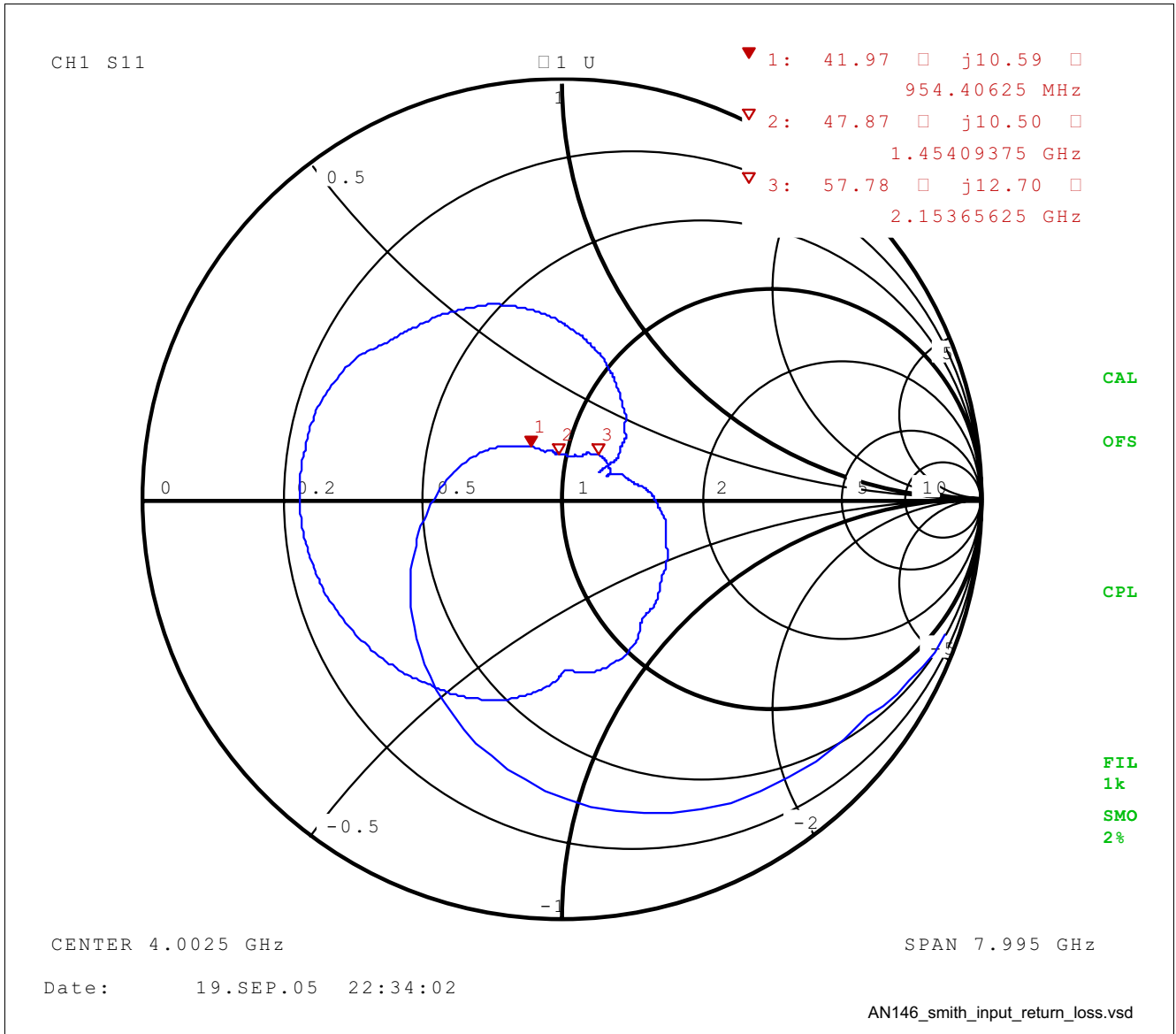


**Figure 11 Smith Chart of Input Return Loss**

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Forward Gain**

5 MHz - 8 GHz Sweep

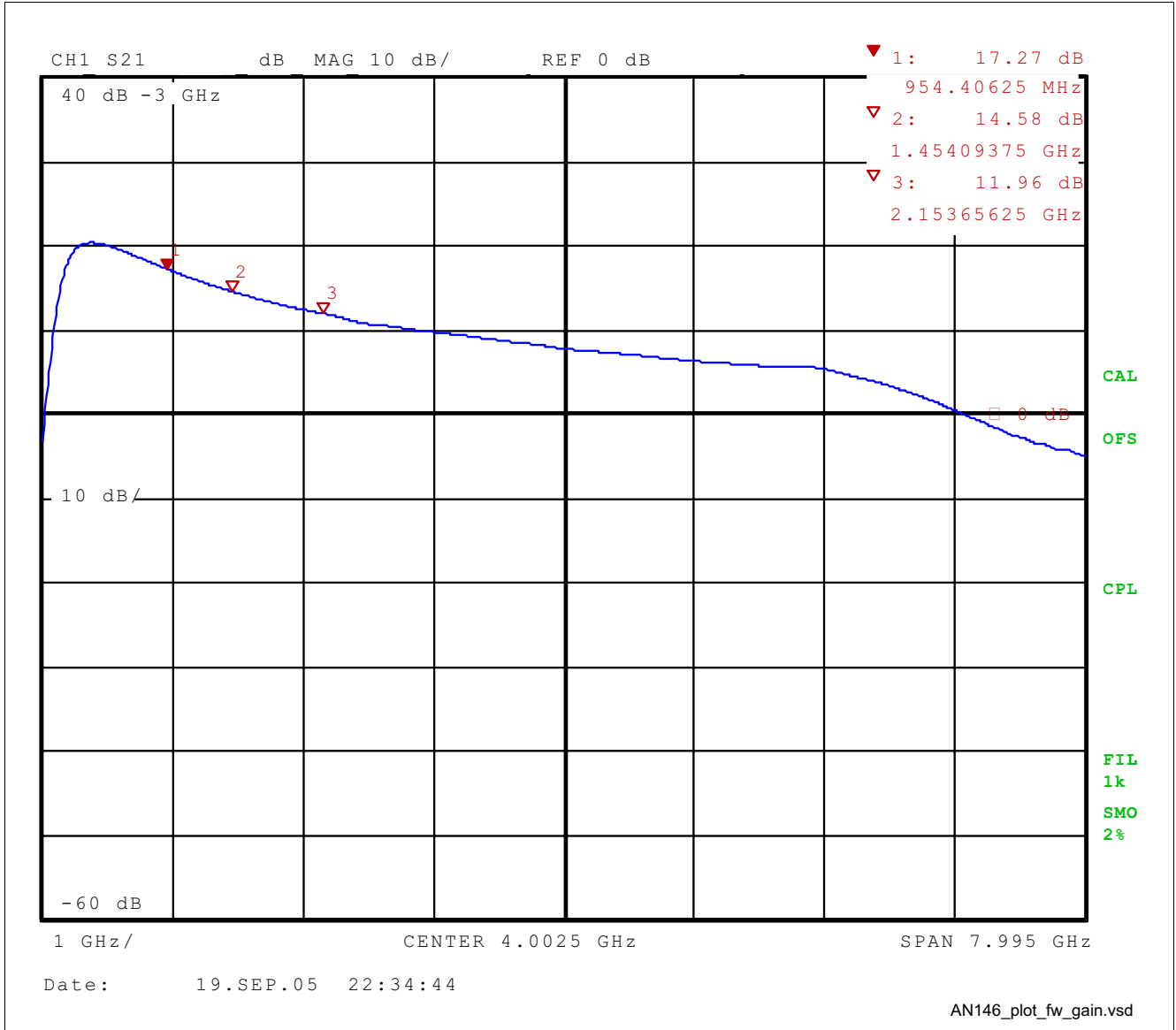

**Figure 12 Plot of Forward Gain**



Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Reverse Isolation

5 MHz - 8 GHz

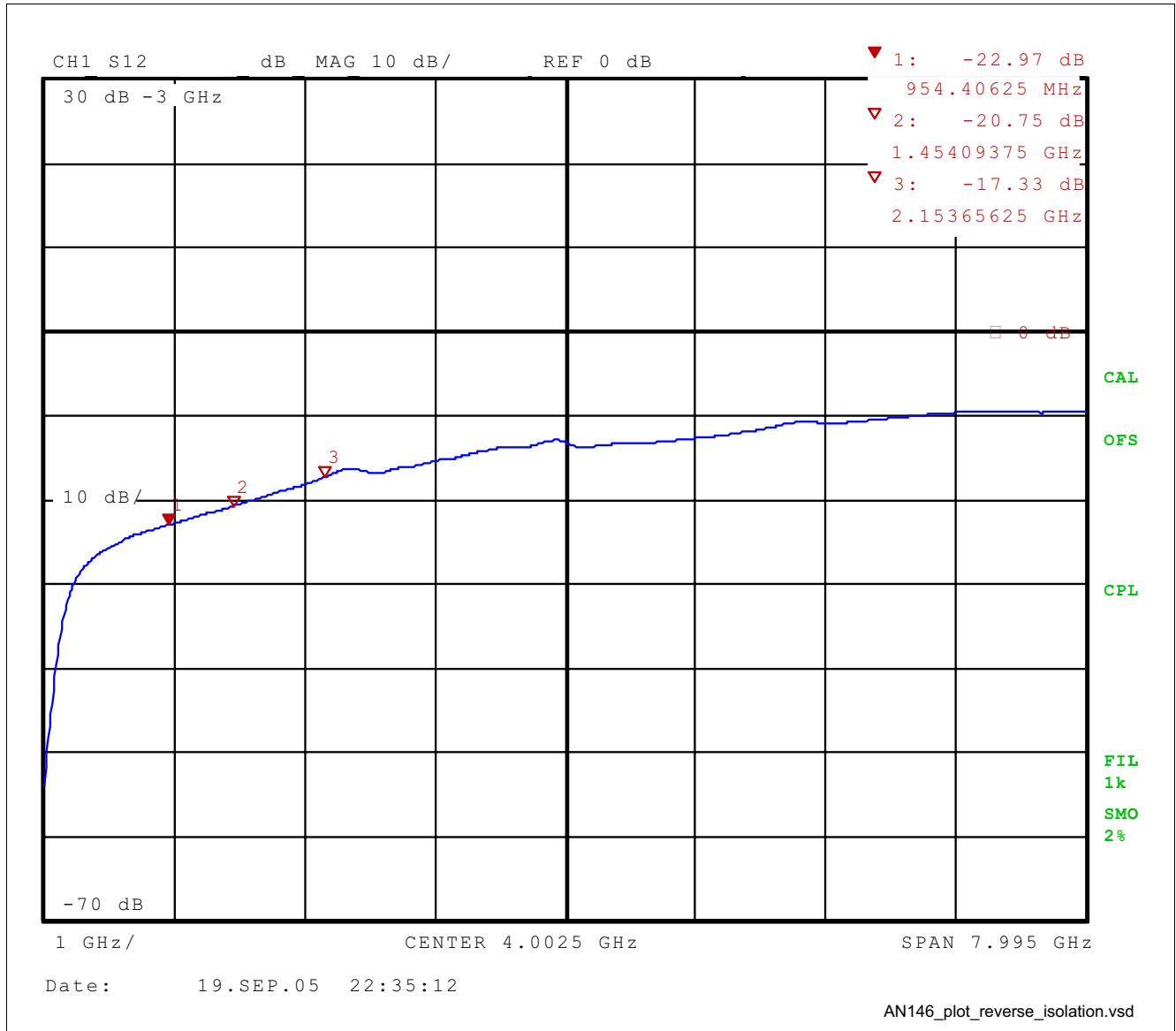


Figure 13 Plot of Reverse Isolation

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

Output Return Loss, Log Mag

5 MHz - 8 GHz


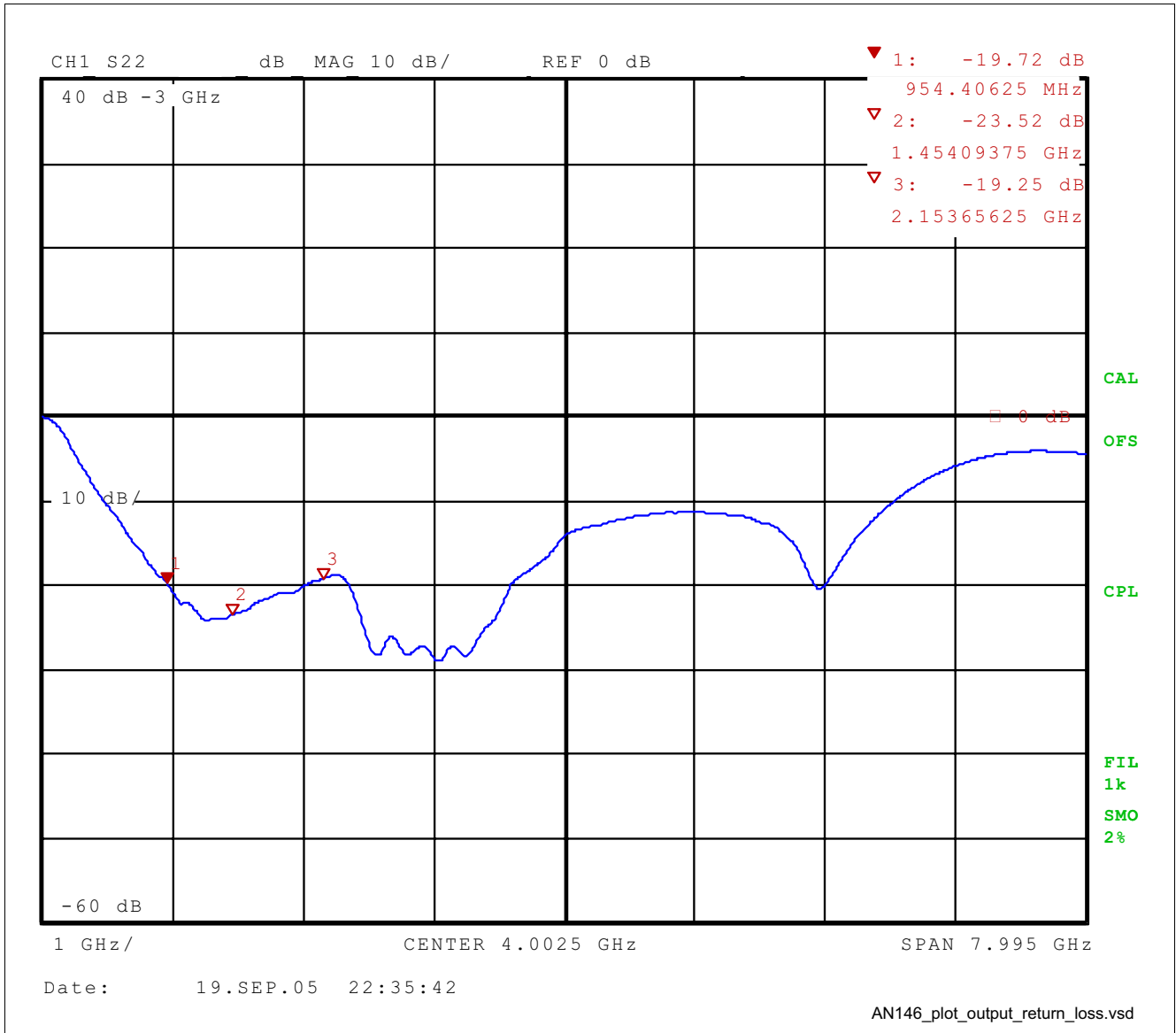


Figure 14 Plot of Output Return Loss

Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Output Return Loss, Smith Chart**

Reference Plane = Output SMA Connector on PC Board  
5 MHz - 8 GHz Sweep

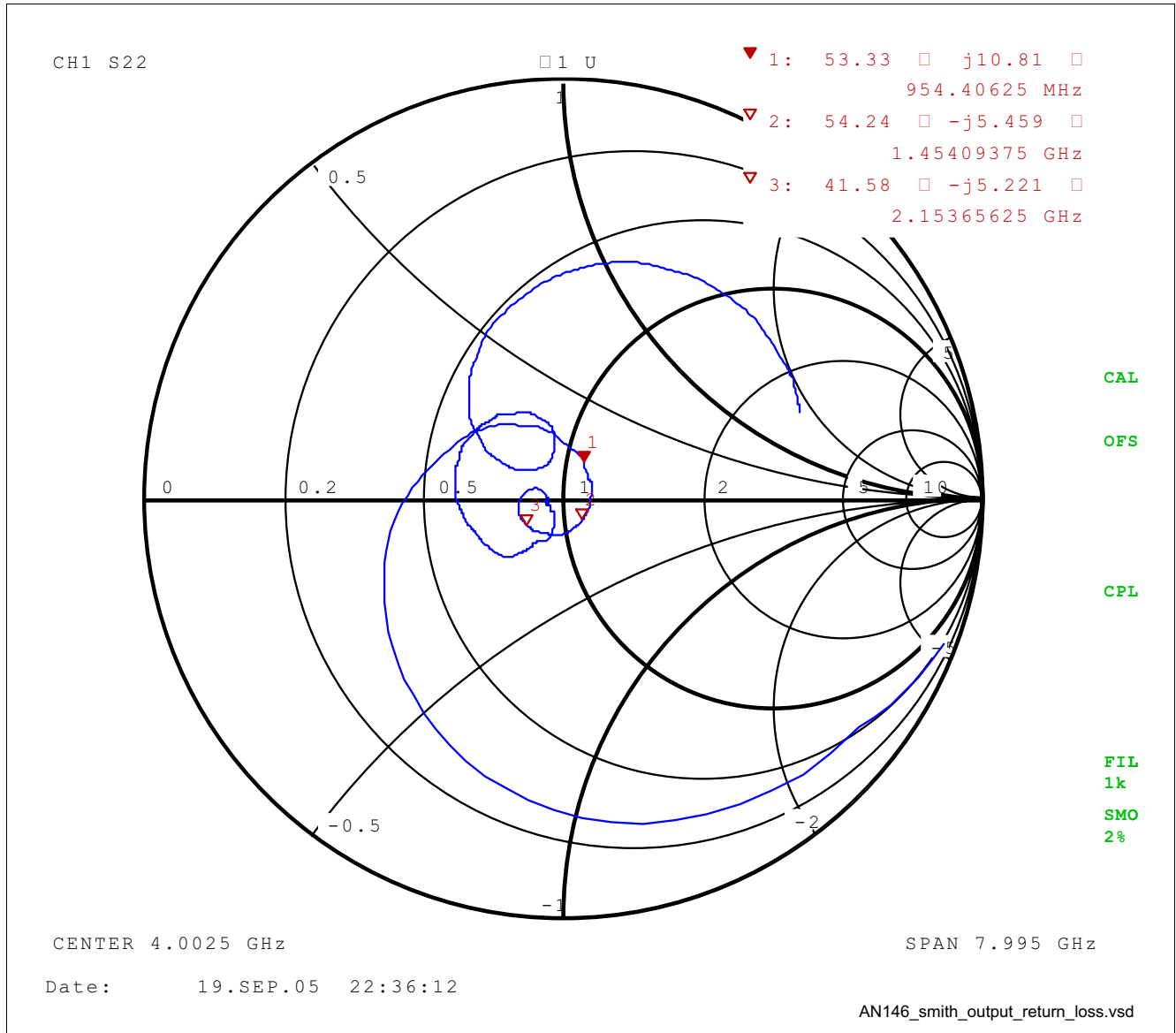

**Figure 15** Smith Chart of Output Return Loss


Low Cost 950 - 2150 MHz Direct Broadcast Satellite (DBS) Amplifier with the

**Amplifier response to Two Tone Test**

Input stimulus:  $f_1 = 1450 \text{ MHz}$ ,  $f_2 = 1451 \text{ MHz}$ ,  $-20 \text{ dBm}$  each tone.

Input  $IP_3 = -20 + (56.6 / 2) = +8.3 \text{ dBm}$

Output  $IP_3 = +8.3 \text{ dBm} + 14.6 \text{ dB gain} = +22.9 \text{ dBm}$

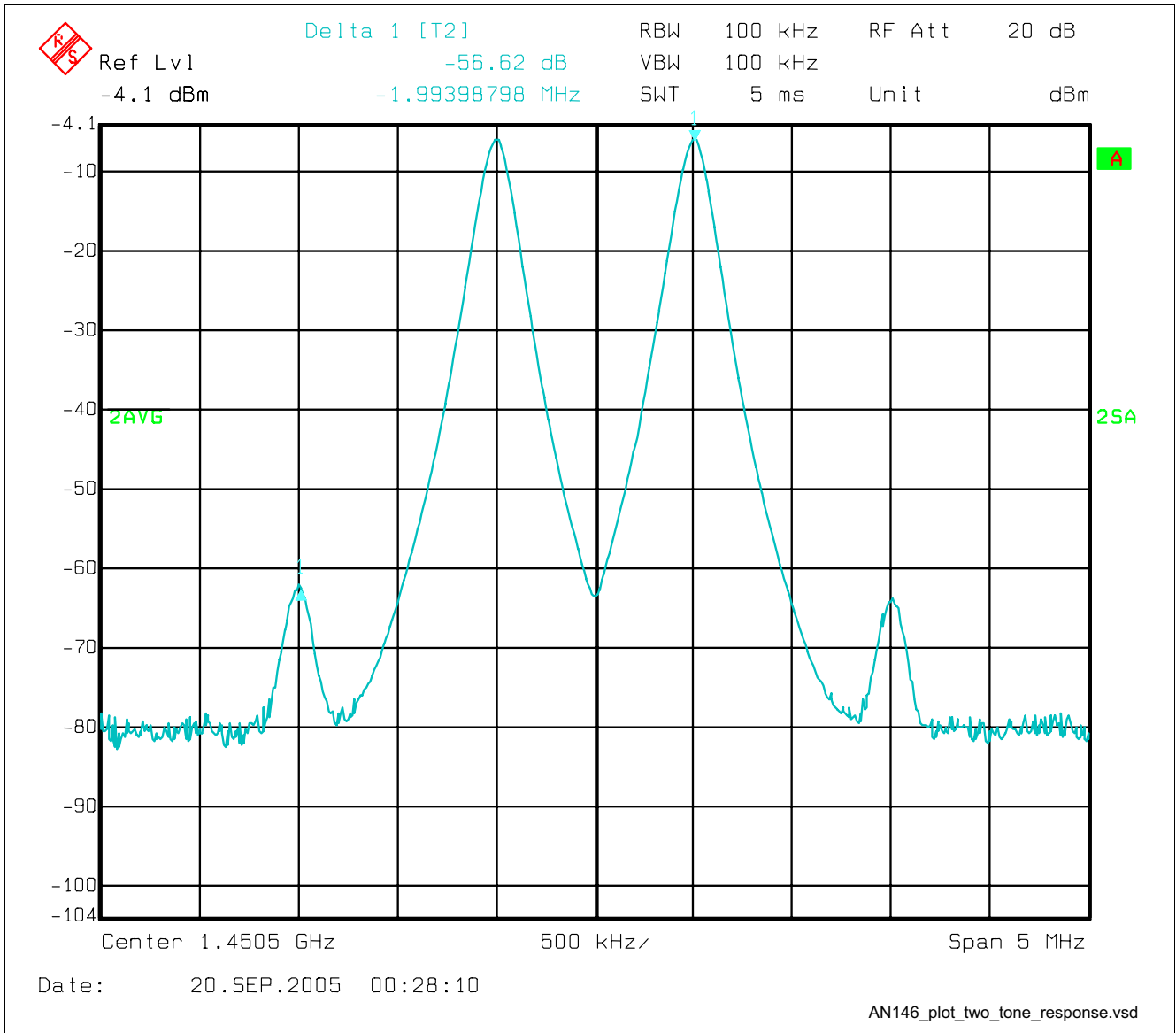

**Figure 16 Two-Tone Test, LNA Response**