

Application Note No. 158

The BFP420 Transistor as a Low-Cost 900 MHz
ISM Band Power Amplifier

RF & Protection Devices



Never stop thinking

Edition 2008-02-27

**Published by
Infineon Technologies AG
81726 München, Germany**

**© Infineon Technologies AG 2009.
All Rights Reserved.**

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Application Note No. 158

Revision History: 2008-02-27, Rev. 1.2

Previous Version: 2000-04-12, Rev. 1.1

Page	Subjects (major changes since last revision)
All	Small changes in figure descriptions

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

1 The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Overview

- The BFP420 is shown in a 902 - 928 MHz Class A Power Amplifier for a cordless phone application. The PC Board used is the BFP620 V3.0 PCB with "sawed-off" inputs and outputs. Low cost components are used (e.g. Murata LQG10A chip inductors) and effort was made to minimize external parts count - a total of 10 external SMT components were used, not including a jumper or DC and RF connectors.
- Test Conditions: $V_{CC} = 3.0\text{ V}$, $I = 33.1\text{ mA}$, $V_{CE} = 2.8\text{ V}$, $T = 25\text{ }^{\circ}\text{C}$.
- Comments: Inductive emitter degeneration is used to reduce excess gain and improve linearity. Two microstripline inductors are used, between each device ground lead and PCB ground plane. Amplifier is shy on 1 dB compression point. BFP420 maximum safe continuous current = 35 mA. Improvement in $P_{1\text{dB}}$ and DC efficiency could be achieved with Class AB bias to amplifier, provided modulation format being used is constant-envelope (e.g. modulation format tolerant of mild levels of PA distortion).

Summary of Data

Table 1 Summary of Data

Parameter	Result / Value 869 MHz
Frequency Range	902 - 928 MHz
DC Current	33.1 mA
DC Voltage, V_{CC}	3.0 V
Input $P_{1\text{dB}}$	$\approx -6.7\text{ dBm @ }915\text{ MHz}$
Output $P_{1\text{dB}}$	$\approx +13.0\text{ dBm @ }902\text{ MHz}$ $\approx +13.1\text{ dBm @ }915\text{ MHz}$ $\approx +13.1\text{ dBm @ }928\text{ MHz}$
Input 3 rd Order Intercept	+5.0 dBm @ 915 MHz
Output 3 rd Order Intercept	+25.8 dBm @ 915 MHz
Noise Figure	2.50 dB @ 902 MHz 2.50 dB @ 915 MHz 2.53 dB @ 928 MHz
Gain	20.7 dB @ 902 MHz 20.8 dB @ 915 MHz 20.8 dB @ 928 MHz
Input return loss	16.5 dB @ 902 MHz 16.1 dB @ 915 MHz 15.7 dB @ 928 MHz
Output return loss	19.2 dB @ 902 MHz 21.0 dB @ 915 MHz 20.4 dB @ 928 MHz
Reverse isolation	28.6 dB @ 902 MHz 27.5 dB @ 915 MHz 27.3 dB @ 928 MHz

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Schematic Diagram

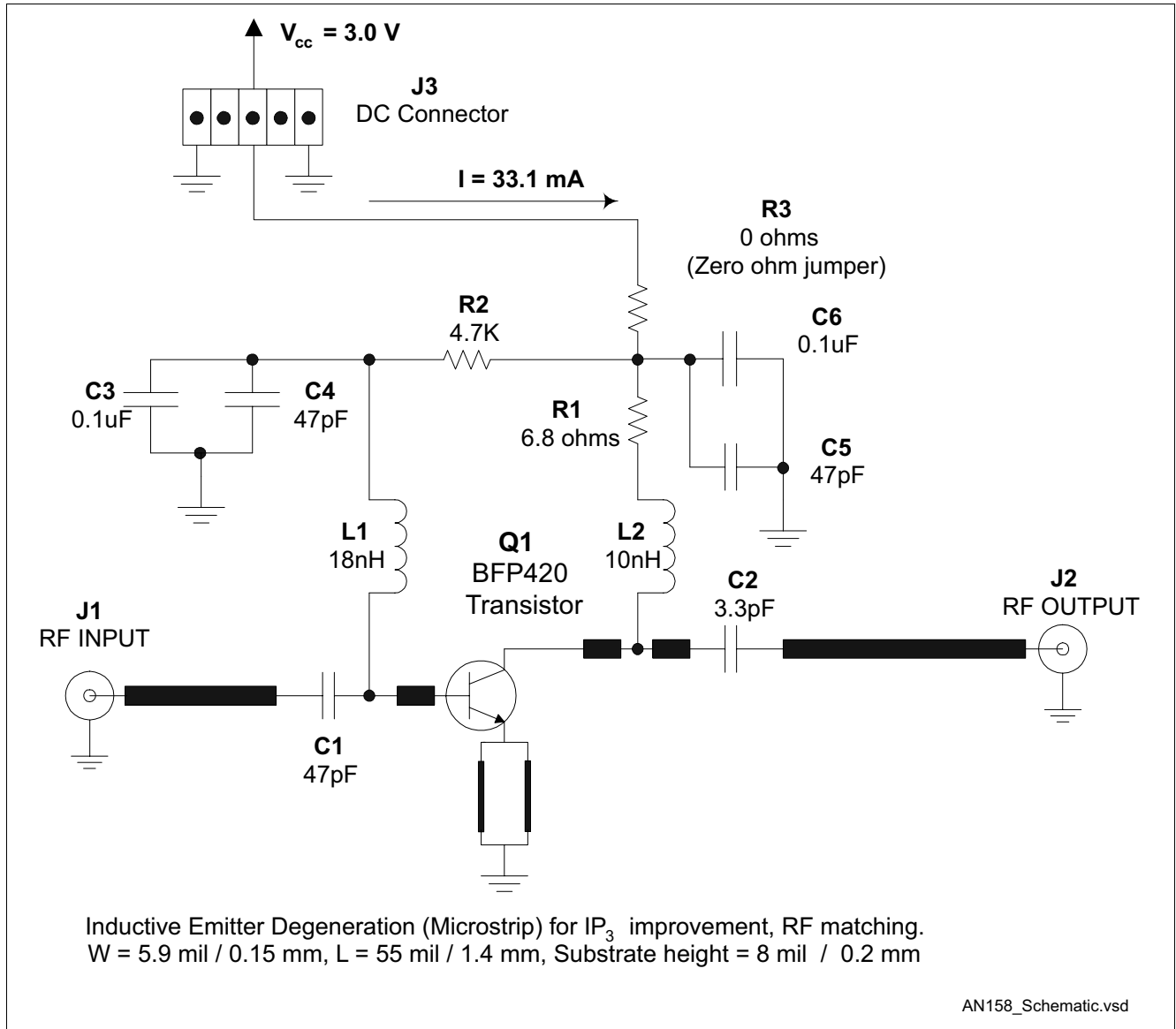


Figure 1 Schematic Diagram

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Bill of Material

Table 2 Bill of Material

Reference Designator	Value	Manufacturer	Case Size	Function
C1	47 pF	Various	0402	Input DC block
C2	3.3 pF	Various	0402	Output DC block, output RF matching.
C3	0.1 μ F	Various	0402	Low frequency ground at base (Input 3 rd Order Intercept improvement).
C4	47 pF	Various	0402	RF bypass / RF block
C5	47 pF	Various	0402	RF bypass / RF block
C6	0.1 μ F	Various	0603	Bypass / block
L1	18 nH	Murata LQG10A	0402	RF choke to DC bias on base, input matching.
L2	10 nH	Murata LQG10A	0402	Output RF match, DC feed to collector.
R1	6.8 Ω	Various	0402	Stability, output matching.
R2	4.7 k Ω	Various	0402	DC bias for base.
R3	0 Ω	Various	0603	Just a jumper.
Q1	-	Infineon Technologies	SOT343	BFP420 transistor, $f_T = 25$ GHz
J1, J2	-	Johnson 142-0701-841	-	RF input / output connectors
J3	-	AMP 5 pin header MTA-100 series 640456-5 (standard pin plating) or 641215-5 (gold plated pins)	-	DC connector Pins 1, 5 = ground Pin 3 = V_{CC} Pins 2, 4 = no connection

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Noise Figure, Plot. Center of Plot (x-axis) is 915 MHz.

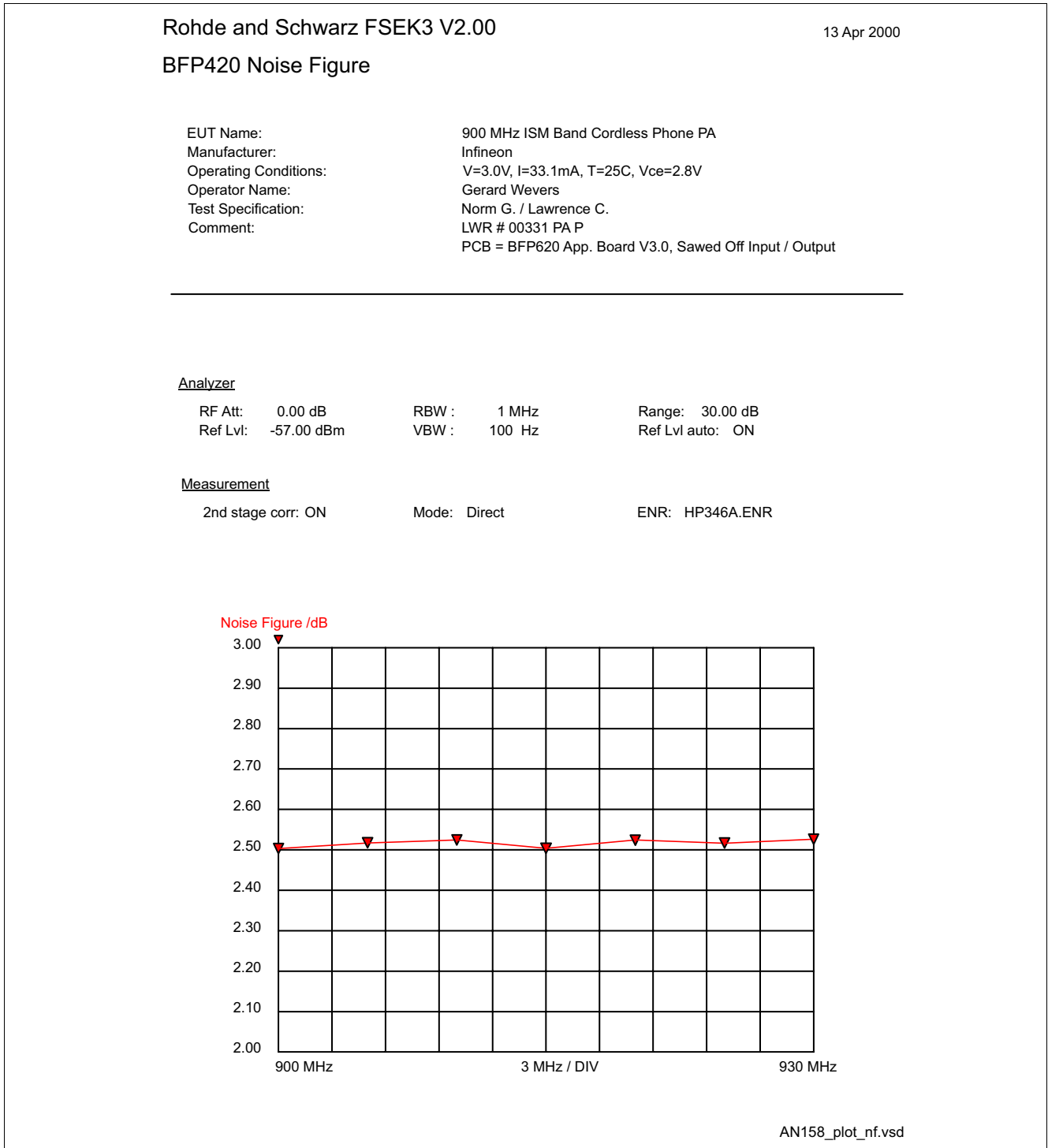


Figure 2 Noise Figure

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier**Noise Figure, Tabular Data****Table 3 Noise Figure**

Frequency	Noise Figure
900 MHz	2.50 dB
905 MHz	2.52 dB
910 MHz	2.52 dB
915 MHz	2.50 dB
920 MHz	2.52 dB
925 MHz	2.52 dB
930 MHz	2.53 dB

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Amplifier Gain Compression at 902, 915 and 928 MHz

Input $P_{1dB} \cong -6.7$ dBm @ 915 MHz

Output $P_{1dB} \cong +13.1$ dBm @ 915 MHz

Table 4 Gain Compression Test, $T = 25$ °C

Output Power, dBm	Gain @ 902 MHz, dB	Gain @ 915 MHz, dB	Gain @ 928 MHz, dB
+5	20.7	20.8	20.8
+6	20.7	20.8	20.8
+7	20.7	20.8	20.8
+8	20.7	20.8	20.7
+9	20.6	20.7	20.7
+10	20.5	20.6	20.6
+11	20.4	20.5	20.5
+12	20.2	20.2	20.2
+13	19.7	19.9	19.9
+14	18.8	19.2	19.3
+15	16.1	17.0	17.4

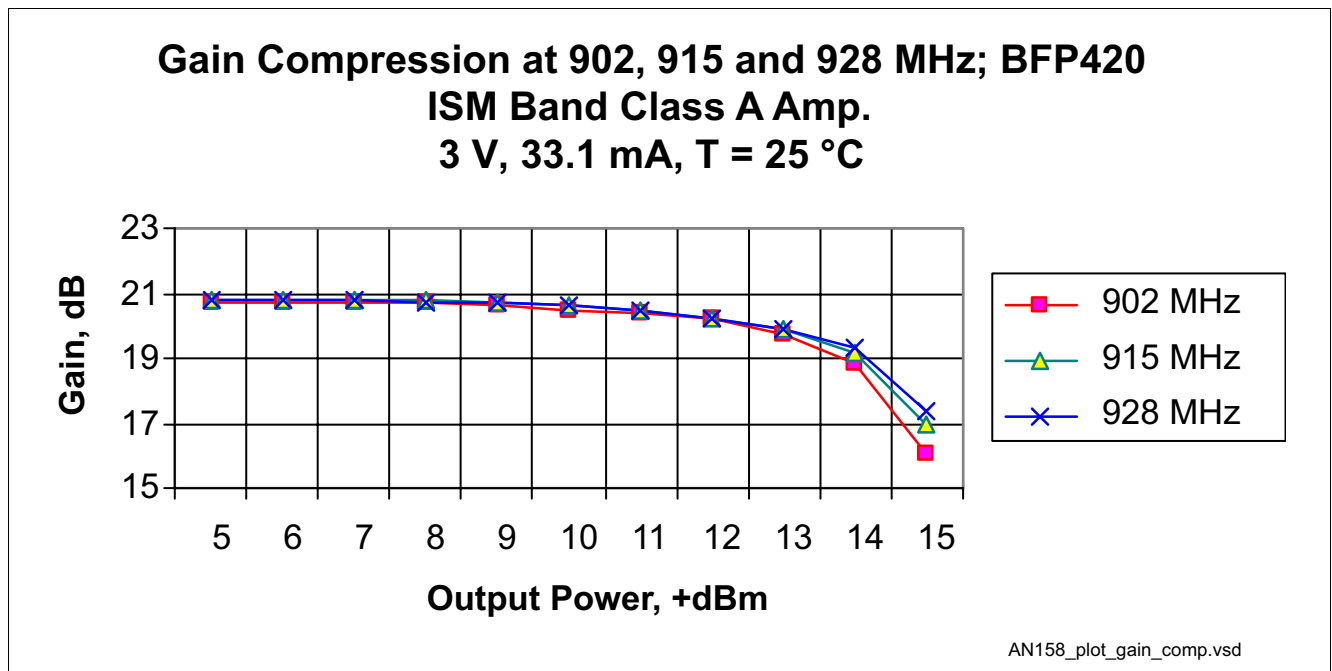


Figure 3 Plot of Gain Compression

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Stability Factors K and B₁

Measured s-parameter file from actual PCB is imported into Ansoft Harmonica V8.0, which then calculates K and B₁. For unconditional stability, K > 1 AND B₁ > 0.

Note red trace is K, blue trace is B₁.

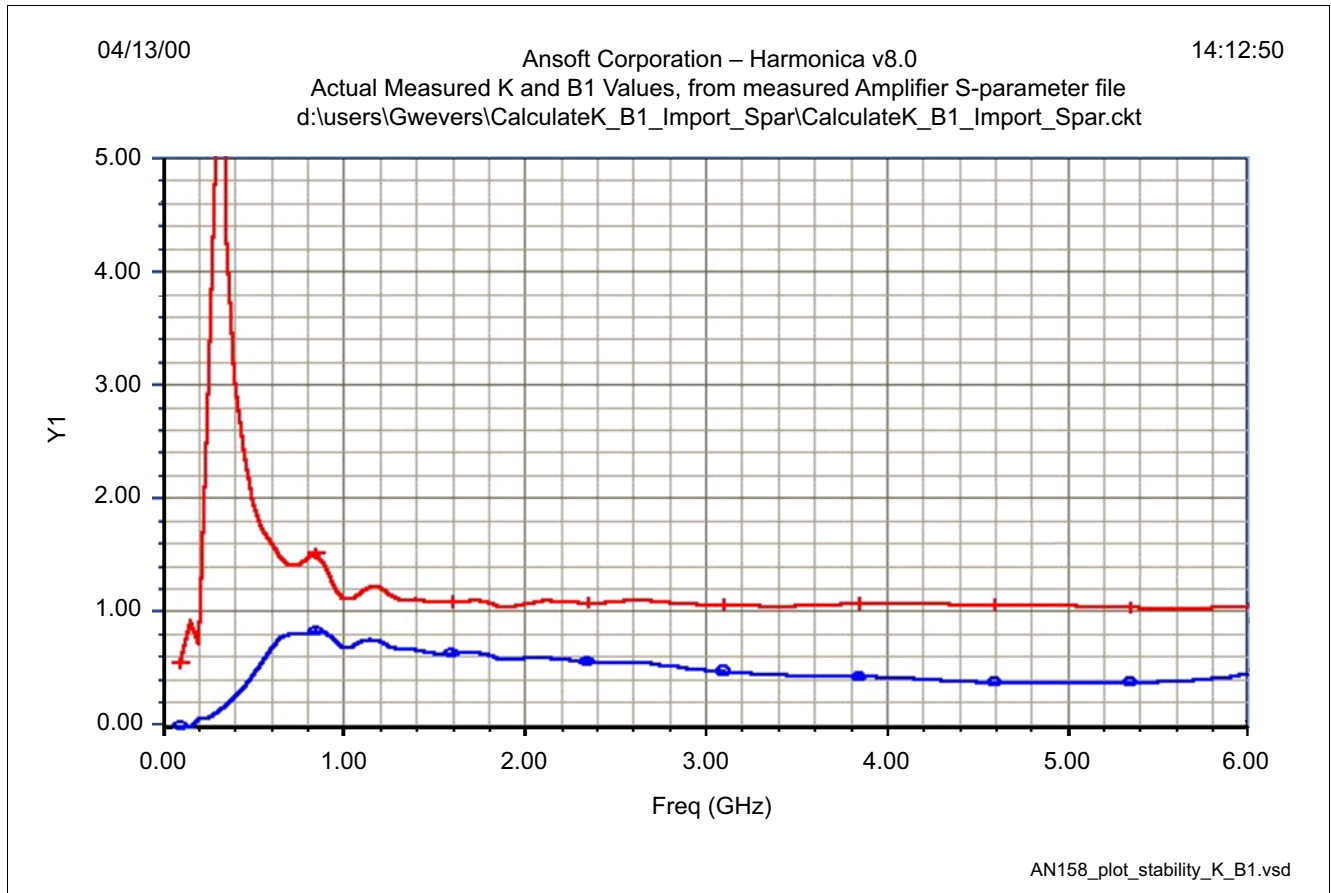


Figure 4 Plot of K(f) and B₁(f)

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Scanned Image of PCB

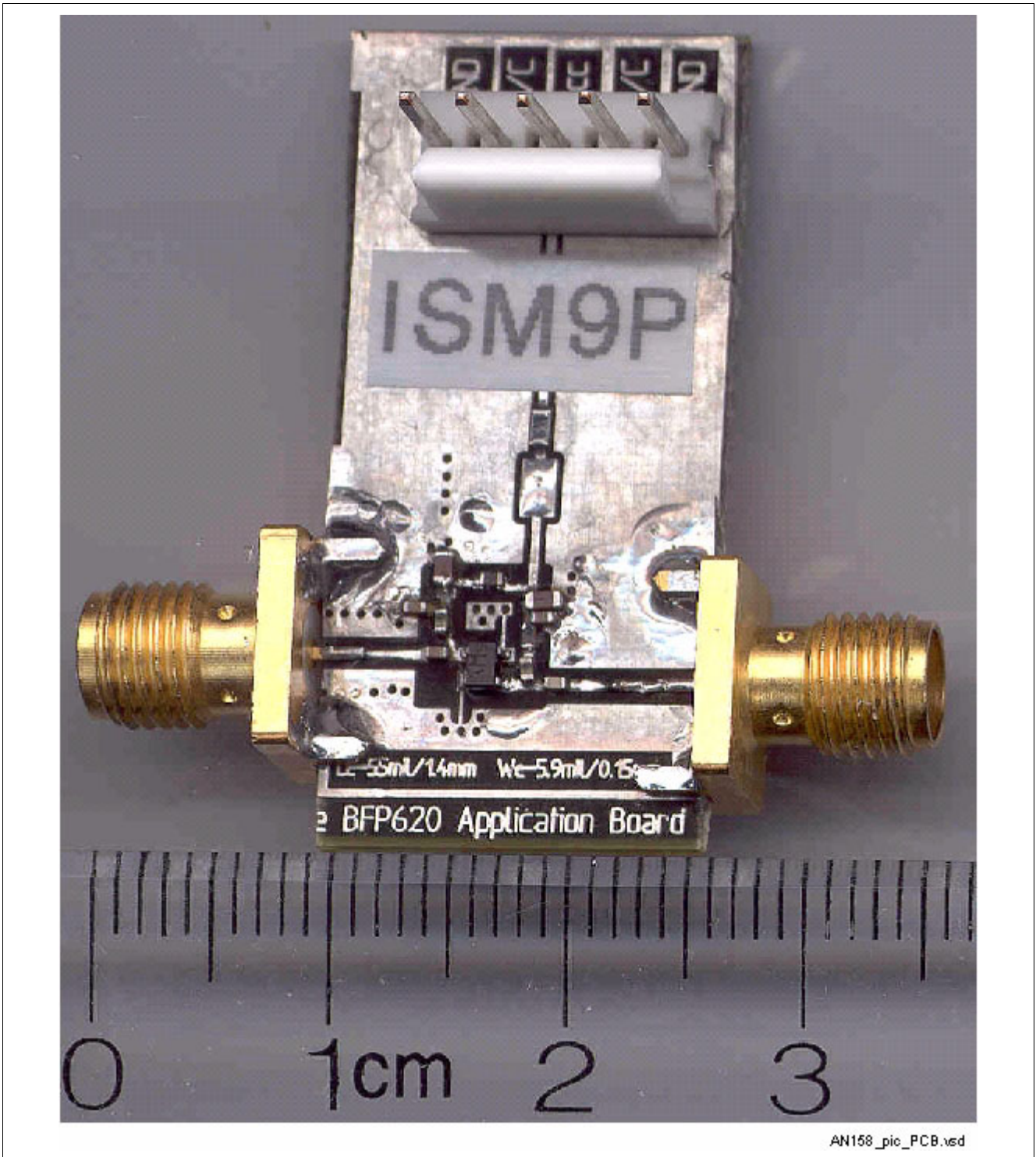


Figure 5 Image of PC Board

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Input Return Loss, Log Mag

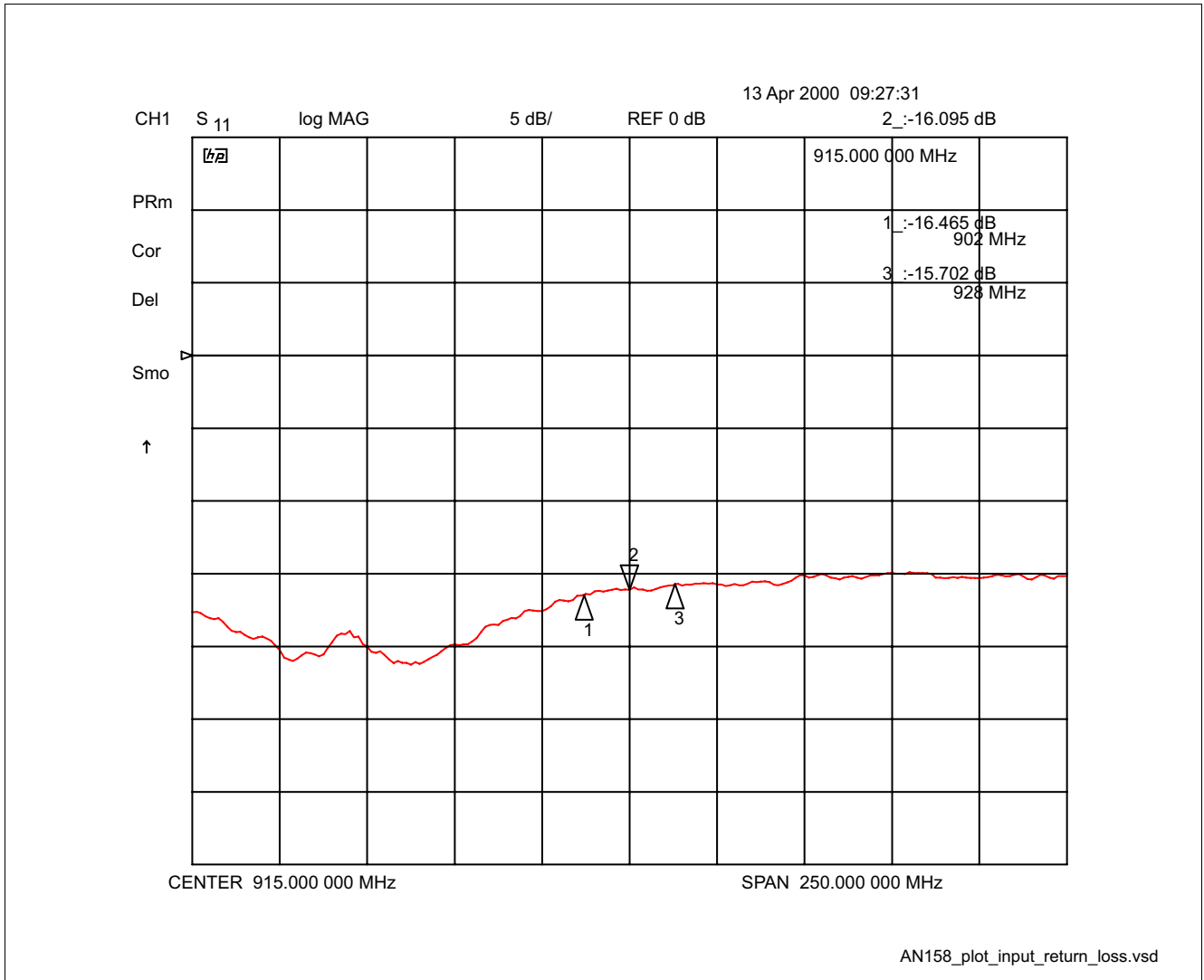


Figure 6 Plot of Input Return Loss

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Input Return Loss, Smith Chart

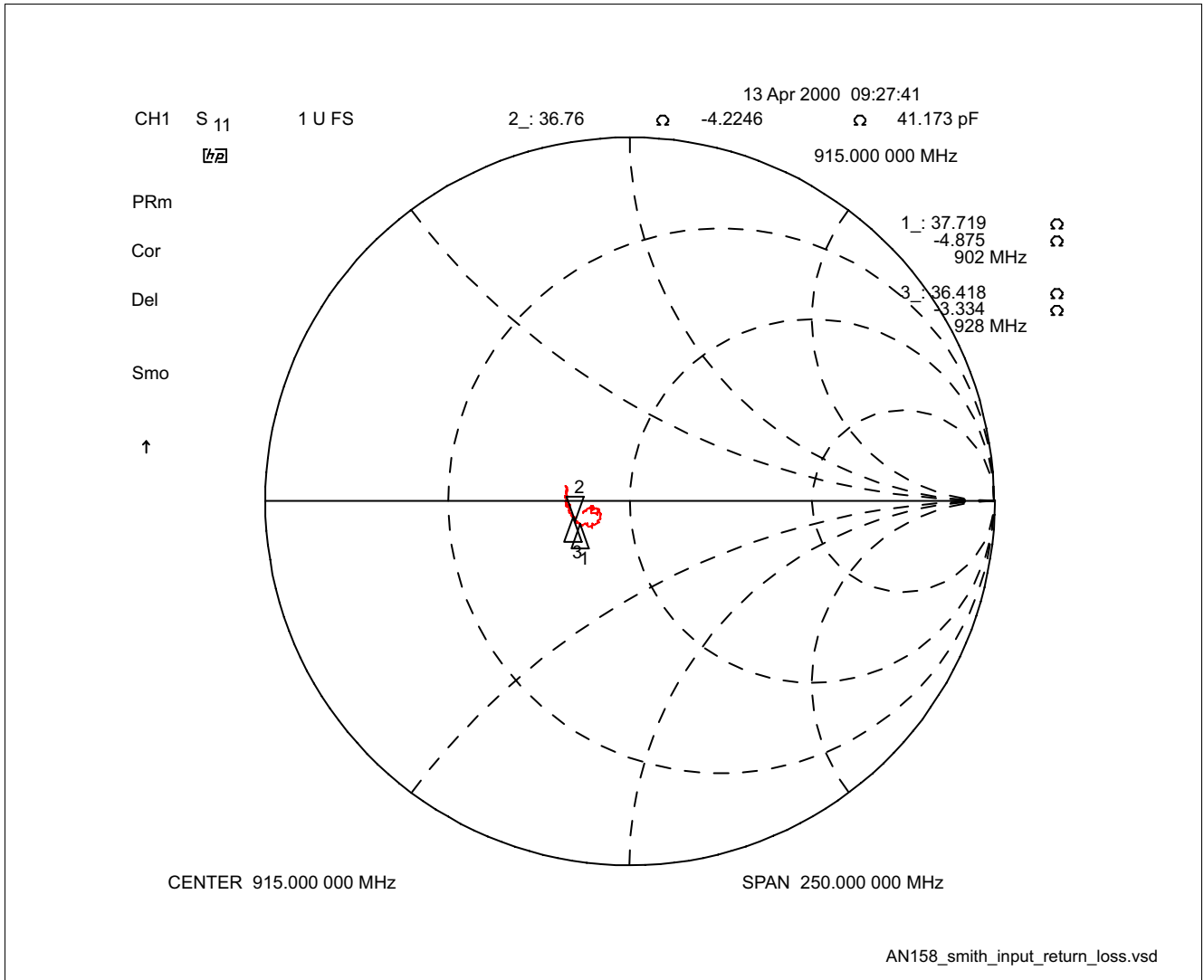


Figure 7 Smith Chart of Input Return Loss

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Forward Gain

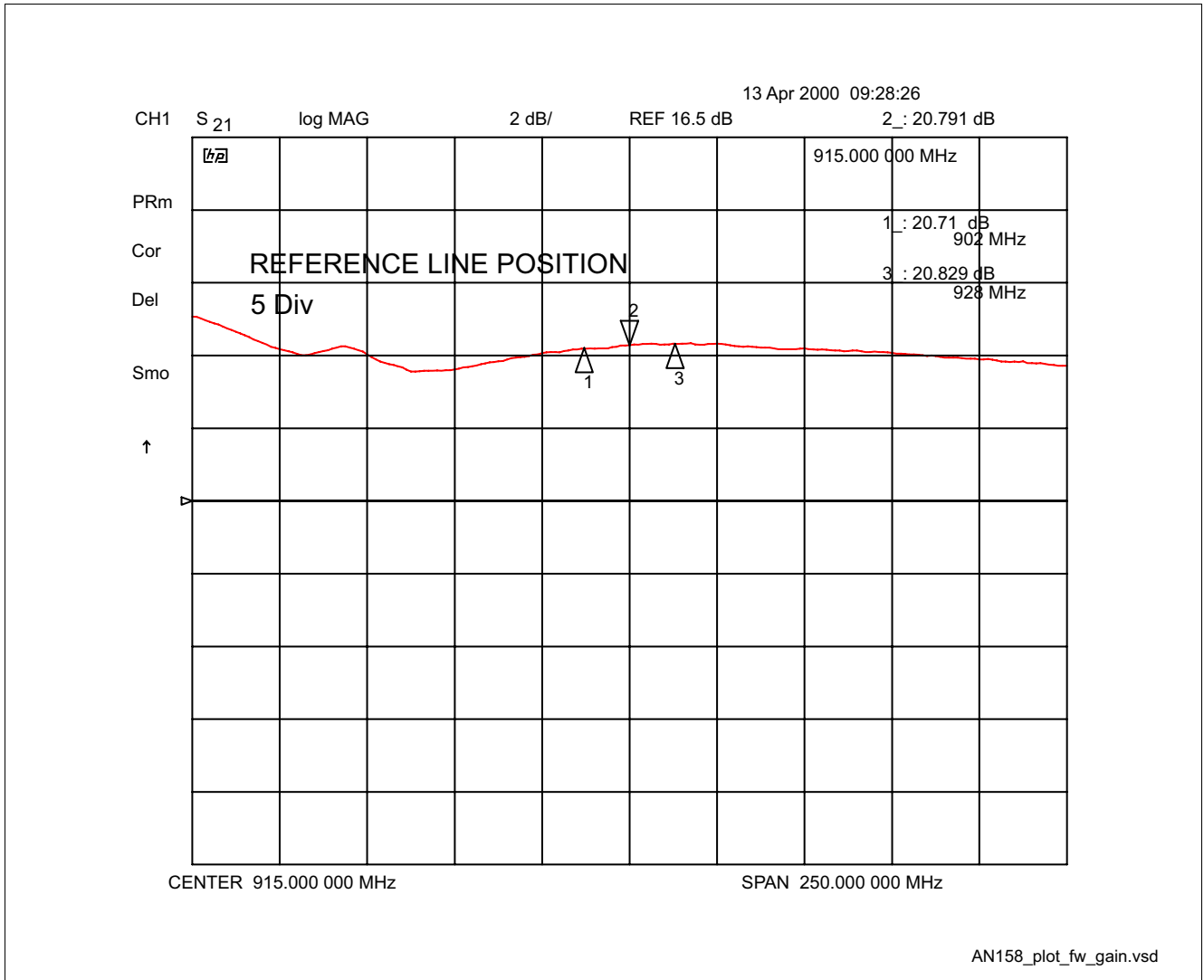


Figure 8 Plot of Forward Gain

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Forward Gain, Wide Span

30 kHz - 6 GHz

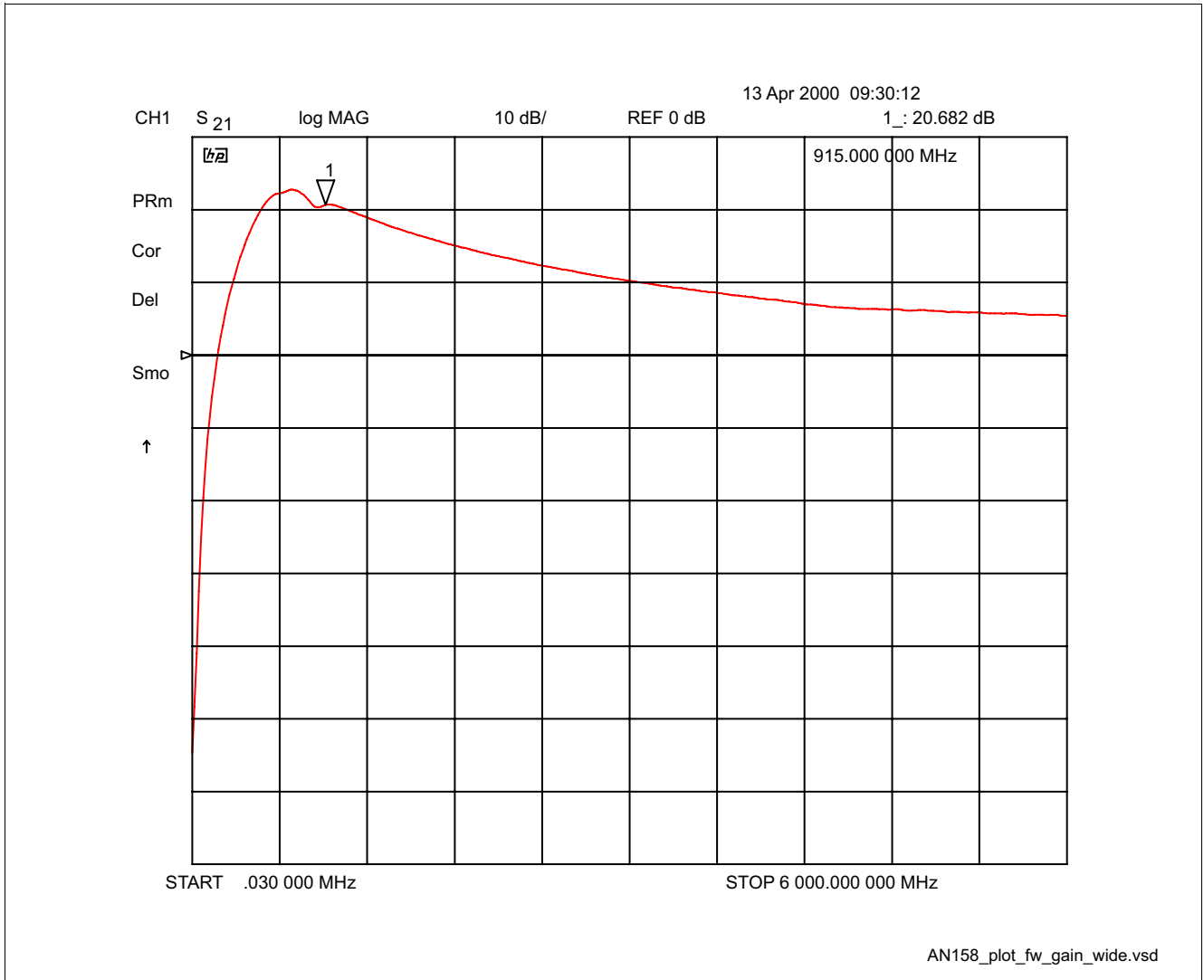


Figure 9 Plot of Forward Gain, Wide Span

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Reverse Isolation

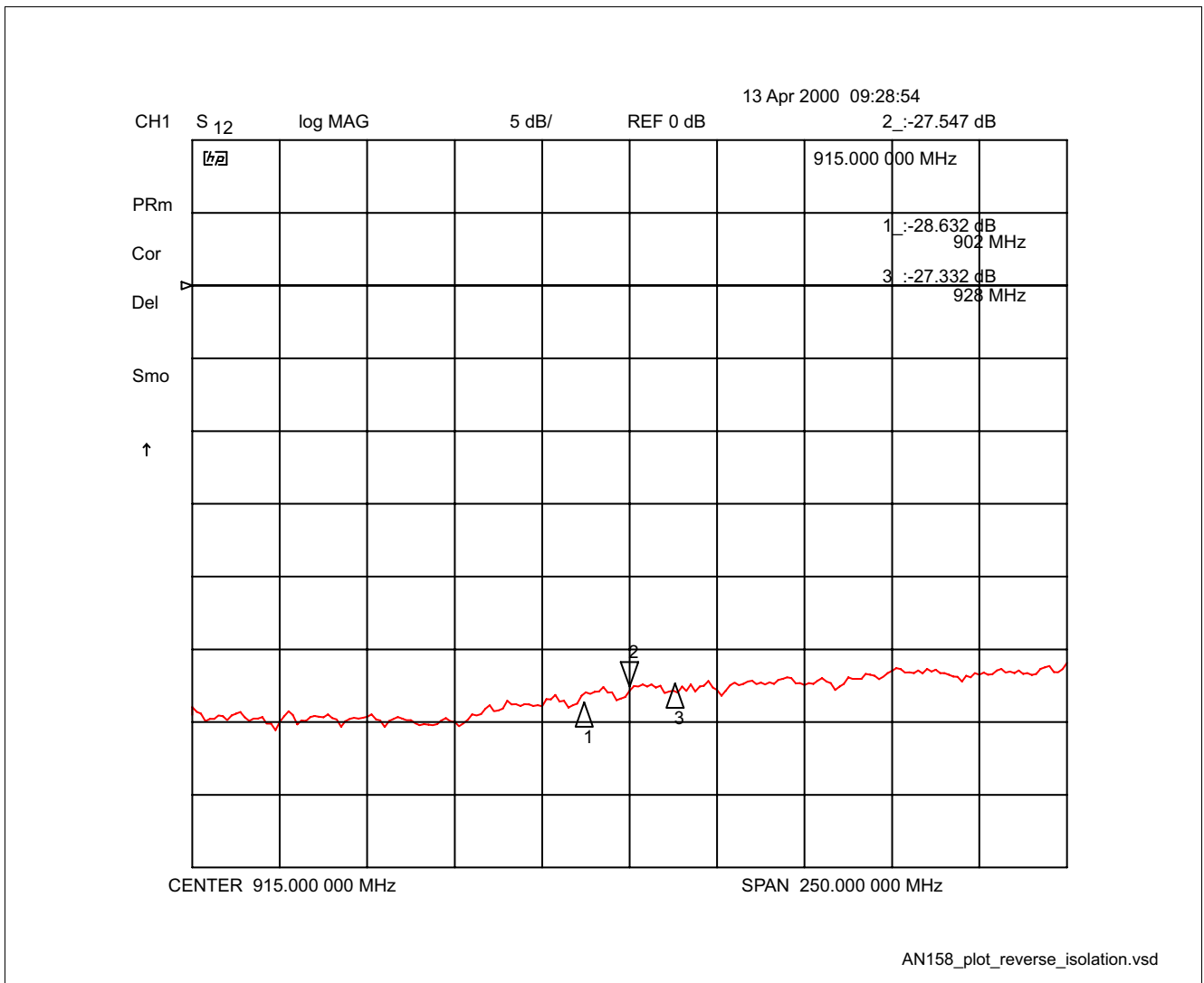


Figure 10 Plot of Reverse Isolation

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Output Return Loss, Log Mag

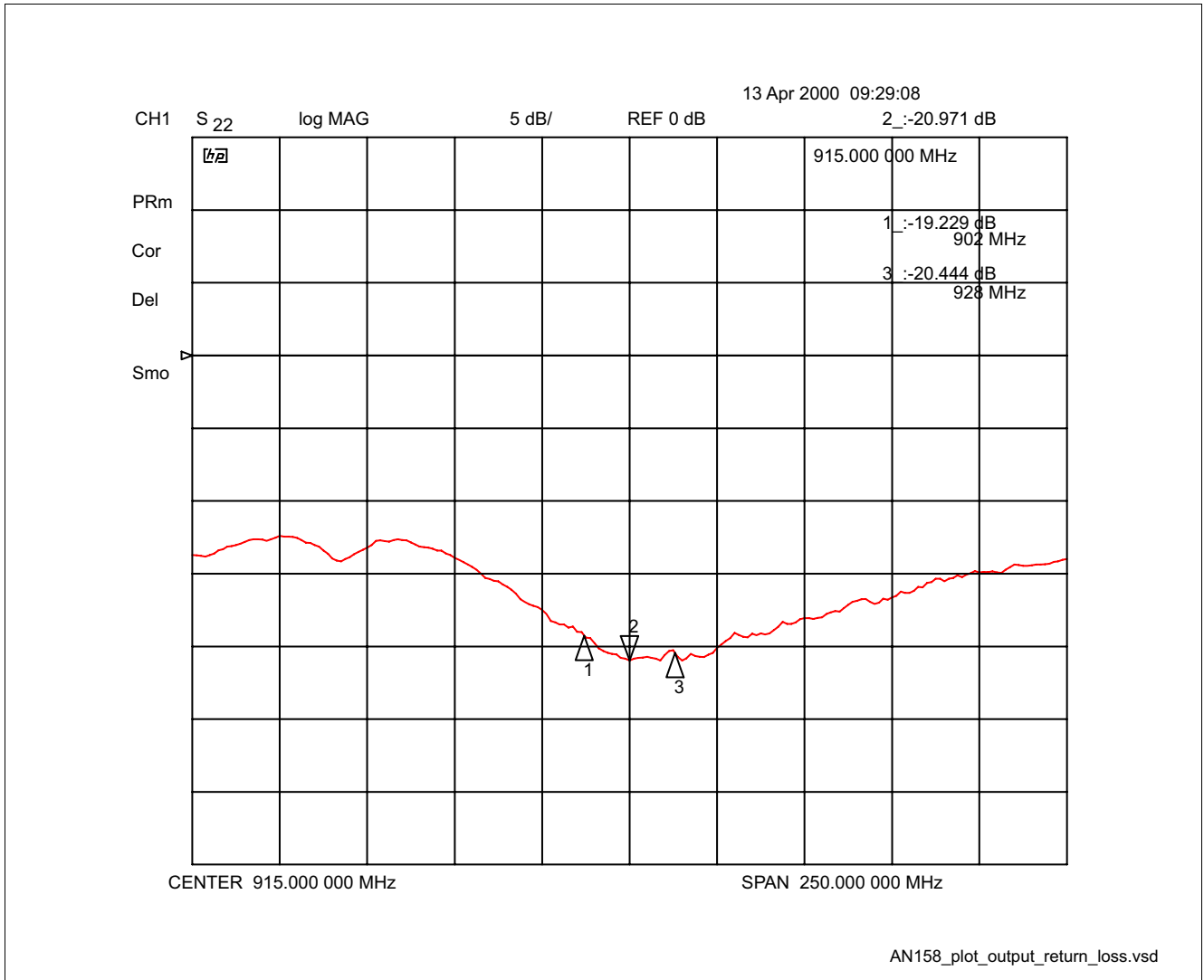


Figure 11 Plot of Output Return Loss

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Output Return Loss, Smith Chart

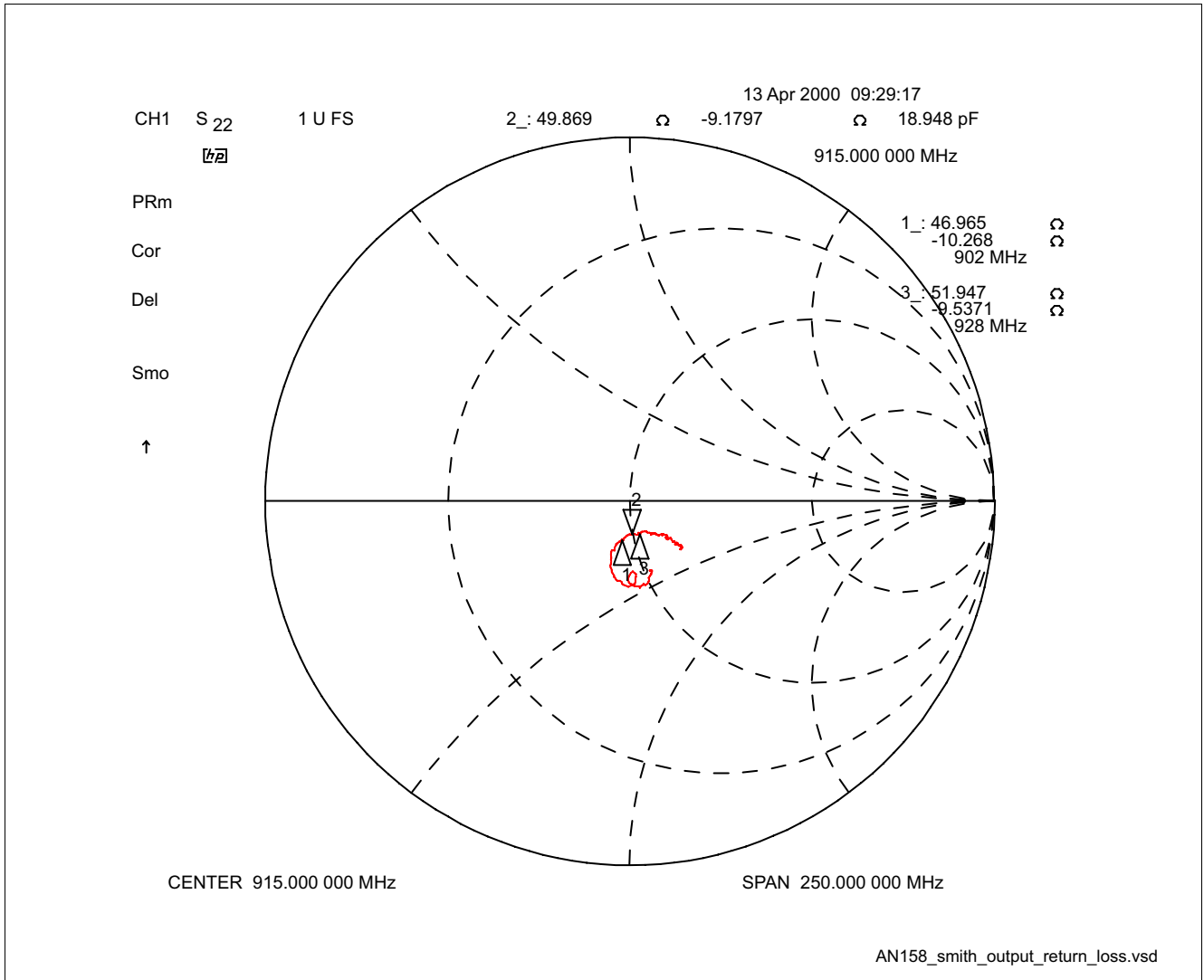


Figure 12 Smith Chart of Output Return Loss

The BFP420 Transistor as a Low-Cost 900 MHz ISM Band Power Amplifier

Two-Tone Test

Output Response of Amplifier to Two-Tone 3rd Order Intercept Test, mid-band (915 MHz). Two tones, -20 dBm each tone, tone spacing = 1 MHz.

Input $IP_3 = -20 + (50.0 / 2) = +5.0$ dBm

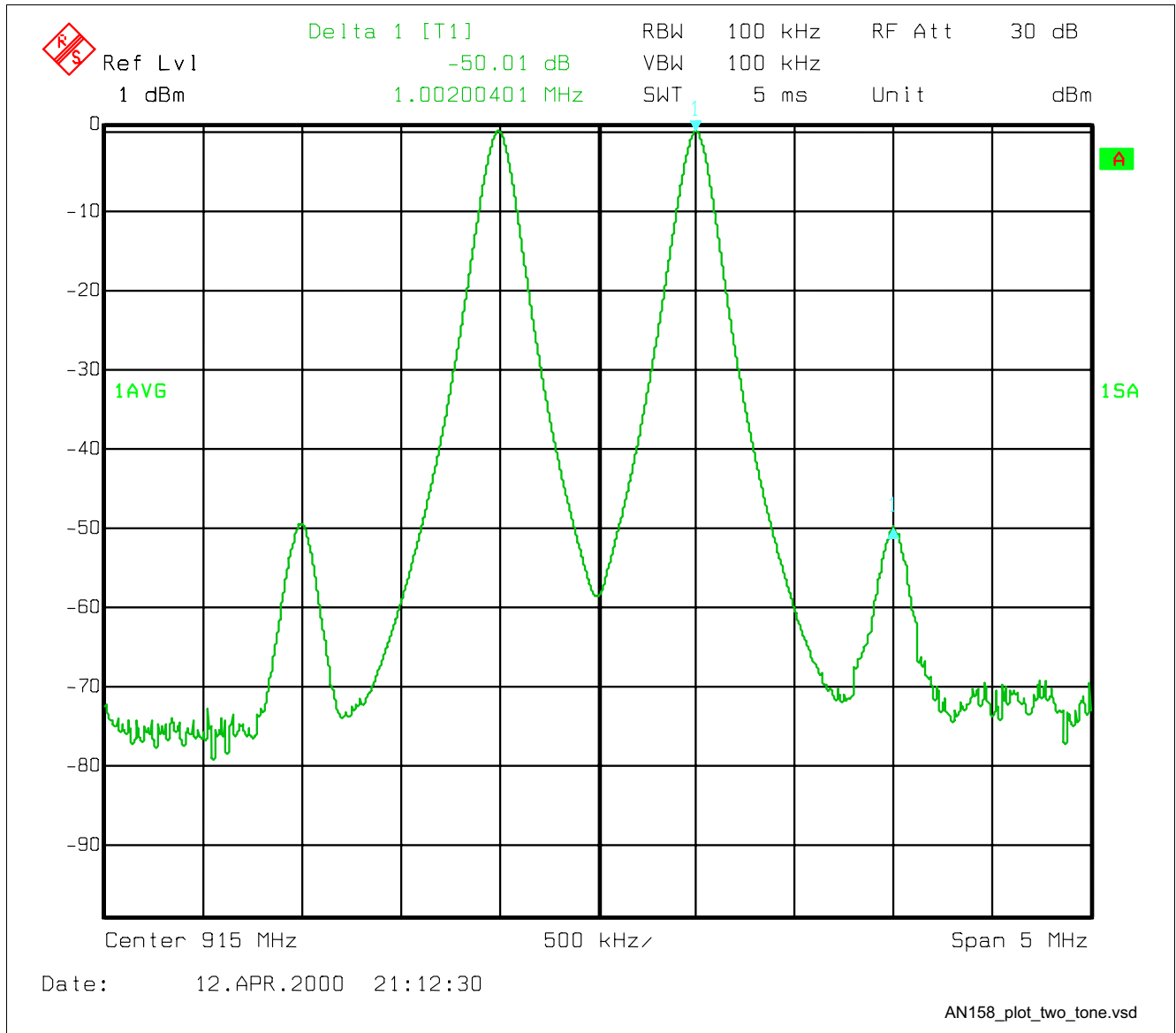


Figure 13 Plot of Two-Tone Test, LNA response