

BGA925L6

IMD Performance of BGA925L6 with Different Application Circuits under Specific Test Conditions

Application Note AN272

Revision: Rev. 1.0
2011-08-11

Edition 2011-09-16

**Published by
Infineon Technologies AG
81726 Munich, Germany**

**© 2011 Infineon Technologies AG
All Rights Reserved.**

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office.

Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Application Note AN272

Revision History: 2011-08-11

Previous Revision: None

Page	Subjects (major changes since last revision)

Trademarks of Infineon Technologies AG

AURIX™, C166™, CanPAK™, CIPOS™, CIPURSE™, EconoPACK™, CoolMOS™, CoolSET™, CORECONTROL™, CROSSAVE™, DAVE™, EasyPIM™, EconoBRIDGE™, EconoDUAL™, EconoPIM™, EiceDRIVER™, eupec™, FCOS™, HITFET™, HybridPACK™, I²RF™, ISOFACE™, IsoPACK™, MIPAQ™, ModSTACK™, my-d™, NovalithIC™, OptiMOS™, ORIGA™, PRIMARION™, PrimePACK™, PrimeSTACK™, PRO-SIL™, PROFET™, RASIC™, ReverSave™, SatRIC™, SIEGET™, SINDRION™, SIPMOS™, SmartLEWIS™, SOLID FLASH™, TEMPFET™, thinQ!™, TRENCHSTOP™, TriCore™.

Other Trademarks

Advance Design System™ (ADS) of Agilent Technologies, AMBA™, ARM™, MULTI-ICE™, KEIL™, PRIMECELL™, REALVIEW™, THUMB™, µVision™ of ARM Limited, UK. AUTOSAR™ is licensed by AUTOSAR development partnership. Bluetooth™ of Bluetooth SIG Inc. CAT-iq™ of DECT Forum. COLOSSUS™, FirstGPS™ of Trimble Navigation Ltd. EMV™ of EMVCo, LLC (Visa Holdings Inc.). EPCOS™ of Epcos AG. FLEXGO™ of Microsoft Corporation. FlexRay™ is licensed by FlexRay Consortium. HYPERTERMINAL™ of Hilgraeve Incorporated. IEC™ of Commission Electrotechnique Internationale. IrDA™ of Infrared Data Association Corporation. ISO™ of INTERNATIONAL ORGANIZATION FOR STANDARDIZATION. MATLAB™ of MathWorks, Inc. MAXIM™ of Maxim Integrated Products, Inc. MICROTEC™, NUCLEUS™ of Mentor Graphics Corporation. Mifare™ of NXP. MIPI™ of MIPI Alliance, Inc. MIPS™ of MIPS Technologies, Inc., USA. muRata™ of MURATA MANUFACTURING CO., MICROWAVE OFFICE™ (MWO) of Applied Wave Research Inc., OmniVision™ of OmniVision Technologies, Inc. Openwave™ Openwave Systems Inc. RED HAT™ Red Hat, Inc. RFMD™ RF Micro Devices, Inc. SIRIUS™ of Sirius Satellite Radio Inc. SOLARIS™ of Sun Microsystems, Inc. SPANSION™ of Spansion LLC Ltd. Symbian™ of Symbian Software Limited. TAIYO YUDEN™ of Taiyo Yuden Co. TEAKLITE™ of CEVA, Inc. TEKTRONIX™ of Tektronix Inc. TOKO™ of TOKO KABUSHIKI KAISHA TA. UNIX™ of X/Open Company Limited. VERILOG™, PALLADIUM™ of Cadence Design Systems, Inc. VLYNQ™ of Texas Instruments Incorporated. VXWORKS™, WIND RIVER™ of WIND RIVER SYSTEMS, INC. ZETEX™ of Diodes Zetex Limited.

Last Trademarks Update 2011-02-24

Table of Content

1	BGA925L6 GPS Front-End LNA for High Performance Integrated Solution.....	6
2	Introduction	7
3	Application Circuits	9
4	Typical Measurement Results.....	10
5	Measured Graphs for different application circuits of BGA925L6.....	13
6	Miscellaneous Measured Graphs	20
7	Evaluation Boards.....	22
8	Authors.....	23

List of Figures

Figure 1	BGA925L6 in TSLP-6-2 Package (0.70mm x 1.1mm x 0.40mm)	6
Figure 2	Block diagram of the BGA925L6 for GNSS band 1559-1615MHz applications	8
Figure 3	Wideband power gain of different application circuits at supply voltage of 1.8V	13
Figure 4	Wideband power gain of different application circuits at supply voltage of 2.8V	13
Figure 5	Narrowband power gain of different application circuits at supply voltage of 1.8V	14
Figure 6	Narrowband power gain of different application circuits at supply voltage of 2.8V	14
Figure 7	Input matching of different application circuits at supply voltage of 1.8V	15
Figure 8	Input matching of different application circuits at supply voltage of 2.8V	15
Figure 9	Output matching of different application circuits at supply voltage of 1.8V	16
Figure 10	Output matching of different application circuits at supply voltage of 2.8V	16
Figure 11	Reverse isolation of different application circuits at supply voltage of 1.8V	17
Figure 12	Reverse isolation of different application circuits at supply voltage of 2.8V	17
Figure 13	Input 1dB compression point of different application circuits at supply voltage of 1.8V	18
Figure 14	Input 1dB compression point of different application circuits at supply voltage of 2.8V	18
Figure 15	Noise figure of different application circuits at supply voltage of 1.8V	19
Figure 16	Noise figure of different application circuits at supply voltage of 2.8V	19
Figure 17	Input matching of different application circuits at supply voltage of 1.8V	20
Figure 18	Input matching of different application circuits at supply voltage of 2.8V	20
Figure 19	Output matching of different application circuits at supply voltage of 1.8V	21
Figure 20	Output matching of different application circuits at supply voltage of 2.8V	21

List of Tables

Table 1	Pin Definition	8
Table 2	Switching Mode	8
Table 3	Schematic diagram of various application circuits based around BGA925L6	9
Table 4	Electrical Characteristics (at room temperature), $V_{cc} = V_{pon} = 1.8\text{ V}$	10
Table 5	Electrical Characteristics (at room temperature), $V_{cc} = V_{pon} = 2.8\text{ V}$	11
Table 6	IMD comparison of different Application Circuits at $V_{cc}=1.8\text{V}$	12
Table 7	IMD comparison of different Application Circuits at $V_{cc}=2.8\text{V}$	12
Table 8	PCBs for different application circuits under consideration	22

1 BGA925L6 GPS Front-End LNA for High Performance Integrated Solution

1.1 Features

- High gain: 15.8 dB
- High out-of-band input 3rd-order intercept point: +7 dBm
- High input 1dB compression point: -5 dBm
- Low noise figure: 0.65 dB
- Low current consumption: 4.8 mA
- Operating frequency: 1550-1615 MHz
- Supply voltage: 1.5 V to 3.6 V
- Digital on/off switch (1V logic high level)
- Ultra small TSLP-6-2 leadless package
- Package dimensions: 0.70mm x 1.1mm x 0.40mm
- B7HF Silicon Germanium technology
- RF output internally matched to 50 Ω
- Only two external SMD components necessary
- 2 kV HBM ESD protection (including AI-pin)
- Pb-free (RoHS compliant) package



Figure 1 BGA925L6 in TSLP-6-2 Package (0.70mm x 1.1mm x 0.40mm)

1.2 Applications

- Global Positioning System (GPS)
- GLONASS (Russian GNSS)
- Galileo (European GNSS)
- COMPASS (Chinese Beidou Navigation System)

2 Introduction

The BGA925L6 is a front-end Low Noise Amplifier (LNA) for Global Navigation Satellite Systems (GNSS) application. It is based on Infineon Technologies' B7HF Silicon-Germanium (SiGe:C) technology, enabling a cost-effective solution in a ultra small TSLP-6-2 package with ultra low noise figure, high gain, high linearity and low current consumption over a wide range of supply voltages from 3.6 V down to 1.5 V. All these features make BGA925L6 an excellent choice for GNSS LNA as it improves sensitivity, provide greater immunity against out-of-band jammer signals, reduces filtering requirement and hence the overall cost of the GNSS receiver.

The ever growing demand to integrate more and more functionality into one device leads to many challenges when transmitter/receiver has to work simultaneously without degrading the performance of each other. In today's smart-phones a GNSS receiver simultaneously co-exists with transceivers in the GSM/EDGE/UMTS/LTE bands. These 3G/4G transceivers transmit high power in the range of +24 dBm which due to insufficient isolation couple to the GNSS receiver. The cellular signals can mix to produce Intermodulation products exactly in the GNSS receiver frequency band.

In this application note, different application circuits based around BGA925L6 have been considered and compared taking into account their IMD performance under special test cases. BGA925L6 can also be preceded with any external pre-filter by adding necessary components required for optimal performance but in this specific application the SAW filter of Infineon's BGM1033N7 module has been used. Table 3 show different application circuits designed to optimize noise figure, matching and increased rejection of jammer signals. The SAW filter used here has insertion loss of around 1dB and high out-of-band rejection. In special cases an additional notch can be added to suppress a specific jammer. In all the application circuits defined in Table 3, an additional "notch" has been added to suppress LTE band-13 jammer signal since its 2nd harmonic falls into GPS band. The component values for the notch are then fine tuned so as to have optimal noise figure, LTE band-13 rejection, gain and input matching.

The Internal circuit diagram of the BGA925L6 is presented in Figure 2. Table 1 shows the pin assignment of BGA925L6. Table 2 shows the truth table to turn on/off BGA925L6 by applying different voltage to the PON pin.

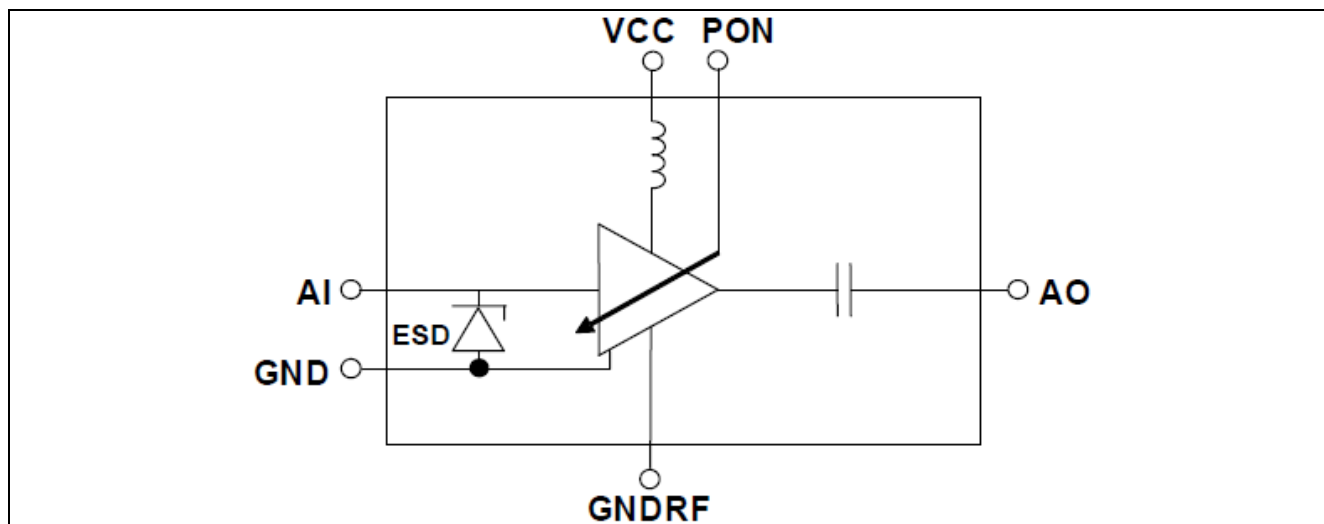


Figure 2 Block diagram of the BGA925L6 for GNSS band 1559-1615MHz applications

Table 1 Pin Definition

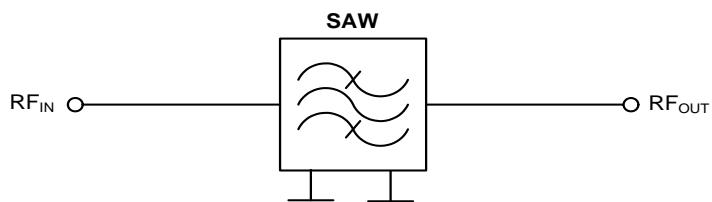
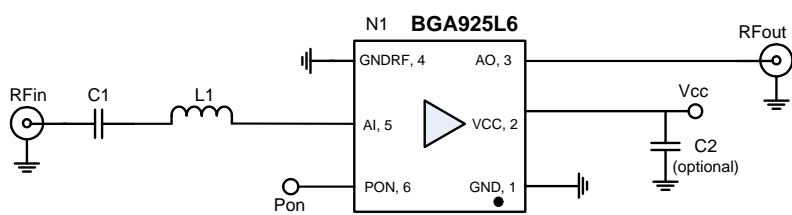
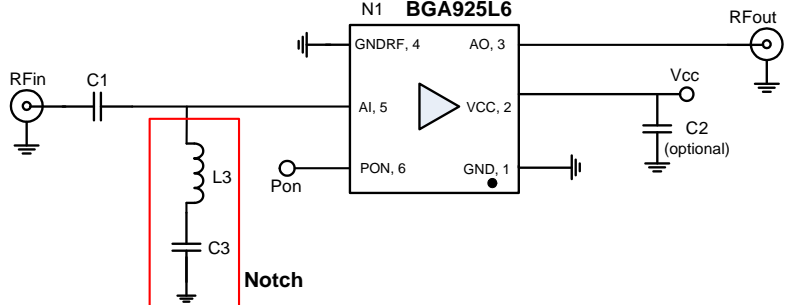
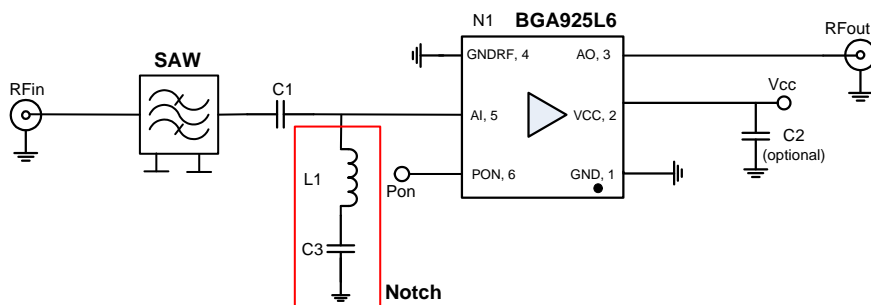
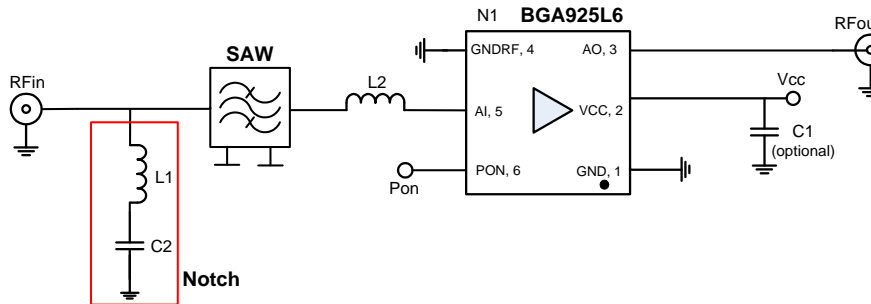
Pin	Symbol	Comment
1	GND	General ground
2	VCC	DC supply
3	AO	LNA output
4	GNDRF	LNA RF ground
5	AI	LNA input
6	PON	Power on control

Table 2 Switching Mode

Mode	Symbol	ON/OFF Control Voltage	
		Min	Max
On	PON, on	1.0V	VCC
Off	PON, off	0	0.4

3 Application Circuits

Table 3 Schematic diagram of various application circuits based around BGA925L6

Application Circuit	Remarks
	<p>SAW filter from BGM1033 is used in all the measurements where it is specified.</p> <p>IL @ 1575 MHz = 0.94 dB</p> <p>IL @ 787 MHz = 20 dB</p>
	<p>AN265 is the standard application circuit for BGA925L6.</p> <p>C1 = 1 nF (0201)</p> <p>C2 = 10 nF (0201)</p> <p>L1 = 5.6 nH (LQP series - 0201)</p> <p>N1 = BGA925L6 (LNA)</p>
	<p>TR1067 is the application which deals with the improvement of band-13 2nd harmonic.</p> <p>C1 = 2.7 pF (0201)</p> <p>C2 = 10 nF (0201)</p> <p>C3 = 6.8 pF (0201)</p> <p>L3 = 5.6 nH (LQG series – 0402)</p> <p>N1 = BGA925L6 (LNA)</p>
	<p>SAW Notch LNA is the application which is designed to improve LTE band-13 2nd harmonic and also suppress other out-of-band jammers using pre-SAW filter.</p> <p>C1 = 2.7 pF (0201)</p> <p>C2 = 10 nF (0201)</p> <p>C3 = 6.8 pF (0201)</p> <p>L1 = 5.6 nH (LQG series – 0402)</p> <p>N1 = BGA925L6 (LNA)</p>
	<p>Notch SAW LNA application circuit is designed to improve the immunity against LTE band-13 jammers and also other out-of-band signals by using a pre-SAW filter.</p> <p>C1 = 10 nF (0201)</p> <p>C2 = 4.7 pF (0201)</p> <p>L1 = 8.2 nH (LQG series – 0402)</p> <p>L2 = 6.8 nH (LQG series – 0402)</p> <p>N1 = BGA925L6 (LNA)</p>

4 Typical Measurement Results

Table 4 to Table 7 show typical measurement result of the application circuits shown in Table 3. The values given in this table include losses of the board and the SMA connectors if not otherwise stated.

Table 4 Electrical Characteristics (at room temperature), $V_{cc} = V_{pon} = 1.8\text{ V}$

Parameter	Symbol	Value				Unit
DC Voltage	V_{cc}	1.8				V
Frequency Range	Freq	1575				MHz
Application Circuit		AN265	TR1067	SAW Notch LNA	Notch SAW LNA	
DC Current	I_{cc}	4.8	4.8	4.8	4.8	mA
Gain	G	15.6	15.2	14.7	15.0	dB
Noise Figure	NF	0.73	0.95	1.69	1.83	dB
Input Return Loss	RL_{in}	12.6	9.5	13.9	17.9	dB
Output Return Loss	RL_{out}	23.4	15.6	15.7	21.8	dB
Reverse Isolation	IR_{rev}	21.8	22.4	23.4	22.6	dB
Input P1dB $f_{gps} = 1575\text{ MHz}$	IP1dB	-8.1	-9.5	-9.5	-7.1	dBm
Output P1dB	OP1dB	6.5	4.6	4.2	6.9	dBm
Stability	k	>1				--

Table 5 Electrical Characteristics (at room temperature), Vcc = Vpon = 2.8 V

Parameter	Symbol	Value				Unit
DC Voltage	Vcc	2.8				V
Frequency Range	Freq	1575				MHz
Application Circuit		AN265	TR1067	SAW Notch LNA	Notch SAW LNA	
DC Current	Icc	5.0	5.0	5.0	5.0	mA
Gain	G	15.6	15.3	14.8	15.0	dB
Noise Figure	NF	0.73	0.96	1.7	1.84	dB
Input Return Loss	RLin	12.6	9.5	13.5	16.4	dB
Output Return Loss	RLout	23.4	14.3	14.2	19.4	dB
Reverse Isolation	IRev	21.8	22.9	23.1	24.0	dB
Input P1dB f _{gps} = 1575 MHz	IP1dB	-7.1	-9.5	-9.3	-6.2	dBm
Output P1dB	OP1dB	6.5	4.7	4.5	7.8	dBm
Stability	k	>1			--	--

Table 6 IMD comparison of different Application Circuits at $V_{CC}=1.8V$

	AN265 ^a	TR1067 ^a	SAW ^b	SAW Notch LNA ^b	Notch SAW LNA ^b	Test Conditions
LTE Band-13 2nd Harmonic Level [dBm]	-31.4	-104.3	-84.6	-68.5	-93.9	a: $f_{IN} = 787.76 \text{ MHz}$, $P_{IN} = -25 \text{ dBm}$ b: $f_{IN} = 787.76 \text{ MHz}$, $P_{IN} = +15 \text{ dBm}$
In-band Output IP3 [dBm]	16.8	10.0		10.8	12.5	a/b: $f_1 = 1575.5 \text{ MHz}$, $P_1 = -30 \text{ dBm}$; $f_2 = 1576.5 \text{ MHz}$, $P_2 = -30 \text{ dBm}$
Out-of-band Output IM3 @ 1575.4 MHz [dBm]	-120.7	-120.8	-95.5	-83.0	-79.1	a: $f_1 = 1712.7 \text{ MHz}$, $P_1 = -41 \text{ dBm}$; $f_2 = 1850 \text{ MHz}$, $P_2 = -41.5 \text{ dBm}$ b: $f_1 = 1712.7 \text{ MHz}$, $P_1 = +10 \text{ dBm}$; $f_2 = 1850 \text{ MHz}$, $P_2 = +10 \text{ dBm}$
Out-of-band Output IM2 @ 1575.4 MHz [dBm]	-17.4	-83.5	-69.2	-53.3	-78.3	a: $f_1 = 787.4 \text{ MHz}$, $P_1 = -20 \text{ dBm}$; $f_2 = 788 \text{ MHz}$, $P_2 = -20 \text{ dBm}$ b: $f_1 = 787.4 \text{ MHz}$, $P_1 = +20 \text{ dBm}$; $f_2 = 788 \text{ MHz}$, $P_2 = +20 \text{ dBm}$
Out-of-band Output IM2 @ 1575.4 MHz [dBm]	-41.2	-66.8	-40.1	-24.5	-23.2	a: $f_1 = 824.6 \text{ MHz}$, $P_1 = -17 \text{ dBm}$; $f_2 = 2400 \text{ MHz}$, $P_2 = -40 \text{ dBm}$ b: $f_1 = 824.6 \text{ MHz}$, $P_1 = +23 \text{ dBm}$; $f_2 = 2400 \text{ MHz}$, $P_2 = 0 \text{ dBm}$

Table 7 IMD comparison of different Application Circuits at $V_{CC}=2.8V$

	AN265 ^a	TR1067 ^a	SAW ^b	SAW Notch LNA ^b	Notch SAW LNA ^b	Test Conditions
LTE Band-13 2nd Harmonic Level [dBm]	-31.7	-104.7	-84.6	-68.5	-93.8	a: $f_{IN} = 787.76 \text{ MHz}$, $P_{IN} = -25 \text{ dBm}$ b: $f_{IN} = 787.76 \text{ MHz}$, $P_{IN} = +15 \text{ dBm}$
In-band Output IP3 [dBm]	17.5	10.1		10.9	12.5	a/b: $f_1 = 1575.5 \text{ MHz}$, $P_1 = -30 \text{ dBm}$; $f_2 = 1576.5 \text{ MHz}$, $P_2 = -30 \text{ dBm}$
Out-of-band Output IM3 @ 1575.4 MHz [dBm]	-119.7	-119.8	-95.5	-83.2	-79.0	a: $f_1 = 1712.7 \text{ MHz}$, $P_1 = -41 \text{ dBm}$; $f_2 = 1850 \text{ MHz}$, $P_2 = -41.5 \text{ dBm}$ b: $f_1 = 1712.7 \text{ MHz}$, $P_1 = +10 \text{ dBm}$; $f_2 = 1850 \text{ MHz}$, $P_2 = +10 \text{ dBm}$
Out-of-band Output IM2 @ 1575.4 MHz [dBm]	-17.5	-83.7	-69.2	-53.3	-78.7	a: $f_1 = 787.4 \text{ MHz}$, $P_1 = -20 \text{ dBm}$; $f_2 = 788 \text{ MHz}$, $P_2 = -20 \text{ dBm}$ b: $f_1 = 787.4 \text{ MHz}$, $P_1 = +20 \text{ dBm}$; $f_2 = 788 \text{ MHz}$, $P_2 = +20 \text{ dBm}$
Out-of-band Output IM2 @ 1575.4 MHz [dBm]	-41.2	-66.9	-40.1	-24.5	-23.1	a: $f_1 = 824.6 \text{ MHz}$, $P_1 = -17 \text{ dBm}$; $f_2 = 2400 \text{ MHz}$, $P_2 = -40 \text{ dBm}$ b: $f_1 = 824.6 \text{ MHz}$, $P_1 = +23 \text{ dBm}$; $f_2 = 2400 \text{ MHz}$, $P_2 = 0 \text{ dBm}$

5 Measured Graphs for different application circuits of BGA925L6

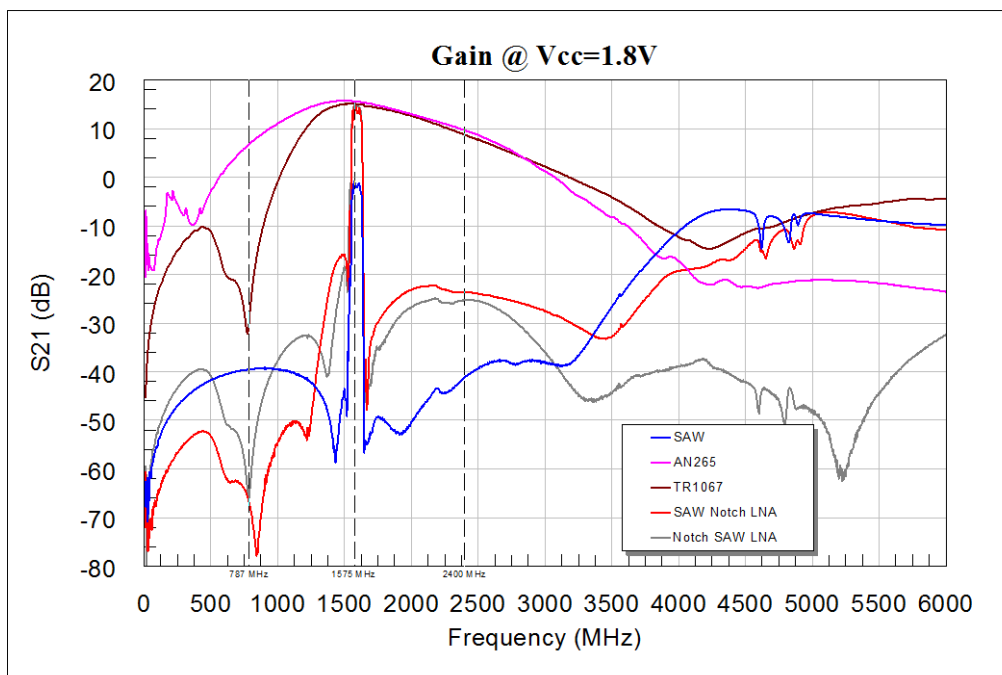


Figure 3 Wideband power gain of different application circuits at supply voltage of 1.8V

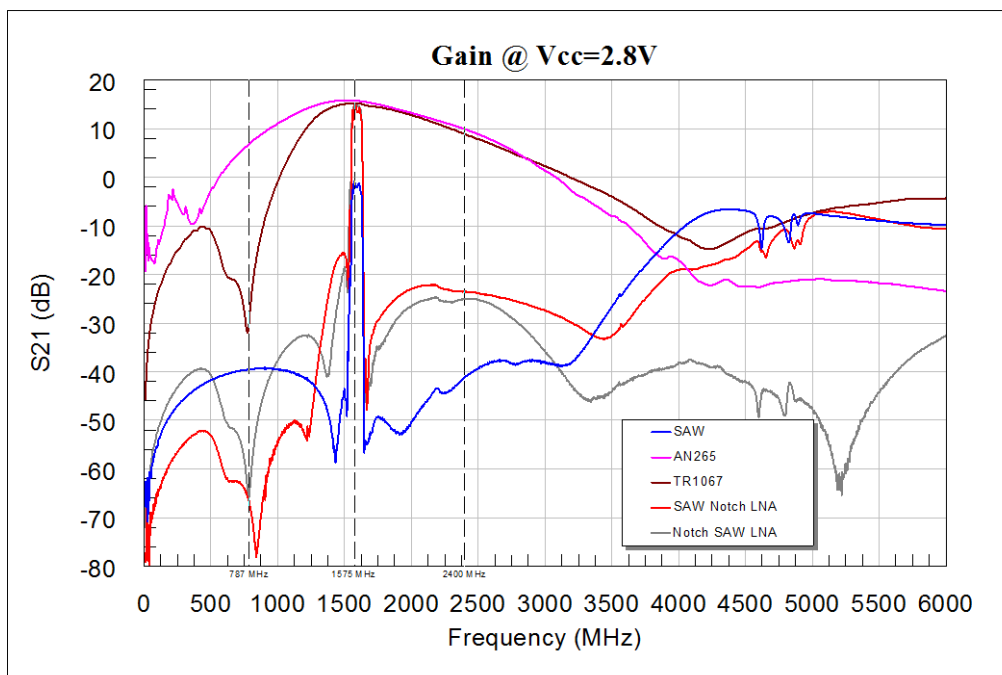


Figure 4 Wideband power gain of different application circuits at supply voltage of 2.8V

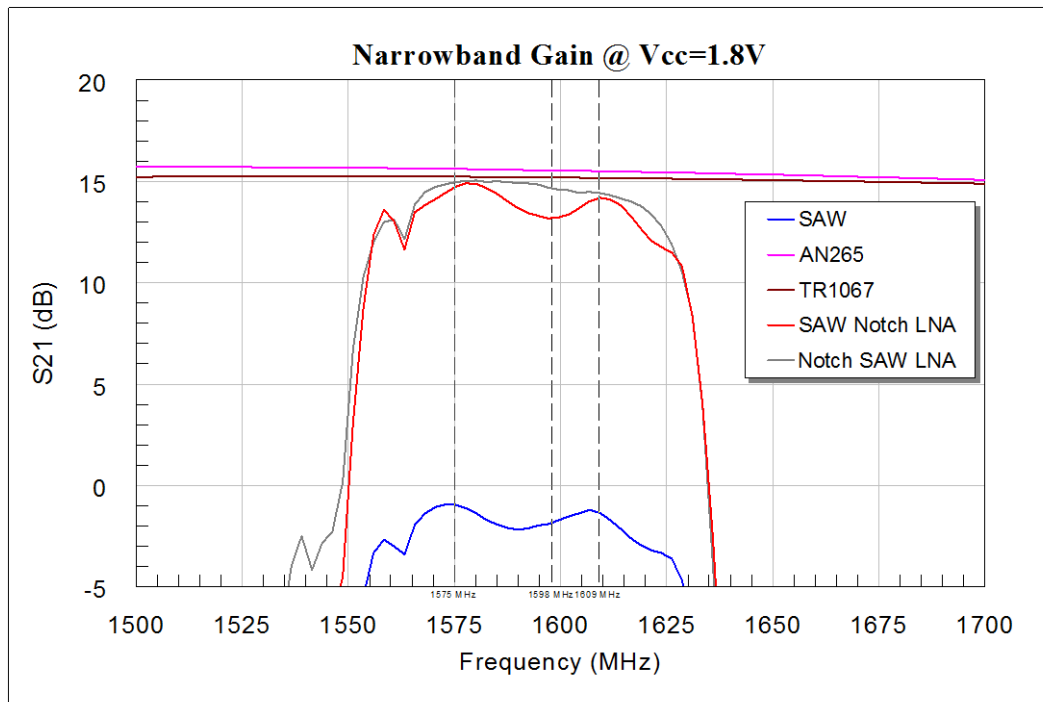


Figure 5 Narrowband power gain of different application circuits at supply voltage of 1.8V

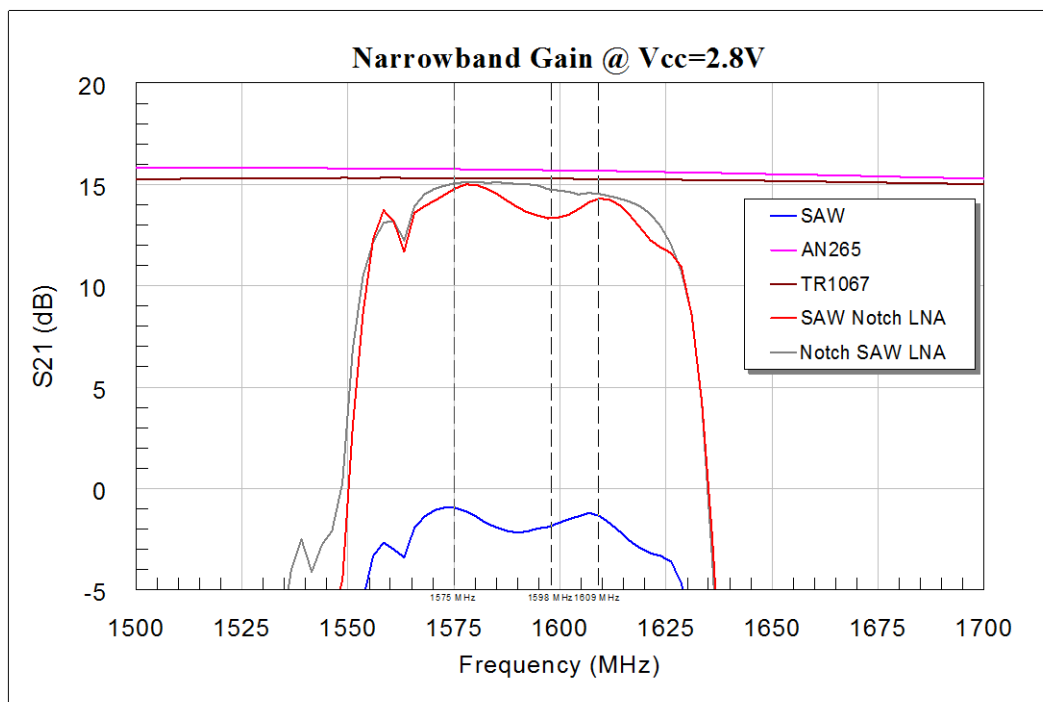


Figure 6 Narrowband power gain of different application circuits at supply voltage of 2.8V

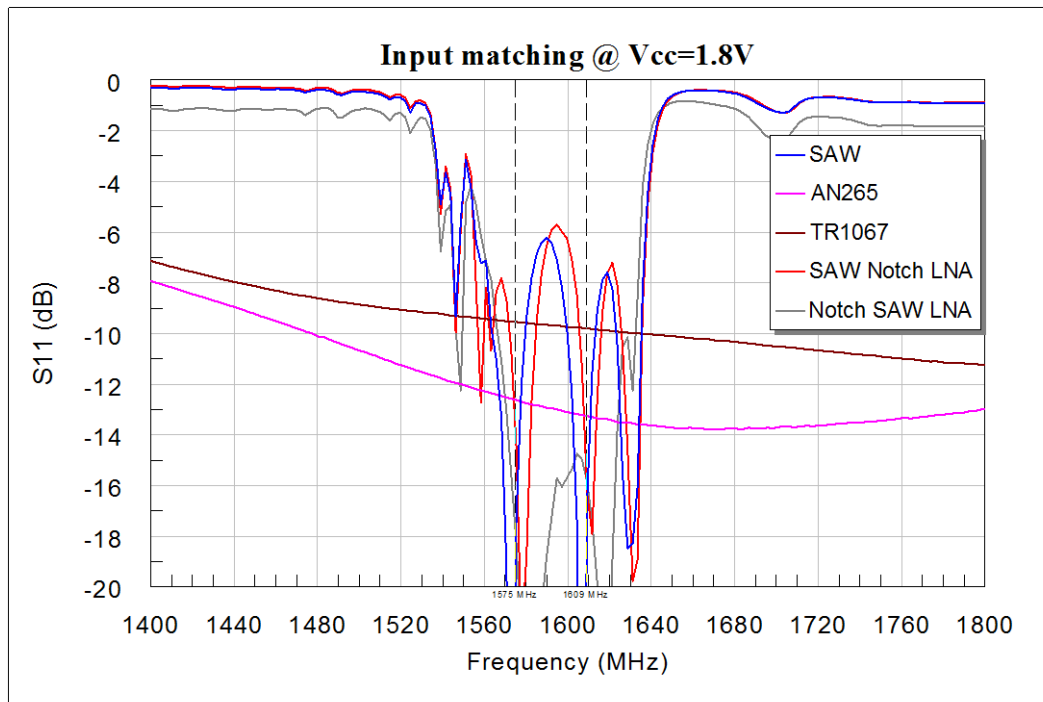


Figure 7 Input matching of different application circuits at supply voltage of 1.8V

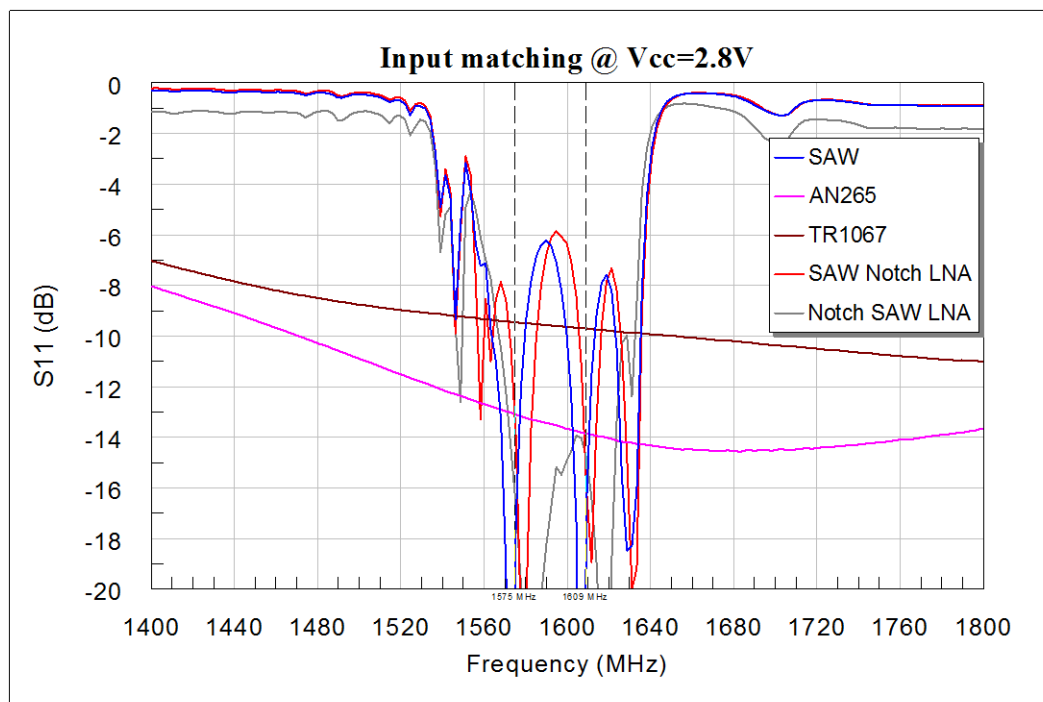


Figure 8 Input matching of different application circuits at supply voltage of 2.8V

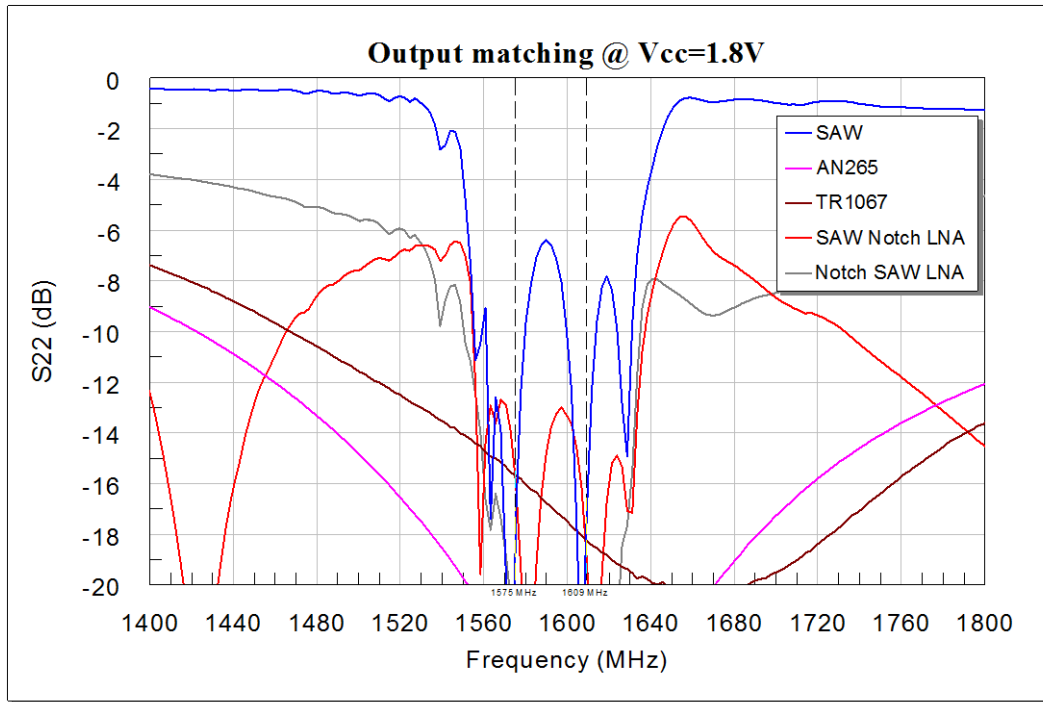


Figure 9 Output matching of different application circuits at supply voltage of 1.8V

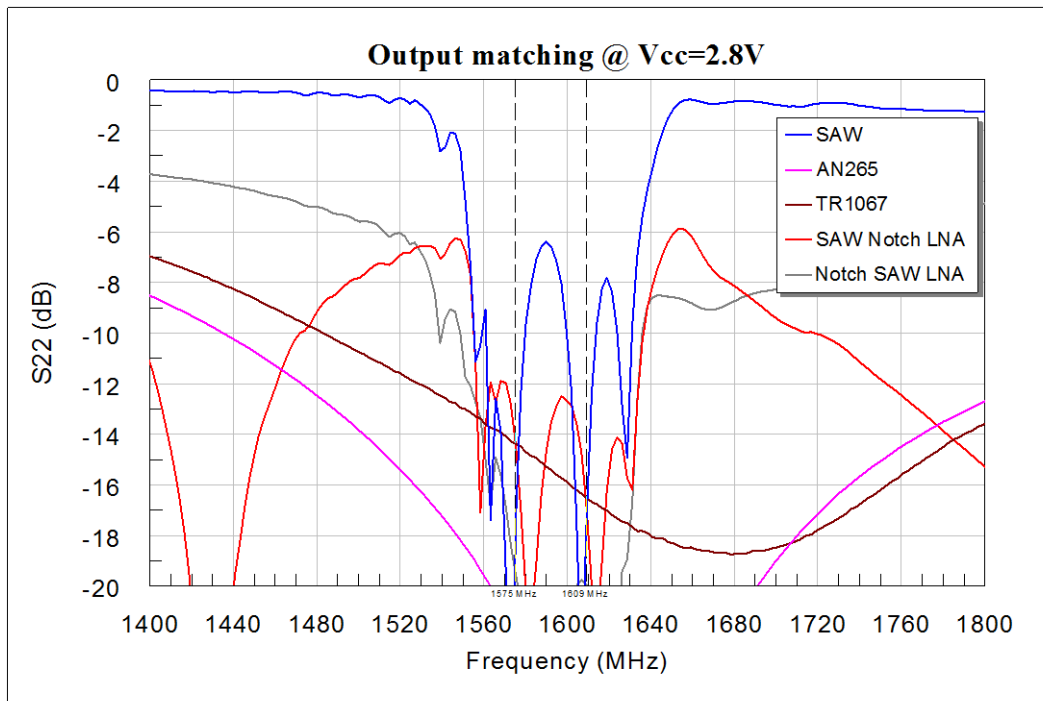


Figure 10 Output matching of different application circuits at supply voltage of 2.8V

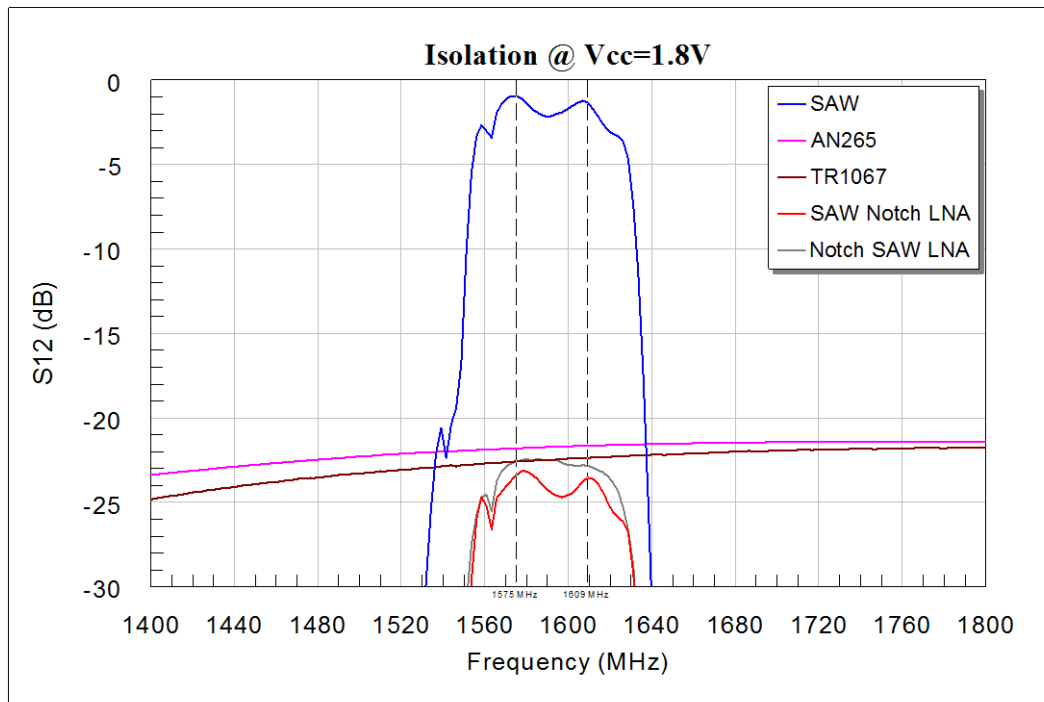


Figure 11 Reverse isolation of different application circuits at supply voltage of 1.8V

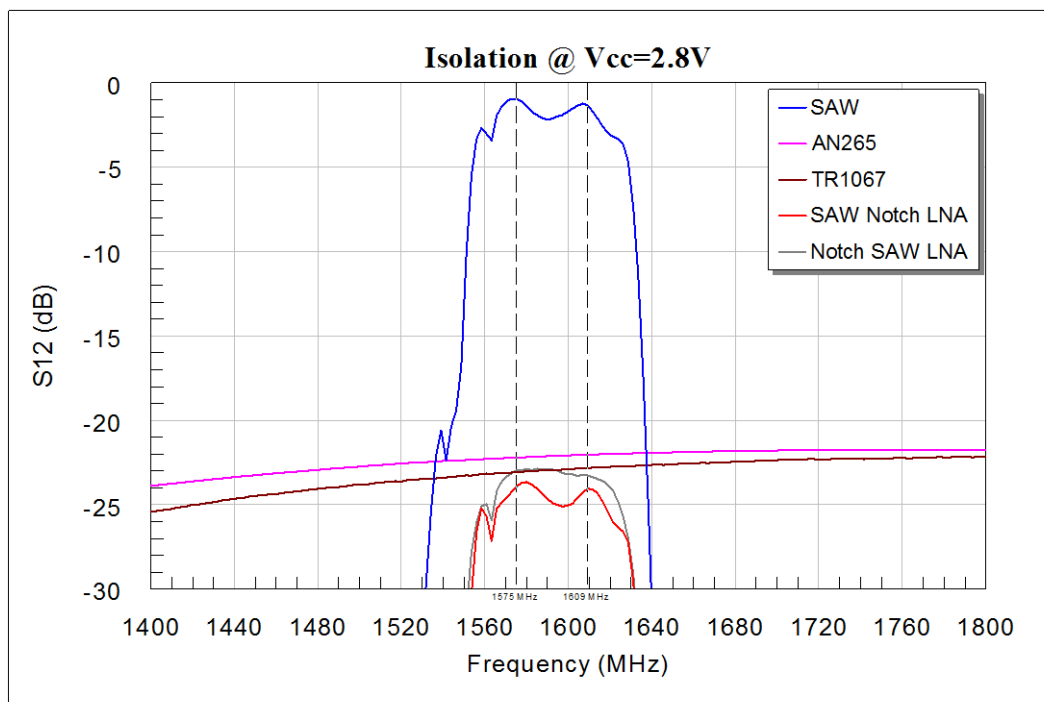


Figure 12 Reverse isolation of different application circuits at supply voltage of 2.8V

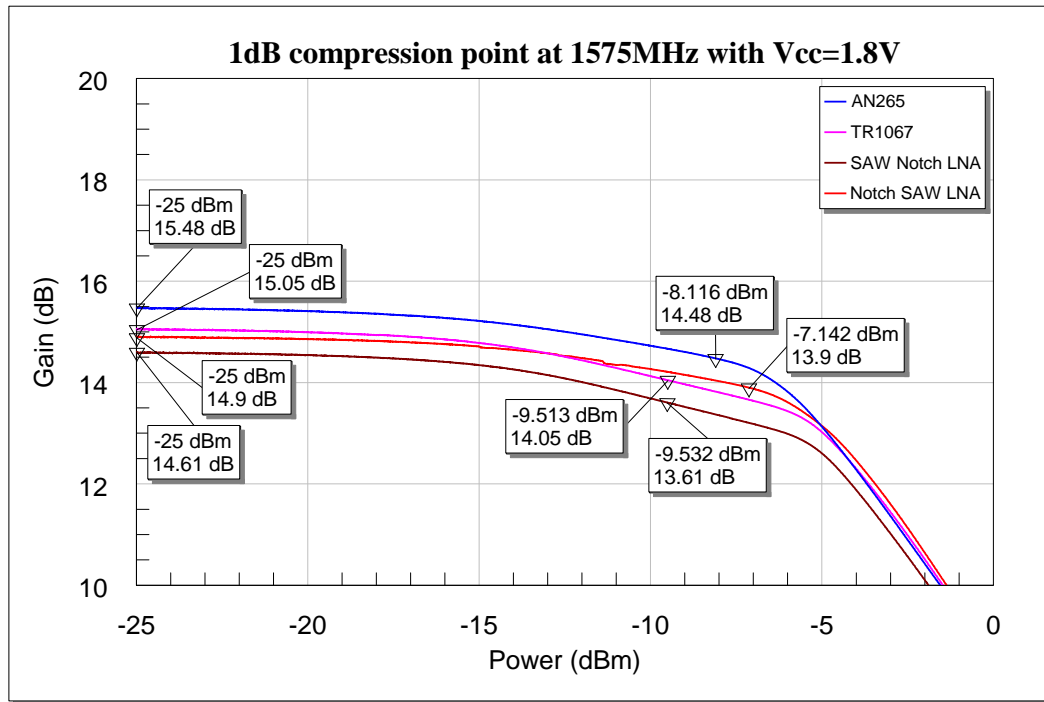


Figure 13 Input 1dB compression point of different application circuits at supply voltage of 1.8V

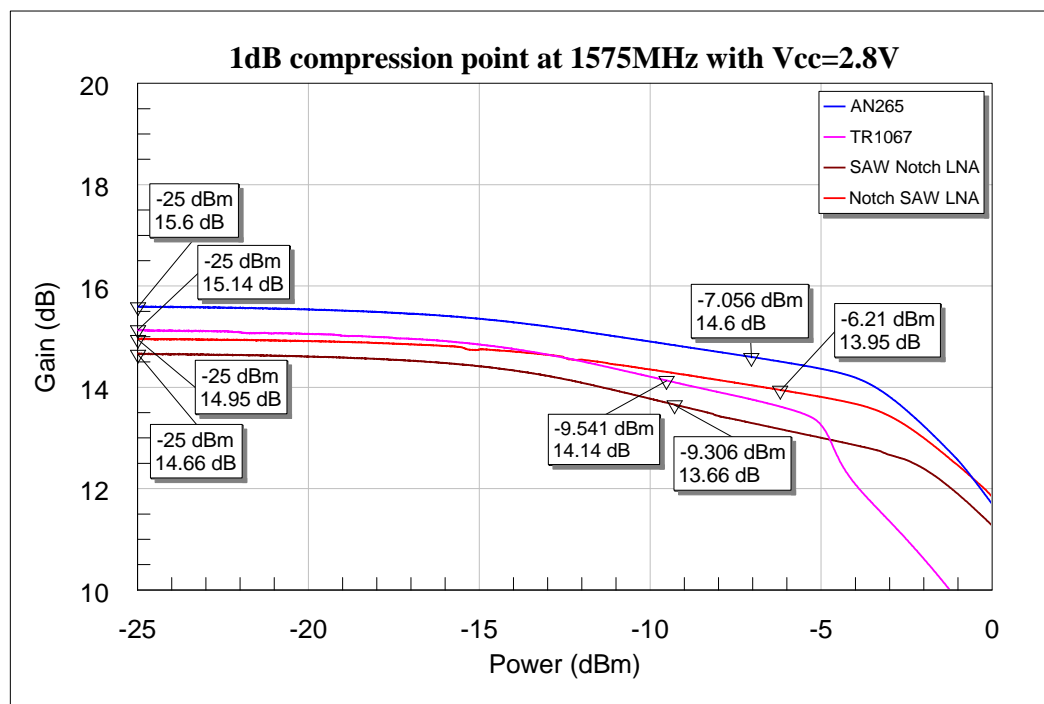


Figure 14 Input 1dB compression point of different application circuits at supply voltage of 2.8V

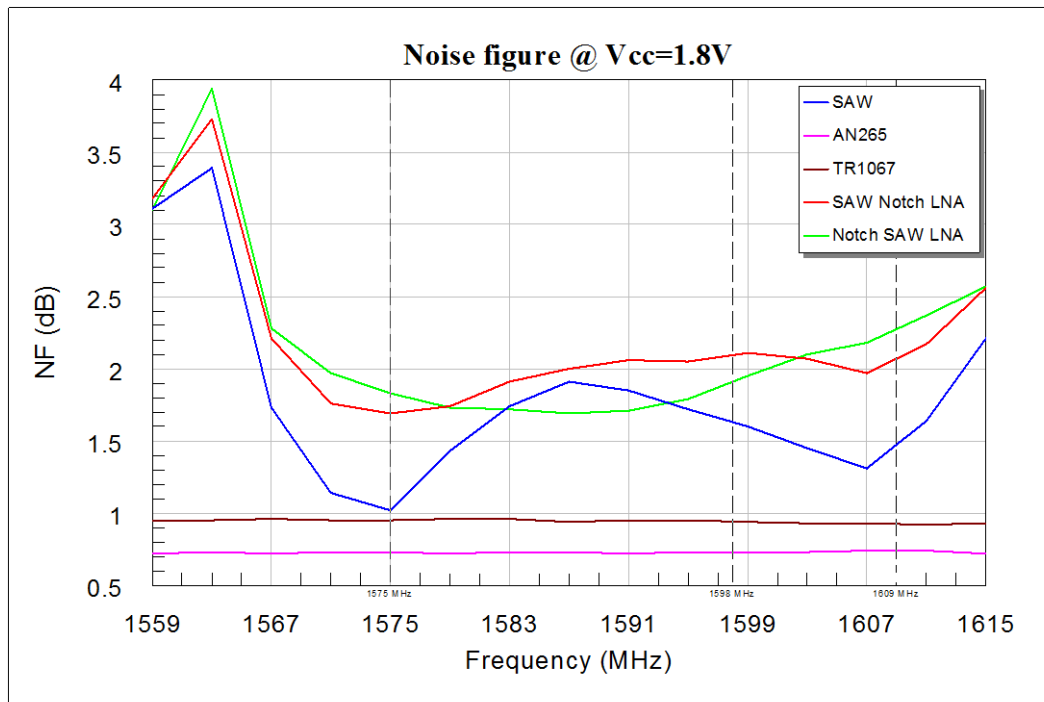


Figure 15 Noise figure of different application circuits at supply voltage of 1.8V

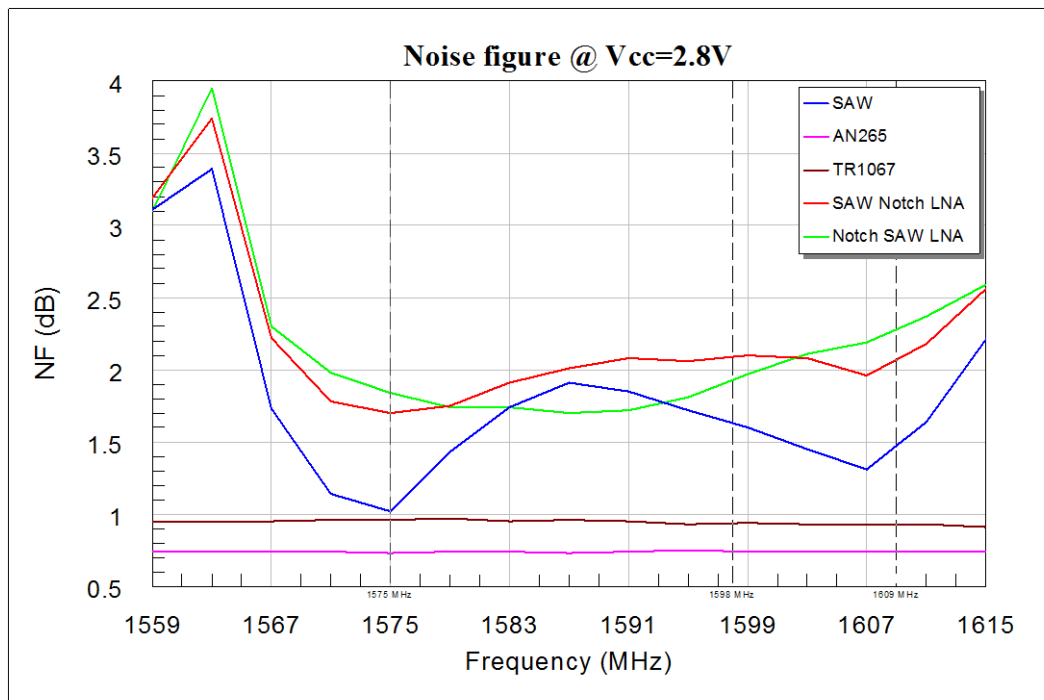


Figure 16 Noise figure of different application circuits at supply voltage of 2.8V

6 Miscellaneous Measured Graphs

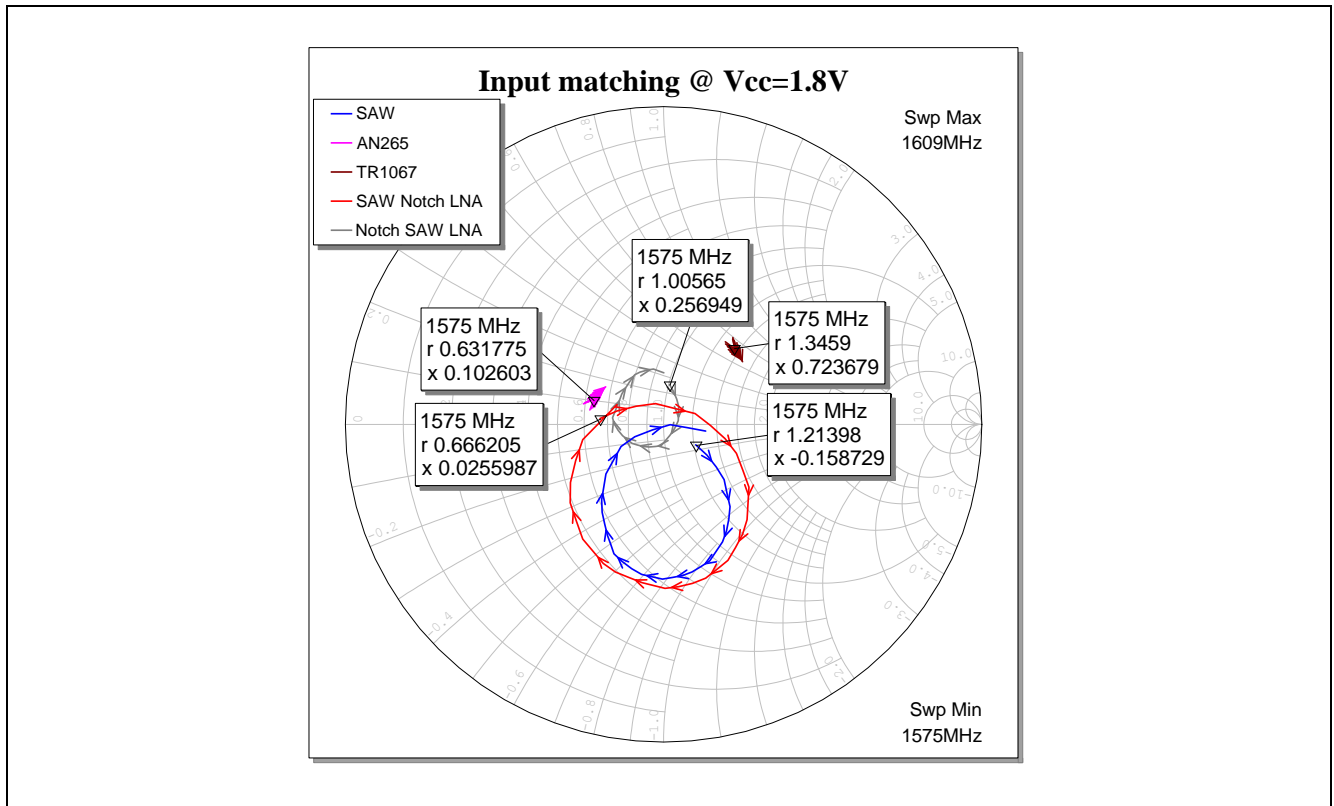


Figure 17 Input matching of different application circuits at supply voltage of 1.8V

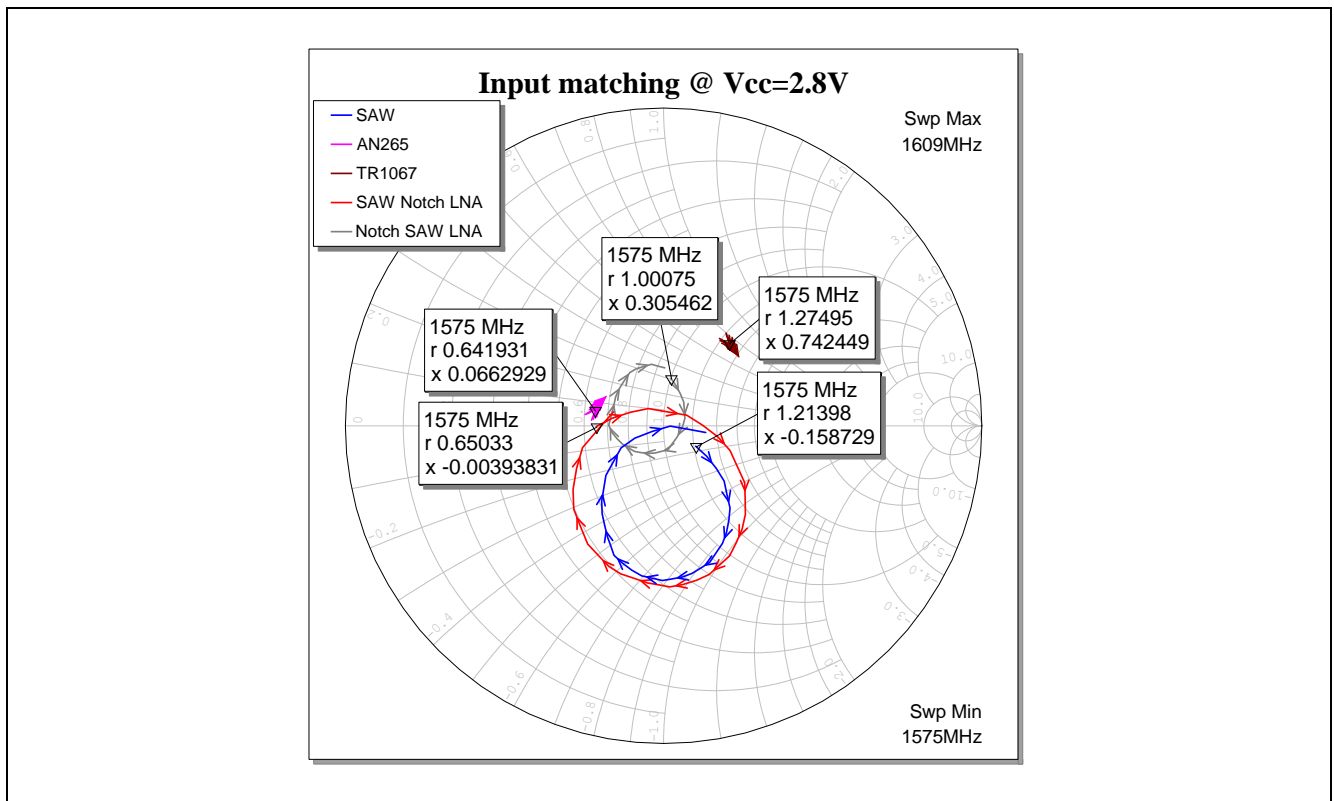


Figure 18 Input matching of different application circuits at supply voltage of 2.8V

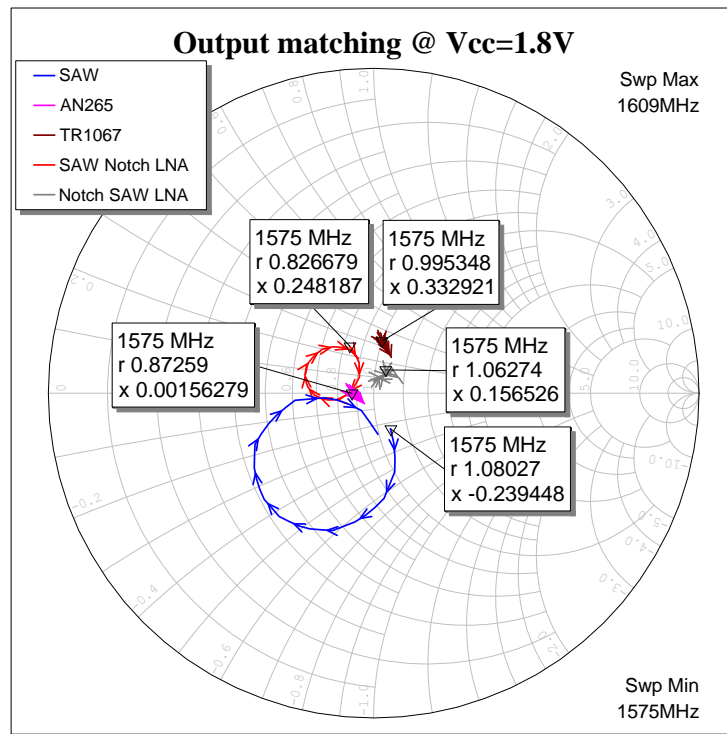


Figure 19 Output matching of different application circuits at supply voltage of 1.8V

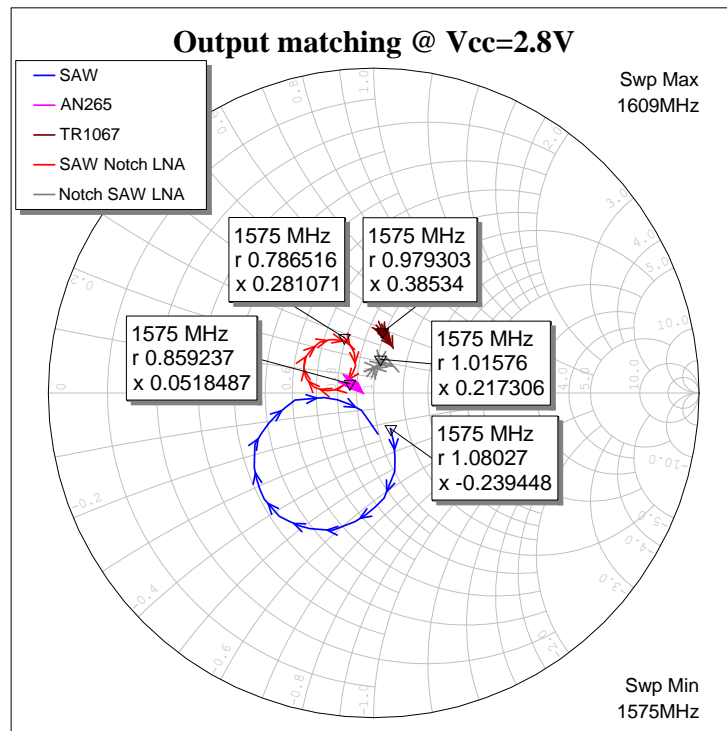



Figure 20 Output matching of different application circuits at supply voltage of 2.8V

7 Evaluation Boards


Table 8 PCBs for different application circuits under consideration




SAW filter (From BGM1033 Module), Rogers

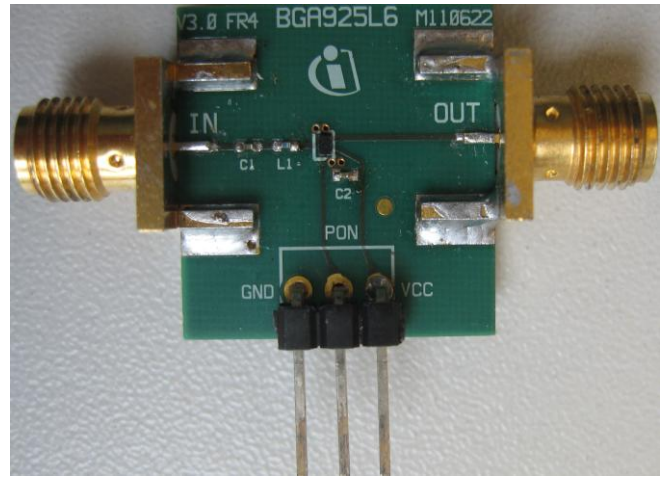


AN265 - Standard Application board BGA925L6, FR4

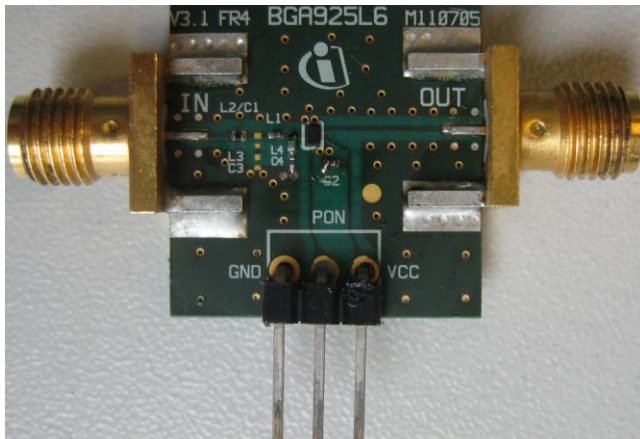

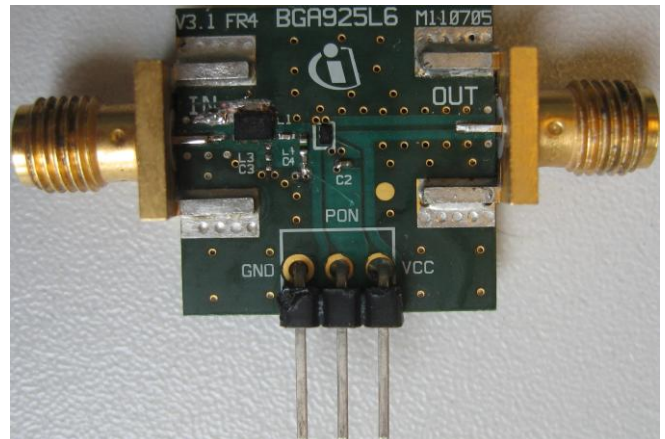
TR1067 – BGA925L6 with 787 MHz notch, FR4



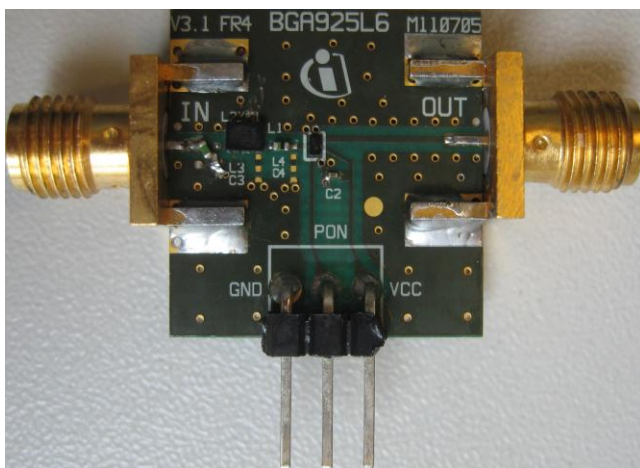SAW Notch LNA – BGA925L6 with SAW filter and Notch, FR4



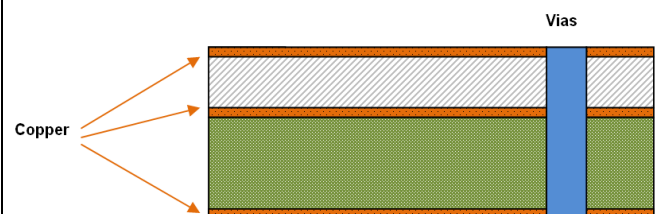Notch SAW LNA – BGA925L6 with Notch and SAW filter, FR4



PCB layer stack

8 Authors

Jagjit Singh Bal, Application Engineer of Business Unit “RF and Protection Devices”.

Dr. Chih-I Lin, Senior Staff Engineer of Business Unit “RF and Protection Devices”.

www.infineon.com