

EVALPFC2-ICE1PCS01

300W PFC Evaluation Board with CCM PFC controller ICE1PCS01

Power Management & Supply



Never stop thinking.

Edition 2006-03-27

**Published by Infineon Technologies Asia Pacific,
168 Kallang Way,
349253 Singapore, Singapore**

**© Infineon Technologies AP 2004.
All Rights Reserved.**

Attention please!

The information herein is given to describe certain components and shall not be considered as a guarantee of characteristics.

Terms of delivery and rights to technical change reserved.

We hereby disclaim any and all warranties, including but not limited to warranties of non-infringement, regarding circuits, descriptions and charts stated herein.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.



EVALPFC2-ICE1PCS01

Revision History:	2006-03	V2.0
Previous Version:	V1.0	
Page	Subjects (major changes since last revision)	
4 - 16	Switching frequency	
4 - 16	PCB layout	

300W PFC Evaluation Board with CCM PFC controller ICE1PCS01
 License to Infineon Technologies Asia Pacific Pte Ltd

Junyang Luo
Jeoh Meng Kiat
Jianwei Liu

We Listen to Your Comments

Any information within this document that you feel is wrong, unclear or missing at all?
 Your feedback will help us to continuously improve the quality of this document.
 Please send your proposal (including a reference to this document) to:

ap-lab.admin@infineon.com





300W CCM PFC Evaluation Board with ICE1PCS01, CoolMOS™ and SiC Diode thinQ!™

The board described here was designed as a typical power factor correction (PFC) circuit in boost topology. The controller **ICE1PCS01** chip used for this application is an 8-pin wide range input IC for active PFC converters. The IC operates in the CCM with average current control and in DCM only under light load condition. The switching frequency is programmable by external resistor at one pin. There are various protection features incorporated to ensure safe system operation conditions. The device has a unique soft-start function which limits the start up inrush current thus reducing the stress on the boost diode. To improve the efficiency, the third generation **CoolMOS™** is used as the power switch due to its lowest area specific $R_{ds(on)}$. High voltage Silicon Carbide (SiC) Schottky diode **thinQ!™** is used as PFC boost diode. Because of its ideal reverse recovery behavior, SiC Schottky diode is extremely suitable for high frequency CCM PFC application.

Evaluation board





Technical specifications:

Input voltage	85VAC~265VAC
Input frequency	50Hz
Output voltage and current	400VDC, 0.75A
Output power	300W
Efficiency	>90% at full load
Switching frequency	62.5kHz

Circuit Description

Line Input

The AC line input side comprises the input fuse F1 as over-current protection. The high frequency current ripple is filtered by R1, L1 and CX1. The choke L2, X2-capacitors CX1 and CX2 and Y1-capacitor CY1 and CY2 are used as radio interference suppressors. RT1 is placed in series to limit inrush current during each power on.

Power Stage – Boost Type PFC Converter

After the bridge rectifier BR1, there is a boost type PFC converter consisting of L3, Q1, D1 and C2. The third generation **CoolMOS™** is used as the power switch Q1. Due to its low $R_{ds(on)}$, the small heat sink can fulfill the dissipation requirement. SiC Schottky diode **thinQ!™** is used for D1. As SiC Schottky diode does not show a reverse recovery behavior, the stress on the MOSFET will be reduced due to very low current spike during turn on transient. Simultaneously higher reliability of the entire system can be achieved. However, due to the poor pulse current capability of SiC Schottky diode, a standard diode D2 is necessary to bypass the high inrush current during each power on transient. Output capacitor C2 provides energy buffering to reduce the output voltage ripple (100Hz) to the acceptable level.

PWM control of Boost Converter

The PWM control is realized by 8-Pin CCM PFC IC **ICE1PCS01**. Unlike the conventional PFC controller, **ICE1PCS01** does not need direct sine wave reference signal. The switching frequency is fixed and programmed by R8. There are two control loops in the circuit, voltage loop and current loop. The output voltage is sensed by the voltage divider of R5, R5A, R5B and R6 and sent to internal error amplifier. The output of error amplifier is used to control current in the inner current loop. The compensation network C4, C5, R7 constitutes the external circuitry of the error amplifier. This circuitry allows the feedback to be matched to various load conditions, thereby providing stable control. In order not to make the response for 100Hz ripple, the voltage loop compensation is implemented with low bandwidth. The inner loop, current control loop, is implemented with average current mode strategy. The instant current is adjusted to be proportional to both of MOSFET off duty D_{OFF} and the error amplifier output voltage of voltage loop. The current is sensed by shunt resistors R2, R2A and R2B and fed into IC through R9. The current sense signal is averaged by an internal operating amplifier and then processed in the PWM generator which drives the gate drive. The averaging is realized by charging and discharging an external capacitor C7.

The IC supply is provided by external voltage source and filtered and buffered by C8 and C9. The IC output gate driver is a fast totem pole gate drive. It has an in-built cross conduction current protection and a Zener diode to protect the external transistor switch against undesirable over voltages. The gate drive resistor R4 is selected to limit and gate pulse current and drive MOSFET for fast switching.

Circuit Operation

Soft Start

When Vcc pin is higher than turn-on threshold, typical 11.2V, PFC is going to start. The unique soft start is integrated. Input current keeps sinusoidal and is increasing gradually until output voltage



reaches 80% of rating. Because the peak current limit is not activated, the boost diode is not stressed with large diode duty cycle under high current.

Enhanced Dynamic Response

Due to inherent low bandwidth of PFC dynamic, in case of load jump, regulation circuit can not response fast enough and it will lead to large output voltage overshoot or drop. To solve this problem in PFC application, enhance dynamic response is implemented in the IC. Whenever output voltage exceeds by $\pm 5\%$, it will bypass the slow compensation operating amplifier and act on the nonlinear gain block to affect the duty cycle directly. The output voltage can be recovered in a short time.

Protection Features

Open loop protection (OLP) / Mains under voltage protection

The open loop protection is available for this IC to safe-guard the output. Whenever V_{SENSE} voltage falls below 0.8V, or equivalently V_{OUT} falls below 16% of its rated value, it indicates an open loop condition (i.e. VSENSE pin not connected). In this case, most of the blocks within the IC will be shutdown. It is implemented using a comparator with a threshold of 0.8V. Insufficient input voltage V_{IN} will also trigger this protection.

Output over-voltage protection

Output over-voltage protection is also available by the same integrated blocks of enhanced dynamic response. Whenever V_{OUT} exceeds the rated value by 5%, the over-voltage protection OVP is active. This is implemented by sensing the voltage at pin V_{SENSE} with respect to a reference voltage of 5.25V. A V_{SENSE} voltage higher than 5.25V will immediately reduce the output duty cycle even down to zero, bypassing the normal voltage loop control. This results in a lower input power and the output voltage V_{OUT} is reduced.

Soft over current control (SOC) and peak current limit

When the amplitude of current sense voltage reaches 0.73V, Soft Over Current Control (SOC) is activated. This is a soft control does not directly switch off the gate drive but acts on the internal blocks to result in a reduced PWM duty cycle.


The IC also provides a cycle by cycle peak current limitation (PCL). It is active when the voltage at current sense voltage reaches -1.08V. The gate output is immediately off after 300ns blanking time.

IC supply under voltage lock out


When VCC voltage is below the under voltage lockout threshold V_{CCUVLO} , typical 10.2V, IC is off the gate drive is internally pull low to maintain the off state. The current consumption is down to 200uA only.




Circuit Diagram

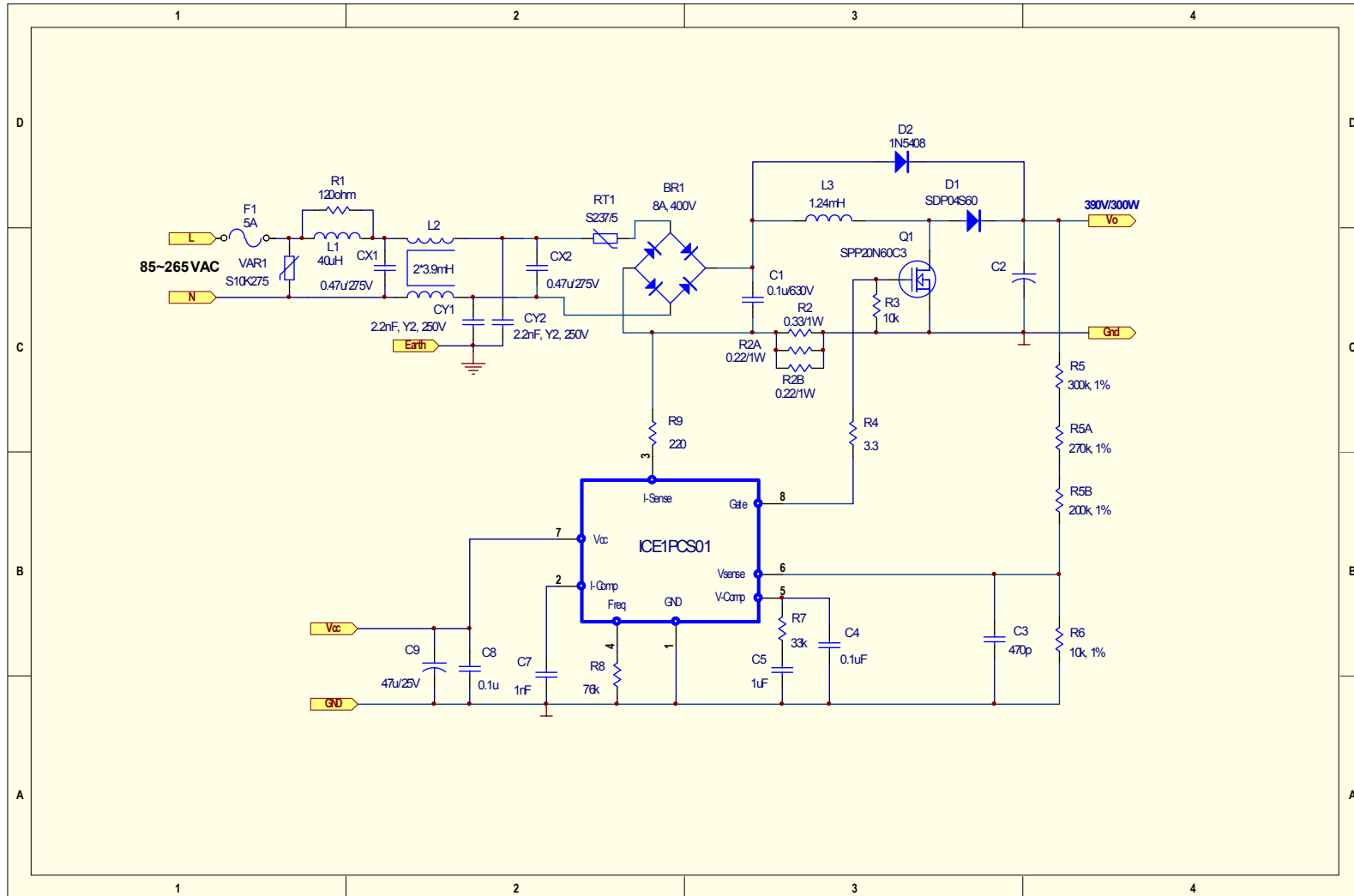

PCB layout top layer

 

PCB layout Bottom:

 

Component List:

Designator	Part Type	Description	Quantity
BR1	8A, 400V	Bridge Rectifier	1
C1	0.1uF/630V	Ceramic Cap	1
C2	220uF/450V	Electrolytic Cap	1
C4	0.1uF/50V	Ceramic Cap	1
C5	1uF/50V	Ceramic Cap	1
C7	1nF/50V	Ceramic Cap	1
C8	0.1uF/50V	Ceramic Cap	1
C9	47uF/25V	Electrolytic Cap	1
CX1	0.47uF, X1, 275V	Ceramic Cap	1
CX2	0.47uF, X1, 275V	Ceramic Cap	1
CY1	2.2nF, Y2, 250V	Ceramic Cap	1
CY2	2.2nF, Y2, 250V	Ceramic Cap	1
		Connector	3
D1	SDT04S60	Diode	1
D2	1N5408	Diode	1
F1	5A	Fuse	1
		Fuse Holder	2
IC1	ICE1PCS01		1
JP1	12.5mm, Φ0.7mm	Jumper	1
JP2	20mm, Φ0.7mm	Jumper	1
JP3	12mm, Φ1.2mm	Jumper	1
JP4	17.5mm, Φ0.7mm	Jumper	1
L1*	Shorted		0
L2	2*3.9mH	CM Choke	1
L3	1.24mH	Choke	1
Q1	SPP20N60C3	Power MOSFET	1
		Heat Sink	1
		TO220 Clip	2
		TO247 Clip	1
		TO220 Isolation Pad	2
		3mm Screw	3
R2	0.33/1W, 5%	Metal Film Resistor	1
R2A	0.22/1W, 5%	Metal Film Resistor	1
R2B	0.22/1W, 5%	Metal Film Resistor	1
R3	10k/0.25W, 5%	Carbon Film Resistor	1
R4	3.3/0.25W, 5%	Carbon Film Resistor	1
R5	300k/0.25W, 1%	Carbon Film Resistor	1
R5A	270k/0.25W, 1%	Carbon Film Resistor	1
R5B	200k/0.25W, 1%	Carbon Film Resistor	1
R6	10k/0.25W, 1%	Carbon Film Resistor	1
R7	33k/0.25W, 5%	Carbon Film Resistor	1
R8	76k/0.25W, 1%	Carbon Film Resistor	1
R9	220/0.25W, 5%	Carbon Film Resistor	1
RT1	S237/5	NTC Thermistor	1
VAR1	S10K275	Varistor	1



Boost Choke Layout

Core: CS468125 toriod

Turns: 83

Wire: 1 x Φ 1.0mm, AWG19

Inductance: L=1.24mH



Test report

Load test (table and figure):

Vin (VAC)	Pin (W)	Iin (A)	Vout (V)	Iout (A)	Pout (W)	efficiency	PF
85	320	3.8	399	0.75	299.3	94%	1
	253	3	399	0.59	235.4	93%	1
	209	2.5	399	0.49	195.5	94%	0.99
	167	2	399	0.39	155.6	93%	0.99
	124	1.5	399	0.29	115.7	93%	0.99
	82	0.99	399	0.19	75.8	92%	0.98
	40	0.51	399	0.09	35.9	90%	0.93
	26	0.37	399	0.06	23.9	92%	0.85
	19	0.29	399	0.043	17.2	90%	0.78
	11	0.18	399	0.024	9.6	87%	0.71
110	7.2	0.13	399	0.015	6.0	83%	0.65
	316	2.9	399	0.75	299.3	95%	0.99
	248	2.3	399	0.59	235.4	95%	0.99
	206	1.9	399	0.49	195.5	95%	0.99
	165	1.5	399	0.39	155.6	94%	0.98
	123	1.2	399	0.29	115.7	94%	0.98
	82	0.78	399	0.19	75.8	92%	0.95
	39	0.43	399	0.09	35.9	92%	0.83
	27	0.31	399	0.06	23.9	89%	0.77
	19	0.24	399	0.043	17.2	90%	0.73
220	11	0.15	399	0.024	9.6	87%	0.65
	7.2	0.11	399	0.015	6.0	83%	0.58
	307	1.4	399	0.75	299.3	97%	0.98
	246	1.2	399	0.6	239.4	97%	0.97
	205	1	399	0.5	199.5	97%	0.96
	164	0.8	399	0.4	159.6	97%	0.94
	124	0.63	399	0.3	119.7	97%	0.9
	83	0.45	399	0.25	79.8	96%	0.82
	43	0.29	399	0.2	40.0	93%	0.66
	25.6	0.21	399	0.1	23.9	93%	0.55
265	17.4	0.15	399	0.04	16.0	92%	0.51
	13.5	0.13	399	0.03	12.0	89%	0.47
	6.7	0.093	399	0.015	6.0	89%	0.33
	305	1.2	399	0.75	299.3	98%	0.97
	244	0.96	399	0.6	239.4	98%	0.96
265	203	0.81	399	0.5	199.5	98%	0.95
	162	0.67	399	0.4	159.6	99%	0.92
	122	0.52	399	0.3	119.7	98%	0.88
	82	0.39	399	0.2	79.8	97%	0.8
	42	0.26	399	0.1	39.9	95%	0.6




	17	0.14	399	0.04	16.0	94%	0.49
	13.5	0.13	399	0.03	12.0	89%	0.41
	6.8	0.11	399	0.015	6.0	88%	0.22

  

Harmonic test according to EN61000-3-2 Class D requirement

1. 85VAC, full load (300W output)

 

16-Nov-05
16:39:50

Harmonic	Frequency[Hz]	Measurement[mA]	Limit[mA]
3	150.00	126.32	1057.05
5	250.00	47.41	590.71
7	350.00	22.33	310.90
9	450.00	7.63	155.45
11	550.00	5.87	108.81
13	650.00	3.55	92.07
15	750.00	13.33	79.89
17	850.00	8.57	70.41
19	950.00	9.99	63.99
21	1050.00	9.14	57.00
23	1150.00	8.13	52.04
25	1250.00	9.65	47.88
27	1350.00	10.14	44.33
29	1450.00	3.40	41.27
31	1550.00	7.57	38.61
33	1650.00	7.07	36.27
35	1750.00	6.66	34.20
37	1850.00	7.16	32.35
39	1950.00	5.60	30.69

LINE POWER

Class D
Frequency
50.00Hz


Show Graph

Units
dBuA

50 kS/s

AUTO

2. 85VAC, 9% of full load (28W output)

 

16-Nov-05
16:42:08

Harmonic	Frequency[Hz]	Measurement[mA]	Limit[mA]
3	150.00	10.62	94.88
5	250.00	2.83	53.02
7	350.00	6.29	27.90
9	450.00	7.92	19.95
11	550.00	5.92	9.77
13	650.00	6.90	8.26
15	750.00	4.01	7.16
17	850.00	5.29	6.32
19	950.00	3.80	5.65
21	1050.00	3.49	5.12
23	1150.00	0.07	4.67
25	1250.00	0.14	4.39
27	1350.00	0.40	3.98
29	1450.00	0.02	3.70
31	1550.00	0.18	3.47
33	1650.00	0.15	3.26
35	1750.00	0.23	3.07
37	1850.00	0.15	2.90
39	1950.00	0.22	2.75

LINE POWER

Class D
Frequency
50.00Hz


Show Graph

Units
dBuA

50 kS/s

AUTO

3. 265VAC, full load (300W output)

 

16-Nov-05
17:33:09

Harmonic	Frequency[Hz]	Measurement[mA]	Limit[mA]
3	150.00	87.74	877.64
5	250.00	10.23	378.68
7	350.00	2.58	199.30
9	450.00	4.27	99.65
11	550.00	3.34	69.76
13	650.00	2.15	59.02
15	750.00	1.79	51.15
17	850.00	2.56	45.14
19	950.00	2.51	40.39
21	1050.00	1.35	36.54
23	1150.00	1.15	33.36
25	1250.00	1.41	30.69
27	1350.00	2.19	28.42
29	1450.00	1.42	26.46
31	1550.00	1.82	24.75
33	1650.00	1.57	23.25
35	1750.00	1.05	21.92
37	1850.00	1.62	20.74
39	1950.00	0.98	19.67

LINE POWER

Class D
Frequency
49.97Hz


Show Graph

Units
dBuA

100 kS/s

AUTO

4. 265VAC, 9% of full load (28W output)

 

16-Nov-05 16:54:15

Harmonic	Frequency [Hz]	Measurement [mV]	Limit [mV]
3	150.00	11.46	44.25
5	250.00	9.78	24.73
7	350.00	4.64	13.01
9	450.00	4.31	6.51
11	550.00	1.37	4.56
13	650.00	0.65	3.85
15	750.00	0.32	3.34
17	850.00	0.23	2.95
19	950.00	0.28	2.64
21	1050.00	0.46	2.39
23	1150.00	0.55	2.18
25	1250.00	0.33	2.00
27	1350.00	0.45	1.86
29	1450.00	0.62	1.73
31	1550.00	0.53	1.62
33	1650.00	0.47	1.52
35	1750.00	0.10	1.43
37	1850.00	0.48	1.35
39	1950.00	0.71	1.28

LINE POWER

Class D
Frequency
50.00Hz


Show Graph

Units
dBuA


50 kS/s
AUTO

Waveforms (soft start, load jump, open loop)


1. Soft start, test at 85VAC, Iout=0.2A

 

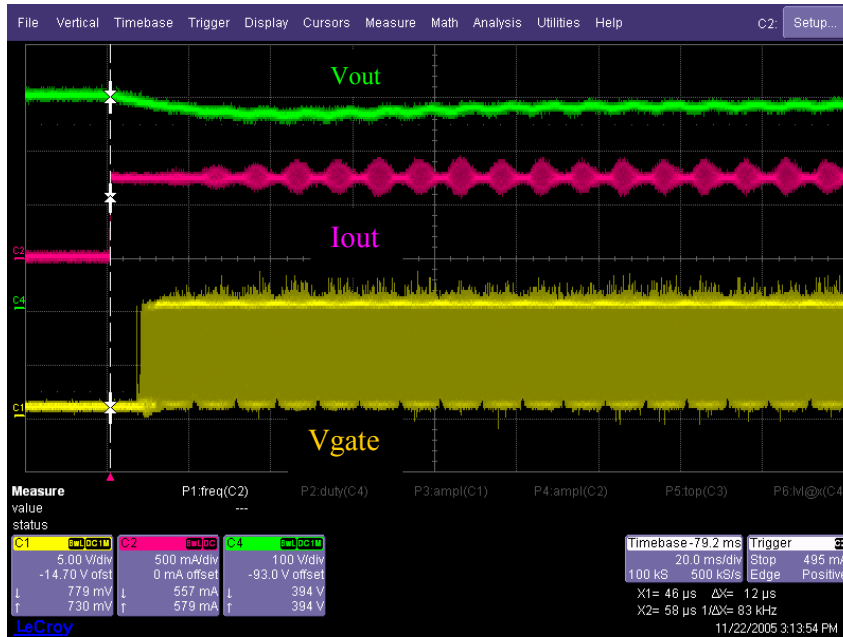
2. Load jump test at 85VAC, Iout from 0A to 0.75A



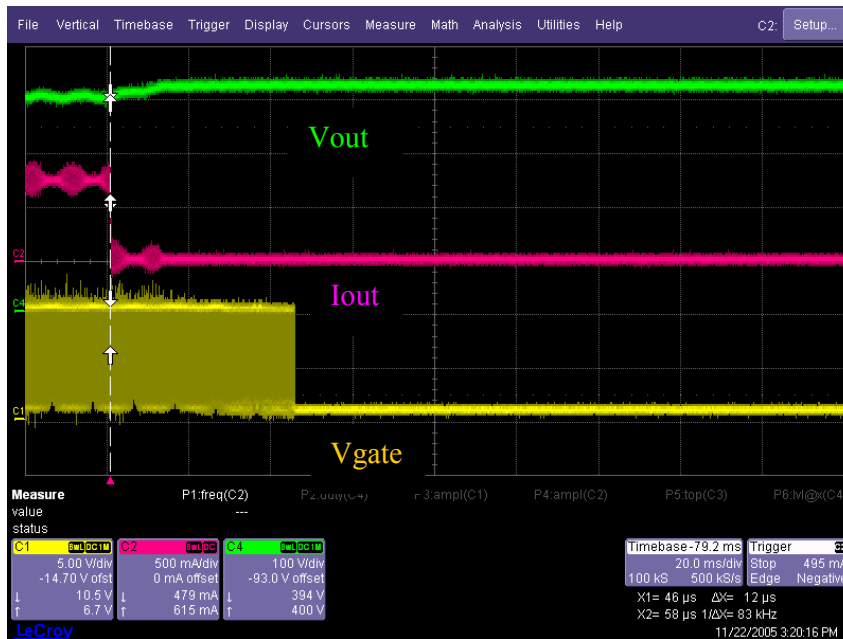3. Load jump test at 85VAC, Iout from 0.75A to 0A



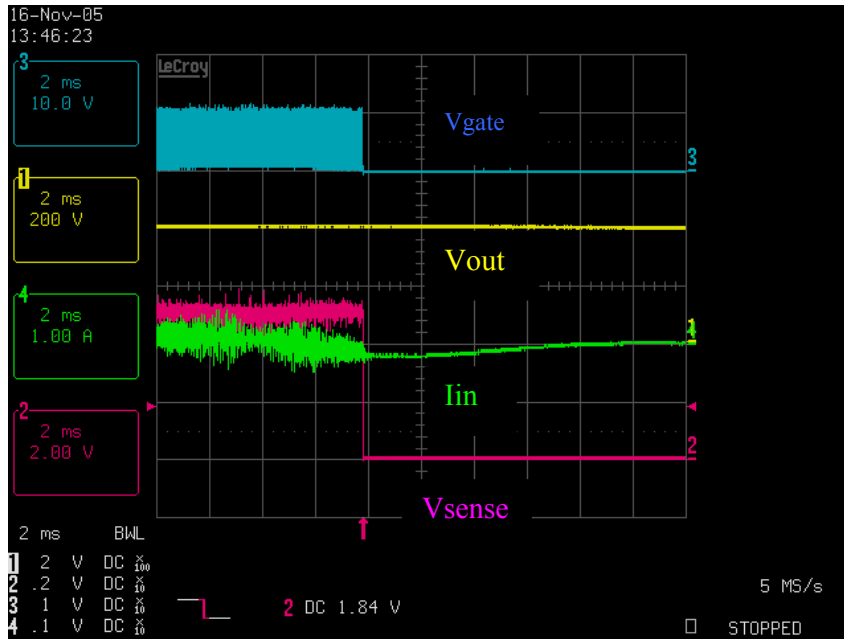4. Open loop test at 265VAC, $I_{out}=0.1A$





References:

- [1] Infineon Technologies: ICE1PCS01 - Standalone Power Factor Correction Controller in Continuous Conduction Mode; Preliminary datasheet; Infineon Technologies; Munich; Germany; May 2003.
- [2] Junyang Luo, Meng Kiat Jeoh, Ming Lik Yew and Heng Cheong Huang, Novel Cost Effective CCM PFC Controller, application note, Infineon Technologies, May 2003.