



Please note that Cypress is an Infineon Technologies Company.

The document following this cover page is marked as “Cypress” document as this is the company that originally developed the product. Please note that Infineon will continue to offer the product to new and existing customers as part of the Infineon product portfolio.

Continuity of document content

The fact that Infineon offers the following product as part of the Infineon product portfolio does not lead to any changes to this document. Future revisions will occur when appropriate, and any changes will be set out on the document history page.

Continuity of ordering part numbers

Infineon continues to support existing part numbers. Please continue to use the ordering part numbers listed in the datasheet for ordering.



THIS SPEC IS OBSOLETE

Spec No: 002-17968

Spec Title: AN217968 - DESIGNING A POWER MANAGEMENT SYSTEM WITH MB3800 BOOST TOPOLOGY

Replaced by: None

Designing a Power Management System with MB3800 Boost Topology

Author: Atsushi Tsurumaru

Associated Part Family: **MB3800**

Related Documents: **MB3800 Datasheet**

AN217968 explains how to select components for a power management system with MB3800, Cypress's one-channel power management IC (PMIC.)

1 Introduction

MB3800 is 1-ch low-voltage PMIC with a built-in soft-start function and short-circuit detection function. The minimum operating voltage is as low as 1.8 V that helps provide optimum power to battery-powered electronic devices. The output voltage can be set by an external resistor. [Figure 1](#) shows a block diagram of 1-ch boost DC/DC controller using MB3800. You should keep certain considerations in mind when you design a power supply system with MB3800.


Figure 1. Power Management System Block Diagram



2 Component Selection for Boost DC/DC Converter

[Figure 2](#) depicts the boost DC/DC converter circuit as an MB3800 application example. This section explains how to choose each component shown in the figure.

Figure 2. Boost Circuit

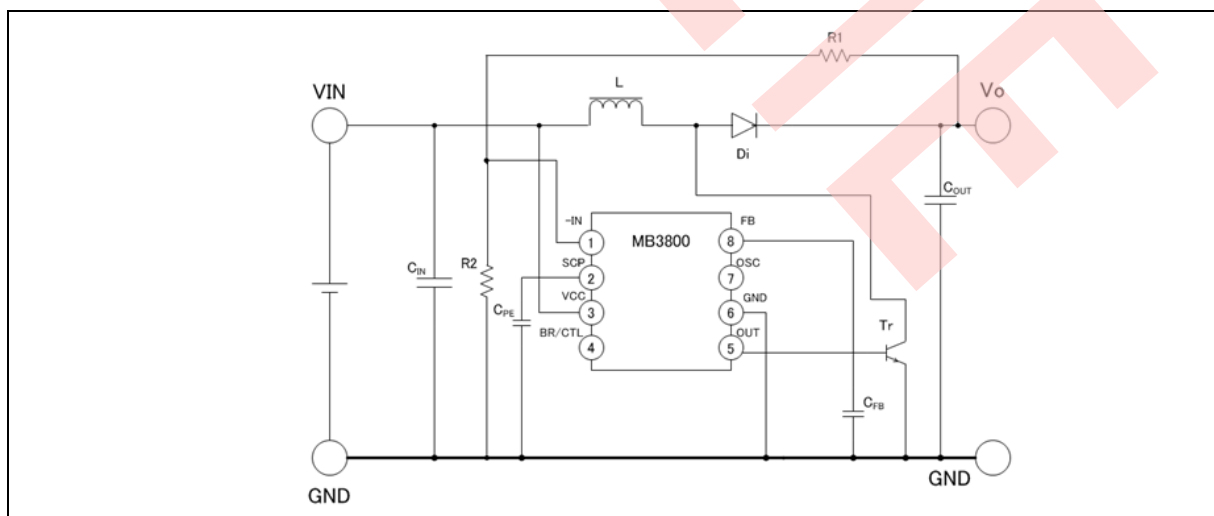

2.1 Output Setting Resistors (R1, R2)

A pair of voltage-dividing resistors (R1 and R2) configures the output voltage (Vo) according to [Equation 1](#).

Equation 1

$$V_o = V_T \times \frac{R1 + R2}{R2}$$

Where:

R1, R2: Output voltage setting resistance (Ω)

V_T: Input threshold voltage at -IN pin = 0.5 (V)

V_o: Output setting voltage (V)

2.2 Inductor (L)

Generally, the inductance of the inductor will be selected along with the value of the E6 series. You should calculate the maximum current value using [Equation 2](#) to confirm whether the electric current that flows through the inductor is within the rated parameters for the inductor.

Equation 2

$$I_{L_MAX} \geq \frac{V_o \times I_{O_MAX}}{V_{IN_MIN}} + \frac{\Delta I_L}{2}, \quad \Delta I_L = \frac{V_{IN_MIN}}{L} \times \frac{V_o - V_{IN_MIN}}{V_o \times f_{osc}}$$

Where:

I_{L_MAX}: Rated current of inductor (A)

I_{O_MAX}: Maximum load current (A)

ΔI_L : Ripple current peak-to-peak value of inductor (A)

L: Inductance of inductor (H)

V_{IN_MIN}: Minimum power supply voltage (V)

V_o: Output setting voltage (V)

f_{osc}: Switching frequency (Hz)

2.3 Input Capacitor (C_{IN})

A ceramic capacitor that has a low equivalent series resistance (ESR), typically less than 10 m Ω , and excellent frequency characteristics—that is, the capacitance is not reduced up to the switching frequency—should be used. Generally, the capacitance will be selected along with the value of the E6 series. A value greater than 20 μ F is recommended. Calculate the necessary rated voltage of the input capacitor by using [Equation 3](#).

Equation 3

$$V_{CIN} > V_{IN}$$

Where

V_{CIN}: Rated voltage of input capacitor (V)

V_{IN}: Power supply voltage (V)

2.4 Output Capacitor (C_{OUT})

A ceramic capacitor that has a low ESR and excellent frequency characteristics should be used. Generally, the capacitance will be selected along with the value of the E6 series. A value greater than 20 μ F is recommended. When considering a ceramic capacitor, you should take into account the reduction of capacitance due to the DC bias characteristics of the capacitor itself. Generally, a large capacitor has a stable DC bias characteristic. Calculate the necessary rated voltage of the output capacitor by using [Equation 4](#).

Equation 4

$$V_{COUT} > V_O$$

Where:

V_{COUT}: Rated voltage of output capacitor (V)

V_O: Output setting voltage (V)

2.5 NPN Switching Transistor (Tr)

Calculate the maximum collector current value using Equation 5 to confirm whether the collector current of the NPN switching transistor is within the rated parameters for the transistor.

Equation 5

$$I_C \geq \frac{V_O \times I_{O_MAX}}{V_{IN_MIN}} + \frac{V_{IN_MIN}}{2L} \times \frac{V_O - V_{IN_MIN}}{V_O \times f_{OSC}}$$

Where:

I_C: Rated current of transistor (A)

I_{O_MAX}: Maximum load current (A)

L: Inductance of inductor (H)

V_{IN_MIN}: Minimum Power supply voltage (V)

V_O: Output setting voltage (V)

f_{OSC}: Switching frequency (Hz)

Calculate the required hfe value using Equation 6 to confirm whether the peak collector current can be supplied by the base current of the NPN switching transistor.

Equation 6

$$hfe \geq \frac{1}{I_B} \times \left(\frac{V_O \times I_{O_MAX}}{V_{IN_MIN}} + \frac{V_{IN_MIN}}{2L} \times \frac{V_O - V_{IN_MIN}}{V_O \times f_{OSC}} \right)$$

Where:

hfe: hfe of NPN switching transistor (A)

I_B: Base current that can be supplied from MB3800=0.02 (A)

I_{O_MAX}: Maximum load current (A)

L: Inductance of inductor (H)

V_{IN_MIN}: Minimum Power supply voltage (V)

V_O: Output setting voltage (V)

f_{OSC}: Switching frequency (Hz)

Calculate the necessary rated voltage of the transistor by using Equation 7.

Equation 7

$$V_{CEO} > V_O$$

Where:

V_{CEO}: Voltage between Tr collector -emitter (V)

V_O: Output setting voltage (V)

2.6 Flyback Diode (Di)

Calculate the necessary rated voltage of the flyback diode by using Equation 8.

Equation 8

$$V_R > V_O$$

Where

V_R : DC reverse voltage (V)

V_O : Output setting voltage (V)

Calculate the necessary rated average current of the diode by using [Equation 9](#).

Equation 9

$$I_{Di} \geq I_O$$

Where

I_{Di} : Diode average current (A)

I_O : Load current (A)

Calculate the necessary rated peak current of the diode by using [Equation 10](#).

Equation 10

$$I_{Dip} \geq \frac{V_O \times I_O}{V_{IN_MIN}} + \frac{V_{IN_MIN}}{2L} \times \frac{V_O - V_{IN_MIN}}{V_O \times f_{OSC}}$$

Where

I_{Dip} : Diode peak current (A)

V_O : Output setting voltage (V)

I_O : Load current (A)

V_{IN_MIN} : Minimum Power supply voltage (V)

L : Inductance of inductor (H)

f_{OSC} : Switching frequency (Hz)

The reverse recovery time of diode ($t_{rr(Di)}$) should be earlier than the turn-on time of the switching T_r ($t_{on(Tr)}$). Calculate the reverse recovery time of diode ($t_{rr(Di)}$) by using [Equation 11](#).

Equation 11

$$t_{on(Tr)} > t_{rr(Di)}$$

Where:

$t_{on(Tr)}$: Turn-on time of the switching T_r (ns)

$t_{rr(Di)}$: Reverse recovery time of diode (ns)

2.7 FB Capacitor (C_{FB})

A ceramic capacitor that has a low ESR and excellent frequency characteristics should be used. Calculate the necessary rated voltage of the capacitor by using [Equation 12](#).

Equation 12

$$V_{CFB} > V_{IN}$$

Where:

V_{IN} : Power supply voltage (V)

V_{CFB} : Rated voltage of FB capacitor (V)

2.8 SCP Capacitor (C_{PE})

The soft-start time and short detection time can be set by the SCP capacitor (C_{PE}).

2.8.1 Soft Start

At power on, the capacitor C_{PE} connected to the SCP pin (pin 2) starts charging. The PWM comparator compares the soft start setting voltage as a proportion of the voltage at the SCP pin with the sawtooth waveform. The comparison controls the ON duty of the OUT pin (pin 5), causing the soft start operation. On completion of the soft start operation, the voltage at the SCP pin stays low, the soft start setting voltage stays high, and the circuit enters the output short circuit detection wait state. Soft start time is the time until the output ON duty reaches approximately 50%.

Equation 13

$$t_S \approx 0.35 \times C_{PE}$$

Where:

t_S : Soft start time (s)

C_{PE} : SCP capacitor value (μF)

A ceramic capacitor that has a low ESR and excellent frequency characteristics should be used for SCP capacitor. Calculate the necessary rated voltage of the capacitor by using [Equation 14](#).

Equation 14

$$V_{CPE} > V_{IN}$$

Where:

V_{IN} : Power supply voltage (V)

V_{CPE} : Rated voltage of SCP capacitor (V)

2.8.2 Short Circuit Protection

Calculate the short-circuit detection time by using [Equation 15](#).

Equation 15

$$t_{PE} \approx 0.8 \times C_{PE}$$

Where:

t_{PE} : Short circuit detection time (s)

C_{PE} : SCP capacitor value (μF)

A ceramic capacitor that has a low ESR and excellent frequency characteristics should be used for SCP capacitor. Calculate the necessary rated voltage of the capacitor by using [Equation 16](#).

Equation 16

$$V_{CPE} > V_{IN}$$

Where:

V_{IN} : Power supply voltage (V)

V_{CPE} : Rated voltage of SCP capacitor (V)

Document History

Document Title: AN217968 – Designing a Power Management System with MB3800 Boost Topology

Document Number: 002-17968

Revision	ECN	Orig. of Change	Submission Date	Description of Change
**	5744956	ATTS	05/26/2017	New application note
*A	6460001	SSAS	01/25/2019	Obsoleted

OBSOLETE

Worldwide Sales and Design Support

Cypress maintains a worldwide network of offices, solution centers, manufacturer's representatives, and distributors. To find the office closest to you, visit us at [Cypress Locations](#).

Products

ARM® Cortex® Microcontrollers	cypress.com/arm
Automotive	cypress.com/automotive
Clocks & Buffers	cypress.com/clocks
Interface	cypress.com/interface
Internet of Things	cypress.com/iot
Memory	cypress.com/memory
Microcontrollers	cypress.com/mcu
PSoC	cypress.com/psoc
Power Management ICs	cypress.com/pmic
Touch Sensing	cypress.com/touch
USB Controllers	cypress.com/usb
Wireless Connectivity	cypress.com/wireless

PSoC® Solutions

[PSoC 1](#) | [PSoC 3](#) | [PSoC 4](#) | [PSoC 5LP](#) | [PSoC 6](#)

Cypress Developer Community

[Forums](#) | [WICED IOT Forums](#) | [Projects](#) | [Videos](#) | [Blogs](#) | [Training](#) | [Components](#)

Technical Support

cypress.com/support

All other trademarks or registered trademarks referenced herein are the property of their respective owners.



Cypress Semiconductor
198 Champion Court
San Jose, CA 95134-1709

© Cypress Semiconductor Corporation, 2017-2019. This document is the property of Cypress Semiconductor Corporation and its subsidiaries, including Spansion LLC ("Cypress"). This document, including any software or firmware included or referenced in this document ("Software"), is owned by Cypress under the intellectual property laws and treaties of the United States and other countries worldwide. Cypress reserves all rights under such laws and treaties and does not, except as specifically stated in this paragraph, grant any license under its patents, copyrights, trademarks, or other intellectual property rights. If the Software is not accompanied by a license agreement and you do not otherwise have a written agreement with Cypress governing the use of the Software, then Cypress hereby grants you a personal, non-exclusive, nontransferable license (without the right to sublicense) (1) under its copyright rights in the Software (a) for Software provided in source code form, to modify and reproduce the Software solely for use with Cypress hardware products, only internally within your organization, and (b) to distribute the Software in binary code form externally to end users (either directly or indirectly through resellers and distributors), solely for use on Cypress hardware product units, and (2) under those claims of Cypress's patents that are infringed by the Software (as provided by Cypress, unmodified) to make, use, distribute, and import the Software solely for use with Cypress hardware products. Any other use, reproduction, modification, translation, or compilation of the Software is prohibited.

TO THE EXTENT PERMITTED BY APPLICABLE LAW, CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS DOCUMENT OR ANY SOFTWARE OR ACCOMPANYING HARDWARE, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. No computing device can be absolutely secure. Therefore, despite security measures implemented in Cypress hardware or software products, Cypress does not assume any liability arising out of any security breach, such as unauthorized access to or use of a Cypress product. In addition, the products described in these materials may contain design defects or errors known as errata which may cause the product to deviate from published specifications. To the extent permitted by applicable law, Cypress reserves the right to make changes to this document without further notice. Cypress does not assume any liability arising out of the application or use of any product or circuit described in this document. Any information provided in this document, including any sample design information or programming code, is provided only for reference purposes. It is the responsibility of the user of this document to properly design, program, and test the functionality and safety of any application made of this information and any resulting product. Cypress products are not designed, intended, or authorized for use as critical components in systems designed or intended for the operation of weapons, weapons systems, nuclear installations, life-support devices or systems, other medical devices or systems (including resuscitation equipment and surgical implants), pollution control or hazardous substances management, or other uses where the failure of the device or system could cause personal injury, death, or property damage ("Unintended Uses"). A critical component is any component of a device or system whose failure to perform can be reasonably expected to cause the failure of the device or system, or to affect its safety or effectiveness. Cypress is not liable, in whole or in part, and you shall and hereby do release Cypress from any claim, damage, or other liability arising from or related to all Unintended Uses of Cypress products. You shall indemnify and hold Cypress harmless from and against all claims, costs, damages, and other liabilities, including claims for personal injury or death, arising from or related to any Unintended Uses of Cypress products.

Cypress, the Cypress logo, Spansion, the Spansion logo, and combinations thereof, WICED, PSoC, CapSense, EZ-USB, F-RAM, and Traveo are trademarks or registered trademarks of Cypress in the United States and other countries. For a more complete list of Cypress trademarks, visit cypress.com. Other names and brands may be claimed as property of their respective owners.