

PSoC® 3 and PSoC 5LP - Single-Cell Lithium-Ion (Li-ion) Battery Charger

Author: Archana Yarlagadda, Rajiv Badiger

Associated Project: Yes

Associated Part Family: All PSoC 3 and PSoC 5LP Parts

Software Version: PSoC® Creator™ 3.3 or Higher

Related Application Notes: [AN55102](#)

More code examples? We heard you.

To access an ever-growing list of hundreds of PSoC code examples, please visit our [code examples web page](#). You can also explore the PSoC 4 video library [here](#).

AN73468 explains a single-cell Lithium-Ion (Li-ion) battery charger implementation using PSoC 3 or PSoC 5LP. Two types of implementations — linear and switching type are supported. An attached PSoC Creator project, which includes a charge display tool, demonstrates Li-ion battery charging.

Contents

Introduction	1
Li-Ion Battery Charging Profile	1
Project Implementation.....	3
PSoC Creator Project.....	4
Battery Parameter Measurement	4
Charging Algorithm in Firmware	7
External Current Control Circuit.....	8
Battery Protection Logic	9
Calibration	11
Test Setup and Results	12
USB Communication	12
Charge Display Tool.....	12
Conclusion	12
Appendix A: Buck Circuit Component Selection.....	13
Appendix B: Schematic and Bill of Materials for Switching Method of Current Control.....	15
Appendix C: USB Driver Installation.....	17
Appendix D: Software Tool Installation and Setup	18
Appendix E: Alternative Implementation Options with Tradeoffs.....	20
Biasing Thermistor using IDAC	20
Over Voltage and Over Current Protection.....	20
Battery Current Control with PWM	21
Document History	22

Introduction

Li-ion batteries are used in a wide range of systems such as cameras, cell phones, electric shavers, and toys. The charging circuit for the batteries can either be an integral part of the system (online charging) or an external plug-in circuit (offline charging). With its wide range of devices, PSoC offers a cost-effective solution in both segments. And with its configurable digital and analog features, PSoC 3 or PSoC 5LP enables implementation of other critical tasks required in the system.


Consider a case of an electric shaver that uses Li-ion battery charger logic and a motor to drive the shaver blade. Both of these major tasks can be run from a single PSoC 3 or PSoC 5LP device, which results in lower cost and small PCB size. Small size is important in battery-operated (portable) systems.

Li-Ion Battery Charging Profile

The charge profile used for charging is the constant current (CC) – constant voltage (CV) method. The Li-ion batteries have different states of charging, based on the voltage of the battery as shown in [Figure 1](#). These are:

- Pre-charging (t_{start}) or activation (t_{act})
- Rapid charge or fast charge
 - Constant current (t_{rapid})
 - Constant voltage ($t_{const_voltage}$)
- Charge complete

Figure 1. Charge Profile for Li-ion Battery

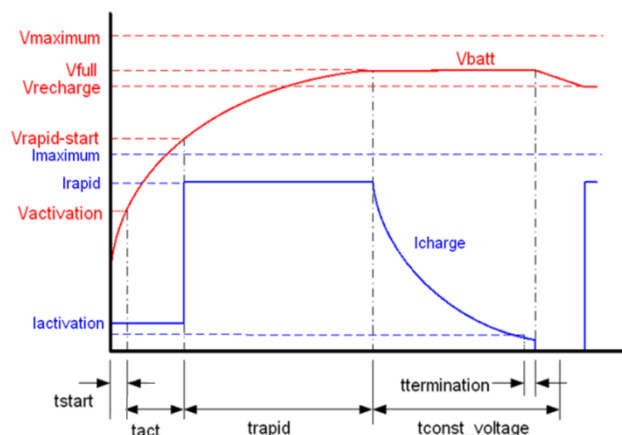

If the battery voltage is less than the activation voltage ($V_{activation}$), the charging process starts with the pre-charge stage where small amount of current ($I_{activation}$ - typically 10% of the battery capacity) is provided to check if the battery is in good condition. Time limit (t_{start}) is kept low for this stage. If the battery voltage does not rise above $V_{activation}$ in t_{start} time, battery is considered faulty and charging is stopped.

When the battery voltage rises above $V_{activation}$, activation stage is entered where charging is continued with the same amount of current. This brings the battery voltage to the rapid charging voltage level. If the battery does not rise to the specified rapid charge voltage within the activation timeout period t_{act} , the battery is considered dead. The activation stage is used when the Li-ion batteries are completely discharged. In most cases, the batteries are not completely discharged and they go directly into the rapid charge stage.

In the rapid charge stage, the charge current is kept equal to the capacity specified for the battery. This constant current is applied until the battery reaches its specified full charge voltage (V_{full}). In this region, the accuracy of voltage measurement is very important for the safety of the battery. The tolerable error in measurement is generally less than $\pm 1\%$ of V_{full} . This application note uses calibration scheme to achieve this target.

After the constant current stage, the battery goes to the constant voltage stage. In this stage, the battery voltage is maintained at a constant level. This requires a decrease in the charging current as the time progresses. When the current value reaches the termination current ($I_{termination}$)


value while the battery voltage is at V_{full} , the charging is considered complete and the current is reduced to zero.

This multi-stage process helps to remove the effects of battery source impedance or any track or connector resistance between the charging system and the battery. The constant current stage features rapid charge until a safest operating voltage (full charge voltage) is reached. The constant voltage stage ensures that the voltage value being read corresponds to the battery voltage and does not include voltage drop across any series resistances.

Besides voltage, temperature of the battery should also be monitored for safety reasons.

Figure 2 shows a simplified block diagram of a battery charger system.

Figure 2. Block Diagram of Battery Charger

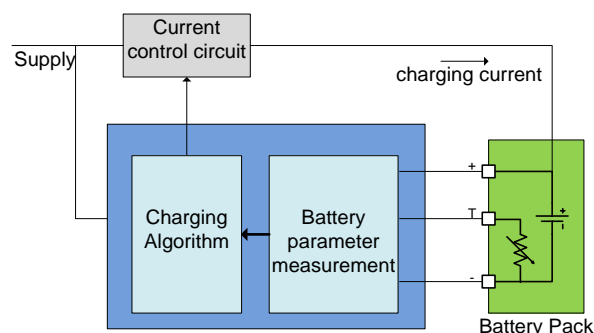

The battery parameter measurement senses the three parameters of the battery: voltage, current, and temperature. These should be maintained within the battery safe range. The logic for controlling these parameters is implemented in the charging algorithm, which can be applied in hardware or in a combination of firmware and hardware. The output of the charging algorithm changes the charge current through the external current control circuit. The current control circuit can be either linear or switching. This application note shows the firmware implementation of both the linear and switching type of charge control. The benefit of a firmware implementation is its adaptability to change in the charging profiles.

The complete block diagram and the functions of each block are explained first, followed by explanation of the PSoC Creator implementation.


Project Implementation

Figure 3 shows the overall block diagram for implementation of the Li-ion battery charger with a PSoC 3 and PSoC 5LP device.

The implementation is divided into the measurement, charging algorithm, and external current control blocks as explained earlier. Additionally, a protection block is added for additional features related to the battery protection. For

more information on each of these blocks and the components used, see [PSoC Creator Project](#). The external current control can be either linear or switching type of implementation. The switching circuit is shown in [Figure 3](#), and the linear circuit is explained in [External Current Control Circuit](#) section. The rest of the circuit and firmware implementation apply to both methods.

Figure 3. Block Diagram for Li-ion Battery Charger with PSoC

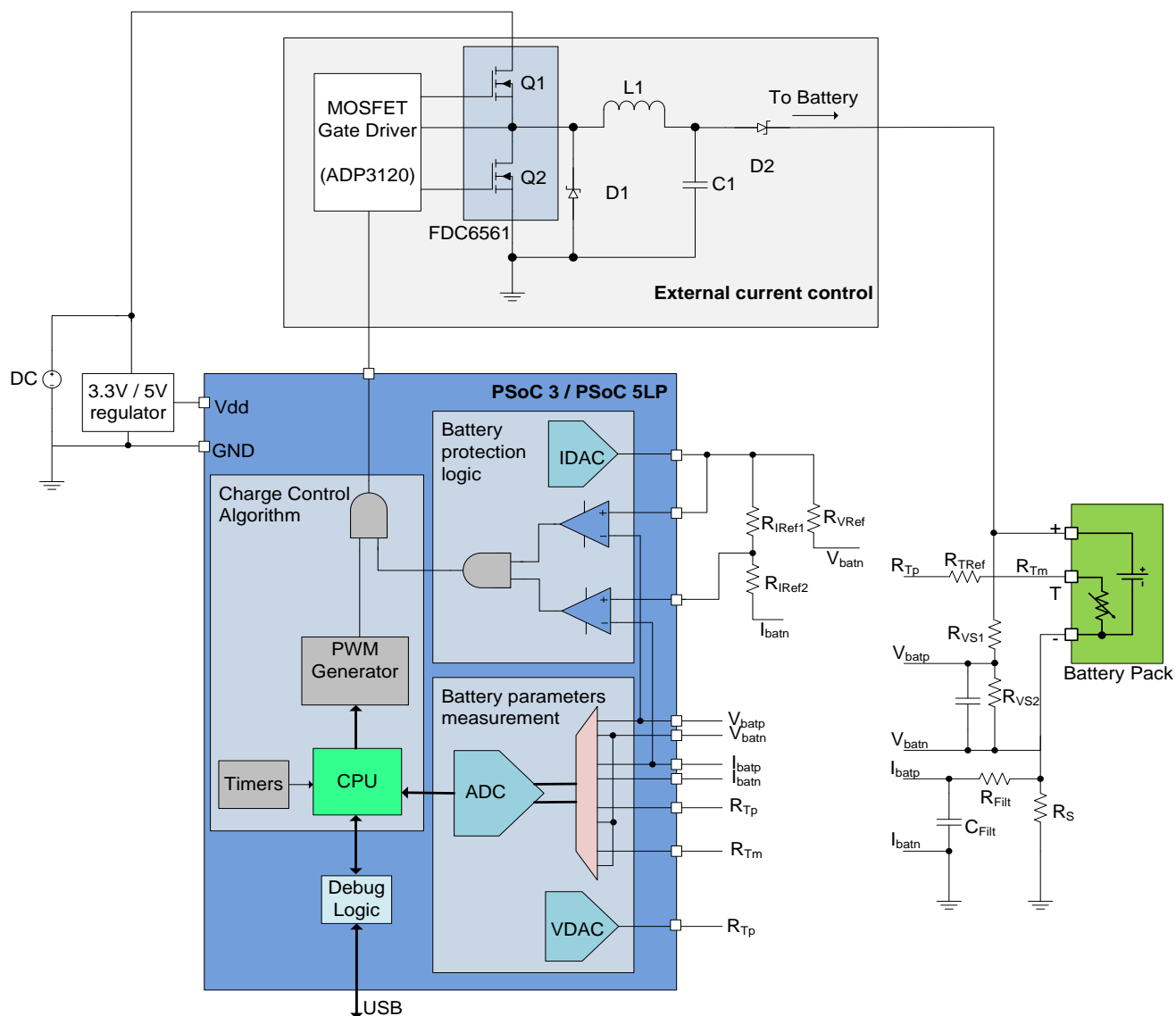


PSoC Creator Project

This section guides you through implementation of the design in PSoC 3 and PSoC 5LP. The complete block diagram is shown in Figure 3, and this section explains each function in detail along with the PSoC components selected to implement them.

Battery Parameter Measurement

Figure 4 shows the battery parameter measurement function in PSoC 3 and PSoC 5LP. The three parameters of interest — voltage, current, and temperature are measured using an ADC

Figure 4. Top Design: Battery Parameter Measurement

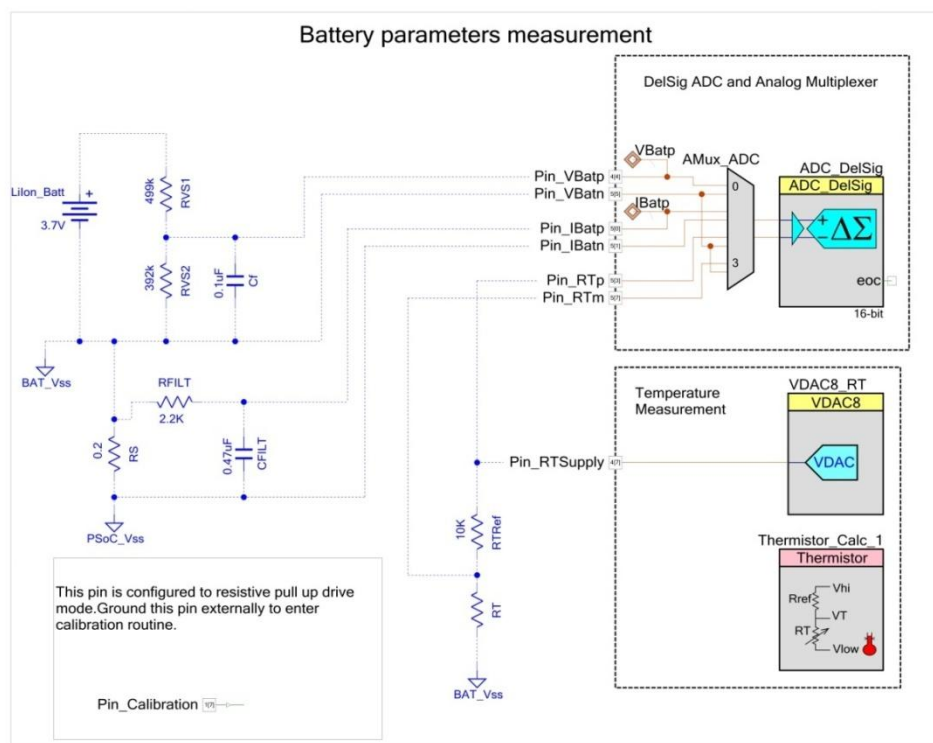


The Delta-Sigma ADC component is multiplexed to measure multiple parameters. For temperature measurement, the standard “Thermistor Calculator” is used in the project. The details about this custom component are provided in application note [AN66477 - PSoC® 3 and PSoC 5LP Temperature Measurement with Thermistor](#). The bias required for this component is generated using the VDAC8 component.

The CPU configures the AMUX channel and reads the ADC to get the parameter values. The configuration of each of these components is described in the following sections.

Delta-Sigma ADC

In the project, the ADC is used to measure battery voltage, charging current, and temperature. Figure 5 shows the ADC_DelSig component configuration.

Figure 5. DelSig ADC Configuration

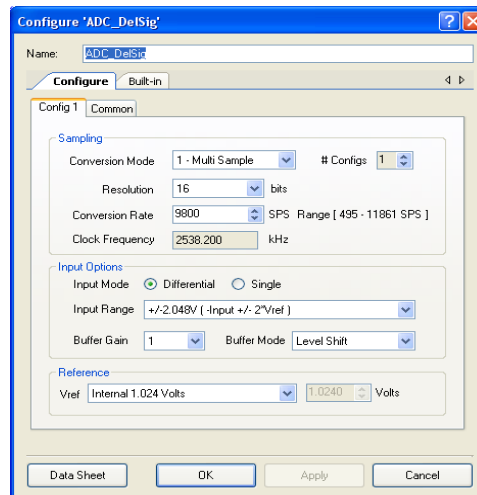

When multiplexing multiple channels to the ADC, set the ADC to Multi-Sample mode. This mode resets the ADC modulator every time a sample is taken, so that the readings for one channel do not affect another channel. The resolution is set to 16 bits with a measurement input range of ± 2.048 V. Based on these settings, the resolution obtained for voltage, current, and temperature is shown in Table 1.

Table 1. Resolution of Parameters Based on ADC Settings

Parameter	Resolution	Notes
Voltage	62.5 μ V / K	<p>K is the scaling factor of the resistor potential divider connected across the battery.</p> $K = \frac{R_{VS1}}{R_{VS1} + R_{VS2}}$ <p>In this design, the following resistors are used:</p> $R_{VS1} = 499 \text{ k}\Omega$ $R_{VS2} = 392 \text{ k}\Omega$ <p>This gives measurement resolution of 142 μV.</p>
Current	62.5 μ V / R_S	In this design, R_S is 0.2 Ω . This gives current resolution of 0.312 mA.
Temperature	± 0.01 °C	<p>Range: 0 to 50 °C</p> <p>$R_{Tref} = 10 \text{ k}\Omega \pm 1\%$ at 25 °C</p>

The conversion rate is set to 9800 samples per second, which can be changed depending on your application requirement.

In the ADC settings, differential measurement is used, because it removes the effect of common mode voltage. Common mode voltage can be a PCB trace voltage drop because of current, induced noise, or offsets.


The DelSig ADC has an input buffer at its differential input. The gain and mode of this buffer are configurable. For this project, “Buffer Gain” is set to 1 and “Buffer Mode” is set to level shift. Level shift mode enables the measurement of voltages close to PSoC ground rail. This is required for current measurement because the voltage across the current sense resistor is very close to the PSoC ground. For example, with a 0.2 Ω current sense resistor and 30 mA termination current, voltage across the sense resistor is 6 mV.

Note These settings are applicable for all the parameters measured. For details of other parameters, see the DelSig ADC component datasheet.

AMUX

The project uses the AMUX component to multiplex different inputs to the ADC. Figure 6 shows the configuration of the AMux_ADC. Four channels are defined, each with a differential type.

Figure 6. AMux_ADC Configuration

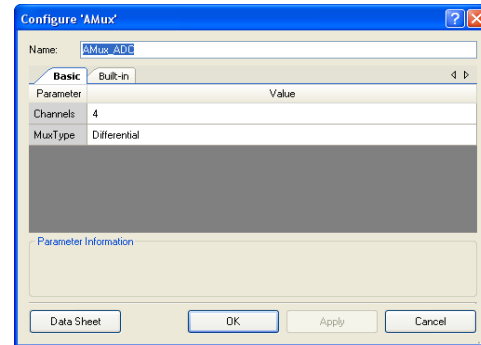

The channel selection is done in firmware. Table 2 shows the allocation of channels.


Table 2. Channel Allocation for AMUX

Channel	Parameter	Port Connections	
		+	-
0	Voltage	Pin_VBatp	Pin_VBatn
1	Current	Pin_IBatp	Pin_IBatn
2	Temperature	Pin_RTp	Pin_VBatn
3	Temperature	Pin_RTm	Pin_VBatn

VDAC

The project uses the VDACC8 component to generate the reference voltage required for the thermistor temperature measurement. Figure 7 shows the configuration of this component.


Figure 7. VDACC8 Configuration

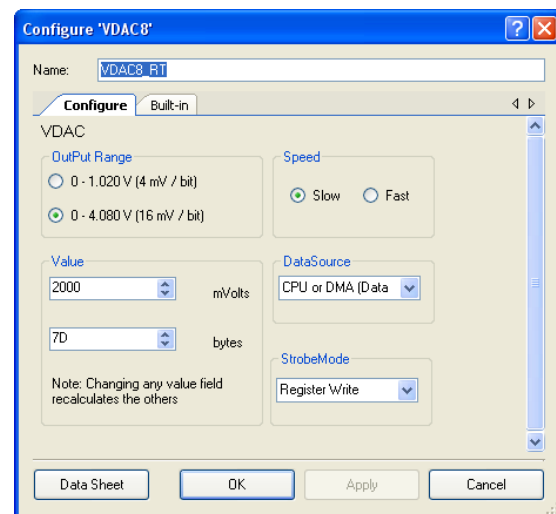

The VDAC output range is set to 4.08 V. This gives a resolution of 16 mV/bit. The VDAC output voltage is used to bias the Thermistor. Make sure that you do not set the VDAC8 output higher than what the ADC DelSig can measure. Note that the ADC measurement range is set to ± 2.048 V. In this project, the VDAC output is set to 2.0 V. This voltage is divided across the reference resistor and the thermistor.

Thermistor Component

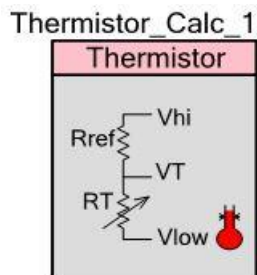
The Thermistor Calculator component is a standard Creator component used with this project.



This component requires one resistor for reference connected in series with the Thermistor. The component takes the ADC readings of both the thermistor voltage and the reference resistor voltage to find the temperature.

The configuration of this component is shown in Figure 8.

Figure 8. Thermistor Configuration

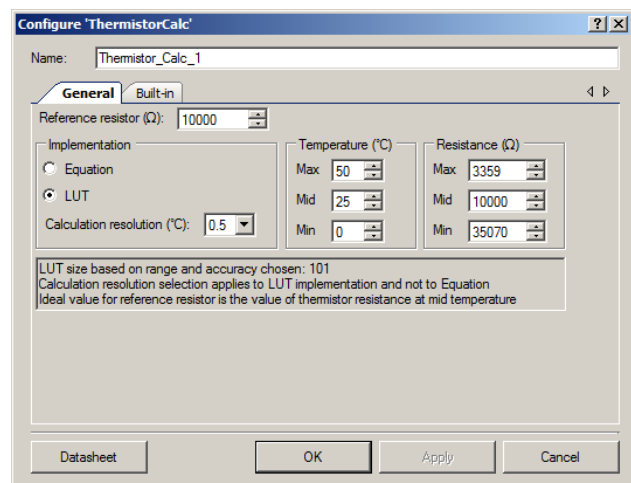


In this design, external reference resistor R_{TRef} of 10 k Ω is connected in series with the Thermistor. Thermistor resistance values at different temperature values are provided for calibration. This design uses Thermistor NTSD1XH103FPB. Its resistance values at three different temperature values (0 °C, 25 °C, and 50 °C) are given to the component for calibration.

For more information about this component, see application note [AN66477 – PSoC® 3 and PSoC 5LP Temperature Measurement with Thermistor](#).

External Circuitry

This section gives details about the external components required for the battery parameter measurement. These components appeared in previous block diagrams and in Figure 9.

Figure 9. External Connections - Measurement

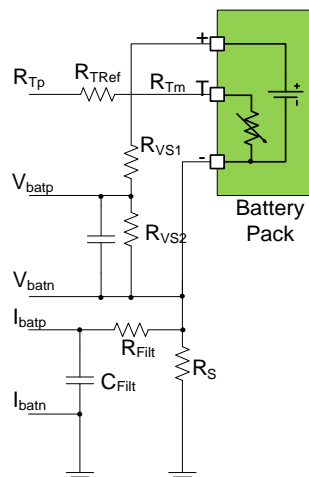

Voltage Sense

Voltage sense is implemented by attenuating the battery voltage to the range of the ADC, using the resistors - R_{VS1} and R_{VS2} . The sum of these resistor values should be greater than 100 k Ω to minimize the loss of charge current through the resistors. The present design uses R_{VS1} of 499 k Ω and R_{VS2} of 392 k Ω .

Current Sense

The current sense is implemented by using a small value resistor on the low side of the battery. The R_S resistor shown in Figure 9 is used for current sense. The value of this resistor should be such that the maximum current allowed through the battery is less than the power rating of the resistor. There is a trade-off between the signal integrity (requires higher R_S) and power dissipation (requires lower R_S). Typically, for a charge current of 1 A, a resistor value less than 0.5 Ω can be used to prevent more than 0.5 W of power dissipation. The actual number for the allowed power dissipation will depend on your target application specification. This design uses R_S of 0.2 Ω .

The voltage across R_S is filtered using an RC low-pass filter to remove switching noise. You must set the cut-off frequency of the filter to be much lower than the switching frequency.

Temperature Sense

The VDAC gives a constant voltage to the thermistor (R_T) and its reference resistance (R_{TRef}). This method has the benefits of offset and gain error cancellations. A Thermistor component is used for the implementation of the temperature measurement. The reference resistor R_{TRef} value should be close to the thermistor resistance at the middle of the temperature range.

An alternative method of implementation is to use an IDAC for constant current implementation. In this method, a constant current is passed through the thermistor, and the change in voltage due to change in thermistor resistance is noted. [Appendix E: Alternative Implementation Options with Tradeoffs](#) shows this option and its implementation.


Charging Algorithm in Firmware

In the project, the CPU has the following major tasks:

- Run the calibration algorithm
- Read the battery voltage, charging current, and temperature
- Update the state machine
- Update the PWM duty cycle


[Figure 10](#) shows the firmware flowchart

Figure 10. Flowchart for Battery Charging

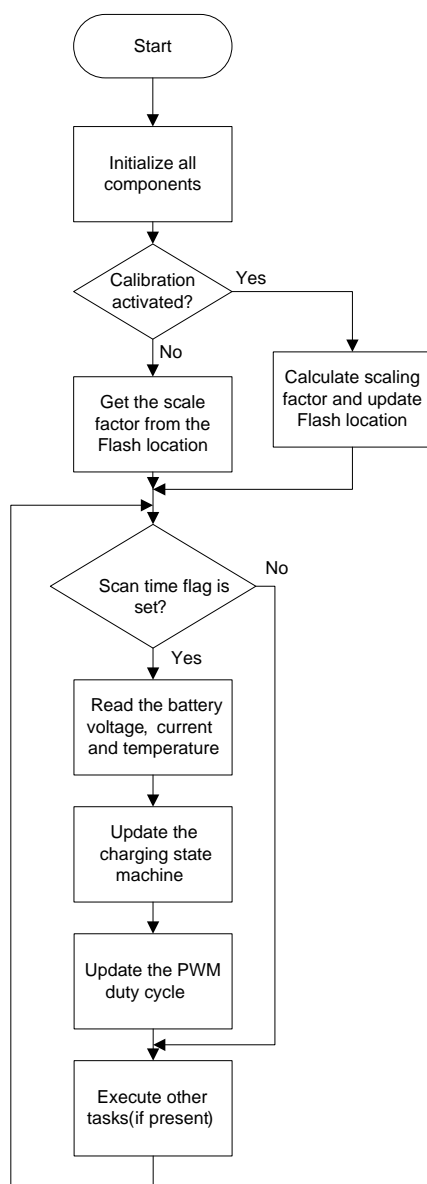

The following is a description of the state machine for the attached project, as shown in Figure 11.

Figure 11. Charger State Machine Diagram

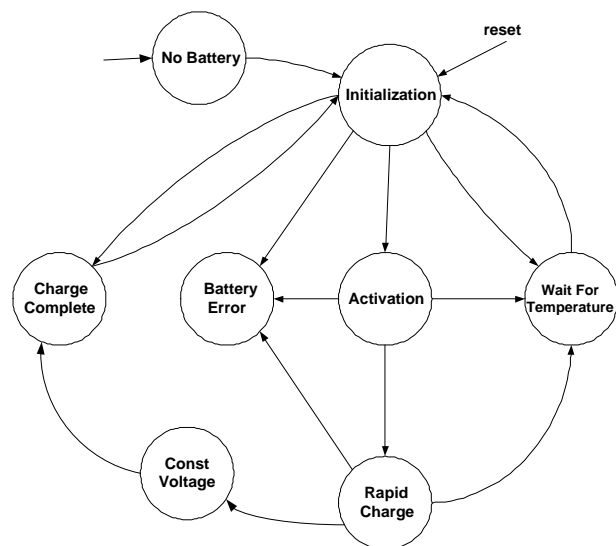

The state machine is updated based on the voltage, temperature, and current charging state of the battery. Figure 11 shows the state machine for the charging process.

- **No Battery state:** The battery is not connected and the charge current is set to zero.
- **Initialization state:** The battery is connected, the voltage is less than the activation voltage, and the charge current is set to activation current.
- **Activation state:** The battery reaches the activation voltage within some time limit. In this state, the charge current is maintained at the activation value.
- **Rapid Charge state:** The voltage is at the rapid charge voltage. The charge current is set to the highest possible value.
- **Constant Voltage state:** The battery voltage is at the rated value, and the current is slowly decreased, while ensuring the battery voltage remains at the rated voltage. The current in this state decreases until the termination current is reached.
- **Charge Complete state:** In this state, battery is completely charged. Charging process is stopped.

During this sequence of steps, if the battery voltage, current, or temperature is out of the specified limits for that state, the state is set to "Battery Error" and the charge current is set to zero to protect the battery.

External Current Control Circuit

As explained earlier, there are two major stages in battery charging: Constant current (CC) and Constant voltage (CV) stage. Both stages require control of charging current. This is achieved by controlling the voltage applied across the battery. Two methods can accomplish this:


- Linear regulator
- Switching regulator

Linear Regulator

This method involves controlling the bias of the series pass transistor (Q2 in Figure 12) to control the current to the battery. The PWM signal is fed to the external RC low-pass filter to get an average DC voltage to bias transistor Q1. Controlling the duty cycle of PWM controls the average DC voltage at the output of the filter. This controls the collector current of Q1 and, therefore, the battery charging current (collector current of Q2). Transistor Q2 also prevents reverse powering of PSoC and reverse current into the supply.

This type of implementation supports limited charging current, for a reasonable cost of the pass transistor. It has the benefit of lower footprint than the switching method.


Figure 12. Linear Current Control Circuit

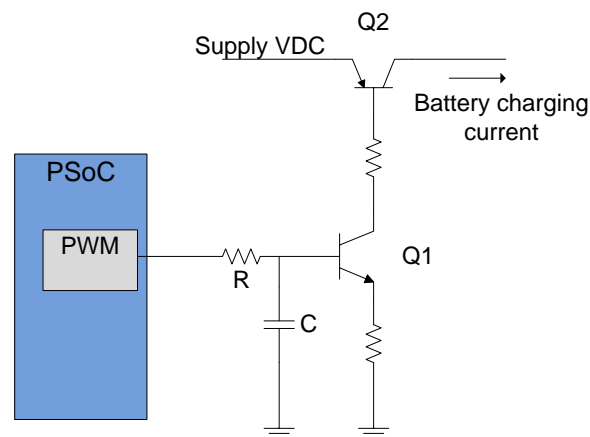

Switching Regulator

This method involves the use of buck or boost switching regulator. This application note uses a buck type switching regulator to supply the required current through the battery. It is implemented using an external MOSFET-FDC6561 and Gate driver ADP3120.

Figure 13. Switching Buck regulator Circuit

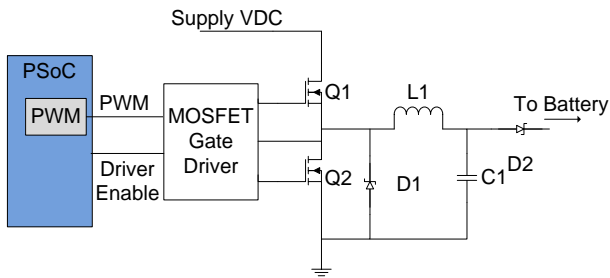

PSoC 3 / PSoC 5LP gives a PWM signal of 500 kHz to the external MOSFET gate driver. The gate driver has two outputs, which drive the gate terminal of two N-channel MOSFETs configured for the buck regulator. Values of inductor L1 and output capacitor C1 are chosen for a desired ripple current and voltage. For more information

on how to select the external components for a buck regulator, see [Appendix A: Buck Circuit Component Selection](#).


Diode D1 is connected across the lower MOSFET to give a freewheeling current path during the dead time when both MOSFETs are off. This dead time is set by the MOSFET gate driver. Diode D2 is used to prevent current from the battery from flowing back to the supply when the supply voltage is less than the battery voltage.

A switching regulator is useful for high-charging currents (>1A) due to its high efficiency.

Battery Protection Logic

Figure 14 shows the over voltage and over current protection logic implementation in PSoC 3 / PSoC 5LP. The output of the comparators controls the PWM generator as shown.

Figure 14. Top Design - Battery Protection

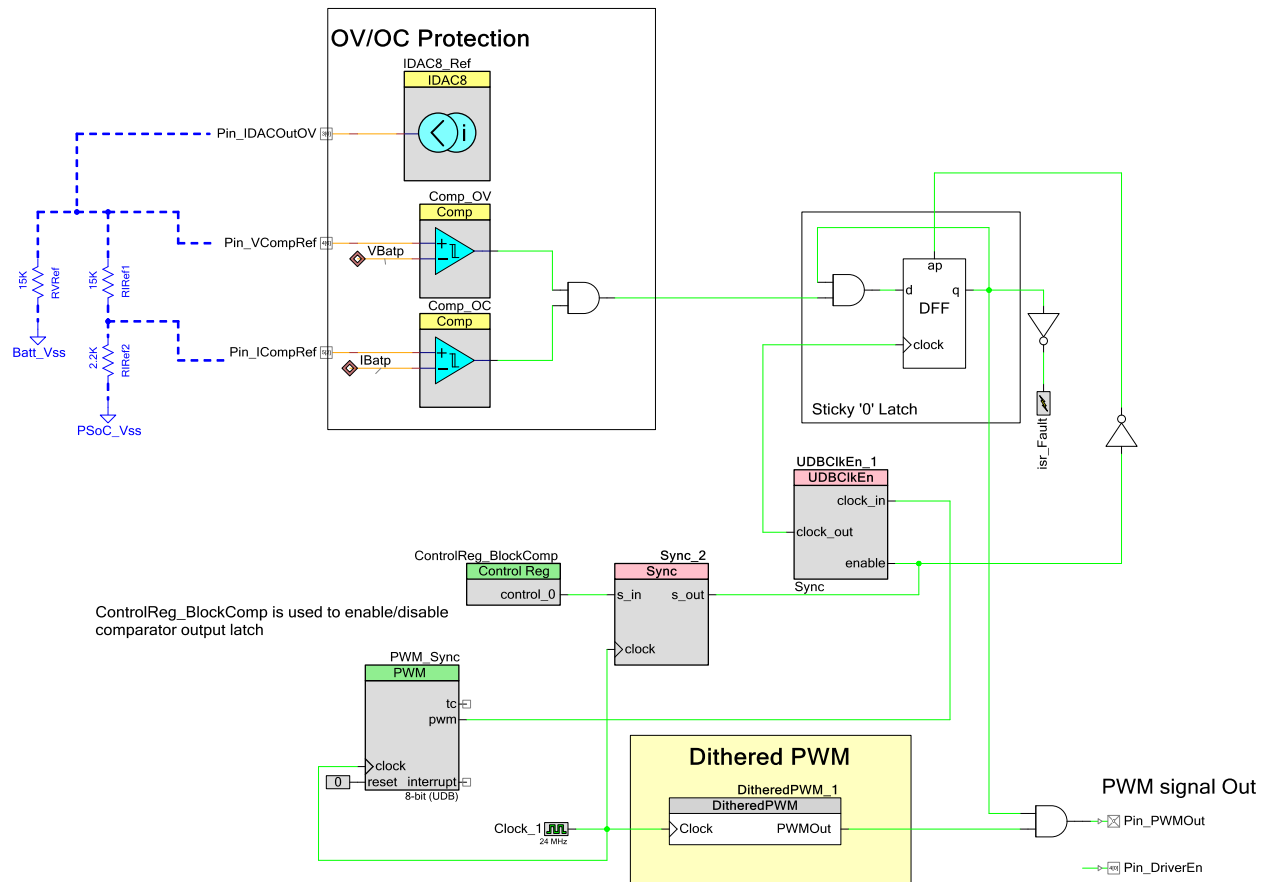

When the battery voltage or battery charging current exceeds the limit set using IDAC8_Ref, the output of comparator goes to zero and is latched in “sticky 0” latch, which disables the PWM. It also causes an interrupt to the CPU to take the required action.


ControlReg_BlockComp is a control register used to enable or disable the latching of comparator output. Comparator output is latched on the rising edge of the PWM_Sync signal. The PWM_Sync signal is generated in such a way that the switching spikes will not trigger the OV/OC protection. During ADC channel switching, comparator output latching is disabled by writing a zero to the ControlReg_BlockComp control register to prevent misfire.

To generate the PWM signal, a custom component “DitheredPWM” is created. It provides higher resolution than the regular PWM component. The configuration of each of the components used in this implementation is explained below:

IDAC8

IDAC8_Ref is used to generate the reference current required to obtain the battery current and voltage limits. The settings for the IDAC are shown in Figure 15. IDAC is configured in sourcing mode in 2.04 mA range. Its value is set based on the threshold voltage required for over voltage and over current in addition to the resistors (RVRef, RIRef1, and RIRef2) selected.


Figure 15. IDAC8 Configuration for OV-OC Circuit

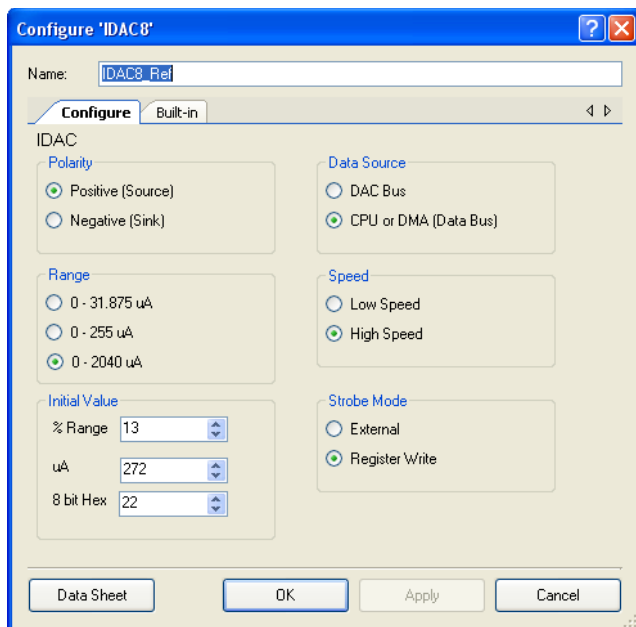

External Circuitry

This section includes the external resistor circuit required along with the internal setup for over voltage and over current implementation.

Figure 16. External Circuitry - Battery Protection

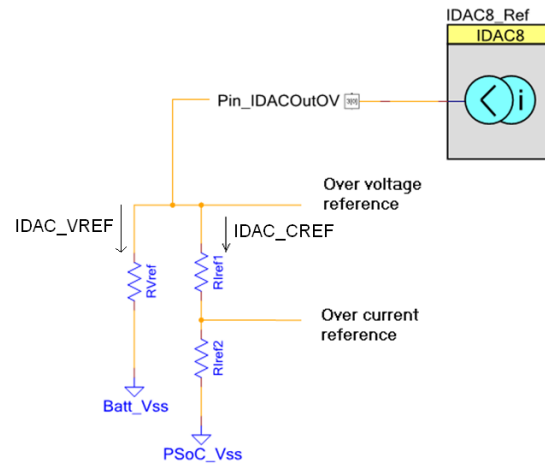

The IDAC current is passed through resistances R_{VRef} , R_{IRef1} , and R_{IRef2} to develop reference voltages.

These resistances must be chosen based on the following equations:

$$R_{VRef} = \frac{V_{max} * R_{Vscale}}{(I_{DAC_VREF})}$$

$$\text{Where } R_{Vscale} = \frac{R_{Vs2}}{(R_{Vs1} + R_{Vs2})}$$

$$R_{IRef1} = \frac{I_{max} * R_s}{(I_{DAC_CREf})}$$

$$R_{IRef2} = \frac{I_{DAC_VREF} * R_{VRef}}{(I_{DAC_CREf})} - R_{IRef1}$$


In these equations, R_{Vs1} , R_{Vs2} , and R_s are chosen based on the requirements described in

Battery Parameter Measurement. V_{max} and I_{max} are defined by the battery chosen. For the sake of calculation, the current in the two resistor paths are assumed first and the resistor values are calculated based on these values. The I_{DAC_VREF} is the current through R_{VRef} . The I_{DAC_CREf} is the current through the reference resistor string, and equal to difference of total IDAC current and I_{DAC_VREF} .

Dithered PWM

Dithered PWM is the custom component included in the project. This design gives high resolution by dithering the duty cycle between two adjacent values. High resolution in the PWM duty cycle is required in the switching method to get a fine variation in current through the battery. Figure 17 shows the design of the Dithered PWM component. These internal components are included for your reference and are placed automatically when the Dithered PWM component is placed.

Figure 17. Dithered PWM Design

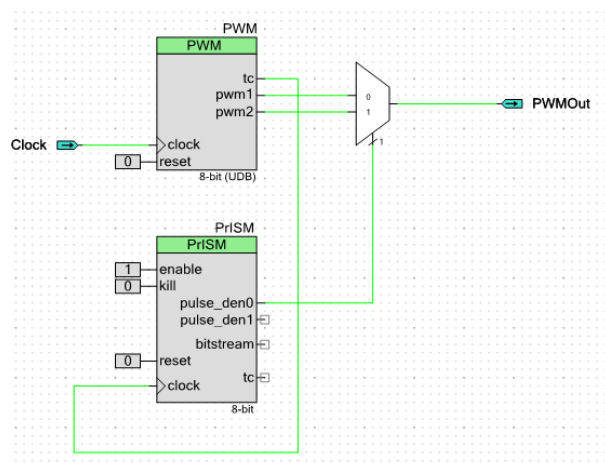

The PWM component generates two PWM signals: pwm1 and pwm2. The pwm2 duty count is kept one more than the pwm1 duty count. Out of the two PWMs, one is selected at a time depending on the PrISM component output. The PrISM component generates a pseudo-random sequence with configurable average duty cycle (or pulse density). It receives a clock input from the terminal count output of the PWM component. By varying the pulse density of the PrISM component, a very fine variation in duty cycle is obtained between two adjacent duty cycle values of the PWM component.

With 8-bit PWM and the PrISM component, you can get a resolution of 16 bits in the duty cycle. The most significant 8 bits of the 16-bit duty cycle value is loaded into the PWM component and the lower significant 8 bits are loaded into the PrISM component.

The Dithered PWM is required for the switching method of implementation. You can use it for the linear method to maintain the same project for the two methods, but a standard Cypress library 16-bit PWM is also sufficient for the linear method. [Appendix E: Alternative Implementation Options with Tradeoffs](#) shows this option of implementation. Other details on custom components can be found in the PSoC Creator Component Author guide.


Timers

Two timers shown in Figure 18 are used in the project for generation of timeouts and interrupts.

Timer_Scan: This 16-bit timer gives periodic interrupts to the CPU to execute the charging state machine.

Timer_TimeOut: This sets the time limit during various stages of battery charging. When a timeout interrupt occurs, charging is stopped.

Figure 18. Timers for Battery Charger

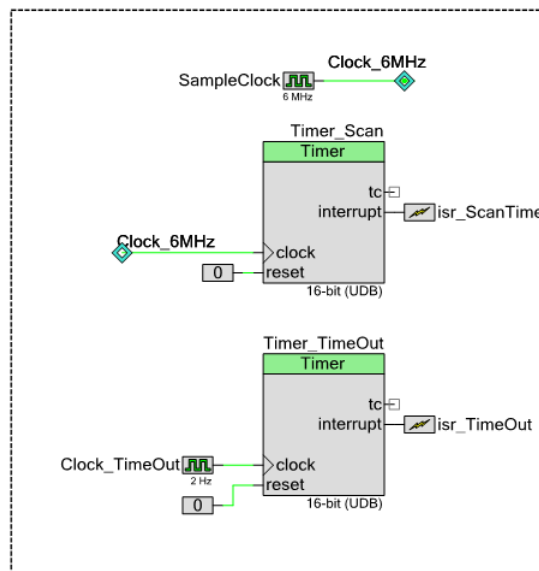

Calibration

During charging, a Li-ion battery requires accurate control of voltage when it is at near full charge; < 0.75% error is widely accepted. As the battery voltage is scaled down using resistors, the scaling factor needs to be accurately known. The error introduced by Delta-Sigma ADC is less than 0.2% error across process, temperature, and supply voltage variations. Therefore, ADC error is negligible. The majority of error is introduced by the potential divider resistor tolerances. Highly accurate resistors with tolerance values as low as 0.01% are available but they are costly. An alternative is to use a low-cost, high-tolerance (1% or 5%) resistor and measure scaling factor in the factory. During this factory calibration, a known voltage can be given in place of the battery. The scaled voltage read by the device divided by the known input voltage is the scaling factor.

In this project, the calibration routine is written which can be invoked by grounding Pin_Calibration (P1[7]). Pin_Calibration is configured in pull-up mode. When the PSoC device is reset, Pin_Calibration is polled to see if it is grounded. If it is, it enters the calibration routine. Otherwise, it takes the scale factor from a flash location.

The flash location will be programmed initially with an approximate value. When the device enters the calibration routine, it assumes a known reference voltage is provided at the battery terminals points. (In this project, 4.2 V is assumed as the reference voltage.) After reading the voltage, scaling factor is calculated and flash location is updated.

Test Setup and Results


A PCB was designed with the external components, for the switching method battery charger, shown in [Figure 2](#). The board was designed to be an expansion board for [CY8CKIT-001](#), as shown in [Figure 19](#). [Appendix B: Schematic and Bill of Materials for Switching Method of Current Control](#) gives the Bill of Materials (BOM) and the schematic for this PCB board. Gerber files for this board is also given provided.

Figure 19. Battery Charger EBK and CY8CKIT-001



A USB component was added to the project, and data from the USB was plotted on a tool developed in C#. The LCD component is also placed to display voltage, current, temperature, and PWM duty cycle count. The additional components required for development and not for production are shown in [Figure 20](#).

Figure 20. Components for Debug and Display

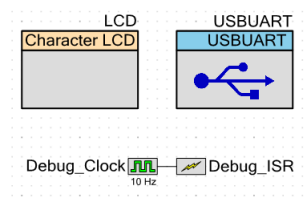


USB Communication

A USB driver is required for USB communication. The INF file is included with this application note. [Appendix C: USB Driver Installation](#) explains the driver installation.

Charge Display Tool

You can plot the battery charging graphs using the tool provided with this application note. The details of setting up this tool are provided in [Appendix D: Software Tool Installation and Setup](#). An example plot of the charging process is shown in [Figure 21](#).

Figure 21. Charge Display Tool for Display and Debug

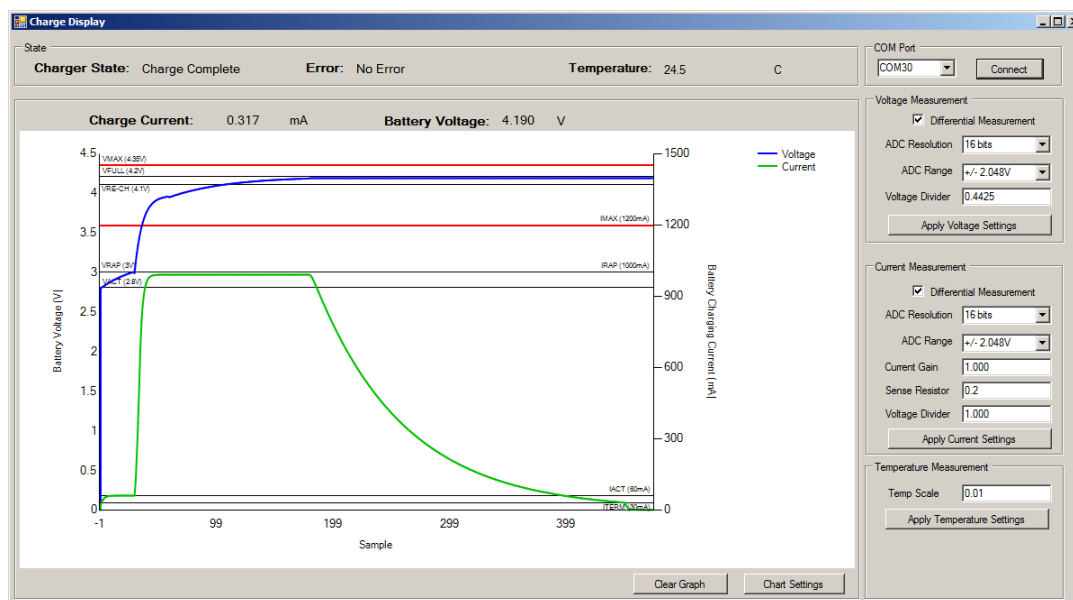

Conclusion

Li-ion battery charging can be done in multiple ways. The firmware method of control and the linear and switching method implementations are discussed in this application note.

Appendix A: Buck Circuit Component Selection

This section helps you select inductor value, output capacitor, and MOSFET.

The following assumptions are made:

- Supply voltage V_{in} : 12 V
- Full charge battery voltage: 4.2 V
- Rapid charging current: 1 A
- PWM switching frequency: 500 kHz
- Inductor ripple current: 300 mA

The selection of the components for the buck regulator is as follows.

Inductor L Selection


Inductor voltage is given by:

$$L = (V_{in} - V_{out}) \times \frac{Duty}{(F_{sw} \times I_{ripple})}$$

For this application, I_{ripple} is assumed to be 30 mA with a charging current of 1 A. The duty cycle at $V_{out} = 4.2$ V (battery full charge voltage) is around 0.35. The actual duty cycle will be a little larger to pump current in the battery. For a PWM frequency of 500 kHz, this gives an inductor value close to 18 μ H. A slightly larger value of inductance of 22 μ H is chosen to keep a margin of safety.

The current handling capability of the inductor should be greater than (load current + ripple current). Load current is the battery charging current, which is 1 A maximum. Because the assumed ripple current is close to 300 mA, the inductor should be able to handle minimum current of 1.3 A.

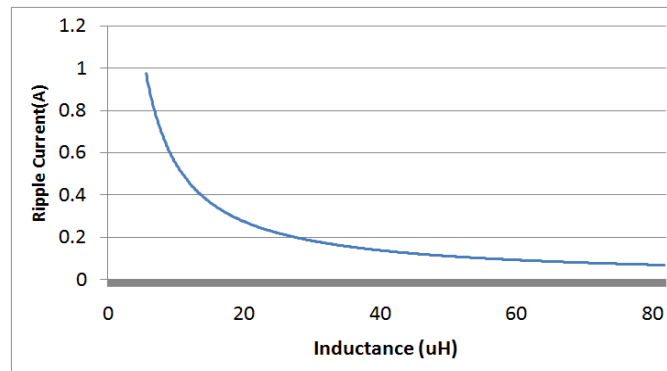The following graph shows the ripple current for a given inductor value for the assumptions mentioned previously.




Output Capacitor C Selection

$$C = \frac{(ripple\ current \times T_{on})}{(ripple\ voltage - (ripple\ current \times ESR))}$$

A low ESR capacitor should be selected to have low ripples in the output voltage. The 30 m Ω ESR capacitor is selected for this application. Duty is assumed to be 50% max; this gives T_{on} as 1 μ s. Capacitance of 22 μ F gives the ripple voltage around 26 mV across the output. This ripple voltage drops across the internal resistance of the battery. Ripple current is taken as 350 mA for inductor value of 22 μ H to keep a margin of safety.

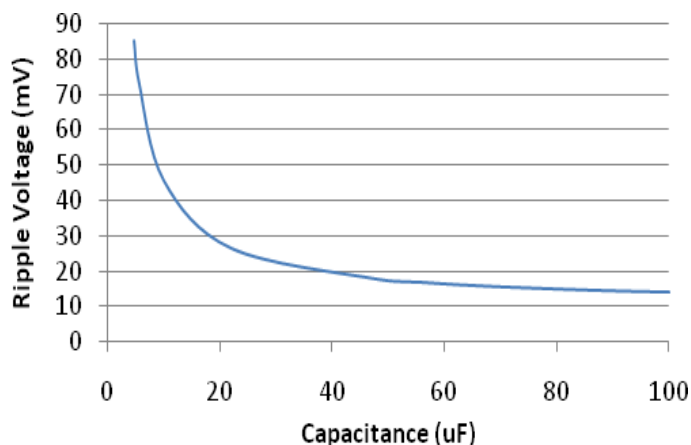The following graph shows the variation in output voltage ripple for capacitance value for the assumptions mentioned previously.



Dual MOSFET Selection

MOSFET selection is based on the load requirement, ripple current, and the supply voltage.

Drain current rating: Both the MOSFETs will handle load current + ripple current that gets bypassed through the output capacitor. Therefore, the MOSFET continuous current rating should be greater than $(1\text{ A} + 0.35\text{ A} = 1.35\text{ A})$.

Drain-Source and Gate-Source voltage rating: This should be greater than the supply voltage.

FDC6561 dual MOSFET IC is selected, which has a 30 V drain-source voltage rating, a 20 V gate-source voltage rating, and a continuous drain current rating of 2.5 A.

Appendix B: Schematic and Bill of Materials for Switching Method of Current Control

This section includes the schematic and the BOM for the EBK to test the battery charger functionality is provided. The main board (CY8CKIT-001) has the PSoC and USB functionality, and the rest of the external circuitry is on this expansion board.

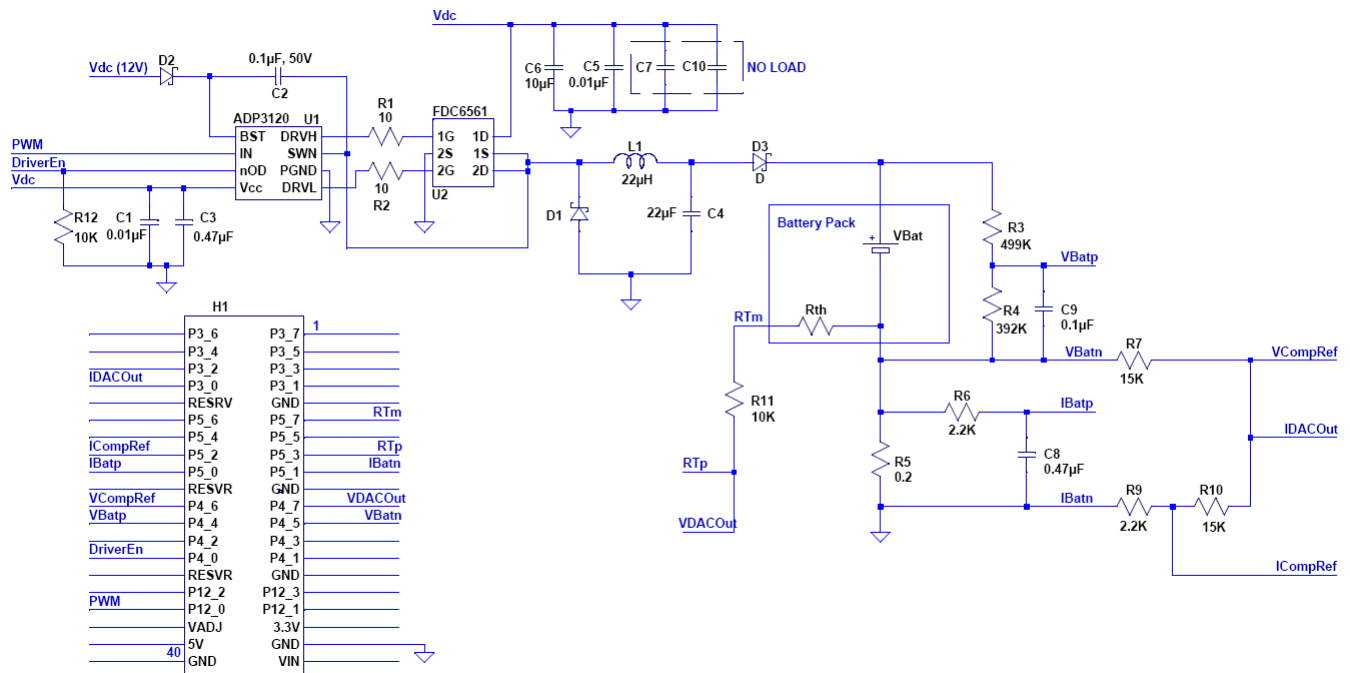


Table 3. Bill of Materials (BOM)


	Manufacturer	Manufacturer Part Number	Reference	Quantity	Description
1	ON SEMICONDUCTOR	ADP3120AJRZ	U1	1	IC MOSFET DVR DUAL 12 V 8-SOIC
2	FAIRCHILD SEMICONDUCTOR (VA)	FDC6561AN	U2	1	MOSFET N-CHAN DUAL 30 V SSOT6
3	NXP SEMICONDUCTORS (VA)	PMEG3020EH,115	D1,D2,D3	3	SCHOTTKY RECT 30 V 2 A SOD123F
4	Generic	Generic	L1	1	INDUCTOR PWR UNSHIELD 22 UH SMD
5	Generic	Generic	BAT	1	HOLDER BATT 1/LI-ION PROTECTED
6	Generic	Generic	C4	1	CAP AL POLY CHIP 22UF 16V ESR 30 mΩ SMD
7	Generic	Generic	R9	1	2.2 kΩ 1% 0805
8	Generic	Generic	R4	1	330 kΩ 5% 0805
9	Generic	Generic	R6	1	2.2 kΩ 5% 0805
10	Generic	Generic	R5	1	0.2 Ω 1/4 W 1% 0805 SMD
11	Generic	Generic	R3	1	499 kΩ 5% 0805
12	Generic	Generic	R12	1	10 kΩ 5% 0805
13	Generic	Generic	R1,R2	2	10 Ω 1/4 W 5% 0805 SMD
14	Generic	Generic	R10	1	15 kΩ 1/4 W 1% 0805 SMD
15	Generic	Generic	R8	1	0.0 Ω 1/8W 0805 SMD
16	Generic	Generic	R7	1	15 kΩ 1% 0.125 W 0805
17	Generic	Generic	C1, C5	3	CAP CERM .01 UF 5% 16 V NP0 0805
18	Generic	Generic	C6	1	CAP CER 10 UF 16 V X5R 20% 0805
19	Generic	Generic	C3	1	CAP CER .47 UF 16 V X7R 0805
20	Generic	Generic	C8, C9	1	CAP .10 UF CERAMIC X7R 0805
22	Generic	Generic	H1	1	CONN HEADER R/A 40POS GOLD SMD
23	Generic	Generic	R11	1	THERMISTOR 10 kΩ NTC 0805 SMD
24	Generic	Generic	C2	1	CAP CER 0.1 UF 50 V X7R 0805

Appendix C: USB Driver Installation

When the demo board is connected to the computer through a USB cable, the “Found New Hardware” message will appear, as shown in the following figure.



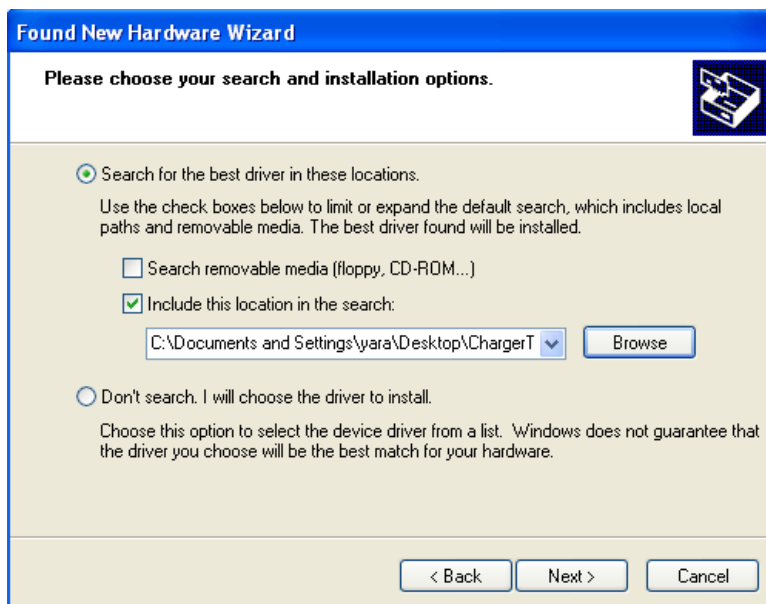Click **Next** on this screen and select **Install from a list or specific location (Advanced)**. Click **Next**. The following screen appears. Use the **Browse** field to find the INF file.



Click **Next** to complete and finish the installation.


Appendix D: Software Tool Installation and Setup

Step 1: Click on the Setup file in the charge display tool folder provided with this application note.

Step 2: Follow the sets as guided by the tool for installation.

Step 3: Open the tool from **Startup > Cypress Semiconductor > Charge display**.

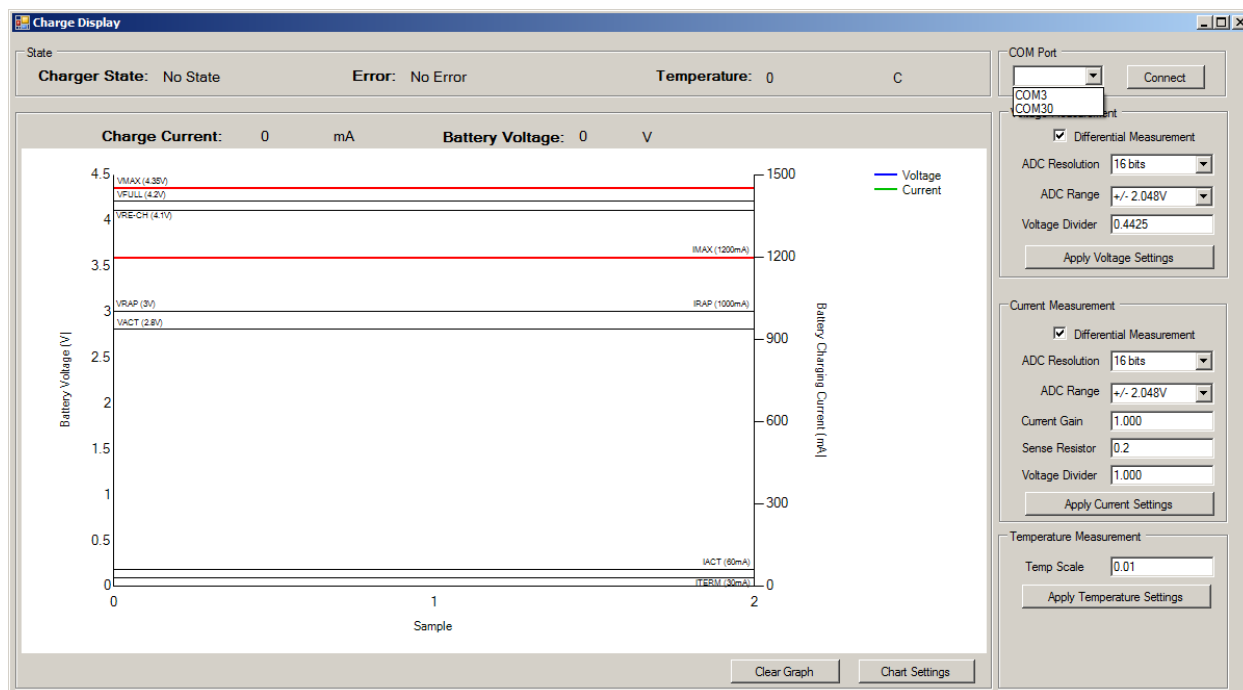Step 4: Connect the COM associated with **Li-ion battery charger**.



Step 5: Enter the parameters of the ADC and the resistors chosen into the appropriate fields

Voltage Measurement

Differential Measurement: Select the box if the ADC is a differential ADC.

Clear the box if it is a single-ended ADC.

ADC resolution: Select the same resolution used for the ADC

ADC Range: Select the same range used for the ADC

Voltage Divider: This is the hardware voltage scale used for the battery voltage attenuation.

$$= \frac{R_{Vsense2}}{(R_{Vsense1} + R_{Vsense2})}$$

Current Measurement

Differential Measurement: Select the box if the ADC is a differential ADC.

Clear the box if it is a single-ended ADC.

ADC resolution: Select the same resolution used for the ADC

ADC Range: Select the same range used for the ADC

Current Gain: Choose the appropriate gain, if additional gain is added to current measurement


Sense Resistor: Enter the current sense resistor value R_{sense}

Temperature Measurement

Temp Scale: The thermistor component returns the temperature value scaled up by 100. For example, it returns 2345 when the temperature is 23.45 °C. This value can be scaled down in firmware or passed onto the tool as it is and scaled in the tool.

Graph Parameter Setup

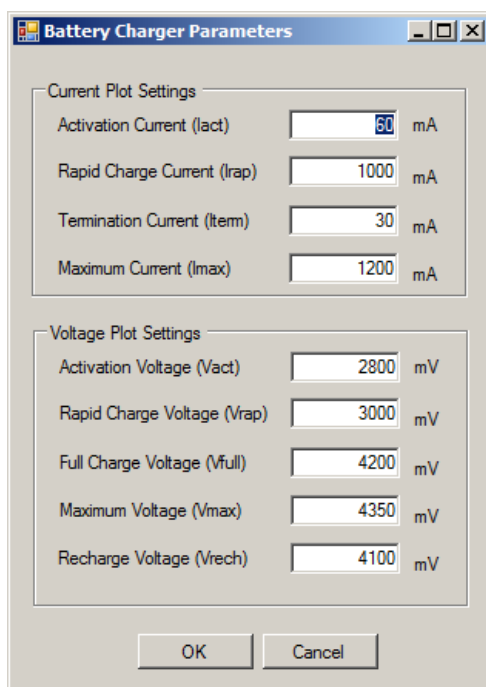When you click **Choose settings**, the following form for the graph settings appears.



The dialog box titled "Battery Charger Parameters" contains two sections: "Current Plot Settings" and "Voltage Plot Settings". Each section has four input fields with corresponding units.

Section	Parameter	Value	Unit
Current Plot Settings	Activation Current (Iact)	60	mA
	Rapid Charge Current (Irap)	1000	mA
	Termination Current (Iterm)	30	mA
	Maximum Current (Imax)	1200	mA
Voltage Plot Settings	Activation Voltage (Vact)	2800	mV
	Rapid Charge Voltage (Vrap)	3000	mV
	Full Charge Voltage (Vfull)	4200	mV
	Maximum Voltage (Vmax)	4350	mV
	Recharge Voltage (Vrech)	4100	mV

At the bottom of the dialog are "OK" and "Cancel" buttons.


This can be used to change the voltage and current threshold levels displayed on the charge display tool, shown in the earlier figure. All the parameters have to be matched to the parameters set in the battery charger project to make sure that the thresholds line up.

Appendix E: Alternative Implementation Options with Tradeoffs

This section shows the alternate implementation methods. The differences between the two methods are only to show different options and tradeoffs during an implementation. You can choose any method that is suitable for your application.

Biasing Thermistor using IDAC


A second approach to measuring temperature with advantages of lower pin and memory usage is provided in this section. In this method, an IDAC is used to source a known amount of current through the thermistor, and the voltage across it is measured to obtain its resistance. The disadvantages are the accuracy will be lower, since the offset and gain errors are not being accounted for, and the coefficients of the thermistor have to be provided by you in firmware.

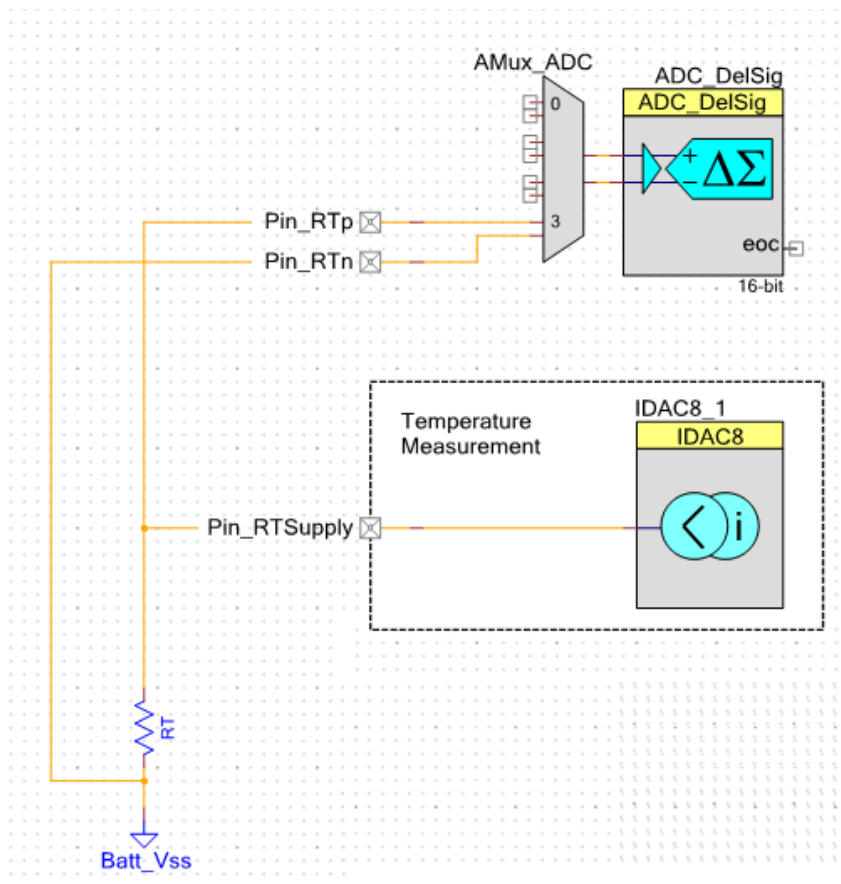

Over Voltage and Over Current Protection


The method explained for the OV/OC in the earlier sections of this application note has the advantage of using one IDAC. Its disadvantage is the complication introduced in calculating the external resistors. Some modifications of the circuit are given in this section to show the options for tradeoffs.

Two IDACs are used instead of one to generate the reference voltages for OV and OC. This makes the resistor selection less complicated for the user than the single IDAC method explained in switching method. The second option shown is to route the signal from the IDAC to the comparator internally, instead of connecting the two pins externally. This option saves a pin, but requires manual routing between the IDAC and the comparator. This is to make sure that the IDAC connection to the resistor is made at the same location as the connection to the comparator. When automatic routing is used, additional switches are used between the comparator connection and the pin, which causes the voltage seen at the comparator to be different from the voltage at the pin and makes the fault detection erroneous.

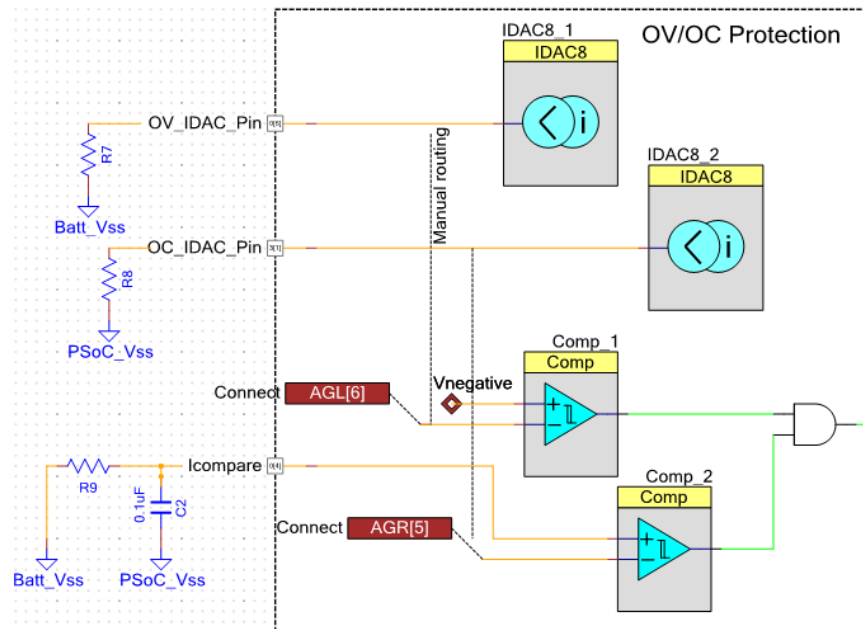

Battery Current Control with PWM

The charge current passed to the battery is decided based on the state of the battery. The dithered PWM was used in the main section of the application note as the duty cycle required for the switching method is high. The dithered PWM can be used for the linear method to maintain consistency in the project used. If you are interested in linear method alone, you can use the standard PWM instead of the dithered PWM for linear method to save additional component and memory usage. The connections for linear method with a regular PWM, instead of a custom Dithered PWM component, is shown in following figure. A PWM-DAC is formed by using external RC low-pass filter. The voltage obtained at the output of the low-pass filter controls the current through Q1 and thereby Q2. The current through Q2 is the charge current to the battery.

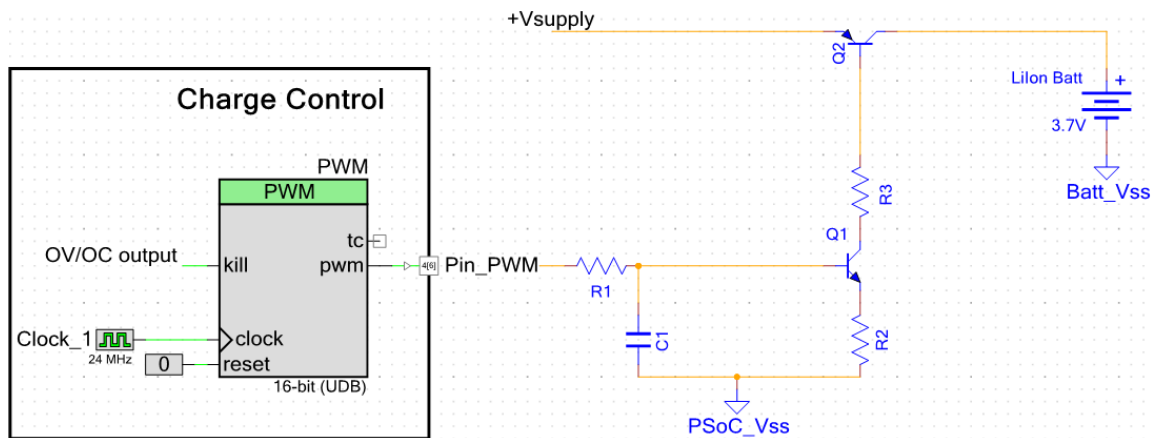

Document History

Document Title: AN73468 – PSoC® 3 and PSoC 5LP - Single-Cell Lithium-Ion (Li-ion) Battery Charger

Document Number: 001-73468

Revision	ECN	Orig. of Change	Submission Date	Description of Change
**	3475721	RJVB	12/26/2011	New application note.
*A	3512389	RJVB	01/30/2012	Updated project files. No technical updates.
*B	3818140	SREH	11/20/2012	Updated to include PSoC 5LP. Project files updated. Update to Battery Protection logic.
*C	4227505	SREH	12/20/2013	Updated Software Version as "PSoC® Creator™ 3.0 or Higher". Updated attached associated projects to Creator 3.0. Updated in new template. Completing Sunset Review.
*D	5048763	SREH	03/01/2016	Updated Software Version as "PSoC® Creator™ 3.3 or Higher". Updated attached associated projects to Creator 3.3 SP1. Updated project to use standard component. Updated the following diagrams: Thermistor Calculator Component. Battery Parameter Measurement. Charge Display Tool for Display and Debug Appendix D images.
*E	5688090	AESATMP8	04/19/2017	Updated logo and Copyright.

Worldwide Sales and Design Support

Cypress maintains a worldwide network of offices, solution centers, manufacturer's representatives, and distributors. To find the office closest to you, visit us at [Cypress Locations](#).

Products

ARM® Cortex® Microcontrollers	cypress.com/arm
Automotive	cypress.com/automotive
Clocks & Buffers	cypress.com/clocks
Interface	cypress.com/interface
Internet of Things	cypress.com/iot
Memory	cypress.com/memory
Microcontrollers	cypress.com/mcu
PSoC	cypress.com/psoc
Power Management ICs	cypress.com/pmic
Touch Sensing	cypress.com/touch
USB Controllers	cypress.com/usb
Wireless Connectivity	cypress.com/wireless

PSoC® Solutions

[PSoC 1](#) | [PSoC 3](#) | [PSoC 4](#) | [PSoC 5LP](#) | [PSoC 6](#)

Cypress Developer Community

[Forums](#) | [WICED IOT Forums](#) | [Projects](#) | [Videos](#) | [Blogs](#) | [Training](#) | [Components](#)

Technical Support

cypress.com/support

All other trademarks or registered trademarks referenced herein are the property of their respective owners.



© Cypress Semiconductor Corporation, 2011-2017. This document is the property of Cypress Semiconductor Corporation and its subsidiaries, including Spansion LLC ("Cypress"). This document, including any software or firmware included or referenced in this document ("Software"), is owned by Cypress under the intellectual property laws and treaties of the United States and other countries worldwide. Cypress reserves all rights under such laws and treaties and does not, except as specifically stated in this paragraph, grant any license under its patents, copyrights, trademarks, or other intellectual property rights. If the Software is not accompanied by a license agreement and you do not otherwise have a written agreement with Cypress governing the use of the Software, then Cypress hereby grants you a personal, non-exclusive, nontransferable license (without the right to sublicense) (1) under its copyright rights in the Software (a) for Software provided in source code form, to modify and reproduce the Software solely for use with Cypress hardware products, only internally within your organization, and (b) to distribute the Software in binary code form externally to end users (either directly or indirectly through resellers and distributors), solely for use on Cypress hardware product units, and (2) under those claims of Cypress's patents that are infringed by the Software (as provided by Cypress, unmodified) to make, use, distribute, and import the Software solely for use with Cypress hardware products. Any other use, reproduction, modification, translation, or compilation of the Software is prohibited.

TO THE EXTENT PERMITTED BY APPLICABLE LAW, CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS DOCUMENT OR ANY SOFTWARE OR ACCOMPANYING HARDWARE, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. To the extent permitted by applicable law, Cypress reserves the right to make changes to this document without further notice. Cypress does not assume any liability arising out of the application or use of any product or circuit described in this document. Any information provided in this document, including any sample design information or programming code, is provided only for reference purposes. It is the responsibility of the user of this document to properly design, program, and test the functionality and safety of any application made of this information and any resulting product. Cypress products are not designed, intended, or authorized for use as critical components in systems designed or intended for the operation of weapons, weapons systems, nuclear installations, life-support devices or systems, other medical devices or systems (including resuscitation equipment and surgical implants), pollution control or hazardous substances management, or other uses where the failure of the device or system could cause personal injury, death, or property damage ("Unintended Uses"). A critical component is any component of a device or system whose failure to perform can be reasonably expected to cause the failure of the device or system, or to affect its safety or effectiveness. Cypress is not liable, in whole or in part, and you shall and hereby do release Cypress from any claim, damage, or other liability arising from or related to all Unintended Uses of Cypress products. You shall indemnify and hold Cypress harmless from and against all claims, costs, damages, and other liabilities, including claims for personal injury or death, arising from or related to any Unintended Uses of Cypress products.

Cypress, the Cypress logo, Spansion, the Spansion logo, and combinations thereof, WICED, PSoC, CapSense, EZ-USB, F-RAM, and Traveo are trademarks or registered trademarks of Cypress in the United States and other countries. For a more complete list of Cypress trademarks, visit cypress.com. Other names and brands may be claimed as property of their respective owners.