

Application Note No. 014

Application Considerations for the Integrated Bias Control Circuits BCR400R and BCR400W

RF & Protection Devices



Never stop thinking

Edition 2006-11-23

**Published by
Infineon Technologies AG
81726 München, Germany**

**© Infineon Technologies AG 2009.
All Rights Reserved.**

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Application Considerations for the Integrated Bias Control Circuits BCR400R and BCR400W

Revision History: 2006-11-23, Rev. 2.0

Previous Version: 2000-07-27

Page	Subjects (major changes since last revision)
All	Document layout change

1 Application Considerations for the Integrated Bias Control Circuit BCR400W

RF transistor controlled by BCR400

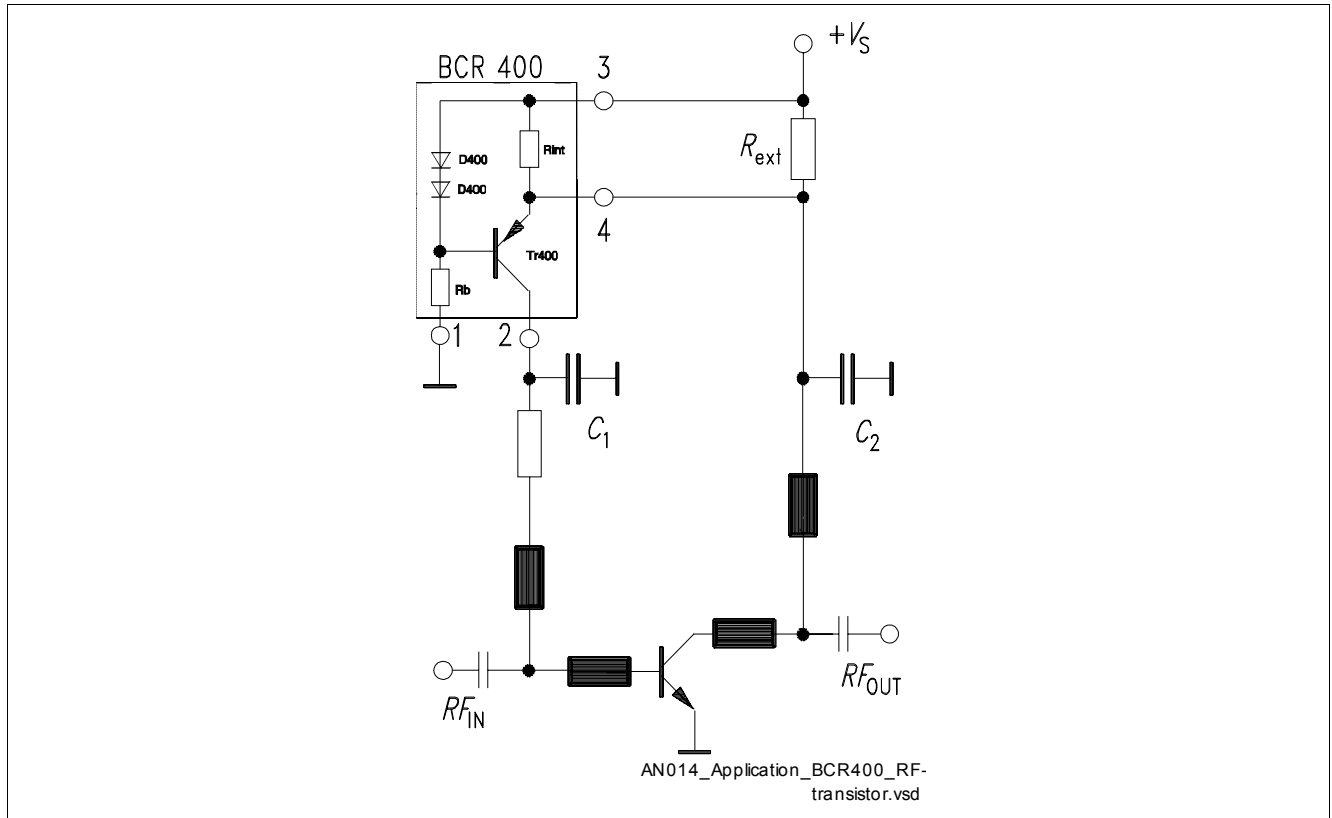


Figure 1 Application with BCR400

Operating point

- BCR400 stabilizes the operating CURRENT (i.e. I_C or I_D), the collector (or drain) voltage depends on the supply voltage: $V_{CE} = V_S - 0.65 \text{ V}$
- The voltage drop of approximately 0.65 V on R_{ext} (i.e. between pins 3 and 4 of BCR400) is almost constant ($R_{ext} = 0.65 \text{ V} \times I_C$).
- In case a lower V_{CE} is really required (e.g. to prevent exceeding of maximum V_{CE} or V_{DS} ratings), an additional resistor $R = (V_S - V_{CE} - 0.65 \text{ V}) / I_C$ can be inserted either between pin 4 and collector (or drain) or in series to the supply voltage V_S , thus providing an additional voltage drop.

Stability

BCR400 stabilizes bias current of transistors in an active control loop. In order to avoid loop oscillation (hunting), time constants must be chosen adequately, i.e. $C_1 \pm 10 \times C_2$. It is strongly recommended that the entire DC circuit is analyzed and optimized for stability with one of the commercially available SPICE simulators.

Thermal considerations

The collector or drain current of a stabilized RF transistor does not directly affect BCR400, as it must only provide the base current (or gate bias current). Even as a stand-alone current source it is not possible to exceed P_{tot} (up to $T_S = 115 \text{ }^\circ\text{C}$), if the maximum ratings of V_S and I_{contr} are adhered to (see data sheet).

Application Considerations for the Integrated Bias Control Circuit BCR400W

Preliminary SPICE parameter

```

*****
.MODEL DI400 D(
+   IS= 6.00E-15      N= 1.20E+00      RS= 5.0E+01
+   IBV= 1.00E-04    BV= 7.50E+01
+   M= 1.00E-01      CJO= 6.87E-13    EG= 1.11E+00
+   TT= 8.66E-09     VJ= 2.00E+00     XTI= 5.00E+00)
* one internal Diode of BCR400
*****

.MODEL TR400 PNP(
+   BF= 3.00E+02      BR= 3.38E+00      CJC= 2.00E-12
+   CJE= 1.56E-11     CJS= 0.00E+00      EG= 1.11E+00      FC= 8.28E-01
+   IKF= 1.00E-02     IKR= 0.40E-02     IRB= 0.30E-06     IS= 0.30E-14
+   ISC= 2.00E-14     ISE= 0.50E-13     ITF= 0.50E-01
+   MJC= 3.49E-01     MJE= 4.18E-01     MJS= 3.30E-01     NC= 1.19E+00
+   NE= 1.83E+00      NF= 1.00E+00      NR= 1.00E+00     PTF= 0.00E+00
+   RB= 1.00E+02      RBM= 1.00E+01     RC= 5.00E+00     RE= 2.00E-01
+   TF= 6.05E-10      TR= 0.00E+00     VAF= 5.90E+01     VAR= 1.74E+01
+   VJC= 3.00E-01     VJE= 8.00E-01     VJS= 7.50E-01     VTF= 4.39E+00
+   XCJC= 1.00E+00    XTB= 0.00E+00     XTF= 5.81E+00     XTI= 1.50E+00)

*****
* internal parallel resistance Rint= 6.5 kOhm
* Rb= 75 kOhm
*****
AN014_SPICE_parameter.vsd

```

Figure 2 SPICE parameters