

# Application Note

High current PROFET™

**BTS50060-1TEA**

Example for external circuitry

Application Note

V1.1 2014-01-29

Automotive Power

---

**BTS50060-1TEA**

**Revision History: V1.1, 2014-01-29**

**Previous Version: V1.0, 2013-07-19**

<b>Page</b>	<b>Subjects (major changes since last revision)</b>
6, 7, 9	Table 4, Table 5, Table 6: BCR133S replaced by BCR10PN

## Table of Contents

1	Abstract.....	4
2	Introduction .....	4
3	Basic circuitry.....	4
4	Circuitry for applications requiring accurate load current sensing .....	5
5	Circuitry for applications sensitive to shift of voltage levels / increased RF robustness of IS signal .....	5
6	Circuitry with “open load at OFF” detection .....	6
7	Summary of circuitry for single device.....	7
8	Multiple devices.....	8
9	Conclusion.....	10
10	Additional Information.....	10

## 1 Abstract

*Note: The following information is given as a hint for the implementation of the device only and shall not be regarded as a description or warranty of a certain functionality, condition or quality of the device.*

This application note is intended to give examples for external circuitry for using Infineon® product BTS50060-1TEA.

## 2 Introduction


Within high current PROFET™ product family, Infineon® offers the BTS50060-1TEA, which is a 6mOhm single channel smart high-side switch. With its unique feature set, it serves a wide range of automotive heating applications, such as driver for glow plugs, PTC heater, or urea heater.

In this application note, the following abbreviations and symbols are used:

- BOM : bill of material
- DI/O : digital output pin of a microcontroller
- ADC : ADC input pin of a microcontroller; ADC = analog-to-digital converter
- RF : radio frequency

## 3 Basic circuitry

Using circuitry as shown in Figure 1 supports basic functionality of BTS50060-1TEA.

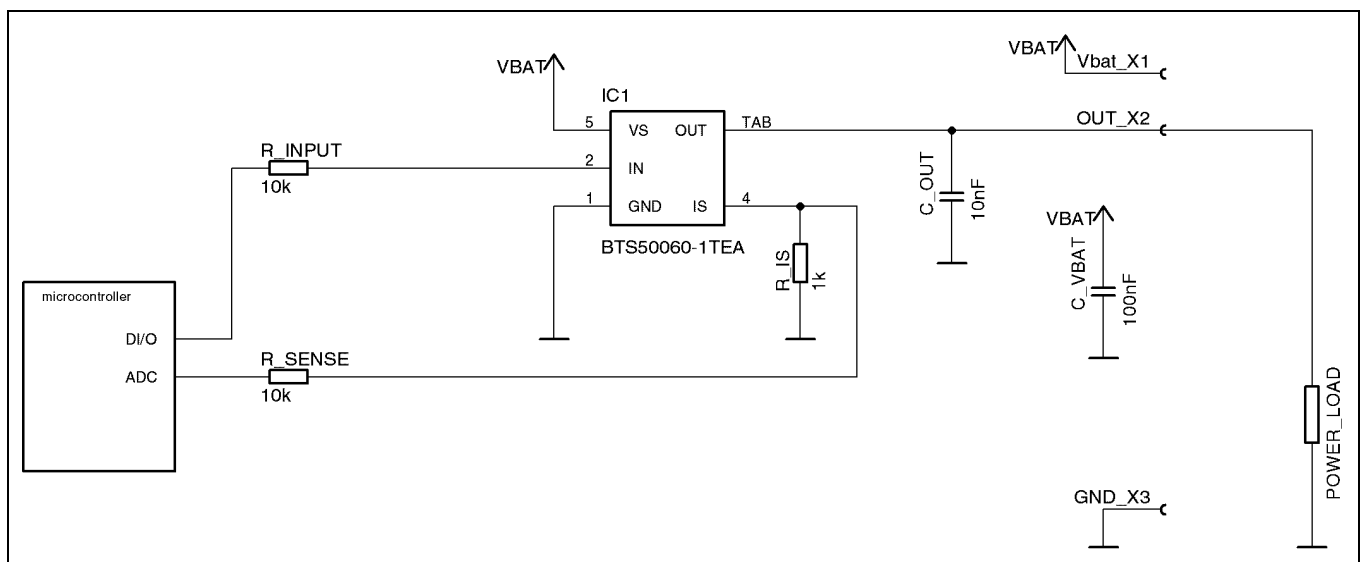

**Figure 1 Example for using BTS50060-1TEA basic circuitry**


**Table 1 BOM single device basic circuitry**

Symbol	Value	Count	Comment
IC1	BTS50060-1TEA	1	Smart High-side switch
Microcontroller	e.g. TLE9832	1	-
R_Input	10k	1	-
R_sense	10k	1	-
R_IS	1k	1	-
C_Vbat	100nF	1	-
C_OUT	10nF	1	-
X	Power connectors	3	-
Power Load	e.g. Diesel glow plug	1	Loads to be driven

## 4 Circuitry for applications requiring accurate load current sensing

The ADVANCED SENSE feature of BTS50060-1TEA allows accurate sensing of the load current. To support this accuracy under severe RF disturbances, it may be necessary to include a resistor R\_GND (100R) in the connection for pin 1 of BTS50060-1TEA. See Figure 2. This may cause a shift of voltage at the GND pin, which influences voltage levels and hysteresis behavior for undervoltage lock-off, input voltage thresholds, open load at off detection.

*Note: All parameters in datasheet are given only in respect to device pins (if not mentioned differently). Voltage drops on external components are not covered by the device specification.*

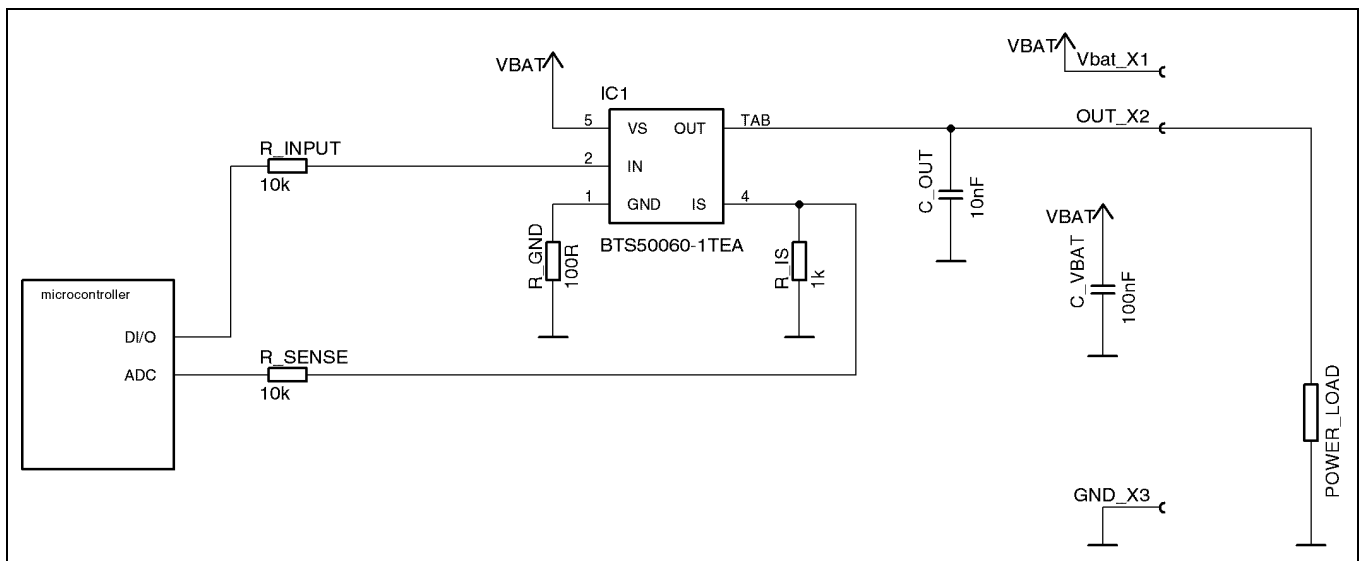
**Figure 2 Example for using BTS50060-1TEA basic circuitry with R\_GND**
**Table 2 Change to BOM for robust IS signal**


Symbol	Value	Count	Comment
R_GND	100 Ohm	1	-

## 5 Circuitry for applications sensitive to shift of voltage levels / increased RF robustness of IS signal

The voltage drop across R\_GND causes a shift of the voltage levels of the device, such as undervoltage threshold, input threshold, or open load at OFF threshold. For applications which are sensitive to a shift of these



## 7 Summary of circuitry for single device

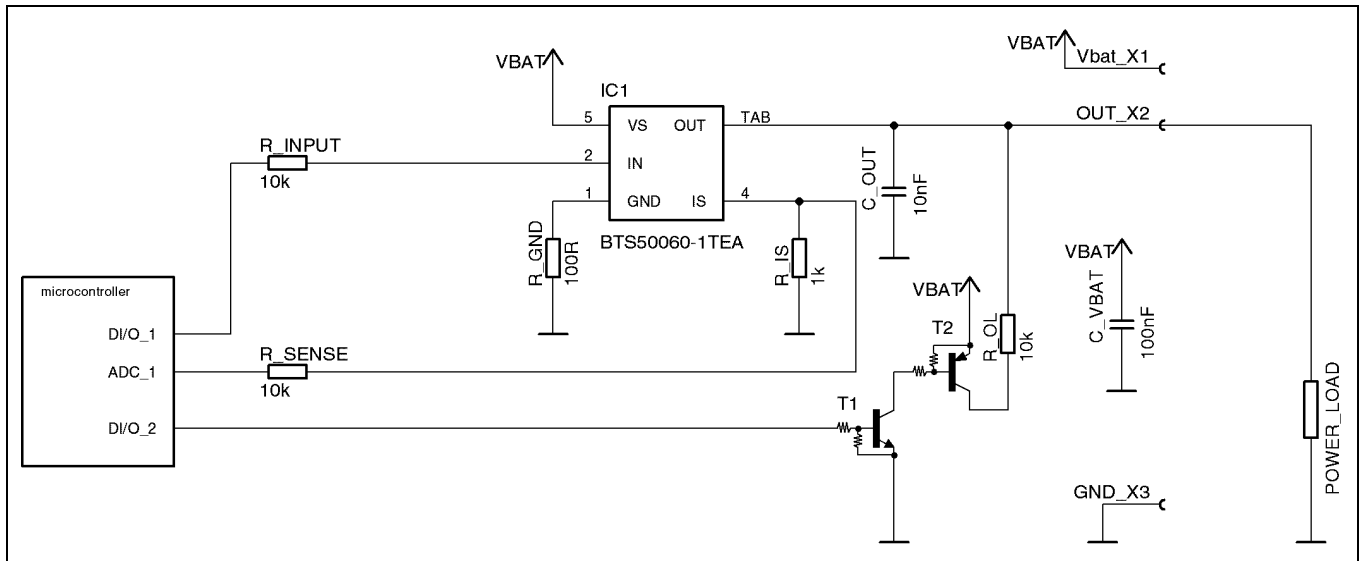

**Figure 4** Example for using BTS50060-1TEA, summarizing above circuitry

**Table 5** BOM single device

Symbol	Value	Count	Comment
IC1	BTS50060-1TEA	1	Smart High-side switch
Microcontroller	e.g. TLE9832	1	-
R_Input	10k	1	-
R_sense	10k	1	-
R_IS	1k	1	-
R_GND	100 Ohm	1	-
C_Vbat	100nF	1	-
C_OUT	10nF	1	-
X	Power connectors	3	-
Power Load	e.g. Diesel glow plug	1	Loads to be driven
T1	NPN bias transistor, e.g. TR1 of BCR10PN	1	For open load detection
T2	PNP bias transistor, e.g. TR2 of BCR10PN		
RL_OL	10k	1	For open load detection

## 8 Multiple devices

Using multiple BTS50060-1TEA for independent outputs on a single board, some parts of the circuitry may be necessary only one time, saving components and microcontroller pins. An example for using 2 units BTS50060-1TEA, with open load detection, can be found in Figure 5.

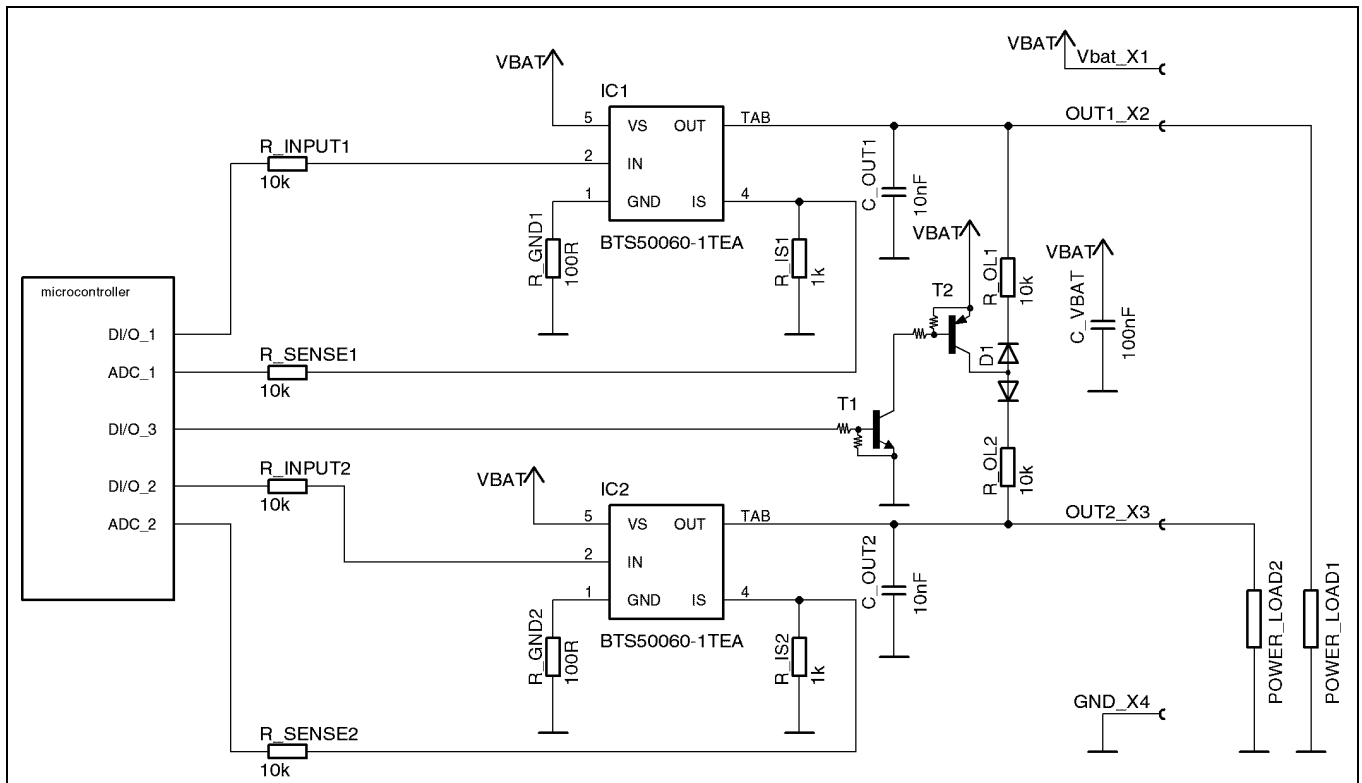


Figure 5 Example for using two BTS50060-1TEA, re-using circuitry and microcontroller pins



**Table 6 BOM for two devices, including “open load at OFF” detection**

Symbol	Value	Count	Comment
IC1	BTS50060-1TEA	2	Smart High-side switch
Microcontroller	e.g. TLE9832	1	-
R_Input	10k	2	-
R_sense	10k	2	-
R_IS	1k	2	-
R_GND	100 Ohm	2	-
C_Vbat	100nF	1	-
C_OUT	10nF	1	-
X	Power connectors	4	-
Power Load	e.g. Diesel glow plug	2	Loads to be driven
T1	NPN bias transistor, e.g. TR1 of BCR10PN	1	For open load detection
T2	PNP bias transistor, e.g. TR2 of BCR10PN		
RL_OL	10k	2	For “open load at OFF”
D1	e.g. BAW56	1	For “open load at OFF”; double diode with common anode

As shown in Figure 6, instead of using a separate R\_GND for each BTS50060-1TEA, using one common L\_GND for multiple BTS50060-1TEA may reduce the number of device count on board. Care has to be taken in board layout to avoid RF coupling from BTS50060-1TEA pin 1 (GND) to module board, bypassing L\_GND. Using single R\_GND for multiple BTS50060-1TEA is not recommended because of voltage drop across R\_GND.

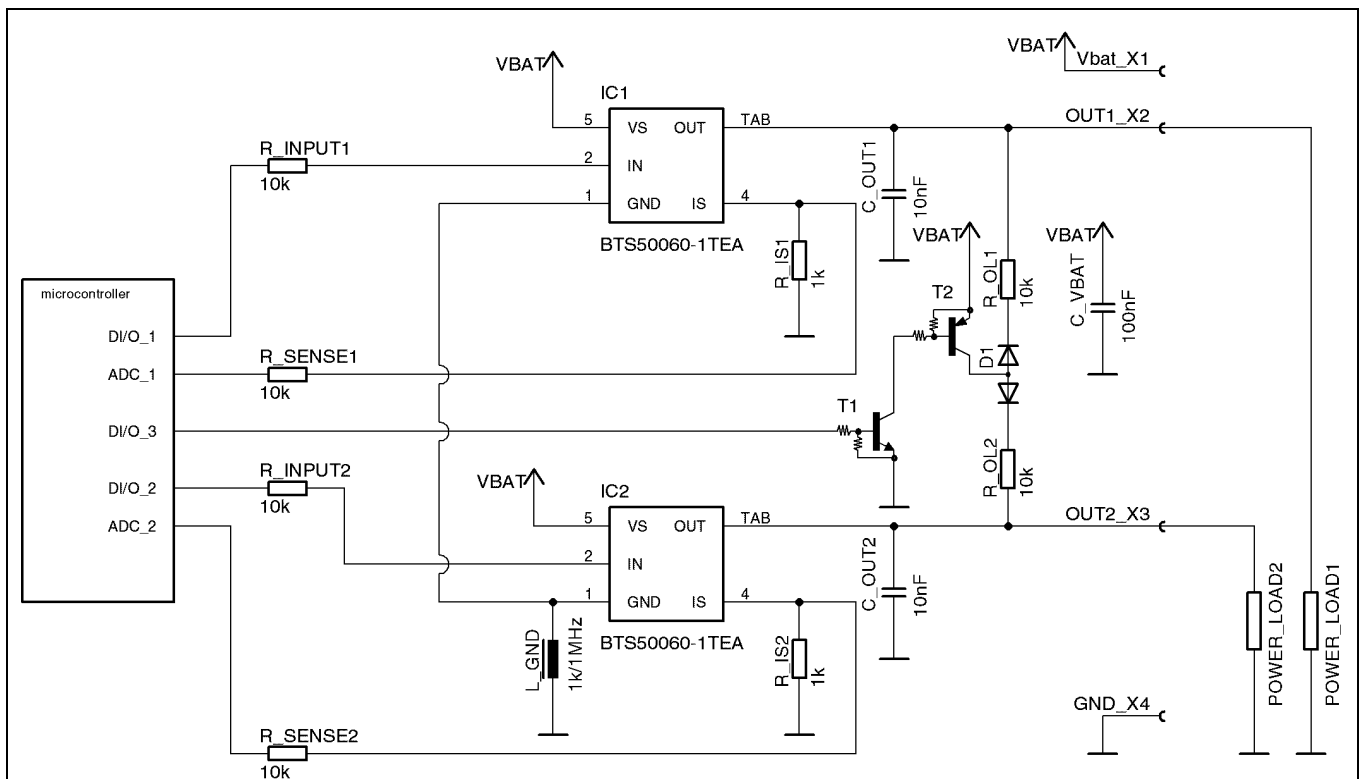

**Figure 6 Example for using two BTS50060-1TEA, re-using circuitry and microcontroller pins, with single L\_GND**

Table 7 Change to BOM for two devices when using single L\_GND

Symbol	Value	Count	Comment
R_GND	100 Ohm	0	Replaced by L_GND
L_GND	e.g. WE 74279205	1	1k@100MHz

## 9 Conclusion

The high current PROFET™ BTS50060-1TEA from Infineon® is a smart high-side switch. It offers the high driving capability of a 6mOhm switch in a DPak package with a high number of protection and diagnostic features. It supports high feature set and low count of external components, for a high variety of applications. Examples of how to make use of that in application design were given in this application note.

## 10 Additional Information

- Data sheet of BTS50060-1TEA can be found at <http://www.infineon.com/PROFET>
- More information on ADVANCED SENSE feature can be found in the application note “ADVANCED SENSE calibration and benefits guide” available at document section of <http://www.infineon.com/PROFET>
- For further information you may contact <http://www.infineon.com>

**Edition 2014-01-29**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2014 Infineon Technologies AG**

**All Rights Reserved.**

#### **LEGAL DISCLAIMER**

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

#### **Information**

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

#### **Warnings**

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office.

Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

[www.infineon.com](http://www.infineon.com)

Published by Infineon Technologies AG