

DrBlade™ 2

DrBlade™ 2nd Generation

Selection of Boot Capacitor Value for DrBlade™ 2

TDA21320, TDA21321

Application Note

About this Document

Scope and purpose

With the DrBlade™ 2 Product family, Infineon has introduced a voltage check of the boot capacitor to protect the high-side (HS) switch against an insufficiently low driving voltage. This document provides guidelines for the choice of value for the boot capacitor depending on the operating conditions.

Intended audience

This document is intended for system design engineers using DrBlade™ 2 products.

Table of Contents

About this Document	1
Table of Contents	1
1 Introduction	2
2 Feature Description	3
2.1 Undervoltage Lockout for Boot Voltage (UVLO _{BOOT}) Protection Feature	3
2.2 Boot Refresh Circuit	4
3 Circuit Interactions	5
3.1 Scenario Showing Lacking Transient Support	5
3.2 Prevention of Unwanted UVLO _{BOOT} Events	6
3.2.1 Effect of UVLO _{BOOT} Refresh Circuit	6
3.2.2 Recharge During LS MOSFET On-Time	7
4 Boot Capacitor Selection Guide	10
4.1 Boot Capacitor Selection Guide for TDA21320	10
4.2 Boot Capacitor Selection Guide for TDA21321	14
5 Conclusion	18

Introduction

1 Introduction

A DrBlade™ 2 power stage integrates power MOSFETs and driver in a common package. It provides a variety of protection features to prevent damage to the device and the load, under almost every foreseeable scenario.

Part of that protection scheme is the surveillance of the voltage across the boot capacitor that drives the HS MOSFET. If this gate to source voltage is too low, the driver stops operating in order to protect the HS MOSFET, regardless of the state of the PWM input signal.

Restrictions on the HS MOSFET turn-on can result in delays in the converters response to load steps. This note discusses the design considerations necessary to ensure a proper transient response in DrBlade™ 2 applications at highly dynamic loads with long tri-state periods leading to charge depletion at the boot capacitor. This charge loss is compensated for by an integrated refresh operation. The choice of the boot capacitor value is an integral part of the design to prevent unwanted UVLO_{BOOT} error states.

In case of an UVLO_{BOOT} error the system controller can initiate shutdown if it discovers a missing phase, phase current mismatch, excessive temperature and/or overcurrent protection (OCP) events on other phases.

To maintain stable driving voltage for the HS MOSFET a larger boot capacitor is generally preferred. When also considering proper cooperation of protection and refresh features in dynamic load applications, as described above, selection of the boot capacitor value requires particular attention.

For other aspects of the DrBlade™ 2 products, refer to the respective datasheets.

2 Feature Description

2.1 Undervoltage Lockout for Boot Voltage (UVLO_{BOOT}) Protection Feature

This feature stops driver operation when the voltage across the boot capacitor is below a critical threshold. This prevents driving the HS MOSFET with an insufficiently low voltage.

Figure 1 depicts the application circuit of a DrBlade™ 2 device, showing the pin names for reference.

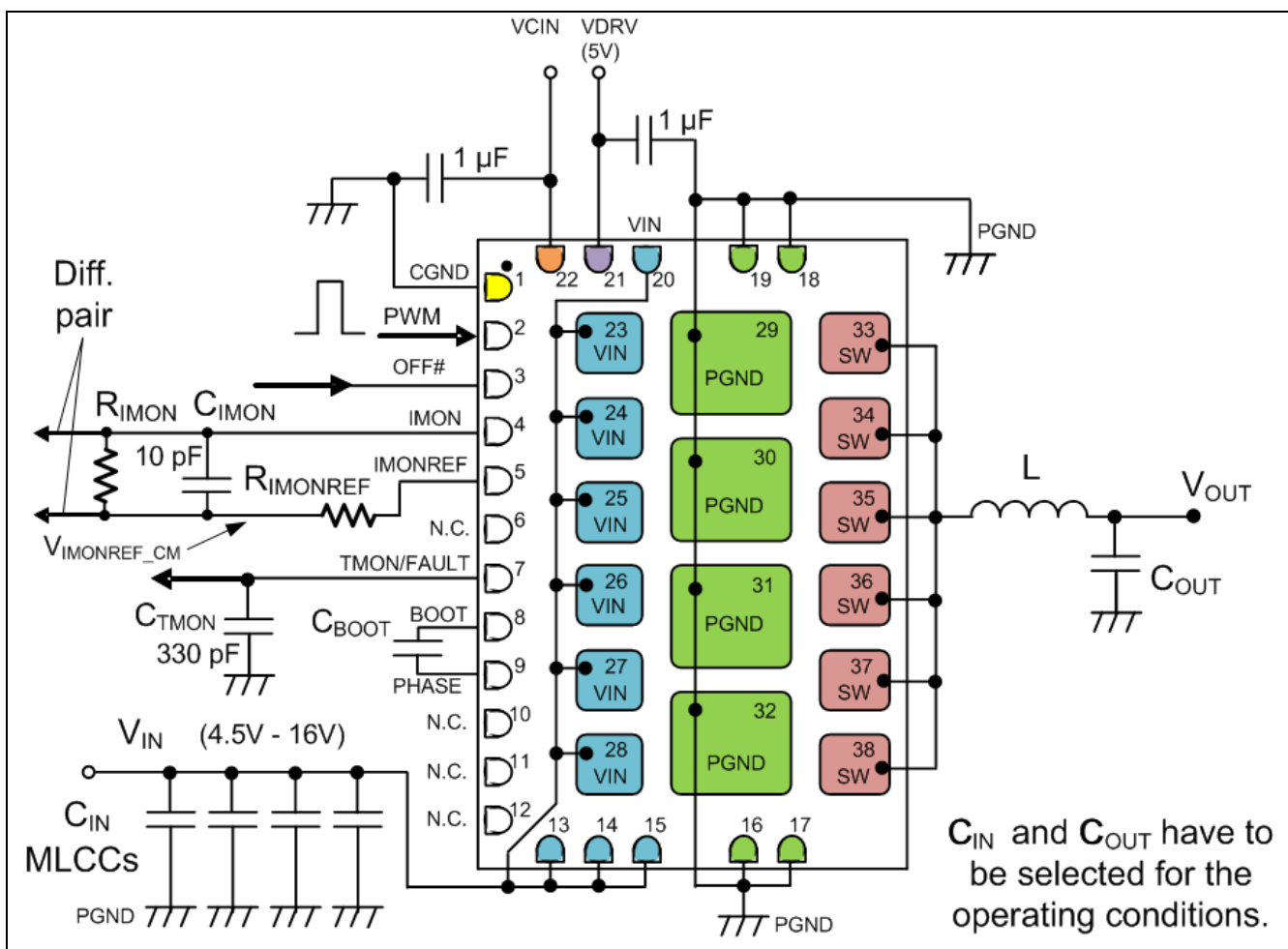


Figure 1 Basic Application Circuit as Example of Implementation

The voltage between the BOOT and SW pins is monitored after V_{CIN} and V_{DRV} have cleared their respective UVLO conditions. The SW pin is replicated as PHASE pin to connect C_{BOOT} . At startup, the low-side MOSFET (LS MOSFET) gate drive (driver output GL) is enabled to respond to the PWM signal when V_{DRV} is active. If the voltage across the boot capacitor is still below the $V_{UVLOboot_R}$ threshold, the active LS MOSFET forces charge into the boot capacitor during the PWM 'L' state. Otherwise, when the boot capacitor voltage exceeds the rising threshold of the undervoltage lockout value of the boot voltage ($V_{UVLOboot_R}$), the HS MOSFET gate drive (driver output GH) is enabled. This is shown at time t_1 in Figure 2.

Feature Description

 


Figure 2 UVLO_{BOOT} at Startup (GH is Enabled at t_1)

At startup and at any time when the boot voltage falls below the falling threshold of the undervoltage lockout value of the boot voltage ($V_{UVLOboot_F}$) an internal boot-error flag is set. The boot-error flag is reset when the boot voltage exceeds the rising threshold of the undervoltage lockout value ($V_{UVLOboot_R}$).

If, during the falling edge of the PWM signal (from 'H' to tri-state or from 'H' to 'L'), the UVLO_{BOOT} error flag is set, an internal UVLO_{BOOT} counter is incremented by one. This counter is reset to zero if, during a falling edge of PWM, the UVLO_{BOOT} error flag is not set, and the counter value is less than three.

When the counter value reaches three, the driver outputs GH and GL remain disabled, and the power stage output is kept in tri-state, regardless of the PWM input.

To reset the driver and resume operation, the PWM input has to be held continuously in tri-state for 19 μ s (typically). When this happens, the UVLO_{BOOT} counter resets to zero and the driver performs the startup sequence described above in order to sufficiently charge the boot capacitor.

The driver will also be reset when VCIN and/or VDRV will be re-cycled.

2.2 Boot Refresh Circuit

When the converter operates in continuous conduction mode (CCM), switching never stops. This ensures that the boot capacitor is properly recharged during each cycle. Other modes of operation – for example, discontinuous conduction mode (DCM), or a disengaged phase in dynamic phase-shedding operation in multiphase buck converters – can lead to extended periods of tri-state operation during which both MOSFETs are kept in the off-state.

To prevent depletion of the boot capacitor during an extended period in tri-state, a boot refresh circuit is used. Lost charge is replenished from a constant current source connected to the VIN terminal of the device. To ensure full current capability of the current source the voltage difference ($V_{IN} - V_{SW}$) should be more than 4.8 V.

The boot refresh circuit is activated only after continuous tri-state has been established for at least 19 μ s (typically), and the voltage across the boot capacitor has fallen below $V_{UVLOboot_F}$. The circuit remains active until the voltage across the boot capacitor has reached $V_{UVLOboot_R}$, or until the PWM input signal leaves the tri-state region.

3 Circuit Interactions

3.1 Scenario Showing Lacking Transient Support

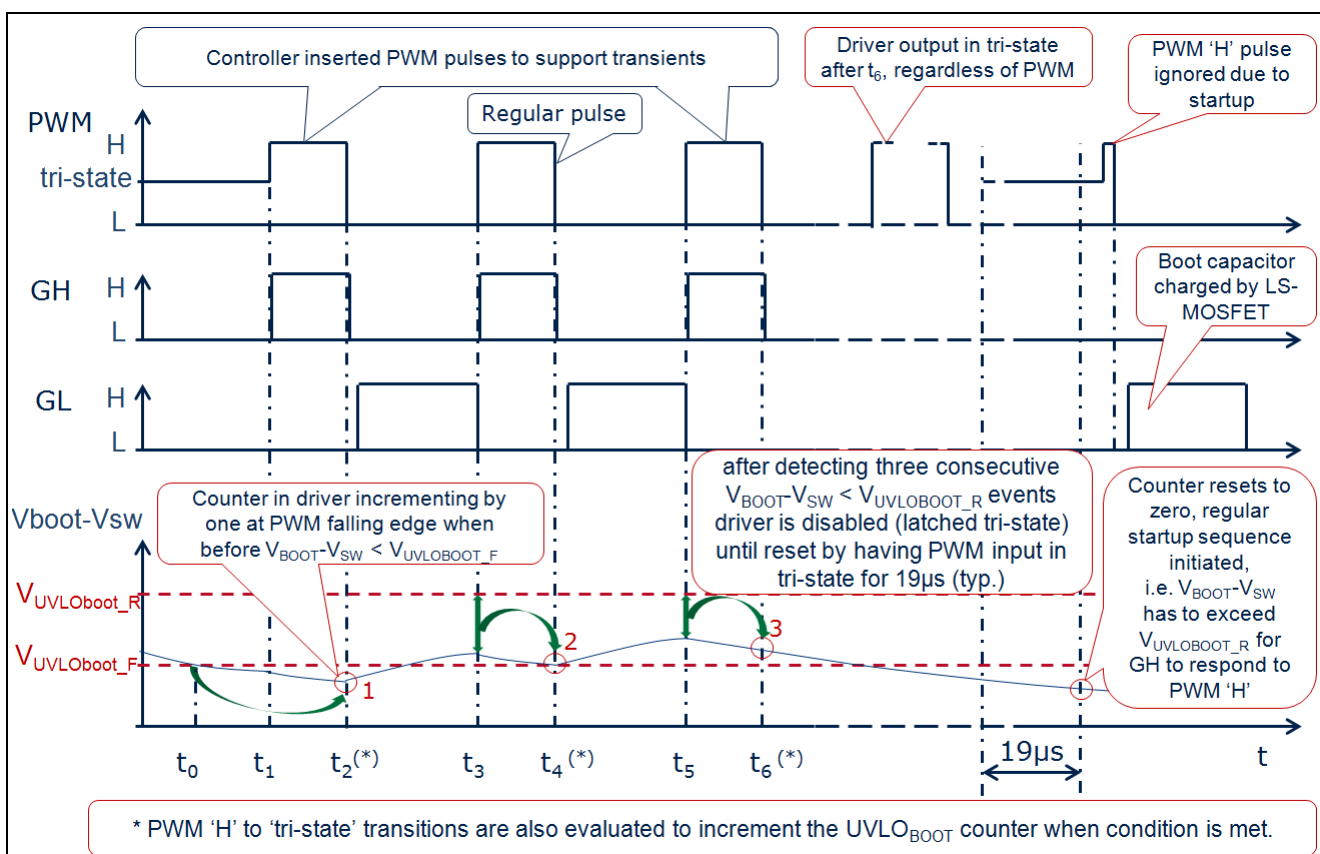


Figure 3 Transient Event Causes Trigger of UVLO_{BOOT}

Figure 3 shows an event that could trigger the UVLO_{BOOT} protection circuit. Up to t_1 , PWM is in the tri-state condition (e.g. disabled phase or end of DCM cycle). At t_0 the voltage across the boot capacitor falls below the lower detection threshold $V_{UVLOBOOT_F}$. At t_1 , a sudden load increase triggers the PWM to go 'H'. The refresh circuit does not engage. The HS MOSFET gate is driven from a voltage close to $V_{UVLOBOOT_F}$. The gate charge for the HS MOSFET is taken from the boot capacitor. At the falling edge of the PWM (t_2), the gate voltage is below $V_{UVLOBOOT_F}$ and the internal UVLO_{BOOT} error flag is set. The UVLO_{BOOT} counter value changes from '0' to '1'. The LS MOSFET now turns on and charge is added to the boot capacitor.

However, in a transient event as shown here, the first PWM 'H' pulse can be the result of the transient support feature, and can be closely followed by a regular pulse. Therefore, the LS MOSFET can be on for a short time only before the second pulse at t_3 turns the HS MOSFET on again. Here, charge is also taken from the boot capacitor. At t_4 (the falling edge of the second PWM 'H' pulse), the voltage across the boot capacitor is still well below $V_{UVLOBOOT_R}$. The error flag remains set and the counter value changes from '1' to '2'. Subsequently, the LS MOSFET turns on again and charge is added to the boot capacitor. With the transient support feature still active, the third PWM 'H' pulse appears at t_5 . The time between the PWM 'H' pulses is too short for the boot capacitor voltage to rise above $V_{UVLOBOOT_R}$. At t_6 (the falling edge of the third PWM 'H' pulse), the error flag is still set and the counter value change from '2' to '3'. At this point, the driver disengages the gate drive of both MOSFETs and the output enters tri-state.

Circuit Interactions

Therefore, the refresh circuit is only used to trickle charge the boot capacitor during extended tri-state periods. It does not play a role in the quick recharge of the boot capacitor to prevent an UVLO_{BOOT} error.

3.2.2 Recharge During LS MOSFET On-Time

The boot capacitor C_{BOOT} is charged by V_{DRV} during the LS MOSFET on-time, via an integrated boot switch. V_{CBOOT} is the voltage across the boot capacitor.

$$V_{CBOOT}(t) = V_{DRV} \cdot (1 - e^{-\frac{t}{\tau}}) \quad [4]$$

$$\tau = C_{BOOT} \cdot R_{BOOT} \quad [5]$$

Since the boot switch consists of a MOSFET in parallel to its body diode, R_{BOOT} depends on the voltage across itself.

$$\tau = C_{BOOT} \cdot R_{BOOT}(V_{RBOOT}) \quad [6]$$

with $V_{RBOOT} = V_{DRV} - V_{CBOOT} \quad [7]$

$$V_{CBOOT}(t) = V_{DRV} \cdot (1 - e^{-\frac{t}{C_{BOOT} \cdot R_{BOOT}(V_{CBOOT})}}) \quad [8]$$

This is an implicit equation and therefore not useful for obtaining the required LS MOSFET on-time. A graphical approach is taken instead.

 


Figure 5 Typical Recharge Time with 47 nF Boot Capacitor as Function of Driving Voltage

Circuit Interactions

 


Figure 6 Typical Recharge Time Characteristic for a 47 nF Boot Capacitor

Different boot capacitor values scale the recharge time linearly.

$$t_{Boot_Recharge} = t_{Boot_Figure3} \cdot (C_{BOOT}/47nF) \quad [9]$$

The actual on-time of the LS MOSFET depends on the switching frequency, the maximum duty cycle setting and the setting of additional transient support pulses.

$$t_{off} = t_{on_LS} = \left(1 - (D_{max} + D_{transient_support})\right) / f_{sw} \quad [10]$$

The application has to ensure that the actual on-time of the LS MOSFET (t_{on_LS}) is at least as long as the time required to recharge the boot capacitor to $V_{UVLOBOOT_R}$.

$$t_{on_LS} \geq t_{Boot_Recharge} \quad [11]$$

As previously described in the $UVLO_{BOOT}$ circuit description, when the error conditions for the boot voltage apply, the third falling edge of the PWM signal triggers the fault.

For further considerations the following assumptions are made:

- high thresholds for the undervoltage lockout ($V_{UVLOBOOT_F} = 3.7V$, $V_{UVLOBOOT_R} = 4.2V$)
- V_{CBOOT} falls to $V_{UVLOBOOT_F}$ when the HS MOSFET is turned on at $t = 0$
- nominal value for C_{BOOT}
- maximum gate charge for the HS MOSFET

Circuit Interactions

Turning on the HS MOSFET just before the boot capacitor voltage reaches $V_{UVLOBOOT_R}$ is the worst case scenario for prolonging the $UVLO_{BOOT}$ condition.

Lastly, the charge taken from the boot capacitor during each HS MOSFET turn-on event before the 3rd pulse has to be considered:

$$Q_{HS_total} = 2 \cdot Q_{G_HS} \quad [12]$$

Additional charging time is required to compensate for the gate charge required.

 


Figure 7 Typical Charging Curve of a 47 nF Boot Capacitor on TDA21320 at $V_{DRV} = 4.5$ V as a Function of Accumulated LS MOSFET On-Time

Figure 7 shows an example of a worst case event during the charging process of a 47 nF boot capacitor. At $t = 0$ charge is taken from the boot capacitor to turn-on the HS MOSFET. $V_{UVLOBOOT_R}$ is exceeded before the third falling edge of the PWM signal. The event does not cause an $UVLO_{BOOT}$ error. A specific case of this scenario is a switching frequency of 500 kHz at a maximum regular duty cycle of 50 %, and one additional transient support pulse with a 25% duty cycle with respect to the switching period.

4 Boot Capacitor Selection Guide

Figure 8 to Figure 22 show the maximum duty cycle permitted against switching frequency depending on the choice of the boot capacitor for a given minimum gate drive voltage V_{DRVmin} (supplying the boot capacitor). These diagrams assume the highest gate charge for the respective device and the nominal value of the respective boot capacitor.

If the controller can introduce one additional pulse per switching cycle to support the transition, the switching frequency has to be read from ' $f_{sw_transient_support}$ '. If the controller simply enhances the duty cycle to support a transient, the switching frequency has to be read from ' $f_{sw_no_added_pulses}$ '. This interprets the count of switching events in case of an $UVLO_{BOOT}$ error condition.

' D_{total} ' is the maximum duty cycle per switching cycle resulting from the sum of the regular pulse (D_{max}) and any additional pulses ($D_{transient_support}$) that may be introduced to support the transient.

The maximum boot capacitor value under consideration is 470 nF. When including tolerance, DC voltage bias and temperature dependency, the smallest recommended nominal value for C_{BOOT} is 47 nF.

The following figures assume 16 V rated boot capacitors with $\pm 10\%$ accuracy. If the operating point is above the line of a specified capacitor, a lower value has to be selected.

4.1 Boot Capacitor Selection Guide for TDA21320

 


Figure 8 Maximum C_{BOOT} for $V_{DRVmin} = 4.5$ V, Note: $D_{total} = D_{max} + D_{transient_support}$

In this example the 68 nF capacitor has to be chosen because the intersection is above the 82 nF line.

Boot Capacitor Selection Guide

 


Figure 9 Maximum C_{BOOT} for $V_{DRVmin} = 4.6\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 10 Maximum C_{BOOT} for $V_{DRVmin} = 4.75\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

Boot Capacitor Selection Guide

 


Figure 11 Maximum C_{BOOT} for $V_{DRVmin} = 4.85\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 12 Maximum C_{BOOT} for $V_{DRVmin} = 5\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

Boot Capacitor Selection Guide

 


Figure 13 Maximum C_{BOOT} for $V_{DRVmin} = 5.15\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 14 Maximum C_{BOOT} for $V_{DRVmin} = 5.25\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 15 Maximum C_{BOOT} for $V_{DRVmin} = 5.5\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

Boot Capacitor Selection Guide

For TDA21320, a boot capacitor of 470 nF can be used at $D_{total} = 75\%$ and $f_{sw_transient_support} = 1200\text{ kHz}$, when $V_{DRVmin} = 5.51\text{ V}$.

4.2 Boot Capacitor Selection Guide for TDA21321

 


Figure 16 Maximum C_{BOOT} for $V_{DRVmin} = 4.5\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

Boot Capacitor Selection Guide

 


Figure 17 Maximum C_{BOOT} for $V_{DRVmin} = 4.6\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 18 Maximum C_{BOOT} for $V_{DRVmin} = 4.75\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

Boot Capacitor Selection Guide

 


Figure 19 Maximum C_{BOOT} for $V_{DRVmin} = 4.85\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 20 Maximum C_{BOOT} for $V_{DRVmin} = 5\text{ V}$, Note: $D_{total} = D_{max} + D_{transient_support}$

Boot Capacitor Selection Guide

 


Figure 21 Maximum C_{BOOT} for $V_{DRVmin} = 5.15$ V, Note: $D_{total} = D_{max} + D_{transient_support}$

 


Figure 22 Maximum C_{BOOT} for $V_{DRVmin} = 5.25$ V, Note: $D_{total} = D_{max} + D_{transient_support}$

For TDA21321, a boot capacitor of 470 nF can be used at $D_{total} = 75\%$ and $f_{sw_transient_support} = 1200$ kHz, when $V_{DRVmin} = 5.49$ V.

Conclusion

5 Conclusion

Viable boot capacitor values range from 47 nF to 470 nF, dependent on circuit conditions. To reliably support load transients, the value of the boot capacitor may not exceed the value obtained from the diagrams provided in this document. It is important to ensure that the operating mode during transients is fully understood, as this affects the countable events for the UVLO_{BOOT} error output.

Primarion™ digital DC/DC controllers can support steep transients since they feature a variety of transient support functions. When using these functions, make sure that you understand the implications of the selection of the boot capacitor, and how this depends on pulse count and the total duty cycle at a given switching frequency and driver supply voltage.

Additional information can be found here:

- [DrBlade™ 2 power stage and Digital VR Controller](#)
- More Info: <http://www.infineon.com/cms/en/product/promopages/DCDC-System-Solution/>
- Power Management Selection Guide: <http://www.infineon.com/powermanagement-selectionguide>
- Where to Buy: www.infineon.com/wheretobuy
- Search for Orderable Part Number (OPN): www.infineon.com/opn
- Contact/Support: www.infineon.com/support

Conclusion

Revision History

Major changes since the last revision

Page or Reference	Description of change

Trademarks of Infineon Technologies AG

AURIX™, C166™, CanPAK™, CIPOST™, CIPURSET™, CoolGaN™, CoolMOS™, CoolSET™, CoolSiC™, CORECONTROL™, CROSSAVET™, DAVE™, DI-POL™, DrBLADE™, EasyPIM™, EconoBRIDGE™, EconoDUAL™, EconoPACK™, EconoPIM™, EiceDRIVER™, eupec™, FCOS™, HITFET™, HybridPACK™, ISOFACE™, IsoPACK™, i-Wafer™, MIPAQ™, ModSTACK™, my-d™, NovalithIC™, OmniTune™, OPTIGA™, OptiMOS™, ORIGA™, POWERCODE™, PRIMARION™, PrimePACK™, PrimeSTACK™, PROFET™, PRO-SIL™, RASIC™, REAL3™, ReverSave™, SatRIC™, SIEGET™, SIPMOS™, SmartLEWIS™, SOLID FLASH™, SPOC™, TEMPFET™, thinQ!™, TRENCHSTOP™, TriCore™.

Other Trademarks

Advance Design System™ (ADS) of Agilent Technologies, AMBA™, ARM™, MULTI-ICE™, KEIL™, PRIMECELL™, REALVIEW™, THUMB™, μVision™ of ARM Limited, UK. ANSI™ of American National Standards Institute. AUTOSAR™ of AUTOSAR development partnership. Bluetooth™ of Bluetooth SIG Inc. CAT-iq™ of DECT Forum. COLOSSUS™, FirstGPS™ of Trimble Navigation Ltd. EMV™ of EMVCo, LLC (Visa Holdings Inc.). EPCOS™ of Epcos AG. FLEXGO™ of Microsoft Corporation. HYPERTERMINAL™ of Hilgraeve Incorporated. MCS™ of Intel Corp. IEC™ of Commission Electrotechnique Internationale. IrDA™ of Infrared Data Association Corporation. ISO™ of INTERNATIONAL ORGANIZATION FOR STANDARDIZATION. MATLAB™ of MathWorks, Inc. MAXIM™ of Maxim Integrated Products, Inc. MICROTEC™, NUCLEUS™ of Mentor Graphics Corporation. MIPI™ of MIPI Alliance, Inc. MIPS™ of MIPS Technologies, Inc., USA. muRata™ of MURATA MANUFACTURING CO., MICROWAVE OFFICE™ (MWO) of Applied Wave Research Inc., OmniVision™ of OmniVision Technologies, Inc. Openwave™ of Openwave Systems Inc. RED HAT™ of Red Hat, Inc. RFMD™ of RF Micro Devices, Inc. SIRIUS™ of Sirius Satellite Radio Inc. SOLARIS™ of Sun Microsystems, Inc. SPANSION™ of Spansion LLC Ltd. Symbian™ of Symbian Software Limited. TAIYO YUDEN™ of Taiyo Yuden Co. TEAKLITE™ of CEVA, Inc. TEKTRONIX™ of Tektronix Inc. TOKO™ of TOKO KABUSHIKI KAISHA TA. UNIX™ of X/Open Company Limited. VERILOG™, PALLADIUM™ of Cadence Design Systems, Inc. VLYNQ™ of Texas Instruments Incorporated. VXWORKS™, WIND RIVER™ of WIND RIVER SYSTEMS, INC. ZETEX™ of Diodes Zetex Limited.

Last Trademarks Update 2014-07-17

www.infineon.com

Edition 2014-09-26

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2014 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about any aspect of this document?

Email: erratum@infineon.com

Document reference

AN_201408_PL11_005

Legal Disclaimer

THE INFORMATION GIVEN IN THIS APPLICATION NOTE (INCLUDING BUT NOT LIMITED TO CONTENTS OF REFERENCED WEBSITES) IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office. Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.