

## AN-REF-15W ADAPTER

15W 5V Adapter Reference Board  
with ICE2QS03G, IPU60R950C6  
BSC067N06LS3 G & BAS21-03W

Application Note AN-REF-15W ADAPTER  
V1.0, 2014-07-02

**Edition 2014-07-02**

**Published by Infineon Technologies AG,  
81726 Munich, Germany.**

**© 2014 Infineon Technologies AG  
All Rights Reserved.**

## **LEGAL DISCLAIMER**

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

### **Information**

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

### **Warnings**

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office.

Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

**Trademarks of Infineon Technologies AG**

AURIX™, C6 6™, CanPAK™, CIPOST™, CIPURSE™, EconoPACK™, CoolMOS™, CoolSET™, CORECONTROL™, CROSSAVE™, DAVE™, DI-POL™, EasyPIM™, EconoBRIDGE™, EconoDUAL™, EconoPIM™, EconoPACK™, EiceDRIVER™, eupec™, FCOS™, HITFET™, HybridPACK™, I<sup>2</sup>RF™, ISOFACE™, IsoPACK™, MIPAQ™, ModSTACK™, my-d™, NovalithIC™, OptiMOS™, ORIGA™, POWERCODE™, PRIMARION™, PrimePACK™, PrimeSTACK™, PRO-SIL™, PROFET™, RASIC™, ReverSave™, SatRIC™, SIEGET™, SINDRION™, SIPMOS™, SmartLEWIS™, SOLID FLASH™, TEMPFET™, thinQ!™, TRENCHSTOP™, TriCore™.

**Other Trademarks**

Advance Design System™ (ADS) of Agilent Technologies, AMBA™, ARM™, MULTI-ICE™, KEIL™, PRIMECELL™, REALVIEW™, THUMB™, μVision™ of ARM Limited, UK. AUTOSAR™ is licensed by AUTOSAR development partnership. Bluetooth™ of Bluetooth SIG Inc. CAT-iq™ of DECT Forum. COLOSSUS™, FirstGPS™ of Trimble Navigation Ltd. EMV™ of EMVCo, LLC (Visa Holdings Inc.). EPCOS™ of Epcos AG. FLEXGO™ of Microsoft Corporation. FlexRay™ is licensed by FlexRay Consortium. HYPERTERMINAL™ of Hilgraeve Incorporated. IEC™ of Commission Electrotechnique Internationale. IrDA™ of Infrared Data Association Corporation. ISO™ of INTERNATIONAL ORGANIZATION FOR STANDARDIZATION. MATLAB™ of MathWorks, Inc. MAXIM™ of Maxim Integrated Products, Inc. MICROTEC™, NUCLEUS™ of Mentor Graphics Corporation. MIPI™ of MIPI Alliance, Inc. MIPS™ of MIPS Technologies, Inc., USA. muRata™ of MURATA MANUFACTURING CO., MICROWAVE OFFICE™ (MWO) of Applied Wave Research Inc., OmniVision™ of OmniVision Technologies, Inc. Openwave™ Openwave Systems Inc. RED HAT™ Red Hat, Inc. RFMD™ RF Micro Devices, Inc. SIRIUS™ of Sirius Satellite Radio Inc. SOLARIS™ of Sun Microsystems, Inc. SPANSION™ of Spansion LLC Ltd. Symbian™ of Symbian Software Limited. TAIYO YUDEN™ of Taiyo Yuden Co. TEAKLITE™ of CEVA, Inc. TEKTRONIX™ of Tektronix Inc. TOKO™ of TOKO KABUSHIKI KAISHA TA. UNIX™ of X/Open Company Limited. VERILOG™, PALLADIUM™ of Cadence Design Systems, Inc. VLYNQ™ of Texas Instruments Incorporated. VXWORKS™, WIND RIVER™ of WIND RIVER SYSTEMS, INC. ZETEX™ of Diodes Zetex Limited.

Last Trademarks Update 2011-11-11

## Revision History

AN\_201406\_PL21\_005

### Major changes since previous revision

Date	Version	Changed By	Change Description
2 Jul 2014	1.0	Kyaw Zin Min	Release of final version

### We Listen to Your Comments

Is there any information in this document that you feel is wrong, unclear or missing? Your feedback will help us to continuously improve the quality of our documentation. Please send your proposal (including a reference to this document title/number) to:

[ctdd@infineon.com](mailto:ctdd@infineon.com)



## Table of Contents

<b>Revision History .....</b>	<b>4</b>
<b>Table of Contents .....</b>	<b>5</b>
<b>1 Abstract .....</b>	<b>7</b>
<b>2 Reference board.....</b>	<b>7</b>
<b>3 Technical specifications .....</b>	<b>8</b>
<b>4 List of features (ICE2QS03G).....</b>	<b>8</b>
<b>5 Circuit description .....</b>	<b>9</b>
5.1 Mains Input Rectification and Filtering .....	9
5.2 PWM Control and switching MosFET .....	9
5.3 Snubber Network .....	9
5.4 Output Stage.....	9
5.5 Feedback Loop .....	9
<b>6 Circuit Operation.....</b>	<b>10</b>
6.1 Startup Operation.....	10
6.2 Normal Mode Operation .....	10
6.3 Primary side peak current control .....	10
6.4 Digital Frequency Reduction.....	10
6.5 Burst Mode Operation .....	10
<b>7 Protection Features.....</b>	<b>11</b>
7.1 VCC over voltage and under voltage protection .....	11
7.2 Over load/Open loop protection.....	11
7.3 Auto restart for over temperature protection.....	11
7.4 Adjustable output overvoltage protection .....	11
7.5 Short winding protection.....	11
7.6 Foldback point protection .....	11
<b>8 Circuit diagram.....</b>	<b>12</b>
<b>9 PCB layout.....</b>	<b>13</b>
9.1 Top side.....	13
9.2 Bottom side.....	13
<b>10 Component list.....</b>	<b>14</b>
<b>11 Transformer construction.....</b>	<b>15</b>
<b>12 Test results.....</b>	<b>16</b>
12.1 Efficiency .....	16
12.2 Input standby power .....	17
12.3 Line regulation .....	18
12.4 Load regulation .....	18
12.5 Maximum power.....	19
12.6 ESD immunity (EN61000-4-2) .....	19
12.7 Surge immunity (EN61000-4-5) .....	19
12.8 Conducted emissions (EN55022 class B) .....	20
12.9 Thermal measurement .....	22


<b>13</b>	<b>Waveforms and scope plots.....</b>	<b>23</b>
13.1	Start up at low/high AC line input voltage with maximum load.....	23
13.2	Soft start.....	23
13.3	Drain voltage and current at maximum load.....	24
13.4	Zero crossing point during normal operation.....	24
13.5	Load transient response (Dynamic load from 10% to 100%).....	25
13.6	Output ripple voltage at maximum load.....	25
13.7	Output ripple voltage during burst mode at 1 W load.....	26
13.8	Active Burst mode operation.....	26
13.9	Over load protection (Auto restart mode).....	27
13.10	Output overvoltage protection (Latched off mode).....	27
13.11	V <sub>CC</sub> under voltage/Short optocoupler protection (Auto restart mode).....	28
<b>14</b>	<b>References .....</b>	<b>28</b>

## 1 Abstract


This application note is an engineering report of a very small form factor reference design for universal input 15W 5V adapter. The adapter is using **ICE2QS03G**, a second generation current mode control quasi-resonant flyback topology controller, **IPU60R950C6**, a sixth generation of high voltage power CoolMOS™ and **BSC067N06LS3 G**, a third series of medium voltage power OptiMOS™, optimized for Synchronous Rectification. The distinguishing features of this reference design are very small form factor, best in class low standby power, very high efficiency, good EMI performance and various modes of protection for high reliable system.

## 2 Reference board


This document contains the list of features, the power supply specification, schematic, bill of material and the transformer construction documentation. Typical operating characteristics such as performance curve and scope waveforms are showed at the rear of the report.

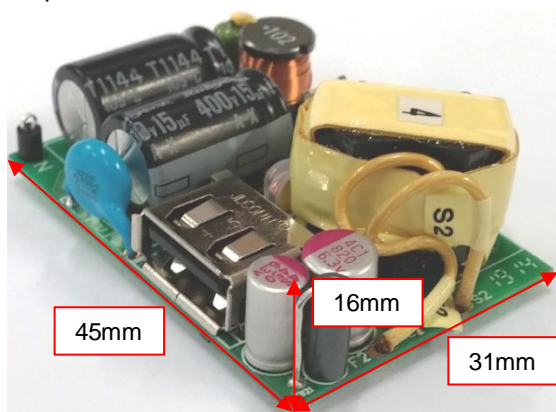

**Figure 1** – REF-ICE2QS03G, IPU60R950C6 & BSC067N06LS3 G 15W ADAPTER [Dimensions L x W x H: 45mm x 31mm x 16mm]

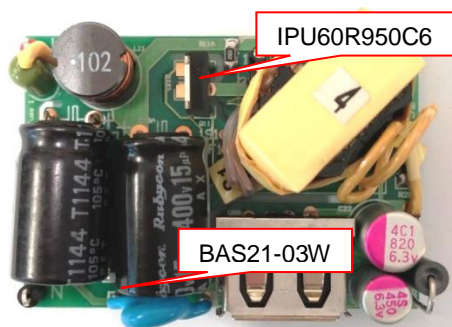

**Figure 2A** – REF-ICE2QS03G, IPU60R950C6 & BSC067N06LS3 G 15W ADAPTER (Top Side)

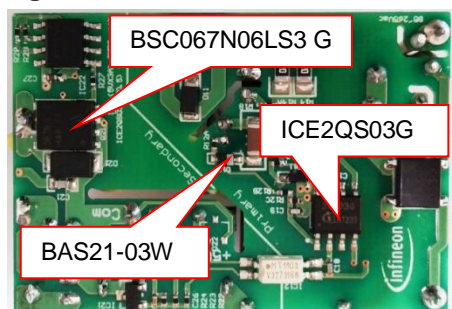

**Figure 2B** – REF-ICE2QS03G, IPU60R950C6 & BSC067N06LS3 G 15W ADAPTER (Bottom Side)

### 3 Technical specifications

Input voltage	85Vac~265Vac
Input frequency	50~60Hz
Output voltage	5V
Output current	3A
Output power	15W
Minimum switching frequency at full load and minimum input voltage	45kHz
Maximum input power(Peak Power) for full input range	< $\pm 6\%$ of input power
No-load power consumption	< 75mW (comply with EU CoC Version 5, Tier 2 and EPS of DOE USA)
Active mode four point average efficiency (25%,50%,75% & 100%load)	>81.84% (comply with EU CoC Version 5, Tier 2 and EPS of DOE USA)
Active mode at 10% load efficiency	>72.48% (comply with EU CoC Version 5, Tier 2)
Form factor case size (L x W x H)	(45 x 31 x 16) mm <sup>3</sup>

### 4 List of features (ICE2QS03G)

Quasi resonant operation till very low load
Active burst mode operation at light/no load for low standby input power (< 100mW)
Digital frequency reduction with decreasing load
HV startup cell with constant charging current
Built-in digital soft-start
Foldback correction and cycle-by-cycle peak current limitation
Auto restart mode for VCC Overvoltage protection
Auto restart mode for VCC Undervoltage protection
Auto restart mode for Overload /Openloop protection
Auto restart mode for Over temperature protection
Latch-off mode for adjustable output overvoltage protection
Latch-off mode for Short Winding



## 5 Circuit description

### 5.1 Mains Input Rectification and Filtering

The AC line input side comprises the input fuse F1 as over-current protection. A rectified DC voltage (120V ~ 374V) is obtained through a bridge rectifier BR1 and a pi filter C13, FB21 and C22. The pi filter also attenuates the differential mode conducted EMI.

### 5.2 PWM Control and switching MosFET

The PWM pulse is generated by the Quasi Resonant PWM current-mode Controller **ICE2QS03G** and this PWM pulse drives the high voltage power CoolMOS™, **IPU60R950C6 (C6)** which designed according to the revolutionary Superjunction (SJ) principle. The CoolMOS™ C6 provides all benefits of a fast switching SJ MOSFET while not sacrificing ease of use. It achieves extremely low conduction and switching losses and can make switching applications more efficient, more compact, lighter and cooler. The PWM switch-on is determined by the zero-crossing input signal and the value of the up/down counter. The PWM switch-off is determined by the feedback signal  $V_{FB}$  and the current sensing signal  $V_{CS}$ . **ICE2QS03G** also performs all necessary protection functions in flyback converters. Details about the information mentioned above are illustrated in the product datasheet.

### 5.3 Snubber Network

A snubber network R11, R11A, C15 and D11 dissipate the energy of the leakage inductance and suppress ringing on the SMPS transformer. Due to the resonant capacitor (MOSFET's drain source capacitance), the overshoot is relatively smaller than fixed frequency flyback converter. Thus the snubber resistor can be used with a larger one which will reduce the snubber loss.

### 5.4 Output Stage

On the secondary side, 5V output, the PWM pulse is generated by synchronous rectification controller **UCC24610**. The synchronous rectification pulse drives the medium voltage power OptiMOS™, **BSC067N06LS3 -G** which is optimized for synchronous rectification such as the lowest  $R_{DS(on)}$ , the perfect switching behavior of fast switching, the smallest footprint and highest power density. The capacitors C22 provides energy buffering following with the LC filter FB21 and C24 to reduce the output ripple and prevent interference between SMPS switching frequency and line frequency considerably. Storage capacitor C22 is designed to have an internal resistance (ESR) as small as possible. This is to minimize the output voltage ripple caused by the triangular current.

### 5.5 Feedback Loop

For feedback, the output is sensed by the voltage divider of R26 and R25 and compared to TL431 internal reference voltage. C25, C26 and R24 comprise the compensation network. The output voltage of TL431 is converted to the current signal via optocoupler IC12 and two resistors R22 and R23 for regulation control.

## 6 Circuit Operation

### 6.1 Startup Operation

Since there is a built-in startup cell in the **ICE2QS03G**, there is no need for external start up resistor, which can improve standby performance significantly. When VCC reaches the turn on voltage threshold 18V, the IC begins with a soft start. The soft-start implemented in **ICE2QS03G** is a digital time-based function. The preset soft-start time is 12ms with 4 steps. If not limited by other functions, the peak voltage on CS pin will increase step by step from 0.32V to 1V finally. After IC turns on, the Vcc voltage is supplied by auxiliary windings of the transformer.

### 6.2 Normal Mode Operation

The secondary output voltage is built up after startup. The secondary regulation control is adopted with TL431 and optocoupler. The compensation network C25, C26 and R24 constitutes the external circuitry of the error amplifier of TL431. This circuitry allows the feedback to be precisely controlled with respect to dynamically varying load conditions, therefore providing stable control.

### 6.3 Primary side peak current control

The MOSFET drain source current is sensed via external resistor R14 and R14A. Since **ICE2QS03G** is a current mode controller, it would have a cycle-by-cycle primary current and feedback voltage control which can make sure the maximum power of the converter is controlled in every switching cycle.

### 6.4 Digital Frequency Reduction

During normal operation, the switching frequency for **ICE2QS03G** is digitally reduced with decreasing load. At light load, the CoolMOS™ **IPU60R950C6** will be turned on not at the first minimum drain-source voltage time, but on the  $n^{\text{th}}$ . The counter is in range of 1 to 7, which depends on feedback voltage in a time-base. The feedback voltage decreases when the output power requirement decreases, and vice versa. Therefore, the counter is set by monitoring voltage  $V_{\text{FB}}$ . The counter will be increased with low  $V_{\text{FB}}$  and decreased with high  $V_{\text{FB}}$ . The thresholds are preset inside the IC.

### 6.5 Burst Mode Operation

At light load condition, the SMPS enters into **Active Burst Mode**. At this stage, the controller is always active but the Vcc must be kept above the switch off threshold. During active burst mode, the efficiency increase significantly and at the same time it supports low ripple on  $V_{\text{out}}$  and fast response on load jump.

For determination of entering Active Burst Mode operation, three conditions apply:

1. The feedback voltage is lower than the threshold of  $V_{\text{FBE}}(1.25\text{V})$ . Accordingly, the peak current sense voltage across the shunt resistor is 0.1667;
2. The up/down counter is 7;
3. And a certain blanking time ( $t_{\text{BEB}}=24\text{ms}$ ).

Once all of these conditions are fulfilled, the Active Burst Mode flip-flop is set and the controller enters Active Burst Mode operation. This multi-condition determination for entering Active Burst Mode operation prevents mis-triggering of entering Active Burst Mode operation, so that the controller enters Active Burst Mode operation only when the output power is really low during the preset blanking time.

During active burst mode, the maximum current sense voltage is reduced from 1V to 0.34V so as to reduce the conduction loss and the audible noise. At the burst mode, the FB voltage is changing like a sawtooth between 3.0 and 3.6V.

The feedback voltage immediately increases if there is a high load jump. This is observed by one comparator. As the current limit is 34% during Active Burst Mode a certain load is needed so that feedback voltage can exceed VLB (4.5V). After leaving active burst mode, maximum current can now be provided to stabilize  $V_{\text{O}}$ . In addition, the up/down counter will be set to 1 immediately after leaving Active Burst Mode. This is helpful to decrease the output voltage undershoot.

## 7 Protection Features

### 7.1 VCC over voltage and under voltage protection

During normal operation, the Vcc voltage is continuously monitored. When the Vcc voltage increases up to  $V_{VCCOV}$  or Vcc voltage falls below the under voltage lock out level  $V_{VCCoff}$ , the IC will enter into autorestart mode.

### 7.2 Over load/Open loop protection

In case of open control loop, feedback voltage is pulled up with internally block. After a fixed blanking time, the IC enters into auto restart mode. In case of secondary short-circuit or overload, regulation voltage  $V_{FB}$  will also be pulled up, same protection is applied and IC will auto restart.

### 7.3 Auto restart for over temperature protection

The IC has a built-in over temperature protection function. When the controller's temperature reaches 140 °C, the IC will shut down switch and enters into auto restart. This can protect power MOSFET from overheated.

### 7.4 Adjustable output overvoltage protection

During off-time of the power switch, the voltage at the zero-crossing pin ZC is monitored for output overvoltage detection. If the voltage is higher than the preset threshold 3.7V for a preset period 100µs, the IC is latched off.

### 7.5 Short winding protection


The source current of the MOSFET is sensed via external resistor R14 and R14A. If the voltage at the current sensing pin is higher than the preset threshold  $V_{CSSW}$  of 1.68V during the on-time of the power switch, the IC is latched off. This constitutes a short winding protection. To avoid an accidental latch off, a spike blanking time of 190ns is integrated in the output of internal comparator.

### 7.6 Foldback point protection

For a quasi-resonant flyback converter, the maximum possible output power is increased when a constant current limit value is used for all the mains input voltage range. This is usually not desired as this will increase additional cost on transformer and output diode in case of output over power conditions.

The internal foldback protection is implemented to adjust the VCS voltage limit according to the bus voltage. Here, the input line voltage is sensed using the current flowing out of ZC pin, during the MOSFET on-time. As the result, the maximum current limit will be lower at high input voltage and the maximum output power can be well limited versus the input voltage.

## 8 Circuit diagram

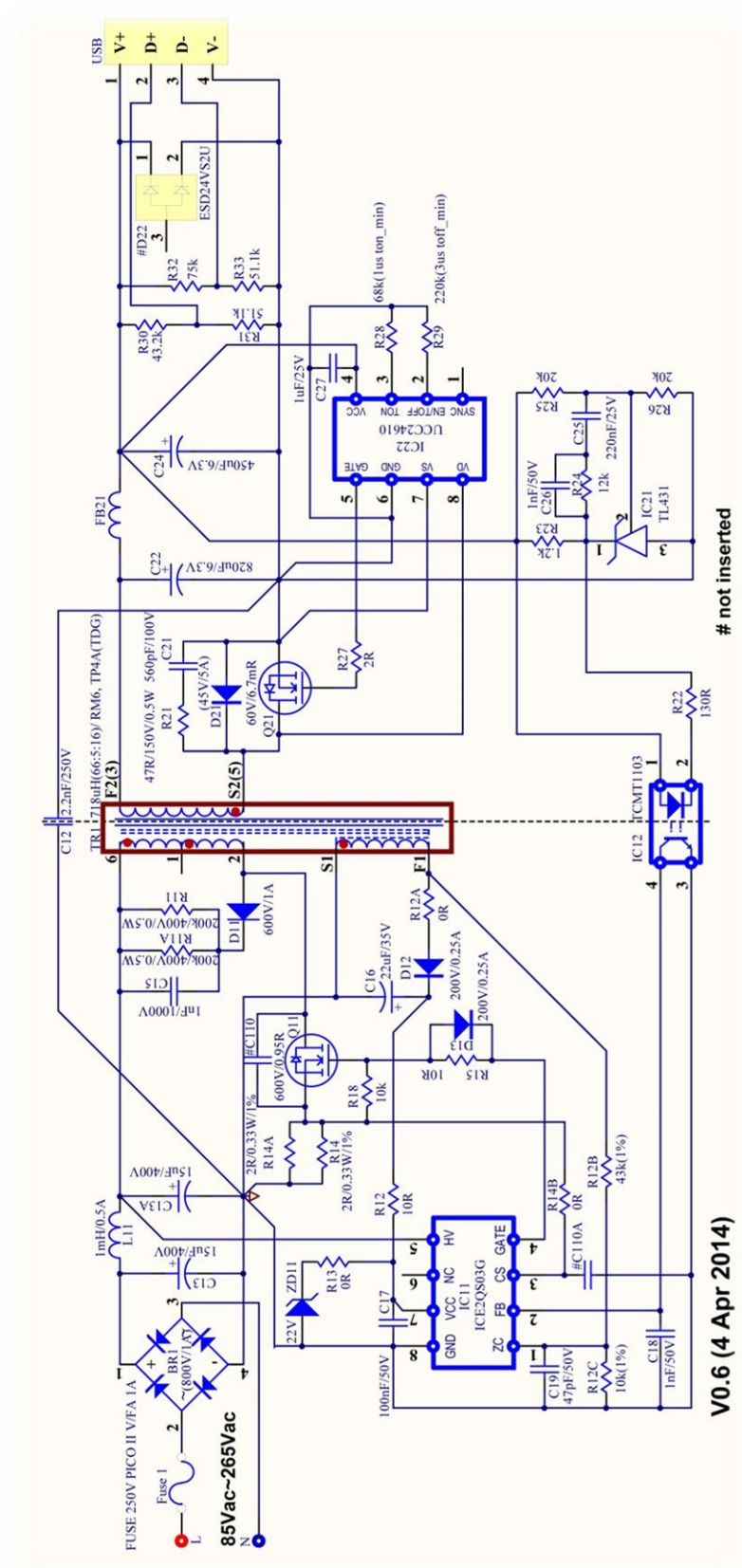

**Figure 3 – 15W 5V ICEICE2QSO3G power supply schematic**

## 9 PCB layout

### 9.1 Top side

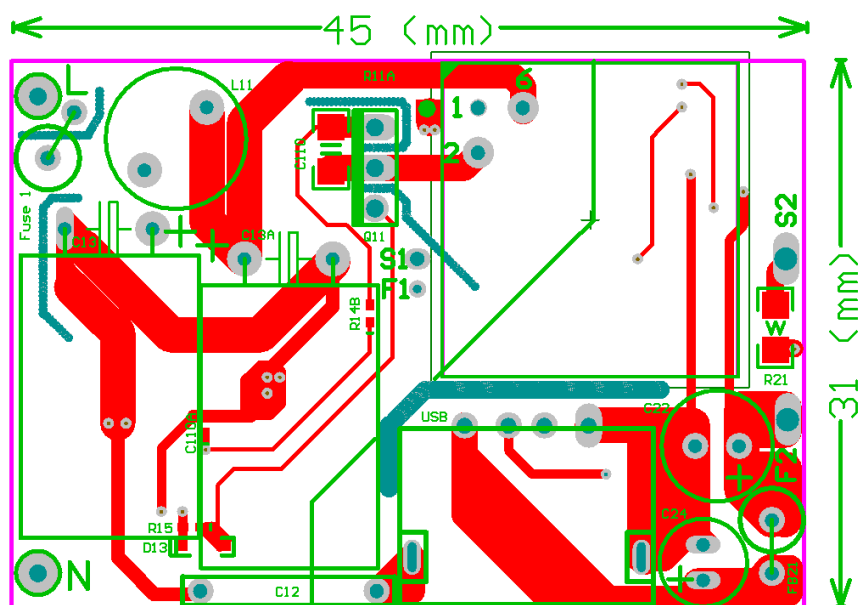


Figure 4 – Top side copper and component legend

### 9.2 Bottom side

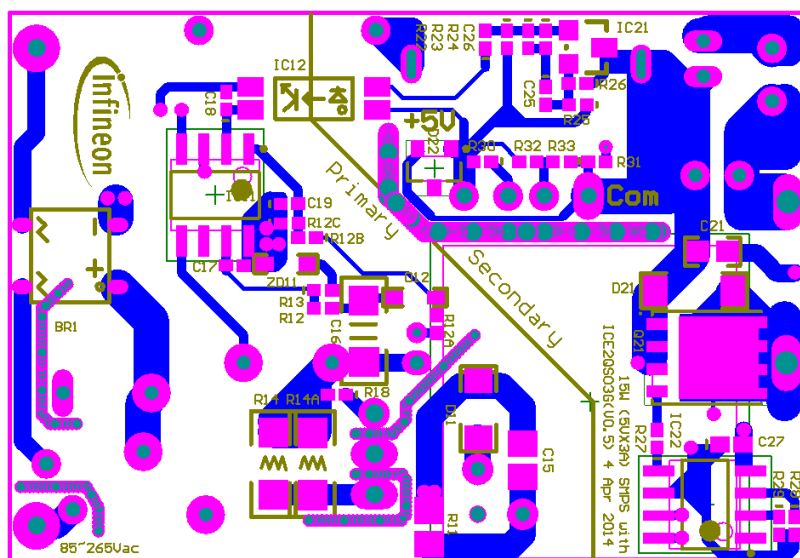


Figure 5 – Bottom side copper and component legend

## 10 Component list

Designator	Description	Footprint	Part Number	Manufacturer	Quantity
BR1	(800V/1A)	SOP-4	D1UBA80	SHINDENGEN	1
C12	2.2nF/250V	MKT2/13/10_0M8	DE1E3KL222MC4BNA1S	MURATA	1
C13, C13A	15uF/400V	RB10H(10x16)	400AX15M10X16	RUBYCON	2
C15	1nF/1000V	0805	C0805X102KDRACU		1
C16	22uF/35V	1206	C3216X5R1V226M		1
C17	100nF/50V	0402	GRM155R71H104KE14D	MURATA	1
C18, C26	1nF/50V	0402	GRM155R71H102KA01D	MURATA	2
C19	47pF/50V	0402	GRM1555C1H470JA01D	MURATA	1
C21	560pF/100V	0603	GRM1885C2A561JA01D	MURATA	1
C22	820uF/6.3V	RB6.3	MP6RL820MC8		1
C24	450uF/6.3V	RB5	MP6RL450MB8		1
C25	220nF/25V	0402	GRM155C81E224KE01D	MURATA	1
C27	1uF/25V	0402	GRM155R61E105KA12D	MURATA	1
D11	600V/1A	Sub SMA	ES1JL		1
D12,D13	200V/0.25A	SOD323	BAS21-03W	INFINEON	2
D21	45V/5A	DO-221AC(slimSMA)	VSSAF5L45		1
F1	250V/1A	AXIAL0.4_V 3mm	0263001.HAT1L		1
FB21	FAIR RITE	AXIAL0.4_V 3mm	2743002112		1
IC11	ICE2QS03G	SO-8	ICE2QS03G	INFINEON	1
IC12	TCMT1103	optocoupler half pitch	TCMT1103		1
IC21	TL431	SOT-23	TL431BFDT		1
IC22	UCC24610	SO-8	UCC24610		1
L	connector	Connector	5000RED		1
L11	1mH/0.5A	CH8	768772102	WURTH ELECTRONICS	1
N	Connector N(2.5diameter)	Connector(2.5diameter)	5001BLACK		1
Q11	600V/0.95R	TO-251(IPAK)	IPU60R950C6	INFINEON	1
Q21	60V/6.7mR	INF-PG-TDSON-8-1	BSC067N06LS3 G	INFINEON	1
R11,R11A	200k/400V/0.5W	0805	ERJP06F2003V		2
R12, R15	10R	0402			2
R12A, R13, R14B	0R	0402			3
R12B	43k/1%	0402			1
R12C	10k/1%	0402			1
R14, R14A	2R/0.33W/1%	1206	ERJ8BQF2R0V		2
R18	10k	0402			1
R21	47R/0.5W	0805	ERJP6WF47R0V		1
R22	130R	0402			1
R23	1.2k	0402			1
R24	12k	0402			1
R25, R26	20k	0402			2
R27	2R	0402			1
R28	68k	0402			1
R29	220k	0402			1
R30	43.2k	0402			1
R31, R33	51.1k	0402			1
R32	75k	0402			1
TR1	718uH(66:5:16) RM6(TP4A)	TR_RM6_THT6Pin			1
USB Port	USBPORT	USB2 Short(Horizontal)	JL-CAF-001		1
ZD11	22V Zener	SOD323	UDZS22B		1




## 11 Transformer construction


Core and material: RM6 TP4A

Bobbin: RM6 with 3 pin

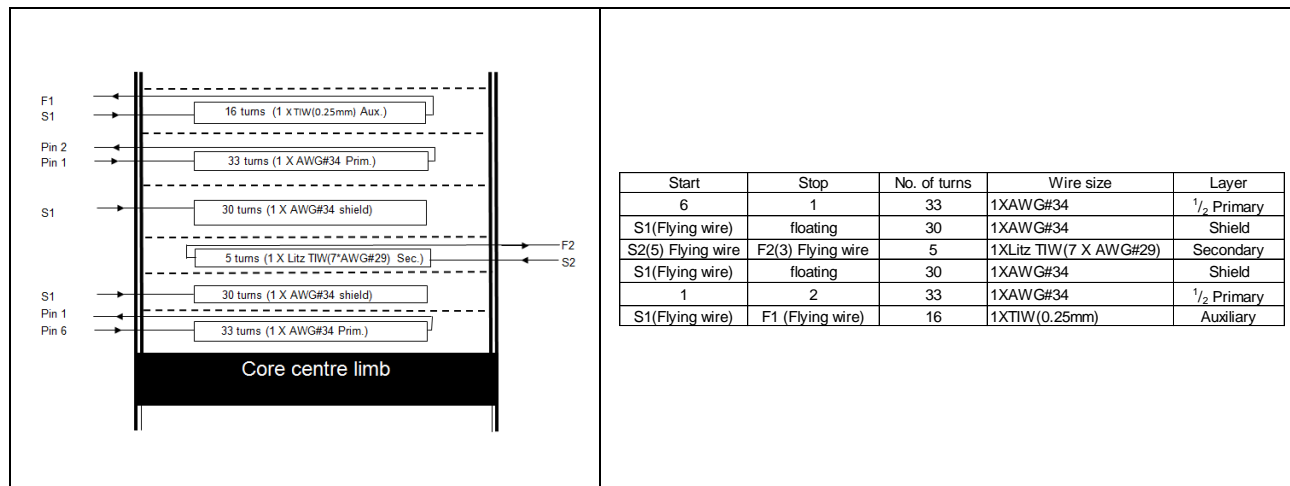Primary Inductance,  $L_p=718 \mu\text{H}$  ( $\pm 10\%$ ), measured between pin 2 and pin 6



CUSTOMER TERMINAL	RoHS	LEAD(Pb)-FREE
Sn96%, Ag4%	Yes	Yes

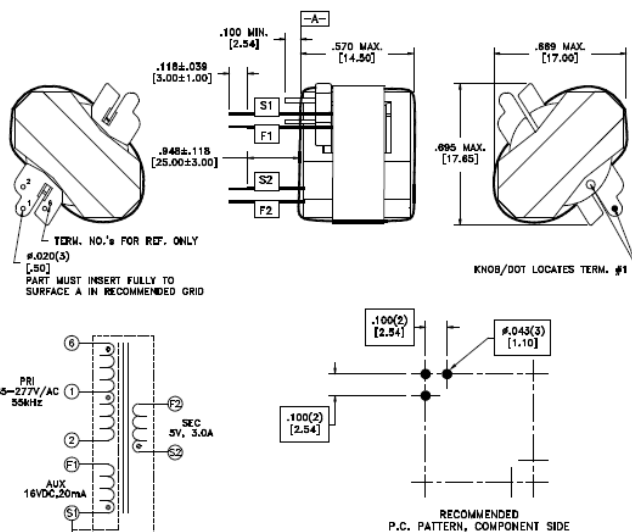

### ELECTRICAL SPECIFICATIONS @ 25°C unless otherwise noted:

PARAMETER	TEST CONDITIONS	VALUE
D.C. RESISTANCE	6-2	1.913 ohms Max
D.C. RESISTANCE	S1-F1	0.393 ohms Max
D.C. RESISTANCE	S2-F2	0.015 ohms Max
INDUCTANCE	6-2	50kHz, 100mVAC, $I_s$
LEAKAGE INDUCTANCE	6-2	tie(S1+F1+S2+F2), 100kHz, 100mVAC, $I_s$
DELECTRIC	1-S2	6250VDC, 1 second
DELECTRIC	S2-Core	6250VDC, 1 second
TURN RATIO	(6-2)-(S1-F1)	4.12:1, $\pm 2\%$
TURN RATIO	(6-2)-(S2-F2)	13.2:1, $\pm 2\%$

### GENERAL SPECIFICATIONS:

OPERATING TEMPERATURE RANGE: -40°C to +125°C including temp rise.

Designed to comply with the following requirements as defined by IEC80950-1, - Reinforced insulation for a primary circuit at a working voltage of 400VDC.

Wire insulation & RoHS status not affected by wire color.  
Wire insulation color may vary depending on availability.


REV.	DATE	Packaging Specifications	Tolerances unless otherwise specified:	DRAWING TITLE	PART NO.
00	02/14	Method: Tray PKG-0103 www.infineon.com/midcom	Angles: $\pm 1^\circ$ Fractions: $\pm 1/64$ This drawing is dual dimensioned. Dimensions in brackets are in millimeters.	TRANSFORMER	XXXXXXXXX
SEE REVISION SHEET FOR REVISION LEVEL					SPECIFICATION SHEET 1 OF 1

Figure 6 – Transformer structure

## 12 Test results


### 12.1 Efficiency

Vin(Vac)	Pin(W)	Vo(Vdc)	Io(A)	V <sub>Out_ripple</sub> _pk_pk (mV)	Po(W)	$\eta$ (%)	Average $\eta$ (%)	OLP P <sub>in</sub> (W)	OLP I <sub>out</sub> (A)
85	0.0308	4.99	0.00	59.70			88.24	19.50	3.37
	1.7300	4.99	0.30	57.40	1.50	86.53			
	4.2300	4.99	0.75	22.60	3.74	88.48			
	8.4200	4.99	1.50	32.10	7.49	88.90			
	12.6800	4.99	2.25	35.20	11.23	88.54			
	17.2000	4.99	3.00	49.70	14.97	87.03			
115	0.0316	4.99	0.00	64.90			89.24	19.36	3.44
	1.7200	4.99	0.30	59.90	1.50	87.03			
	4.2200	4.99	0.75	20.10	3.74	88.68			
	8.3700	4.99	1.50	29.80	7.49	89.43			
	12.5200	4.99	2.25	35.00	11.23	89.68			
	16.7900	4.99	3.00	40.30	14.97	89.16			
230	0.0352	4.99	0.00	70.20			87.98	21.25	3.66
	1.7600	4.99	0.30	81.30	1.50	85.06			
	4.3700	4.99	0.75	22.40	3.74	85.64			
	8.4100	4.99	1.50	33.50	7.49	89.00			
	12.5400	4.99	2.25	35.30	11.23	89.53			
	17.0600	4.99	3.00	37.00	14.97	87.75			
265	0.0376	4.99	0.00	76.00			87.01	21.50	3.79
	1.7860	4.99	0.30	77.90	1.50	83.82			
	4.4500	4.99	0.75	22.90	3.74	84.10			
	8.4800	4.99	1.50	33.70	7.49	88.27			
	12.6400	4.99	2.25	36.60	11.23	88.83			
	17.2400	4.99	3.00	38.80	14.97	86.83			

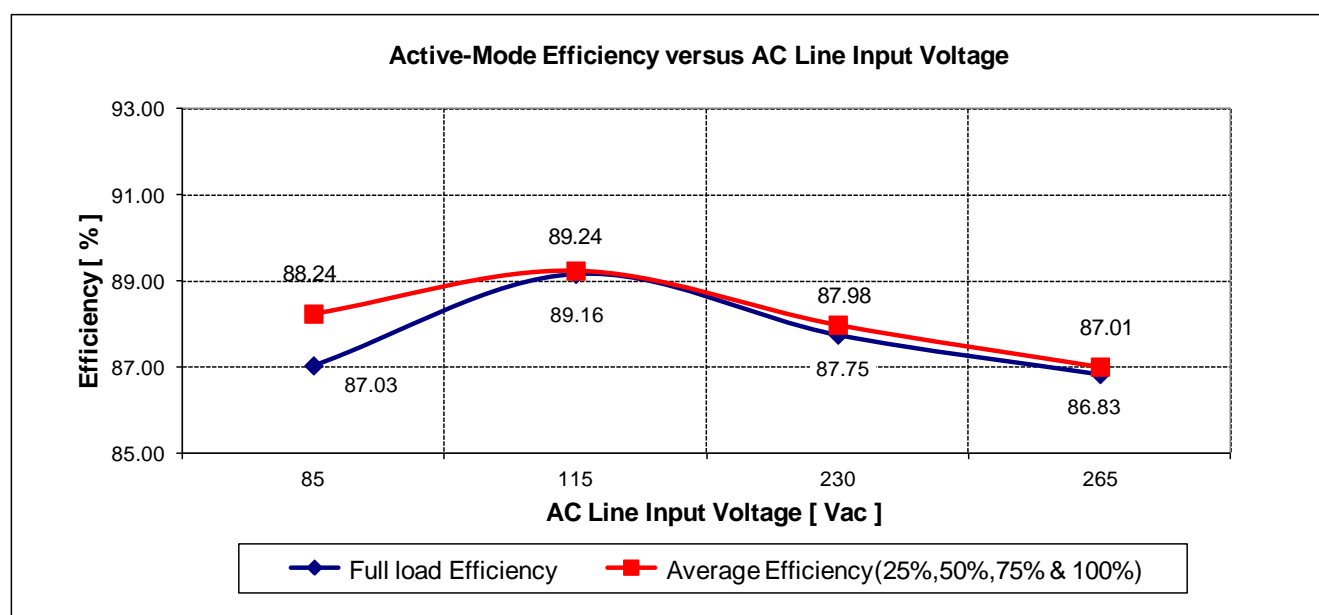


**Figure 7** – Efficiency vs AC line input voltage



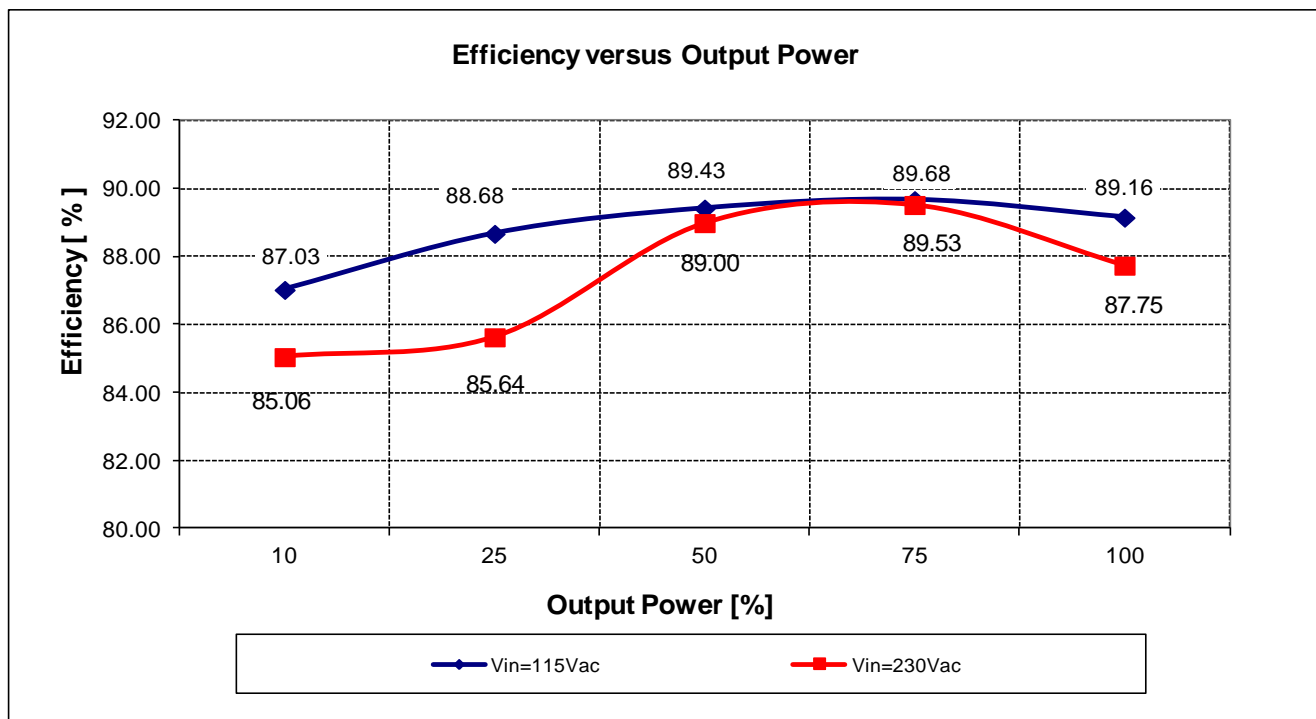


**Figure 8** – Efficiency vs output power @ 115Vac and 230V line

## 12.2 Input standby power

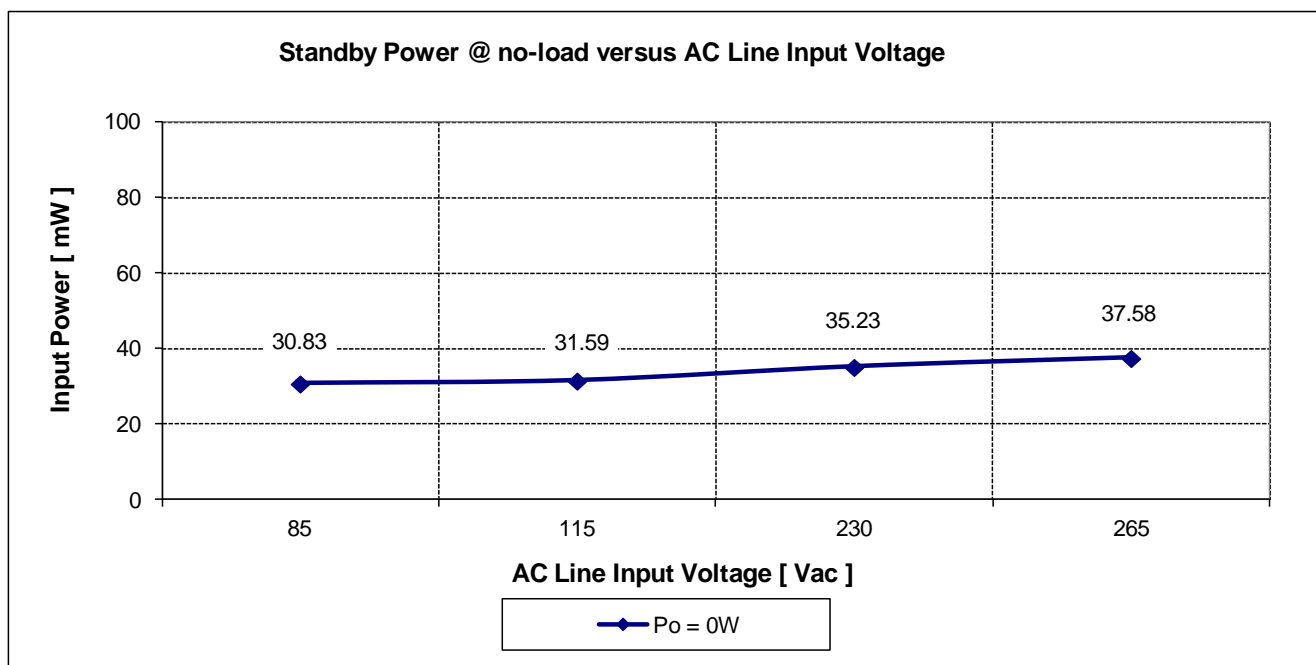


**Figure 9** – Input standby power @ no load vs AC line input voltage (measured by Yokogawa WT210 power meter - integration mode)

### 12.3 Line regulation

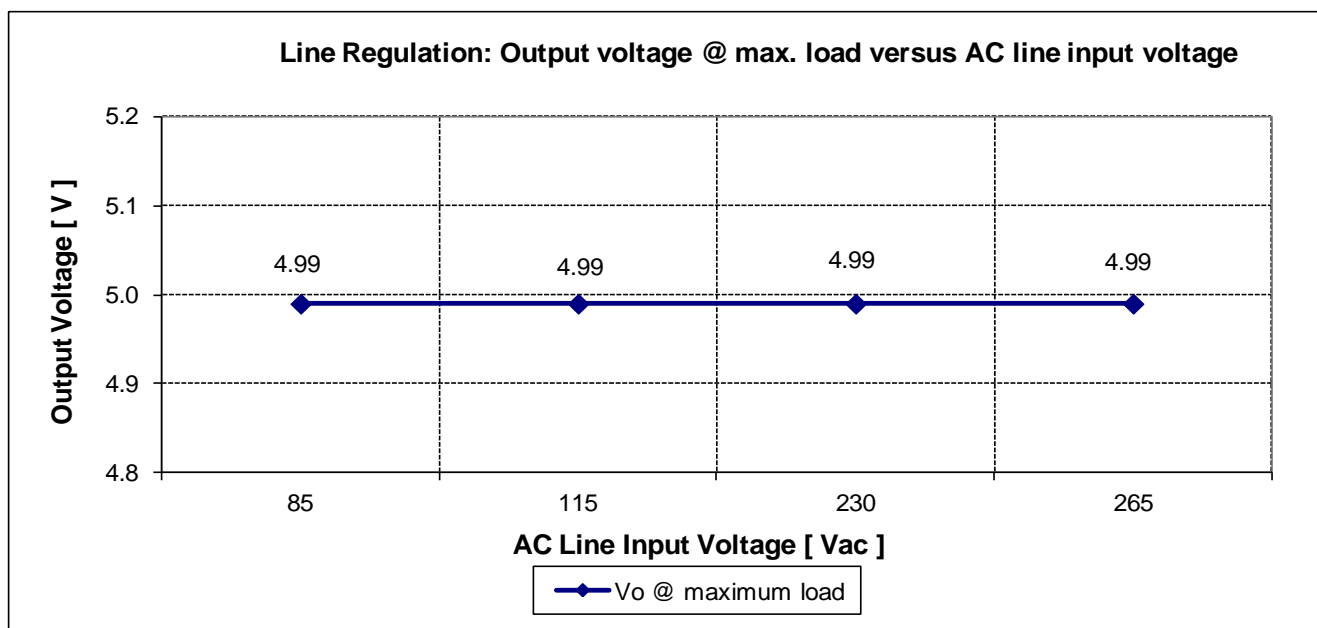

**Figure 10** – Line regulation Vo @ full load vs AC line input voltage

### 12.4 Load regulation

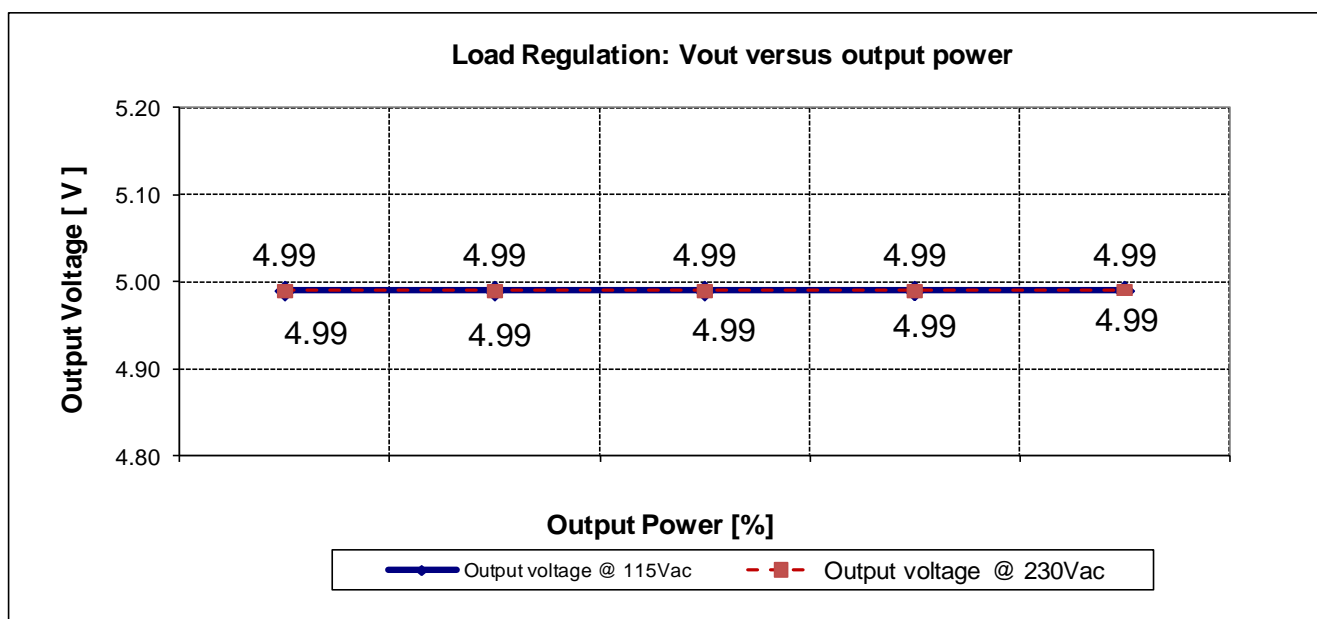

**Figure 11** – Load regulation Vo vs output power

## 12.5 Maximum power

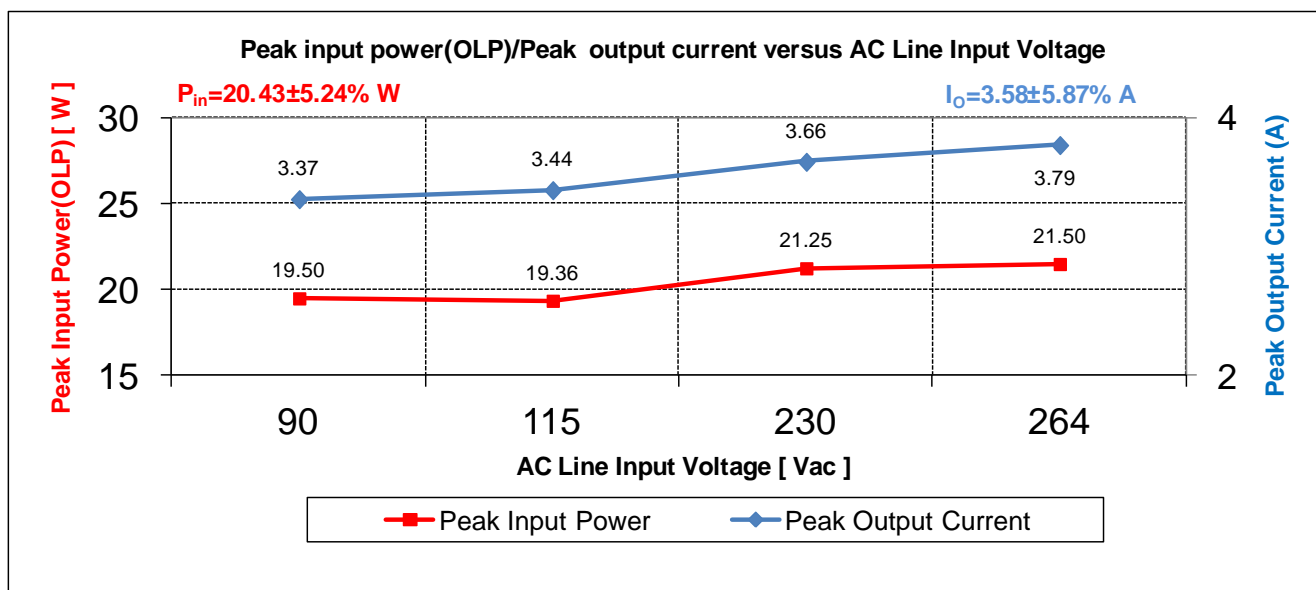


Figure 12 – Maximum input power (before over-load protection) vs AC line input voltage

## 12.6 ESD immunity (EN61000-4-2)

Pass EN61000-4-2 level 3 ( $\pm 6\text{kV}$ ) contact discharge

## 12.7 Surge immunity (EN61000-4-5)

Pass EN61000-4-5 Installation class 3 (2kV: common mode)

## 12.8 Conducted emissions (EN55022 class B)

The conducted EMI was measured by Schaffner (SMR25503) and followed the test standard of EN55022 (CISPR 22) class B. The demo board was set up at maximum load (15W) with input voltage of 115Vac and 230Vac.

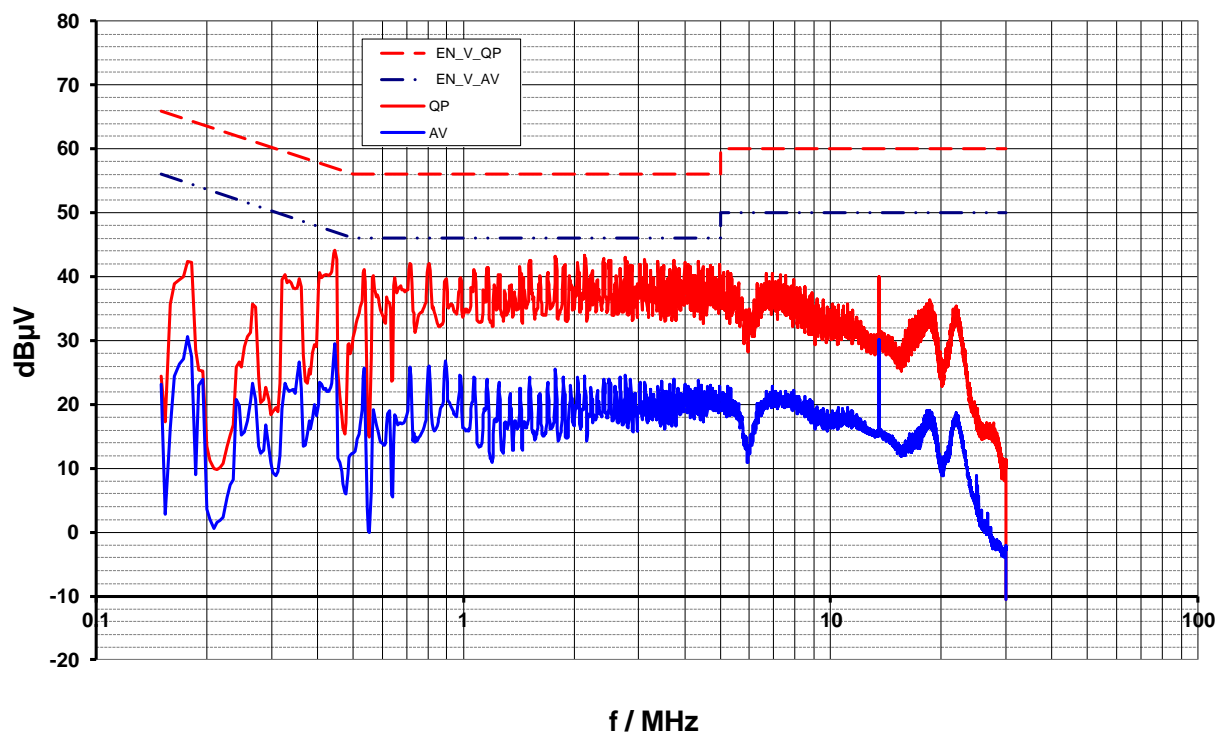


Figure 13 – Max. Load (15W) with 115 Vac (Line)



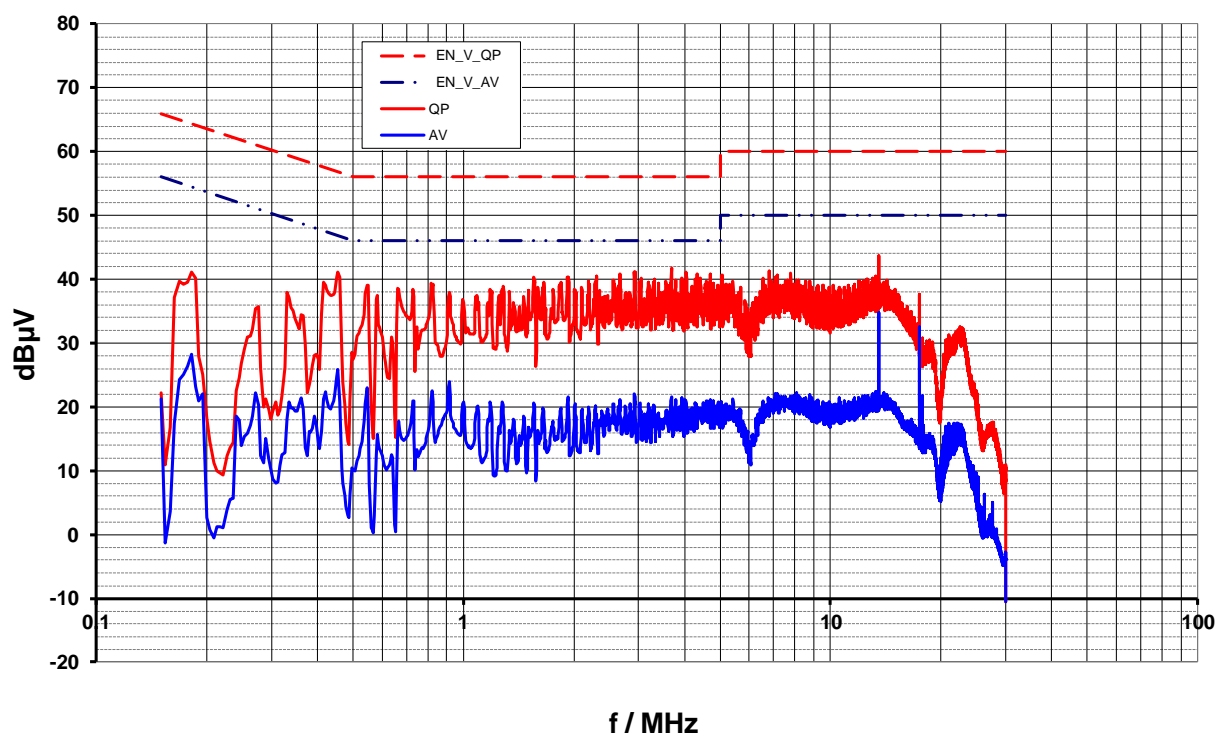


Figure 14 – Max. Load (15W) with 115 Vac (Neutral)

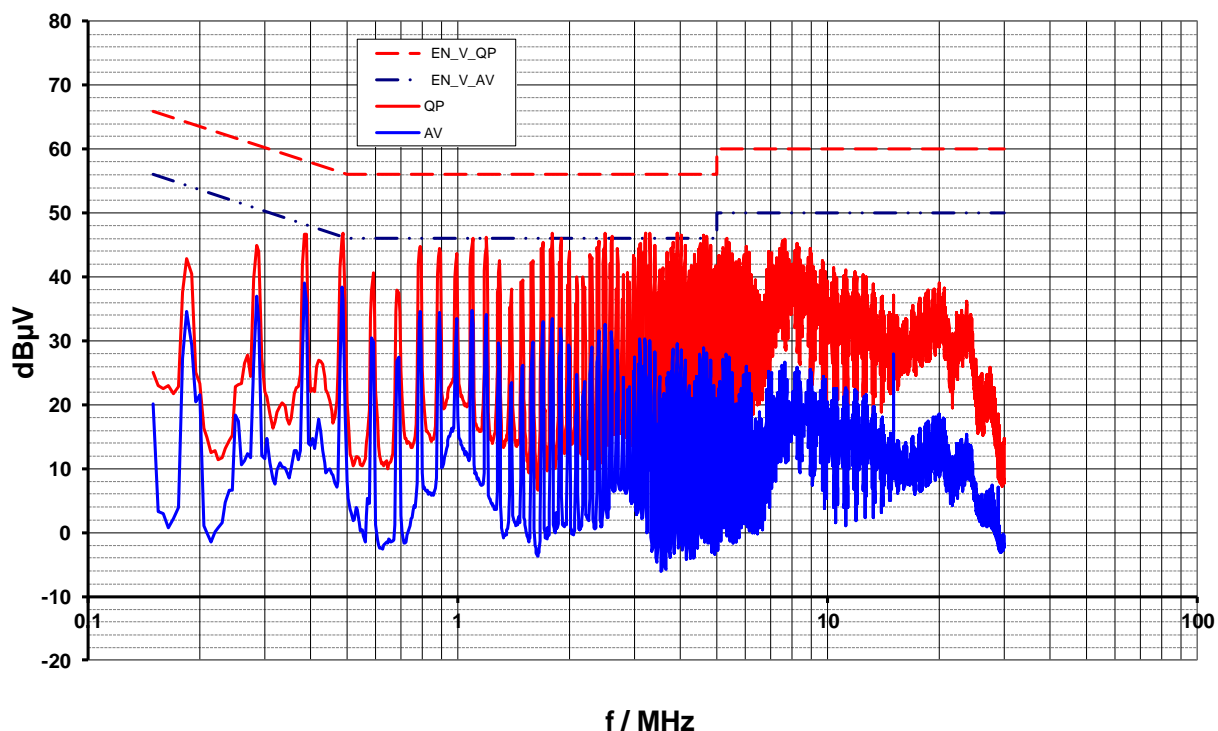

**Figure 15** – Max. Load (15W) with 230 Vac (Line)

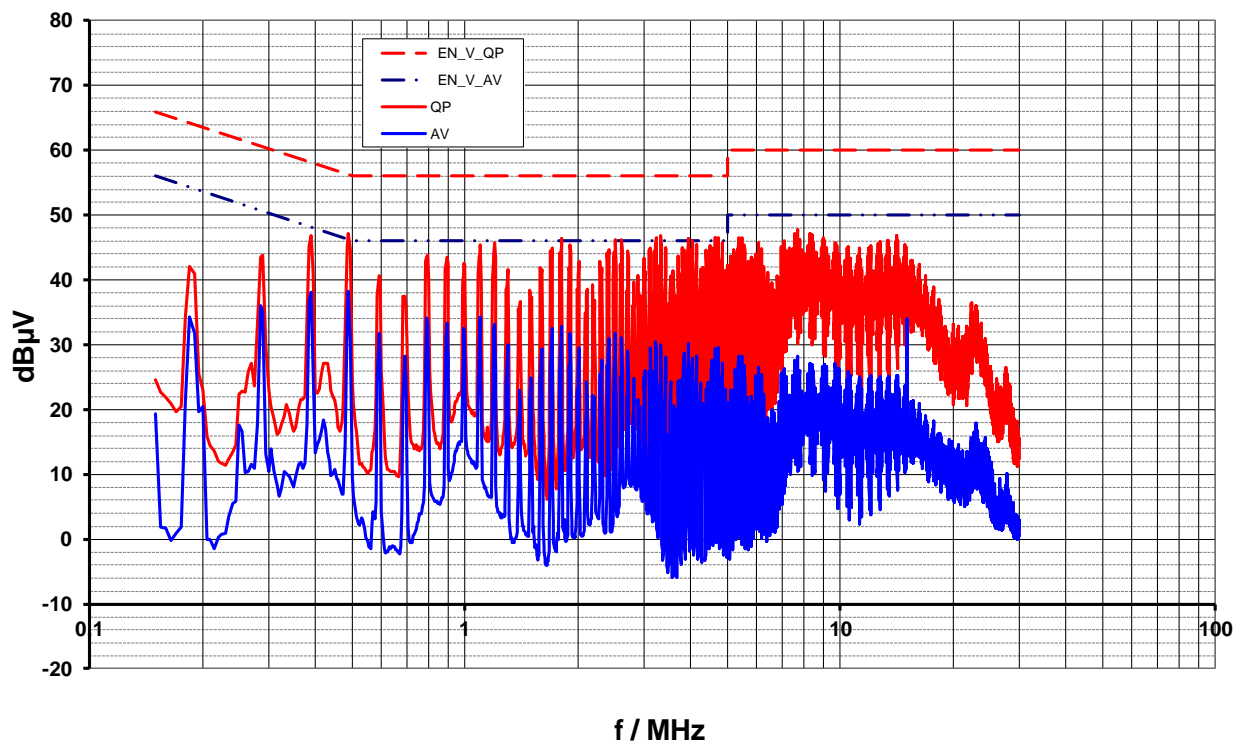


**Figure 16** – Max. Load (15W) with 230 Vac (Neutral)

Pass conducted EMI EN55022 (CISPR 22) class B with > 9dB margin for QP.

## 12.9 Thermal measurement

The reference adapter's thermal test was done on key components inside a dummy adapter plastic case which is covered by the transparent box (W x L x H: 17mm x 17mm x 23mm). The measurements were taken with thermocouple data logger (GL220 & 87V) after two hours running with full load (15W).

	Major component	85Vac (°C)	115Vac (°C)	230Vac (°C)	265Vac (°C)
1	Q11 (IPU60R950C6)	93.8	81.5	91.8	100.8
2	Q21 (BSC067N06LS3G)	80.0	72.3	82.5	87.6
3	IC22 (SR IC)	76.1	69.2	76.7	81.2
4	TR1 (Transformer)	78.0	70.4	75.2	79.0
5	IC11 (ICE2QS03G)	68.9	62.0	62.8	65.1
6	BR1 (bridge diode)	67.9	58.4	53.1	53.8
7	Case Bottom (PCB bottom side)	50.5	46.4	48.4	50.2
8	Case Top (PCB component side)	49.5	45.8	46.8	49.0
9	Ambient (1cm above EUT)	30.1	30.0	29.9	30.3

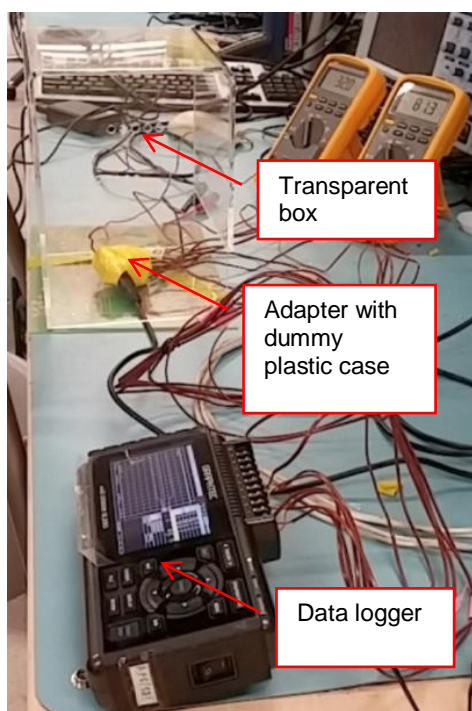


**Figure 17** – Thermal measurement setup

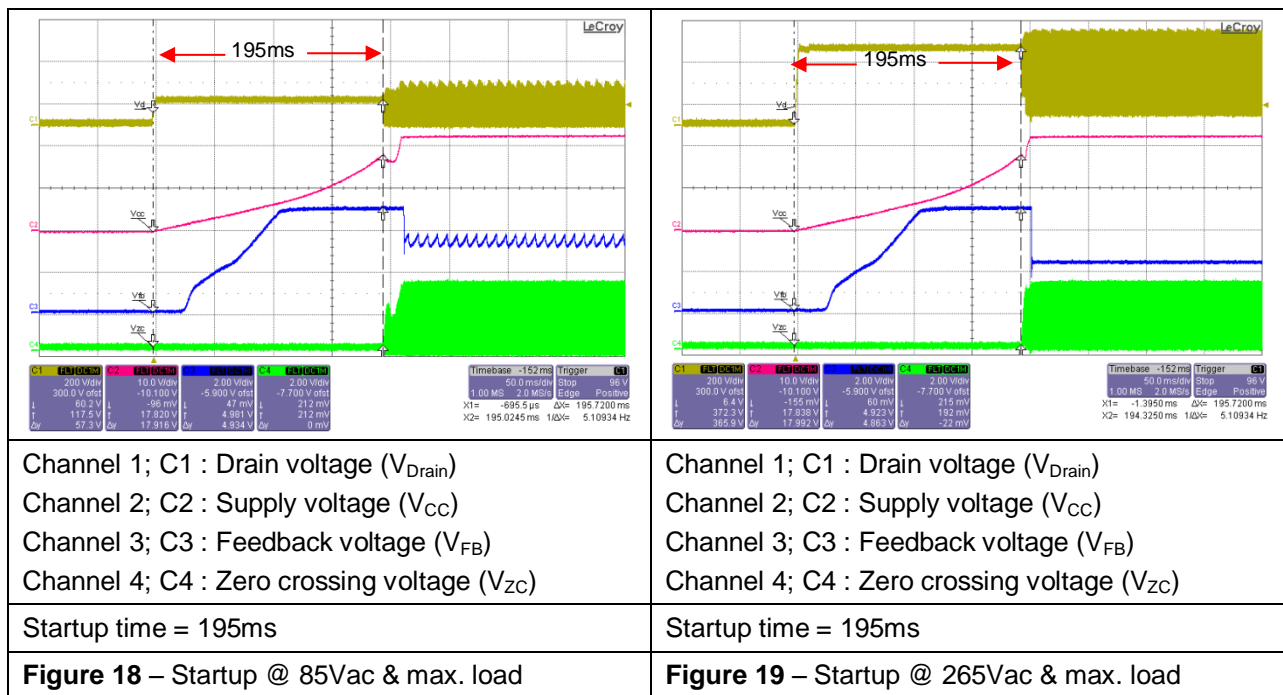
## 13 Waveforms and scope plots

All waveforms and scope plots were recorded with a LeCroy 6050 oscilloscope


### 13.1 Start up at low/high AC line input voltage with maximum load




### 13.2 Soft start

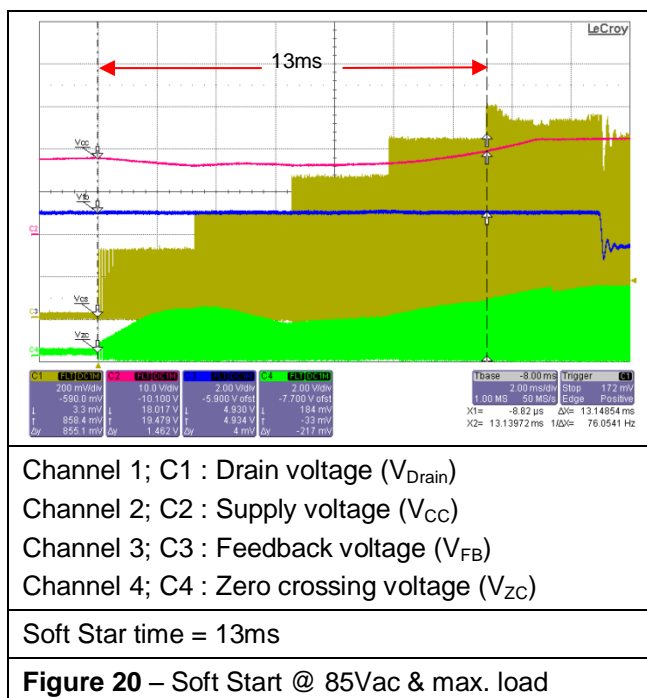
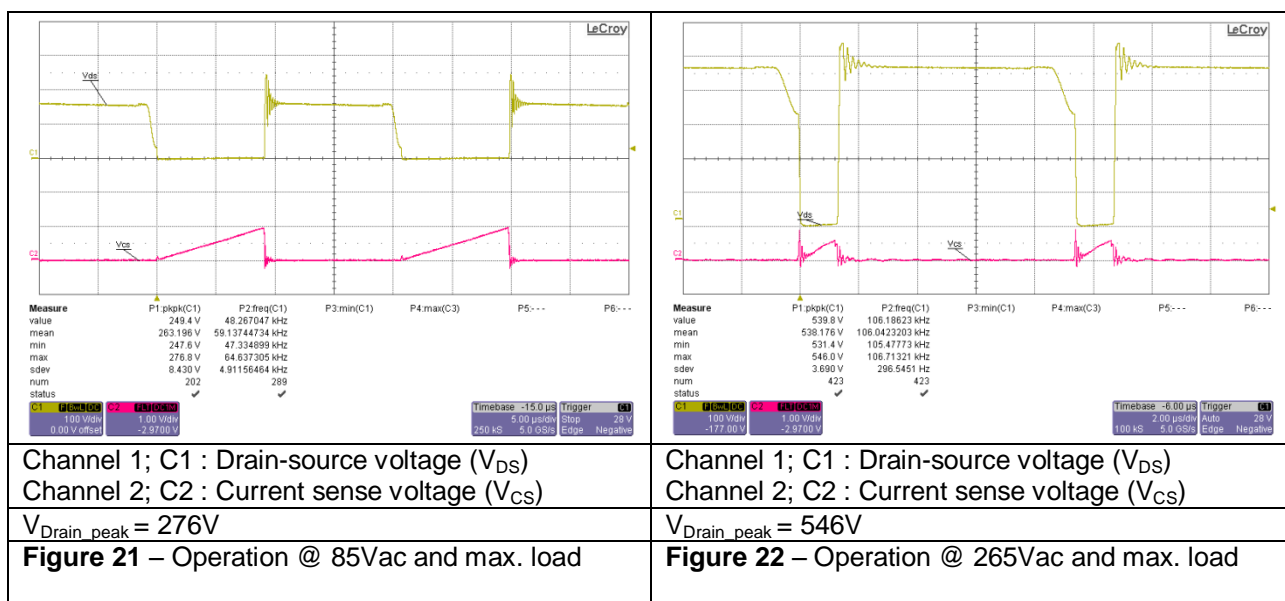
### 13.3 Drain voltage and current at maximum load



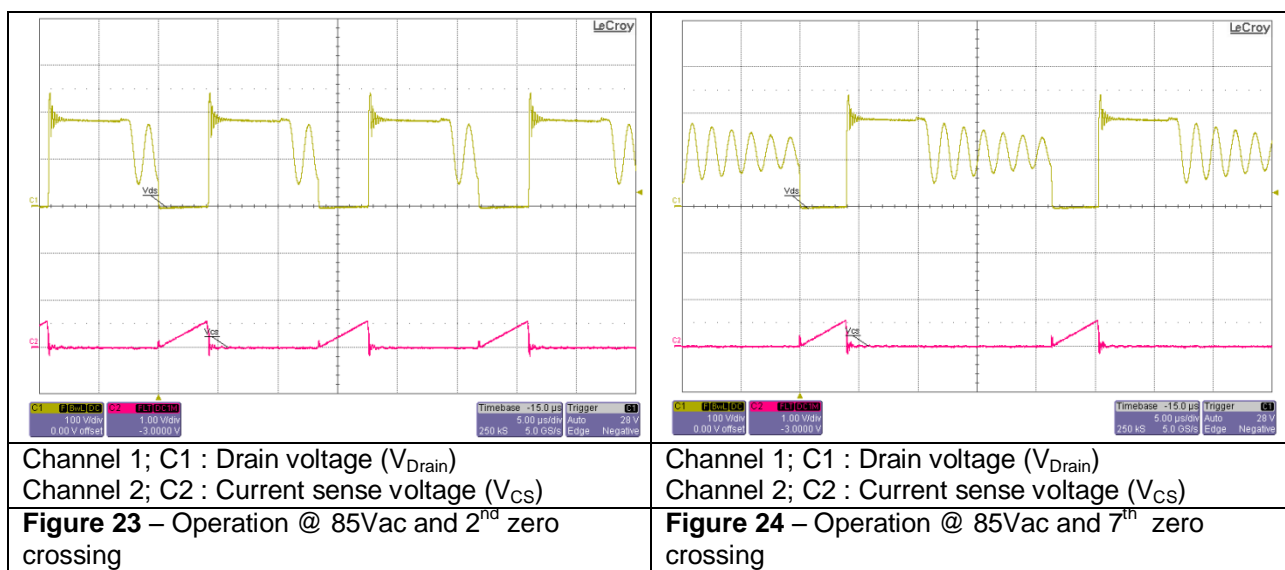
### 13.4 Zero crossing point during normal operation







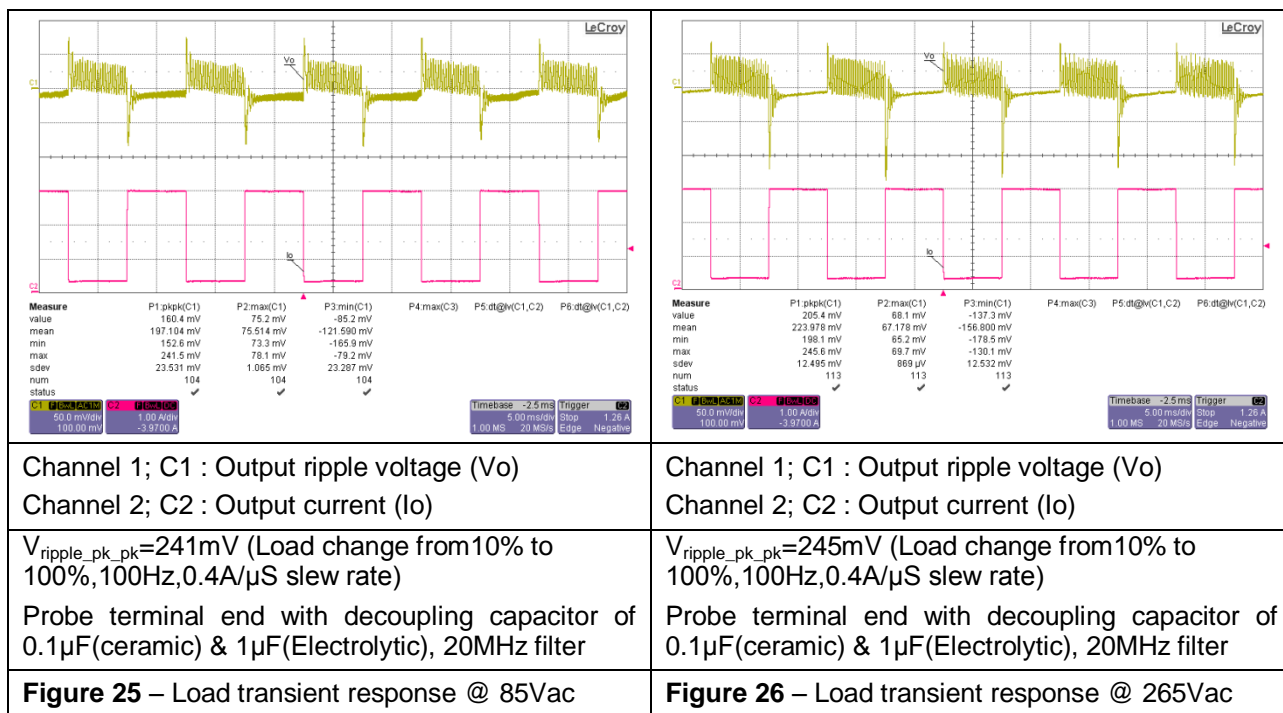
### 13.5 Load transient response (Dynamic load from 10% to 100%)



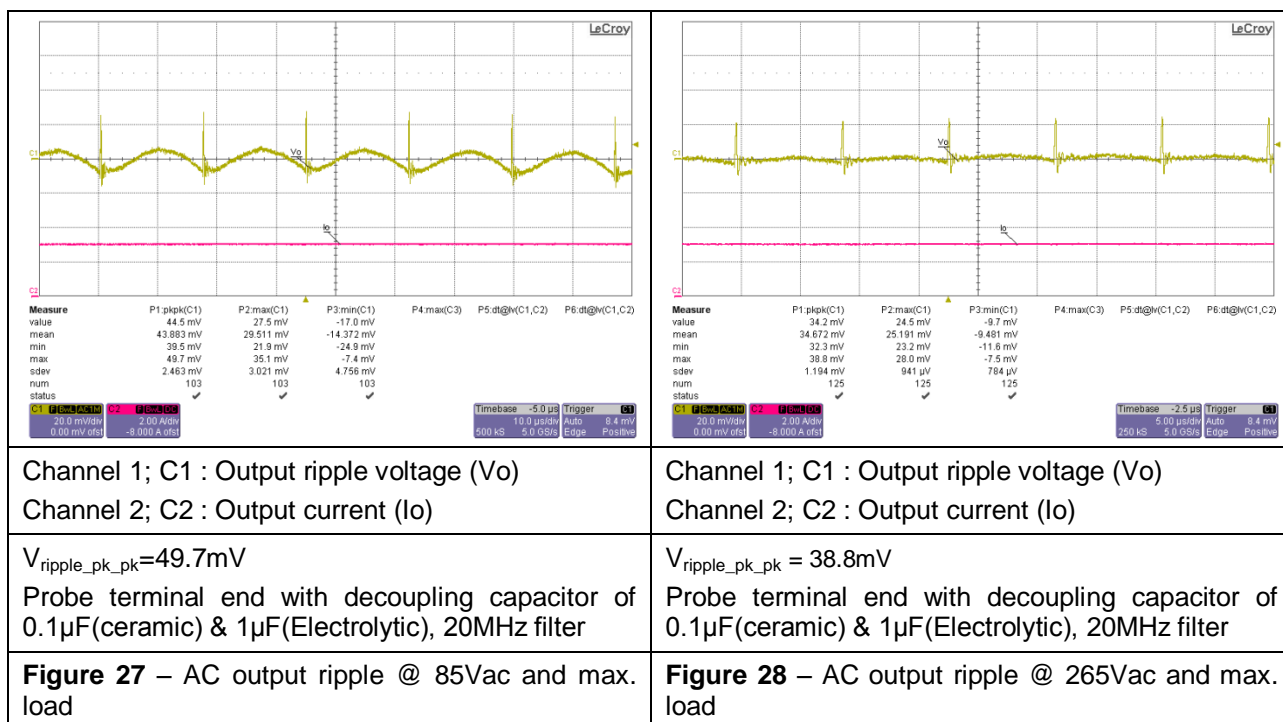
### 13.6 Output ripple voltage at maximum load



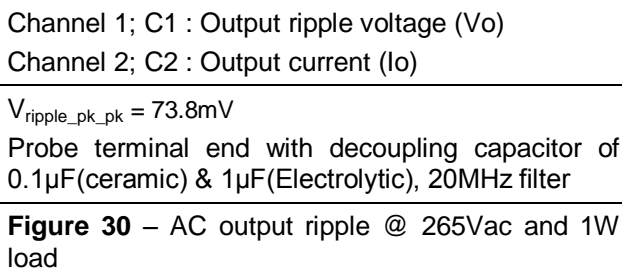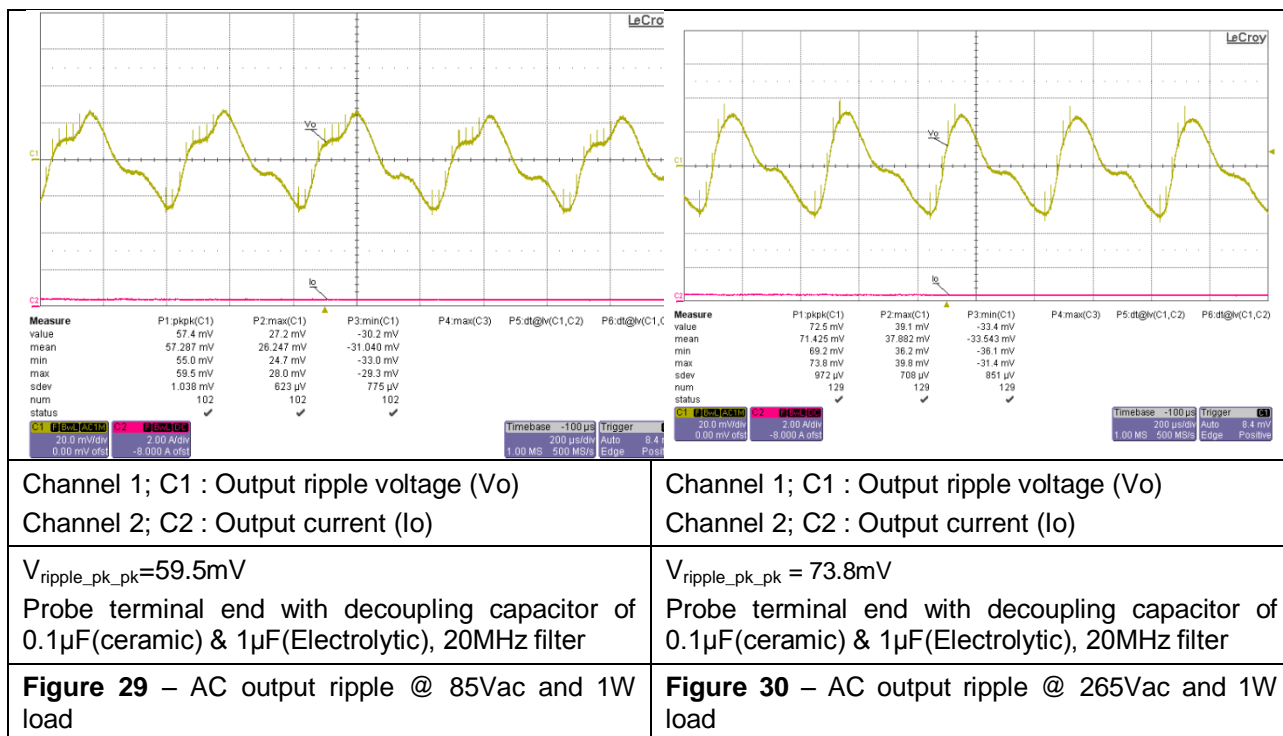
### 13.7 Output ripple voltage during burst mode at 1 W load




### 13.8 Active Burst mode operation

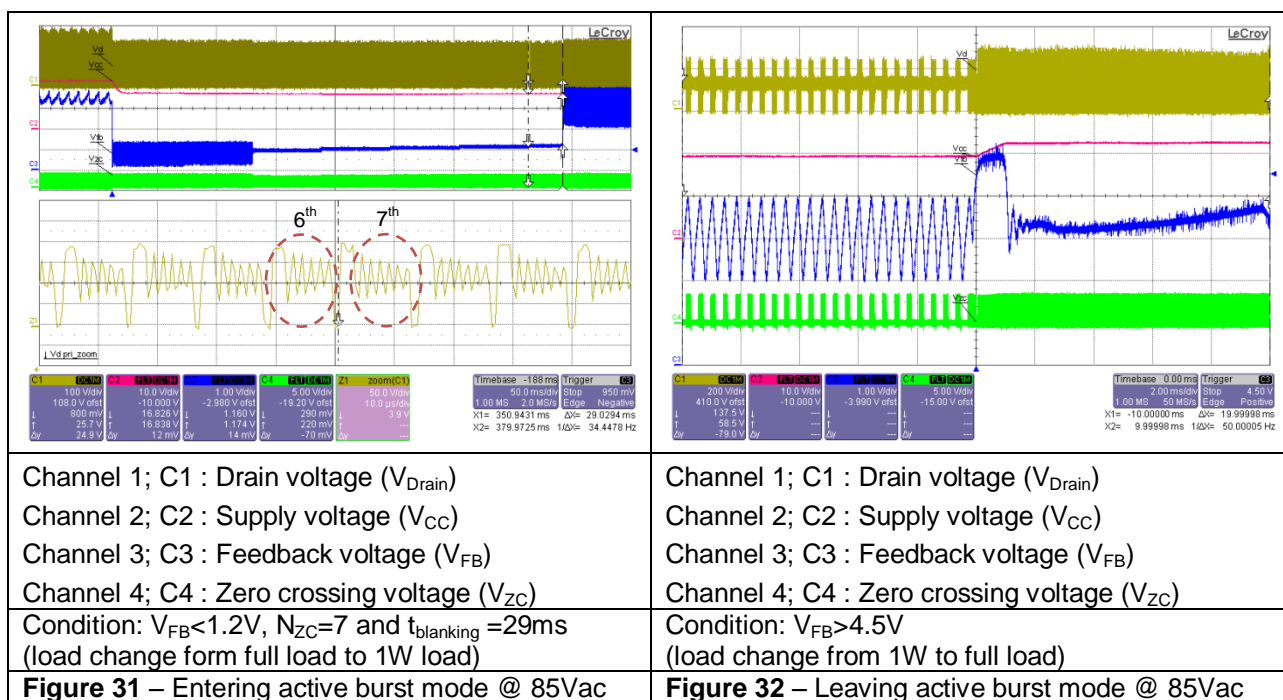

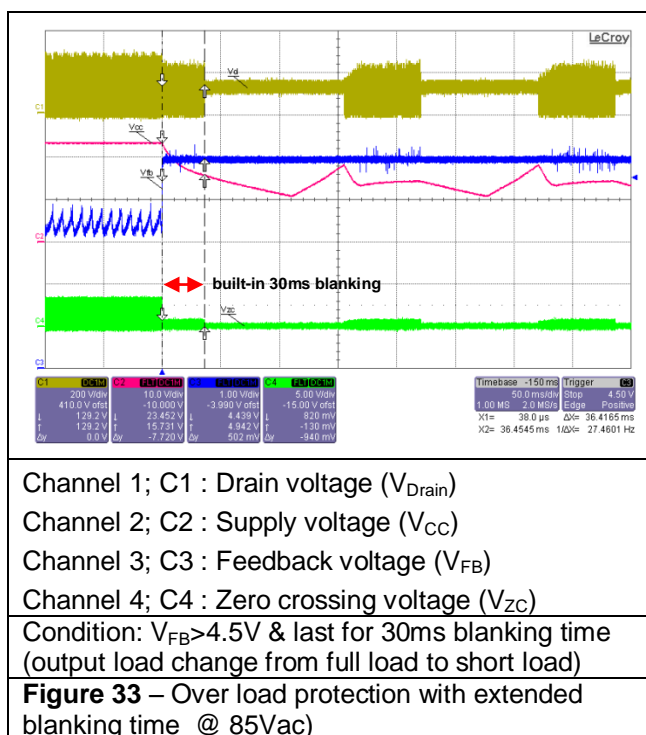
### 13.9 Over load protection (Auto restart mode)


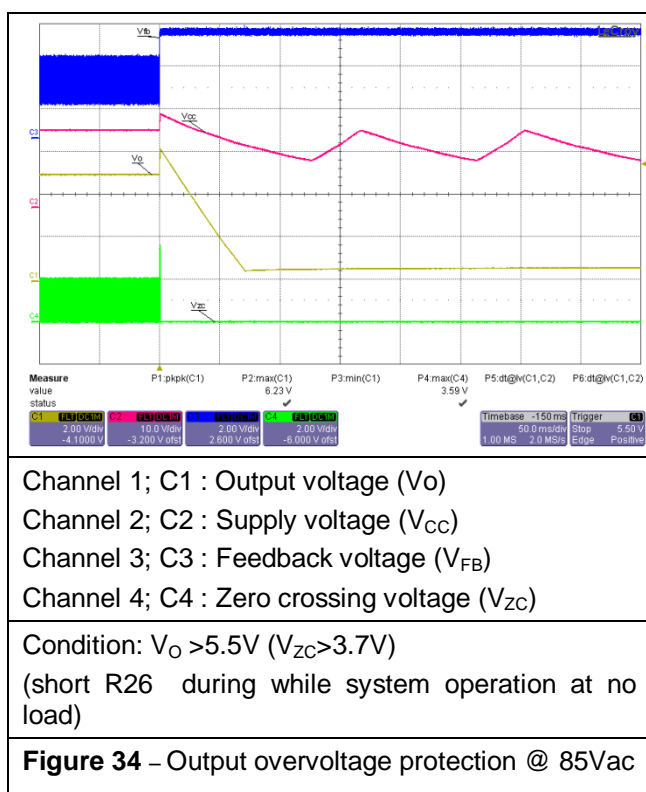
### 13.10 Output overvoltage protection (Latched off mode)


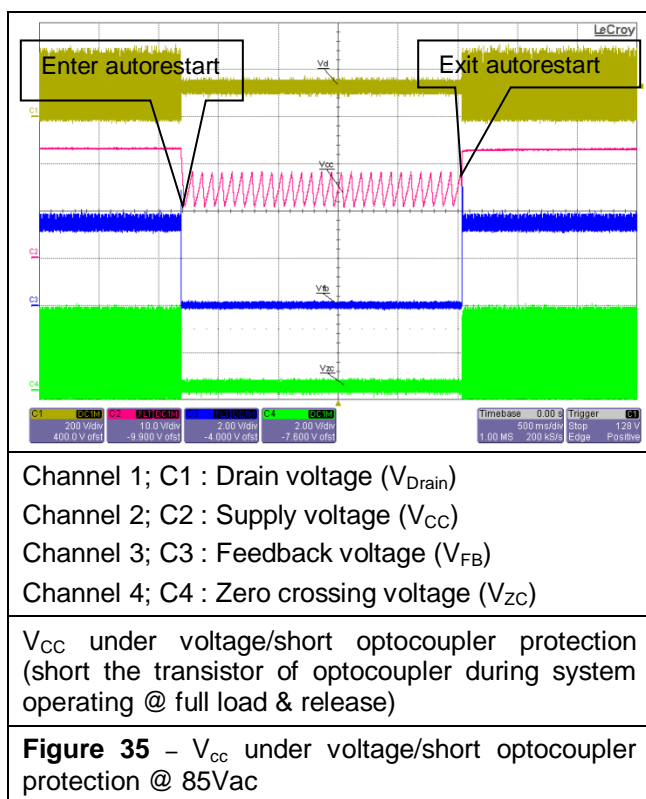
### 13.11 $V_{CC}$ under voltage/Short optocoupler protection (Auto restart mode)



## 14 References

- [1] ICE2QS03G data sheet, Infineon Technologies AG
- [2] IPU60R950C6 data sheet, 600V CoolMOS™ C6 Power Transistor, Infineon Technologies AG
- [3] BSC067N06LS3 G data sheet, 60V OptiMOS™ 3 Power Transistor, Infineon Technologies AG
- [4] BAS21-03W data sheet, Infineon Technologies AG
- [5] Converter Design Using the Quasi-Resonant PWM Controller ICE2QS01, Infineon Technologies AG, 2006. [ANPS0003]
- [6] Design tips for flyback converters using the Quasi-Resonant PWM controller ICE2QS01, Infineon Technologies, 2006. [ANPS0005]
- [7] Determine the switching frequency of Quasi-Resonant flyback converters designed with ICE2QS01, Infineon Technologies, 2006. [ANPS0004]
- [8] ICE2QS03G design guide. [ANPS0027]
- [9] 36W Evaluation Board with Quasi-Resonant PWM Controller ICE2QS03G, 2011. [AN-PS0040]

[www.infineon.com](http://www.infineon.com)