

12 W auxiliary SMPS for energy-efficient refrigerator using ICE5QR2270AZ

REF_5QR2270AZ_12W1

About this document

Scope and purpose

This document is a reference design for a 12 W auxiliary SMPS for a refrigerator with the latest fifth-generation Infineon QR CoolSET™ [ICE5QR2270AZ](#). The power supply is designed with a universal input compatible with most geographic regions and isolated output (+12 V/1 A) on a single-layer PCB, as typically employed in most home appliances.

Highlights of the auxiliary power supply for a refrigerator:

- High efficiency under light and heavy load conditions to meet ENERGY STAR requirements
- Simplified circuitry with good integration of power and protection features
- Single-layer PCB design for compatibility with wave-soldering process and low-cost manufacturing
- Auto-restart protection scheme to minimize interruption to enhance end-user experience

Intended audience

This document is intended for power supply design or application engineers, etc. who want to design auxiliary power supplies for refrigerators that are efficient under light and heavy load conditions, reliable and easy to design.

Table of contents

| | |
|---|----------|
| About this document..... | 1 |
| Table of contents..... | 1 |
| 1 System introduction..... | 3 |
| 1.1 High efficiency under light and heavy load conditions to meet ENERGY STAR requirements..... | 4 |
| 1.2 Simplified circuitry with good integration of power and protection features..... | 4 |
| 1.3 Auto-restart protection scheme to minimize interruption to enhance end-user experience..... | 4 |
| 2 Reference design board | 5 |
| 3 Power supply specifications | 6 |
| 4 Circuit diagram | 7 |
| 5 Circuit description..... | 8 |
| 5.1 EMI filtering and line rectification..... | 8 |
| 5.2 Flyback converter power stage..... | 8 |
| 5.3 Control of Flyback converter through fifth-generation QR CoolSET™ ICE5QR2270AZ..... | 8 |
| 5.3.1 Integrated HV power MOSFET | 8 |
| 5.3.2 Fast self-start-up and sustaining of V _{CC} | 8 |
| 5.3.3 QR switching with valley sensing..... | 9 |
| 5.3.4 Current Sensing (CS) | 9 |
| 5.3.5 Feedback (FB) and compensation network | 9 |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Table of contents

| | | |
|-----------|--|-----------|
| 5.3.6 | System robustness and reliability through protection features | 9 |
| 5.4 | Clamper circuit | 10 |
| 5.5 | PCB design tips | 10 |
| 5.6 | EMI reduction tips | 11 |
| 6 | PCB layout..... | 12 |
| 6.1 | Top side | 12 |
| 6.2 | Bottom side | 12 |
| 7 | BOM..... | 13 |
| 8 | Transformer specification | 15 |
| 9 | Measurement data and graphs..... | 16 |
| 9.1 | Efficiency curve..... | 18 |
| 9.2 | Standby power | 19 |
| 9.3 | Line and load regulation | 19 |
| 9.4 | Maximum input power | 20 |
| 9.5 | Switching frequency through digital frequency reduction | 20 |
| 9.6 | ESD immunity (EN 61000-4-2) | 21 |
| 9.7 | Surge immunity (EN 61000-4-5) | 21 |
| 9.8 | Conducted emissions (EN 55022 class B) | 22 |
| 9.9 | Thermal measurement | 24 |
| 10 | Waveforms and oscilloscope plots..... | 25 |
| 10.1 | Start-up at full load | 25 |
| 10.2 | Soft-start at full load | 25 |
| 10.3 | Drain and CS voltage at full load | 26 |
| 10.4 | Output ripple voltage at full load | 26 |
| 10.5 | Output ripple voltage at ABM (100 mA load) | 27 |
| 10.6 | Load transient response (dynamic load from 10 percent to 100 percent)..... | 27 |
| 10.7 | Entering ABM | 28 |
| 10.8 | During ABM | 28 |
| 10.9 | Leaving ABM | 29 |
| 10.10 | Over-load protection..... | 29 |
| 10.11 | Output over-voltage protection..... | 30 |
| 10.12 | Brown-in/brown-out protection..... | 30 |
| 10.13 | Input line OVP | 31 |
| 11 | Appendix A: Transformer design and spreadsheet [3] | 32 |
| 12 | Appendix B: WE transformer specification | 39 |
| 13 | References | 40 |
| | Revision history..... | 41 |

1 System introduction

With the growing household trend for internet-connected devices, the new generation of home appliances such as refrigerators are equipped with advanced features which often include communication capability, such as wireless communication, touch screen display and sensors. These will transform a static product into an interactive and intelligent home appliance, capable of adapting to the smart-home theme. To support this trend, Infineon has introduced the latest fifth-generation QR CoolSET™ to address this need in an efficient and cost-effective manner.

An auxiliary SMPS is needed to power the various modules and sensors, which typically operate from a stable DC voltage source. The Infineon CoolSET™ (as shown in Figure 1) forms the heart of the system, providing the necessary protection and AC-DC conversion from the mains to multiple regulated DC voltages to power the various blocks.

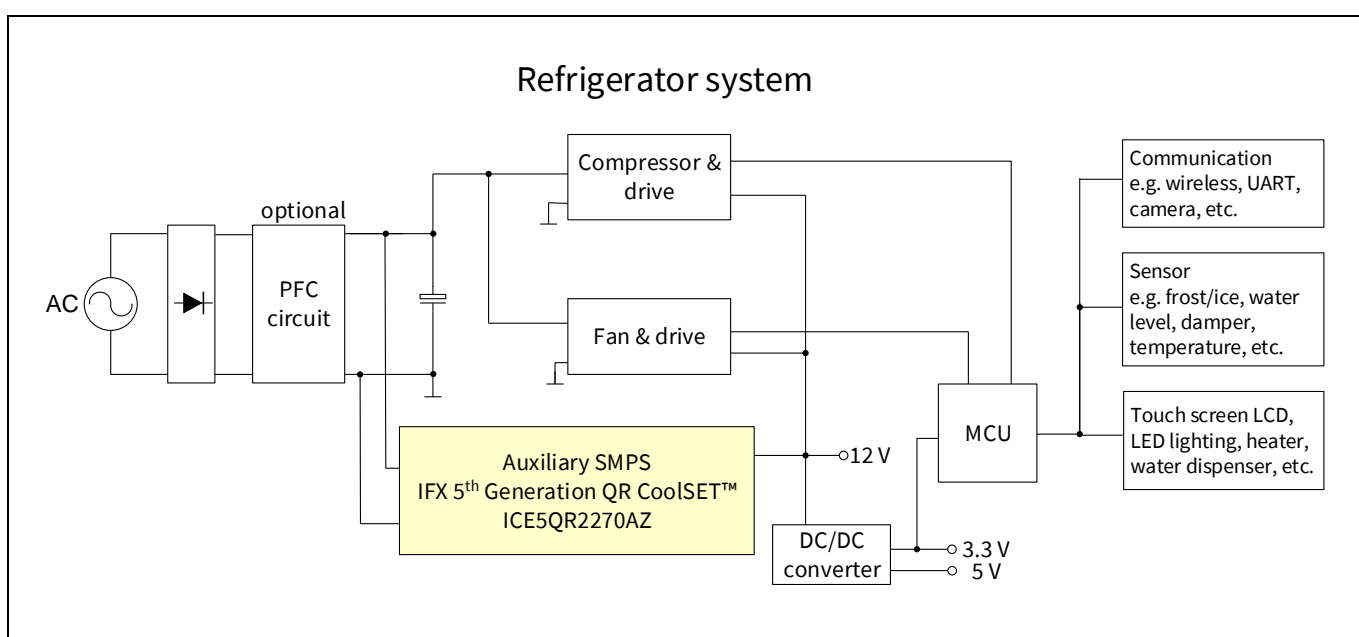


Figure 1 Simplified refrigerator system block diagram

Table 1 lists the system requirements for a refrigerator, and the corresponding Infineon solution is shown in the right-hand column.

Table 1 System requirements and Infineon solutions

| | System requirement for a refrigerator | Infineon solution – ICE5QR2270AZ |
|---|--|---|
| 1 | High efficiency under light and heavy load conditions to meet ENERGY STAR requirements | New QR control and Active Burst Mode (ABM) |
| 2 | Simplified circuitry with good integration of power and protection features | Embedded 700 V MOSFET and controller in DIP-7 package |
| 3 | Auto-restart protection scheme to minimize interruption to enhance end-user experience | All protections are in auto-restart |

1.1 High efficiency under light and heavy load conditions to meet ENERGY STAR requirements

During typical refrigerator operation, the power requirement fluctuates according to various use cases. However, in most cases, the refrigerator will reside in an idle state in which the loading toward the auxiliary power supply is low. It is crucial that the auxiliary power supply operates as efficiently as possible, because it will be in this particular state for a prolonged period. Under light load conditions, losses incurred with the power switch are usually dominated by the switching operation. The choice of switching scheme and frequency play a crucial role in ensuring high conversion efficiency.

In this reference design, ICE5QR2270AZ was primarily chosen due to its QR switching scheme. Compared with a traditional Flyback switching scheme, the CoolSET™ will attempt to turn on its integrated HV MOSFET in the valley of the resonant period, thereby minimizing switching losses. Additionally, the fifth-generation QR series has the highest detection rate in the industry, of up to 10 valleys, thereby lowering the switching frequency further along with a reduction in load. Therefore, an efficiency of more than 80 percent is achievable under 10 percent loading conditions.

1.2 Simplified circuitry with good integration of power and protection features

To relieve the designer of the complexity of PCB layout and circuit design, this CoolSET™ is a highly integrated device with both a controller and an HV MOSFET integrated into a single, space-saving DIP-7 package. These certainly help the designer to reduce component count as well as simplifying the layout into a single-layer PCB design for ease of manufacturing, using the traditional, cost-effective wave-soldering process.

To counter abnormal line-input conditions, CoolSET™ has integrated line-input Over-Voltage Protection (OVP) as well as brown-in/brown-out protection to increase the robustness of the auxiliary power supply. In the event of such faults, the controller within the CoolSET™ will halt the switching operation of the integrated HV MOSFET, thereby preventing permanent damage. These features allow the designer to reduce the complexity of introducing additional external circuitry and yield a saving of as many as 15 components.

Additional protection features are integrated into the CoolSET™, such as output OV, V_{CC} OV, V_{CC} Under Voltage (UV), over-load/open-loop, over-temperature and Current Sense (CS) short-to-GND. It also has limited charging current for V_{CC} short-to-GND.

1.3 Auto-restart protection scheme to minimize interruption to enhance end-user experience

For a refrigerator it would be annoying to both the end user and the manufacturer if the system were to halt and latch after protection. To minimize interruption, the CoolSET™ implements auto-restart mode for all protections.

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Reference design board



2 Reference design board

This document provides complete design details including specifications, schematics, Bill of Materials (BOM), PCB layout, and transformer design and construction information. Performance results pertaining to line/load regulation, efficiency, transient load, thermal conditions, conducted EMI scans and so on are also included.

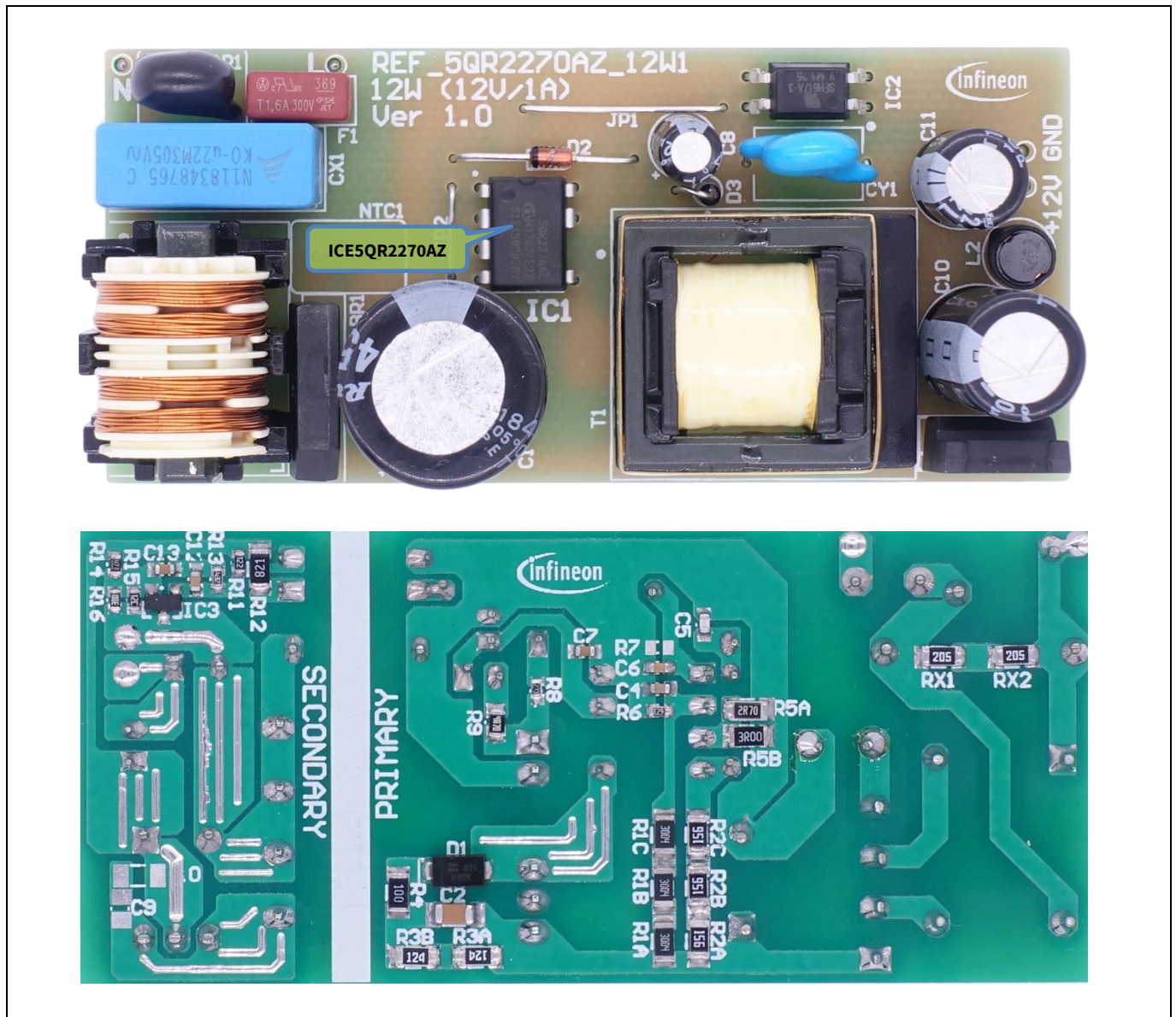


Figure 2 REF_5QR2270AZ_12W1 top and bottom

Power supply specifications

3 Power supply specifications

The table below shows the minimum acceptable performance of the design at 25°C ambient temperature. Actual performance is listed in the measurements section.

Table 2 Specifications of REF_5QR2270AZ_12W1

| Description | Symbol | Min. | Typ. | Max. | Units | Comments |
|---|-----------------------|--------------|-------|------|-----------------|--|
| Input | | | | | | |
| Voltage | V _{IN} | 85 | – | 264 | V AC | Two-wire (no P.E.) |
| Frequency | f _{LINE} | 47 | 50/60 | 64 | Hz | |
| No-load input power | P _{stby_NL} | – | – | 75 | mW | 220 V AC |
| Output | | | | | | |
| Output voltage | V _{OUT} | – | 12 | – | V | ± 1 percent |
| Output current | I _{OUT} | – | – | 1 | A | |
| Output power | P _{OUT_Nom} | – | – | 12 | W | 20 MHz bandwidth |
| Output voltage ripple | V _{RIPPLE} | – | – | 100 | mV | |
| Output over-current protection | I _{OCP} | – | 1.4 | – | A | |
| Start-up time | t _{start_up} | – | – | 250 | ms | |
| Efficiency | | | | | | |
| Maximum power | η | 89 | – | – | % | 115 V AC/220 V AC |
| Average efficiency (25 percent, 50 percent, 75 percent and 100 percent) | η _{avg} | 88 | – | – | % | |
| 10 percent load efficiency | η _{10%} | 80 | – | – | % | |
| | | | | | | |
| Environmental | | | | | | |
| Conducted EMI | | 6 | | | dB | Margin, CISPR 22 class B EN 61000-4-2 EN 61000-4-5 |
| ESD | | ±8 | | | kV | |
| Surge immunity | | | | | | |
| Differential Mode (DM) | | ± 2 | | | kV | |
| Common Mode (CM) | | ± 4 | | | kV | |
| Ambient temperature | T _{amb} | 0 | – | 50 | °C | Free convection, sea level |
| Form factor | | 80 × 36 × 30 | | | mm ³ | L × W × H |

4 Circuit diagram

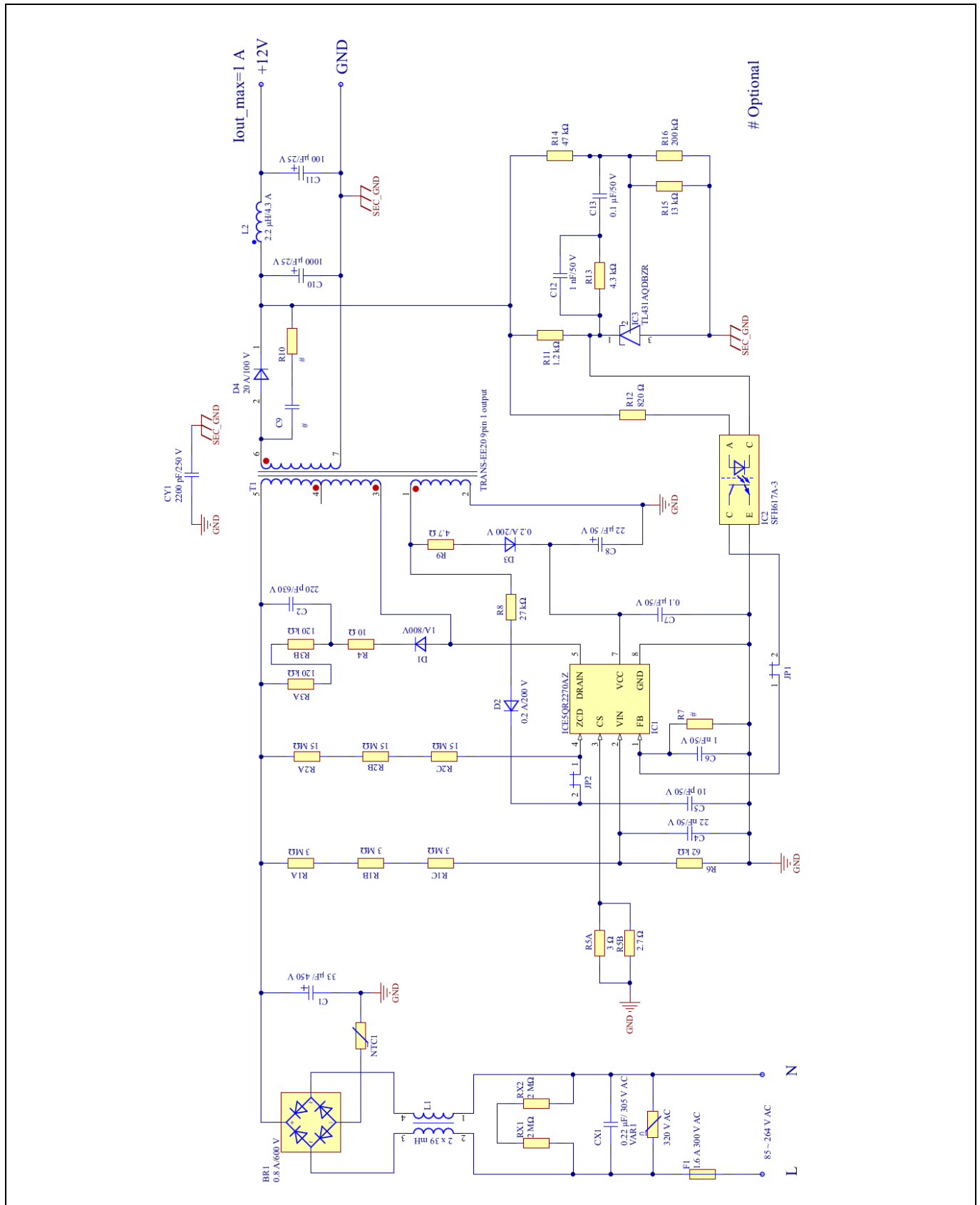


Figure 3 Schematic diagram of REF_5QR2270AZ_12W1

5 Circuit description

In this section, the reference design circuit for refrigerator auxiliary power supply will be briefly described by the different functional blocks. For details of the design procedure and component selection for the Flyback circuitry, please refer to the IC design guide [2] and calculation tool [3].

5.1 EMI filtering and line rectification

The input of the refrigerator auxiliary power unit is taken from the AC power grid, which is in the range of 85 V AC ~ 264 V AC. The fuse F1 is directly connected to the input line to protect the system in case of excess current entering the system circuit due to any fault. Following is the varistor VAR1, which is connected across L and N to absorb the line surge transient. CM choke L1 and X-capacitor CX1 are filters to attenuate the DM and CM conducted EMI noise. Resistors RX1 and RX2 are used to discharge the X-capacitor when the AC is off in order to fulfill the IEC61010-1 and UL1950 safety requirement. The bridge rectifier BR1 rectifies the AC input into DC voltage, filtered by the bulk capacitor C1.

5.2 Flyback converter power stage

The Flyback converter power stage consists of transformer T1, a primary HV MOSFET (integrated into ICE5QR2270AZ), secondary rectification diode D4 and secondary output capacitors and filtering (C10, L2 and C11).

When the integrated HV MOSFET turns on, energy is stored in the transformer. When it turns off, the stored energy is discharged to the output capacitors and into the output load.

Secondary winding is sandwiched between two layers of primary winding to reduce leakage inductance. This improves efficiency and reduces voltage spikes.

For the output rectification, lower forward voltage and ultra-fast recovery diodes can improve efficiency. Capacitor C10 stores the energy needed during output load jumps, and it should have low ESR. LC filter L2 and C11 reduces the high-frequency ripple voltage.

5.3 Control of Flyback converter through fifth-generation QR CoolSET™ ICE5QR2270AZ

5.3.1 Integrated HV power MOSFET

The ICE5QR2270AZ CoolSET™ is a seven-pin device in a DIP-7 package. It has been integrated with the new QR PWM controller and all necessary features and protections, and most importantly the 700 V power MOSFET, Infineon superjunction (SJ) CoolMOS™. Hence, the schematic is much simplified and the circuit design is made much easier.

5.3.2 Fast self-start-up and sustaining of V_{CC}

The IC uses a cascode structure to fast-charge the V_{CC} capacitor. Pull-up resistors R2A, R2B and R2C connected to the multi-function ZCD pin (pin 4) is used to initiate the start-up phase. At first, 0.2 mA is used to charge the V_{CC} capacitor from 0 V to 1.1 V. This is a protection which reduces the power dissipation of the power MOSFET during V_{CC} short-to-GND condition. Thereafter, a much higher charging current of 3.2 mA will charge the V_{CC} capacitor until the V_{CC_ON} is reached. Start-up time of less than 250 ms is achievable with a V_{CC} capacitor of 22 μ F.

After start-up, the IC V_{CC} supply is sustained by the auxiliary winding of transformer T1, which needs to support the V_{CC} to be above Under-Voltage Lockout (UVLO) voltage (10 V typ.) through the rectifier circuit R9, D3 and C8.

Circuit description

5.3.3 QR switching with valley sensing

ICE5QR2270AZ is a QR Flyback controller, which turns the HV MOSFET on at the lowest valley point of the drain voltage to minimize the switching losses. The IC senses the valley point through the ZCD pin (pin 4), which monitors auxiliary winding voltage through R8, D2 and C5 together with the internal resistor R_{ZCD} . When the ZCD voltage drops below 100 mV (typ.), the HV MOSFET switches on.

The IC employs digital frequency reduction to avoid the inherent increasing switching frequency during load reduction of QR operation. With ICE5QR2270AZ, the HV MOSFET switches on from first to eighth valley for low-line or third to tenth valley for high-line.

5.3.4 Current Sensing (CS)

The ICE5QR2270AZ is a current mode controller. The peak current is controlled cycle-by-cycle through the CS resistors R5A and R5B in the CS pin (pin 3). Transformer saturation can be avoided through Peak Current Limitation (PCL); therefore, the system is more protected and reliable.

5.3.5 Feedback (FB) and compensation network

V_{OUT} is sensed by resistor dividers R14, R15 and R16 connected to the input of error amplifier TL431 (IC3). A type-2 compensation network (C12, C13 and R13) is connected to the input and output of IC3. The output of IC3 is coupled to the FB pin via optocoupler IC2.

The FB pin of ICE5QR2270AZ is a multi-function pin, which is used to select the entry/exit burst power level through a resistor at the FB pin (R7) and also the burst-on/burst-off sense input during ABM.

5.3.6 System robustness and reliability through protection features

Protection is one of the major factors in determining whether the system is safe and robust – therefore sufficient protection is necessary. ICE5QR2270AZ provides comprehensive protection to ensure the system is operating safely. This includes brown-in/brown-out, V_{IN} OV, V_{OUT} OV, V_{CC} OV and UV, open-loop/over-load, over-temperature, CS short-to-GND and V_{CC} short-to-GND. When those faults are found, the system will enter protection mode. Once the fault is removed, the system resumes normal operation. A list of protections and the failure conditions is shown in the table below.

Table 3 Protection functions of ICE5QR2270AZ

| Protection function | Failure condition (typical values) | Protection mode |
|---------------------|--|-------------------------|
| V_{CC} OV | V_{VCC} more than 25.5 V | Odd-skip auto-restart |
| V_{CC} UV | V_{VCC} less than 10 V | Auto-restart |
| V_{OUT} OV | V_{ZCD} more than 2 V for 10 consecutive pulses | Non-switch auto-restart |
| V_{IN} OV | V_{VIN} more than 2.9 V | Non-switch auto-restart |
| Brown-in/brown-out | V_{VIN_BI} less than 0.66 V/ V_{VIN_BO} less than 0.40 V | Non-switch auto-restart |
| Open-loop/over-load | V_{FB} more than 2.75 V and lasts for 30 ms | Odd-skip auto-restart |
| Over-temperature | T_J more than 140°C (40°C hysteresis) | Non-switch auto-restart |
| CS short-to-GND | V_{CS} less than 0.1 V, lasts for 5 μ s and three consecutive pulses | Odd-skip auto-restart |

| Protection function | Failure condition (typical values) | Protection mode |
|---|--|-----------------|
| V_{CC} short-to-GND ($V_{CC} = 0$ V, start-up = 50 M Ω and $V_{DRAIN} = 90$ V) | V_{CC} less than 1.1 V, $I_{VCC_Charge1} \approx -0.2$ mA | Cannot start up |

5.4 Clamper circuit

A clamper network consisting of D1, C2, R4, R3A and R3B is used to reduce the switching voltage spikes across the DRAIN pin, which are generated from the leakage inductance of the transformer T1. This is a dissipative circuit; therefore, R3A, R3B and C2 need to be fine-tuned depending on the voltage derating factor and efficiency requirement.

5.5 PCB design tips

For a good PCB design layout, there are several points to note.

- The switching power loop needs to be as small as possible (see Figure 4). There are two power loops in the reference design; one on the primary side and one on the secondary side. The primary-side loop starts from the bulk capacitor (C1) positive terminal, primary transformer winding (pin 4 and pin 6 of T1), CoolSET™, CS resistors and back to the C1 negative terminal. The secondary-side loop starts at the secondary transformer winding (pin 8 of T1), output diode D4, output capacitor C10 and back to pin 11 of T1.

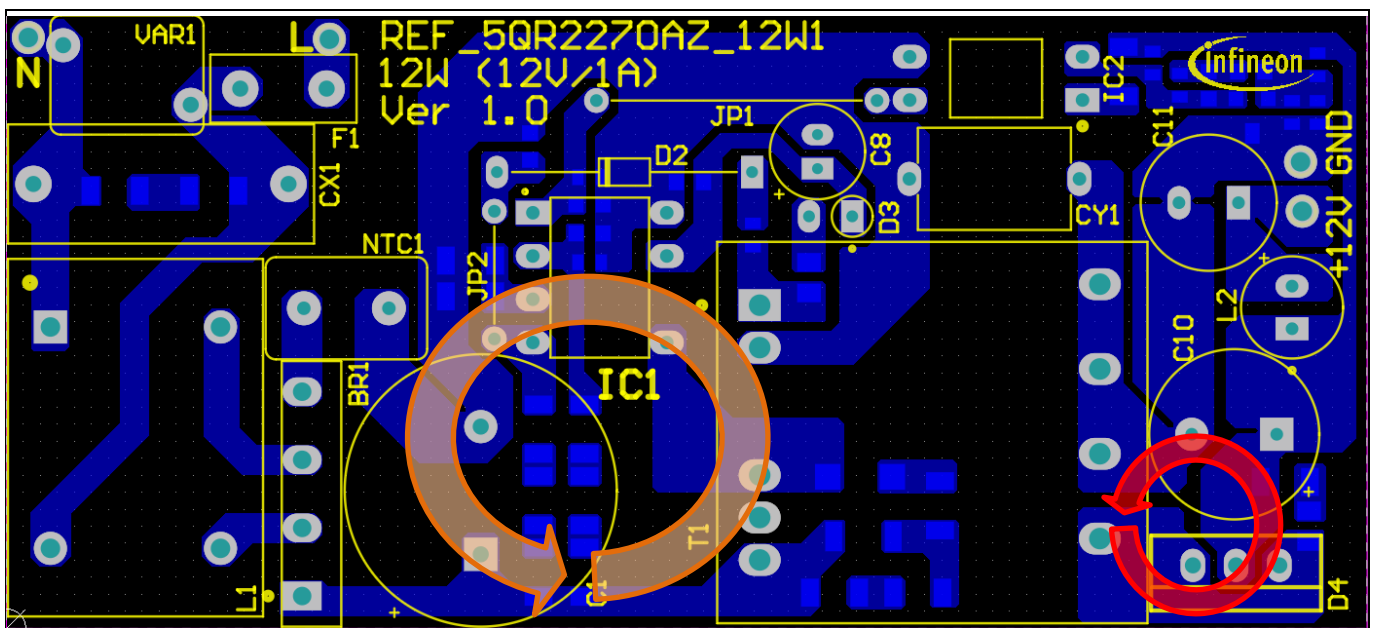


Figure 4 PCB layout tips

- Star-ground connection should be used to reduce HF noise coupling, which can affect the functional operation. The ground of the small-signal components, e.g. R6, R7, C4, C5, C6, C7, and the emitter of the optocoupler (pin 3 of IC2) should connect directly to the IC ground (pin 8 of IC1).
- Separating the HV components and LV components, e.g. clamper circuit (D1, C2, R3A, R3B and R4), at the bottom part of the PCB and the other LV components at the upper part of the PCB can reduce the spark-over chance of the high energy surge during ESD or a lightning surge test.
- Make the PCB copper pour on the DRAIN pin of the MOSFET cover as wide an area as possible to act as a heatsink.

5.6 EMI reduction tips

EMI compliance is always a challenge for the power supply designer. There are several critical points to consider in order to achieve a satisfactory EMI performance.

- A proper transformer design can significantly reduce EMI. Low leakage inductance can incur a low switching spike and HF noise. Interlaced winding technique is the most common practice to reduce leakage inductance. Winding shield, core shield and whole transformer shield are also some of the techniques used to reduce EMI.
- Input CMC and X-capacitor greatly reduce EMI, but this is costly and impractical especially for low-power applications.
- Short-switching power-loop design in the PCB (as described in section 5.5) can reduce radiated EMI due to the antenna effect.
- The Y-capacitor CY1 dampens the HF noise generated between the primary and secondary, thus reducing the EMI noise.
- The secondary diode snubber circuit (R10 and C9) can reduce HF noise.
- Ferrite beads can reduce HF noise, especially on critical nodes such as the DRAIN pin, clamper diode and secondary diode terminals. There is no ferrite bead used in this design, as this can reduce the efficiency due to additional losses, especially on the MOSFET and secondary diode.

6 PCB layout

6.1 Top side

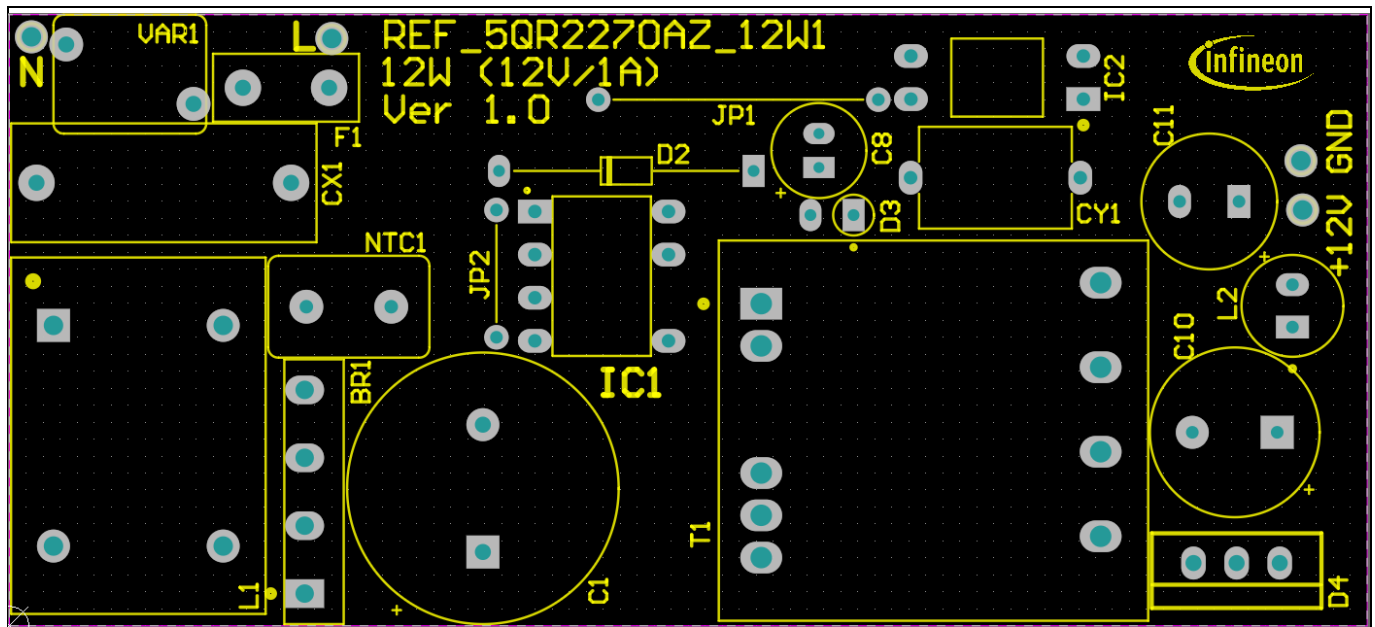


Figure 5 Top side component legend

6.2 Bottom side

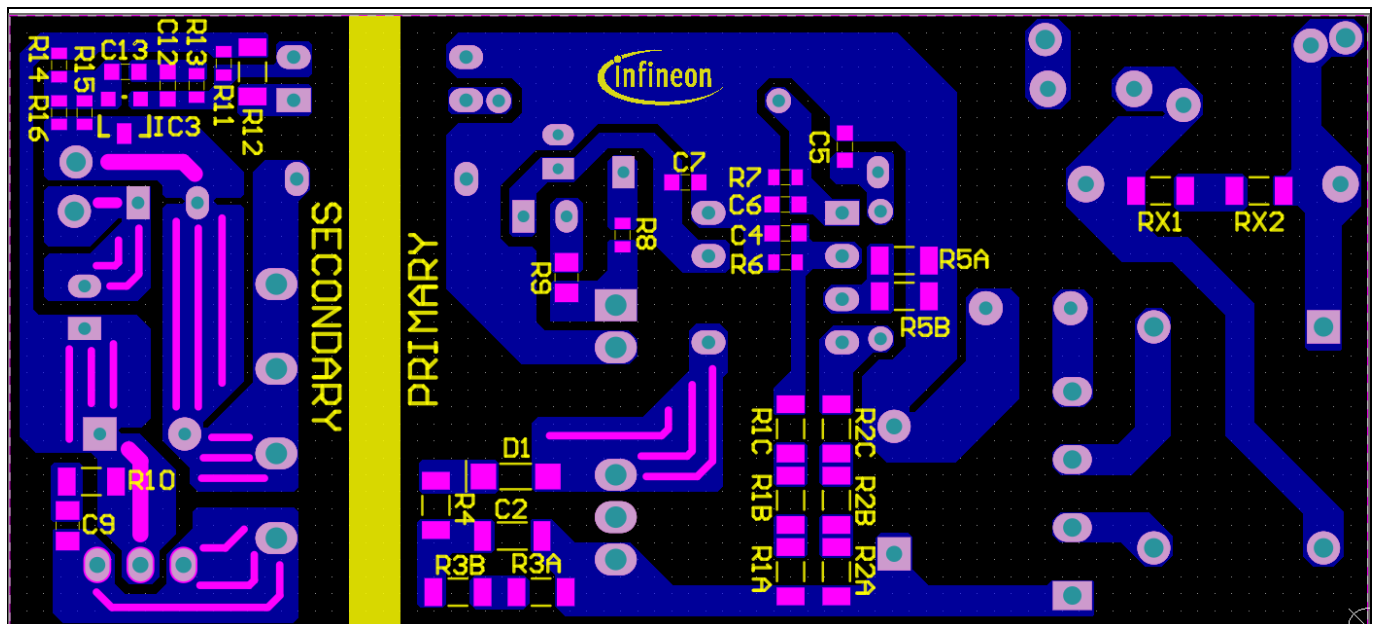


Figure 6 Bottom side copper and component legend

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



BOM

7 BOM

Table 4 BOM

| Item | Designator | Description | Part no. | Manufacturer | Qty. |
|------|---------------|---------------------------------------|--------------------|-------------------|------|
| 1 | BR1 | 1 A/600 V | KBP06G | Shindengen | 1 |
| 2 | C1 | 33 μ F/450 V | 450BXC33MEFC16X25 | Rubycon | 1 |
| 3 | C2 | 220 pF/630 V/1206 | | | 1 |
| 4 | C4 | 22 nF/50 V/0603 | | | 1 |
| 5 | C5 | 47 pF/50 V/0603 | | | 1 |
| 6 | C6 | 4.7 nF/50 V/0603 | | | 1 |
| 7 | C12 | 1 nF/50 V/0603 | | | 1 |
| 8 | C7, C13 | 100 nF/50 V/0603 | | | 2 |
| 9 | C8 | 22 μ F/50 V | 50PX22MEFC5X11 | Rubycon | 1 |
| 10 | C10 | 1000 μ F/25 V | 25ZLH1000MEFC10X23 | Rubycon | 1 |
| 11 | C11 | 220 μ F/25 V | 25ZLG220MEFC8X11.5 | Rubycon | 1 |
| 12 | CX1 | 0.22 μ F/305 V/X2 | B32922C3224 | Epcos | 1 |
| 13 | CY1 | 2200 pF/250 V/X1/Y1 | DE1E3KX222MA4BN01F | Murata | 1 |
| 14 | D1 | 1 A/800 V | US1K-13-F | | 1 |
| 15 | D2 | 0.2 A/150 V | FDH400 | | 1 |
| 16 | D3 | 0.2 A/200 V | 1N485B | | 1 |
| 17 | D4 | 20 A/100 V | STPS20M100SFP | | 1 |
| 18 | F1 | 1.6 A/300 V | 36911600000 | Littlefuse | 1 |
| 19 | IC1 | QR CoolSET™ | ICE5QR2770AZ | Infineon | 1 |
| 20 | IC2 | Optocoupler | SFH617A-3 | | 1 |
| 21 | IC3 | 2.5 V _{ref} | TL431AQDBZR | | 1 |
| 22 | JP1, JP2 | | Jumper | | 2 |
| 23 | L1 | 2 x 39 mH | 750343586 | Würth Electronics | 1 |
| 24 | L2 | 2.2 μ H/4.3 A | 7447462022 | Würth Electronics | 1 |
| 25 | NTC1 | Shorted | | | 1 |
| 26 | R1A, R1B, R1C | 3 M Ω /0.25 W/1 percent/1206 | | | 3 |
| 27 | R2A, R2B, R2C | 15 M Ω /0.25 W/5 percent/1206 | | | 3 |
| 28 | R3A, R3B | 120 k Ω /0.25 W/5 percent/1206 | | | 2 |
| 29 | R4 | 10 Ω /0.25 W/5 percent/1206 | | | 1 |
| 30 | R5A | 2.7 Ω /0.25 W/1 percent/1206 | | | 1 |
| 31 | R5B | 3 Ω /0.25 W/1 percent/1206 | | | 1 |
| 32 | R6 | 62 k Ω /0.1 W/1 percent/0603 | | | 1 |
| 33 | R8 | 27 k Ω /0.1 W/1 percent/0603 | | | 1 |
| 34 | R9 | 4.7 Ω /0.1 W/5 percent/0805 | | | 1 |
| 35 | R11 | 1.2 k Ω /0.1 W/5 percent/0603 | | | 1 |
| 36 | R12 | 820 Ω /0.25 W/5 percent/1206 | | | 1 |
| 37 | R13 | 4.3 k Ω /0.1 W/5 percent/0603 | | | 1 |
| 38 | R14 | 47 k Ω /0.1 W/1 percent/0603 | | | 1 |
| 39 | R15 | 13 k Ω /0.1 W/1 percent/0603 | | | 1 |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



BOM

| | | | | | |
|----|----------|--|------------|-------------------|---|
| 40 | R16 | 200 k Ω /0.1 W/1 percent/0603 | | | 1 |
| 41 | RX1, RX2 | 2 M Ω /0.25 W/5 percent/1206 | | | 2 |
| 42 | T1 | 1.3 mH/EE20 | 750344229 | Wurth Electronics | 1 |
| 43 | VAR1 | Varistor, 0.3 W/320 V | ERZE07A511 | Panasonic | 1 |
| 44 | PCB | 80 mm x 36 mm(L x W), single layer, 2 oz., FR-4 | | | 1 |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Transformer specification

8 Transformer specification

Refer to Appendix A: Transformer design and spreadsheet [3] for transformer design and Appendix B: WE transformer specification for WE transformer specification.

Würth Electronics core part number: 150-1945 (EE20/10/6)

Würth Electronics bobbin: 070-5643 (14-Pin EXT, THT, horizontal version)

Primary inductance: $L_p = 1300 \mu\text{H}$ (± 10 percent), measured between pin 4 and pin 6

Manufacturer and part number: Würth Electronics Midcom (750344229)

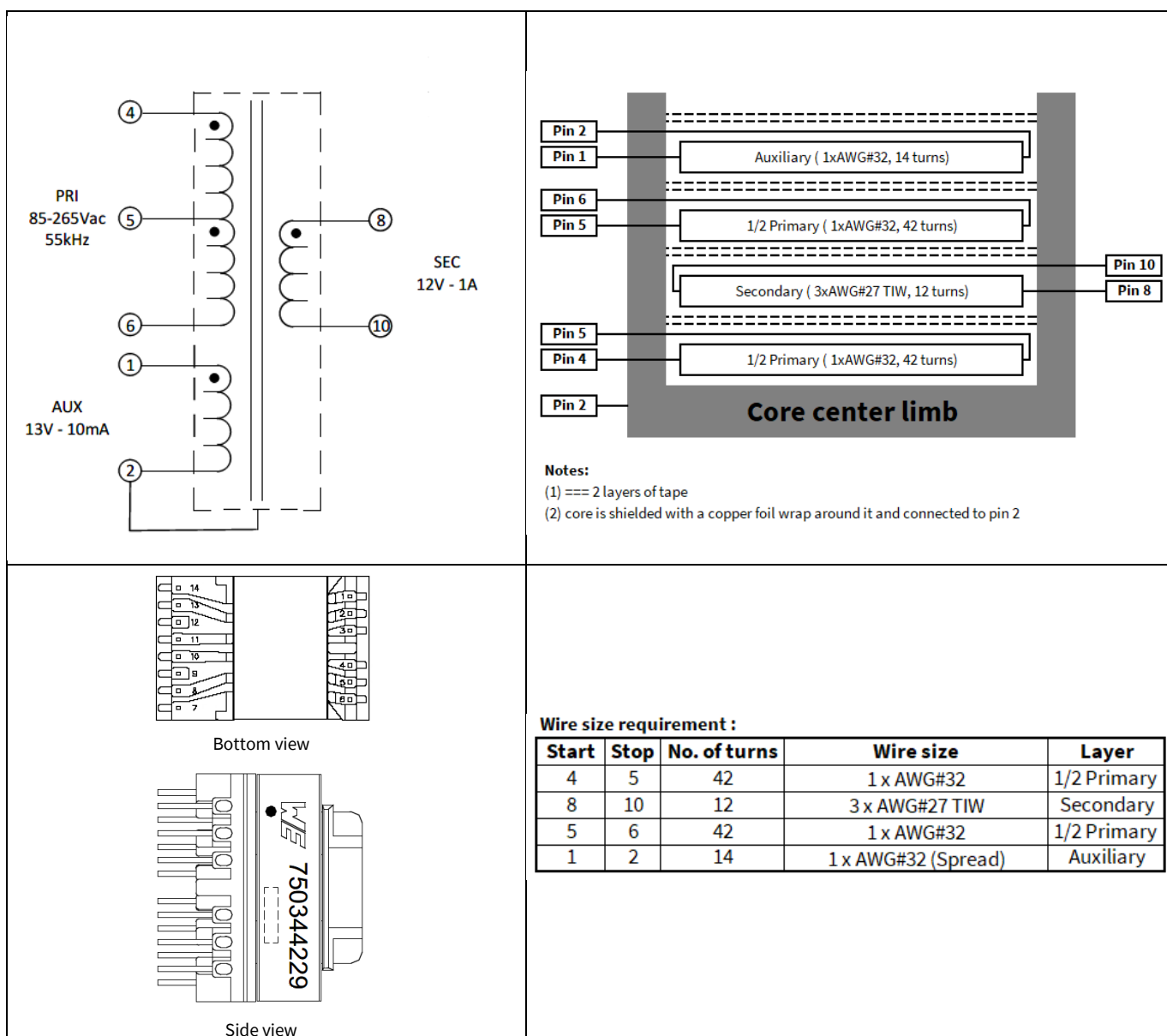


Figure 7 Transformer structure

9 Measurement data and graphs

Table 5 Measurement data

| Input (V AC/Hz) | Loading condition | P _{IN} (W) | V _{OUT} (V) | I _{OUT} (A) | P _{OUT} (W) | Efficiency (%) | Average efficiency (%) | OLP P _{IN} (W) | OLP I _{OUT} (A) |
|--------------------|------------------------|------------------------|-------------------------|-------------------------|-------------------------|-------------------|------------------------------|----------------------------|-----------------------------|
| 85 V AC/ 60 Hz | No load | 0.034 | 12.055 | 0.0000 | 0.00 | | | 17.11 | 1.24 |
| | 10 percent load | 1.413 | 12.054 | 0.1000 | 1.21 | 85.29 | | | |
| | 25 percent load | 3.404 | 12.052 | 0.2506 | 3.02 | 88.73 | 88.64 | | |
| | 50 percent load | 6.776 | 12.050 | 0.5006 | 6.03 | 89.03 | | | |
| | 75 percent load | 10.165 | 12.047 | 0.7506 | 9.04 | 88.96 | | | |
| | 100 percent load | 13.720 | 12.044 | 1.0006 | 12.05 | 87.84 | | | |
| 115 V AC/ 60 Hz | No load | 0.038 | 12.055 | 0.0000 | 0.00 | | | 18.56 | 1.36 |
| | 10 percent load | 1.424 | 12.053 | 0.1000 | 1.21 | 84.65 | | | |
| | 25 percent load | 3.394 | 12.052 | 0.2506 | 3.02 | 89.00 | 89.51 | | |
| | 50 percent load | 6.730 | 12.049 | 0.5006 | 6.03 | 89.62 | | | |
| | 75 percent load | 10.066 | 12.047 | 0.7506 | 9.04 | 89.84 | | | |
| | 100 percent load | 13.453 | 12.044 | 1.0006 | 12.05 | 89.58 | | | |
| 220 V AC/ 50 Hz | No load | 0.057 | 12.056 | 0.0000 | 0.00 | | | 19.83 | 1.48 |
| | 10 percent load | 1.419 | 12.049 | 0.1000 | 1.20 | 84.94 | | | |
| | 25 percent load | 3.447 | 12.045 | 0.2506 | 3.02 | 87.57 | 89.25 | | |
| | 50 percent load | 6.739 | 12.043 | 0.5006 | 6.03 | 89.46 | | | |
| | 75 percent load | 10.051 | 12.039 | 0.7506 | 9.04 | 89.91 | | | |
| | 100 percent load | 13.373 | 12.036 | 1.0006 | 12.04 | 90.06 | | | |
| 264 V AC/ 50 Hz | No load | 0.069 | 12.055 | 0.0000 | 0.00 | | | 20.69 | 1.54 |
| | 10 percent load | 1.445 | 12.049 | 0.1000 | 1.20 | 83.39 | | | |
| | 25 percent load | 3.491 | 12.043 | 0.2506 | 3.02 | 86.46 | 88.69 | | |
| | 50 percent | 6.781 | 12.040 | 0.5006 | 6.03 | 88.89 | | | |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Measurement data and graphs

| | | | | | | | | | |
|--|------------------------|--------|--------|--------|-------|-------|--|--|--|
| | load | | | | | | | | |
| | 75 percent load | 10.090 | 12.036 | 0.7506 | 9.03 | 89.53 | | | |
| | 100 percent load | 13.396 | 12.033 | 1.0006 | 12.04 | 89.88 | | | |

9.1 Efficiency curve

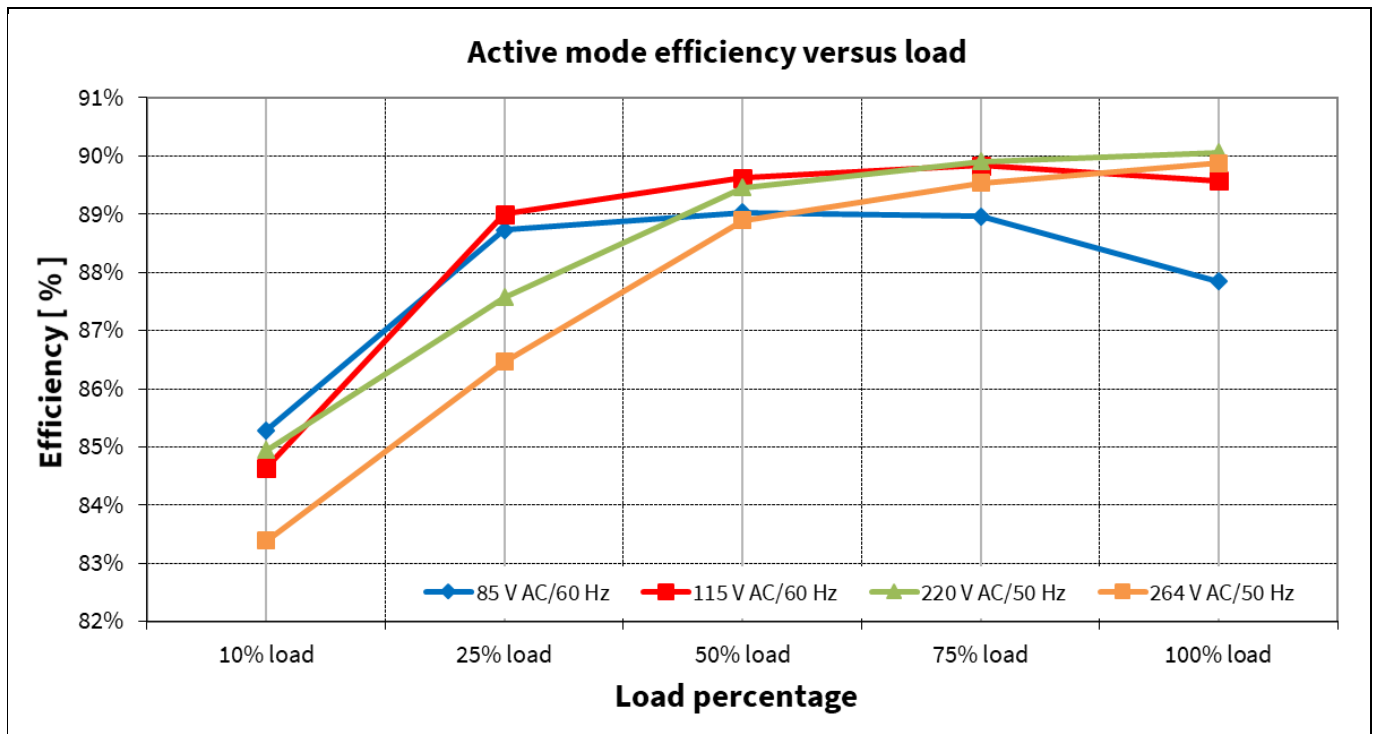


Figure 8 Active mode efficiency vs. load

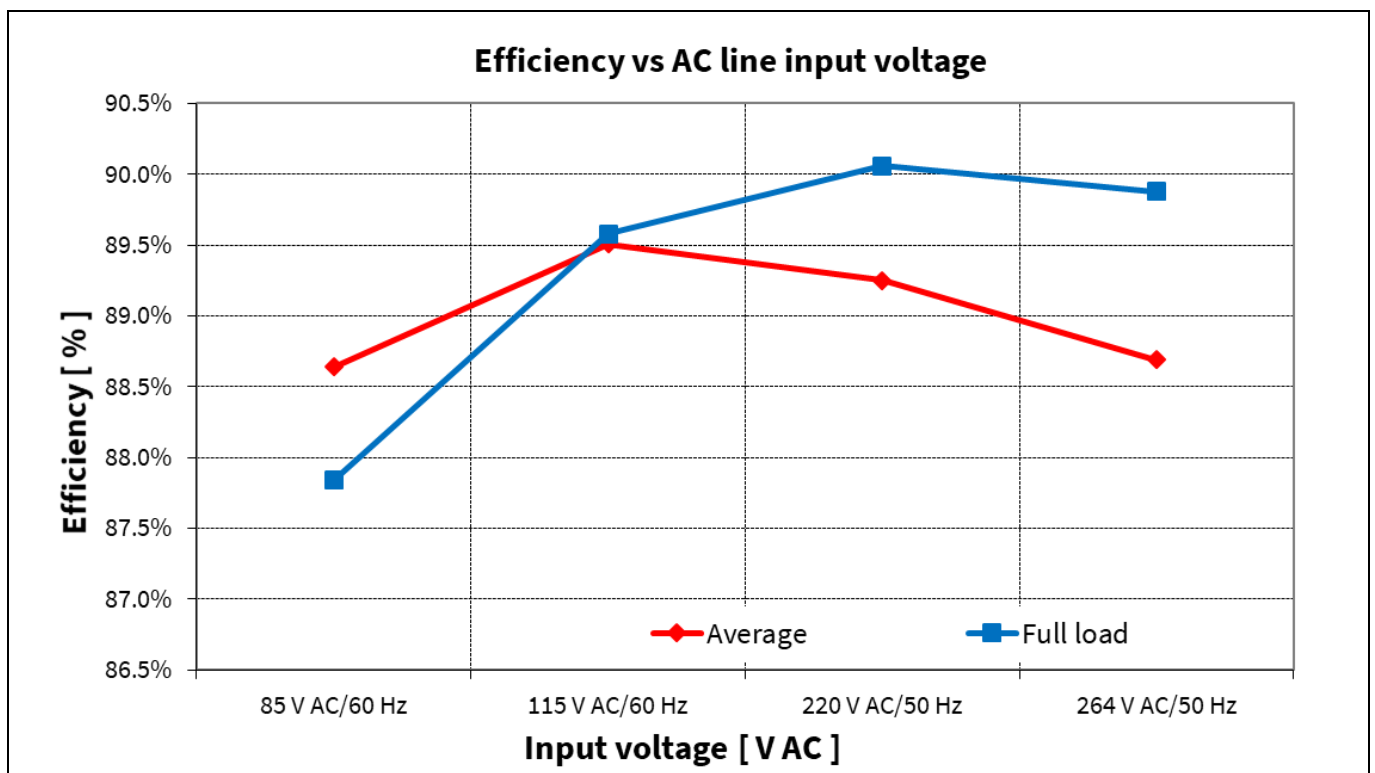


Figure 9 Efficiency vs. AC-line input voltage

9.2 Standby power

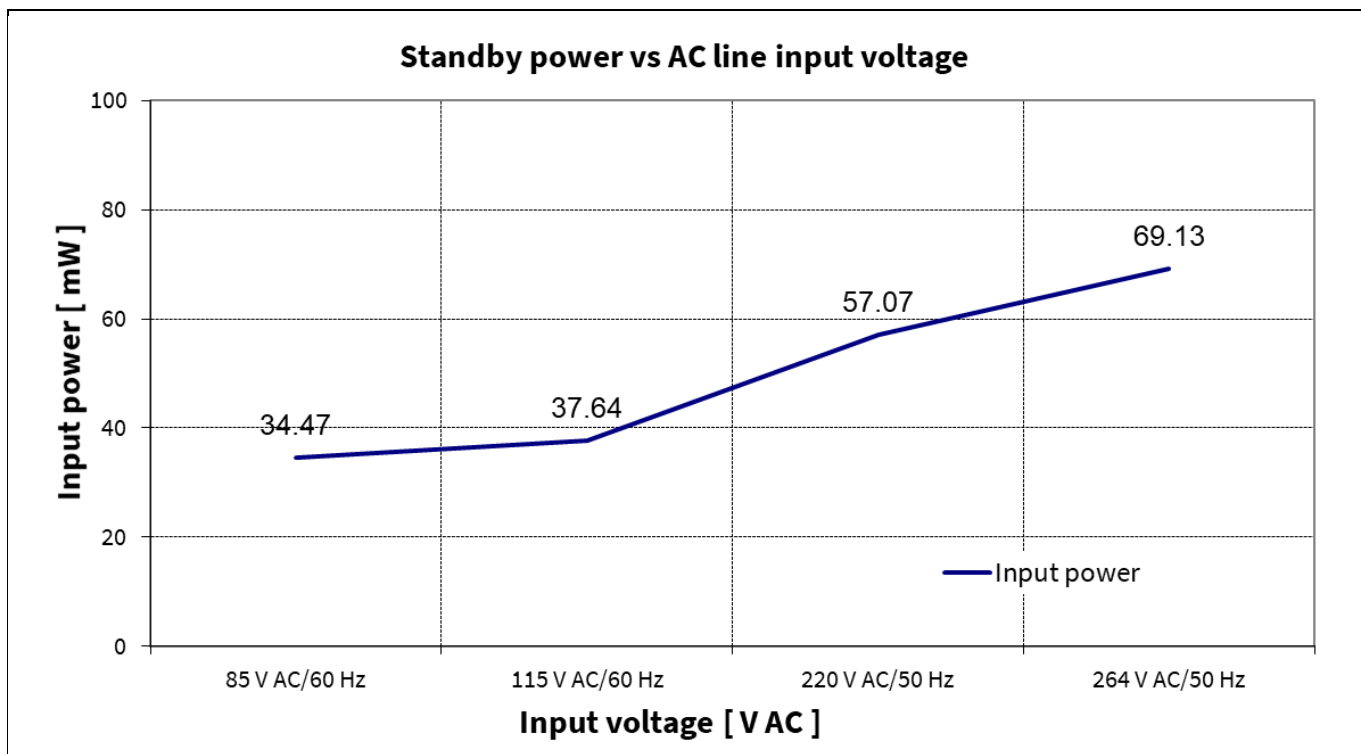


Figure 10 Standby power at no load vs. AC-line input voltage (measured by Yokogawa WT210 power meter – integration mode)

9.3 Line and load regulation

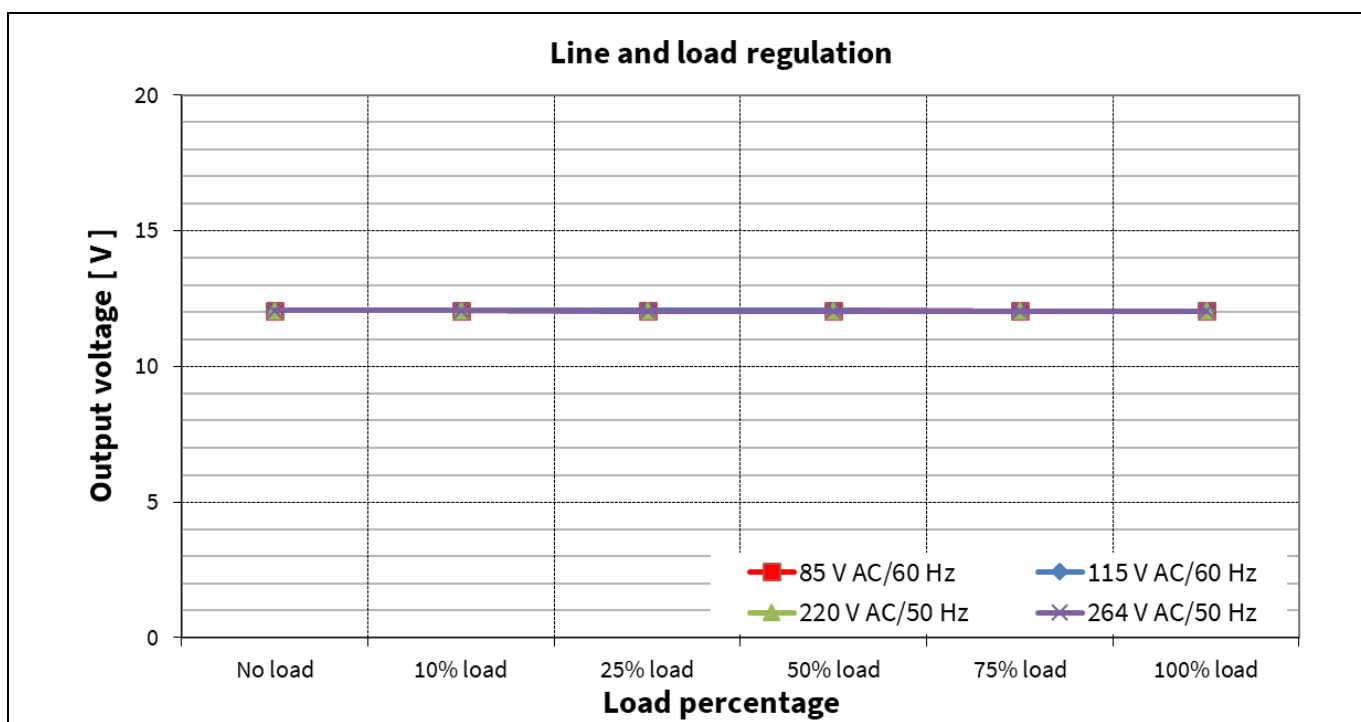


Figure 11 Output regulation vs. load at different AC-line input voltages

9.4 Maximum input power

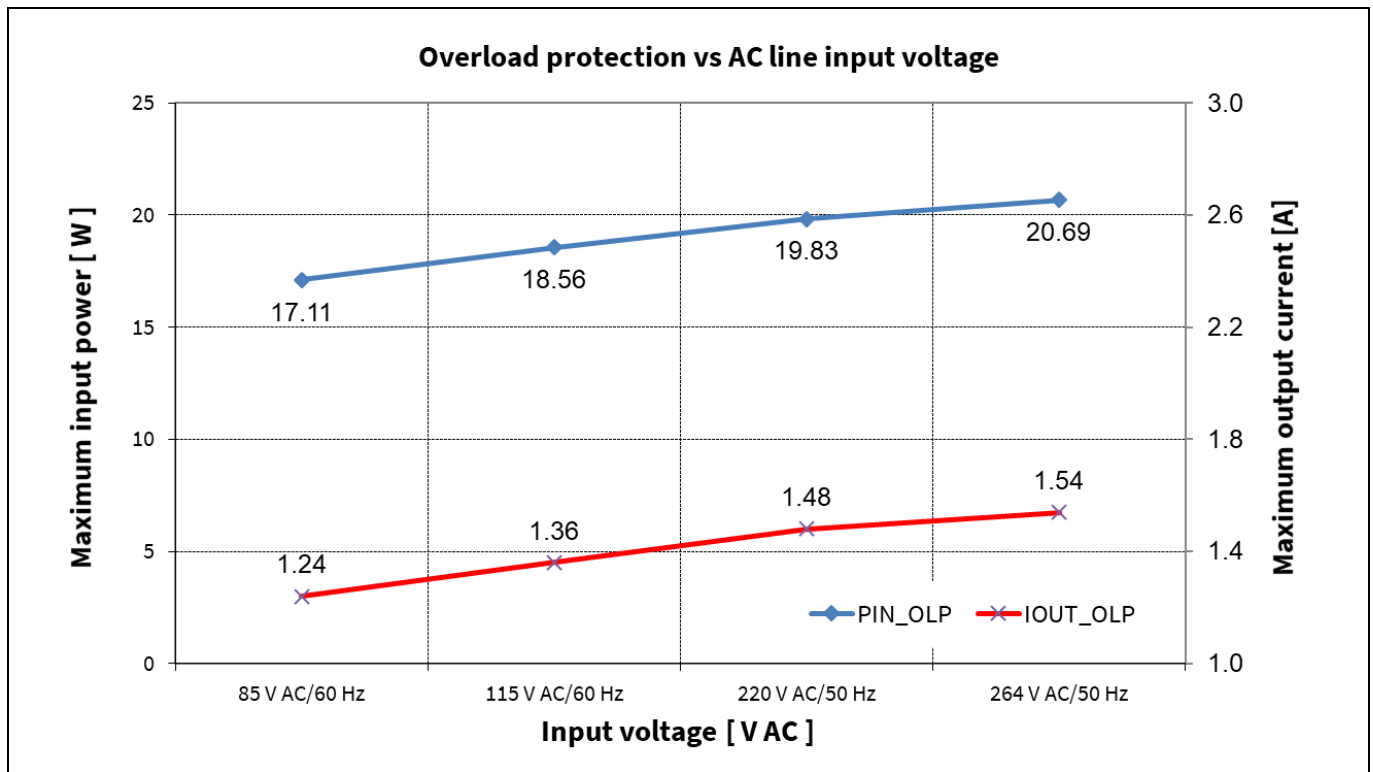


Figure 12 Maximum input power and output current (before over-load protection) vs. AC-line input voltage

9.5 Switching frequency through digital frequency reduction

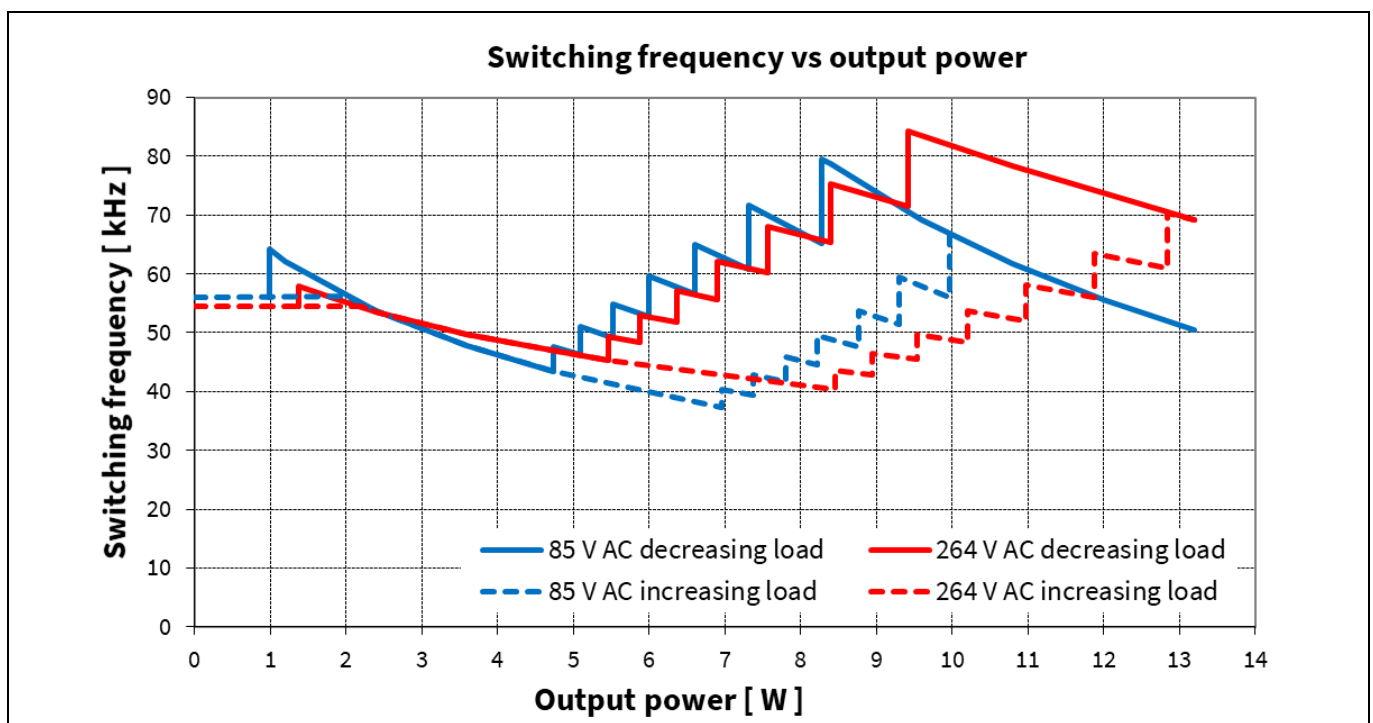


Figure 13 Switching frequency vs. output load

9.6 ESD immunity (EN 61000-4-2)

The reference board was subjected to a ± 8 kV contact and air discharge ESD test according to EN 61000-4-2. It was tested at full load (12 W) using resistive load (12Ω) at an input voltage of 115 V AC and 220 V AC. A test failure was defined as non-recoverable and/or system auto-restart.

- ± 8 kV contact discharge: pass
- ± 8 kV air discharge: pass

Table 6 System ESD test result

| Description | ESD test | Level | Number of strikes | | Test result |
|--|----------|-------|----------------------|-----|-------------|
| | | | +12 V _{OUT} | GND | |
| 115 V AC, 12 W ($12 \Omega R_{LOAD}$) | Contact | +8 kV | 10 | 10 | Pass |
| | | -8 kV | 10 | 10 | Pass |
| | Air | +8 kV | 10 | 10 | Pass |
| | | -8 kV | 10 | 10 | Pass |
| 220 V AC, 12 W ($12 \Omega R_{LOAD}$) | Contact | +8 kV | 10 | 10 | Pass |
| | | -8 kV | 10 | 10 | Pass |
| | Air | +8 kV | 10 | 10 | Pass |
| | | -8 kV | 10 | 10 | Pass |

9.7 Surge immunity (EN 61000-4-5)

The reference board was subjected to a surge immunity test (± 2 kV DM and ± 4 kV CM) according to EN 61000-4-5. It was tested at full load (12 W) using resistive load (12Ω) at an input voltage of 220 V AC. Output GND is connected to P.E. during testing. A test failure was defined as non-recoverable.

- ± 2 kV DM: pass
- ± 4 kV CM: pass

Table 7 System surge immunity test result

| Description | Test | Level | | Number of strikes | | | | Test result |
|--|------|-------|---------------------|-------------------|------------|-------------|-------------|-------------|
| | | | | 0 degrees | 90 degrees | 180 degrees | 270 degrees | |
| 220 V AC, 12 W ($12 \Omega R_{LOAD}$) | DM | +2 kV | L \rightarrow N | 3 | 3 | 3 | 3 | Pass |
| | | -2 kV | L \rightarrow N | 3 | 3 | 3 | 3 | Pass |
| | CM | +4 kV | L \rightarrow GND | 3 | 3 | 3 | 3 | Pass |
| | | +4 kV | N \rightarrow GND | 3 | 3 | 3 | 3 | Pass |
| | | -4 kV | L \rightarrow GND | 3 | 3 | 3 | 3 | Pass |
| | | -4 kV | N \rightarrow GND | 3 | 3 | 3 | 3 | Pass |

9.8 Conducted emissions (EN 55022 class B)

The conducted EMI was measured by Schaffner (SMR4503) and followed the test standard of EN55022 (CISPR 22) class B. The reference board was tested at full load (12 W) using resistive load (12 Ω) at an input voltage of 115 V AC and 220 V AC.

- 115 V AC: pass with more than 9 dB margin
- 220 V AC: pass with more than 9 dB margin

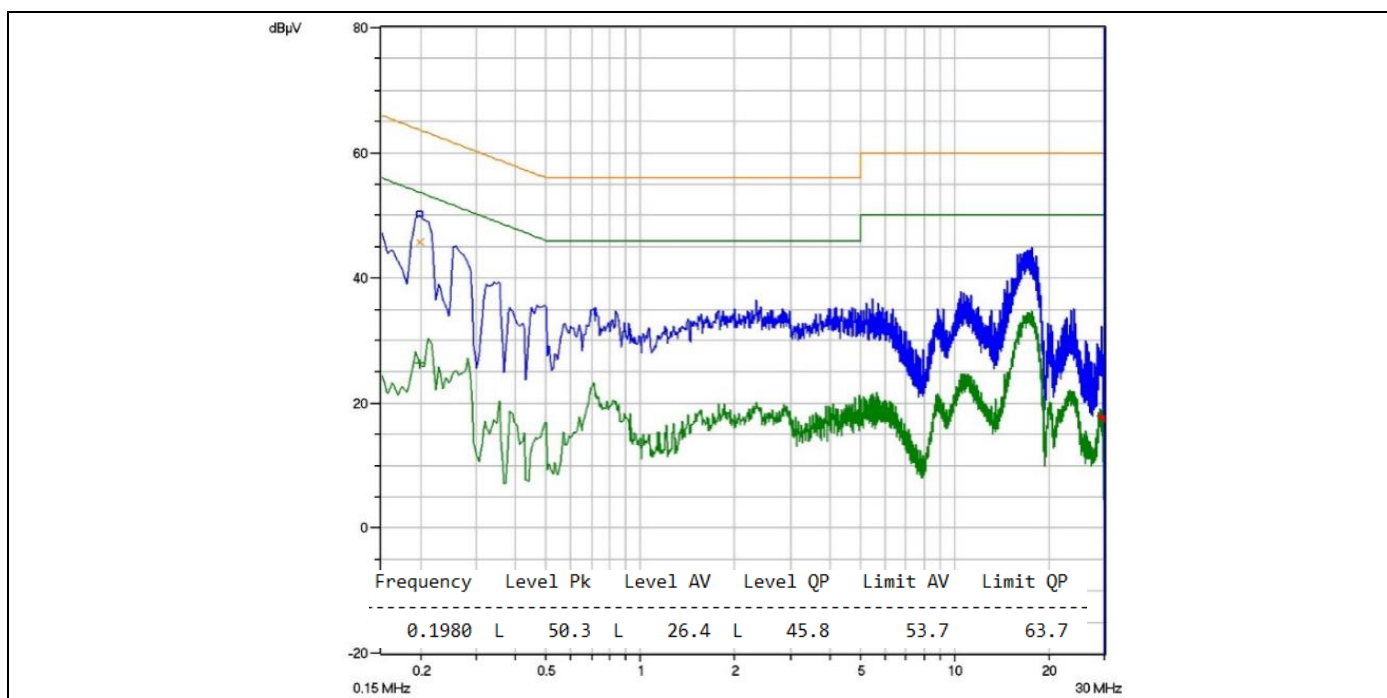


Figure 14 Conducted emissions (line) at 115 V AC and full load

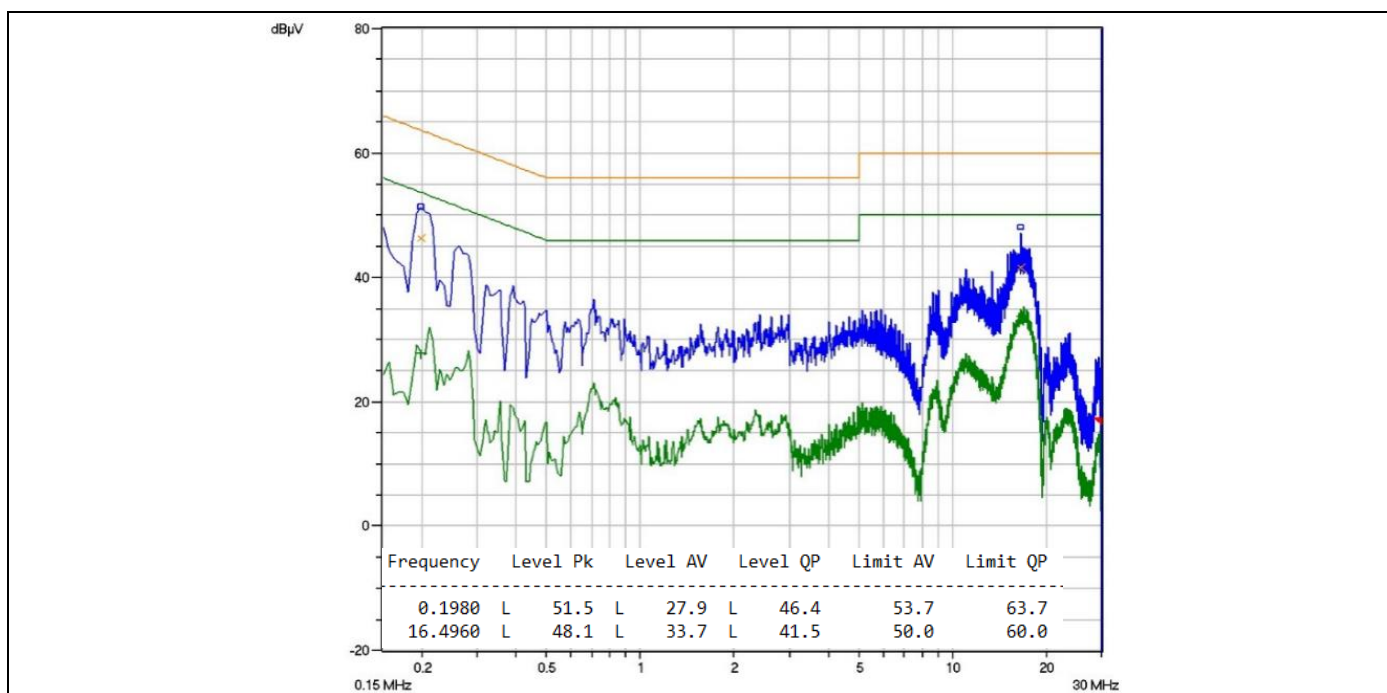


Figure 15 Conducted emissions (neutral) at 115 V AC and full load

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Measurement data and graphs

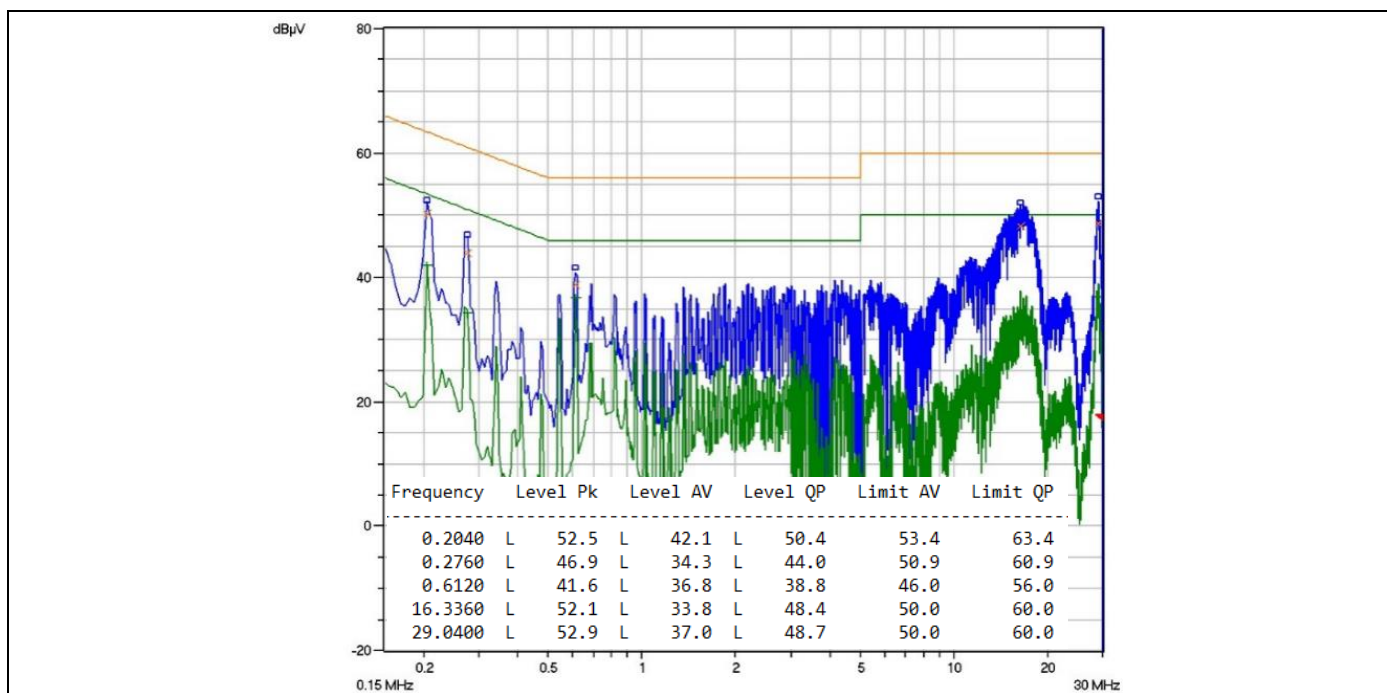


Figure 16 Conducted emissions (line) at 220 V AC and full load

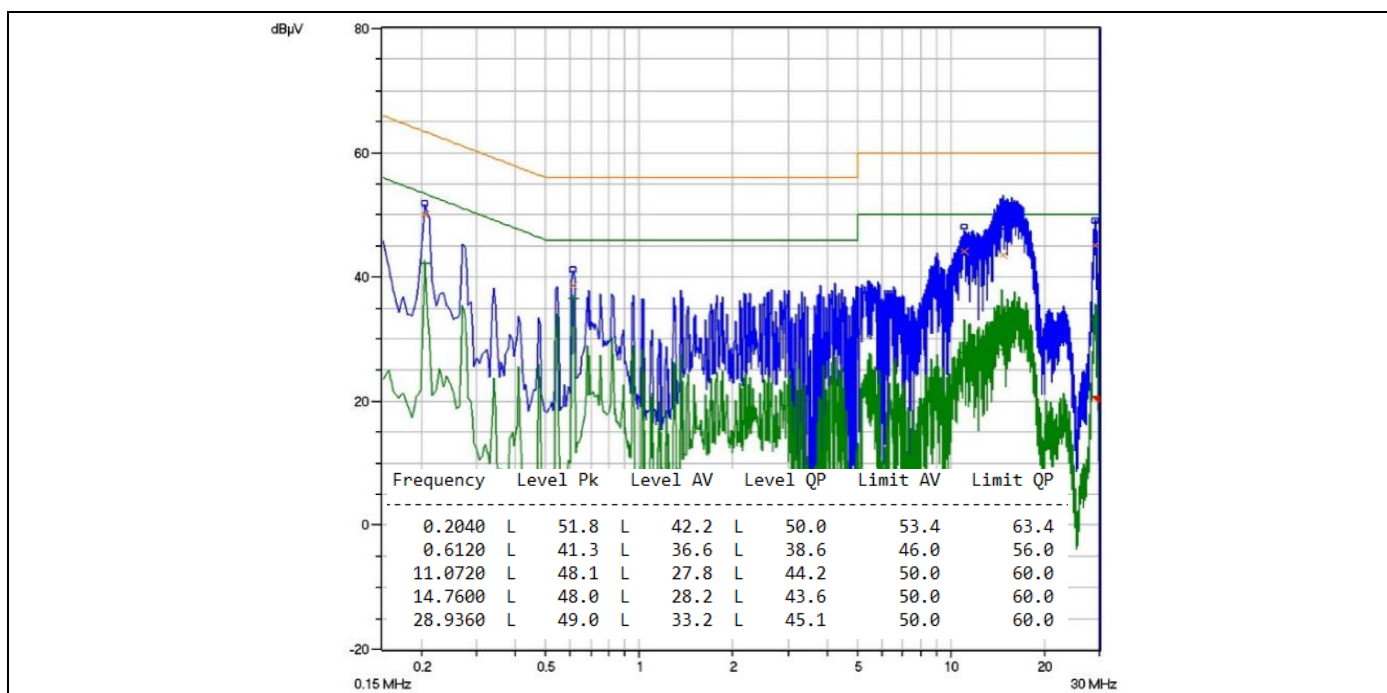


Figure 17 Conducted emissions (neutral) at 220 V AC and full load

9.9 Thermal measurement

Thermal measurement was done using an infrared thermography camera (FLIR-T62101) at an ambient temperature of 25°C, after one hour running at full load. The temperature of the components was taken in an open-frame set-up.

Table 8 Thermal measurement on components (open frame)

| No. | Component | Temperature at 85 V AC (°C) | Temperature at 264 V AC (°C) |
|-----|-----------------------------|-----------------------------|------------------------------|
| 1 | D4 (secondary diode) | 53.4 | 53.1 |
| 2 | T1 (transformer) | 49.3 | 50.1 |
| 3 | IC1 (ICE5QR2270AZ) | 46.1 | 43.4 |
| 4 | PCB (under secondary diode) | 47.7 | 47.4 |

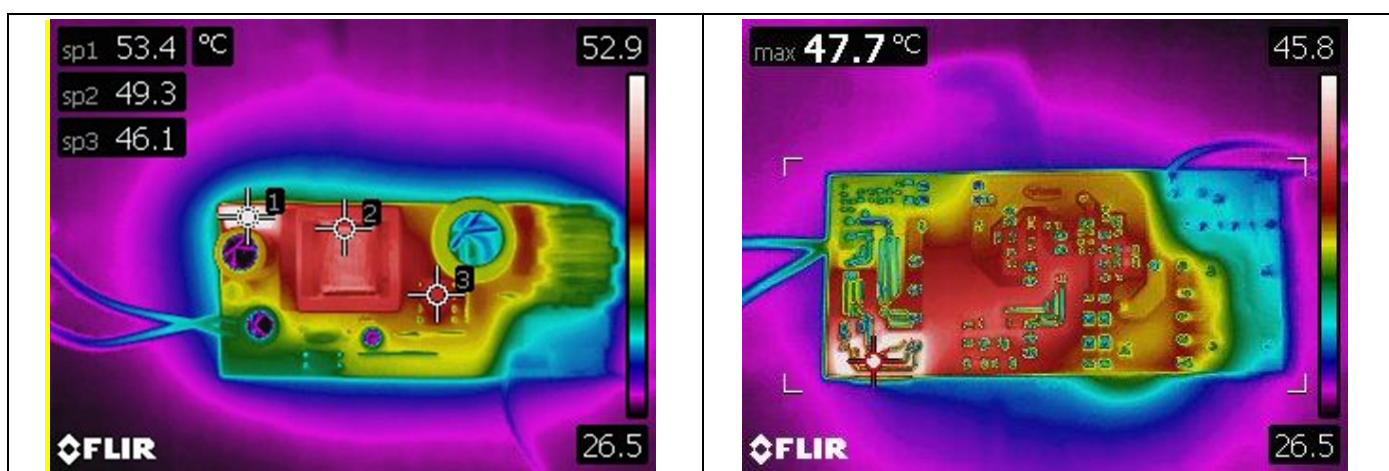


Figure 18 Top layer (left) and bottom layer (right) thermal image at 85 V AC input voltage

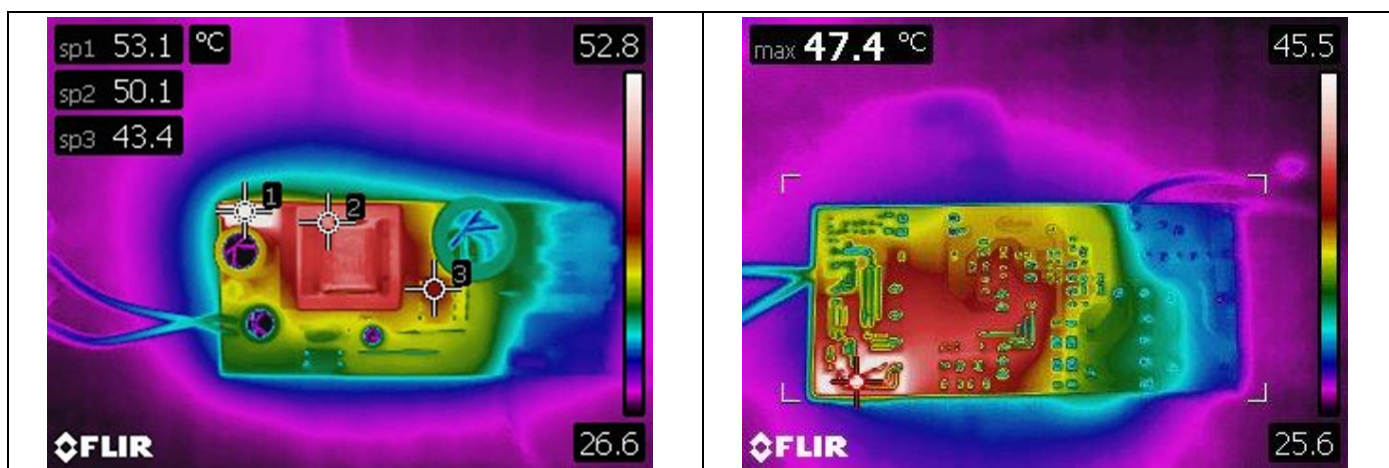


Figure 19 Top layer (left) and bottom layer (right) thermal image at 264 V AC input voltage

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Waveforms and oscilloscope plots

10 Waveforms and oscilloscope plots

All waveforms and scope plots were recorded with a LeCroy 44Xi oscilloscope.

10.1 Start-up at full load

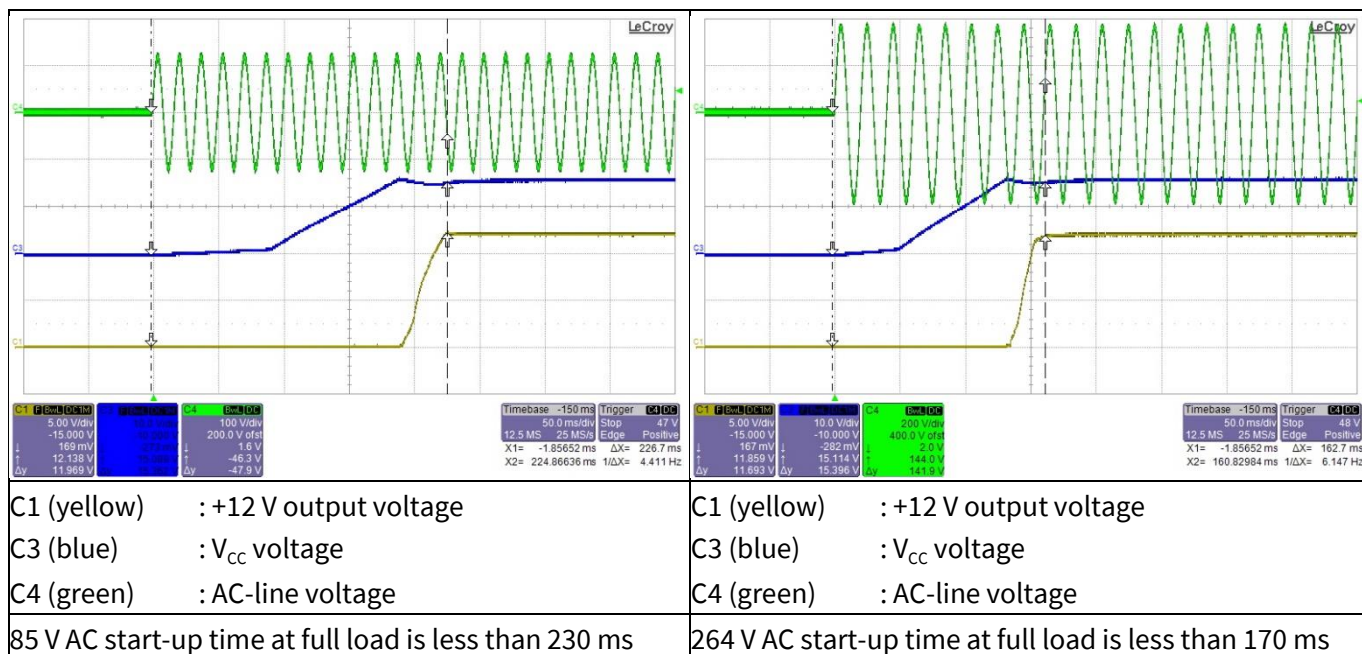


Figure 20 Start-up

10.2 Soft-start at full load

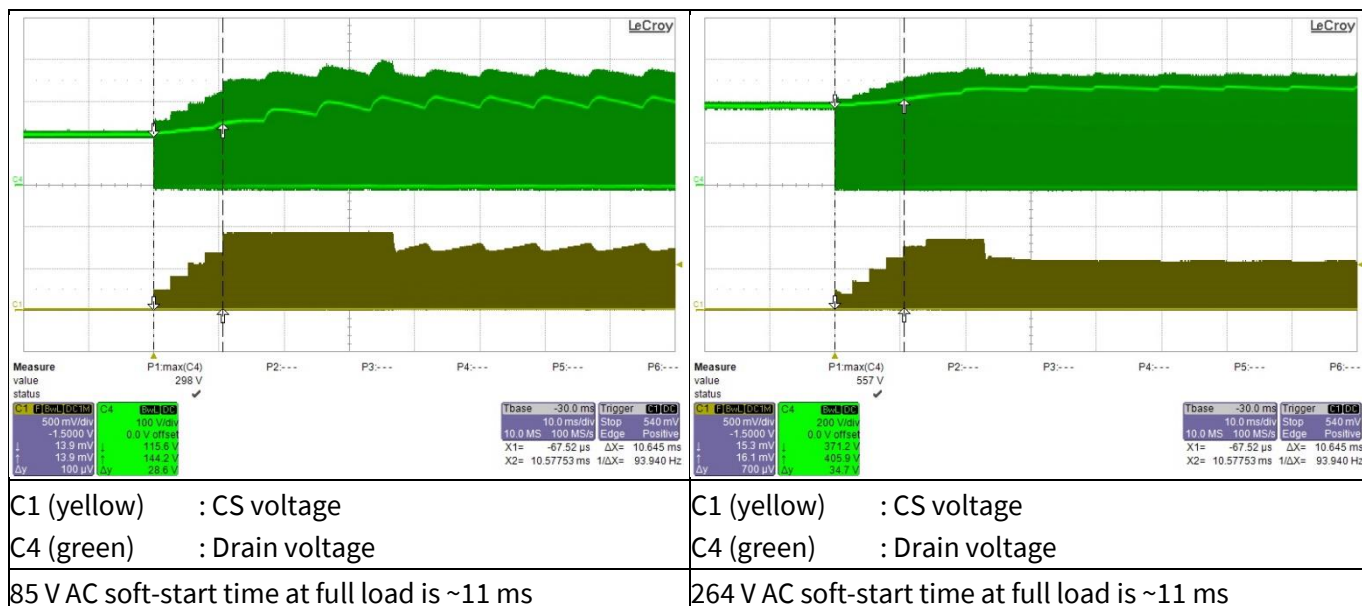


Figure 21 Soft-start

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Waveforms and oscilloscope plots

10.3 Drain and CS voltage at full load

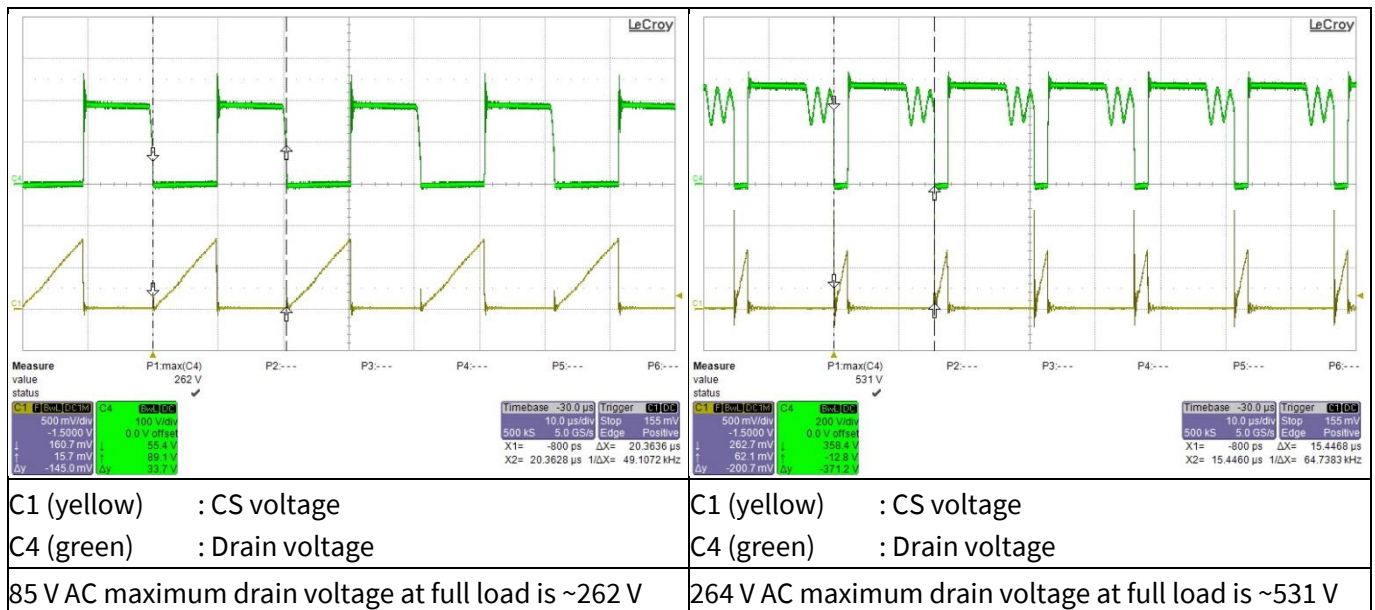


Figure 22 Drain and CS voltage

10.4 Output ripple voltage at full load

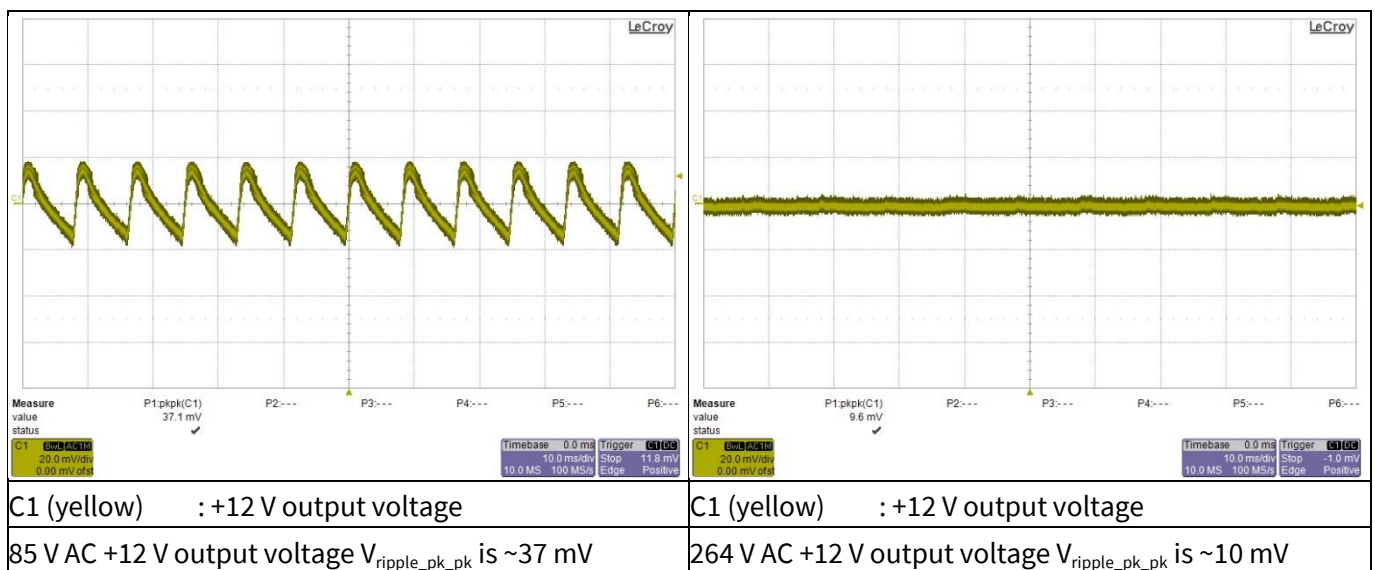


Figure 23 Output ripple voltage at full load. Probe terminals are connected on the PCB end and decoupled with 1 μ F electrolytic and 0.1 μ F ceramic capacitors. Oscilloscope is bandwidth filter limited to 20 MHz.

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Waveforms and oscilloscope plots

10.5 Output ripple voltage at ABM (100 mA load)

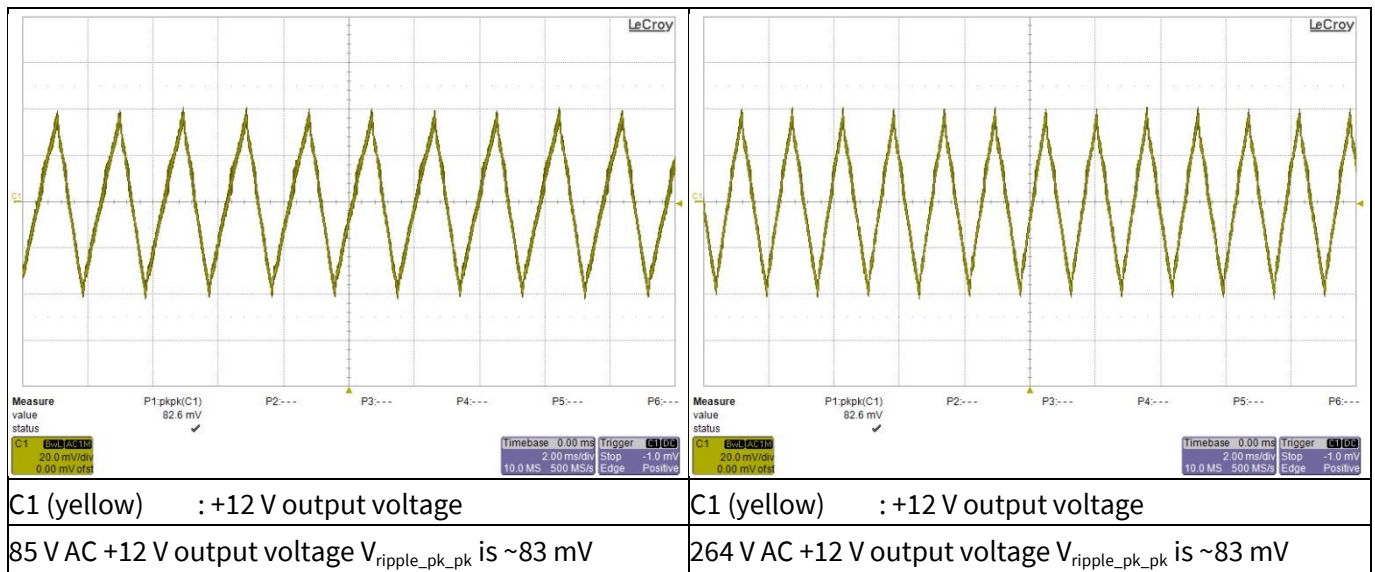


Figure 24 Output ripple voltage at 100 mA load. Probe terminals are connected on the PCB end and decoupled with 1 μF electrolytic and 0.1 μF ceramic capacitors. Oscilloscope is bandwidth filter limited to 20 MHz.

10.6 Load transient response (dynamic load from 10 percent to 100 percent)

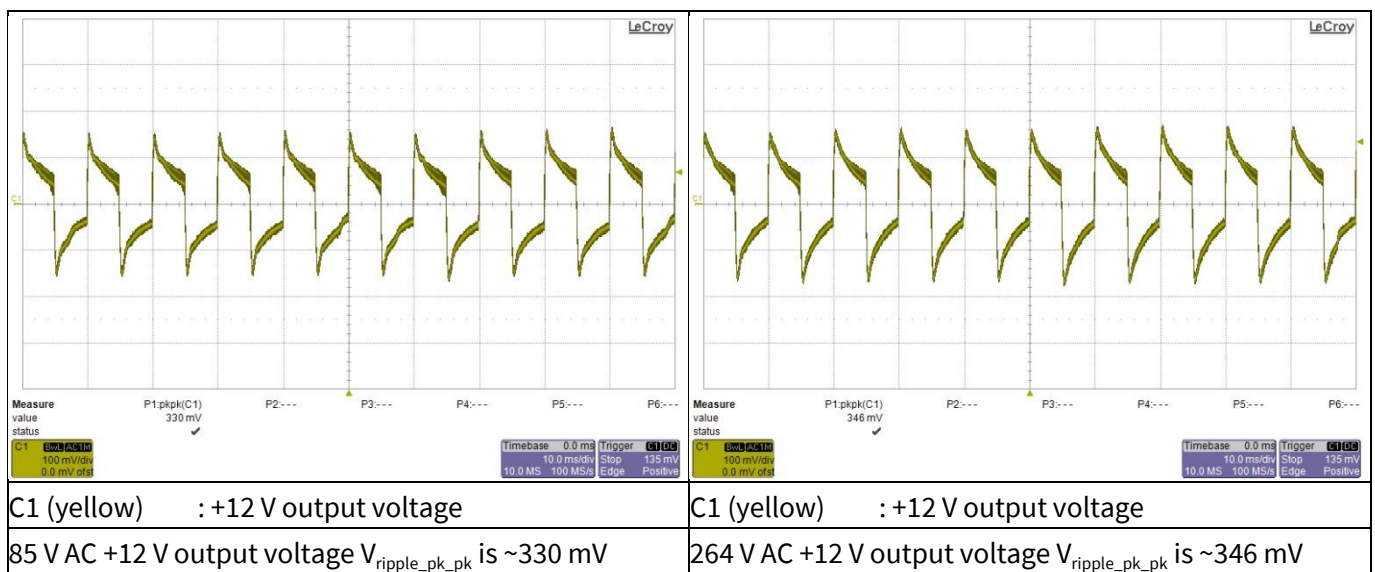


Figure 25 Load transient response with +12 V output load change from 10 percent to 100 percent at 0.4 A/ μs slew rate, 100 Hz. Probe terminals are connected on the PCB end and decoupled with 1 μF electrolytic and 0.1 μF ceramic capacitors. Oscilloscope is bandwidth filter limited to 20 MHz.

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Waveforms and oscilloscope plots

10.7 Entering ABM

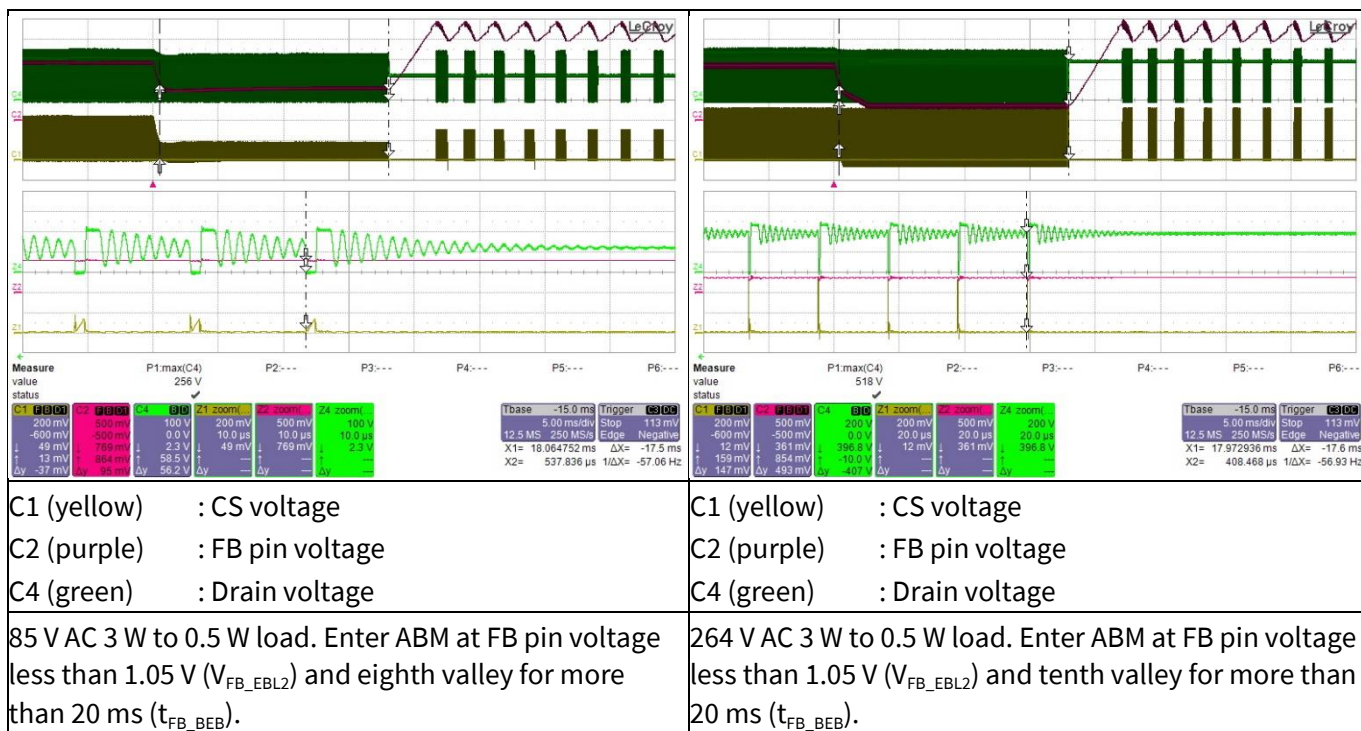


Figure 26 Entering ABM. Output at 3 W to 0.5 W load.

10.8 During ABM

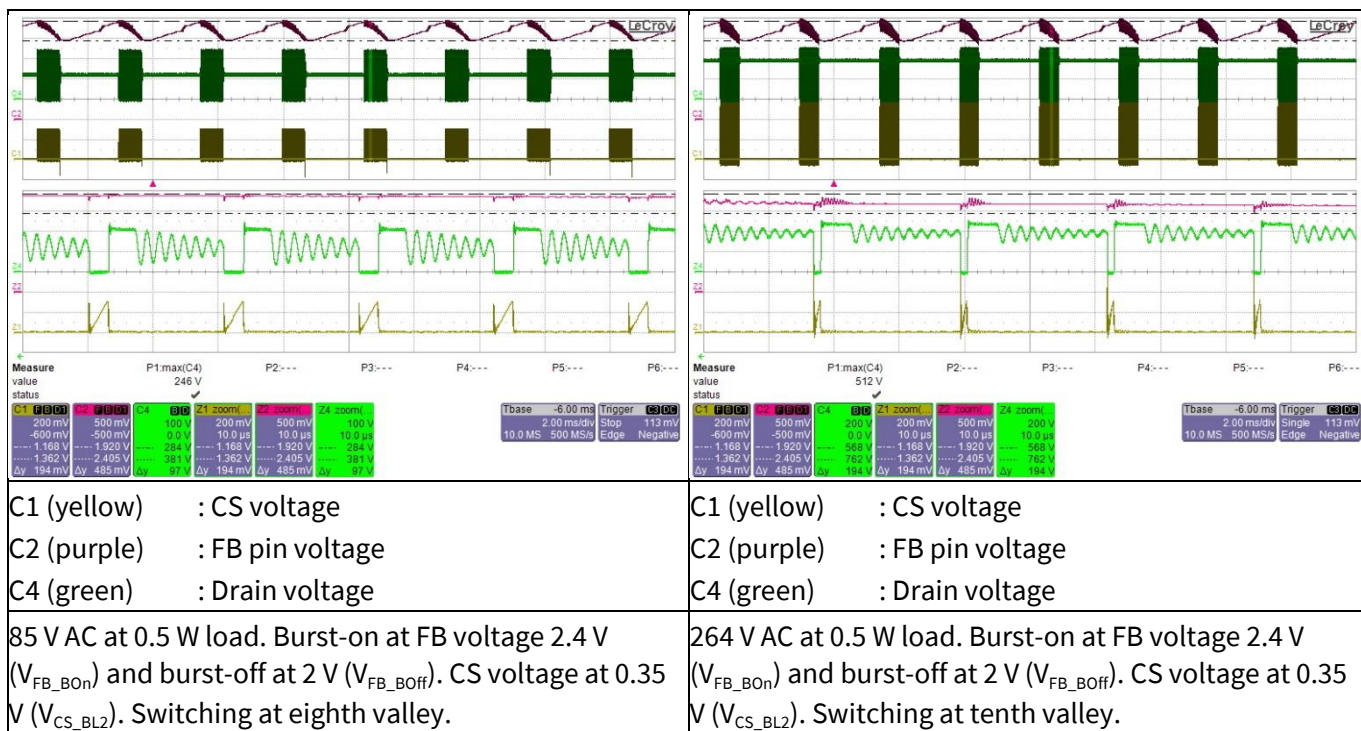


Figure 27 During ABM. Output at 0.5 W load.

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Waveforms and oscilloscope plots

10.9 Leaving ABM

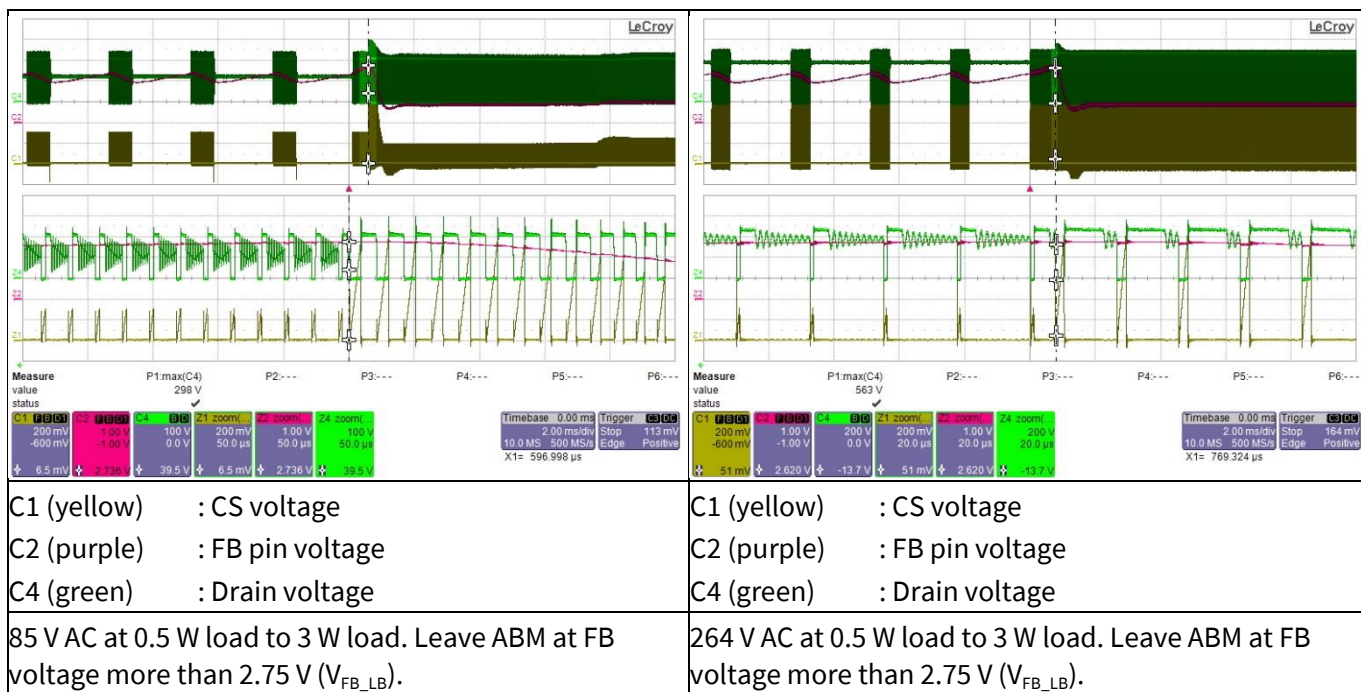


Figure 28 Leaving ABM. Output at 0.5 W load to 3 W load.

10.10 Over-load protection


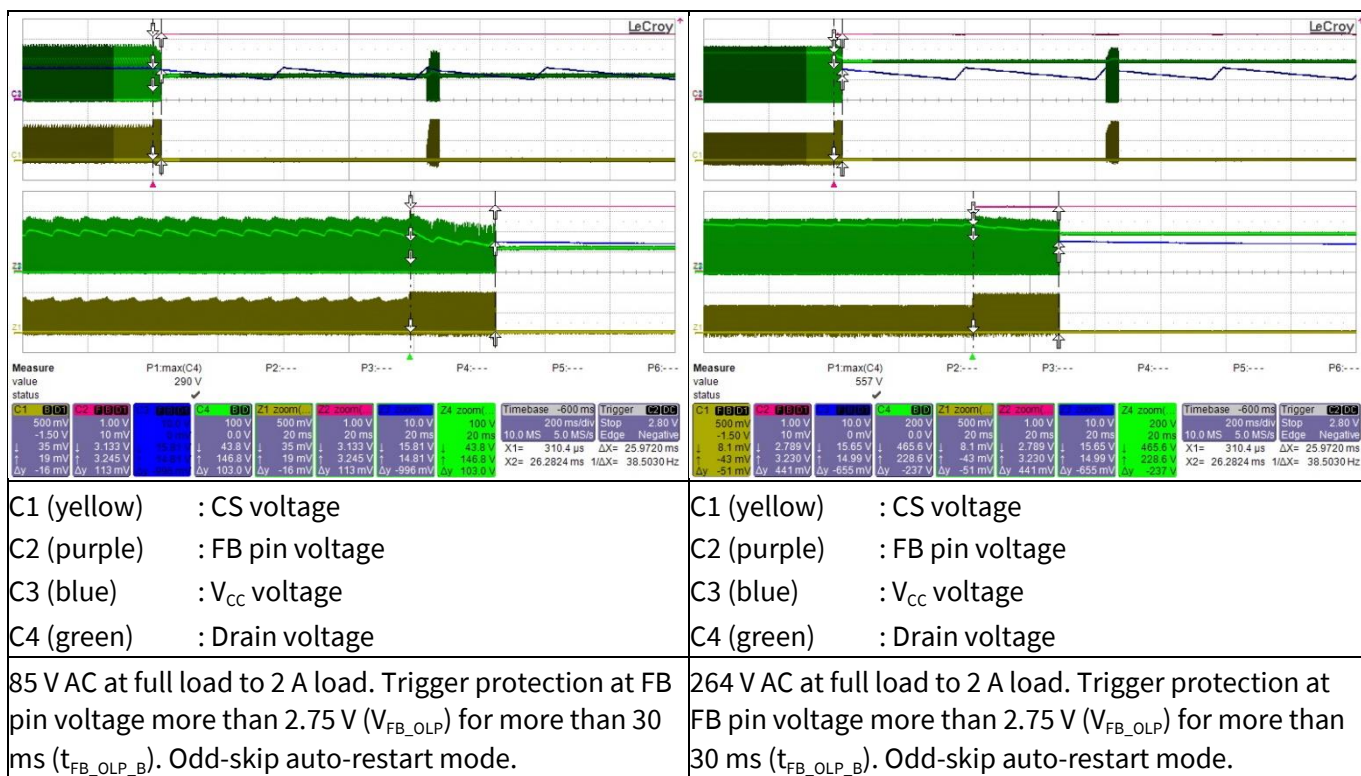


Figure 29 Over-load protection. Load increased from full load to 2 A load to trigger protection.

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Waveforms and oscilloscope plots

10.11 Output over-voltage protection

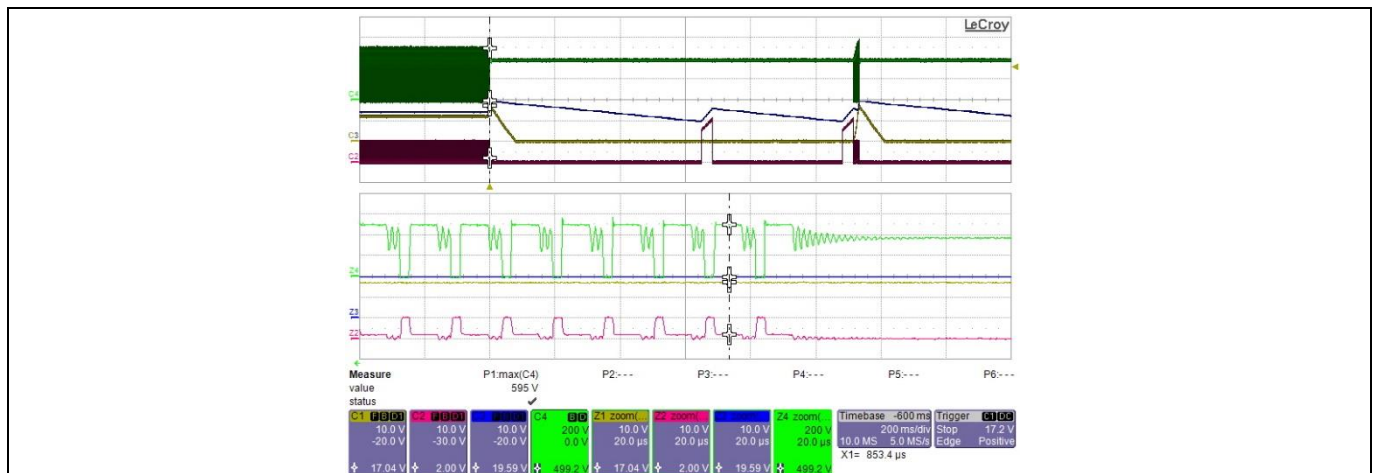


- C1 (yellow) : +12 V output voltage
- C2 (purple) : ZCD pin voltage
- C3 (blue) : V_{CC} voltage
- C4 (green) : Drain voltage

264 V AC 3 W load output over-voltage at ZCD more than 2 V (V_{ZCD_OVP}) for 10 consecutive pulses. Protection triggered at ~17 V output voltage and V_{CC} voltage at ~19.6 V. Odd-skip auto-restart mode.

Figure 30 Output over-voltage protection


10.12 Brown-in/brown-out protection

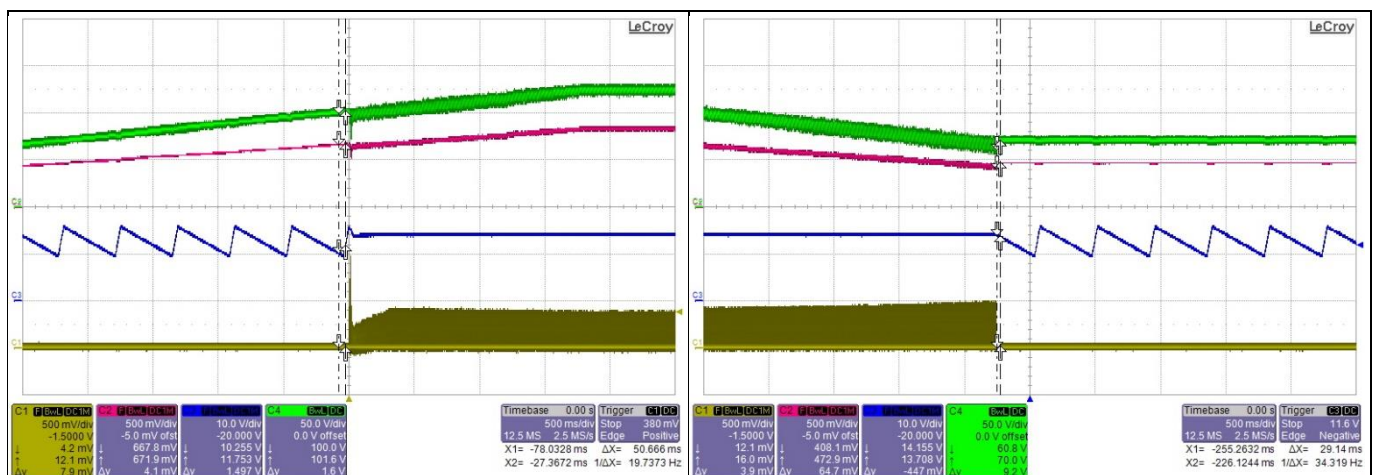

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Waveforms and oscilloscope plots

10.13 Input line OVP

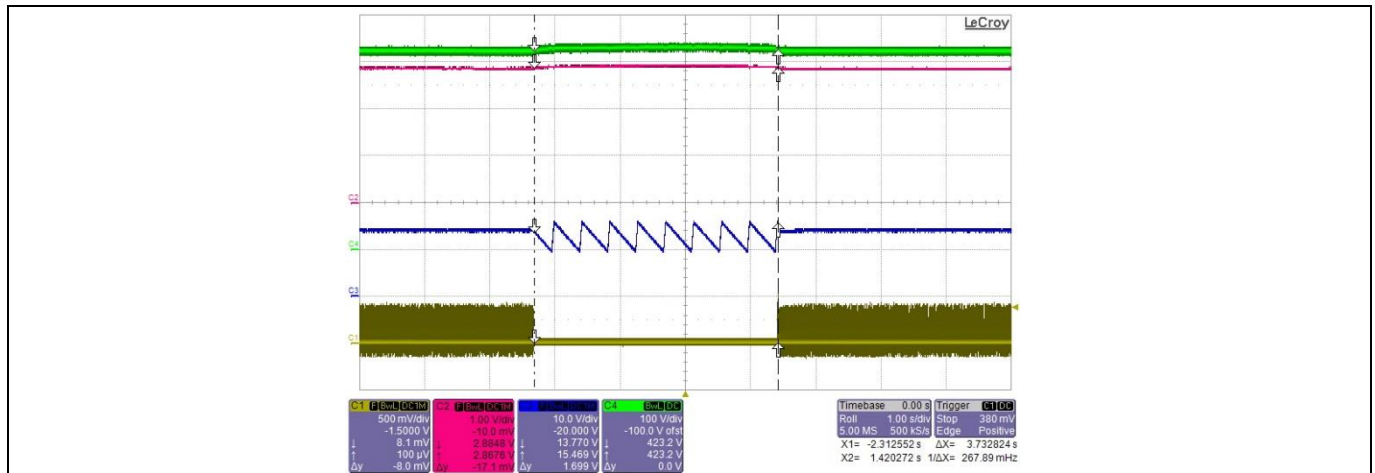

C1 (yellow) : CS voltage
 C2 (purple) : VIN pin voltage
 C3 (blue) : V_{CC} voltage
 C4 (green) : V_{BUS} voltage

AC voltage increasing and decreasing at 3 W load. Shut-down and restart at VIN voltage 2.9 V (V_{VIN_LOVP}) and V_{BUS} at 423 V (300 V AC). Non-switch auto-restart mode.

Figure 32 Input line over-voltage protection at 3 W

11 Appendix A: Transformer design and spreadsheet [3]

Design procedure for QR Flyback converter using Q5 CoolSET™ 5QrxxxxAx (version 1.1)


| | |
|--------------|---|
| Project: | 12 W auxiliary SMPS for refrigerator using ICE5QR2270AZ |
| Application: | 85 to 264 V AC, 12 V/1 A single-output FB |
| CoolSET: | ICE5QR2270AZ |
| Date: | |
| Revision: | |

Enter design variables in orange colored cells

Read design results in green colored cells

Equation numbers are according to the application note

| | | | Unit | Value |
|--------|---|--------------------|------|-------|
| Input | Minimum AC input voltage | $V_{AC\ Min}$ | [V] | 85 |
| Input | Maximum AC input voltage | $V_{AC\ Max}$ | [V] | 264 |
| Input | Line frequency | f_{AC} | [Hz] | 60 |
| Input | Bus capacitor (C13) DC ripple voltage | $V_{DC\ Ripple}$ | [V] | 26 |
| Input | Output voltage 1 | V_{Out1} | [V] | 12 |
| Input | Output current 1 | I_{Out1} | [A] | 1.00 |
| Input | Forward voltage of output diode (D21) | $V_{F\ Out1}$ | [V] | 0.3 |
| Input | Output ripple voltage | $V_{Out\ Ripple}$ | [V] | 0.24 |
| Input | Maximum output power for start-up, transient response and OLP | $P_{Out\ Max}$ | [W] | 12 |
| Result | Nominal output power | $P_{Out\ Nor}$ | [W] | 12.00 |
| Input | Minimum output power | $P_{Out\ Min}$ | [W] | 3 |
| Input | Efficiency | H | | 0.88 |
| Result | Drain-to-source capacitance of MOSFET (including $C_{O(er)}$ of MOSFET) | $C_{DS}+C_{O(er)}$ | [pF] | 10.00 |

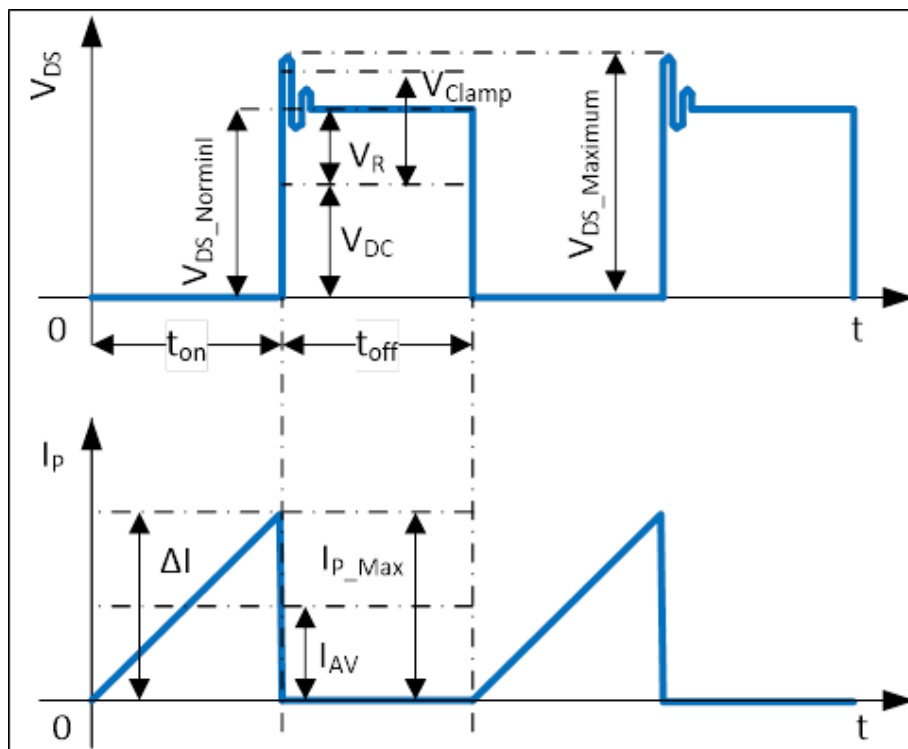

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Appendix A: Transformer design and spreadsheet [3]

| | | | | |
|--------|---|---------------|------|--------------|
| Input | Reflection voltage | V_R | [V] | 85 |
| Input | V_{CC} voltage | V_{VCC} | [V] | 14 |
| Input | Forward voltage of V_{CC} diode (D12) | V_{FVCC} | [V] | 0.6 |
| Result | CoolSET™ | CoolSET™ Q5 | | ICE5QR2270AZ |
| Input | Low-line min. switching frequency | f_S | [Hz] | 55000 |
| Input | Targeted max. drain source voltage | $V_{DS\ Max}$ | [V] | 600 |
| Input | Max. ambient temperature | T_a | [°C] | 50 |

Diode bridge (BR1)

| | | | | |
|--------|-------|-------------------|------|--------|
| Result | Eq 1 | $P_{In\ Max}$ | [W] | 13.64 |
| Result | Eq 2 | $I_{AC\ RMS}$ | [A] | 0.267 |
| Result | Eq 3 | $V_{DC\ Max\ Pk}$ | [V] | 373.35 |
| Result | Eq 4 | $V_{DC\ Min\ Pk}$ | [V] | 120.21 |
| Result | Eq 10 | $V_{DC\ Min}$ | [V] | 95.04 |
| Result | Eq 6 | T_D | [ms] | 6.56 |
| Result | Eq 7 | W_{in} | [Ws] | 0.09 |
| Result | Eq 11 | D_{Max} | | 0.4721 |

Input capacitor (C13)

| | | | | |
|--------|------------------------|----------------|------|-------|
| Result | Eq 8 | C_{in} (C13) | [μF] | 32.07 |
| Input | Select input capacitor | C_{in} (C13) | [μF] | 33 |

Transformer (TR1)

| | | | | |
|--------|-------|--------------|-----|-----------|
| Result | Eq 12 | L_P | [H] | 1.290E-03 |
| Result | Eq 13 | I_{AV} | [A] | 0.30 |
| Result | Eq 14 | ΔI | [A] | 0.632 |
| Result | Eq 15 | $I_{P\ Max}$ | [A] | 0.62 |
| Result | Eq 16 | I_{valley} | [A] | 0.0 |
| Result | Eq 17 | $I_{P\ RMS}$ | [A] | 0.24 |

Select core type

| | | | | |
|--------|----------------------------------|---------------|-------|-----------|
| Input | Select core type | | | 1 |
| Result | | Core type | | EE20/10/6 |
| Result | | Core material | | TP4A(TDG) |
| Result | Maximum flux density | B_{Max} | [T] | 0.3 |
| Result | Effective magnetic cross-section | A_e | [mm²] | 32 |
| Result | Bobbin width | BW | [mm] | 11 |
| Result | Winding cross-section | A_N | [mm²] | 34 |
| Result | Average length of turn | l_N | [mm] | 41.2 |

Winding calculation

| | | | | |
|--------|----------------------------------|-----------|-------|-------|
| Result | Eq 18 | N_P | Turns | 83.33 |
| Input | Choose number of primary turns | N_P | Turns | 84 |
| Result | Eq 19 | N_{S1} | Turns | 12.16 |
| Input | Choose number of secondary turns | N_{S1} | Turns | 12 |
| Result | Eq 20 | N_{VCC} | Turns | 14.24 |
| Input | Choose number of auxiliary turns | N_{VCC} | Turns | 14 |
| Result | Auxiliary supply voltage (Eq 21) | V_{VCC} | [V] | 13.75 |

Post calculation

| | | | | |
|--------|-------|------------|-----|-------|
| Result | Eq 23 | V_R | [V] | 86.10 |
| Result | Eq 24 | D_{Max} | | 0.47 |
| Result | Eq 25 | D_{Max}' | | 0.52 |
| Result | Eq 26 | B_{Max} | [T] | 0.298 |

CS resistor (R14)

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Appendix A: Transformer design and spreadsheet [3]

| | | | | |
|--------------|--|--------------------------|------------|-------------|
| Input | CS threshold value from datasheet | V_{csth} | [V] | 1 |
| Result | Eq 21 | R _{Sense} (R14) | [Ω] | 1.61 |
| Result | Eq 22 | P _{SR} | [W] | 0.10 |
| Input | PWM-OP gain from datasheet | A_v | | 2.05 |
| Result | Eq 94 | Z _{PWM} | [V/A] | 3.3 |

Transformer winding design

| | | | | |
|--------------|--|-----------------------|-------------|------------|
| Input | Margin according to safety standard | M | [mm] | 0 |
| Input | Copper space factor | f_{cu} | | 0.4 |

Primary

| | | | | |
|--------------|---------------------------------|---|----------------------|-------------|
| Input | Insulation thickness | INS | [mm] | 0.02 |
| Result | Eq 32 | A _p (area of primary wire) | [mm ²] | 0.08 |
| Result | Eq 36 | d (diameter of primary wire) | [mm] | 0.32 |
| Result | Eq 35 | AWG | | 28 |
| Input | Selected wire size | AWG | | 32 |
| Input | Number of parallel wires | N_p | | 1 |
| Result | Eq 37 | d (diameter of primary wire) | [mm] | 0.20 |
| Result | Eq 38 | (Eff. copper area of primary) | [mm ²] | 0.0326 |
| Result | Eq 39 | S _p (primary current density) | [A/mm ²] | 7.47 |
| Result | Eq 30 | BW _e (effective bobbin width) | [mm] | 11.0 |
| Result | Eq 40 | Od _p (diameter of primary wire including insulation) | [mm] | 0.24 |
| Result | Eq 41 | NL _p (max. primary turns/layer) | Turns/layer | 45 |
| Result | Eq 42 | Ln _p (primary layers) | layers | 2 |

Secondary

| | | | | |
|--------------|---------------------------------|---|----------------------|-------------|
| Input | Insulation thickness | INS | [mm] | 0.02 |
| Result | Eq 33 | A _s (area of secondary wire) | [mm ²] | 0.51 |
| Result | Eq 36 | d (diameter of secondary wire) | [mm] | 0.81 |
| Result | Eq 35 | AWG | | 20 |
| Input | Selected wire size | AWG | | 27 |
| Input | Number of parallel wires | N_p | | 3 |
| Result | Eq 37 | dia (diameter of secondary wire) | [mm] | 0.36 |
| Result | Eq 38 | (Eff. copper area of secondary) | [mm ²] | 0.3103 |
| Result | Eq 39 | S _s (secondary current density) | [A/mm ²] | 5.81 |
| Result | Eq 30 | BW _e (effective bobbin width) | [mm] | 11.0 |
| Result | Eq 40 | Od _s (diameter of secondary wire including insulation) | [mm] | 0.40 |
| Result | Eq 41 | NL _s (max. secondary turns/layer) | Turns/layer | 9 |
| Result | Eq 42 | Ln _s (secondary layers) | Layers | 2 |

Leakage inductance

| | | | | |
|--------------|-------|--|------------|----------|
| Input | | Leakage Inductance as percentage of L_p | [%] | 1 |
| Result | Eq 45 | L _{LK} | [H] | 1.29E-05 |

RCD clamping circuit (D11, R11 and C15)

| | | | | |
|--------------|---|--------------------------------|-------------|-------------|
| Result | Eq 44 | V _{clamp} | [V] | 140.55 |
| Result | Eq 46 | C _{clamp} (C15) | [nF] | 0.2 |
| Input | Selected C_{clamp} capacitor value | C_{clamp} (C15) | [nF] | 0.22 |
| Result | Eq 47 | R _{clamp} (R11) | [kΩ] | 322.2 |
| Input | Selected R_{clamp} value | R_{clamp} (R11) | [kΩ] | 240 |

Output and V_{CC} diode (D21, D22 and D12)

| | | | | |
|--------|--------|---|-----|-------|
| Result | Eq 43a | V _{RDiode1} (for output diode D21) | [V] | 65.34 |
|--------|--------|---|-----|-------|

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Appendix A: Transformer design and spreadsheet [3]

| | | | | |
|--------|--------|-----------------------------------|-----|-------|
| Result | Eq 28 | $I_{S\ Max1}$ | [A] | 4.34 |
| Result | Eq 29 | $I_{S\ RMS1}$ | [A] | 1.80 |
| Result | Eq 43b | V_{Rdiode} (for V_{CC} diode) | [V] | 76.23 |

Output capacitor (C22 and C23)

| | | | | |
|--------|---|------------------|------------|------|
| Input | Max. voltage overshoot at output capacitor (C22, C23) | ΔV_{Out} | [V] | 0.36 |
| Input | Number of clock periods | n_{cp} | | 20 |
| Result | Eq 49 | I_{Ripple} | [A] | 1.50 |
| Result | Eq 50 | C_{Out} | [μ F] | 1010 |

Zero frequency of output capacitor (C22 and C23) and associated ESR

| | | | | |
|--------|---|-------------|--------------|-------|
| Input | Selected output capacitor value | C22 | [μ F] | 1000 |
| Input | ESR (Z_{max}) value from datasheet at 100 kHz | ESR | [Ω] | 0.018 |
| Input | I_{ACmax} value from datasheet at 100 kHz | I_{acmax} | [Arms] | 1.76 |
| Input | Number of parallel capacitors | n_c | | 1 |
| Result | Eq 51 | f_{ZCOut} | [kHz] | 8.84 |

Ripple voltage first stage

| | | | | |
|--------|-----------------------------------|-----------------|------------|------|
| Result | Eq 52 | $V_{Ripple\ 1}$ | [V] | 0.08 |
| Input | Selected LC filter inductor value | L_{out} (L21) | [μ H] | 2.2 |

Calculating the necessary capacitance for the output LC-filter (C24)

| | | | | |
|--------|----------------------------------|----------------|------------|-------|
| Result | Eq 53 | C_{LC} (C24) | [μ F] | 147.3 |
| Input | Selected output inductance value | C_{LC} (C24) | [μ F] | 220 |
| Result | Eq 54 | f_{LC} | [kHz] | 7.23 |

Ripple voltage second stage

| | | | | |
|--------|-------|-----------------|------|------|
| Result | Eq 55 | $V_{Ripple\ 2}$ | [mV] | 1.33 |
|--------|-------|-----------------|------|------|

Soft-start time

| | | | | |
|-------|---------------------------------------|-----------------|------|----|
| Input | Chosen soft-start time from datasheet | $t_{softstart}$ | [ms] | 12 |
|-------|---------------------------------------|-----------------|------|----|

V_{CC} capacitor (C16) and start-up time

| | | | | |
|--------|---|-------------------|------------|---------|
| Input | Chosen $I_{VCC,Charge3}$ from datasheet | $I_{VCC,Charge3}$ | [mA] | 3 |
| Input | Chosen $V_{VCCchys}$ from datasheet | $V_{VCCchys}$ | [mV] | 6 |
| Result | Eq 56A | C_{VCC} | [μ F] | 6.00 |
| Input | Select V_{CC} capacitor | C_{VCC} (C16) | [μ F] | 22 |
| Input | Select $V_{VCC,STG}$ from datasheet | $V_{VCC,STG}$ | [V] | 1.1 |
| Input | Select $I_{VCC,Charge1}$ from datasheet | $I_{VCC,Charge1}$ | [mA] | 0.2 |
| Input | Select $V_{VCC,ON}$ from datasheet | $V_{VCC,ON}$ | [V] | 16 |
| Result | Eq 56B | $t_{StartUp}$ | [ms] | 238.333 |

Calculation of losses

Input diode bridge

| | | | | |
|--------|-------|-----------|-----|------|
| Result | Eq 57 | P_{DIN} | [W] | 0.53 |
|--------|-------|-----------|-----|------|

Transformer copper losses

| | | | | |
|--------|-------|-----------|---------------|---------|
| Result | Eq 58 | R_{PCu} | [m Ω] | 1826.18 |
| Result | Eq 58 | R_{SCu} | [m Ω] | 27.40 |
| Result | Eq 59 | P_{PCu} | [mW] | 108.37 |
| Result | Eq 60 | P_{SCu} | [mW] | 89.09 |
| Result | Eq 61 | P_{Cu} | [W] | 0.1975 |

Output rectifier diode

| | | | | |
|--------|-------|------------------------|-----|------|
| Result | Eq 62 | $P_{Out\ DIODE}$ (D21) | [W] | 0.54 |
|--------|-------|------------------------|-----|------|

RCD clamper circuit

| | | | | |
|--------|-------|---------------|-----|------|
| Result | Eq 63 | $P_{clamper}$ | [W] | 0.22 |
|--------|-------|---------------|-----|------|

MOSFET

| | | | | |
|-------|-----------------------------|---|--------------|------|
| Input | $R_{DS(on)}$ from datasheet | $R_{DS(on)}$ at $T_A = 125^\circ\text{C}$ | [Ω] | 4.31 |
|-------|-----------------------------|---|--------------|------|

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Appendix A: Transformer design and spreadsheet [3]

| | | | | |
|-------|--|--------------------|------|----|
| Input | C _{o(er)} from datasheet | C _{o(er)} | [pF] | 10 |
| Input | External drain-to-source capacitance of MOSFET | C _{ds} | [pF] | 0 |

MOSFET losses at V_{ACmin} + P_{max}

| | | | | |
|--------|-------|-------------------|-----|-------------|
| Result | Eq 65 | P _{SON} | [W] | 0.000021967 |
| Result | Eq 66 | P _{cond} | [W] | 0.2558 |
| Result | Eq 67 | MOSFET losses | [W] | 0.2558 |

MOSFET losses at V_{ACmax} + P_{max}

| | | | | |
|--------|-------|-------------------|-----|--------|
| Result | Eq 68 | P _{SON} | [W] | 0.0295 |
| Result | Eq 69 | P _{cond} | [W] | 0.0846 |
| Result | Eq 70 | MOSFET losses | [W] | 0.1141 |

Temperature calculation

| | | | | |
|--------|---|-------------------|--------|-------|
| Input | Enter MOSFET losses | MOSFET losses | [W] | 0.26 |
| Input | Enter thermal resistance junction – ambient | R _{th} | [°K/W] | 103.0 |
| Result | Eq 74 | ΔT | [°K] | 26.3 |
| Result | Eq 75 | T _{jmax} | °C | 76.3 |

Controller

| | | | | |
|--------|--|-------------------|-----|--------|
| Result | I _{VCC,Normal} × V _{VCC} | Controller losses | [W] | 0.0124 |
|--------|--|-------------------|-----|--------|

Sum of losses

| | | | | |
|--------|-------|---------------------|-----|------|
| Result | Eq 77 | P _{Losses} | [W] | 1.76 |
|--------|-------|---------------------|-----|------|

Efficiency after losses

| | | | | |
|--------|-------|----------------|--|--------|
| Result | Eq 78 | η _L | | 0.8720 |
|--------|-------|----------------|--|--------|

Calculation of the regulation loop (R22, R23, R24, R25, R26, C25, C26)

| | | | | |
|--------|--|------------------------------------|-------|--------|
| Input | Min. current for TL431 reference | I _{KAmin} | [mA] | 1 |
| Input | Optocoupler gain | G _C (200 percent) | | 1.5 |
| Input | Max. current for optocoupler diode | I _{Fmax} | [mA] | 10 |
| Input | Second resistor of TL431 voltage divider | R26 | [kΩ] | 12.2 |
| Input | 0 db crossover frequency | F _g | [kHz] | 3 |
| Result | Eq 81 | R25 | [kΩ] | 46.36 |
| Input | Selected value of R25 | R25 | [kΩ] | 47 |
| Result | Eq 82 | R22 | [kΩ] | 0.8250 |
| Input | Selected value of R22 | R22 | [kΩ] | 0.82 |
| Input | V _{REF} from datasheet | V _{REF} | [V] | 3.3 |
| Input | V _{FB,OLP} from datasheet (over-load/open-loop detection limit at FB pin) | V _{FB,OLP} | [V] | 2.75 |
| Input | R _{FB} from datasheet | R _{FB} | [kΩ] | 15 |
| Result | Eq 83 | R23 | [kΩ] | 1.27 |
| Input | Selected value of R23 | R23 | [kΩ] | 1.2 |
| Result | Eq 84 | V _{OUT,RL} | [V] | 12.1 |
| Result | Eq 85 | K _{FB} | | 27.44 |
| Result | Eq 86 | G _{FB} | [db] | 28.77 |
| Result | Eq 87 | K _{VD} | | 0.21 |
| Result | Eq 88 | G _{VD} | [db] | -13.72 |
| Result | Eq 89 | R _{LH} | [Ω] | 12.00 |
| Result | Eq 90 | R _{LL} | [Ω] | 48.00 |
| Result | Eq 91 | f _{OH} | [Hz] | 26.53 |
| Result | Eq 92 | f _{OL} | [Hz] | 6.63 |
| Result | Eq 93 | f _{OM} | [Hz] | 13.26 |
| Result | Eq 95 | F _{PWR} (f _g) | | 0.052 |
| Result | Eq 96 | G _{PWR} (f _g) | [db] | -25.72 |
| Result | Eq 99 | Gr | [db] | 10.671 |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Appendix A: Transformer design and spreadsheet [3]

| | | | | |
|--------|-----------------------|-----|------|--------|
| Result | Eq 100 | R24 | [kΩ] | 33.09 |
| Input | Selected value of R24 | R24 | [kΩ] | 33 |
| Result | Eq 101 | C26 | [nF] | 1.608 |
| Input | Selected value of C26 | C26 | [nF] | 1 |
| Result | Eq 102 | C25 | [nF] | 362.64 |
| Input | Selected value of C25 | C25 | [nF] | 470 |

Zero crossing detection and output OVP calculation

| | | | | |
|--------|-----------------------------------|--------------------|-------|-------|
| Input | Designed V_{OUT_OVP} | V_{OUT_OVP} | [V] | 16 |
| Input | $V_{ZC_OVP_MIN}$ from datasheet | $V_{ZC_OVP_MIN}$ | [V] | 1.9 |
| Input | R_{ZCD_MIN} from datasheet | R_{ZCD} | [kΩ] | 3 |
| Result | Eq 103 | R_{ZC} (R15) | [kΩ] | 27.03 |
| Input | Selected value of R15 | R_{ZC} (R15) | [kΩ] | 27 |
| Input | f_{OSC2} by measurement | f_{OSC2} | [kHz] | 1000 |
| Result | Eq 104 | C_{ZC} (C19) | [pF] | 81 |
| Input | Selected value of C_{ZC} (C19) | C_{ZC} (C19) | [pF] | 47 |

Line OVP is the first priority and its associated brown-out, brown-in and line selection

| | | | | |
|--------|------------------------------------|--|--------|-----------|
| Input | | R_{I1} (R18) | [Ω] | 9,000,000 |
| Input | | Line over-voltage (V_{OVP_AC}) | [V AC] | 300 |
| Input | | V_{DC} Ripple | [V] | 26 |
| Result | Eq 105A | R_{I2} (R19) | [Ω] | 61,942 |
| Input | Selected value of R19 (R_{I2}) | R_{I2} (R19) | [Ω] | 62,000 |
| Result | Eq 106 | Brown-in voltage ($V_{Brownin_AC}$) | [V AC] | 68 |
| Result | Eq 107 | Brown-out voltage for full load which considers V_{DC} RIPPLE ($V_{Brownout_AC}$) | [V AC] | 60 |
| Result | Eq 107 | Brown-out voltage for light load which neglects V_{DC} RIPPLE ($V_{Brownout_AC}$) | [V AC] | 41 |
| Result | Eq 108 | Line selection threshold with V_{DC} RIPPLE ($V_{VIN} = 1.52$ V) | [V AC] | 175 |
| Result | Eq 108 | Line selection threshold without V_{DC} RIPPLE ($V_{VIN} = 1.52$ V) | [V AC] | 157 |

Brown-out is the first priority and its associated line OVP and line selection

| | | | | |
|--------|------------------------------------|--|--------|-----------|
| Input | | R_{I1} (R18) | [Ω] | 9,000,000 |
| Input | | Brown-in voltage (V_{OVP_AC}) | [V AC] | 70 |
| Input | | V_{DC} Ripple | [V] | 26 |
| Result | Eq 105B | R_{I2} (R19) | [Ω] | 60,406 |
| Input | Selected value of R19 (R_{I2}) | R_{I2} (R19) | [Ω] | 62 |
| Result | Eq 107 | Brown-out voltage for full load which considers V_{DC} RIPPLE ($V_{Brownout_AC}$) | [V AC] | 41076 |
| Result | Eq 107 | Brown-out voltage for light load which neglects V_{DC} RIPPLE ($V_{Brownout_AC}$) | [V AC] | 41058 |
| Result | Eq 114 | Line over-voltage (V_{OVP_AC}) | [V AC] | 297671 |
| Result | Eq 108 | Line selection threshold with V_{DC} RIPPLE ($V_{VIN} = 1.52$ V) | [V AC] | 156039 |
| Result | Eq 108 | Line selection threshold without V_{DC} RIPPLE ($V_{VIN} = 1.52$ V) | [V AC] | 156021 |

Electrical

| | | | |
|-----------------------|--|-----|------|
| Minimum AC voltage | | [V] | 85 |
| Maximum AC voltage | | [V] | 264 |
| Maximum input current | | [A] | 0.16 |
| Minimum DC voltage | | [V] | 95 |
| Maximum DC voltage | | [V] | 373 |
| Maximum output power | | [W] | 12.0 |
| Output voltage | | [V] | 12.0 |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ



Appendix A: Transformer design and spreadsheet [3]

| | | | |
|--------------------------|--|------|-------------|
| Output ripple voltage | | [mV] | 1.3 |
| Inductor peak current | | [A] | 0.62 |
| Maximum duty cycle | | | 0.47 |
| Reflected output voltage | | [V] | 86 |
| Copper losses | | [W] | 0.20 |
| MOSFET losses | | [W] | 0.26 |
| Sum of losses | | [W] | 1.76 |
| Efficiency | | | 0.87 |

Transformer

| | | | |
|------------------------------------|--|--------------------|------------------|
| Core type | | | EE20/10/6 |
| Core material | | | TP4A(TDG) |
| Effective core area | | [mm ²] | 32 |
| Maximum flux density | | [mT] | 298 |
| Inductance | | [μH] | 1290 |
| Magin | | [mm] | 0 |
| Primary turns | | Turns | 84 |
| Primary copper wire size | | AWG | 32 |
| Secondary turns (N _{S1}) | | Turns | 12 |
| Secondary copper wire size | | AWG | 27 |
| Number of parallel secondary wires | | | 3 |
| Auxiliary turns | | Turns | 14 |
| Leakage inductance | | [μH] | 12.9 |
| Turns ratio | | | 7.00 |
| Primary layers | | Layer | 2 |
| Secondary layers | | Layer | 2 |

Components

| | | | |
|---------------------------|-----|------|---------------|
| Input capacitor | C13 | [μF] | 33.0 |
| Output capacitor | C22 | [μF] | 1000.0 |
| LC filter capacitor | C24 | [μF] | 220.0 |
| LC filter inductor | L21 | [μH] | 2.2 |
| V _{CC} capacitor | C16 | [μH] | 22.0 |
| ZC capacitor | C19 | [pF] | 47 |
| ZC resistor | R15 | [kΩ] | 27 |
| Sense resistor | R14 | [Ω] | 1.61 |
| Clamping resistor | R11 | [kΩ] | 240.0 |
| Clamping capacitor | C15 | [nF] | 0.22 |
| Voltage divider | R25 | [kΩ] | 46.4 |
| Voltage divider | R26 | [kΩ] | 12.2 |
| Regulator component | R22 | [kΩ] | 0.82 |
| Regulator component | R23 | [kΩ] | 1.2 |
| Regulator component | R24 | [kΩ] | 33.0 |
| Regulator component | C25 | [nF] | 470.0 |
| Regulator component | C26 | [nF] | 1.00 |

12 W auxiliary SMPS for energy efficient refrigerator using ICE5QR2270AZ

Appendix B: WE transformer specification

12 Appendix B: WE transformer specification

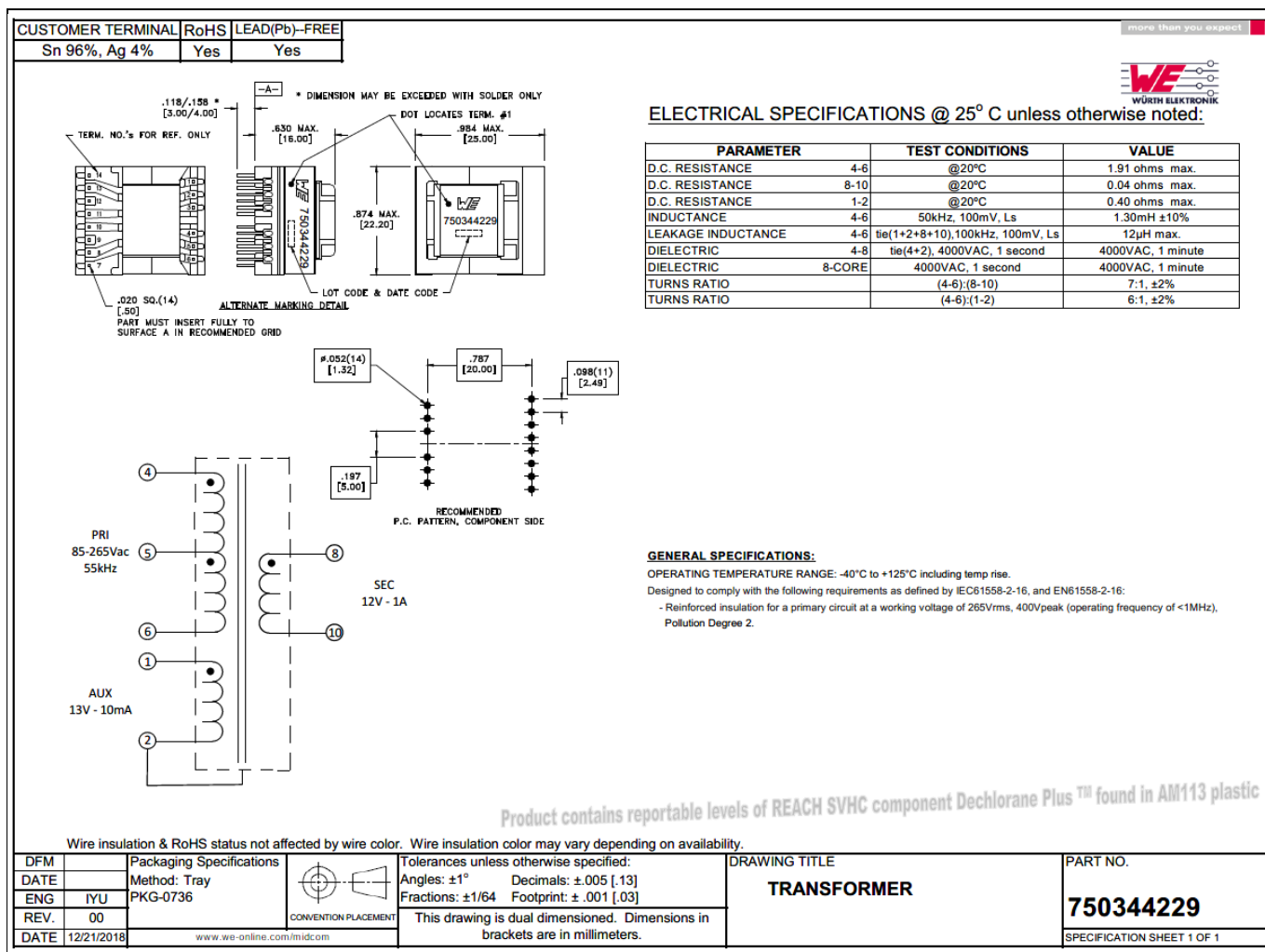


Figure 33 WE transformer specification

References

13 References

- [1] [ICE5QRxxxxAx datasheet, Infineon Technologies AG](#)
- [2] [AN-201609_PL83_026-5th Generation QR Design Guide](#)
- [3] [Calculation Tool Quasi Resonant CoolSET™ Generation 5](#)

Revision history

| Document version | Date of release | Description of changes |
|-------------------------|------------------------|-------------------------------|
| Rev. 1.0 | 2019-03-26 | First release |
| | | |
| | | |

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2019-03-26

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2019 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference

AN_1903_PL83_1904_083141

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.