

Fifth-generation fixed-frequency design guide

Design guide - ICE5ARxxxxBZS

About this document

Scope and purpose

This document is a design guide for a fixed-frequency flyback converter using Infineon's newest fifth-generation fixed-frequency CoolSET™, ICE5ARxxxxBZS, which offer high-efficiency, low-standby power with selectable entry and exit standby power options, wider V_{CC} operating range with fast start-up, and various protection modes for a highly reliable system.

Intended audience

This document is intended for power-supply design/application engineers, students, etc. who wish to design power supplies with Infineon's newest fifth-generation fixed-frequency CoolSET™, ICE5ARxxxxBZS.

Table of contents

About this document.....	1
Table of contents.....	1
1 Abstract	3
2 Description.....	4
2.1 List of features	4
2.2 Pin configuration and functionality.....	4
3 Overview of fixed-frequency flyback converter	6
4 Functional description and component design	7
4.1 V_{CC} pre-charging and typical V_{CC} voltage during start-up	7
4.1.1 V_{CC} capacitor	8
4.2 Soft-start.....	8
4.3 Normal operation.....	9
4.3.1 PWM operation and peak current mode control	9
4.3.1.1 Switch-on determination.....	9
4.3.1.2 Switch-off determination	9
4.3.2 Current sensing	10
4.3.3 Frequency reduction	11
4.3.4 Slope compensation	11
4.3.5 Oscillator and frequency jittering.....	12
4.3.6 Modulated gate drive	12
4.4 Peak Current Limitation (PCL)	13
4.4.1 Propagation delay compensation	13
4.5 ABM with selectable power level	14
4.5.1 Entering ABM operation.....	15
4.5.2 During ABM operation	15
4.5.3 Leaving ABM operation	15
4.5.4 ABM configuration.....	17
4.6 Non-isolated/isolated configuration.....	17
4.6.1 Non-isolated FB.....	18

Abstract

4.6.2	Isolated FB.....	18
4.7	Protection functions	19
4.7.1	V _{CC} OV/UV	20
4.7.2	Over-load/open-loop	20
4.7.3	Over-temperature	20
4.7.4	CS short-to-GND	20
4.7.5	V _{CC} short-to-GND.....	20
4.7.6	Protection modes.....	20
5	Typical application circuit	23
6	PCB layout recommendation	24
7	Output power of fifth-generation fixed-frequency ICs	25
8	Fifth-generation fixed-frequency FLYCAL design example	27
8.1	Pre-calculation	27
8.2	Input diode bridge (BR1).....	28
8.3	Input capacitor (C1).....	28
8.4	Transformer design (T1).....	30
8.5	Post calculation.....	32
8.6	Transformer winding design.....	33
8.6.1	Primary winding	33
8.6.2	Secondary 1 winding (V _{Out1}).....	34
8.6.3	Secondary 2 winding (V _{Out2}).....	35
8.7	Clamping network	36
8.8	CS resistor.....	37
8.9	Output rectifier.....	37
8.9.1	Output 1.....	37
8.9.2	Output 2.....	38
8.10	V _{CC} diode and capacitor.....	39
8.11	Calculation of losses.....	40
8.12	CoolSET™/MOSFET temperature.....	41
8.13	Output regulation (non-isolated)	41
9	References	42
	Revision history.....	43

Abstract

1 Abstract

This design guide is for a fixed-frequency flyback converter using Infineon's newest fifth-generation fixed-frequency CoolSET™, ICE5ARxxxxBZS.

The IC is optimized for off-line SMPS applications including home appliances/white goods, TVs, PCs, servers, Blu-ray players, set-top boxes and notebook adapters. The frequency reduction with soft gate-driving and frequency-jitter operation offers lower EMI and better efficiency between light and medium loads. The selectable entry/exit standby power Active Burst Mode (ABM) enables flexibility and low power consumption in standby mode with small and controllable output voltage ripple. The product has a wide operating range (10~25.5 V) of IC power supply and lower power consumption. The numerous protection functions give full protection to the power supply system in failure situations. All of these features make the ICE5ARxxxxBZS an outstanding CoolSET™ for fixed-frequency flyback converters.

Description

2 Description

2.1 List of features

- Integrated 700 V/800 V avalanche rugged CoolMOS™
- Enhanced ABM with selectable entry and exit standby power
- Digital frequency reduction for better overall system efficiency
- Fast start-up, achieved with cascode configuration
- Discontinuous Conduction Mode (DCM) and Continuous Conduction Mode (CCM) operation with slope compensation
- Frequency jitter and soft gate-driving for low EMI
- Built-in digital soft-start
- Cycle-to-cycle Peak Current Limitation (PCL)
- Integrated error amplifier to support direct feedback (FB) in a non-isolated flyback converter
- Comprehensive protection with V_{CC} OV, V_{CC} Under Voltage (UV), over-load/open-loop, over-temperature and Current Sense (CS) short-to-GND
- All protections are in auto-restart mode
- Limited charging current for V_{CC} short-to-GND
- Pb-free lead plating, halogen-free mold compound, RoHS compliant

2.2 Pin configuration and functionality

The pin configuration is shown in Figure 1 and the functions are described in Table 1.

 


Figure 1 Pin configuration

Table 1 Pin definitions and functions

Pin	Symbol	Function
1	VERR	Error amplifier The VERR pin is internally connected to the transconductance error amplifier for non-isolated flyback applications. Connect this pin to GND for isolated flyback applications.

Description

Pin	Symbol	Function
2	FB	FB and ABM entry/exit control The FB pin combines the functions of FB control, selectable burst entry/exit control and over-load/open-loop protection.
3	CS	CS The CS pin is connected to the shunt resistor for the primary current sensing externally and to the PWM signal generator block for switch-off determination (together with the FB voltage) internally. CS short-to-GND protection is also sensed via this pin.
4	GATE	Gate driver output The GATE pin is connected to the gate of the power MOSFET, and a pull-up resistor is connected from the bus voltage to turn on the power MOSFET for charging up the V_{CC} capacitor during start-up.
5	DRAIN	Drain (drain of integrated CoolMOS™) The DRAIN pin is connected to the drain of the integrated CoolMOS™.
7	V_{CC}	V_{CC} (positive voltage supply) The V_{CC} pin is the positive voltage supply to the IC. The operating range is between V_{VCC_OFF} and V_{VCC_OVP} .
8	GND	Ground The GND pin is the common ground of the controller.

3 Overview of fixed-frequency flyback converter

Figure 2 show the typical application of ICE5ARxxxxBZS in an isolated fixed-frequency flyback converter using TL431 and an optocoupler.

Figure 3 show the typical application of ICE5ARxxxxBZS in a non-isolated fixed-frequency flyback converter using an integrated error amplifier.

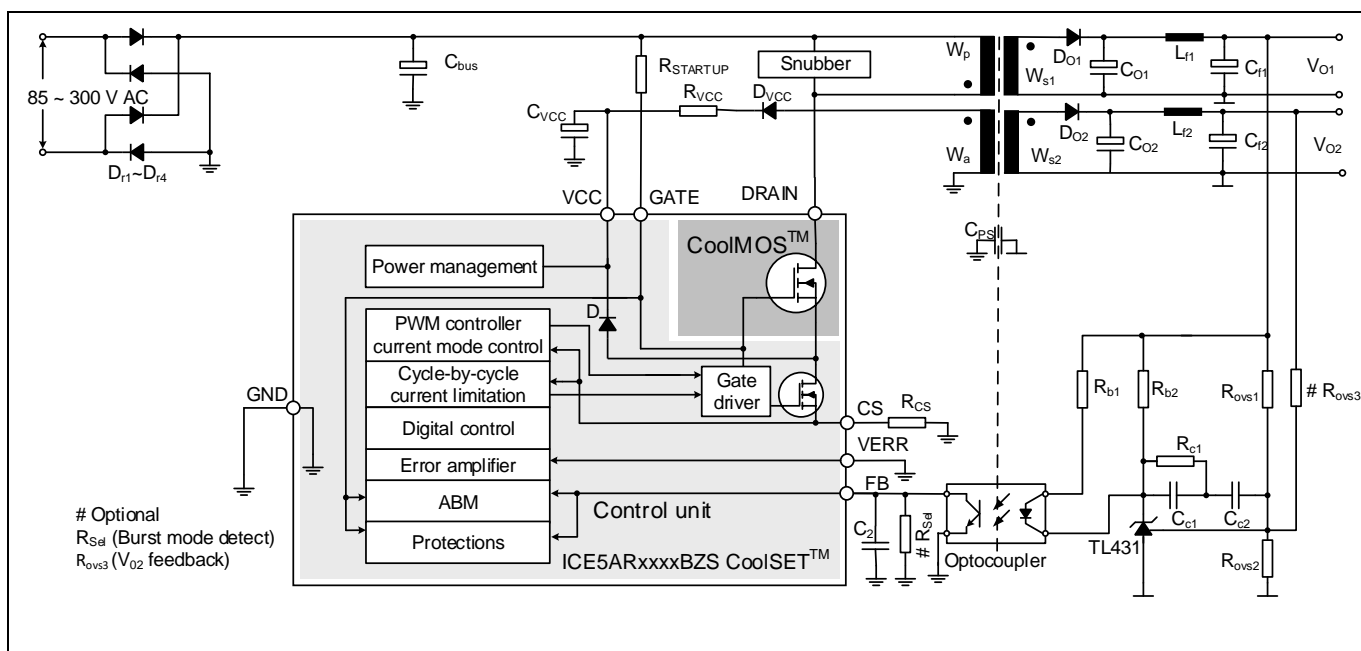


Figure 2 Typical application in an isolated fixed-frequency flyback converter using TL431 and an optocoupler

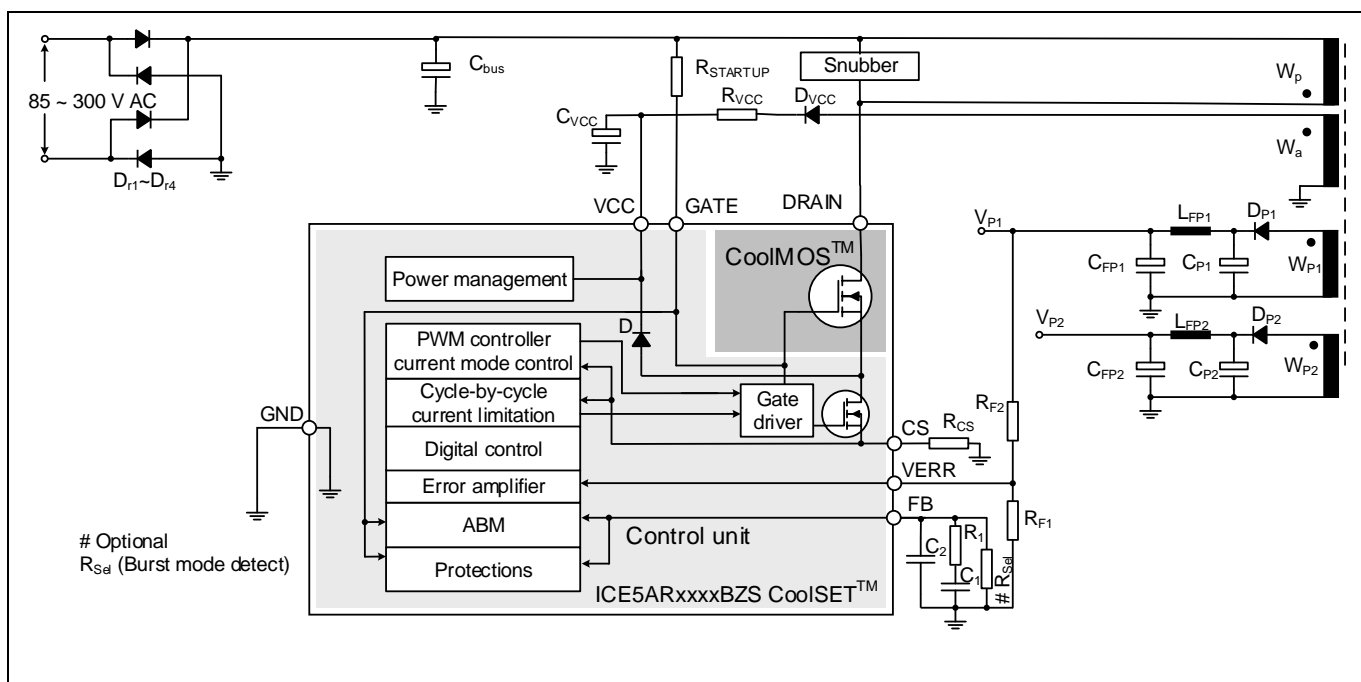


Figure 3 Typical application in a non-isolated flyback converter using an integrated error amplifier

4 Functional description and component design

4.1 V_{CC} pre-charging and typical V_{CC} voltage during start-up

When AC-line input voltage is applied, a rectified voltage appears across the capacitor C_{bus} (see Figure 2). The pull-up resistor $R_{StartUp}$ provides a current to charge the C_{iss} (input capacitance) of the power MOSFET, generating one voltage level. If the voltage across C_{iss} is sufficiently high, the power MOSFET will turn on and the V_{CC} capacitor will be charged through primary inductance of transformer L_p , the power MOSFET and the internal diode with two steps of constant current source $I_{VCC_Charge1}$ ¹ and $I_{VCC_Charge3}$ ¹.

A very small constant current source ($I_{VCC_Charge1}$) charges the V_{CC} capacitor until V_{CC} reaches V_{VCC_SCP} to protect the controller from a V_{CC} pin short-to-GND during start-up. After this, the second step constant current source ($I_{VCC_Charge3}$) is provided to further charge the V_{CC} capacitor, until V_{CC} exceeds the turn-on threshold V_{VCC_ON} . As shown in Phase I in Figure 4, the V_{CC} voltage increases almost linearly, with two steps.

Note: The recommended typical value for $R_{StartUp}$ is 50 M Ω (20 M Ω ~100 M Ω). $R_{StartUp}$ value is directly proportional to $t_{StartUp}$ and inversely proportional to no-load standby power.

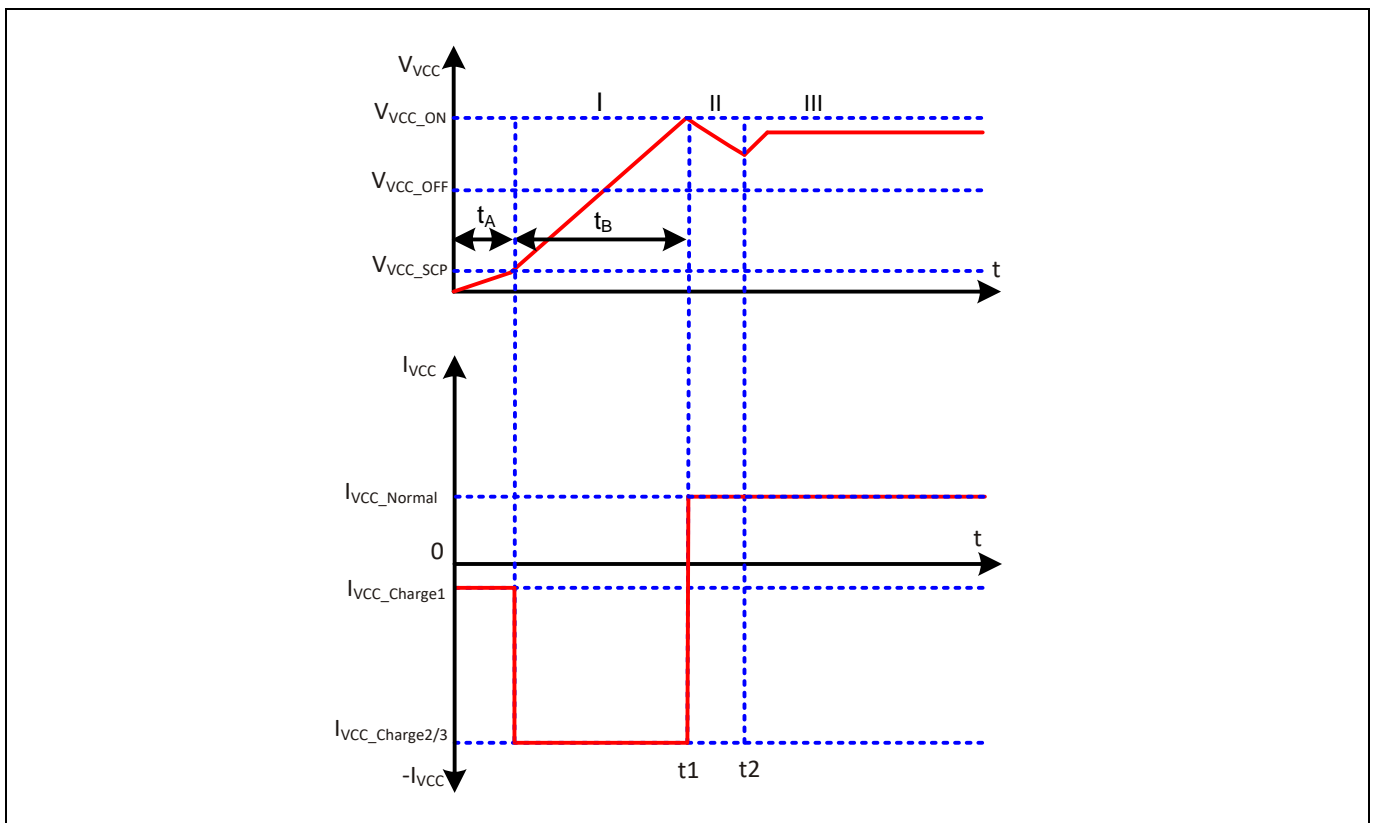


Figure 4 V_{CC} voltage and current at start-up

The time taken for the V_{CC} pre-charging can then be approximated as:

$$t_{StartUp} = t_A + t_B = \frac{V_{VCC_SCP} \cdot C_{VCC}}{I_{VCC_Charge1}} + \frac{(V_{VCC_ON} - V_{VCC_SCP}) \cdot C_{VCC}}{I_{VCC_Charge3}} \quad (\text{Eq 1})$$

¹ $I_{VCC_Charge1/2/3}$ is charging current from the controller to the V_{CC} capacitor during start-up.

Functional description and component design

where V_{VCC_SCP} : V_{CC} short-circuit protection voltage

C_{VCC} : V_{CC} capacitor

V_{VCC_ON} : V_{CC} turn-on threshold voltage

$I_{VCC_Charge1}$: V_{CC} charge current 1

$I_{VCC_Charge3}$: V_{CC} charge current 3

When the V_{CC} voltage exceeds the V_{VCC_ON} at time t_1 , the IC begins to operate with a soft-start. Due to power consumption of the IC and the fact that there is still no energy from the auxiliary winding to charge the V_{CC} capacitor before the output voltage is built up, the V_{CC} voltage drops (Phase II). Once the output voltage rises close to regulation, the auxiliary winding starts to charge the V_{CC} capacitor from the time t_2 onward, delivering the power to the IC. The V_{CC} will then reach a constant value depending on output load.

4.1.1 V_{CC} capacitor

Since there is a V_{CC} UV protection, the V_{CC} capacitor should be selected to be large enough to ensure that enough energy is stored in the V_{CC} capacitor so that the V_{CC} voltage will not drop below the V_{CC} UV protection threshold V_{VCC_OFF} before the auxiliary power kicks in. Therefore, the minimum capacitance should fulfill the following requirement:

$$C_{VCC} > \frac{I_{VCC_Charge3} \times t_{ss}}{V_{VCC_ON} - V_{VCC_OFF}} \quad (\text{Eq 2})$$

where C_{VCC} : V_{CC} capacitor

$I_{VCC_Charge3}$: V_{CC} charge current 3

t_{ss} : soft-start time

During ABM condition where the auxiliary winding cannot provide enough power to supply the IC because of the burst switching, the V_{CC} voltage may drop below the V_{VCC_OFF} . Therefore the capacitance needs to be increased, as the calculation above may not be enough.

4.2 Soft-start

After the supply voltage of the IC exceeds 16 V, which corresponds to t_1 of Figure 4, the IC starts switching with a soft-start. The soft-start implemented is a digital time-based function. The preset soft-start time is t_{ss} (12 ms) with four steps (see Figure 5). If not limited by other functions, the peak voltage on the CS pin will increase incrementally from 0.3 V to V_{CS_N} (0.8 V). The normal FB loop will take over the control when the output voltage reaches its regulated value.

 


Figure 5 Maximum CS voltage during soft-start

4.3 Normal operation

During normal operation the PWM controller consists of a digital signal processing circuit, including regulation control, and an analog circuit, including a current measurement unit and a comparator. Details of normal operation are illustrated in the following paragraphs.

4.3.1 PWM operation and peak current mode control

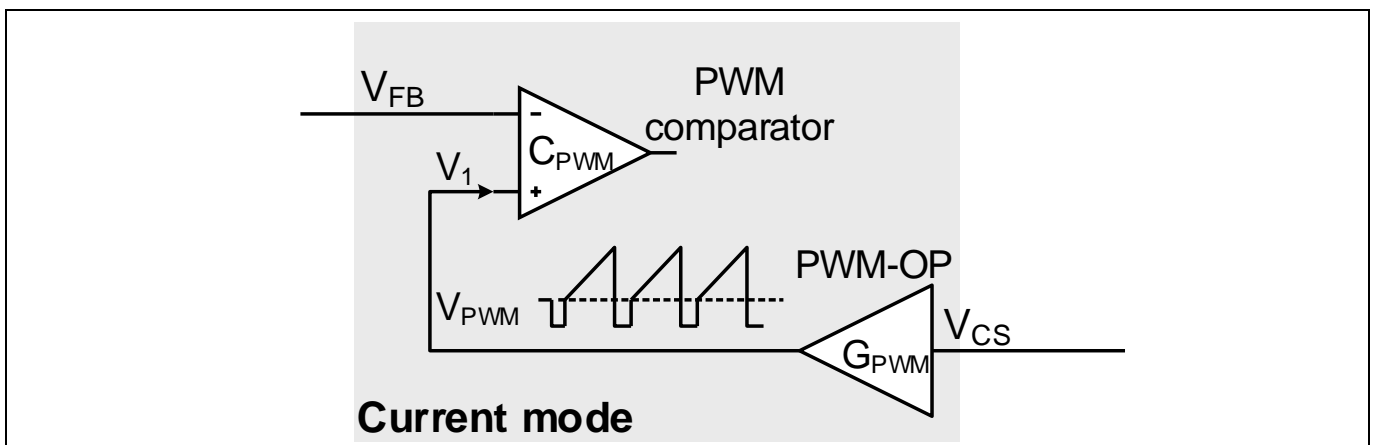


Figure 6 PWM block

4.3.1.1 Switch-on determination

The power MOSFET turn-on is synchronized with the internal oscillator, with a switching frequency F_{sw} that corresponds to the voltage level V_{FB} (see Figure 8).

4.3.1.2 Switch-off determination

In peak current mode control, the PWM comparator monitors voltage V_1 (see Figure 6), which is the representation of the instantaneous current of the power MOSFET. When V_1 exceeds V_{FB} , the PWM comparator sends a signal to switch off the gate of the power MOSFET. Therefore, the peak current of the power MOSFET is controlled by the FB voltage V_{FB} (see Figure 7).

Functional description and component design

At switch-on transient of the power MOSFET, a voltage spike across R_{CS} can cause V_1 to increase and exceed V_{FB} . To avoid a false switch-off, the IC has a blanking time t_{CS_LEB} before detecting the voltage across R_{CS} to mask the voltage spike. Therefore, the minimum turn-on time of the power MOSFET is t_{CS_LEB} .

If the voltage level at V_1 takes a long time to exceed V_{FB} , the IC will implement a maximum duty cycle control to force the power MOSFET to switch off when $D_{MAX} = 0.75$.

 


Figure 7 PWM

4.3.2 Current sensing

The power MOSFET current generates a voltage V_{CS} across the CS resistor R_{CS} connected between the CS pin and the GND pin. V_{CS} is amplified with gain G_{PWM} , then added with an offset V_{PWM} to become V_1 , as described below.

$$V_{CS} = I_D \times R_{CS} \quad (\text{Eq 3})$$

$$V_1 = V_{CS} * G_{PWM} + V_{PWM} \quad (\text{Eq 4})$$

where V_{CS} : CS pin voltage

I_D : power MOSFET current

R_{CS} : resistance of the CS resistor

V_1 : voltage level compared to V_{FB} as described in section 4.3.1.2

G_{PWM} : PWM-OP gain

V_{PWM} : offset for voltage ramp

4.3.3 Frequency reduction

Frequency reduction is implemented to achieve better efficiency at light load. At light load, the reduced switching frequency F_{SW} improves efficiency by reducing the switching losses.

When load decreases, V_{FB} decreases as well. F_{SW} is dependent on the V_{FB} as shown in Figure 8. Therefore, F_{SW} decreases as the load decreases.

Typically, F_{SW} at high load is 100 kHz and starts to decrease at $V_{FB} = 1.7$ V. There is no further frequency reduction once it reaches the f_{OSC_MIN} even if the load is further reduced.

 


Figure 8 Frequency reduction curve

4.3.4 Slope compensation

In CCM operation, a duty cycle greater than 50 percent may generate a sub-harmonic oscillation. A small perturbation on the transformer flux ϕ can result in loop instability where the system cannot auto-correct itself, as can be seen in the figure below right, where $\Delta\phi_2$ is greater than $\Delta\phi_1$. $\Delta\phi_2$ should be less than $\Delta\phi_1$ for a system to be stable (figure below left). DCM operation is more stable, as the transformer flux always goes to zero.

 


Figure 9 Perturbed transformer charging and discharging flux (black line is the stabilized transformer flux)

Functional description and component design

ICE5ARxxxxBZS can operate in CCM. To avoid the sub-harmonic oscillation, slope compensation is added to V_{CS} when the gate of the power MOSFET is turned on for more than 40 percent of the switching cycle period. The relationship between V_{FB} and the V_{CS} for CCM operation is described in the equation below:

$$V_{FB} = V_{CS} * G_{PWM} + V_{PWM} + M_{COMP} * (T_{ON} - 40\% * T_{PERIOD}) \quad (\text{Eq 5})$$

where T_{ON} : gate turn-on time of the power MOSFET

M_{COMP} : slope compensation rate

T_{PERIOD} : switching cycle period

As a result of slope compensation, $\Delta\phi_2$ is reduced to smaller than $\Delta\phi_1$, and therefore the system is able to stabilize itself as shown in the figure below.

 


Figure 10 Perturbed transformer flux with slope compensation

The slope compensation circuit is disabled and no slope compensation is added to the V_{CS} pin during ABM to save on power consumption.

4.3.5 Oscillator and frequency jittering

The oscillator generates a frequency of 100 kHz with frequency jittering of ± 4 percent at a jittering period of T_{JITTER} (4 ms). The frequency jittering helps to reduce conducted EMI.

A capacitor, current source and current sink which determine the frequency are integrated. The charging and discharging current of the implemented oscillator capacitor are internally trimmed in order to achieve a highly accurate switching frequency.

Once the soft-start period is over and when the IC goes into normal operating mode, the frequency jittering is enabled. There is also frequency jittering during frequency reduction.

4.3.6 Modulated gate drive

The drive stage is optimized for EMI consideration. The switch-on speed is slowed down before it reaches the power MOSFET turn-on threshold. There is a slope control on the rising edge at the output of the driver (see Figure 11). In this way the leading switch spike during turn-on is minimized.

The gate drive is 10 V (V_{GATE_HIGH}). For a 1 nF load capacitance, the typical values of rise time and fall time are 117 ns and 27 ns respectively.

 


Figure 11 Gate – rising waveform

Attention: *Do not add a gate discharge resistor on the gate of the power MOSFET or the GATE pin. The discharge resistor together with the $R_{StartUp}$ forms a voltage divider. With the high ratio of the resistance of $R_{StartUp}$ with discharge resistor, the gate voltage of the power MOSFET may not be enough turn it on and charge the V_{CC} to exceed V_{VCC_ON} . Similarly, connecting a voltage probe on the GATE pin may result in a non-start-up or a longer start-up time, depending on the probe resistance.*

4.4 Peak Current Limitation (PCL)

There is a cycle-by-cycle PCL realized by the current limit comparator to provide primary Over Current Protection (OCP). The primary current generates a voltage V_{CS} across the CS resistor R_{CS} connected between the CS pin and the GND pin. If the voltage V_{CS} exceeds an internal voltage limit V_{CS_N} , the comparator immediately turns off the gate drive.

The primary peak current I_{PEAK_PRI} can be calculated as below:

$$I_{PEAK_PRI} = V_{CS_N} / R_{CS} \quad (\text{Eq 6})$$

where I_{PEAK_PRI} : maximum peak current in the primary

V_{CS_N} : threshold voltage for the PCL

R_{CS} : resistance of the CS resistor

To avoid mis-triggering caused by MOSFET switch-on transient voltage spikes, a Leading Edge Blanking (LEB) time (t_{CS_LEB}) is integrated into the current sensing path.

Note: *In case of high switch-on noise at the CS pin, the IC may switch off immediately after the LEB time, especially at light-load high-line conditions. To avoid this, a noise-filtering ceramic capacitor (e.g. 100 pF~100 nF) can be added across the CS pin and the GND pin.*

4.4.1 Propagation delay compensation

In case of OC detection, there is always a propagation delay from sensing the V_{CS} to switching off the power MOSFET. An overshoot on the peak current I_{peak} caused by the delay depends on the ratio of dI/dt of the primary current (see Figure 12).

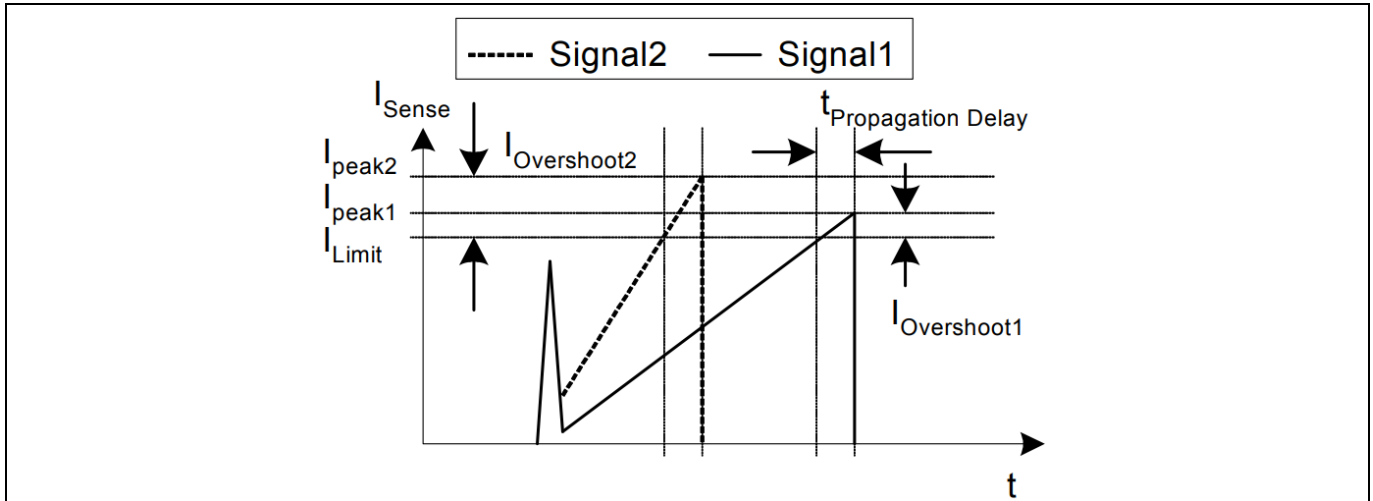


Figure 12 Current limiting

The overshoot of Signal2 is larger than Signal1 due to the steeper rising waveform. This change in the slope depends on the AC input voltage. Propagation delay compensation is integrated to reduce the overshoot due to dI/dt of the rising primary current. Thus the propagation delay time between exceeding the CS threshold V_{CS_N} and the switching off of the power MOSFET is compensated over a wide bus voltage range. Current limiting becomes more accurate, which will result in a minimum difference of over-load protection triggering power between low and high AC-line input voltage.

Under CCM operation, the same V_{CS} does not result in the same power. In order to achieve a close over-load triggering level for CCM, ICE5ARxxxxBZS has implemented a two-curve compensation, as shown in Figure 13. One of the curves is used for T_{ON} greater than 0.40 duty cycle and the other is for T_{ON} lower than 0.40 duty cycle.

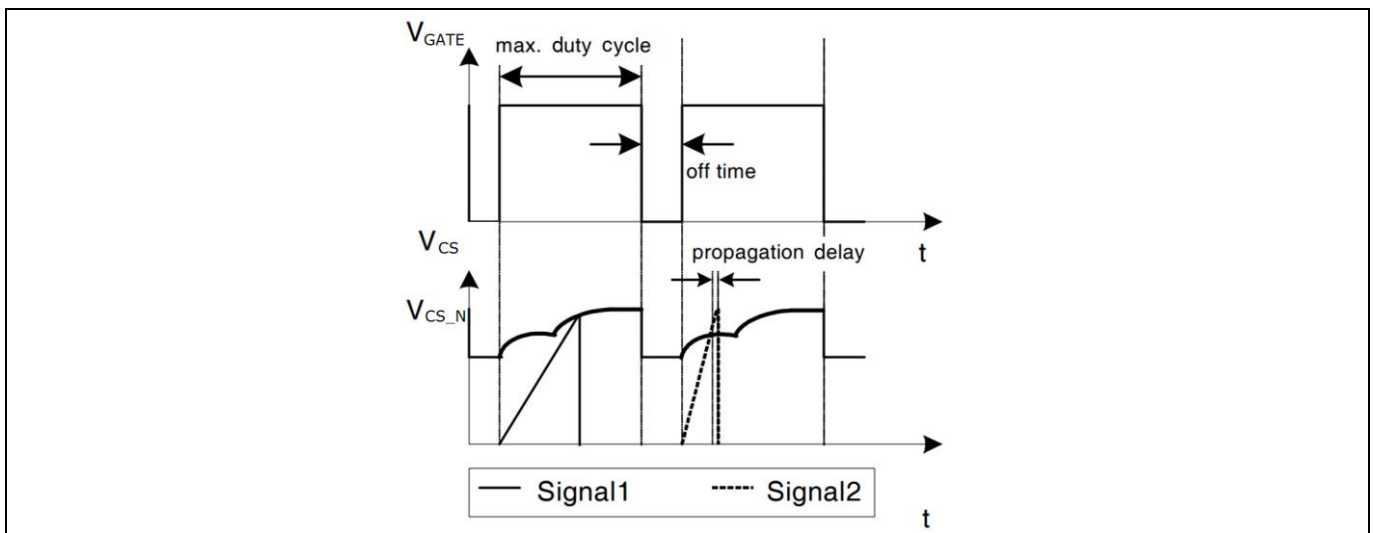


Figure 13 Dynamic voltage threshold V_{CS_N}

Similarly, the same concept of propagation delay compensation is also implemented in ABM at a reduced level. With this implementation, the entry and exit burst mode power can remain close between low and high AC-line input voltage.

4.5 ABM with selectable power level

At light load, the IC enters ABM operation to minimize power consumption. Details of ABM operation are explained in the following paragraphs.

4.5.1 Entering ABM operation

The system will enter ABM operation when two conditions are met:

- the FB voltage is lower than the threshold of V_{FB_EBLP}/V_{FB_EBHP} depending on burst configuration option set-up;
- and a certain blanking time t_{FB_BEB} .

Once both of these conditions are fulfilled, the ABM flip-flop is set and the controller enters ABM operation. This dual-condition determination for entering ABM operation prevents mis-triggering of ABM, so that the controller enters ABM operation only when the output power is really low.

The threshold power to enter burst mode can be determined using the equation below.

$$P_{enter_burst} = \frac{1}{2} \cdot L_p \cdot f_{OSC4_MIN} \cdot \left(\frac{V_{FB_EBxP} - V_{PWM}}{R_{CS} \cdot G_{PWM}} \right)^2 \quad (\text{Eq 7})$$

where L_p : primary inductance

f_{OSC4_MIN} : minimum switching frequency

V_{FB_EBxP} : V_{FB} entering ABM

The burst power as a ratio to the maximum input power P_{IN_Max} can be expressed in the equation below.

$$\frac{P_{enter_burst}}{P_{IN_Max}} = \frac{f_{OSC4_MIN}}{f_{OSC4}} \cdot \left(\frac{V_{FB_EBxP} - V_{PWM}}{V_{CS_N} \cdot G_{PWM}} \right)^2 \quad (\text{Eq 8})$$

4.5.2 During ABM operation

After entering ABM, the PWM section will be inactive, making the V_{Out} start to decrease. As the V_{Out} decreases, V_{FB} rises. Once V_{FB} exceeds V_{FB_BOn} , the internal circuit is again activated by the internal bias to start the switching.

If the PWM is still operating and the output load is still low, V_{Out} increases and the V_{FB} signal starts to decrease. When V_{FB} reaches the low threshold V_{FB_BOff} , the internal bias is reset again and the PWM section is disabled, with no switching until V_{FB} increases and once again exceeds the V_{FB_BOn} threshold.

In ABM, V_{FB} is like a sawtooth waveform swinging between V_{FB_BOff} and V_{FB_BOn} , as shown in Figure 14.

During ABM, the switching frequency f_{OSC4_ABM} is 83 kHz. The peak current I_{PEAK_ABM} of the power MOSFET is defined by:

$$I_{PEAK_ABM} = V_{CS_BxP} / R_{CS} \quad (\text{Eq 9})$$

where V_{CS_BxP} is the PCL in ABM

4.5.3 Leaving ABM operation

The FB voltage immediately increases if there is a sudden increase in the output load. When V_{FB} exceeds V_{FB_LB} , it will leave ABM and the PCL threshold voltage will return back to V_{CS_N} immediately.

The power on leaving ABM can be determined using the equation below.

$$P_{leave_burst} = \frac{1}{2} \cdot L_p \cdot f_{OSC4_ABM} \cdot \left(\frac{V_{CS_BxP}}{R_{CS}} \right)^2 \quad (\text{Eq 10})$$

where f_{OSC4_ABM} : ABM switching frequency

V_{CS_BxP} : PCL in ABM

Therefore, the ratio of the power on leaving ABM to maximum input power can be determined using the equation below.

$$\frac{P_{leave_burst}}{P_{IN_Max}} = \frac{f_{OSC4_ABM}}{f_{OSC4}} \cdot \left(\frac{V_{CS_BxP}}{V_{CS_N}} \right)^2 \quad (\text{Eq 11})$$

 


Figure 14 Signals in ABM

4.5.4 ABM configuration

The burst mode entry level can be selected by changing the resistance R_{sel} at the FB pin. There are three configuration options depending on R_{sel} , which corresponds to the options of no ABM (Option 1), low range of ABM power (Option 2) and high range of ABM power (Option 3). The table below shows the control logic for the entry and exit levels with the FB voltage.

Table 2 ABM configuration option set-up

Option	R_{sel}	V_{FB}	V_{CS_BxP}	Entry level		Exit level	
				V_{FB_EBxP}	Percentage of P_{IN_Max}	V_{FB_LB}	Percentage of P_{IN_Max}
1	Less than 470 k Ω	V_{FB} less than $V_{FB_P_BIAS1}$	–	–	No ABM	–	No ABM
2	720~790 k Ω	$V_{FB_P_BIAS1}$ less than V_{FB} less than $V_{FB_P_BIAS2}$	0.22 V	0.93 V	~3 percent	2.73 V	~6.2 percent
3 (default)	Greater than 1210 k Ω	V_{FB} greater than $V_{FB_P_BIAS2}$	0.27 V	1.03 V	~4.5 percent	2.73 V	~9.4 percent

P_{IN_Max} is the input power before the over-load protection is triggered.

During start-up of the IC, the controller presets the ABM selection to Option 3, the FB resistor (R_{FB}) is turned off by internal switch S_2 (see Figure 15) and a current source I_{sel} is turned on instead. From $V_{CC} = 4.44$ V to the V_{CC} on-threshold, the FB pin will start to charge resistor R_{sel} with current I_{sel} to a certain voltage level. When V_{CC} reaches the V_{CC} on-threshold, the FB voltage is sensed. The burst mode option is then chosen according to the FB voltage level. After finishing the selection, any change on the FB level will not change the burst mode option, and the current source (I_{sel}) is turned off while the FB resistor (R_{FB}) is connected back to the circuit.

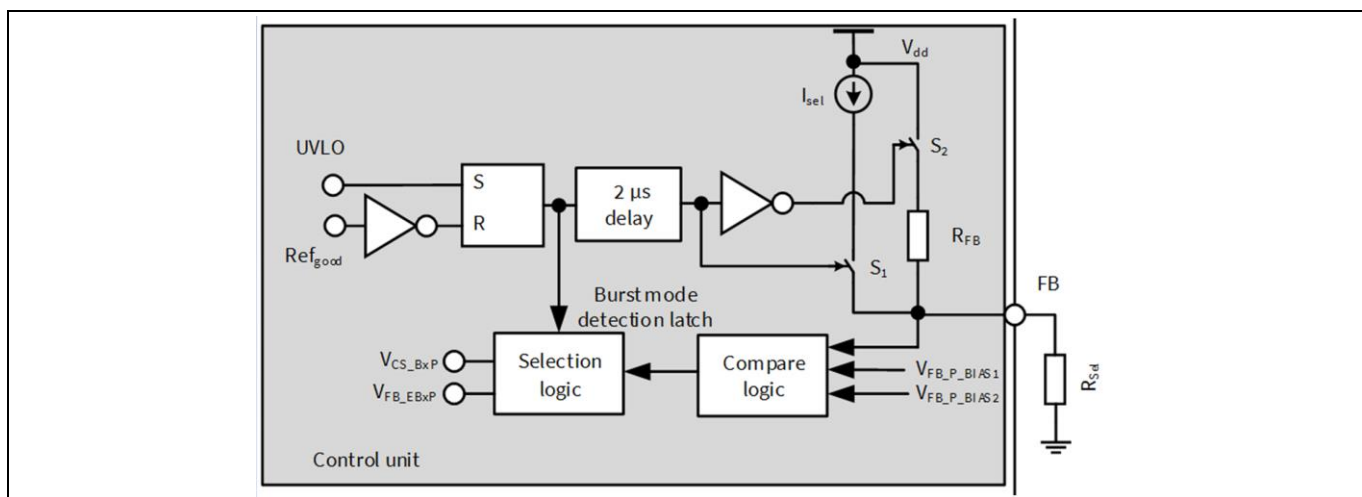


Figure 15 ABM detect and adjust

4.6 Non-isolated/isolated configuration

ICE5ARxxxxBZS has a VERR pin, which is connected to the input of an integrated error amplifier to support non-isolated flyback application (see Figure 3). When the V_{CC} is charging and before reaching the V_{CC} on-threshold, a current source $I_{ERR_P_BIAS}$ from the VERR pin together with R_{F1} and R_{F2} will generate a voltage across it. If the VERR

Functional description and component design

voltage is more than $V_{ERR_P_BIAS}$ (0.2 V), non-isolated configuration is selected; otherwise, isolated configuration is selected. In isolated configuration, the error amplifier output is disconnected from the FB pin.

Connect the VERR pin to GND if an error amplifier is not used or if isolated configuration is selected.

4.6.1 Non-isolated FB

In case of non-isolated configuration (see Figure 3), the voltage divider R_{F1} and R_{F2} is used to sense the output voltage and compare it with the internal reference voltage V_{ERR_REF} . The difference between the sensed voltage and the reference voltage is converted as an output current by the error amplifier. The output current will charge/discharge the resistor and capacitor network connected at the FB pin for the loop compensation.

To properly detect a non-isolated configuration, the minimum resistance for the parallel combination of resistors R_{F1} and R_{F2} is calculated below:

$$R_{F1//F2} \geq V_{ERR_P_BIAS_max} / I_{ERR_P_BIAS_min} = 0.24 \text{ V} / 9.5 \mu\text{A} = 25.3 \text{ k}\Omega \quad (\text{Eq 12})$$

where $R_{F1//F2}$: parallel combination of R_{F1} and R_{F2}

$V_{ERR_P_BIAS_max}$: maximum voltage for error amplifier mode

$I_{ERR_P_BIAS_min}$: minimum bias current for error amplifier mode

The output voltage V_{P1} (see Figure 3) is set by R_{F1} and R_{F2} using the equation below:

$$R_{F2} = R_{F1} \cdot \left(\frac{V_{P1}}{V_{ERR_REF}} - 1 \right) \quad (\text{Eq 13})$$

where R_{F1} and R_{F2} : voltage divider resistors

V_{P1} : output voltage

V_{ERR_REF} : error amplifier reference voltage

4.6.2 Isolated FB

In isolated configuration, the output is usually sensed by a TL431, and the output is fed to the FB pin by the optocoupler (see Figure 16). Inside the IC, the FB pin is connected to a (V_{REF}) 3.3 V reference voltage through an internal pull-up resistor R_{FB} . Outside the IC, this pin is connected to the collector of the optocoupler. Normally, a ceramic capacitor C_{FB} , e.g. 1 nF, can be placed between this pin and GND to filter out noise.

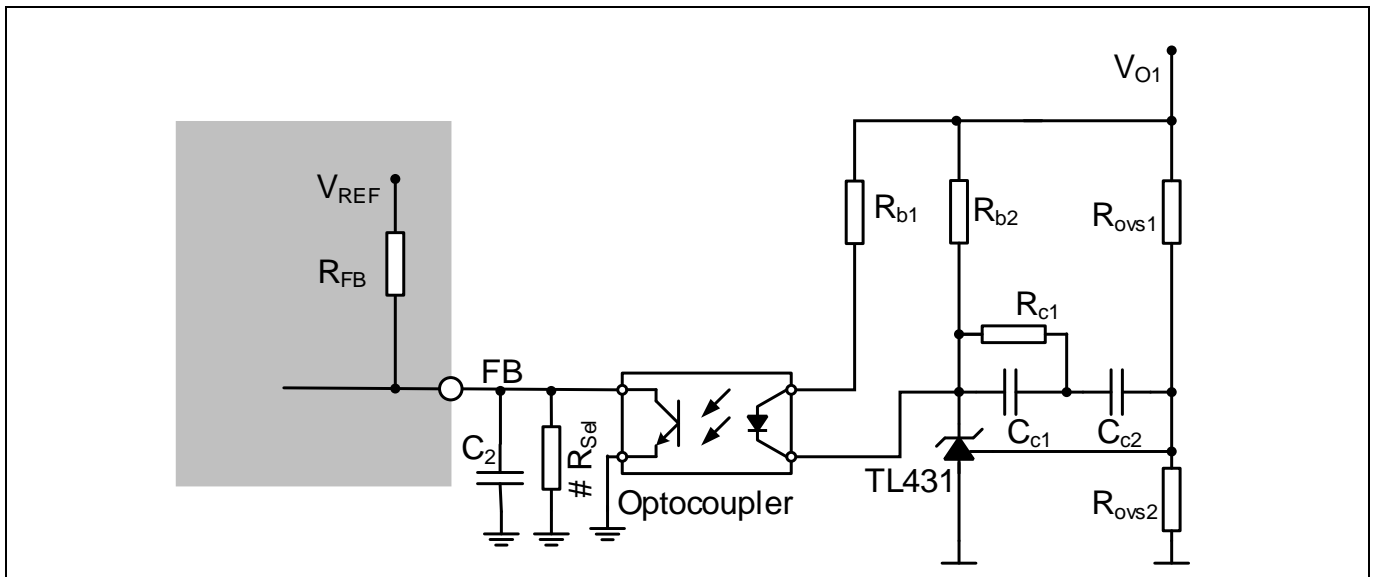


Figure 16 FB circuit for isolated configuration

The output voltage V_{O1} (see Figure 16) is set by R_{OVS1} and R_{OVS2} using the equation below:

$$R_{OVS1} = R_{OVS2} \left(\frac{V_{O1}}{V_{REF_TL}} - 1 \right) \quad (\text{Eq 14})$$

where R_{OVS1} and R_{OVS2} : voltage divider resistors

V_{O1} : output voltage

V_{REF_TL} : TL431 reference voltage

4.7 Protection functions

The ICE5ARxxxxBZS provides numerous protection functions that considerably improve the power supply system robustness, safety and reliability. The following table summarizes these protection functions and the corresponding protection mode, whether non-switch auto-restart, auto-restart or odd-skip auto-restart. Refer to Figure 17, Figure 18 and Figure 19 for the waveform illustration of the protection modes.

Table 3 Protection functions

Protection functions	Normal mode	Burst mode		Protection mode
		Burst ON	Burst OFF	
V_{CC} OV	√	√	NA ¹	Odd-skip auto-restart
V_{CC} UV	√	√	√	Auto-restart
Over-load/open-loop	√	NA ¹	NA ¹	Odd-skip auto-restart
Over-temperature	√	√	√	Non-switch auto-restart
CS short-to-GND	√	√	NA ¹	Odd-skip auto-restart
V_{CC} short to GND	√	√	√	No start-up

¹ Not applicable

4.7.1 V_{CC} OV/UV

During operation, the V_{CC} voltage is continuously monitored. If V_{CC} is either below V_{VCC_OFF} for 50 μs ($t_{VCC_OFF_B}$) or above V_{VCC_OVP} for 55 μs ($t_{VCC_OVP_B}$), the power MOSFET is kept switched off. After the V_{CC} voltage falls below the threshold V_{VCCoff} , the new start-up sequence is activated. The V_{CC} capacitor is then charged up. Once the voltage exceeds the threshold V_{VCC_ON} , the IC begins to operate with a new soft-start.

4.7.2 Over-load/open-loop

In case of open control-loop or output over-load, the FB voltage will be pulled up. When V_{FB} exceeds V_{FB_OLP} after a blanking time of $t_{FB_OLP_B}$, the IC enters odd-skip auto-restart mode. The blanking time enables the converter to provide peak power in case the increase in V_{FB} is due to a sudden load increase.

4.7.3 Over-temperature

If the junction temperature of the controller exceeds T_{jcon_OTP} , the IC enters Over Temperature Protection (OTP) in auto-restart mode. The IC is also implemented with a 40°C hysteresis. That means the IC can only be recovered from OTP when the controller junction temperature drops 40°C lower than the OT trigger point.

4.7.4 CS short-to-GND

If the voltage at the CS pin is lower than the preset threshold V_{CS_STG} with a certain blanking time $t_{CS_STG_B}$ for three consecutive pulses during the on-time of the power switch, the IC enters CS short-to-GND protection.

When CS pin is shorted to GND, the Drain peak current I_D will depend on bus voltage and transformer primary inductance. IC may be damaged if the Drain peak current exceeds the maximum Pulse drain current limit I_{D_Pulse} for CoolSET™ or maximum Single pulse source current at SOURCE pin I_{S_pulse} for standalone under the Absolute Maximum Ratings in datasheet before the CS short-to-GND protection is triggered.

4.7.5 V_{CC} short-to-GND

To limit the power dissipation of the start-up circuit at V_{CC} short-to-GND, the V_{CC} charging current is limited to a minimum level of $I_{VCC_Charge1}$. With such low current, the power loss of the IC is limited to prevent over-heating.

4.7.6 Protection modes

All the protections are in auto-restart mode with a new soft-start sequence. The three auto-restart modes are illustrated in the following figures.

Fifth-generation fixed-frequency design guide

Design guide - ICE5ARxxxxBZS

Functional description and component design

 


Figure 17 Non-switch auto-restart mode

 


Figure 18 Auto-restart mode

 


Figure 19 Odd-skip auto-restart

5 Typical application circuit

A 14.5 W demo board schematic circuit with ICE5AR4780BZS is shown below.

 


Figure 20 **Schematic of DEMO_5AR4780BZS_14W1**

6 PCB layout recommendation

In an SMPS, the PCB layout is crucial to a successful design. Below are some recommendations (see Figure 20).

1. Minimize the loop with pulse share current or voltage; examples are the loop formed by the bus voltage source, primary winding, main power switch (power switch CoolMOS™ inside the CoolSET™) and CS resistor or the loop consisting of the secondary winding, output diode and output capacitor, or the loop of the V_{CC} power supply.
2. Star the ground at the bulk capacitor C1: all primary grounds should be connected to the ground of the bulk capacitor C1 separately at one point. This can reduce the switching noise entering the sensitive pins of the CoolSET™ device. The primary star ground can be split into four groups as follows:
 - i. Combine signal (all small-signal grounds connecting to the controller/CoolSET™ GND pin such as the filter capacitor C4, C6, C8, C9 and optocoupler ground) and power ground (CS resistor R8A and R8B).
 - ii. V_{CC} ground includes the V_{CC} capacitor C3 ground and the auxiliary winding ground, pin 2 of the power transformer.
 - iii. EMI return ground includes the Y capacitor for isolated flyback application.
 - iv. DC ground from the bridge rectifier BR1.
3. Place the filter capacitor close to the controller ground: filter capacitors C4, C6, C8 and C9 should be placed as close to the controller ground and the controller pin as possible so as to reduce the switching noise coupled into the controller.
4. HV traces clearance: HV traces should maintain sufficient spacing to the nearby traces. Otherwise, arcing could occur.
 - i. 400 V traces (positive rail of bulk capacitor C1) to nearby traces: greater than 2.0 mm.
 - ii. 700/800 V traces (DRAIN pin of CoolSET™ IC1 [see Figure 20]) to nearby traces: greater than 3 mm.
5. Recommended minimum of 232 mm² copper area at the DRAIN pin to add to the PCB for better thermal performance of the CoolSET™.

7 Output power of fifth-generation fixed-frequency ICs

Table 4 Output power of fifth-generation fixed-frequency controllers

Type	Package	Marking	V _{DS}	F _{sw}	R _{DSon} ¹	220 V AC ±20 percent ² at DCM	85–300 V AC ² at DCM	85–300 V AC ² at CCM
ICE5AR4770BZS	PG-DIP-7	5AR4770BZS	700 V	100 kHz	4.73 Ω	26.5 W	14.5 W	16 W
ICE5AR4780BZS	PG-DIP-7	5AR4780BZS	800 V	100 kHz	4.13 Ω	27.5 W	15 W	16 W
ICE5AR0680BZS	PG-DIP-7	5AR0680BZS	800 V	100 kHz	0.71 Ω	66 W	39 W	41 W

The calculated output power curves showing typical output power against ambient temperature are shown below. The curves are derived based on an open-frame design at T_a = 50°C, T_J = 125°C (integrated HV MOSFET for CoolSET™), using the minimum pin copper area in a 2 oz copper single-sided PCB and steady-state operation only (no design margins for abnormal operation modes are included). The output power figure is for selection purposes only. The actual power can vary depending on the specific design.

 


Figure 21 Output power curve of ICE5AR4770BZS

¹ Typ. at T_J = 25°C (inclusive of low-side MOSFET).

² Calculated maximum output power rating in an open-frame design at T_a = 50°C, T_J = 125°C (integrated HV MOSFET) and using minimum drain pin copper area in a 2 oz copper single-sided PCB. The output power figure is for selection purposes only. The actual power can vary depending on the particular design. Please contact a technical expert from Infineon for more information.

Output power of fifth-generation fixed-frequency ICs

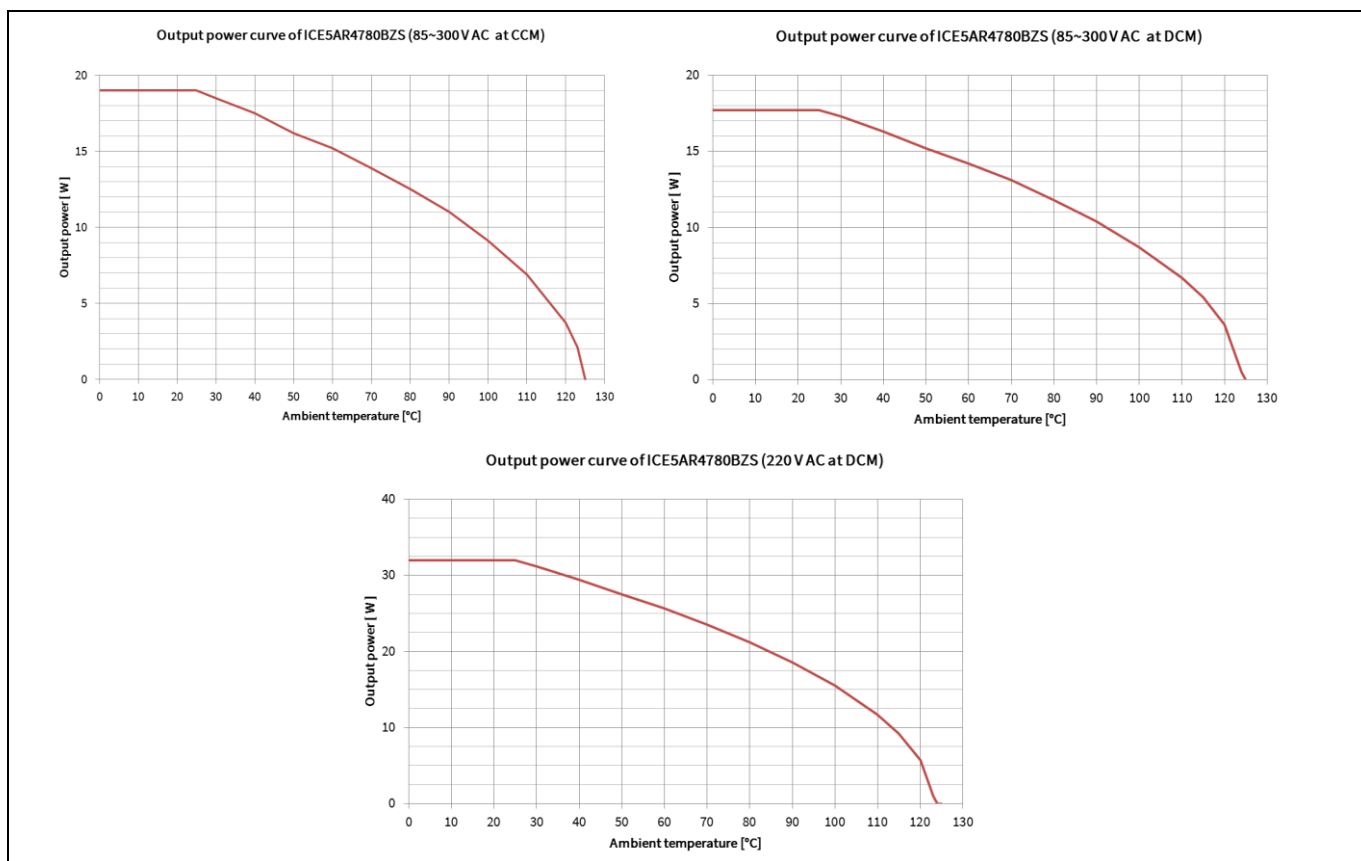


Figure 22 Output power curve of ICE5AR4780BZS

 


Figure 23 Output power curve of ICE5AR0680BZS

8 Fifth-generation fixed-frequency FLYCAL design example

A design example of a 14.5 W 15 V 5 V fixed-frequency non-isolated DCM flyback converter with ICE5AR4780BZS is shown below.

Define input parameters:		
Minimum AC input voltage:	V_{ACMin}	85 V AC
Maximum AC input voltage:	V_{ACMax}	330 V AC
Line frequency:	f_{AC}	60 Hz
Bulk capacitor DC ripple voltage:	$V_{DCRipple}$	27 V
Output voltage 1:	V_{Out1}	15 V
Output current 1:	I_{Out1}	0.83 A
Forward voltage of output diode 2:	V_{FOut1}	0.6 V
Output ripple voltage 1:	$V_{OutRipple1}$	0.2 V
Output voltage 2:	V_{Out2}	5 V
Output current 2:	I_{Out2}	0.4 A
Forward voltage of output diode 2:	V_{FOut2}	0.2 V
Output ripple voltage 2:	$V_{OutRipple2}$	0.2 V
Maximum output power:	P_{OutMax}	17 W
Minimum output power:	P_{OutMin}	1 W
Efficiency at V_{ACMin} and P_{OutMax} :	η	83 percent
Reflection voltage:	V_{RSET}	97.5 V
V_{CC} voltage:	V_{Vcc}	14 V
Forward voltage of V_{CC} diode (D2):	V_{FVcc}	0.6 V
Fifth-generation FF CoolSET™:	CoolSET™	ICE5AR4780BZS
Switching frequency:	f_s	100 kHz
Breakdown voltage:	V_{DSMax}	800 V
Drain-to-source capacitance of MOSFET (including $C_{O(er)}$ of MOSFET):	C_{DS}	7 pF
Effective output capacitance of MOSFET:	$C_{O(er)}$	3 pF
Start-up resistor $R_{StartUp}$ (R2A, R2B, R2C):	$R_{StartUp}$	45 MΩ
Maximum ambient temperature:	T_a	50 °C

8.1 Pre-calculation

Output power of output 1:

$$P_{Out1} = V_{Out1} \cdot I_{Out1} \quad (\text{Eq 15}) \quad P_{Out1} = 15V \cdot 0.83A = 12.45W$$

Output power of output 2:

$$P_{Out2} = V_{Out2} \cdot I_{Out2} \quad (\text{Eq 16}) \quad P_{Out2} = 5V \cdot 0.4A = 2W$$

Nominal output power:

$$P_{OutNom} = P_{Out1} + P_{Out2} \quad (\text{Eq 17}) \quad P_{OutNom} = 12.45W + 2W = 14.45W$$

Fifth-generation fixed-frequency FLYCAL design example

Output power 1 load weight:

$$K_{L1} = P_{Out1} / P_{OutNom} \quad (\text{Eq 18}) \quad K_{L1} = 12.45W / 14.45W = 0.86$$

Output power 2 load weight:

$$K_{L2} = P_{Out2} / P_{OutNom} \quad (\text{Eq 19}) \quad K_{L1} = 2W / 14.45W = 0.14$$

Maximum input power:

$$P_{InMax} = \frac{P_{OutMax}}{\eta} \quad (\text{Eq 20}) \quad P_{InMax} = \frac{17W}{0.83} = 20.48W$$

8.2 Input diode bridge (BR1)

Input RMS current:

$$I_{ACRMS} = \frac{P_{InMax}}{V_{ACMin} \cdot \cos\varphi} \quad (\text{Eq 21}) \quad \cos\varphi = 0.6 \quad I_{ACRMS} = \frac{20.48W}{85V \cdot 0.6} = 0.402 A$$

Maximum DC input voltage:

$$V_{DCMaxPk} = V_{ACMax} \cdot \sqrt{2} \quad (\text{Eq 22}) \quad V_{DCMaxPk} = 330V \cdot \sqrt{2} = 466.7V$$

8.3 Input capacitor (C1)

Peak voltage at minimum AC input:

$$V_{DCMinPk} = V_{ACMin} \cdot \sqrt{2} \quad (\text{Eq 23}) \quad V_{DCMinPk} = 85V \cdot \sqrt{2} = 120.2V$$

Minimum DC input voltage-based ripple voltage setting:

$$V_{DCMinSet} = V_{DCMinPk} - V_{DCRipple} \quad (\text{Eq 24}) \quad V_{DCMinSet} = 120.2V - 27V = 93.2V$$

Discharging time at each half-line cycle:

$$T_D = \frac{1}{4 \cdot f_{AC}} \cdot \left(1 + \frac{\sin^{-1} \frac{V_{DCMinSet}}{V_{DCMinPk}}}{90} \right) \quad (\text{Eq 25}) \quad T_D = \frac{1}{4 \cdot 60Hz} \cdot \left(1 + \frac{\sin^{-1} \frac{93.2V}{120.2V}}{90} \right) = 6.52ms$$

Required energy at discharging time of input capacitor:

$$W_{IN} = P_{INMax} \cdot T_D \quad (\text{Eq 26}) \quad W_{IN} = 20.48W \cdot 6.52ms = 0.13W \cdot s$$

Calculated input capacitor:

$$C_{INCal} = \frac{2 \cdot W_{IN}}{V_{DCMinPk}^2 - V_{DCMinSet}^2} \quad (\text{Eq 27}) \quad C_{INCal} = \frac{2 \cdot 0.13W \cdot s}{(120.2V)^2 - (93.2V)^2} = 46.35\mu F$$

Fifth-generation fixed-frequency FLYCAL design example

Alternatively, a rule of thumb for estimating the input capacitor may be applied based on maximum input power, as shown below:

Input voltage	Factor
115 V AC	2 μ F/W
230 V AC	1 μ F/W
85–265 V AC	2–3 μ F/W

Applying the rule of thumb using the 2 μ F/W factor:

$$C_{INest} = P_{INMax} \cdot factor \quad (\text{Eq 28}) \quad \left| \quad C_{INest} = 20.48 \cdot 2\mu = 41\mu F \right.$$

Choose a capacitance greater than or equal to calculated (Eq 27) or estimated (Eq 28) value, whichever is greater. The voltage rating should be greater than or equal to the maximum DC input voltage.

Input capacitor	C_{IN}	$47 \mu F / 500 V$
-----------------	----------	--------------------

Recalculation after input capacitor selection:

$$V_{DCMin} = \sqrt{V_{DCMinPk}^2 - \frac{2 \cdot W_{IN}}{C_{IN}}} \quad (\text{Eq 29}) \quad \left| \quad V_{DCMin} = \sqrt{(120.2V)^2 - \frac{2 \cdot 0.13W \cdot s}{47\mu F}} = 93.63V \right.$$

Note: Special requirements for hold-up time, including cycle skip/drop-out, or other factors which affect the resulting minimum DC input voltage and capacitor discharging time, are not considered above.

8.4 Transformer design (T1)

 


Figure 24 Typical waveforms of DCM operation

Maximum duty cycle:

$$D_{Max} = \frac{V_{RSET}}{V_{RSET} + V_{DCMin}} \quad (\text{Eq 30}) \quad \left| \quad D_{Max} = \frac{97.5V}{97.5V + 93.63V} = 0.51 \right.$$

Primary inductance:

$$L_P = \frac{(V_{DCMin} \times D_{Max})^2}{2 \times P_{InMax} \times f_s \times K_{RF}} \quad (\text{Eq 31}) \quad \left| \quad L_P = \frac{(93.63V \times 0.51)^2}{2 \times 20.48W \times 100kHz \times 1} = 556.7 \mu H \right.$$

Primary average current during turn-on:

$$I_{AV} = \frac{P_{InMax}}{V_{DCMin} \times D_{Max}} \quad (\text{Eq 32}) \quad \left| \quad I_{AV} = \frac{20.48W}{93.63V \times 0.51} = 0.43A \right.$$

Fifth-generation fixed-frequency FLYCAL design example

Primary peak-to-peak current:

$$\Delta I = \frac{V_{DCMin} \times D_{Max}}{L_p \times f_s} \quad (\text{Eq 33}) \quad \left| \quad \Delta I = \frac{93.63V \times 0.51}{556.7 \mu H \times 100kHz} = 0.86A \right.$$

Primary peak current:

$$I_{PMax} = I_{AV} + \frac{\Delta I}{2} \quad (\text{Eq 34}) \quad \left| \quad I_{PMax} = 0.43A + \frac{0.86A}{2} = 0.86A \right.$$

Primary valley current:

$$I_{Valley} = I_{PMax} - \Delta I \quad (\text{Eq 35}) \quad \left| \quad I_{Valley} = 0.86A - 0.86A = 0A \right.$$

Primary RMS current:

$$I_{PRMS} = \sqrt{[3 \times (I_{AV})^2 + (\frac{\Delta I}{2})^2] \times \frac{D_{max}}{3}} \quad (\text{Eq 36}) \quad \left| \quad I_{PRMS} = \sqrt{[3 \times (0.43)^2 + (\frac{0.86A}{2})^2] \times \frac{0.51}{3}} = 0.35A \right.$$

Choose core type and bobbin from magnetics suppliers that can support the required power. Maximum flux density, typically from 200 mT to 400 mT, depends on the type of ferrite material. Below is the selected transformer material:

Core type	: E 20/10/6
Core material	: N87
Maximum flux density (B _s)	: 390 mT at 100°C
Cross-sectional area (A _e)	: 32 mm ²
Bobbin width (BW)	: 11 mm
Winding cross-section (A _N)	: 34 mm ²
Winding perimeter (l _N)	: 41.2 mm

Set maximum flux density	B _{MAX}	200 mT
--------------------------	------------------	--------

Calculate minimum primary number of turns:

$$N_{PCal} \geq \frac{I_{PMax} \cdot L_p}{B_{Max} \cdot A_e} \quad (\text{Eq 37}) \quad \left| \quad N_{PCal} \geq \frac{0.86A \times 556.7 \mu H}{200mT \times 32mm^2} = 74.6Turns \right.$$

Primary number of turns	N _P	78 turns
-------------------------	----------------	----------

Calculate secondary number of turns for V_{Out1}:

$$N_{S1Cal} = \frac{N_P \cdot (V_{Out1} + V_{FOut1})}{V_R} \quad (\text{Eq 38}) \quad \left| \quad N_{S1Cal} = \frac{78Turns \times (15V + 0.6V)}{97.5V} = 12.48Turns \right.$$

Secondary 1 number of turns	N _{S1}	12 turns
-----------------------------	-----------------	----------

Calculate secondary number of turns for V_{Out2}:

$$N_{S2Cal} = \frac{N_P \cdot (V_{Out2} + V_{FOut2})}{V_R} \quad (\text{Eq 39}) \quad \left| \quad N_{S2Cal} = \frac{78Turns \times (5V + 0.2V)}{97.5V} = 4.16Turns \right.$$

Secondary 2 number of turns	N _{S2}	4 turns
-----------------------------	-----------------	---------

Fifth-generation fixed-frequency FLYCAL design example

Calculate number of turns for V_{CC} :

$$N_{VccCal} = \frac{N_P \cdot (V_{Vcc} + V_{FVcc})}{V_R} \quad (\text{Eq 40}) \quad \left| \quad N_{VccCal} = \frac{78\text{Turns} \times (14V + 0.6V)}{97.5V} = 11.7\text{Turns}$$

Auxiliary number of turns

$$N_{Vcc} \quad | \quad 11 \text{ turns}$$

Auxiliary supply voltage:

$$V_{VccCal} = (V_{Out1} + V_{FOut1}) \cdot N_{Vcc} / N_{S1} - V_{FVcc} \quad (\text{Eq 41}) \quad \left| \quad V_{VccCal} = (15V + 0.6V) \cdot 11 / 12 - 0.6V = 13.7V$$

8.5 Post calculation

Primary to secondary 1 turns ratio:

$$N_{PS1} = N_P / N_{S1} \quad (\text{Eq 42}) \quad \left| \quad N_{PS1} = 78\text{turns} / 12\text{turns} = 6.5$$

Primary to secondary 2 turns ratio:

$$N_{PS2} = N_P / N_{S2} \quad (\text{Eq 43}) \quad \left| \quad N_{PS2} = 78\text{turns} / 4\text{turns} = 19.5$$

Post-calculated reflected voltage:

$$V_{RPost} = (V_{Out1} + V_{FOut1}) \cdot N_P / N_{S1} \quad (\text{Eq 44}) \quad \left| \quad V_{RPost} = (15V + 0.6V) \cdot 78 / 12 = 101.4V$$

Post-calculated maximum duty cycle:

$$D_{MaxPost} = \frac{V_{RPost}}{V_{RPost} + V_{DCMin}} \quad (\text{Eq 45}) \quad \left| \quad D_{MaxPost} = \frac{101.4V}{101.4V + 93.63V} = 0.52$$

Duty cycle prime:

$$D'_{Max} = \frac{L_P \cdot f_s \cdot (I_{PMax} - I_{Valley})}{V_{RPost}} \quad (\text{Eq 46}) \quad \left| \quad D'_{Max} = \frac{556.7\mu H \cdot 100kHz \cdot (0.86A - 0A)}{101.4V} = 0.47$$

Actual flux density:

$$B_{MaxAct} = \frac{L_P \cdot I_{PMax}}{N_P \cdot A_e} \quad (\text{Eq 47}) \quad \left| \quad B_{MaxAct} = \frac{556.7\mu H \cdot 0.86A}{78 \cdot 32mm^2} = 191mT$$

Maximum DC input voltage for CCM operation:

$$V_{DCmax CCM} = \left(\frac{1}{\sqrt{2 \cdot P_{InMax} \cdot L_P \cdot f_s}} - \frac{1}{V_{RPost}} \right)^{-1} \quad (\text{Eq 48}) \quad \left| \quad V_{DCmax CCM} = \left(\frac{1}{\sqrt{2 \cdot 20.48W \cdot 557\mu H \cdot 100kHz}} - \frac{1}{101.4V} \right)^{-1} = 90.3V$$

8.6 Transformer winding design

Transformer design plays a significant role in efficiency. Interlacing primary and output windings can reduce leakage inductance, and this is one way to improve efficiency. It is also critical for safety concerns, especially in isolated applications. Therefore, creepage and clearance should also be given serious consideration.

Standard safety margins between primary and secondary winding:

M = 4 mm for European safety standard

M = 3.2 mm for UL1950

M = 0 mm for triple-insulated wire on either primary or secondary winding

Standard safety margin	M	0 mm
Copper space factor	f_{Cu}	0.4 (0.2–0.4)

Effective bobbin width:

$$BW_E = BW - (2 \times M) \quad (\text{Eq 49}) \quad BW_E = 11\text{mm} - (2 \times 0) = 11\text{mm}$$

Effective winding cross-section:

$$A_{Ne} = \frac{A_N \times BW_e}{BW} \quad (\text{Eq 50}) \quad A_{Ne} = \frac{34\text{mm}^2 \times 11\text{mm}}{11\text{mm}} = 34\text{mm}^2$$

The effective winding cross-section must be divided between the primary and secondary windings. The design example is divided as follows:

Winding	Factor
Primary winding (AF_{NP})	50 percent
Secondary winding 1 (AF_{NS1})	30 percent
Secondary winding 2 (AF_{NS2})	15 percent
Auxiliary winding (AF_{NVCC})	5 percent

8.6.1 Primary winding

Calculate copper wire cross-sectional area:

$$A_{PCal} = \frac{AF_{NP} \times f_{Cu} \times A_{Ne}}{N_P} \quad (\text{Eq 51}) \quad A_{PCal} = \frac{0.5 \times 0.4 \times 34\text{mm}^2}{78} = 0.087\text{mm}^2$$

Calculate maximum wire size:

$$AWG_{PCal} = 9.97 \cdot \left(1.8277 - \left(2 \cdot \log \left(2 \cdot \sqrt{\frac{A_{PCal}}{\pi}} \right) \right) \right) \quad (\text{Eq 52}) \quad AWG_{PCal} = 9.97 \cdot \left(1.8277 - \left(2 \cdot \log \left(2 \cdot \sqrt{\frac{0.087}{\pi}} \right) \right) \right) = 28$$

Selected wire size	AWG _P	30
Number of parallel wires	n_P	1

Copper wire diameter:

$$d_P = 10^{\left(\frac{1.8277 - AWG_P}{2} - \frac{2.997}{2.997} \right)} \quad (\text{Eq 53}) \quad d_P = 10^{\left(\frac{1.8277 - 30}{2} - \frac{2.997}{2.997} \right)} = 0.26\text{mm}$$

Fifth-generation fixed-frequency FLYCAL design example

Copper wire cross-sectional area:

$$A_p = \frac{\pi}{4} \cdot d_p^2 \cdot n_p \quad (\text{Eq 54}) \quad \left| \quad A_p = \frac{\pi}{4} \cdot (0.26\text{mm})^2 \cdot 1 = 0.0517\text{mm}^2 \right.$$

Wire current density:

$$S_p = \frac{I_{PRMS}}{A_p} \quad (\text{Eq 55}) \quad \left| \quad S_p = \frac{0.35\text{A}}{0.052\text{mm}^2} = 6.8\text{A/mm}^2 \right.$$

Note: Recommended wire current density is less than 8 A/mm².

Number of turns per layer using INS = 0.01 mm:

$$NL_p = \frac{BW_E}{n_p \cdot (d_p + 2 \cdot INS)} \quad (\text{Eq 56}) \quad \left| \quad NL_p = \frac{1\text{mm}}{1 \cdot (0.26\text{mm} + 2 \cdot 0.01\text{mm})} = 39\text{Turns/layer} \right.$$

Note: Insulation thickness (INS) for single-, double- and triple-insulated wire is 0.01, 0.02 and 0.04 mm respectively. Ask the magnetics supplier for the actual insulation thickness.

Number of layers:

$$Ln_p = N_p / NL_p \quad (\text{Eq 57}) \quad \left| \quad Ln_p = 78\text{Turns} / (39\text{Turns/layer}) = 2\text{layers} \right.$$

8.6.2 Secondary 1 winding (V_{out1})

Calculate copper wire cross-sectional area:

$$A_{NS1Cal} = \frac{AF_{NS1} \times f_{Cu} \times A_{Ne}}{N_{S1}} \quad (\text{Eq 58}) \quad \left| \quad A_{NS1Cal} = \frac{0.30 \times 0.4 \times 34\text{mm}^2}{12} = 0.34\text{mm}^2 \right.$$

Calculate maximum wire size:

$$AWG_{NS1Cal} = 9.97 \cdot \left(1.8277 - \left(2 \cdot \log \left(2 \cdot \sqrt{\frac{A_{NS1Cal}}{\pi}} \right) \right) \right) \quad (\text{Eq 59}) \quad \left| \quad AWG_{NS1Cal} = 9.97 \cdot \left(1.8277 - \left(2 \cdot \log \left(2 \cdot \sqrt{\frac{0.34\text{mm}^2}{\pi}} \right) \right) \right) = 22 \right.$$

Selected wire size

AWG_{S1} 26

Number of parallel wires

n_{S1} 2

Copper wire diameter:

$$d_{S1} = 10^{\left(\frac{1.8277 - AWG_{S1}}{2.997} \right)} \quad (\text{Eq 60}) \quad \left| \quad d_{S1} = 10^{\left(\frac{1.8277 - 26}{2.997} \right)} = 0.407\text{mm} \right.$$

Copper wire cross-sectional area:

$$A_{S1} = \frac{\pi}{4} \cdot d_{S1}^2 \cdot n_{S1} \quad (\text{Eq 61}) \quad \left| \quad A_{S1} = \frac{\pi}{4} \cdot (0.407)^2 \cdot 2 = 0.261\text{mm}^2 \right.$$

Fifth-generation fixed-frequency FLYCAL design example

Peak current:

$$I_{S1Max} = I_{PMax} \cdot K_{L1} \cdot N_{PS1} \quad (\text{Eq 62}) \quad \left| \quad I_{S1Max} = 0.86 \text{ A} \cdot 0.86 \cdot 6.5 = 4.8 \text{ A} \right.$$

RMS current:

$$I_{S1RMS} = I_{PRMS} \cdot K_{L1} \cdot \sqrt{\frac{1 - D_{MaxPost}}{D_{MaxPost}}} \cdot N_{PS1} \quad (\text{Eq 63}) \quad \left| \quad I_{S1RMS} = 0.35 \text{ A} \cdot 0.86 \cdot \sqrt{\frac{1 - 0.52}{0.52}} \cdot 6.5 = 1.9 \text{ A} \right.$$

Wire current density:

$$S_{S1} = \frac{I_{S1RMS}}{A_{S1}} \quad (\text{Eq 64}) \quad \left| \quad S_{S1} = \frac{1.9 \text{ A}}{0.261 \text{ mm}^2} = 7.3 \text{ A/mm}^2 \right.$$

Number of turns per layer using INS = 0.01 mm (non-isolated design does not need triple-insulated wire):

$$NL_{S1} = \left\lfloor \frac{BW_E}{nw_{S1} \cdot (d_{S1} + 2 \cdot INS_{S1})} \right\rfloor \quad (\text{Eq 65}) \quad \left| \quad NL_{S1} = \left\lfloor \frac{1 \text{ mm}}{2 \cdot (0.407 \text{ mm} + 2 \cdot 0.01 \text{ mm})} \right\rfloor = 12 \text{ Turns/layer} \right.$$

Number of layers of secondary 1 winding:

$$Ln_{S1} = \lceil N_{S1} / NL_{S1} \rceil \quad (\text{Eq 66}) \quad \left| \quad Ln_{S1} = \lceil 12 \text{ Turns} / (12 \text{ Turns/layer}) \rceil = 1 \text{ layers} \right.$$

8.6.3 Secondary 2 winding (V_{out2})

Calculate copper wire cross-sectional area:

$$A_{NS2Cal} = \frac{AF_{NS2} \times f_{Cu} \times A_{Ne}}{N_{S2}} \quad (\text{Eq 67}) \quad \left| \quad A_{NS2Cal} = \frac{0.15 \times 0.4 \times 34 \text{ mm}^2}{4} = 0.51 \text{ mm}^2 \right.$$

Calculate maximum wire size:

$$AWG_{NS2Cal} = 9.97 \cdot \left(1.8277 - \left(2 \cdot \log \left(2 \cdot \sqrt{\frac{A_{NS2Cal}}{\pi}} \right) \right) \right) \quad (\text{Eq 68}) \quad \left| \quad AWG_{NS2Cal} = 9.97 \cdot \left(1.8277 - \left(2 \cdot \log \left(2 \cdot \sqrt{\frac{0.34}{\pi}} \right) \right) \right) = 20 \right.$$

Selected wire size

AWG_{S2} 26

Number of parallel wires

n_{S2} 1

Copper wire diameter:

$$d_{S2} = 10^{\left(\frac{1.8277 - AWG_{S2}}{2.997} \right)} \quad (\text{Eq 69}) \quad \left| \quad d_{S2} = 10^{\left(\frac{1.8277 - 26}{2.997} \right)} = 0.407 \text{ mm} \right.$$

Copper wire area:

$$A_{S2} = \frac{\pi}{4} \cdot d_{S2}^2 \cdot n_{S2} \quad (\text{Eq 70}) \quad \left| \quad A_{S2} = \frac{\pi}{4} \cdot (0.407)^2 \cdot 1 = 0.13 \text{ mm}^2 \right.$$

Peak current:

$$I_{S2Max} = I_{PMax} \cdot K_{L2} \cdot N_{PS2} \quad (\text{Eq 71}) \quad \left| \quad I_{S2Max} = 0.86 \text{ A} \cdot 0.14 \cdot 19.5 = 2.3 \text{ A} \right.$$

Fifth-generation fixed-frequency FLYCAL design example

RMS current:

$$I_{S2RMS} = I_{PRMS} \cdot K_{L2} \cdot \sqrt{\frac{1 - D_{MaxPost}}{D_{MaxPost}}} \cdot N_{PS2} \quad (\text{Eq 72}) \quad \left| \quad I_{S2RMS} = 0.35 \text{ A} \cdot 0.14 \cdot \sqrt{\frac{1 - 0.52}{0.52}} \cdot 19.5 = 0.9 \text{ A} \right.$$

Wire current density:

$$S_{S2} = \frac{I_{S2RMS}}{A_{S2}} \quad (\text{Eq 73}) \quad \left| \quad S_{S2} = \frac{0.9 \text{ A}}{0.130 \text{ mm}^2} = 7 \text{ A/mm}^2 \right.$$

Number of turns per layer using INS = 0.01 mm (non-isolated design does not need triple-insulated wire):

$$NL_{S2} = \left\lfloor \frac{BW_E}{nw_{S2} \cdot (d_{S2} + 2 \cdot INS_{S2})} \right\rfloor \quad (\text{Eq 74}) \quad \left| \quad NL_{S2} = \left\lfloor \frac{1 \text{ mm}}{1 \cdot (0.407 \text{ mm} + 2 \cdot 0.01 \text{ mm})} \right\rfloor = 25 \text{ Turns/layer} \right.$$

Number of layers:

$$Ln_{S2} = \lceil N_{S2} / NL_{S2} \rceil \quad (\text{Eq 75}) \quad \left| \quad Ln_{S2} = \lceil 4 \text{ Turns} / 25 \text{ Turns/layer} \rceil = 1 \text{ layer} \right.$$

8.7 Clamping network

For calculating the clamping network, it is necessary to know the leakage inductance L_{LK} . The most common approach is to have the L_{LK} value given in a percentage of the L_p . If it is known that the transformer construction is consistent, the L_{LK} can be measured by shorting the secondary windings (assuming the availability of a good LCR meter).

Leakage inductance:

$$\begin{array}{ll} \text{Leakage inductance percentage} & L_{LK\%} \\ L_{LK} = L_{LK\%} \cdot L_p & (\text{Eq 76}) \end{array} \quad \left| \quad \begin{array}{l} 2.5 \text{ percent} \\ L_{LK} = 2.5\% \times 556.7 \mu\text{H} = 13.9 \mu\text{H} \end{array} \right.$$

Clamping voltage:

$$V_{Clamp} = V_{DSMax} - V_{DCMaxPk} - V_{RPost} \quad (\text{Eq 77}) \quad \left| \quad V_{Clamp} = 700 \text{ V} - 466.7 \text{ V} - 101.4 \text{ V} = 131.9 \text{ V} \right.$$

Calculate clamping capacitor:

$$C_{ClampCal} = \frac{I_{PMax}^2 \cdot L_{LK}}{(V_{RPost} + V_{Clamp}) \cdot V_{Clamp}} \quad (\text{Eq 78}) \quad \left| \quad C_{ClampCal} = \frac{(0.86 \text{ A})^2 \times 13.9 \mu\text{H}}{(101.4 \text{ V} + 131.9 \text{ V}) \times 131.9 \text{ V}} = 334 \text{ pF} \right.$$

Clamping capacitor

$$C_{Clamp} \quad \left| \quad 1 \text{ nF} \right.$$

Calculate clamping resistor:

$$R_{ClampCal} = \frac{(V_{Clamp} + V_{RPost})^2 - V_{RPost}^2}{0.5 \cdot L_{LK} \cdot I_{PMax}^2 \cdot f_s} \quad (\text{Eq 79}) \quad \left| \quad R_{ClampCal} = \frac{(131.9 \text{ V} + 101.4 \text{ V})^2 - (101.4 \text{ V})^2}{0.5 \times 13.9 \mu\text{H} \times (0.86 \text{ A})^2 \times 100 \text{ kHz}} = 86 \text{ k}\Omega \right.$$

Clamping resistor

$$R_{Clamp} \quad \left| \quad 68 \text{ k}\Omega \right.$$

8.8 CS resistor

The CS resistor value defines the peak current of the power MOSFET. Therefore, the transformer should be designed not to saturate at this peak current value. Because the IC cycle-by-cycle PCL is defined by this resistor, it also defines the maximum output power that can be delivered.

CS resistor:

PCL threshold	V_{CS_N}	0.8 V
$R_{Sense} = \frac{V_{CS_N}}{I_{PMax}}$	(Eq 80)	$R_{Sense} = \frac{0.8\text{ V}}{0.86\text{ A}} = 0.93\Omega$

8.9 Output rectifier

A low forward voltage and an ultrafast diode such as a Schottky diode are recommended for a highly efficient design. These diodes are subjected to large peak and RMS current stress. The minimum voltage rating (not including voltage spikes) and minimum current rating (not including peak power transients) are calculated below.

The output capacitor is necessary to minimize the output ripple. It also holds the necessary energy needed during high load jumps. Therefore, the output capacitor should have enough capacitance and low ESR. It should also meet the ripple current rating.

An LC filter can be added to further reduce the output ripple.

8.9.1 Output 1

Diode reverse voltage:

$V_{RDioda} = V_{Out1} + \left(\frac{V_{DCMaxPK}}{N_{PS1}} \right)$	(Eq 81)	$V_{RDioda} = 15\text{ V} + \left(\frac{466.7\text{ V}}{6.5} \right) = 86.8\text{ V}$
--	----------------	--

Diode RMS current	I_{S1RMS}	1.9 A
-------------------	-------------	----------------

Output capacitor ripple current:

Maximum voltage undershoot	ΔV_{Out1}	0.3 V
Number of clock periods	n_{CP1}	20
$I_{Rippla} = \sqrt{(I_{S1RMS})^2 - (I_{Out1})^2}$	(Eq 82)	$I_{Rippla} = \sqrt{(1.9\text{ A})^2 - (0.83\text{ A})^2} = 1.71\text{ A}$

Calculated output capacitance:

$C_{Out1Cal} = \frac{I_{Out1} \cdot n_{CP1}}{\Delta V_{OUT1} \cdot f_s}$	(Eq 83)	$C_{Out1Cal} = \frac{0.83\text{ A} \cdot 20}{0.3\text{ V} \cdot 100\text{ kHz}} = 553\text{ }\mu\text{F}$
--	----------------	---

Output capacitor	C_{Out1}	$680\text{ }\mu\text{F}$
------------------	------------	--------------------------

ESR	R_{ESR1}	$32\text{ m}\Omega$
-----	------------	---------------------

Number of output capacitors in parallel	n_{COut1}	1
---	-------------	-----

Fifth-generation fixed-frequency FLYCAL design example

Zero-frequency output capacitor:

$$f_{ZCOut1} = \frac{1}{2 \cdot \pi \cdot R_{ESR1} \cdot C_{Out1}} \quad (\text{Eq 84}) \quad \left| \quad f_{ZCOut1} = \frac{1}{2 \cdot \pi \cdot 32m\Omega \cdot 680\mu F} = 7.3kHz \right.$$

Ripple voltage of first stage:

$$V_{Ripple1} = \frac{I_{S1Max} \cdot R_{ESR1}}{nC_{Out1}} \quad (\text{Eq 85}) \quad \left| \quad V_{Ripple1} = \frac{4.8A \cdot 32m\Omega}{1} = 0.15V \right.$$

Calculated LC filter capacitor:

Select LC filter inductor

$$C_{LCCall} = \frac{(C_{Out1} \cdot R_{ESR1})^2}{L_{Out1}} \quad (\text{Eq 86}) \quad \left| \quad C_{LCCall} = \frac{(680\mu F \cdot 32m\Omega)^2}{2.2\mu H} = 215\mu F \right.$$

LC filter capacitor

$$C_{LC1} \quad 680 \mu F$$

LC filter frequency:

$$f_{LC1} = \frac{1}{2 \cdot \pi \cdot \sqrt{C_{LC1} \cdot L_{OUT1}}} \quad (\text{Eq 87}) \quad \left| \quad f_{LC1} = \frac{1}{2 \cdot \pi \cdot \sqrt{680 \mu F \cdot 2.2\mu H}} = 4.1kHz \right.$$

Second stage ripple voltage:

$$V_{2ndRipple} = V_{Ripple1} \cdot \frac{\frac{1}{2 \cdot \pi \cdot f_s \cdot C_{LC1}}}{\frac{1}{2 \cdot \pi \cdot f_s \cdot C_{LC1}} + (2 \cdot \pi \cdot f_s \cdot L_{OUT1})} \quad (\text{Eq 88}) \quad \left| \quad V_{2ndRipple} = 0.15V \cdot \frac{\frac{1}{2 \cdot \pi \cdot 100kHz \cdot 680\mu F}}{\frac{1}{2 \cdot \pi \cdot 100kHz \cdot 680\mu F} + (2 \cdot \pi \cdot 100kHz \cdot 2.2\mu H)} = 0.26mV \right.$$

8.9.2 Output 2

Diode reverse voltage:

$$V_{RDiod2} = V_{Out2} + \left(\frac{V_{DCMaxPk}}{N_{PS2}} \right) \quad (\text{Eq 89}) \quad \left| \quad V_{RDiod2} = 5V + \left(\frac{466.7V}{19.5} \right) = 28.9V \right.$$

Diode RMS current

$$I_{S2RMS} \quad 0.92 A$$

Output capacitor ripple current for V_{Out2} :

Maximum voltage undershoot (V_{Out2})

$$\Delta V_{Out2} \quad 0.15 V$$

Number of clock periods

$$n_{CP2} \quad 20$$

$$I_{Ripple2} = \sqrt{(I_{S2RMS})^2 - (I_{Out2})^2}$$

$$(\text{Eq 90}) \quad \left| \quad I_{Ripple2} = \sqrt{(0.92A)^2 - (0.4A)^2} = 0.83A \right.$$

Calculated output capacitance:

$$C_{Out2} = \frac{I_{Out2} \cdot n_{CP2}}{\Delta V_{OUT2} \cdot f_s} \quad (\text{Eq 91}) \quad \left| \quad C_{Out2} = \frac{0.4A \cdot 20}{0.15V \cdot 100kHz} = 533 \mu F \right.$$

Output capacitor

$$C_{Out2} \quad 680 \mu F$$

ESR

$$R_{ESR2} \quad 32 m\Omega$$

Number of output capacitors in parallel

$$nC_{Out2} \quad 1$$

Fifth-generation fixed-frequency FLYCAL design example

Zero-frequency output capacitor:

$$f_{ZCO_{out2}} = \frac{1}{2 \cdot \pi \cdot R_{ESR2} \cdot C_{Out2}} \quad (\text{Eq 92}) \quad \left| \quad f_{ZCO_{out2}} = \frac{1}{2 \cdot \pi \cdot 32m\Omega \cdot 680\mu F} = 7.3kHz \right.$$

Ripple voltage of first stage:

$$V_{Ripple2} = \frac{I_{S2Max} \cdot R_{ESR2}}{nC_{Out2}} \quad (\text{Eq 93}) \quad \left| \quad V_{Ripple2} = \frac{2.31A \cdot 32m\Omega}{1} = 0.07V \right.$$

Calculated LC filter capacitor:

$$C_{LCCal2} = \frac{(C_{Out2} \cdot R_{ESR2})^2}{L_{out2}} \quad (\text{Eq 94}) \quad \left| \quad C_{LCCal2} = \frac{(680\mu F \cdot 32m\Omega)^2}{2.2\mu H} = 215\mu F \right.$$

LC filter capacitor

$$C_{LC2} \quad 330 \mu F$$

LC filter frequency:

$$f_{LC2} = \frac{1}{2 \cdot \pi \cdot \sqrt{C_{LC2} \cdot L_{OUT2}}} \quad (\text{Eq 95}) \quad \left| \quad f_{LC2} = \frac{1}{2 \cdot \pi \cdot \sqrt{330 \mu F \cdot 2.2\mu H}} = 5.9kHz \right.$$

Second stage ripple voltage:

$$V_{2ndRipple2} = V_{Ripple2} \cdot \frac{\frac{1}{2 \cdot \pi \cdot f_s \cdot C_{LC2}}}{\frac{1}{2 \cdot \pi \cdot f_s \cdot C_{LC2}} + (2 \cdot \pi \cdot f_s \cdot L_{OUT2})} \quad (\text{Eq 96}) \quad \left| \quad V_{2ndRipple2} = 0.07V \cdot \frac{\frac{1}{2 \cdot \pi \cdot 100kHz \cdot 330\mu F}}{\frac{1}{2 \cdot \pi \cdot 100kHz \cdot 330\mu F} + (2 \cdot \pi \cdot 100kHz \cdot 2.2\mu H)} = 0.26mV \right.$$

8.10 V_{CC} diode and capacitor

Auxiliary diode reverse voltage:

$$V_{RDiodeVCC} = V_{VccCal} + \left(V_{DCMaxPk} \cdot \frac{N_{Vcc}}{N_P} \right) \quad (\text{Eq 97}) \quad \left| \quad V_{RDiodeVCC} = 13.7V + \left(466.7 \times \frac{11}{78} \right) = 79.5V \right.$$

Calculate minimum V_{CC} capacitor:

Soft-start time from datasheet

$$t_{SS} \quad 12 \text{ ms}$$

I_{VCC_Charge3} from datasheet

$$I_{VCC_Charge3} \quad 3 \text{ mA}$$

V_{VCC_ON} from datasheet

$$V_{VCC_ON} \quad 16 \text{ V}$$

V_{VCC_OFF} from datasheet

$$V_{VCC_OFF} \quad 10 \text{ V}$$

$$C_{VccCal} > \frac{I_{VCC_Charge3} \cdot t_{SS}}{V_{VCC_ON} - V_{VCC_OFF}}$$

$$(\text{Eq 98}) \quad C_{VccCal} > \frac{3mA \cdot 12ms}{16V - 10V} = 6\mu F$$

Selected V_{CC} capacitor

$$C_{VCC} \quad 22 \mu F$$

Start-up time:

V_{CC} short threshold from datasheet

$$V_{VCC_SCP} \quad 1.1 \text{ V}$$

I_{VCC_Charge1} from datasheet

$$I_{VCC_Charge1} \quad 0.2 \text{ mA}$$

$$t_{StartUp} = \frac{V_{VCC_SCP} \cdot C_{VCC}}{I_{VCC_Ch arg e1}} + \frac{(V_{VCC_ON} - V_{VCC_SCP}) \cdot C_{VCC}}{I_{VCC_Ch arg e3}} \quad (\text{Eq 99}) \quad \left| \quad t_{StartUp} = \frac{1.1V \cdot 22\mu F}{0.2mA} + \frac{(16V - 1.1V) \cdot 22\mu F}{3mA} = 230ms \right.$$

8.11 Calculation of losses

Input diode bridge loss:

Diode bridge forward voltage

$$P_{DIN} = I_{ACRMS} \cdot V_{FBR} \cdot 2$$

V_{FBR}

1 V

(Eq 100)

$$P_{DIN} = 0.4A \cdot 1V \cdot 2 = 0.8W$$

Transformer copper loss:

Copper resistivity at 100°C

ρ_{100}

0.0172 $\Omega \cdot mm^2/m$

$$R_{PCu} = \frac{I_N \cdot N_P \cdot \rho_{100}}{A_P}$$

(Eq 101)

$$R_{PCu} = \frac{41.2mm \cdot 78 \cdot 0.0172\Omega \cdot mm^2 / m}{0.052mm^2} = 1068.5m\Omega$$

$$R_{S1Cu} = \frac{I_N \cdot N_{S1} \cdot \rho_{100}}{A_{S1}}$$

(Eq 102)

$$R_{S1Cu} = \frac{41.2mm \cdot 12 \cdot 0.0172\Omega \cdot mm^2 / m}{0.2602mm^2} = 32.6m\Omega$$

$$R_{S2Cu} = \frac{I_N \cdot N_{S2} \cdot \rho_{100}}{A_{S2}}$$

(Eq 103)

$$R_{S1Cu} = \frac{41.2mm \cdot 4 \cdot 0.0172\Omega \cdot mm^2 / m}{0.13mm^2} = 21.8m\Omega$$

$$P_{PCu} = I_{PRMS}^2 \cdot R_{PCu}$$

(Eq 104)

$$P_{PCu} = (0.35A)^2 \cdot 1068.5m\Omega = 133.63mW$$

$$P_{S1Cu} = I_{S1RMS}^2 \cdot R_{S1Cu}$$

(Eq 105)

$$P_{S1Cu} = (1.9A)^2 \cdot 32.6m\Omega = 118mW$$

$$P_{S2Cu} = I_{S2RMS}^2 \cdot R_{S2Cu}$$

(Eq 106)

$$P_{S2Cu} = (0.92A)^2 \cdot 21.8m\Omega = 18mW$$

$$P_{Cu} = P_{PCu} + P_{S1Cu} + P_{S2Cu}$$

(Eq 107)

$$P_{Cu} = 133mW + 118mW + 18mW = 270mW$$

Output rectifier diode loss:

$$P_{Diod1} = I_{S1RMS} \cdot V_{FOut1}$$

(Eq 108)

$$P_{Diod1} = 1.9A \cdot 0.6V = 1.14W$$

$$P_{Diod2} = I_{S2RMS} \cdot V_{FOut2}$$

(Eq 109)

$$P_{Diod2} = 0.92A \cdot 0.2V = 0.18W$$

RCD clamper loss:

$$P_{Clamper} = \frac{1}{2} \cdot L_{LK} \cdot I_{PMax}^2 \cdot f_S \cdot \frac{V_{Clamp} + V_{RPost}}{V_{Clamp}}$$

(Eq 110)

$$P_{Clamper} = \frac{1}{2} \cdot 13.9\mu H \cdot (0.86A)^2 \cdot 100kHz \cdot \frac{132V + 101.4V}{132V} = 0.91W$$

CS resistor loss:

$$P_{CS} = (I_{PRMS})^2 \cdot R_{CS}$$

(Eq 111)

$$P_{CS} = (0.35A)^2 \cdot 0.93\Omega = 0.12W$$

MOSFET loss:

$R_{DS(on)}$ at $T_J = 125^\circ C$ from datasheet

$R_{DS(on)}$

8.69 Ω

$C_{o(er)}$ from datasheet

$C_{o(er)}$

3 pF

External drain-to-source capacitance

C_{DS}

0 pF

$$P_{SONMinAC} = \frac{1}{2} \cdot (C_{o(er)} + C_{DS}) \cdot (V_{DCMin} + V_{RPost})^2 \cdot f_S$$

(Eq 112)

$$P_{SONMinAC} = \frac{1}{2} \cdot (3pF + 0pF) \cdot (93.6V + 101.4V)^2 \cdot 100kHz = 5.7mW$$

Fifth-generation fixed-frequency FLYCAL design example

$P_{condMinAC} = I_{PRMS}^2 \cdot R_{DSon}$	(Eq 113)	$P_{condMinAC} = (0.35A)^2 \cdot 8.69\Omega = 1.087W$
$P_{MOSMinAC} = P_{SONMinAC} + P_{condMinAC}$	(Eq 114)	$P_{MOSMinAC} = 5.7mW + 1.087W = 1.093W$
$P_{SONMaxAC} = \frac{1}{2} \cdot (C_{o(er)} + C_{DS}) \cdot (V_{DCMaxPk} + V_{RPost})^2 \cdot f_s$	(Eq 115)	$P_{SONMaxAC} = \frac{1}{2} \cdot (3pF + 0pF) \cdot (466.7V + 101.4V)^2 \cdot 100kHz = 48.4mW$
$P_{condMaxAC} = \frac{1}{3} \cdot R_{DSon} \cdot I_{PMax}^2 \cdot \left(\frac{L_p \cdot I_{PMax} \cdot f_s}{V_{DCMaxPk}} \right)$	(Eq 116)	$P_{condMaxAC} = \frac{1}{3} \cdot 8.69\Omega \cdot (0.86A)^2 \cdot \left(\frac{557\mu H \cdot 0.86A \cdot 100kHz}{466.7V} \right) = 0.22W$
$P_{MOSMaxAC} = P_{SONMaxAC} + P_{condMaxAC}$	(Eq 117)	$P_{MOSMaxAC} = 48.4mW + 0.22W = 0.27W$

Controller loss:

Controller current consumption	I_{VCC_Normal}	0.9 mA
$P_{Ctrl} = V_{VCCal} \cdot I_{VCC_Normal}$	(Eq 118)	$P_{Ctrl} = 13.7V \cdot 0.9mA = 12.3mW$

Total power loss:

$P_{losses} = P_{DIN} + P_{Cu} + P_{Diode1} + P_{Diode2} + P_{Clamper} + P_{CS} + P_{MOS} + P_{Ctrl}$	(Eq 119)	$P_{losses} = 0.8 + 0.27 + 1.14 + 0.18 + 0.91 + 0.12 + 1.1 + 0.01 = 4.53W$
---	----------	--

Efficiency after losses:

$\eta_{Post} = P_{OutMax} / (P_{OutMax} + P_{losses})$	(Eq 120)	$\eta_{Post} = 17W / (17W + 4.53W) = 78.97\%$
--	----------	---

8.12 CoolSET™/MOSFET temperature

CoolSET™/MOSFET temperature:

Assumed junction-to-ambient thermal impedance (include copper pour)	R_{thJA_As}	65 K/W
$\Delta T = R_{thJA_As} \cdot P_{MOS}$	(Eq 121)	$\Delta T = 65 K / W \cdot 1.093W = 71^\circ K$
$T_{jmax} = \Delta T + T_{amax}$	(Eq 122)	$T_{jmax} = 71 + 50 = 121^\circ C$

8.13 Output regulation (non-isolated)

Setting resistor dividers for two non-isolated outputs:

Error amplifier reference voltage	V_{ERR_REF}	1.8 V
Weighted regulation factor of V_{Out1}	W_1	31 percent
Select voltage divider RO1	R_{O1}	39 kΩ
$R_{O2Cal} = \frac{V_{Out1} - V_{ERR_REF}}{W_1 \cdot V_{ERR_REF} / R_{O1}}$	(Eq 123)	$R_{O2Cal} = \frac{15V - 1.8V}{31\% \cdot 1.8V / 39k\Omega} = 922k\Omega$
Select voltage divider RO2	R_{O2}	910 kΩ
$R_{O3Cal} = \frac{V_{Out2} - V_{ERR_REF}}{\frac{V_{ERR_REF}}{R_{O1}} - \frac{V_{Out1} - V_{ERR_REF}}{R_{O2}}}$	(Eq 124)	$R_{O3Cal} = \frac{5V - 1.8V}{\frac{1.8V}{39k\Omega} - \frac{15V - 1.8V}{910k\Omega}} = 101k\Omega$
Select voltage divider RO3	R_{O3}	100 kΩ

9 References

- [1] ICE5ARxxxxBZS datasheet, Infineon Technologies AG
- [2] ER_201708_PL83_017 14 W 15 V 5 V SMPS demo board with ICE5AR4780BZS
- [3] Infineon-CalculationTool_Fixed_Frequency_CoolSET_ICE5ARxxxxBZS_Generation5-DT-v01_00-EN

Revision history

Revision history

Document version	Date of release	Description of changes
V 1.1	24 Jul 2019	Page 20, section 4.7.4 Addition of statement when CS pin is shorted to GND
V 1.0	16 Jan 2018	First release

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2019-07-24

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2022 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference

DG_1801_PL83_1802_071129

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.