

ICE3Bxx65J(G)

CoolSET[®] F3 Jitter Version Design Guide
(DIP-8 & DSO-16/12)

Power Management & Supply



N e v e r s t o p t h i n k i n g .

Published by
Infineon Technologies AG
81726 Munich, Germany
© 2013 Infineon Technologies AG
All Rights Reserved.

Legal Disclaimer

The information given in this document shall in no event be regarded as a guarantee of conditions or characteristics. With respect to any examples or hints given herein, any typical values stated herein and/or any information regarding the application of the device, Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind, including without limitation, warranties of non-infringement of intellectual property rights of any third party.

Information

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office (www.infineon.com).

Warnings

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office. Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

ICE3Bxx65J(G)

Revision History: 2013-03

V1.0

Previous Version:

| Page | Subjects (major changes since last revision) |
|------|--|
| | |
| | |
| | |
| | |
| | |
| | |
| | |
| | |

CoolSET® F3 Jitter Version Design Guide (DIP-8 & DSO-16/12):
License to Infineon Technologies Asia Pacific Pte Ltd

AN-PS0076

Kyaw Zin Min
Kok Siu Kam Eric

We Listen to Your Comments

Any information within this document that you feel is wrong, unclear or missing at all?
Your feedback will help us to continuously improve the quality of this document.
Please send your proposal (including a reference to this document) to:

ap-lab.admin@infineon.com



| Table of Contents | Page |
|--|-----------|
| 1 Introduction | 5 |
| 2 List of Features | 5 |
| 3 Package | 6 |
| 4 Block Diagram | 7 |
| 5 Typical Application Circuit | 8 |
| 6 Functional description and component design | 9 |
| 6.1 Startup time | 9 |
| 6.2 Soft Start..... | 9 |
| 6.2.1 Vcc capacitor | 10 |
| 6.3 Low standby power - Active Burst Mode | 10 |
| 6.3.1 Entering Active Burst Mode | 10 |
| 6.3.2 Working in Active Burst Mode..... | 11 |
| 6.3.3 Leaving Active Burst Mode..... | 12 |
| 6.3.4 Minimum V _{CC} supply voltage during burst mode | 13 |
| 6.4 Low EMI noise | 13 |
| 6.4.1 Frequency jittering..... | 13 |
| 6.4.2 Other suggestions to solve EMI issue | 14 |
| 6.5 Tight control in maximum power (Propagation delay compensation) | 14 |
| 6.6 Protection Features..... | 15 |
| 6.6.1 Auto restart protection mode | 15 |
| 6.6.2 Blanking Time for over load protection..... | 15 |
| 7 Product portfolio of CoolSET®-F3 Jitter Version (DIP-8 & DSO-16/12) | 16 |
| 8 Useful formula for the SMPS design | 16 |
| 9 References | 17 |

1 Introduction

The CoolSET[®] - F3(Jitter Version), **ICE3Bxx65J(G)** is the further development of the third generation CoolSET[®] -F3 with a frequency jitter feature for better EMI and BiCMOS technology to provide a wider V_{cc} operating range and a lower controller power consumption. The switching frequency is running at 67 kHz and it targets for DVD player, set-top box, portable game console, white goods, smart meter, auxiliary power supply for server/PC, etc.


This application note provides detail functional description of the new features. The description of all other functions and calculations are shown in the datasheet as well as in the application note "AN-PS0076".

2 List of Features

| |
|---|
| 650V Avalanche Rugged CoolMOS [®] with built in Startup Cell |
| Active Burst Mode for lowest Standby Power @ light load controlled by Feedback Signal |
| Fast Load Jump Response in Active Burst Mode |
| 67 kHz fixed Switching Frequency |
| Auto Restart Mode for Over temperature Detection |
| Auto Restart Mode for Over voltage Detection |
| Auto Restart Mode for Over load and Open Loop |
| Auto Restart Mode for VCC Under voltage |
| User defined Soft Start |
| Minimum of external Components required |
| Max Duty Cycle 75% |
| Overall Tolerance of Current Limiting < ±5% |
| Internal Leading Edge Blanking |
| BiCMOS technology provides wide VCC Range |
| Frequency Jittering for Low EMI |

3 Package

 
The package for F3(Jitter Version) ICE3Bxx65J product is DIP-8.



| Pin | Name | Description |
|-----|-------|--|
| 1 | SoftS | Soft-Start |
| 2 | FB | Feedback |
| 3 | CS | Current Sense/650V CoolMOS [®] Source |
| 4 | Drain | 650V ¹ CoolMOS [®] Drain |
| 5 | Drain | 650V ¹ CoolMOS [®] Drain |
| 6 | N.C | Not Connected |
| 7 | VCC | Controller Supply Voltage |
| 8 | GND | Controller Ground |

Figure 1 Pin configuration - ICE3Bxx65J

 The package for F3(Jitter Version) ICE3Bxx65JG product is DSO-16/12



| Pin | Name | Description |
|-----|-------|--|
| 1 | N.C. | Not Connected |
| 2 | SoftS | Soft-Start |
| 3 | FB | FeedBack |
| 4 | CS | Current Sense/650V CoolMOS [®] Source |
| 5 | Drain | 650V ¹ CoolMOS [®] Drain |
| 6 | Drain | 650V ¹ CoolMOS [®] Drain |
| 7 | Drain | 650V ¹ CoolMOS [®] Drain |
| 8 | Drain | 650V ¹ CoolMOS [®] Drain |
| 9 | N.C. | Not Connected |
| 10 | N.C. | Not Connected |
| 11 | VCC | Controller Supply Voltage |
| 12 | GND | Controller Ground |

Figure 2 Pin configuration - ICE3Bxx65JG

¹ at T_J=110°C

4 Block Diagram

 


Figure 3 Block Diagram of ICE3Bxx65J(G)

5 Typical Application Circuit

 


Figure 4 Typical application circuit with ICE3B0565J 12W 5V

6 Functional description and component design

6.1 Startup time

Startup time is counted from applying input voltage to IC turn on. ICE3Bxx65J(G) has a startup cell which is connected to input bulk capacitor. When there is input voltage, the startup cell will act as a constant current source to charge up the Vcc capacitor and supply energy to the IC. When the Vcc capacitor reaches the Vcc_on threshold 18V, the IC turns on. Then the startup cell is turned off and the Vcc is supplied by the auxiliary winding. Start up time is independent from the AC line input voltage and it can be calculated by the equation (1). Figure 4 shows the start up time of 85Vac line input.

$$t_{startUp} = \frac{V_{VCCon} \times C_{VCC}}{I_{VCCcharge}} \quad (1)$$

where, $I_{VCCcharge}$: 0.965mA (average current of $I_{VCCcharge2}$ and $I_{VCCcharge3}$)
 V_{VCCon} : IC turns on threshold (18V)
 C_{VCC} : Vcc capacitor

Please refer to the datasheet for the symbol used in the equation.

 


Figure 5 The start-up time at AC line input voltage of 85Vac

Pre-caution : For a typical application, start up should be VCC ramps up first, other pin (such as FB pin) voltage will follow VCC voltage to ramp up. It is recommended not to have any voltage on other pins (such as FB; SoftS and CS) before VCC ramps up.

6.2 Soft Start

When the IC is turned on after the start-up time, the soft start capacitor at pin1, C_{SoftS} is immediately charged up to approximately 0.8V and from this point IC starts switching. The soft start voltage V_{SoftS} is generated by C_{SoftS} and the internal pull up resistor R_{SoftS} . The duty cycle of the gate drive is determined by the V_{SoftS} during the soft start phase, which is terminated when V_{SoftS} reaches 3.1V. Afterward, IC goes into normal mode and the duty cycle is dependent on the FB signal. The duration of the soft start can be estimated by the equation (2). Figure 6 shows the soft start behaviour at 85VAC input and full load. It can be seen that the primary peak current follows V_{SST} voltage and slowly increase to the maximum. The soft start time is approximately 35.6ms.

$$t_{SS} = C_{SoftS} \times R_{SoftS} \times \ln \frac{5 - 0.8}{5 - 3.1} = 0.793 \times C_{SoftS} \times R_{SoftS} \quad (2)$$

where, R_{SoftS} : internal soft start resistor (45k Ω)
 C_{SoftS} : Soft start capacitor

 


Figure 6 Soft start at AC line input voltage of 85 Vac & full load

6.2.1 Vcc capacitor

The minimum value of the Vcc capacitor is determined by voltage drop during the soft start time. The formula is expressed in equation (3).

$$C_{VCC} = \frac{I_{VCCsup_g_max} \times t_{ss}}{V_{VCC_{hys}}} \times \frac{2}{3} \quad (3)$$

where, $I_{VCCsup_g_max}$: supply current with active gate (3.6mA)
 t_{ss} : soft start time (35.6ms)
 $V_{VCC_{hys}}$: Vcc turn-on/off hysteresis voltage (7.7V)

Therefore, the minimum Vcc capacitance can be 11.09μF. In order to give more margins, 22μF is taken for the design. The startup time $t_{StartUp}$ is then 0.41s. The measured start up time is 0.49s (Figure 5). A 0.1μF filtering capacitor is always needed to add as near as possible to the Vcc pin to filter the high frequency noise.

6.3 Low standby power - Active Burst Mode

The IC will enter Active Burst Mode function at light load condition which enables the system to achieve the lowest standby power requirement of less than 100mW. Active Burst Mode means the IC is always in the active state and can therefore immediately response to any changes on the FB signal, V_{FB}.

6.3.1 Entering Active Burst Mode

Because of the current mode control scheme, the feedback voltage V_{FB} actually controls the power delivery to output. When the output load is getting lower, the feedback voltage V_{FB} drops. If it stays below 1.35V for a timeframe set by the blanking time, the IC enters into the burst mode operation. The threshold power to enter burst mode is:

$$P_{burst_enter} = \frac{1}{2} \times L_p \times \left(\frac{V_{FBC5} - V_{Max-Ramp}}{A_V \times R_{CS}} \right)^2 \times f_s \quad (4)$$

where, L_p : transformer primary inductance
 V_{FBC5} : feedback level to enter burst mode (1.35V)
 $V_{Max-Ramp}$: voltage ramp offset (0.6V)
 f_s : switching frequency
 A_V : PWM OP gain (3.2)
 R_{CS} : current sense resistor

Figure 7 shows the waveform with the load drops from nominal load to light load. After the 21ms blanking time IC goes into burst mode. The blanking time to enter burst mode is:

$$t_{blanking} = C_{softs} \times R_{softs} \times \ln \frac{5-3.4}{5-4} = 0.47 \times C_{softs} \times R_{softs} \quad (5)$$

where, R_{softs} : internal soft start resistor (45k Ω)
 C_{softs} : Soft start capacitor

 


Figure 7 Entering active burst mode

6.3.2 Working in Active Burst Mode

In the active burst mode, the IC is constantly monitoring the output voltage by feedback pin, V_{FB} , which controls burst duty cycle and burst frequency. The burst "ON" starts when V_{FB} reaches 3.61V and it stops when V_{FB} is dropped to 3V. During burst "ON", the primary current limit is reduced to V_{cs2} (32% of maximum peak current) to reduce the conduction losses and to avoid audible noise. The FB voltage is swinging like a saw tooth between 3V and 3.61V. The corresponding secondary output ripple (peak to peak) is controlled to be small. It can be calculated by equation (6).

$$V_{out_ripple_pp} = \frac{R_{opto} \times \Delta V_{fb}}{R_{fb} \times G_{opto} \times G_{TL431}} \quad (6)$$

where, R_{opto} :series resistor with opto-coupler at secondary side (e.g. Rc6 in Figure 4)
 R_{fb} :IC internal pull up resistor connected to FB pin ($R_{fb}=14K\Omega$)
 G_{opto} :current transfer gain of opto-coupler
 G_{TL431} :voltage transfer gain of the loop compensation network (e.g. Rc1, Rc2, Rc3, Rc4, Rc5, Rc6, Cc1, Cc2 in Figure 4)
 ΔV_{fb} : feedback voltage change (0.61V)

Figure 8 is the output ripple waveform of the 12W 5V demo board. The burst ripple voltage is about 19mV.

 


Figure 8 Output ripple during Active Burst Mode at light load

6.3.3 Leaving Active Burst Mode

When the output load increases to be higher than the maximum exit level of burst mode, V_{out} will drop a little and V_{FB} will rise up fast to exceed 4.5V. The system leaves burst mode immediately when V_{FB} reaches 4.5V. Once system leaves burst mode, the current sense voltage limit is set to $V_{csth}=1.06V$ & the feedback voltage V_{FB} swings back to the normal control level.

The leaving burst power threshold (i.e. maximum power to be handled during burst operation) is expressed in equation (7). However, the actual power can be higher as it would include propagation delay time.

$$\begin{aligned}
 P_{burst_leave} &= 0.5 \times L_p \times \left(\frac{V_{cs2}}{R_{CS}} \right)^2 \times f_s \\
 &= 0.5 \times L_p \times \left(\frac{V_{cs2}}{V_{csth}} \times \frac{V_{csth}}{R_{CS}} \right)^2 \times f_s \\
 &= \left(\frac{V_{cs2}}{V_{csth}} \right)^2 \times P_{in_max}
 \end{aligned} \tag{7}$$

where, V_{cs2} : peak current in the burst mode (0.32V)
 V_{csth} : maximum current limit threshold at CS pin
 P_{in_max} : maximum input power
 R_{CS} : current sense resistor
 L_p : primary inductance of transformer

The leave burst mode timing diagram is shown in Figure 9.

 


Figure 9 V_{out_drop} during leaving burst mode

The maximum output drop during the transition can be estimated in equation (8).

$$V_{out_drop_max} = \frac{R_{opto}}{R_{fb} \times G_{opto} \times G_{TL431}} \times \left(4.5 - \frac{3.6 + 3}{2} \right) = \frac{1.2 \times R_{opto}}{R_{fb} \times G_{opto} \times G_{TL431}} \tag{8}$$

where, R_{opto} : series resistor with opto-coupler at secondary side (e.g. Rc6 in Figure 4)
 R_{fb} : IC internal pull up resistor connected to FB pin ($R_{fb}=14K\Omega$)
 G_{opto} : current transfer gain of opto-coupler
 G_{TL431} : voltage transfer gain of the loop compensation network (e.g. Rc1, Rc2, Rc3, Rc4, Rc5, Rc6, Cc1, Cc2 in Figure 4)

Figure 10 is the captured waveform when there is a load jump from light load to full load. The output ripple drop during the transition is about 123mV.

 


Figure 10 Leaving burst mode waveform

6.3.4 Minimum V_{CC} supply voltage during burst mode

It is particularly important that the V_{CC} voltage must stay above V_{VCCoff} (i.e. 10.3V). Otherwise, the expected low standby power cannot be achieved. The IC will go into auto-restart mode instead. A reference V_{CC} circuit is presented in Figure 4. This is for a low cost transformer design where the transformer coupling is not too good. Thus the circuit ZD1 is added to clamp the V_{CC} voltage exceeding 25.5V in extreme case such as high load and the V_{CC} OVP protection is triggered. If the transformer coupling is good, this circuit is not needed.

6.4 Low EMI noise

6.4.1 Frequency jittering

The IC is running at a fixed frequency of 67kHz with jittering frequency of $\pm 4\%$ ($\pm 2.7kHz$) and adjustable jittering period in a switching modulation period by changing the value of the capacitor, C_{SoftS} . This kind of frequency modulation can effectively help to obtain a low EMI noise level particularly for conducted EMI. The jittering frequency measured for ICE3B0565J is 63 KHz ~ 68 KHz with a jittering period of 3.2ms which is controlled by C_{SoftS} (refer to Figure 11).

$$T_{FJ} = K_{FJ} \times C_{SoftS} \quad (9)$$

where, $K_{FJ} = \frac{4ms}{\mu F}$

 


Figure 11 Switching frequency jittering

6.4.2 Other suggestions to solve EMI issue

Some more suggestions to improve the EMI performance are listed below.

1. Add RCD clamper circuit to the primary winding of the transformer: RCD clamper circuit (D1, R1 & C3) can absorb the current due to leakage inductance of transformer during switch off time of the MOSFET, so voltage spike of the drain can clamp to desired voltage level and suppress the EMI noise (refer to Figure 4).
2. Add capacitor (C_{DS}) at the drain source pin: C_{DS} can slow down the turn off speed of the MOSFET and the high $\Delta V/\Delta t$ noise will be reduced and so is the EMI noise. The drawback is more energy will be dissipated due to slower turn off speed of MOSFET.
3. Add snubber circuit to the output rectifier: Most of the radiated EMI noise comes out from the output of the system especially for a system with output cable. Adding snubber circuit (R21 and C23) to the output rectifier is a more direct way to suppress those EMI noise (refer to Figure 4).
4. Reduce the reflection voltage: if the secondary to primary reflection voltage is reduced, the switching voltage at drain can also be reduced. Hence the voltage switching noise is reduced and so is the EMI noise. The drawback is the reverse voltage of the secondary rectifier will increase.

6.5 Tight control in maximum power (Propagation delay compensation)

The maximum power of the system is changed with the input voltage; higher voltage got higher maximum power. This is due to the propagation delay of the IC and the different rise time of the primary current under different input voltage. The propagation delay time is around 200ns. But if the primary current rise time is faster, the maximum power will increase. The power difference can be as high as >14% between high line and low line. In order to make the maximum power control become tight, a propagation delay compensation network is implemented so that the power difference is greatly reduced to best around 2%. Figure 14 shows the compensation scheme of the IC. The equation (10) explains the rate of change of the current sense voltage is directly proportional to the input voltage and current sense resistor. For a DCM operation, the operating range for the dV_{sense}/dt is from 0.1 to 0.7. It can show in Figure 12 that higher dV_{sense}/dt will give more compensation; i.e. lower value of V_{sense} .

$$\frac{dI_p}{dt} = \frac{V_{in}}{L_p} \Rightarrow R_{sense} \cdot \frac{dI_p}{dt} = R_{sense} \cdot \frac{V_{in}}{L_p} \Rightarrow \frac{dV_{sense}}{dt} = R_{sense} \cdot \frac{V_{in}}{L_p} \quad (10)$$

where, I_p : primary peak current, V_{in} : input voltage, L_p : primary inductance of the transformer,
 V_{sense} : current sense voltage, R_{sense} : current sense resistor

This function is limited to discontinuous conduction mode flyback converter only.

 


Figure 12 Propagation delay compensation curve

6.6 Protection Features

Protection is one of the major factors to determine whether the system is safe and robust. Therefore sufficient protection is necessary. A list of protections and the failure conditions are shown in the following table.

| Protection function | Failure condition | Protection Mode |
|--|--|-------------------|
| Vcc over-voltage | $V_{CC} > 20.5V$ & $V_{SOFTS} < 4V$ & $V_{FB} > 4.5V$ & last for $8\mu s$ | Auto Restart Mode |
| Over-temperature (controller junction) | $T_J > 140^{\circ}C$ & last for $8\mu s$ | Auto Restart Mode |
| Over-load / Open loop | $V_{FB} > 4.5V$ & $V_{SOFTS} > 4V$ (blanking time counted from charging C_{SST} from (3.2V~3.6V to 4V) | Auto Restart Mode |
| Vcc under-voltage / short opto-coupler | $V_{CC} < 10.3V$ | Auto Restart Mode |

6.6.1 Auto restart protection mode

When the failure condition meets the auto restart protection mode, the IC will go into auto restart. The switching pulse will stop. Then the Vcc voltage will drop. When the Vcc voltage drops to 10.3V, the startup cell will turn on again. The Vcc voltage is then charged up. When it hits 18V, the IC will turn on and the startup cell will turn off. It would then start the startup phase with soft start. After the startup phase the failure condition is checked to determine whether the fault persists. If the fault is removed, it will go to normal operation. Otherwise, the IC will repeat the auto restart protection and the switching pulse stop again.

6.6.2 Blanking Time for over load protection

The IC controller provides a blanking window before entering into the auto restart mode due to output overload/short circuit. The purpose is to ensure that the system will not enter protection mode unintentionally. The blanking time calculation for overload protection is same as active burst mode blanking window (equation 5).

 
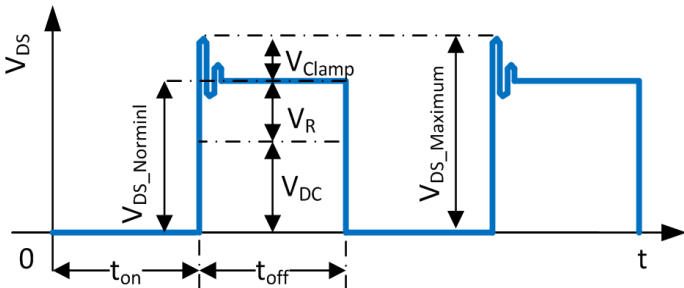


Figure 13 blanking window for over load protection

7 Product portfolio of CoolSET[®]-F3 Jitter Version (DIP-8 & DSO-16/12)

| Device | Package | V _{DS} | Frequency / kHz | R _{dson} /Ω ¹ | 230Vac±15% ² | 85-265Vac ² |
|-------------|--------------|-----------------|-----------------|-----------------------------------|-------------------------|------------------------|
| ICE3B0365J | PG-DIP-8 | 650V | 67 | 6.45 | 22W | 10W |
| ICE3B0565J | PG-DIP-8 | 650V | 67 | 4.70 | 25W | 12W |
| ICE3B1565J | PG-DIP-8 | 650V | 67 | 1.70 | 42W | 20W |
| ICE3B2065J | PG-DIP-8 | 650V | 67 | 0.92 | 57W | 28W |
| ICE3B0365JG | PG-DSO-16/12 | 650V | 67 | 6.45 | 22W | 10W |
| ICE3B0565JG | PG-DSO-16/12 | 650V | 67 | 4.70 | 25W | 12W |

8 Useful formula for the SMPS design

| Transformer (DCM flyback) | |
|----------------------------|--|
| Input data | <p> $V_{DC_min} = 90V, V_{DC_max} = 374V,$ $V_{DS_normal} = 450V$ for 600V Mosfet (Reflection voltage, $V_R = V_{DS_normal} - V_{DC_max}$) $D_{max} < 0.50(50\%)$ </p>  <p>Drain to source voltage composition</p> |
| Turn ratio | $N_{ratio} = \frac{V_{DS_normal} - V_{DC_max}}{V_{out} + V_{FDiode}} = \frac{V_R}{V_{out} + V_{FDiode}}$ |
| Duty maximum | $D_{max} = \frac{V_R}{V_R + V_{DC_min}}$ |
| Primary Inductance | $L_P = \frac{(V_{DC_min} \times D_{max})^2}{2 \times P_{in} \times f_s}$ |
| Primary peak current | $I_{P_max} = \frac{V_{DC_min} \times D_{max}}{L_P \times f_s}$ |
| Primary rms current | $I_{P_rms} = I_{P_max} \times \sqrt{\frac{D_{max}}{3}}$ |
| Primary turns | $N_P \geq \frac{I_{P_max} \times L_P}{B_{max} \times A_e}$ |

¹ Typ @ 25°C

² Calculated maximum input power rating at T_a=75°C, T_j=125°C and without copper area as heat sink.

| | |
|---|---|
| Secondary turns | $N_S = \frac{N_P}{N_{ratio}}$ |
| Auxiliary turns | $N_{aux} = \frac{V_{cc} + V_{FDiode}}{V_{out} + V_{FDiode}} \times N_S$ |
| ICE3Bxx65J(G) other components | |
| Current sense resistor | $R_{CS} \leq \frac{V_{csth}}{I_{P_max}}$ |
| Soft start time | $t_{SS} = C_{SoftS} \times R_{SoftS} \times \ln \frac{5 - 0.8}{5 - 3.1} = 0.793 \times C_{SoftS} \times R_{SoftS}$ where, $R_{SoftS} = 45k\Omega$ |
| Vcc capacitor | $C_{VCC} = \frac{I_{VCCsup_g_max} \times t_{SS}}{V_{VCCchys}} \times \frac{2}{3}$ |
| Startup time | $t_{StartUp} = \frac{V_{VCCcon} \times C_{VCC}}{I_{VCCcharge}}$ where, $I_{VCCcharge}$ is the average current of $I_{VCCcharge2}$ and $I_{VCCcharge3}$ |
| Enter burst mode power | $P_{burst_enter} = \frac{1}{2} \times L_P \times \left(\frac{V_{FBC5} - V_{Max-Ramp}}{A_V \times R_{CS}} \right)^2 \times f_s$ where, $V_{FBC5} = 1.35V$, $A_V = 3.2$, $f_s = 67kHz$, $V_{Max-Ramp} = 0.6V$ |
| Output ripple during burst mode | $V_{out_ripple_pp} = \frac{R_{opto} \times \Delta V_{fb}}{R_{fb} \times G_{opto} \times G_{TL431}}$ |
| Leave burst mode power | $P_{burst_leave} = 0.5 \times L_P \times \left(\frac{V_{cs2}}{R_{CS}} \right)^2 \times f_s$ where, $V_{cs2} = 0.32V$ |
| Blanking time for over load protection/ active burst mode | $t_{blanking} = C_{SoftS} \times R_{SoftS} \times \ln \frac{5 - 3.4}{5 - 4} = 0.47 \times C_{SoftS} \times R_{SoftS}$ where, $R_{SoftS} = 45k\Omega$ |

9 References

- [1] Infineon Technologies, Datasheet “CoolSET®-F3(Jitter Version) ICE3Bxx65J Off-Line SMPS Current Mode Controller with Integrated 650V CoolMOS® and Startup Cell in DIP-8”
- [2] Infineon Technologies, Datasheet “CoolSET®-F3(Jitter Version) ICE3Bxx65JG Off-Line SMPS Current Mode Controller with Integrated 650V CoolMOS® and Startup Cell in DSO-16/12”
- [3] Kok Siu Kam Eric, Jeoh Meng Kiat, Infineon Technologies, Application Note “AN-EVALSF3-ICE3B0565J, 12W 5V SMPS Evaluation Board with CoolSET®-F3 ICE3B0565J”
- [4] Kyaw Zin Min, Kok Siu Kam Eric, He Yi, Jeoh Meng Kiat, Infineon Technologies, Application Note “AN-EVALSF3-ICE3B0365J, 5W 2 outputs (5V & 18V) DC/DC SMPS Demo Board with CoolSET®-F3 ICE3B0365J”