

# Designing with power MOSFETs

## How to avoid common issues and failure modes

**Author:** Peter B. Green

 Feedback

### About this document

#### Scope and purpose

In common with all power semiconductor devices, power MOSFETs have their own technical strengths, weaknesses and subtleties, which need to be properly understood if the designer is to avoid reliability issues. In this application note some of the most common dos and don'ts of using power MOSFETs are discussed. The objective is to help the system designer understand how to use these devices correctly and avoid common mistakes, thereby reducing design time. A list of useful references is provided at the end for more in-depth study.

#### Intended audience

Power engineers and students designing with power MOSFETs. This is intended for engineers with a basic familiarity with MOSFETs but limited experience of designing with them.

### Table of contents

<b>About this document</b> .....	<b>1</b>
<b>Table of contents</b> .....	<b>1</b>
<b>1 Introduction to power MOSFETs</b> .....	<b>3</b>
<b>2 Handling and testing power MOSFETs</b> .....	<b>5</b>
<b>3 Reverse blocking characteristics</b> .....	<b>6</b>
3.1 Avalanche failure mechanisms .....	6
3.1.1 Latch-up .....	6
3.1.2 Thermal failure .....	7
3.2 Avalanche testing .....	7
3.3 Single and repetitive avalanche conditions .....	8
3.4 How to avoid avalanche .....	9
<b>4 MOSFET current ratings and heatsinking</b> .....	<b>10</b>
<b>5 Gate-to-source voltage transients</b> .....	<b>12</b>
<b>6 Safe operating area</b> .....	<b>13</b>
6.1 $R_{DS(on)}$ limit (blue).....	14
6.2 Maximum operating current limit (red) .....	14
6.3 Power limit (dark green) .....	15
6.4 Thermal stability limit (light green) .....	15
6.5 Breakdown voltage (yellow) .....	16
<b>7 Induced turn-on and shoot-through</b> .....	<b>17</b>
7.1 How to avoid induced turn-on.....	18
<b>8 Body diode</b> .....	<b>19</b>
<b>9 Package and board layout considerations</b> .....	<b>21</b>




**Table of contents**

**10 Paralleling of power MOSFETs .....23**  
**11 Conclusion .....24**  
**References.....25**  
**Revision history.....26**

# 1 Introduction to power MOSFETs


Power MOSFETs were first introduced in the 1970s, and became the most widely used power transistors in the world. They offer many advantages over older technologies such as bipolar power transistors in both linear and switching applications. These advantages include greatly improved switching, easy paralleling capability, the absence of the second breakdown effect, and a wider safe operating area (SOA). MOSFETs are voltage-driven transconductance devices.

The differently doped layers of silicon from which the MOSFET die is constructed fall into two broad technology categories, referred to as planar and trench, as shown in **Figure 1**.

 

**Figure 1 Planar and trench MOSFET die layers**

A power MOSFET die is composed of many individual cells or planar strips connected in parallel with a meshed gate connection.

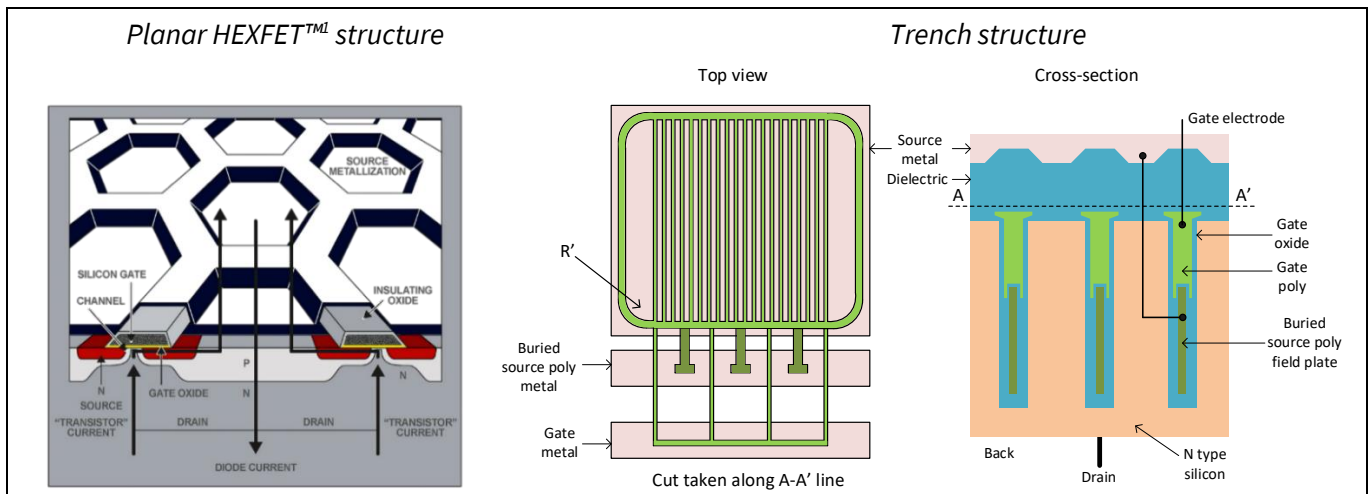

**Figure 2 MOSFET device structures**

<sup>1</sup> A hexagonal type of power MOSFET developed at Stanford University in 1977 by Alex Lidow and Tom Herman, and commercialized by International Rectifier in 1978.

### Introduction to power MOSFETs

Infineon OptiMOS™ devices are based on trench technology, while CoolMOS™ devices are based on superjunction, which is an enhancement of planar technology that enables lower on-resistance and supersedes the older HEXFET™ devices.

The topics discussed in this application note are applicable to all of these silicon power MOSFET technologies, but may not apply to other power devices and technologies such as IGBTs, silicon carbide (SiC) FETs or gallium nitride (GaN) high-electron-mobility transistors (HEMTs). The focus will be on N-channel enhancement mode devices, which account for the majority of power MOSFETs produced.

Although power MOSFETs may initially appear to be simple three-terminal voltage-driven switches, this is a very misleading idea. In reality, these devices are somewhat more complicated, and therefore a solid understanding of the basic characteristics and behavior is essential before embarking on any design project. This should greatly reduce frustrating failures and burned circuits! When it comes to power MOSFETs, or for that matter any other power semiconductor devices, taking the time to gain an understanding of the aspects described in the following sections will ultimately save time.

## **2 Handling and testing power MOSFETs**

The user's first contact with a MOS-gated transistor could be a package of parts arriving on their desk. Even at this stage, it is important to be knowledgeable about some elementary precautions. Being MOS devices with very high gate impedance, power MOSFETs can be damaged by static discharge during handling, testing or installation into a circuit. ESD damage of MOSFETs typically occurs when the gate-to-source voltage is high enough to arc across the gate dielectric. This burns a microscopic hole in the gate oxide, causing the part to fail immediately or later during operation.

Power MOSFET devices have high enough input capacitance to absorb some static charge without excessive build-up of voltage. However, to avoid possible problems, the following procedures should be followed as a matter of good practice, wherever possible:

- MOS-gated transistors should be left in their anti-static shipping bags, or conductive foam, or they should be placed in metal containers or conductive bins until required for testing or connection into a circuit. The person handling the device should ideally be grounded through a suitable wrist strap, though in reality this added precaution is seldom essential.
- Devices should be handled by the package, not by the leads. When checking the electrical characteristics of the MOS-gated transistors on a curve tracer, or in a test circuit, the following precautions should be observed:
  1. Test stations should use electrically conductive floor and grounded anti-static mats on the test bench.
  2. When inserting the device in a curve tracer or a test circuit, voltage should not be applied until all terminals are solidly connected into the circuit.
  3. When using a curve tracer, a resistor should be connected in series with the gate to damp spurious oscillations that can otherwise occur on the trace. A suitable value of resistance is 100  $\Omega$ .
- The next step is to connect the device into an actual circuit. The following simple precautions should be observed:
  1. Workstations should use electrically grounded table and floor mats.
  2. Soldering irons should be grounded.

Now that the device has been connected into its circuit, it is ready for the power to be applied. From here on, success in applying the device becomes a matter of the integrity of the circuit design and depends on whether the necessary circuit design precautions have been taken to guard against unintentional abuse of its ratings.

The following sections describe the interrelated device and circuit considerations that lead to reliable, trouble-free design.

### 3 Reverse blocking characteristics

All power MOSFET devices are rated for a maximum reverse voltage,  $V_{(BR)DSS}$ . If the drain-to-source voltage exceeds this threshold, high electric fields are produced across reverse biased p-n junctions. Due to impact ionization, these high electric fields create electron-hole pairs, which undergo an uncontrolled multiplication effect, causing carrier concentration to increase further. This is called the avalanche effect, and it leads to increased current flow through the device, resulting in high power dissipation, rapid temperature rise and potential device destruction. Avalanche typically occurs when the breakdown voltage of the MOSFET is exceeded, usually due to unclamped inductive switching (UIS), where the part is being used outside of its datasheet specification. Consequently, the designer should make all reasonable attempts NOT to operate a MOSFET in avalanche. In reality, in high-current applications, high-voltage switch-off transients are produced due to parasitic inductance in the MOSFET package and PCB traces or leakage inductance from transformers (for example in a flyback converter). Avalanche is observed by the clamping effect of the drain voltage.

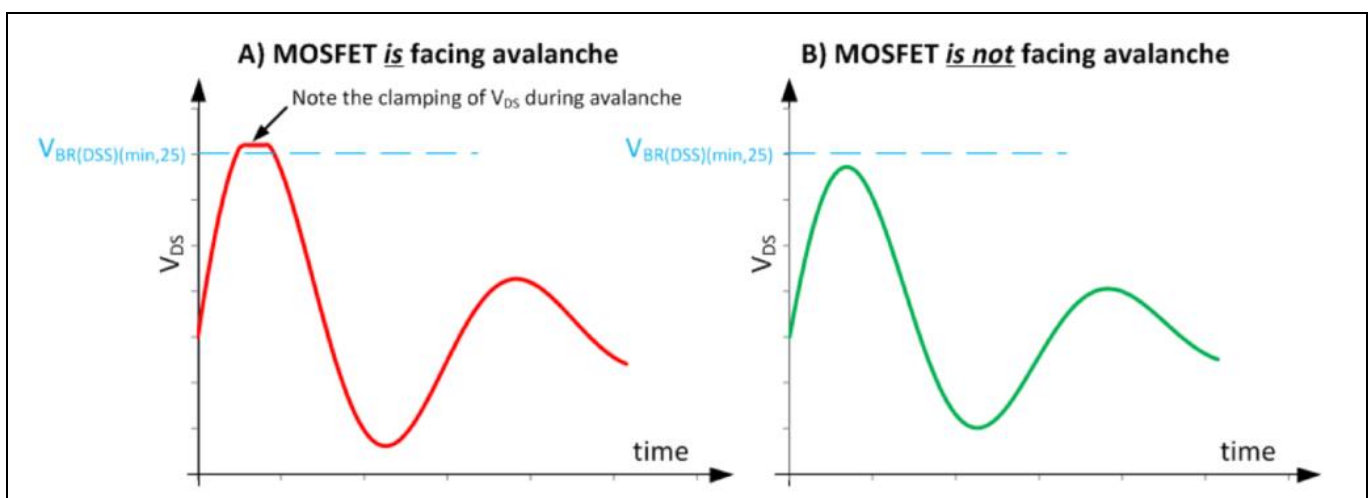


Figure 3  $V_{DS}$  switch-off transient voltages due to UIS

The datasheet  $V_{(BR)DSS}$  rating of MOSFETs is the minimum value over process variations, meaning that although some devices may clamp at a higher level, the designer should consider the worst-case condition given by the datasheet.  $V_{(BR)DSS}$  increases slightly with temperature, which is shown in a datasheet graph.

#### 3.1 Avalanche failure mechanisms


##### 3.1.1 Latch-up

In this case, the avalanche event generates a drain current, the amplitude of which will be greater where the electric field has greater intensity. Latch-up is a consequence of the parasitic NPN bipolar junction transistor (BJT) that resides within power MOSFETs. If the device technology is structured in such a way that the electric field is high in the vicinity of the parasitic BJT, a significant amount of current will flow through its base resistor, producing a voltage between base and emitter. If this voltage reaches a certain threshold, the bipolar transistor turns on and most of the avalanche current then flows through it with potentially damaging effects, as there is no means of controlling it. Since the latch-up mechanism is well understood, Infineon has strived to mitigate its impact during the development of all OptiMOS™ technologies. Hence, in many of these technologies, latch-up does not occur. However, this is not the case for all MOSFET technologies, so it is important to study the datasheet carefully to understand the type of technology a particular device utilizes, and its strengths and weaknesses.

# Designing with power MOSFETs

## How to avoid common issues and failure modes

### Reverse blocking characteristics

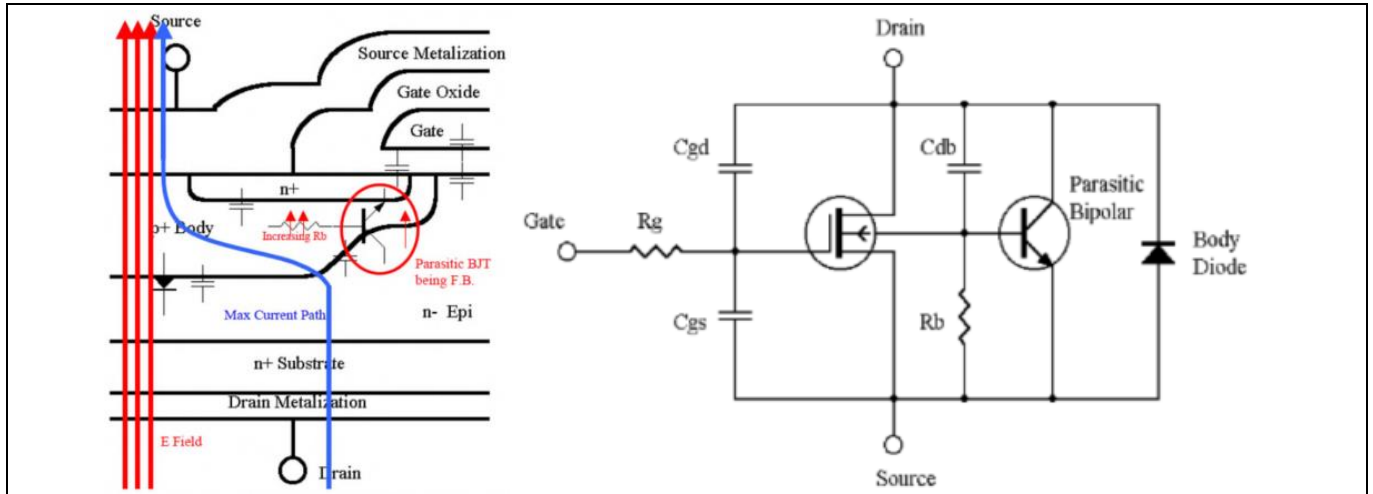

**Figure 4** The MOSFET parasitic BJT silicon structure and equivalent circuit


### 3.1.2 Thermal failure

Thermal destruction occurs when the junction temperature of the MOSFET reaches  $T_{j,destr}$ .  $T_{j,destr}$  is close to the intrinsic temperature of silicon, that is the temperature at which the density of thermally generated carriers equals the background doping. Hence, when such a temperature is reached, the MOSFET will no longer behave like a semiconductor device. There is not much variation in  $T_{j,destr}$  among OptiMOS™ families and the value is typically close to 400°C. Given the precautions taken against latch-up during the technology development of Infineon OptiMOS™ families, thermal destruction is responsible for the majority of failures caused by avalanche. Even for technologies prone to latch-up, thermal failure is more likely to occur.

Unfortunately, coping with thermal destruction requires some trade-offs in technology design, because it impacts some key drivers of high-performance technologies, specifically the FOM  $R_{DS(on)} \times A$ . Indeed, whereas a technology reduction of  $R_{DS(on)} \times A$  allows smaller chip sizes for a defined  $R_{DS(on)}$  value, a larger die area is necessary to mitigate the temperature increase caused by high-energy avalanche events.

### 3.2 Avalanche testing

MOSFET avalanche withstand capability is tested by means of a single-pulse UIS test circuit, as shown below.

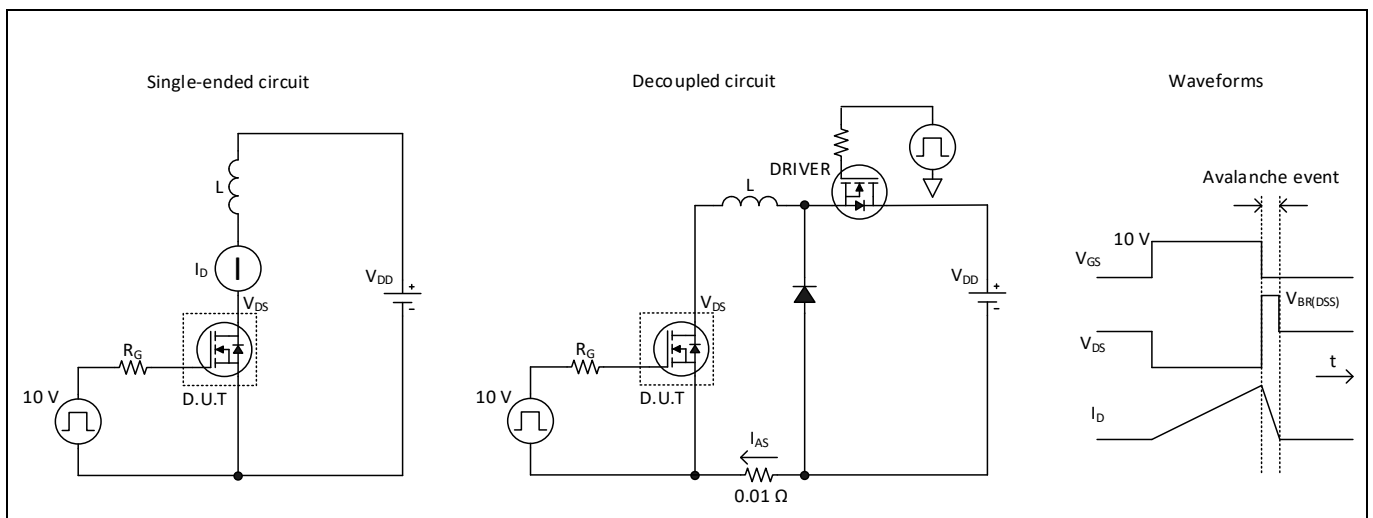

**Figure 5** Avalanche test circuits

### Reverse blocking characteristics

In these circuits, a pulse of defined duration is applied to the MOSFET gate to switch the device on so that the drain current rises linearly due to the series inductor. The MOSFET is then switched off, at which point a large negative  $di/dt$  occurs that produces a voltage transient. In the decoupled circuit both MOSFETs are switched on and off at the same time, so that the inductor voltage is equal to that applied between the MOSFET drain and source. The switch-off transient rises above  $V_{(BR)DSS}$  so that the energy stored in the inductor (defined by the pulse length and inductance) can be transferred into the MOSFET during an avalanche condition. Infineon performs avalanche stress testing to assure conformance with the  $E_{AS}$  rating, validate ruggedness and screen for defective parts.

### 3.3 Single and repetitive avalanche conditions

There is a defined maximum amount of avalanche energy that a MOSFET is able to withstand in a single pulse, which is specified as  $E_{AS}$  in the MOSFET datasheet under a certain set of test conditions. As its name suggests, a single-pulse avalanche event should only be allowed to occur once, particularly if the conditions are close to the limits provided in the datasheet. This is because those limits correspond to junction temperatures above the  $T_{j,max}$  of the MOSFET, therefore repeating such events would impair the operating lifetime of the MOSFET. Please remember that avalanche is not a recommended operating condition.

In the case of *repetitive* avalanche, the events occur continuously at a fast repetition rate, which is typically the same as the switching frequency ( $f_{sw}$ ) of an application circuit such as a switching power converter. The safe quantity of avalanche energy allowable per event is much lower than for single-pulse avalanche.

In most repetitive avalanche cases, due to the relatively low energy of each avalanche event, the silicon temperature rise is negligible compared to the worst-case single-pulse avalanche condition. The observed  $V_{DS}$  spikes only slightly exceed the  $V_{(BR)DSS,(min,25)}$  rating of the MOSFET, as opposed to the  $1.2\sim 1.3 \times V_{(BR)DSS,(min,25)}$  amplitudes recorded during high-energy single-pulse avalanche testing. A relevant difference between single and repetitive avalanche ratings relates to the permitted  $T_{j,max}$  caused by such events. In fact, although the junction temperature is permitted to exceed  $T_{j,max}$  during single-pulse avalanche, this is NOT the case for repetitive avalanche.

Exceeding  $T_{j,max}$  during repetitive avalanche has a cumulative effect, which risks reducing the reliability of the device over its lifetime, leading to early failure.  $T_{j,max}$  can be as low as 150°C for parts in QFN 5x6 (SuperSO8) or S308 packages. This is a limitation of the package rather than the silicon itself, which can usually withstand 175°C. As a result, in some cases MOSFETs with the same die, when housed within a different package (e.g., TO-220 or D<sup>2</sup>PAK) are rated at 175°C.

It is very important to distinguish between single-pulse and repetitive avalanche, because the way they can affect normal MOSFET behavior differs significantly. The two device failure modes for single-pulse avalanche are caused either by high current (latch-up) or high energy (thermal destruction). These failure modes are catastrophic; however, in the case of repetitive avalanche, deterioration is incremental, impacting the device very slowly through repeated micro-damage. Even a low-energy avalanche event generates some hot carriers, which are charges injected along the trench oxide of the power MOSFET. The repetition of such avalanche events leads to an accumulation of such charges, which slowly impair reliability. This can result in field failures occurring after a period of time.

It is worth mentioning that to significantly reduce the impact of repetitive avalanche on technology parameters, Infineon would need to compromise significantly on other figures of merit that are dominant in the vast majority of applications. This would be too high a price to pay for an event that does not correspond to a normal usage of a MOSFET, which a designer should strive to avoid. Consequently, Infineon does not insert repetitive avalanche ratings within the OptiMOS™ “Industrial and Standard Grades” datasheets.



Reverse blocking characteristics

### 3.4 How to avoid avalanche

First and foremost, it is necessary to select a device with the right  $V_{(BR)DSS}$  rating for the application. This means that the maximum steady-state voltage across the drain and source of the device under worst-case operating conditions should be considered with a safety margin of at least 20 percent. In cases where large switch-off transients occur, a much higher safety margin will be required to achieve reliable operation. For example, in motor drive inverters it is not unusual to select a MOSFET with  $V_{(BR)DSS}$  rating of twice the DC bus voltage. It is, however, a mistake to choose a part with a higher rating than needed, because this would give a higher  $R_{DS(on)}$  and probably cost more.

Methods that can be employed to reduce the switch-off transient include slowing down the MOSFET switch-off by adjusting the gate drive network and adding RC snubbers between the drain and source. Naturally, both of these create additional switching losses, which reduces system efficiency.

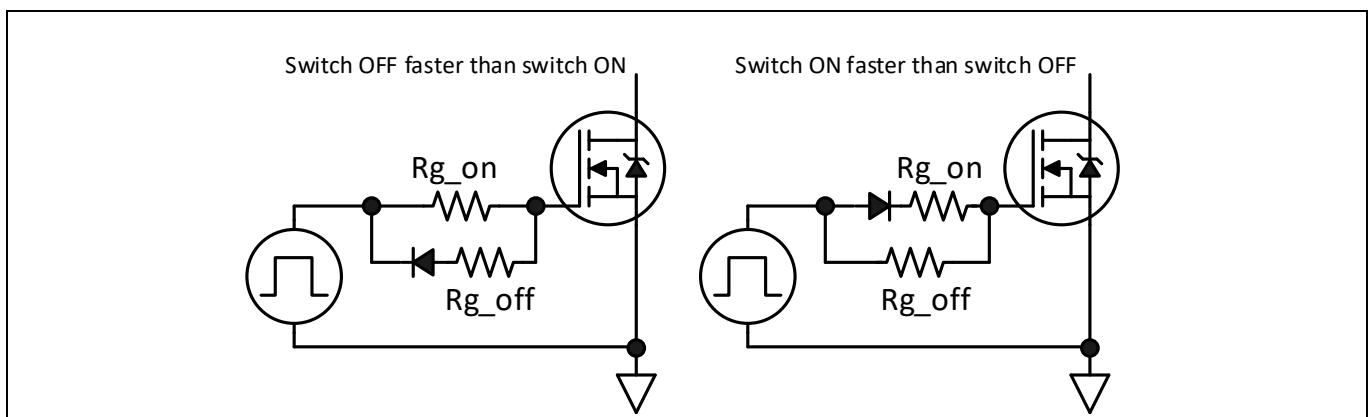


Figure 6 Gate drive circuits

Depending on the specifics of the design, one of the above gate drive circuits can be used to control the switch-on and switch-off speeds. Adjusting  $R_{g\_off}$  allows the designer to reduce the switch-off transient voltage without affecting the switch-on speed. However, in hard-switching half-bridge circuits, the value of  $R_{g\_off}$  cannot be too high, as this could result in an induced turn-on spike appearing at the low-side gate, caused by the  $C_{GD} \cdot di/dt$  effect. If large enough, this spike can exceed the MOSFET  $V_{GS(th)}$  and cause dangerous shoot-through currents (this is discussed further in [section 7](#)). Careful consideration of the gate drive resistor values is essential to achieve the best trade-off between minimizing switch-off transient amplitude, avoiding induced turn-on (if applicable) and controlling EMI emissions.

As previously mentioned, a series RC snubber can be added across the drain and source to absorb some of the switch-off transient, thereby reducing its peak voltage; however, this produces additional switch-on losses.

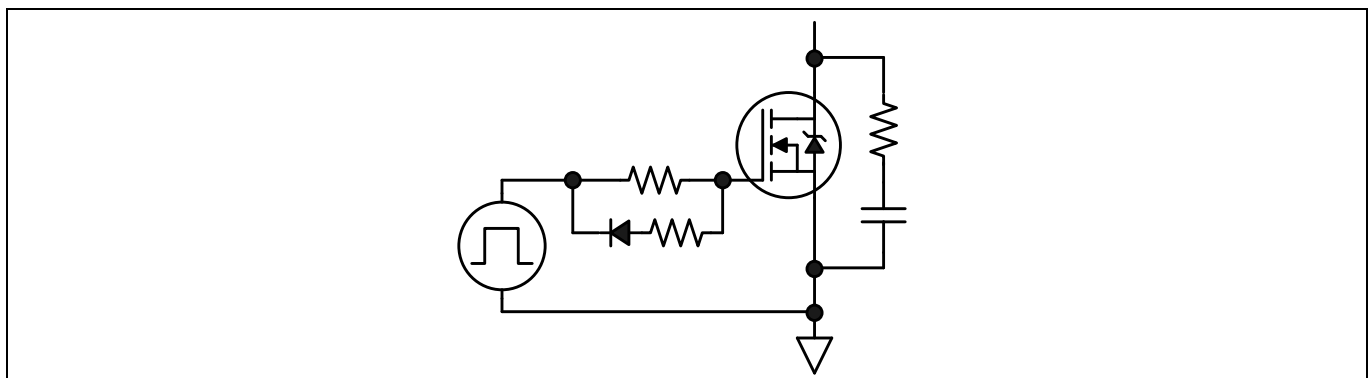


Figure 7 RC snubber connected across a MOSFET drain and source

## 4 MOSFET current ratings and heatsinking

The inexperienced user may assume that the continuous drain current rating  $I_{D(MAX)}$  that appears on a MOSFET datasheet represents the current at which the device can be operated in a practical system. However, it is important to realize that this is not the case!


Such  $I_{D(MAX)}$  ratings are based on ideal test conditions not achievable in a practical design. Test conditions often involve very large heatsinks or die temperatures to be maintained at a low level through artificial cooling.

It should be noted that different manufacturers use different criteria (some more conservative than others) for determining the  $I_{D(MAX)}$  rating claimed for their MOSFETs, and these methods have also evolved over time. It is therefore a mistake to rely on these ratings to compare the capabilities of different devices! The method now used by Infineon is described in [5].

A more realistic approach to comparing different devices would be on the basis of power loss and how it causes the die and package temperatures to rise under a given set of conditions.

As a first criteria to look at, it is useful to compare  $R_{DS(on)}$  at 25°C, because this provides a common basis for comparison.  $R_{DS(on)}$  is composed of series die and package resistances<sup>1</sup>, with the former being dependent on the gate-to-source voltage  $V_{GS}$ .

$R_{DS(on)}$ , taken in conjunction with the junction-case thermal resistance  $R_{TH(JC)}$ ,<sup>2</sup> gives a much better indication of a power MOSFET's true current-handling capability. The following cross-section of a typical SMD power MOSFET soldered to a PCB gives a clearer picture. The bottom side of the die is connected to the metal tab, which makes the drain connection to the board. The source and gate connections are made through bond wires to the leadframe that forms the external lead wires. Because the drain current passes through the source, several bond wires and sometimes several source leads are used. In some high-current devices, a copper clip is used to replace the source bond wires to provide lower resistance.

 

**Figure 8 PCB-mounted D<sup>2</sup>PAK SMD MOSFET package cross-section**

Clearly, when current passes through the drain-source path, conduction losses are generated that produce heat. Switching losses are also produced in switching power converters, which dissipate a quantity of energy each switching cycle, making the switching loss frequency dependent. The total losses comprise the sum of both conduction and switching losses, which transfers through the top and/or bottom package. The type of cooling varies depending on the package. Most packages are bottom or back-side cooled, as shown in the

<sup>1</sup> Package resistance in power packages is only significant for MOSFETs with on-resistances in the range below around 10 mΩ.


<sup>2</sup> Separate values of junction-to-case thermal resistance are sometimes provided to the top and the bottom of the package.

# Designing with power MOSFETs

## How to avoid common issues and failure modes

### MOSFET current ratings and heatsinking

above example, where most of the heat passes through the drain tab to the PCB, which needs to include a large number of thermal vias underneath the drain pad to transfer heat through to the bottom of the board. A heatsink may then be mounted under the board. There are also top-side cooled packages, such as the TOLT package, in which the internal arrangement of the die and lead-frame within the package is different; they have an exposed metal pad on top of the package where a heatsink may be mounted.

 

**Figure 9 Bottom and top-side cooling**


The heatsink must be sized to be able to transfer enough heat from the MOSFET die so that its junction temperature remains below the maximum rated level. The designer must first select the correct MOSFET die size and package option to limit power loss, and then they must choose a suitable heatsink to maintain a safe junction temperature.

Apart from the heatsink size and surface area (determined by the shape and number of fins), the thermal resistance from junction to ambient must also be considered. This depends on the heatsinking arrangement used, and can be calculated by adding all of the series thermal resistances (including PCB, thermal insulation material/TIM, etc.) between the junction and the heatsink and that of the heatsink itself (see **Figure 9**). Clearly, a low junction-to-ambient thermal resistance is required to effectively transfer the heat from the MOSFET die and allow it to safely conduct the highest possible current.

In conclusion, it makes more sense to look at the whole picture in terms of current handling than to pay too much attention to datasheet  $I_{D(MAX)}$  ratings.

## 5 Gate-to-source voltage transients

Excessive voltage transients can punch through the thin gate-source oxide layer and result in permanent damage. Unfortunately, such transients are produced in power switching circuits and can be coupled to the sensitive MOSFET gate input. The designer is strongly advised to look closely at the gate drive waveforms to ensure that neither positive nor negative transients are present that exceed the device limits (typically +/-20 V for power MOSFETs, but this should be checked on the datasheet).

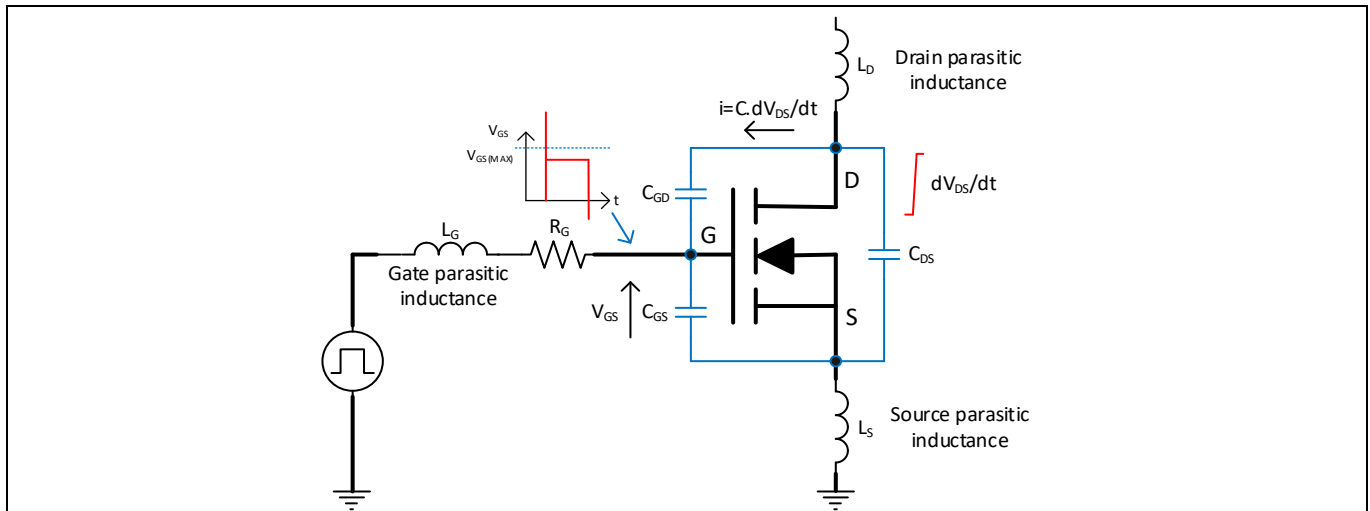

**Figure 10** Rapidly changing drain-source voltages produce gate-source transients

During the switch-on or switch-off operations of the gate drive, a high  $dV_{DS}/dt$  is produced as the device transitions from the on-state to the off-state and vice-versa. Considering the presence of parasitic inductances in the gate, source and drain leads, and also the MOSFET  $C_{GD}$  (Miller capacitance), it can be understood that transient voltages will be produced between the gate and source resulting from a combination of these parasitic elements. Fortunately, the gate capacitance  $C_{GS}$  acts to reduce this effect.

The ratio of  $C_{GS}/C_{GD}$  must be as high as possible to minimize drain-to-source voltage coupling. It is also essential to optimize the PCB layout to reduce parasitic inductance as much as possible. In some cases, designers add small gate-source capacitors to help reduce these spikes, though this also slows down the MOSFET switching.

The values of  $C_{GS}$  and  $C_{GD}$  are voltage dependent and because of this, usually are not directly quoted on a MOSFET datasheet. It is therefore more convenient instead to look at the related charge values  $Q_{GD}$  and  $Q_{GS}$ . The charge ratios are often expressed as:  $Q_{GD}/Q_{GS}$  or  $Q_{GD}/Q_{GS(TH)}$ , where a lower value means the device is less susceptible to induced turn on coupled through  $C_{GD}$ .

## 6 Safe operating area

The development of modern power MOSFETs has focused on fast switching with ultralow  $R_{DS(on)}$ , for which reduction of die area has been the trend. The power-handling capabilities of devices for a specific  $R_{DS(on)}$  have therefore generally decreased, especially in linear operation mode (in the saturation region). When designing in power MOSFETs (or any other type of power transistor), it is essential to pay close attention to the SOA diagram and ensure that the device will never be operated outside of the defined limit-lines. A reliable design is not possible if these limits are violated!

In order to accurately set these limits, Infineon carries out extensive testing on many samples, which involves testing parts to destruction. There are certain applications in which operation takes place in the saturation region for an extended period of time, such as inrush current limiting or “hot swap”. In these cases, particular attention must be paid to the SOA limits for the required pulse duration to ensure these are never exceeded.

 



Figure 11 Ohmic (triode or linear)<sup>1</sup> region and saturation region of a power MOSFET

SOA cannot be overlooked in typical switching applications because the device also passes through the saturation region every switching cycle unless it is a zero-voltage or current-switching transition. These transitions happen rapidly, and therefore the MOSFET can withstand a much higher current pulse under the defined conditions. However, it is advisable to check that it is operating within the SOA limits. It is important to keep in mind that when slowing down the switch-on or switch-off of a MOSFET (as discussed in [section 3.4](#)) to reduce EMI or switch-off transients, the period of operating time in the saturation region is increased.

<sup>1</sup> Linear *region* is different from linear *mode*. Operating in linear mode means in the saturation region, not the ohmic region.

**Safe operating area**

The SOA diagram of an Infineon power MOSFET (**BSC010NE2LS** in this example) is shown below. The SOA curves for other MOSFETs typically include at least some of the same limit-lines, but may appear somewhat different. The five limit-lines defining the SOA diagram are the  $R_{DS(on)}$  limit-line (blue line), the current limit-line (red line), the maximum power limit-line (dark green line), the thermal instability limit-line (light green line) and the breakdown voltage limit-line (yellow line). Within these limit-lines the green shaded area gives the area where the MOSFET can be safely operated. In this example, the limit-lines are shown for a constant case temperature of  $T_c = 25^\circ\text{C}$  and a single pulse with duration of  $100\ \mu\text{s}$ . A full SOA graph found in a device datasheet provides additional limit-lines for various pulse lengths and for continuous (DC) operation.

 

**Figure 12** Power MOSFET SOA limits

**6.1  $R_{DS(on)}$  limit (blue)**

The  $R_{DS(on)}$  limit-line is dictated by Ohm’s law for a specific drain-to-source voltage for  $V_{GS} = 10\ \text{V}$  and  $T_j = 150^\circ\text{C}$ . The value of  $R_{DS(on)}$  has a positive temperature coefficient, so at lower temperatures a higher drain current is possible.

**6.2 Maximum operating current limit (red)**

This defines the maximum current-handling capability of the package, above which it would fail, although the MOSFET die within it may remain undamaged. Packages with bond wires (e.g., DPAK) have different maximum current-handling capabilities compared to packages with clip-bonding technology (e.g., SuperSO8). Die active area also impacts the current-handling capability of the package, as it determines the bonding scheme (number of bond wires, bond wire diameter, clip dimensions). The package limit-line does not change according to temperature or other conditions.

### Safe operating area

## 6.3 Power limit (dark green)

This is calculated from the maximum power the device is permitted to dissipate that produces a stable junction temperature  $T_j$  of 150°C in thermal equilibrium, where  $T_c = 25^\circ\text{C}$ . Considering the junction-to-case thermal impedance of the package  $Z_{thJC}$ , defined in  $^\circ\text{C per W}$ , a certain power dissipation produces a  $\Delta T$  of 125°C. This provides the power limit-line, where the product of  $V_{DS}$  and  $I_D$  remains constant to determine the slope.

For short pulses the value of  $Z_{thJC}$  depends on the pulse length and its duty cycle.  $Z_{thJC}$  can be taken from the corresponding diagram in the datasheet. The SOA diagram illustrates that an increased pulse duration shifts the maximum thermal limit-line downward, reflecting the higher thermal impedance at longer pulse lengths and/or higher duty cycle.

In a real application  $T_j$  will not remain at 25°C, so it will not be possible to operate the device within the SOA at the power limit. Depending on the package, the heatsink and whether forced air-cooling is used, the maximum permissible power dissipation will be that which results in a steady-state  $T_j$  of 150°C. As always it is advisable not to operate the device at its limit, so in practice some safety margin should be included.

## 6.4 Thermal stability limit (light green)

The thermal stability limit-line is also of critical importance to achieve reliable power MOSFET operation. In some cases, especially for older devices, the datasheet SOA graph may not include this limit-line though the device may exhibit a thermal stability limitation. In general terms, thermal instability is the condition in which power loss rises more rapidly than power dissipation with respect to temperature so that thermal equilibrium cannot be achieved. Instead thermal runaway occurs due to current crowding in hotter cells of the device (see [section 1](#)). This is referred to as the Spirito effect,<sup>1</sup> where as a cell becomes hotter it draws more current, causing its temperature to rise further until it is eventually destroyed. Under this condition, current cannot be evenly distributed among cells.

Thermal instability can be expressed as follows:

$$\frac{\partial P_{generated}}{\partial T} > \frac{\partial P_{dissipated}}{\partial T} \quad [1]$$

In such a condition the temperature of the system is not stable and is not in thermal equilibrium, unlike the case for the maximum power limit line (above).

$$P_{generated} = I_{DS} \cdot I_D \quad [2]$$

and

$$P_{dissipated} = \frac{T_j - T_{ambient}}{Z_{thJC}} \quad [3]$$

Assuming  $V_{DS}$  is constant over temperature, the inequality can be rearranged to:

$$V_{DS} \cdot \frac{\delta I_D}{\delta T} > \frac{1}{Z_{thJC}(t_{pulse})} \quad [4]$$


The above equation defines the operating range where the MOSFET may encounter thermal instability. The term  $\delta I_D / \delta T$  is called the temperature coefficient. Since  $V_{DS} > 0$ , thermal instability occurs if the temperature coefficient is positive.

---

<sup>1</sup> Named after professor Pablo Spirito, who discovered it.

**Safe operating area**

Thermal instability occurs if the drain current increases with temperature at a given value of  $V_{GS}$ . This occurs for  $V_{GS}$  values below the zero-temperature coefficient (ZTC) point. At higher  $V_{GS}$  levels the drain current reduces with temperature. This is illustrated in **Figure 13**.

 

**Figure 13 Thermal stability related to  $I_D$  vs.  $V_{GS}$**

The change of temperature coefficient from positive to negative over  $V_{GS}$  is caused by two competing effects. The resistance of a MOSFET increases with temperature due to lower electron mobility, while the threshold voltage ( $V_{TH}$ ) decreases with temperature because more electrons have been excited into the conduction band. At low temperatures the effect of decreasing threshold voltage over increasing temperature dominates and current increases with temperature, whereas at higher temperatures, the increase of  $R_{DS(on)}$  dominates and  $I_D$  then decreases with temperature.

As shown above, thermal instability occurs when  $V_{GS}$  is below the ZTC point. Thus, MOSFETs with a ZTC at high currents and high  $V_{GS}$  voltages will be more prone to thermal instability. The ZTC point is in direct relationship to the MOSFET transconductance ( $g_m$  or  $g_{fs}$ ). With increasing transconductance the ZTC point will move toward higher  $V_{GS}$ . Modern power MOSFETs exhibit ever-increasing transconductances and therefore also ZTC points at higher  $V_{GS}$ .

To avoid failures due to thermal instability, the designer needs to ensure that the SOA thermal stability limit will not be violated.


**6.5 Breakdown voltage (yellow)**

This represents the device  $V_{(BR)DSS}$  rating described in **section 3**.




## 7 Induced turn-on and shoot-through

Induced turn-on is a phenomenon that occurs when MOSFETs are used in fast-switching applications where high  $dV_{DS}/dt$  transitions appear at the drain while the device is in the off-state. This typically occurs in hard-switching<sup>1</sup> applications such as switching power supplies and motor drive inverters, where two MOSFETs are used in a half-bridge configuration.

 

**Figure 14** MOSFET half-bridge

The high- and low-side MOSFETs switch on and off alternately, with a small dead time between switch-off of one device and switch-on of the other to prevent overlap that would result in very high current pulses. When the low-side MOSFET switches off, after the dead time has expired, the high-side switches on. When this happens the HB node transitions rapidly from zero volts to  $V_{BUS}$ .

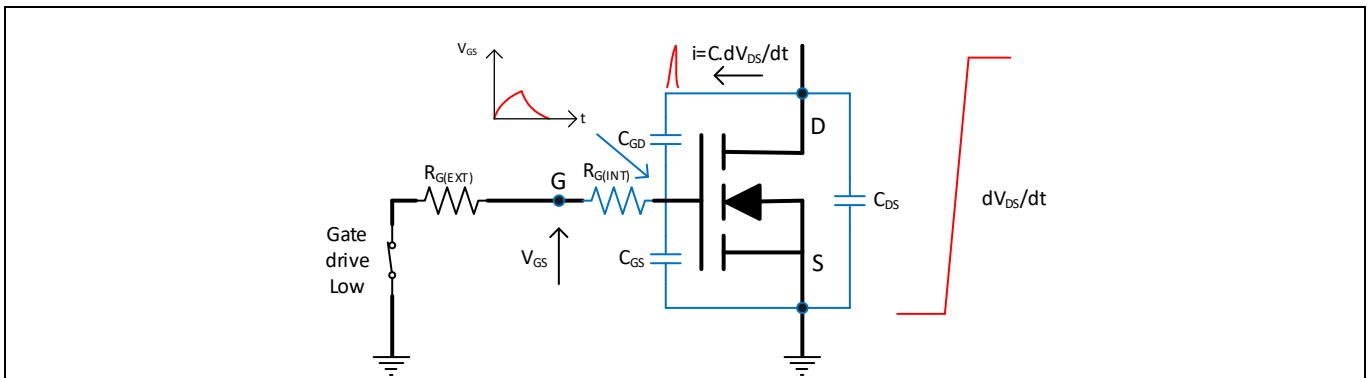

**Figure 15** Induced turn-on mechanism

**Figure 15** shows how “ $C \cdot dv/dt$ ” causes a current pulse to couple through  $C_{GD}$  to the gate, which is pulled to zero volts through  $R_{G(EXT)}$ . This current pulse can be sufficient to induce a voltage spike at the gate. It is important to remember that the MOSFET may also have a significant internal gate resistance  $R_{G(INT)}$ , so that the induced gate spike appearing at the silicon may be larger than that observed at the gate terminal.

If the induced turn-on spike exceeds the MOSFET  $V_{TH}$  then the device will partially turn on for a brief time before the high-side MOSFET has fully turned off. With both devices partially on, a high current can flow through the half-bridge, which can violate SOA limits and destroy one or both devices.

<sup>1</sup> Hard-switching occurs when a MOSFET switches on with a non-zero  $V_{DS}$ .

## 7.1 How to avoid induced turn-on

As mentioned in [section 5](#), MOSFETs with higher  $C_{GS}/C_{GD}$ , which means lower  $Q_{GD}/Q_{GS}$  and  $Q_{GD}/Q_{GS(TH)}$ , are less susceptible drain-to-source voltage coupling. A  $Q_{GD}/Q_{GS}$  of 0.5 to 0.8 and  $Q_{GD}/Q_{GS(TH)}$  less than 1.0 is recommended for hard switching applications. It should be noted that lower  $Q_{GD}/Q_{GS}$  devices may suffer from greater ringing in the gate voltage waveform, however this depends on the value of  $R_{G(INT)}$  and the circuit loop inductance.

Induced turn-on may be reduced by slowing down the switching transition and therefore lowering the  $dv/dt$ . This can be done by slowing down the switch-on of the high-side device by increasing  $R_{g\_on}$  (refer to [Figure 6](#)). Depending on the circuit switching behavior the high- and low-side gate drive network may be the same or may be different. Slowing down the turn-on also reduces radiated EMI, but at the same time increases switching losses, therefore it is a trade-off to be considered carefully.

Another way to reduce induced turn-on is to use a “switch off faster than switch on” type gate drive network, which includes a diode and resistor to allow a strong pull-down for the gate while allowing a slower turn-on. This is good during the off-state but also leads to a fast switch-off, which tends to produce higher drain-transient voltages that may create a risk of avalanche – another trade-off to be considered during design. It is worth mentioning that some smart gate driver ICs<sup>1</sup> now available from Infineon include a programmable gate drive where the gate current can be defined during different phases of operation, thereby eliminating resistor-diode gate driver networks and enabling precise tailoring of the gate drive to allow optimization during switching and in the off-state.

A third method involves adding an external gate-to-source capacitor. This can reduce the magnitude of the induced gate transient by increasing the effective  $C_{GS}/C_{GD}$ , though again it slows down the switching and so should be applied only when necessary and kept to a minimum value.


---

<sup>1</sup> MOTIX™ 6EDL7141 smart gate driver IC for motor drive applications.

Body diode


## 8 Body diode

The body diode is intrinsic to the MOSFET structure, formed by the p-n junction between p-body and n-epi layers shown in [Figure 4](#). Power MOSFETs are three-terminal devices where the body and source are connected internally.<sup>1</sup> This can be understood by looking at the circuit symbols for n- and P-channel devices.

 

**Figure 16** N-channel (left) and P-channel (right) MOSFET circuit symbols, showing the body diodes

Like other p-n junction diodes, the MOSFET body diode exhibits minority carrier reverse recovery, resulting in a finite reverse recovery time. Reverse recovery occurs when the diode is reverse biased while carrying a forward current. Reverse recovery is characterized in datasheets by time  $t_{rr}$  and the reverse recovery charge  $Q_{rr}$  tested under a specified set of conditions.

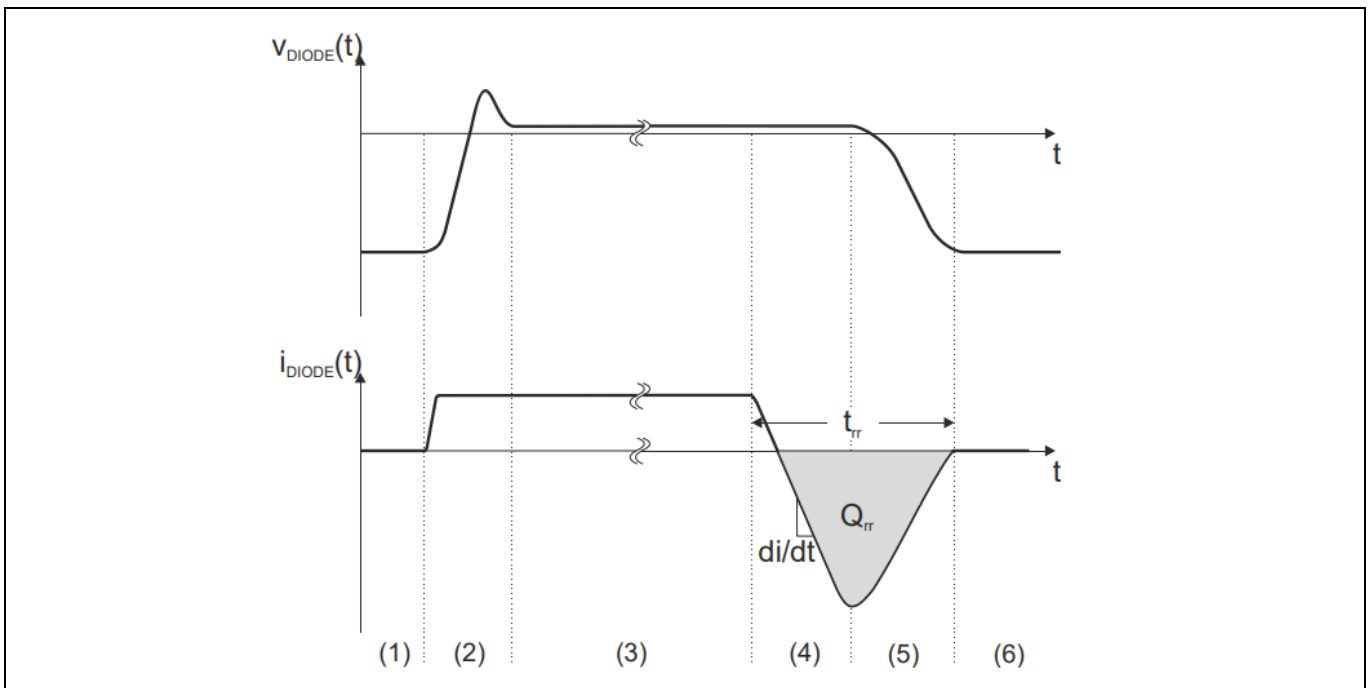

**Figure 17** Forward and reverse biasing of the body diode


At interval (1), the diode is in the off-state, and it starts to turn on in interval (2). At the end of the turn-on process, the diode becomes forward biased. The reverse recovery charge accumulates and is stored while the forward biased diode carries a positive current during interval (3). At the start of the turn-off interval (4), the current reduces to zero then flows in the opposite direction. During interval (5) reverse recovery is completed

<sup>1</sup> This is necessary to avoid the “body effect”, which affects the value of  $V_{TH}$ .

### Body diode

and the turn-off process is completed by interval (6), in which the diode is blocking. The shaded area in the diagram indicates  $Q_{rr}$ , the key device parameter for hard-commutation ruggedness.

In half-bridge power-switching circuits as described in the previous section, body diode reverse recovery becomes significant when switching high current into an inductive load. Consider a synchronous buck regulator operating in continuous conduction mode (CCM) with Q1 on and Q2 off where a current  $I_L$  is flowing from the half-bridge switching node.

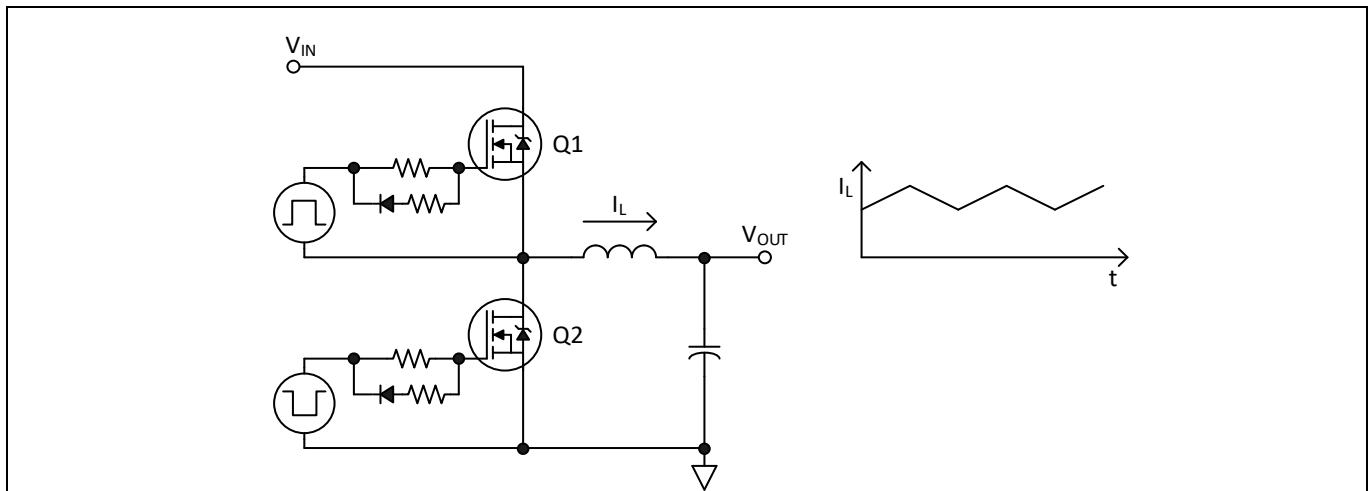

**Figure 18** Synchronous buck regulator

When Q1 switches off, the inductor current is commutated through the body diode of Q2, which then switches on after the dead time has ended. At the end of the Q2 conduction (synchronous rectification) period it switches off again so that the current once again flows through its body diode. At the end of the dead time period Q1 switches on, and this is where the body diode recovery of Q2 becomes critical. If Q1 switches on too rapidly, the peak reverse recovery current of the integral body diode Q2 will rise too rapidly, exceeding the peak reverse recovery current rating, and the device may be destroyed!

Different MOSFET technologies have different degrees of body diode ruggedness and different reverse recovery speeds. It is important to select devices that are suited to applications where hard commutation occurs, even if this is only under some operating conditions. Infineon's high-voltage CoolMOS™ family of superjunction MOSFETs includes the CFD family of parts, which have fast-recovery body diodes. In addition, there are several series of low- and mid-voltage OptiMOS™ trench devices. As a general rule, it is important to choose the right type of power MOSFET for a particular design based on the type of switching that takes place.

The peak reverse recovery current of the body diode can be reduced by slowing down the rate of change of current during the commutation process. The rate of change of current can be controlled by slowing down the rate of rise of the gate driving pulse, as shown in **Figure 6** and discussed in sections **3.4** and **7.1**. Using this technique, the peak reverse recovery current can be reduced to an acceptable level at the expense of prolonging the high dissipation switching period, so as always there is a trade-off to consider. For operation at frequencies up to around 20 kHz, slowing the applied gate drive signal to reduce the peak reverse recovery current of the "opposite" device's body diode offers a good practical solution. At higher frequencies the designer must pay particular attention to the voltages and currents that the MOSFETs are required to switch and choose an appropriate device and gate drive scheme.


## 9 Package and board layout considerations

Different power MOSFET packages have different parasitic inductances, leaded packages have higher inductances than SMD packages, and the amount of inductance present in an SMD package depends on the internal geometry of the drain and source connections. It is therefore necessary to consider which type of package is required for any design based not only on its thermal characteristics but also on package inductance, which may not be specified in the datasheet. In short, where high currents are being switched in hard commutation, an SMD package with lowest possible inductance in conjunction with a well laid-out PCB will be required to achieve acceptable performance and avoid reliability and potential EMI issues. When laying out a PCB for a power application it is advisable to use the manufacturer's recommended device footprint and to ensure that handling and soldering guidelines are followed [11].

Stray inductance in power switching circuits increases the amplitude and energy of overvoltage transients, making it necessary to reduce switching speed to avoid avalanching. Transients are produced by rapid changes in current:

$$V_{DS} = L_S \frac{di_d}{dt} \quad [5]$$

where  $L_S$  is determined by the current loop that starts at the closest bus decoupling capacitor, passes through the switching elements and then returns to the capacitor.

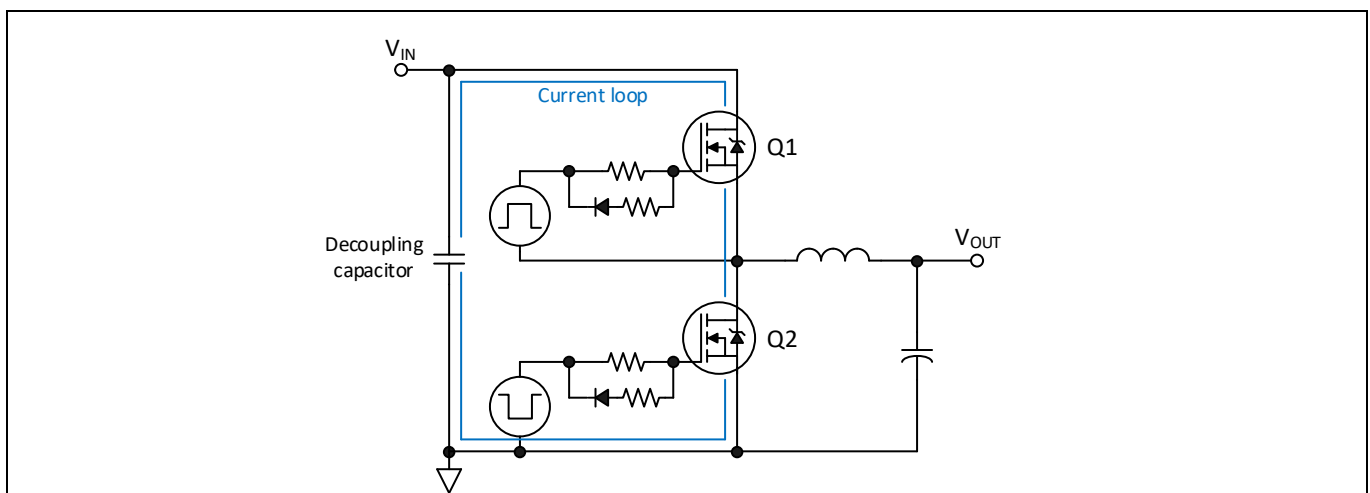

**Figure 19 Loop of switching current in a half-bridge**


In a physical board layout, the inductance of the current loop depends on how tightly spaced the traces are that form it, and on how far away the DC bus decoupling capacitor is located from the MOSFETs. Long traces and larger loop areas also produce radiated EMI. The loop can be minimized by placing the MOSFETs as close to each other and the DC bus decoupling capacitor as possible. This is accomplished by using two or more layers of copper in the PCB and placing the return current path directly underneath the current path, starting at the decoupling capacitor and passing through the MOSFETs to provide tight coupling. The return path is often in the form of a power ground plane. It is common to reserve one or more copper layers in a multi-layer PCB to create this. It should be mentioned here that signal/digital grounds and power grounds should be kept separated to avoid “ground bounce”, which can affect sensitive control circuitry. Power and signal grounds are ideally joined together at one point, preferably the decoupling capacitor ground connection.

A cross-section is shown below of a simplified layout utilizing top and bottom copper layers to create a tight current loop, indicated by the dashed red line. The two layers are connected with multiple vias, which are also used to transfer heat to the bottom side of the board.

# Designing with power MOSFETs

## How to avoid common issues and failure modes

### Package and board layout considerations

 

**Figure 20** PCB layout optimization example for SMD MOSFET packages

## 10 Paralleling of power MOSFETs

Understanding and controlling the steady-state and dynamic current balance between parallel MOSFETs is important in power systems operating with high current. With regard to steady-state current balancing, this may be achieved when the device is operating in the ohmic region (see [Figure 11](#)), because  $R_{DS(on)}$  has a positive temperature coefficient. This allows currents to balance, because if one device were to conduct more current due to having a lower  $R_{DS(on)}$  than its parallel device, its die temperature would rise, thereby raising its  $R_{DS(on)}$  and thus balancing the current. To work effectively the devices should be placed close together, with similar copper trace lengths and widths connected to their drains and sources.

However, paralleling becomes more of a challenge under switching conditions, and more so as frequency increases. This is because dynamic effects now come into play during each switch-on and switch-off operation, which may stress one device more than the other(s). Mis-matches in the following device parameters can affect current sharing and power dissipation during switching: gate threshold ( $V_{TH}$ ), transconductance ( $g_{fs}$ ), gate-source capacitance ( $C_{GS}$ ), Miller capacitance ( $C_{GD}$ ) and body diode recovery ( $Q_{rr}$ ), as well as  $R_{DS(on)}$ . If parts are mis-matched, one device may carry most of the current during switching, which may violate SOA limits. Pay particular attention to the power and thermal stability limits. Besides this, the thermal balancing mechanism described earlier requires some time to reach equilibrium, and this may not be possible when fast switching is taking place. In paralleling applications, the designer should look at the datasheet tolerances given for the parameters mentioned, because tighter tolerances will yield better dynamic balancing.

In the PCB layout, gate loop and current path inductances need to be kept as similar as possible. Circuit layout should be kept as symmetrical as possible to maintain balanced currents in parallel connected MOSFETs. The gates of parallel connected devices may be decoupled by small ferrite beads placed over the gate connections, or by individual resistors in series with each gate to prevent parasitic oscillations.

Design of the gate drive circuitry is also critical. Because parallel MOSFETs are unlikely to turn on or off simultaneously when the first MOSFET turns on, a rapid voltage swing occurs at the source node. This may couple through the  $C_{GD}$  of the slower parallel connected device and produce a voltage spike at the shared gate connection. This can create oscillation as the MOSFETs rapidly turn on and off, which is likely to damage the MOSFETs and the gate driver. To prevent this, each parallel MOSFET should have its own gate drive network placed between the gate and the shared connection to the gate driver.

 


Figure 21 MOSFET paralleling with separated gate drives

A detailed discussion on paralleling is beyond the scope of this application note, but detailed literature is available online.

**Conclusion**

## **11 Conclusion**

This application note has given a short introduction to power MOSFETs and described the key attributes that must be understood when designing with them. It has explained how designing power conversion systems based on MOSFETs requires careful consideration of the trade-offs between switching speed and losses, turn-off transients that may cause avalanching, remaining within the different SOA limits, and the reverse recovery of the body diode. The first step is to choose the best-suited device and heatsinking arrangement to meet the performance requirements of the design, which is then followed by optimization of the gate drive to balance switch-off transients and body diode stress against switching losses. Finally, the PCB layout should be optimized to minimize parasitic inductance in the high-current switching path.

Applying these guidelines should save system development time and unnecessary component failures during testing, which we hope will benefit our customers.



### References

## References

- [1] International Rectifier AN-936A (HEXFET™ power MOSFET designer's manual, 1993), The dos and don'ts of using MOS-gated transistors, Brian R. Pelly.
- [2] International Rectifier AN-1084, **Power MOSFET basics**, Vrej Barkhordarian.
- [3] International Rectifier AN-955, Protecting IGBTs and MOSFETs from ESD, Steve Brown, Bob Ghent.
- [4] International Rectifier AN-1005, **Power MOSFET avalanche design guidelines**, Tim McDonald, Marco Soldano, Anthony Murray, Teodor Avram.
- [5] Infineon AN\_201611\_PL11\_002, **Some key facts about avalanche**, Olivier Guillemant.
- [6] Infineon AN\_201709\_PL11\_006, **A new approach to datasheet maximum drain current ID rating of low voltage MOSFETs**, Gerhard Noebauer, Elvir Kahrimanovic.
- [7] Infineon AP99007, **Linear mode operation and safe operating diagram of power MOSFETs**, Johannes Schoiswohl.
- [8] Infineon AN\_201403, **Hard commutation of power MOSFETs**, Alan Huang.
- [9] International Rectifier, **Paralleling of power MOSFETs for higher power output**, James B. Forsythe.
- [10] International Rectifier, **From planar to trench – evaluation of ruggedness across various generations of power MOSFETs and implications in in-circuit performance**, Hemal Shah, Steve Oknaian, Eric Persson, Rongjun Huang.
- [11] Infineon, **Recommendations for board assembly of Infineon discrete packages without leads**.
- [12] Electronic Design, MOSFET design basics you need to know, Paul Schimel.
- [13] Wikipedia, Power MOSFETs, [https://en.wikipedia.org/wiki/Power\\_MOSFET](https://en.wikipedia.org/wiki/Power_MOSFET).

**Revision history**

**Revision history**

<b>Document version</b>	<b>Date of release</b>	<b>Description of changes</b>
V 1.0	2022-01-10	First release
V 1.1	2022-02-10	Updated sections 5 and 7 to include references to $Q_{GD}/Q_{GS}$ and $Q_{GD}/Q_{GS(TH)}$ in addition to $C_{GS}/C_{GD}$ to comply with more common terminology.

#### Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

**Edition 2022-02-10**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2022 Infineon Technologies AG.**

**All Rights Reserved.**

**Do you have a question about this document?**

**Email:** [erratum@infineon.com](mailto:erratum@infineon.com)

**Document reference**

**AN\_2112\_PL18\_2112\_024619**

#### IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office ([www.infineon.com](http://www.infineon.com)).

#### WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.