XMC in Application – Dimmable LED Current Control

XMC Microcontrollers October 2015





Learning objectives

- Know the key features of the dimmable LED current control application
- Understand how the peripherals of the XMC1000 microcontroller can be used to implement the key features of the dimmable LED current control application



Agenda

- 1 Overview
- 2 Key Features
- 3 Specification
- 4 System Block Diagram
- 5 Hardware Overview
- 6 Highlight MCU Features
- 7 Resource Listing

Dimmable LED Current Control – Overview



- This training slides showcase a low cost yet high quality dimmable LED current control solution for a single LED channel, using an XMC1000 microcontroller.
- The HOT covers the key features and controls of the dimmable LED current control solution.

Dimmable LED Current Control – Key Features



Target Application

Dimmable LED Current Control

Key Features

- Inverse-buck with <u>peak current control</u>
 - Fast LED current control for flicker-free light (switching speed up to 3MHz)
- Modulation dimming for accurate dimming levels
- High efficiency
- Compact low cost design

Dimmable LED Current Control – Specification




Specifications

- Up to 30V_{DC} input voltage
- Up to 700mA average output current
- Up to 1A peak current

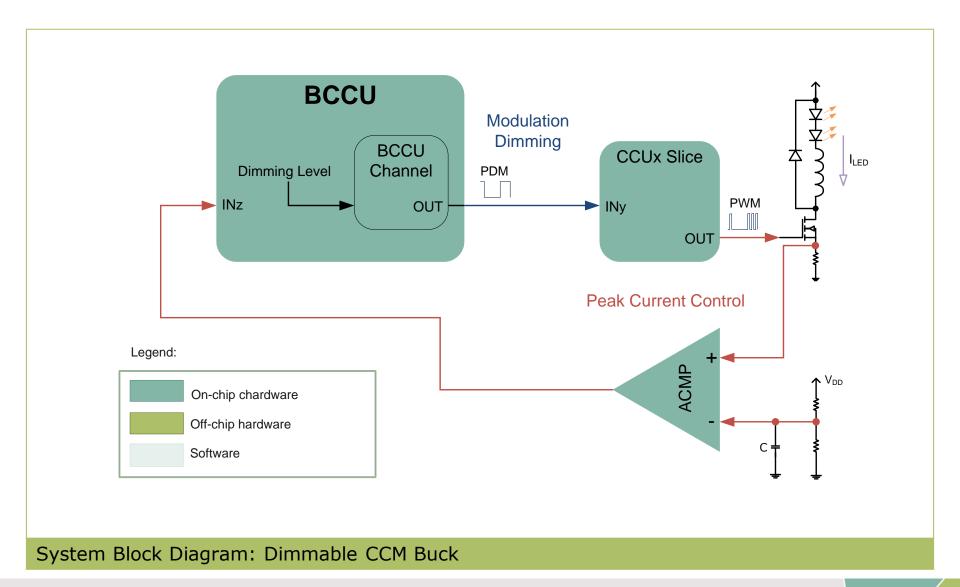Dimmable LED Current Control – System Block Diagram





Dimmable LED Current Control – Highlight MCU Features



- CCU4/8 PWM
 - Generate PWM signal for driving MOSFET
 - External stop function with ACMP for peak current control
 - Timer function for fixed current ripple off-time
 - External modulation function with BCCU for dimming control
- ACMP
 - Peak current detection
 - Gating input signal for BCCU
- BCCU
 - LED dimming control
 - Modulation signal for CCUx

Dimmable LED Current Control – Hands-on Training




- 1. Key Feature Peak Current Control
- 2. Key Feature Modulation Dimming
- Hands-on Training



Key Feature – Peak Current Control

Peak Current Control Block Diagram




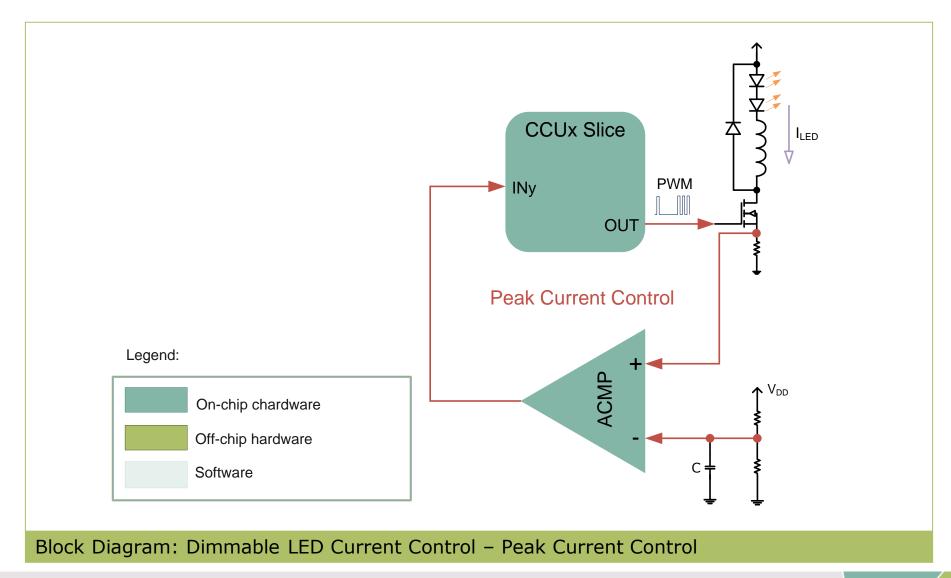

Peak Current Control – LED Current (1/3)



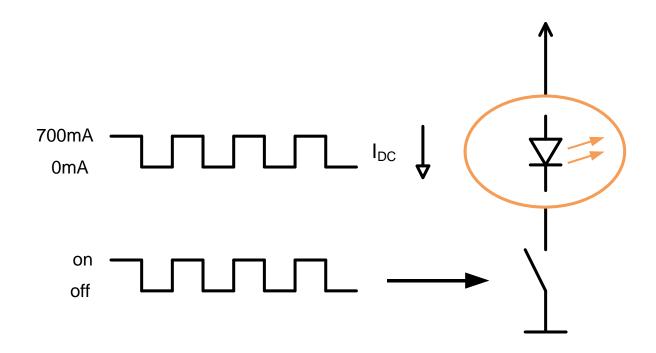
- LEDs are usually driven by a modulating signal
 - Periods of ON and OFF
- The main objective:
 - Ensure LED current is stable during ON times




Peak Current Control – LED Current (2/3)



Ideal

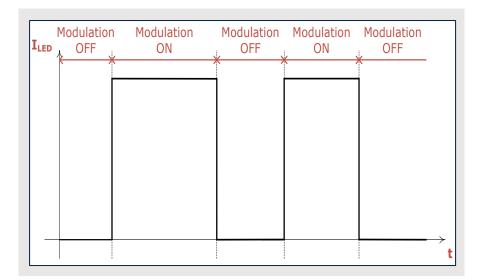

Reality

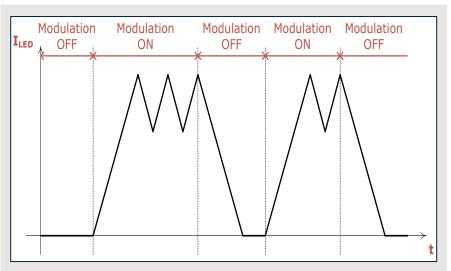


- Current rises and falls instantly
- No ripple
- Fast modulation for high quality light possible

- Current takes time to rise and fall
- Ripple (switch-mode control)
- Fast modulation for high quality light challenging

Peak Current Control – LED Current (3/3)



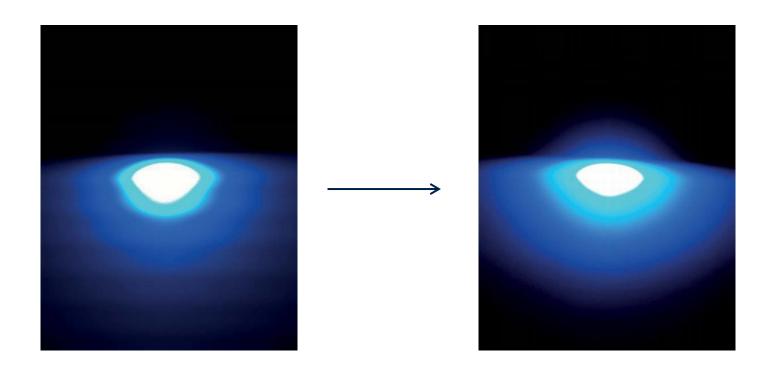
- Fast control loop is required for flicker-free light
 - High speed modulation dimming
 - Fast changes in current required




Peak Current Control – LED Current Control Circuit (1/3)



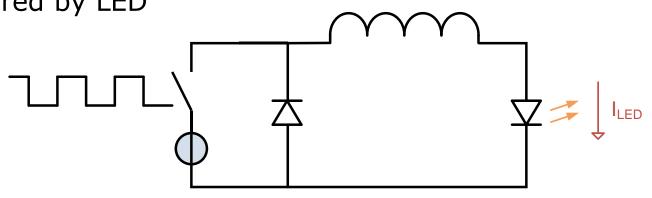- Buck converter is commonly used
 - Efficient for converting supplied voltage down to voltage required by LED




Continuous operation mode

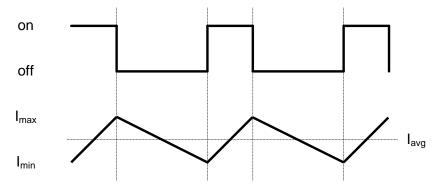

Peak Current Control – LED Current Control Circuit (2/3)



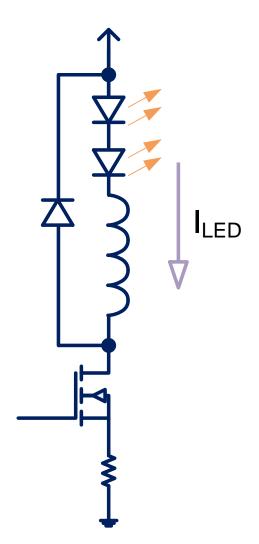
- Inverted buck topology
- Low cost
 - 1 MOSFET
 - 1 inductor
 - 1 diode
 - 1 shunt



Peak Current Control – LED Current Control Circuit (3/3)



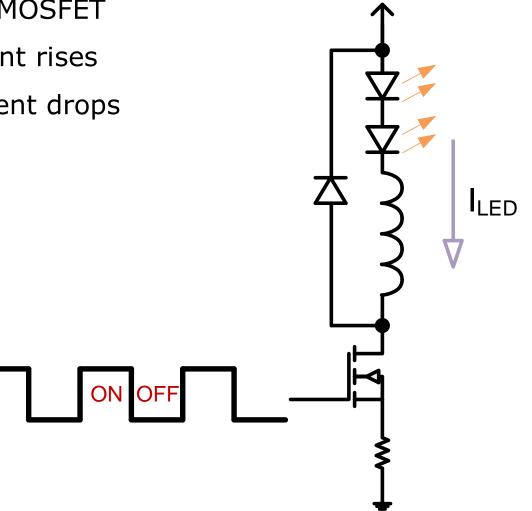- Modulation signal drives MOSFET
- MOSFET ON → LED current rises
- MOSFET OFF → LED current drops




Peak Current Control – LED Current Control with XMC1 (1/13)



I_{LED}

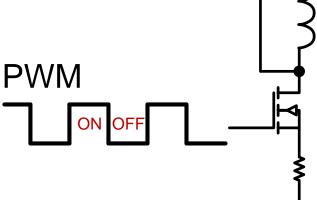- Capture/Compare Unit (CCUx)
 - 16-bit timer
 - Compare channel(s)
 - Pulse-width modulated (PWM) output






Peak Current Control – LED Current Control with XMC1 (2/13)



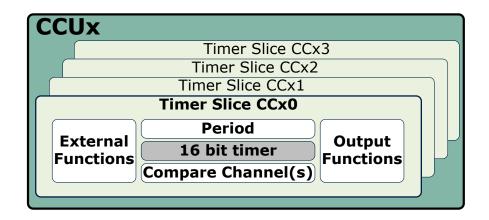
- Each CCUx kernel has 4 identical timer slices
- Each timer slice can be configured independently from one another
 - Which means we can have 4 different timers!
 - Timer operation modes:
 - Center aligned/edge aligned
 - External functions:
 - External start/stop/modulation
 - Output functions:
 - Passive level
 - Trap



Peak Current Control – LED Current Control with XMC1 (3/13)




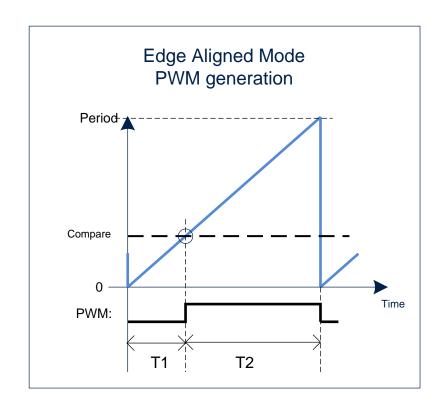- 16-bit CCUx slice timer starts counting up
- PWM signal stays passive till timer reaches compare value (compare match)
- PWM signal stays active till timer reaches period value (period match)
- Timer gets cleared and restarts counting
- Duty cycle = $\frac{T2}{T1+T2} \times 100$



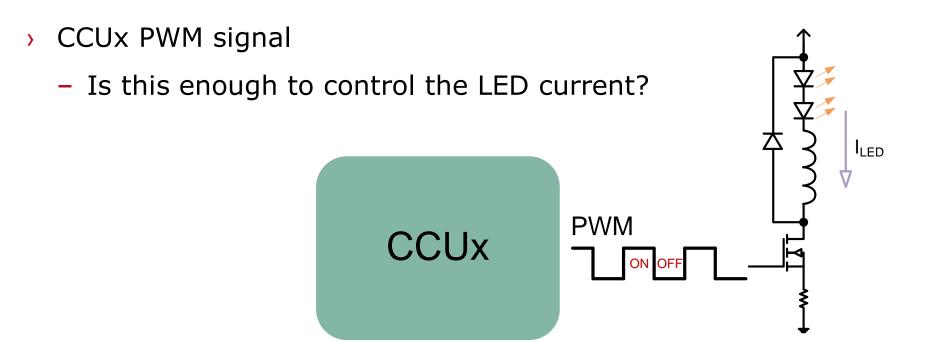Peak Current Control – LED Current Control with XMC1 (4/13)






No! What problems can you foresee?

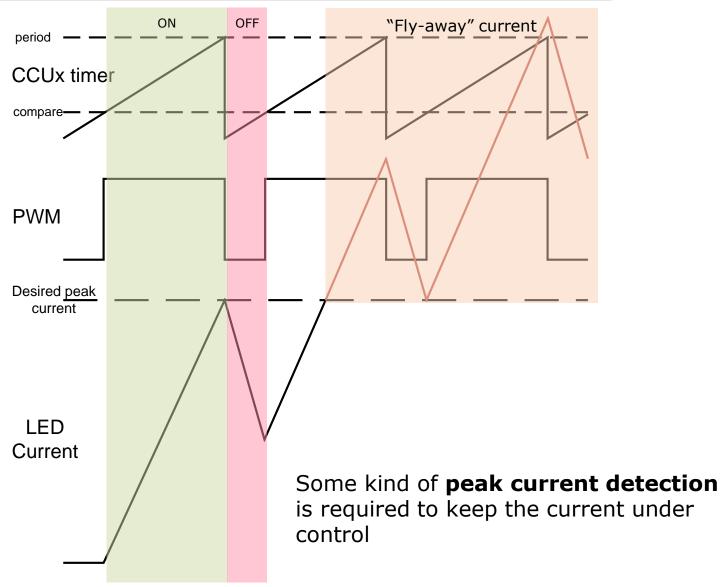Peak Current Control – LED Current Control with XMC1 (5/13)






Peak Current Control – LED Current Control with XMC1 (6/13)



- Analog comparator (ACMP)
 - Detects when desired peak level is reached
 - Sends a trigger signal to CCUx to turn MOSFET OFF
 - Stops LED current from rising further


CCUx

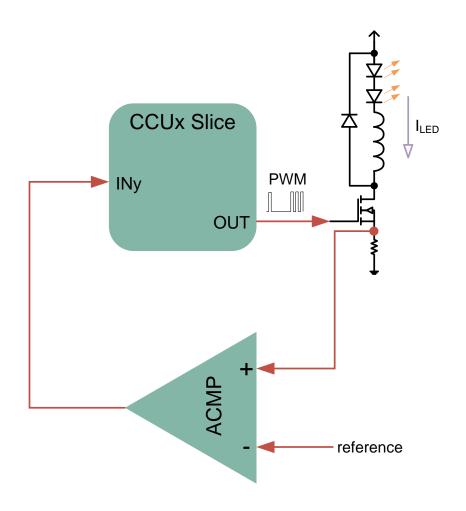- Upon receiving trigger signal from ACMP, clears its timer and starts counting up again
 - This is the external stop feature



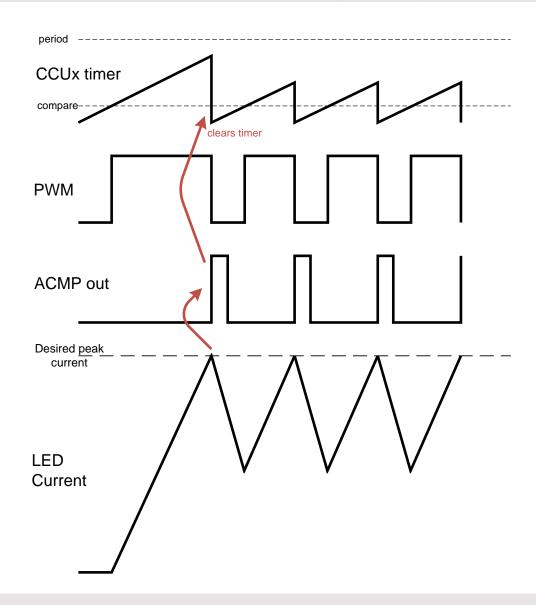Peak Current Control – LED Current Control with XMC1 (7/13)







Peak Current Control – LED Current Control with XMC1 (8/13)



- ACMP Configuration
 - Filter active
 - Hysteresis OFF
 - Output inversion depends on input connections

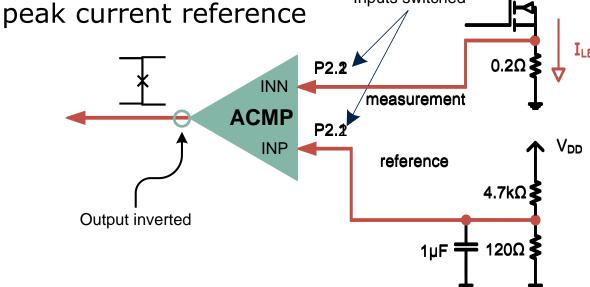- Resistive divider circuit for Inputs switched




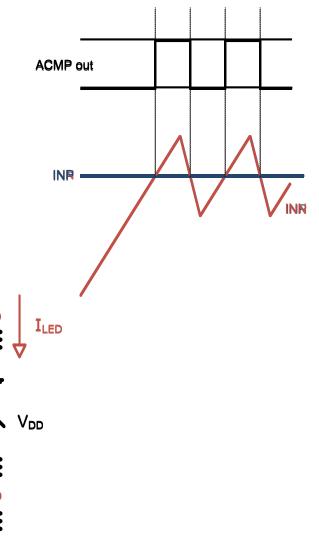


Peak Current Control – LED Current Control with XMC1 (9/13)



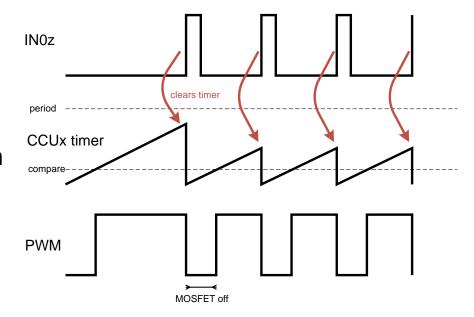- CCUx Configuration
 - Event Y
 - Trigger on rising edge
 - Trigger external stop function
 - Clears timer (flush)




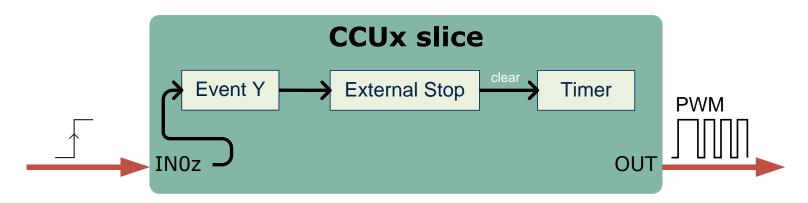

Peak Current Control – LED Current Control with XMC1 (10/13)



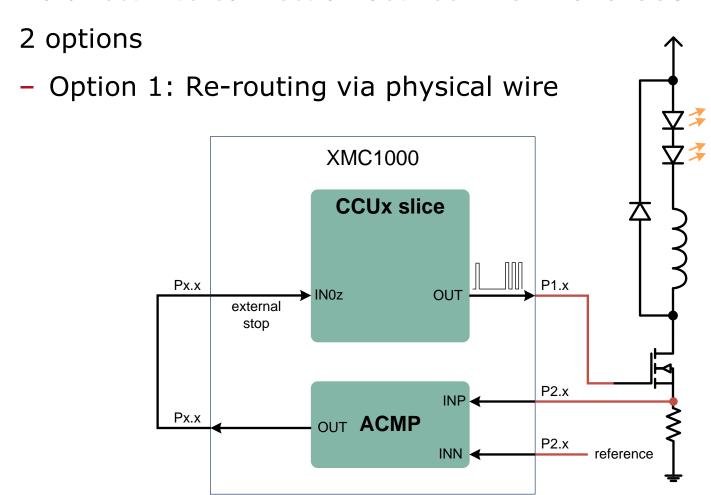
No direct interconnection between ACMP and CCUx



Peak Current Control – LED Current Control with XMC1 (11/13)



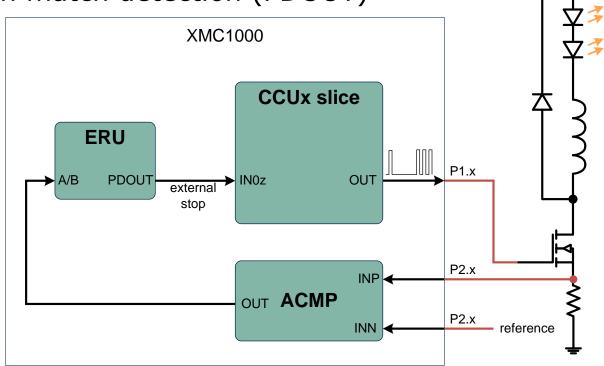
- Option 2: Re-routing via ERU
 - Direct input A or B
 - Detect rising edge
 - Pattern match detection (PDOUT)



Peak Current Control – LED Current Control with XMC1 (12/13)



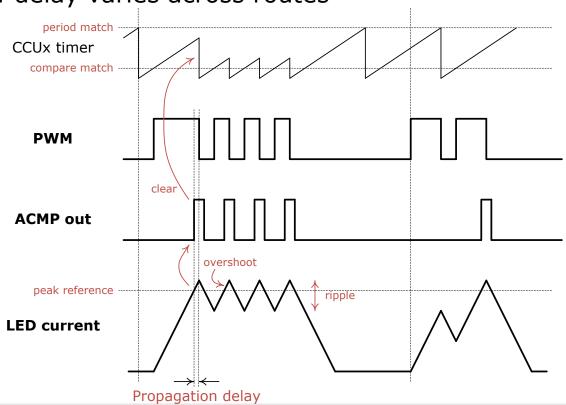
- > Propagation delay
 - Between ACMP out trigger and clearing of CCUx timer
 - Results in LED current overshoot
 - Length of delay varies across routes



Peak Current Control – LED Current Control with XMC1 (13/13)



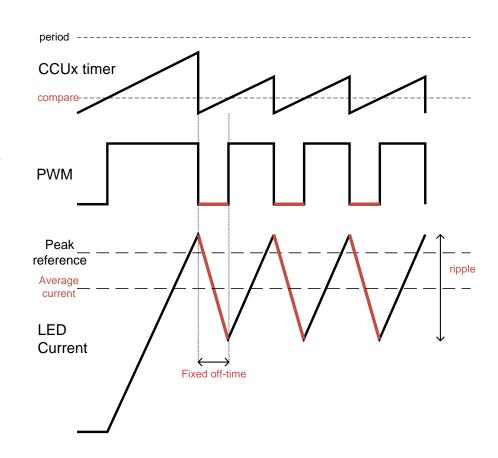- CCUx timer compare value affects the MOSFET off-time
 - This affects the size of the current ripple (amount of current drop)
- LED average current is half of the current ripple
- Higher compare value =Larger ripple =Lower average current value
- Fixed off-time






2. Key Feature – Modulation Dimming

Modulation Dimming – Dimmable Current Control with XMC1 (1/8)



- LED brightness can be controlled by varying the LED current
- Also known as analog dimming

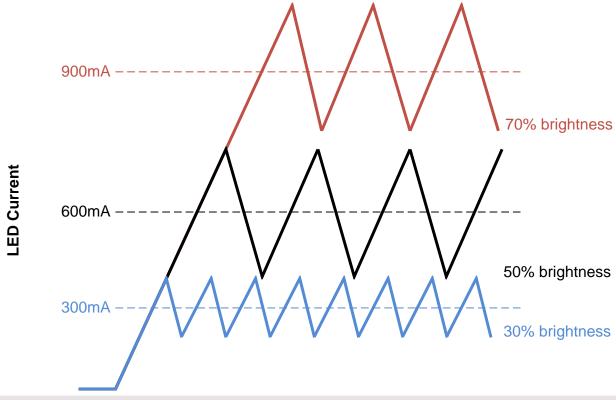
Disadvantage: Non-linear relationship between current and brightness



Modulation Dimming – Dimmable Current Control with XMC1 (2/8)



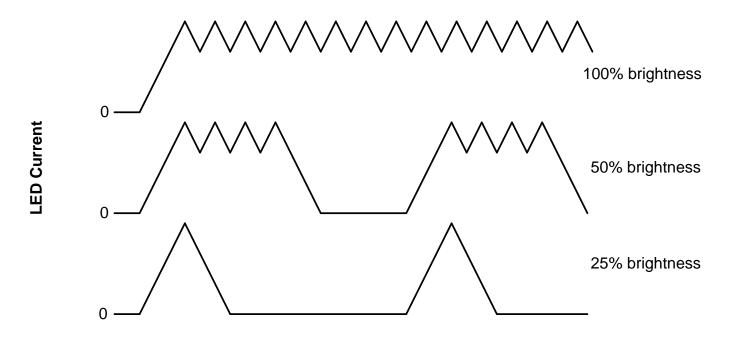
- Alternatively, LED brightness can be controlled by varying the duration of the LED current
 - i.e. MOSFET on-time
- Also known as modulation dimming
- Advantage: Linear relationship between on-time and brightness



Modulation Dimming – Dimmable Current Control with XMC1 (3/8)



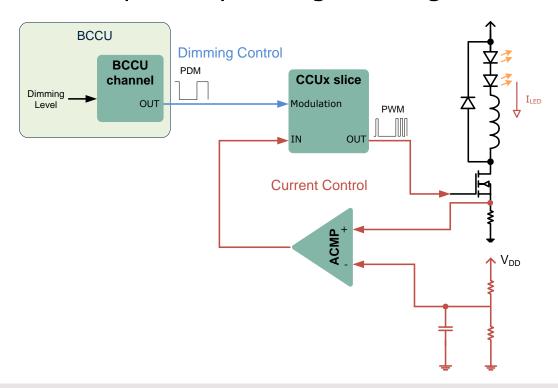
- BCCU channel generates PDM signal
 - Contains dimming level information
- > PDM signal used as modulation input to CCUx slice
 - PWM signal is output only during PDM signal ON-times



Modulation Dimming – Dimmable Current Control with XMC1 (4/8)




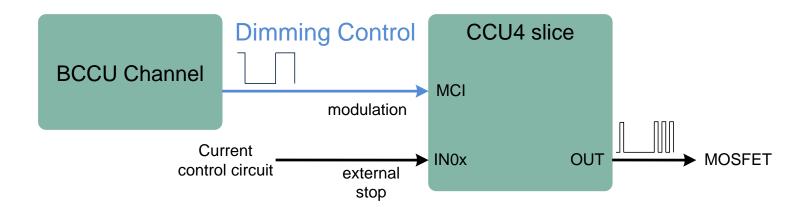- Multi-channel mode enabled for CCU4 slice
 - PDM output used as multi-channel input control signal



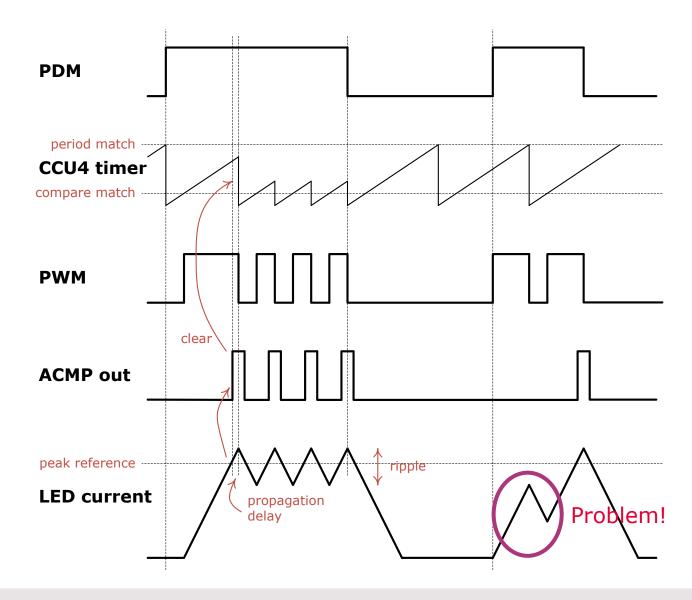Modulation Dimming – Dimmable Current Control with XMC1 (5/8)






Modulation Dimming – Dimmable Current Control with XMC1 (6/8)



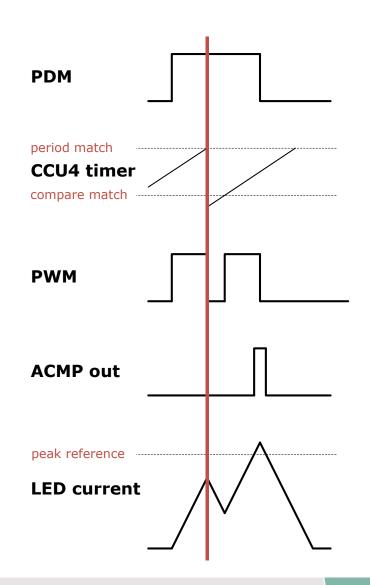
- CCU4 timer period match reached before LED current reaches peak reference value
- > Effect
 - A momentary drop in average LED current value
 - Noticed as shimmer at low brightness levels
- Workaround
 - Set CCU4 period value to max to minimize occurrence
 - Use CCU8 instead of CCU4



Modulation Dimming – Dimmable Current Control with XMC1 (7/8)




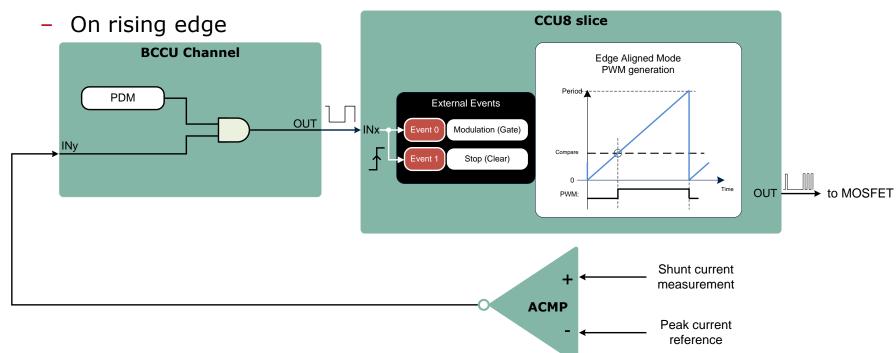- Inverted ACMP out as gating input to BCCU channel
- BCCU output as input to CCU8 slice for 2 external events
 - Modulation (gate CCU8 output)
 - Not synchronized
 - 2. Stop (clear timer)



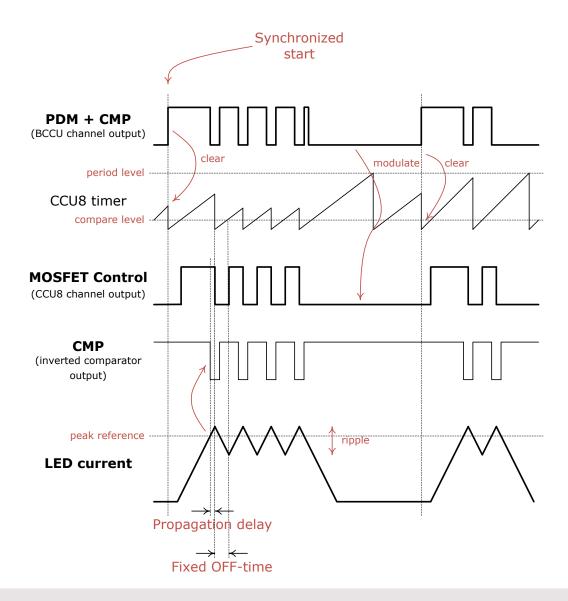Modulation Dimming – Dimmable Current Control with XMC1 (8/8)







Support material:

Collaterals and Brochures





- Product Briefs
- Selection Guides
- Application Brochures
- Presentations
- Press Releases, Ads

www.infineon.com/XMC

Technical Material





- Application Notes
- Technical Articles
- Simulation Models
- Datasheets, MCDS Files
- PCB Design Data

- www.infineon.com/XMC
- > Kits and Boards
- DAVETM
- Software and Tool Ecosystem

Videos



- Technical Videos
- Product Information Videos

- Infineon Media Center
- XMC Mediathek

Contact



- Forums
- Product Support

- > Infineon Forums
- <u>Technical Assistance Center (TAC)</u>



Glossary abbreviations

- ACMP Analog Comparator
- BCCU Brightness and Color Control Unit
- CCM Continuous Conduction Mode
- CCU Capture/Compare Unit
- DAVE™ Free development IDE for XMC™
- ERU Event Request Unit
- LED Light Emitting Diode
- MOSFET Metal-oxide-semiconductor field-effect transistor
- PDM Pulse-density Modulation
- > PWM Pulse Width Modulation



Disclaimer

The information given in this training materials is given as a hint for the implementation of the Infineon Technologies component only and shall not be regarded as any description or warranty of a certain functionality, condition or quality of the Infineon Technologies component.

Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this training material.



Part of your life. Part of tomorrow.

