

# Full GaN 65 W active clamp flyback evaluation board

## EVAL\_ACF\_65W\_FULLGAN

### About this document



### Scope and purpose

This engineering report explains how to set up and run Full GaN 65 W active clamp flyback (ACF) universal charger/adaptor evaluation board featuring ICQ800NLS CoolGaN™ SG HEMT as well as CoolGaN™ integrated power stage (IPS) half-bridge as shown in **Figure 1**. The board converts the universal AC input voltage to a constant 20 V DC output. At full load, the average operating frequency of this unit varies from 290 kHz to 350 kHz depending on the input voltage level. To demonstrate the operation of the board, some test points are provided to observe the signals with proper test equipment. Finally, some of the unit's performance metrics, such as hardware thermal imaging, and efficiency vs. load, are evaluated.

### Intended audience

This engineering report is intended for power electronic design engineers, application engineers, and students who are familiar with power converters.

### Infineon components featured

- [IQC800NLS](#)
- [IGI60F2020A1L](#)
- [BSS126](#)



**Figure 1** Full GaN 65 W ACF evaluation board featuring ICQ800NLS CoolGaN™ SG HEMT

## Table of contents

<b>About this document</b> .....	<b>1</b>
<b>Table of contents</b> .....	<b>2</b>
<b>1 Introduction</b> .....	<b>3</b>
1.1 Evaluation board specifications .....	4
<b>2 Functional description</b> .....	<b>5</b>
2.1 CoolGaN™ half-bridge IPS circuitry.....	6
2.1.1 Low-side gate driver.....	7
2.1.2 High-side gate driver.....	7
<b>3 Setup and use</b> .....	<b>8</b>
3.1 Test equipment needed .....	8
3.2 Measurement points .....	9
3.3 Power-up and power-down sequencing .....	9
3.4 Full-power test .....	11
3.5 Efficiency performance .....	14
3.6 Thermal performance .....	16
<b>4 PCB layout</b> .....	<b>18</b>
<b>5 Bill of materials</b> .....	<b>20</b>
<b>References</b> .....	<b>24</b>
<b>Revision history</b> .....	<b>25</b>

Introduction

# 1 Introduction

This hardware provides a quick way to evaluate the Infineon CoolGaN™ technology both in primary and secondary sides in the low-power adapter application in high-frequency ACF topology (for more information refer to [1] and [2]). As shown in Figure 2, the main switch and the clamp switch in an ACF converter can be replaced with low- and high-side devices in a half-bridge IPS device. The hardware features the easy-to-use IPS chipset in a small PCB area interfacing with the ACF controller, as shown in Figure 3.

To observe the thermal performance of the components installed on the PCB, the PCB layout is designed in a non-compact form factor with least occupied space. This board is an evaluation board and not a reference design; therefore, the PCB layout optimization and the hardware volume reduction depend on the designers' preference in terms of manufacturing approach.

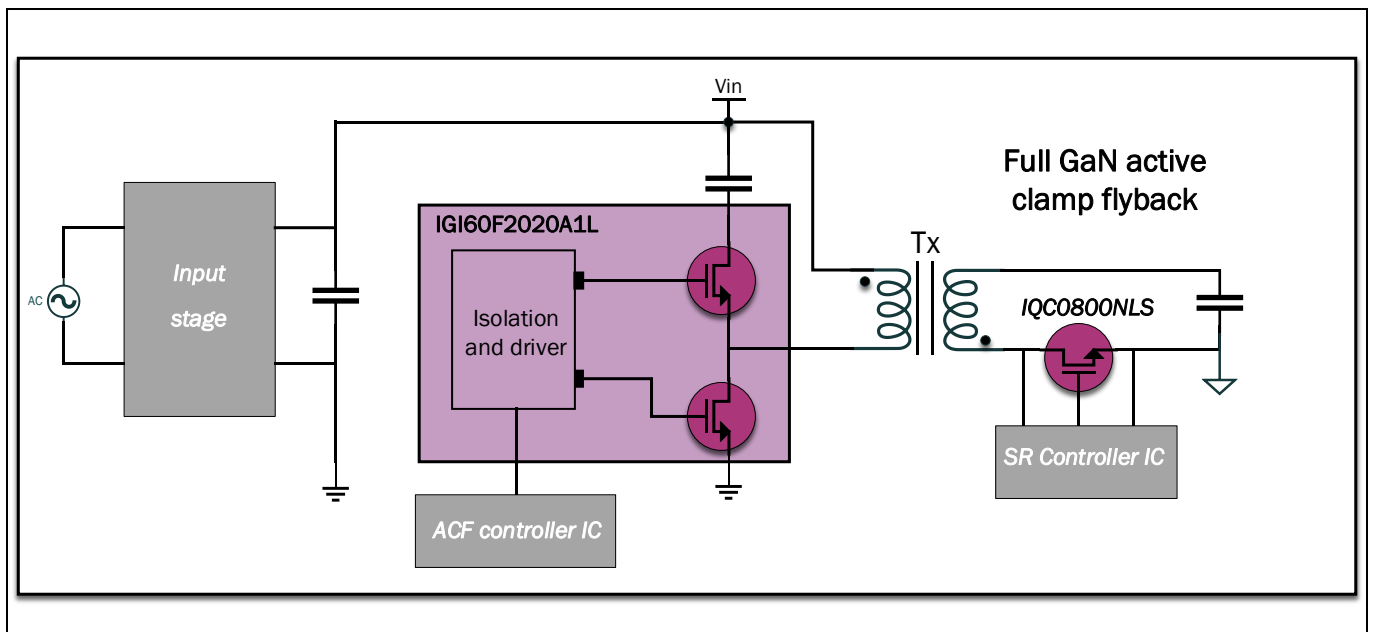


Figure 2 CoolGaN™ technology in ACF topology

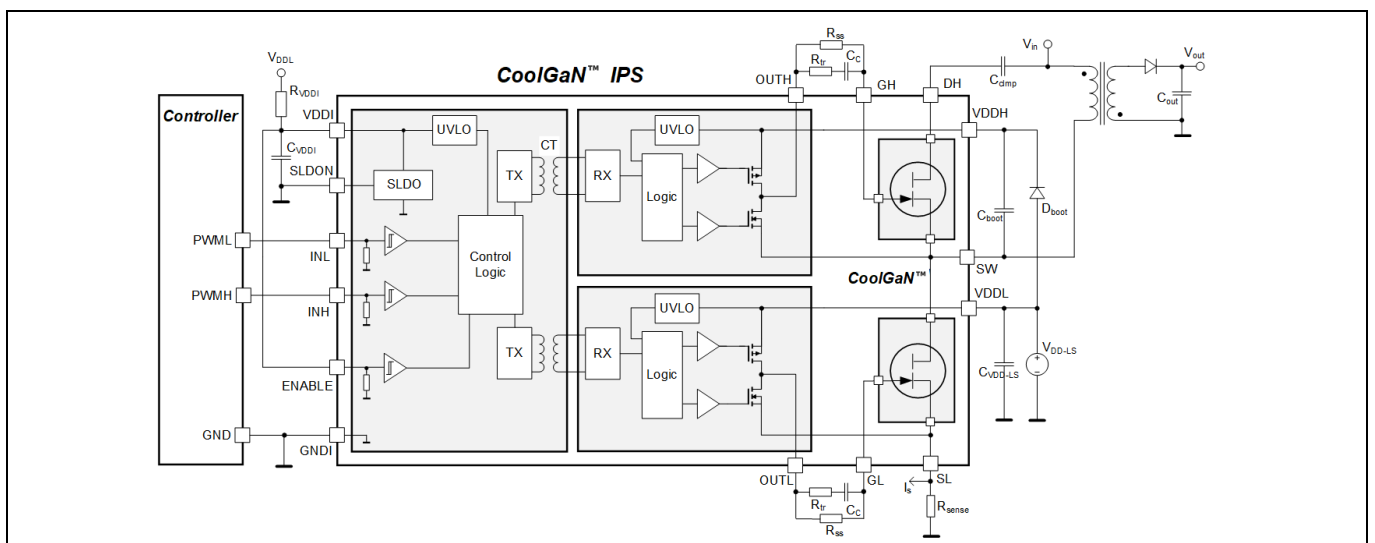


Figure 3 CoolGaN™ IPS circuitry in ACF topology [3]

## Introduction

### 1.1 Evaluation board specifications

**Table 1** Evaluation board specifications and limits


Parameter	Values			Unit	Notes
	Min.	Typ.	Max.		
AC input voltage	100		240	V	
AC input voltage frequency	49		62	Hz	
AC input current			2	A	
DC output voltage	19	20	21	V	
DC output current	0		3.25	A	
Efficiency (peak)			93.3	%	
Standby power consumption			< 300	mW	
Rated power			65	W	
Operating frequency at full power	300		500	kHz	Changes based on the input voltage
Operating ambient temperature		25		°C	

Note: The PCB dimensions are 59 x 84 mm (max.).


Functional description

## 2 Functional description

The block diagram of the hardware and their functions is shown in **Figure 4**. The AC input stage includes the protection fuse, EMI filter and rectifier stage. The CoolGaN™ IPS includes the main and clamp switches. The ACF controller drives the high-side and low-side through the PWM signals generated referred to the DC bus negative rail. The feedback signals to the controller are provided by the current sensing resistor and the optocoupler. The optocoupler is regulated by an analog shunt regulator, and it is set to regulate the output DC voltage at 20 V. The SR FET is driven by its individual controller referred to the output voltage negative rail. **Figure 5** shows a different section of the evaluation board.

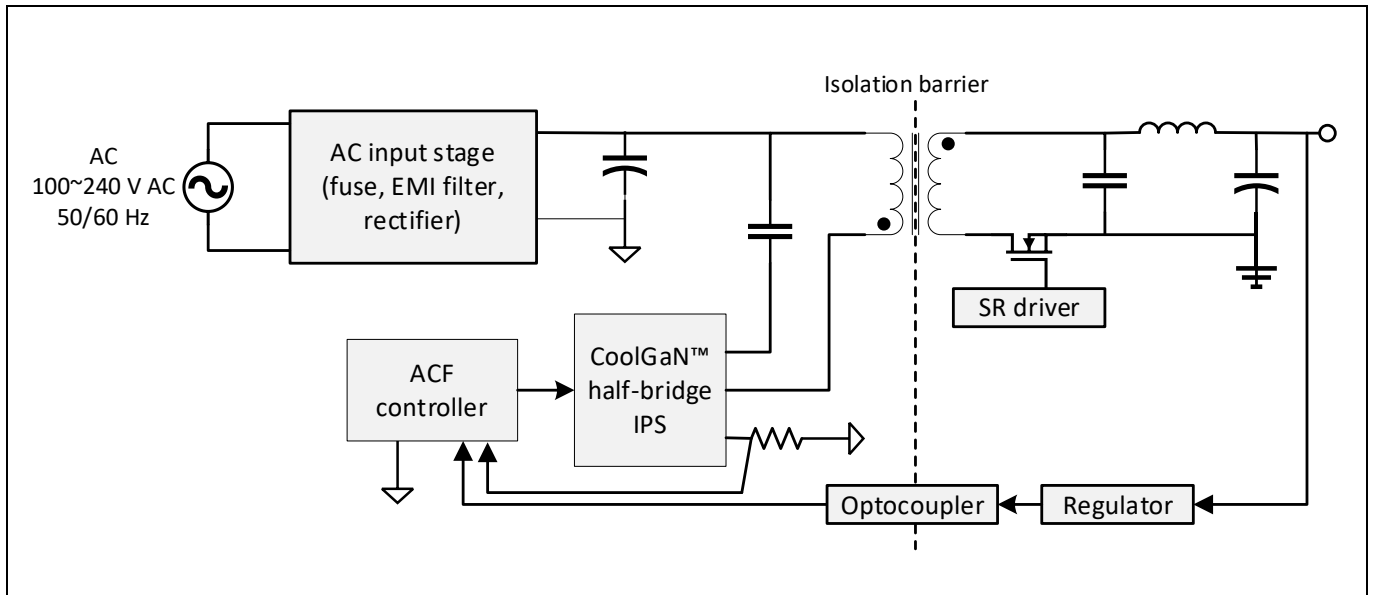

**Figure 4** Block diagram of the CoolGaN™ IPS evaluation hardware in ACF topology [3]

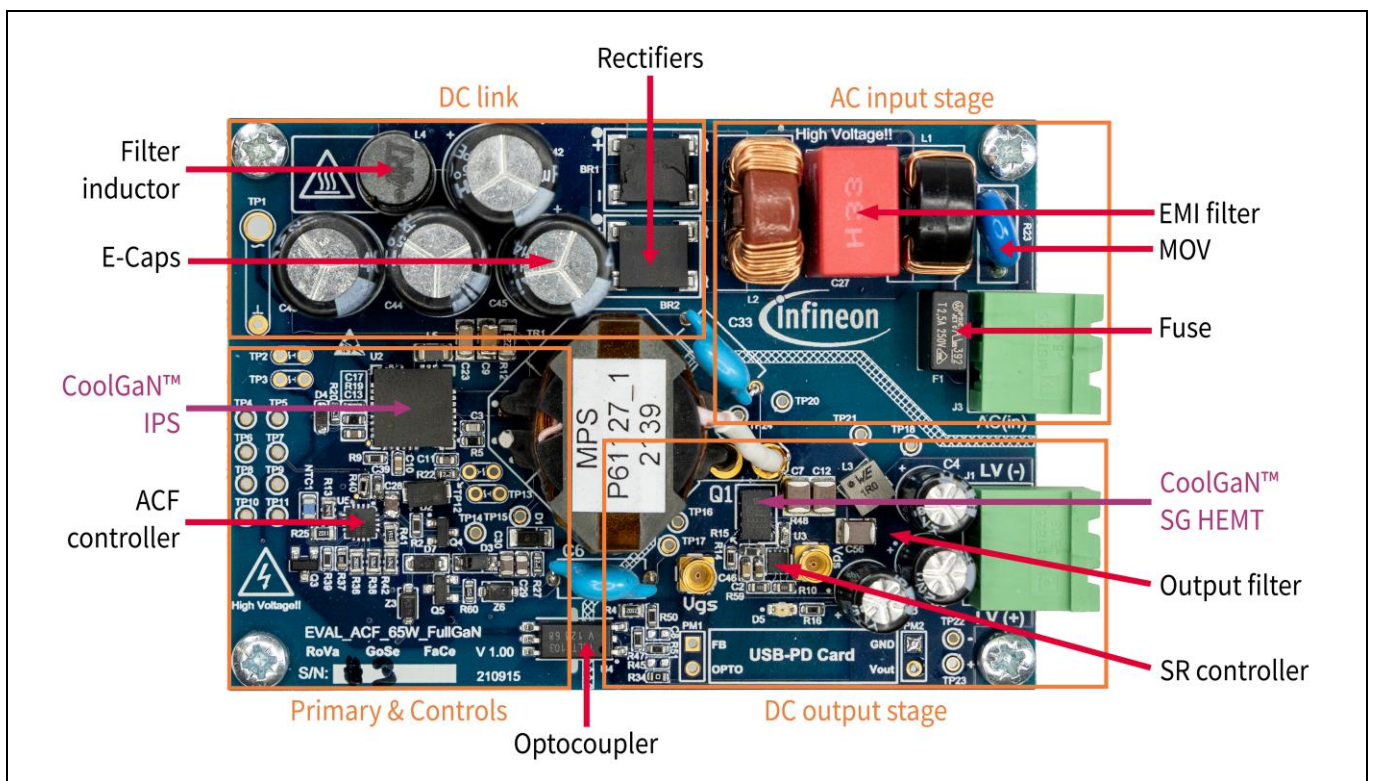


**Figure 5** Evaluation board sections



### Functional description

The schematic is shown in **Figure 6**. The following sections explain each item of hardware in detail.

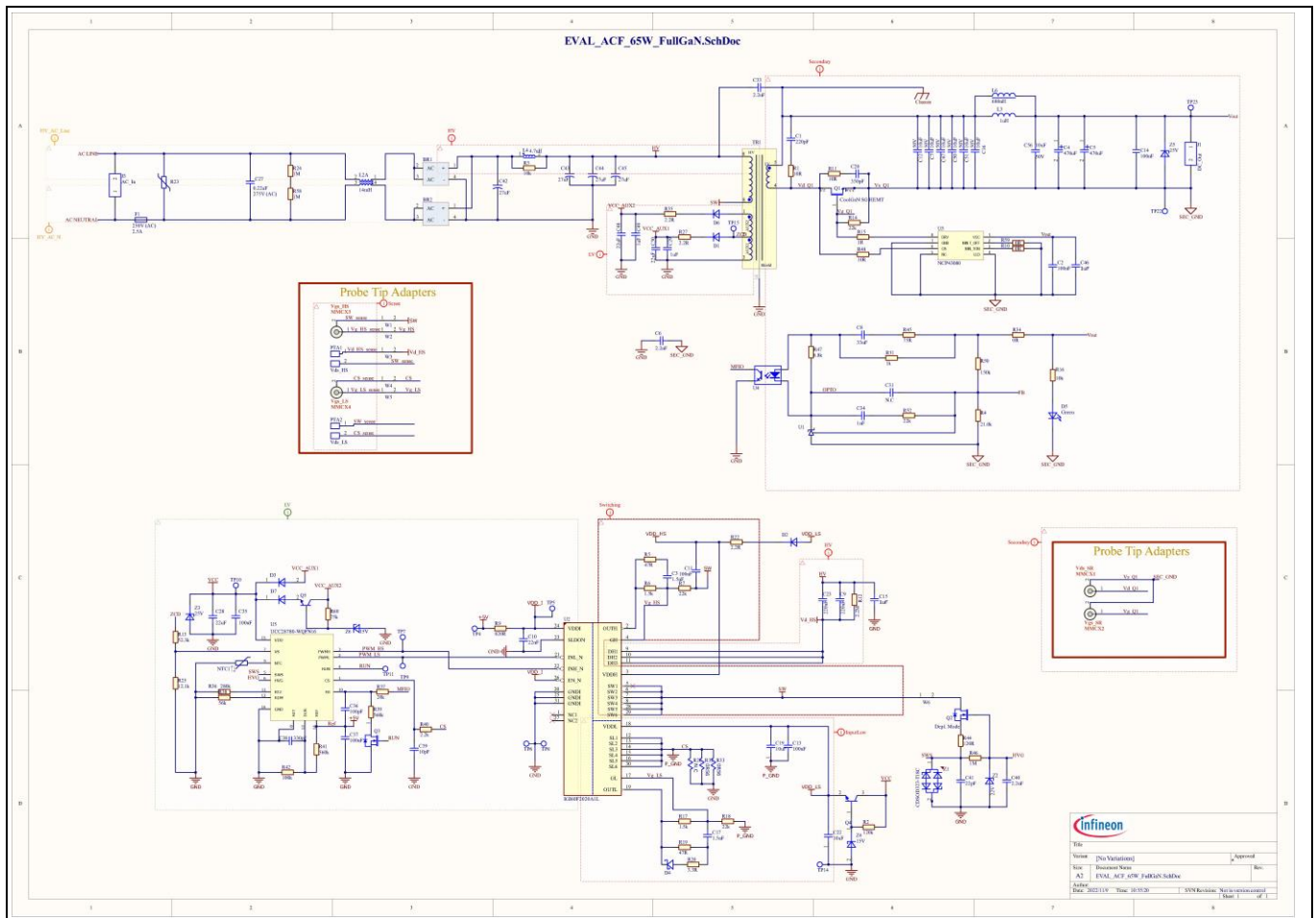

**Figure 6 Full GaN 65 W ACF evaluation board hardware schematic**

## 2.1 CoolGaN™ half-bridge IPS circuitry

**Figure 7** shows the circuitry around the CoolGaN™ IPS half-bridge IGI60F2020A1L in this evaluation board. The ACF controller drives the logic inputs of the IPS chipset. In this application, the 3.3 V regulator inside the IPS is activated by pulling down SLDON pin 23, and the 5 V reference ACF controller is used to supply the VDDI pin through the shunt resistor (R9). The R9 value will provide about 2 mA supply to the VDDI pin, which is sufficient to operate the chipset in this application.

Functional description

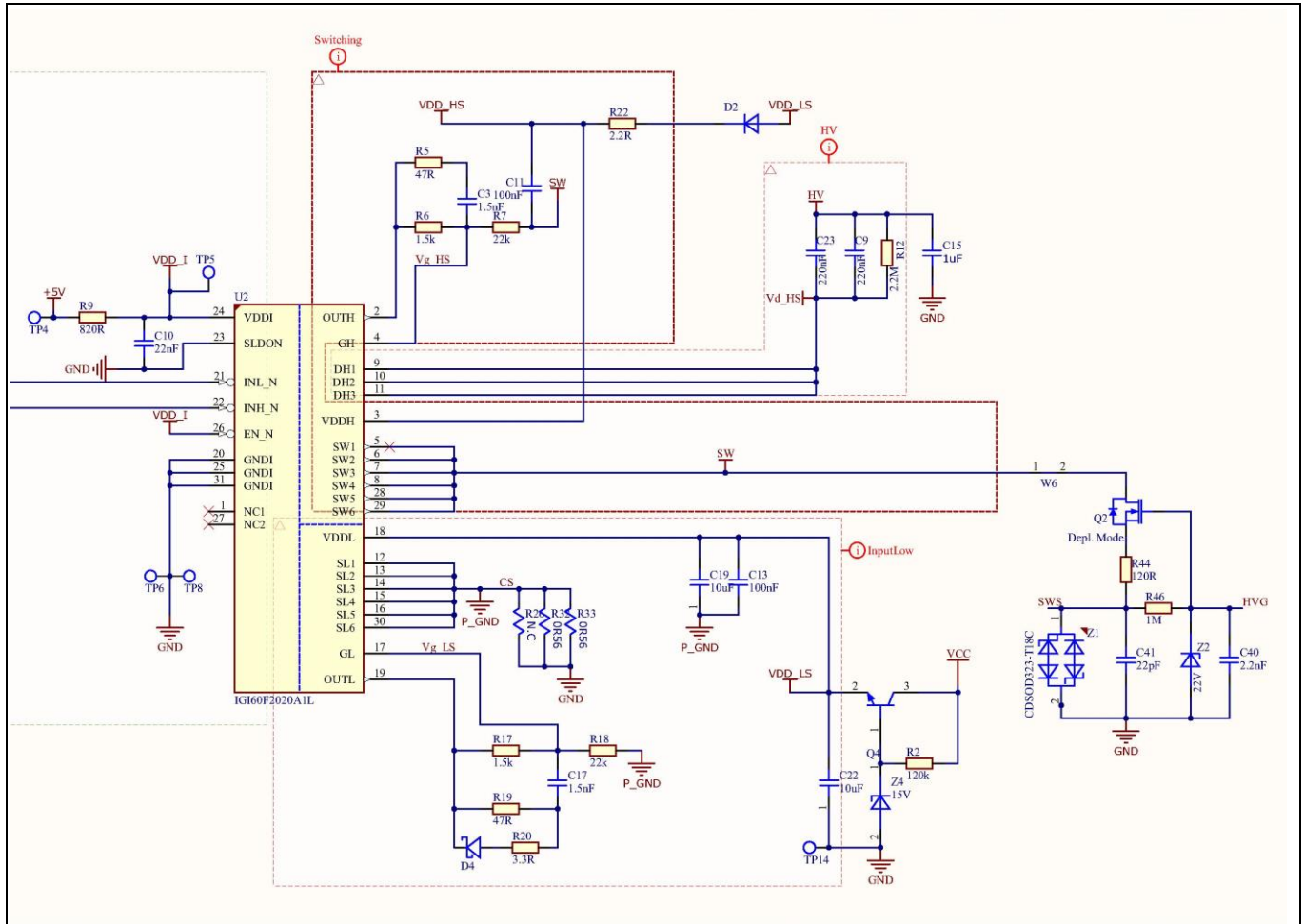


Figure 7 CoolGaN™ IPS circuitry in ACF adapter topology

### 2.1.1 Low-side gate driver

Low-side gate driver power is provided by Q4 and Z5 supplied by V<sub>CC</sub> (supplied by transformer AUX winding rectified output). The RRC network consists of R17, R19, R20, D4, and C17 is used to drive the low-side GaN gate. For sizing of the circuit values refer to the [IGI60F2020A1L](#) datasheet. R18 is a standard 22k gate pull-down resistor to ensure the gate-source voltage remains at zero even when the gate driver is unpowered during start-up.

### 2.1.2 High-side gate driver

A bootstrap circuit consisting of D2, inrush limiter R22 and C11 is used to supply the high-side gate driver sourced by VDD\_LS. The RRC network for this channel consists of R5, R6 and C3. As for the low-side, a standard 22k resistor is used to ensure pull-down of the high-side GaN gate during start-up.

Setup and use

### 3 Setup and use

Figure 8 shows the recommended configuration to measure the efficiency of the evaluation board using two channels of a power analyzer. If a power analyzer is not used, connect the AC source directly to the AC(in) terminal (J3) and the DC load to LV(+) and LV(-) on the J1 terminal. If the DC load is an electronic load, note the polarity to avoid damaging the load.

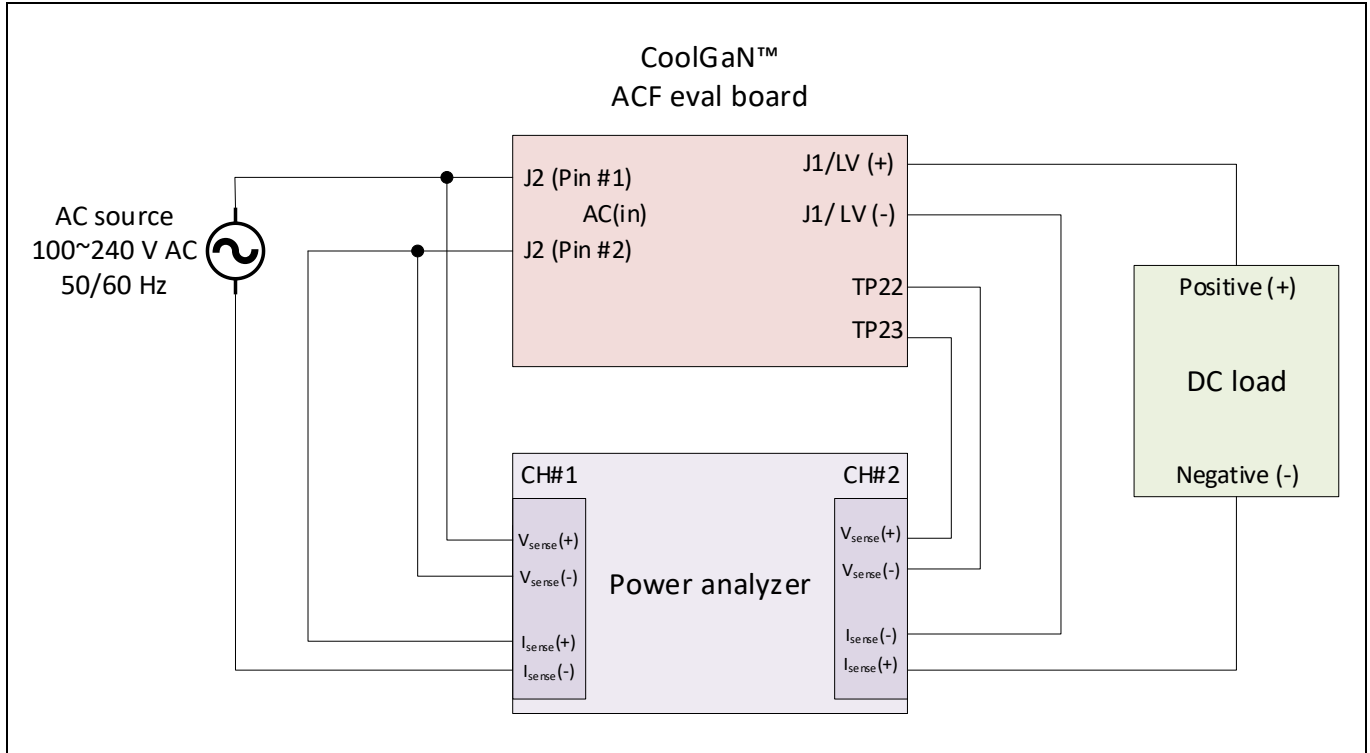


Figure 8 Recommended connections for efficiency measurements [3]

**Attention:** *This evaluation board has high-voltage terminals and exposed areas. To avoid electric shock, take appropriate measures. The hardware does not have any overvoltage protection system. Use an appropriate protective epoxy shield or box to cover the hardware to prevent any possible injury.*

**Attention:** *Always observe the input and output voltages. Do not operate the board above the specified input voltage (240 V AC). Use a lab test power supply with a current limit and set it to a proper value to avoid catastrophic damage to the board in case of any failure. Eye and ear protection are recommended for safety, as all power electronic labs employ it. For any safety concerns and technical questions reach out to your sales team.*

#### 3.1 Test equipment needed

- AC power supply up to 240 V with sufficient current ( $\sim 2 A_{RMS}$ ) and with proper high-voltage cables.
- Oscilloscope for measurements and observations with standard passive probes.
- Power analyzer (two channels) to measure efficiency.
- Isolated current probe (Rogowski type) to observe the transformer current.
- Voltmeter to measure the output DC voltage.
- DC electronic load.



Setup and use

### 3.2 Measurement points

There are multiple test points to connect the oscilloscope for observation (either through-hole pad-pair, or single-point access). [Table 2](#) describes the test points.

**Table 2** Test point descriptions

Test point label	Description
TP4	ACF controller +5 V reference voltage signal
TP5	This test point is to observe if the VDDI logic supply of the chipset is active with about 3.3 V voltage level with respect to the digital ground
TP10	V <sub>CC</sub> test point for the ACF controller voltage monitoring
TP7	Input to the high-side logic of the IPS (INH) – ACF controller PWMH signal
TP6,TP8	GND reference point (for TP3)
TP9	Input to the low-side logic of the IPS (INL) – ACF controller PWML signal
TP23	Adapter DC output positive
TP22	Adapter DC output negative (secondary ground)

### 3.3 Power-up and power-down sequencing

**Power up:**

Because the DC bus of the adapter is discharged at start-up, to avoid the inrush current in powering up, the AC source must be programmed to ramp up its output voltage (1~5 V/ms). Disconnect or turn off the DC load. The adapter might not start up under the load (the controller OCP might trigger). Turn on the AC source with 120 V AC/60 Hz and observe the output DC voltage (it should be around 20.3 V at no load). [Figure 9](#) shows the start-up of the adapter with 240 V AC supply turn-on. To apply load, DC load can be turned on after adapter power-up (we suggest using current mode and applying 0 A to 3.25 A for full-power test). [Figure 10](#) shows the output voltage transient when a full load-step change is applied and also when the load is turned off. Less than 1 V overshoot and undershoot is observed in a full load-step change.

**Power down:**

To power off the adapter, simply turn off the AC source. Because the DC bus has no bleeder resistor, the DC bus will remain energized if the adapter is turned off in no-load condition; therefore, we suggest turning off the AC source while the load is connected with less than 1 W load. This will de-energize the DC bus.

**Attention:** *This evaluation board does not have bleeder resistors, so the DC bus might remain energized. To avoid electric shock and discharge the DC bus, always turn off the source when the DC load is applied.*

*Do not touch any exposed area on the PCB even when the hardware is not operating.*

*If the LED (D5) is off, it does not indicate that the DC bus is discharged. The controller will be off when the voltage is above 50 V and below 75 V, and touching the hardware can cause electric shock.*

Setup and use

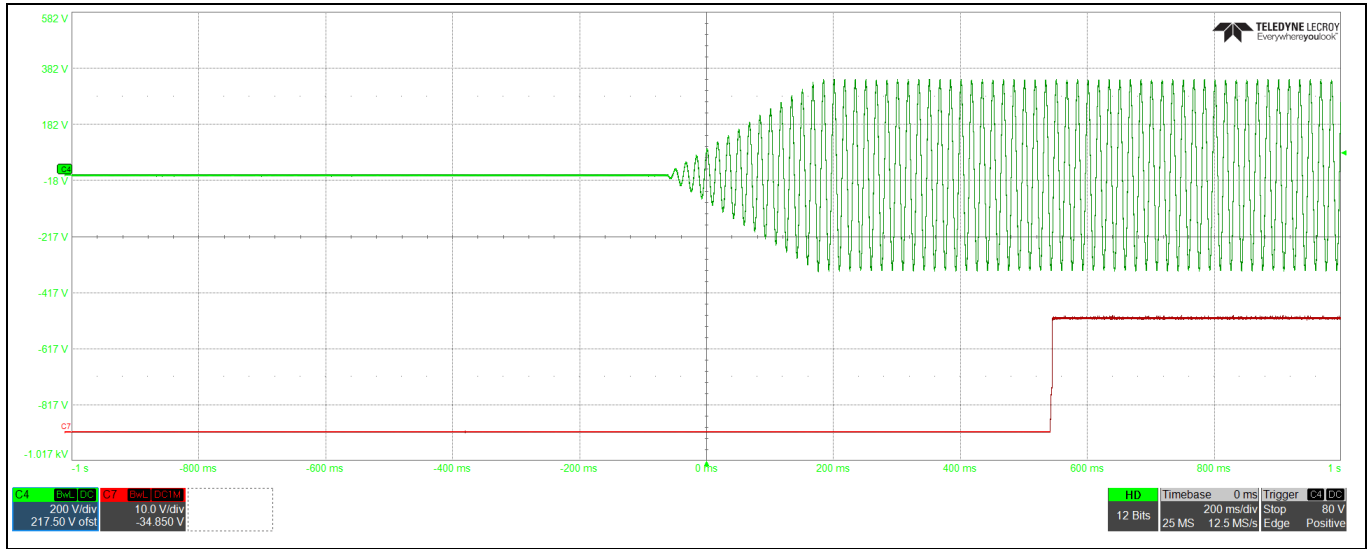


Figure 9 DC output start-up transient with 240 V AC input (Ch4: AC input, Ch7: DC output)

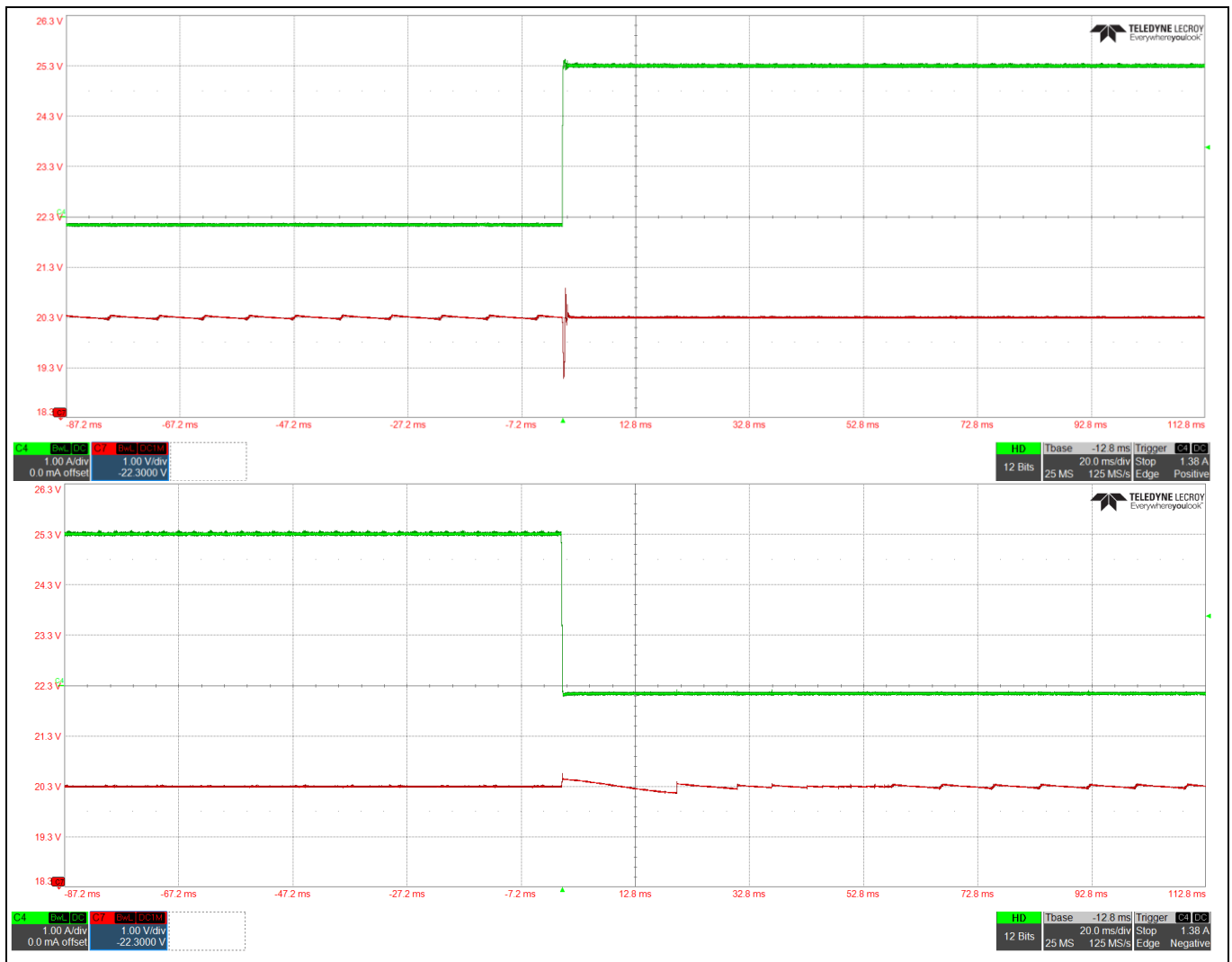



Figure 10 DC output transient with full load-step change under 240 V AC input (Ch4: DC output load current, Ch7: DC output with 20 V offset)

Setup and use

### 3.4 Full-power test

After power-up at no load, different loads (0~3.25 A) can be applied. Note that the temperature of the set-up will rise depending on the load, and the efficiency measurement will be most accurate when the hardware has reached its steady-state thermal condition (transformer core has minimal loss at 70°C to 90°C). We suggest at least 30 minutes' running time to capture any efficiency data. The electrical signals can be observed immediately on the oscilloscope. **Figure 11** shows some of the waveforms captured at full power with 240 V AC input voltage.

In this condition the adapter operates at full ZVS condition at around 300 kHz. Because the current probes used here are Rogowski coil type (AC), the DC offsets are eliminated by the current probes. The active clamp resonance can be observed on the transformer secondary current when the low-side pulse-width modulation signal is off.

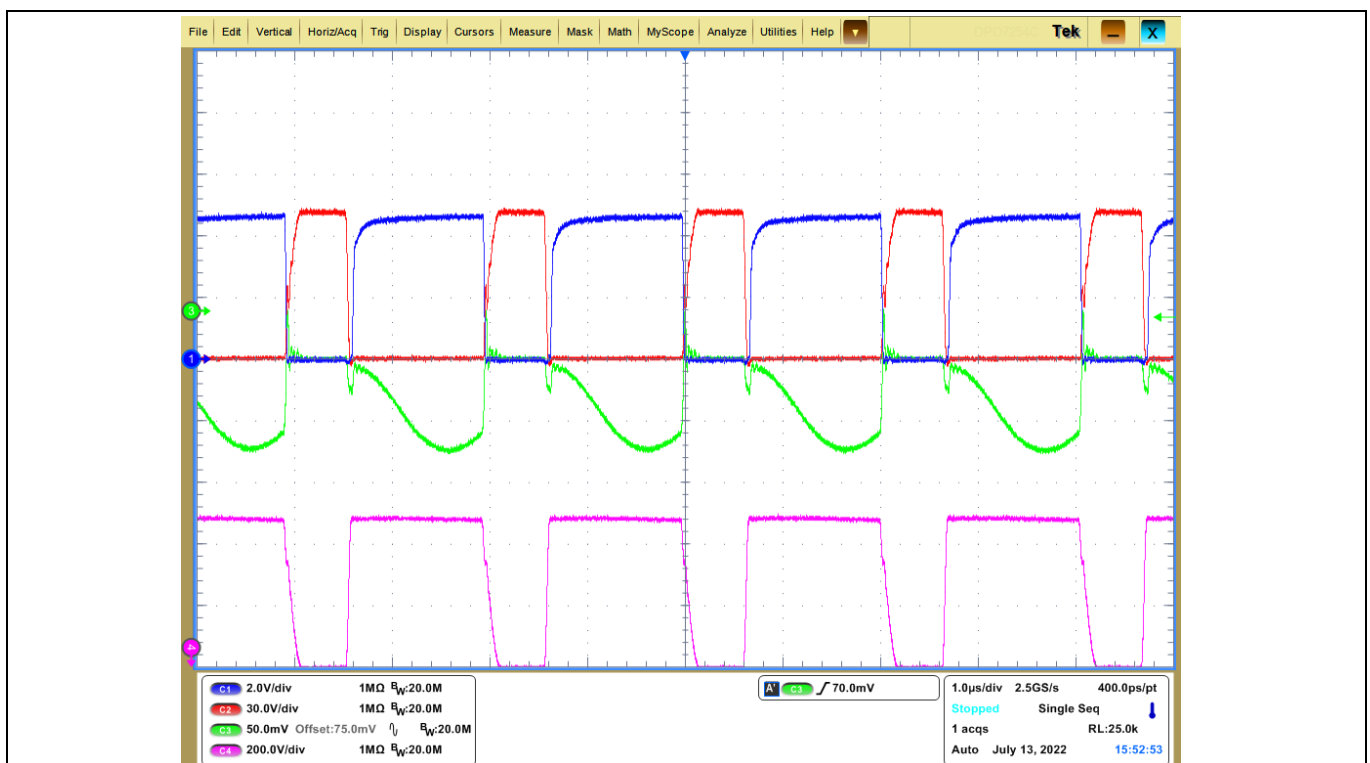

**Figure 11** ACF waveforms at full load and 240 V AC input (Ch1: SR gate voltage, SR drain-source voltage, Ch3: SR drain current (10mV/A) Ch4: Primary switching point)

**Figure 12** shows the waveforms with 90 V AC and 120 V AC input. This evaluation board is tuned to operate at ZVS in all voltage ranges from 55 percent to full-power level. Note that increasing the input voltage increases the frequency. **Figure 13** shows the waveforms with 240 V AC input and different load conditions. Below 55 percent load the adapter operation mode changes to burst mode (the hysteresis to enter and exit burst mode might be different for each of the tested units depending on component tolerances).

Setup and use



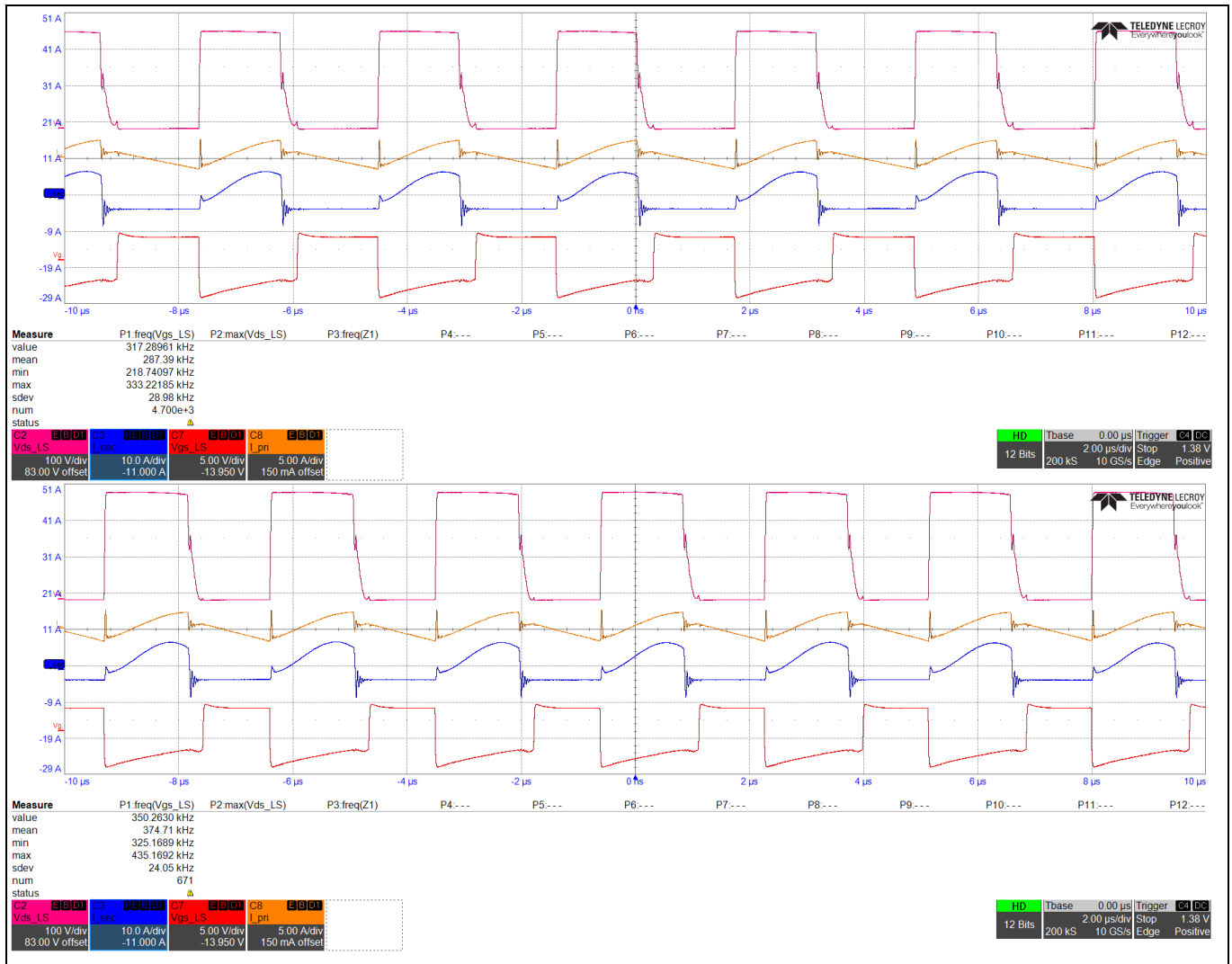


Figure 12 ACF waveforms at full load with 90 V AC (left/ $F_{sw} = 317$  kHz) and 120 V AC (right/ $F_{sw} = 350$  kHz) (Ch8: transformer primary current 5 A/div, Ch3: transformer secondary current 10 A/div, Ch2/Ch7: low-side GaN V<sub>DS</sub>/PWM)

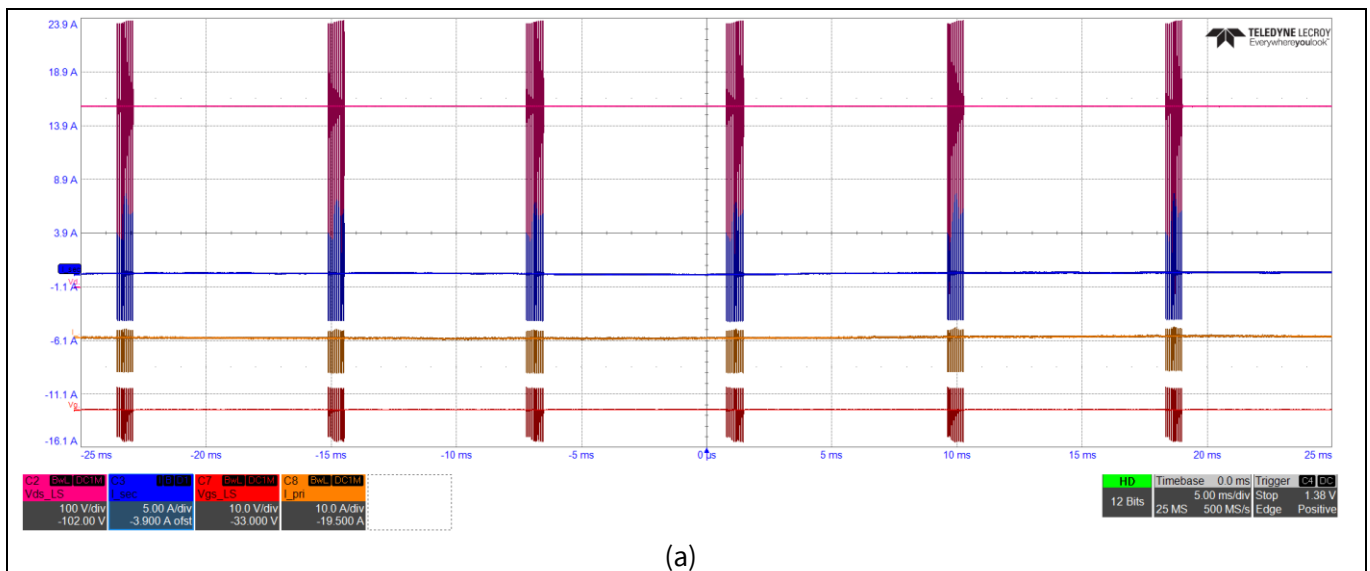


(a)

### Setup and use

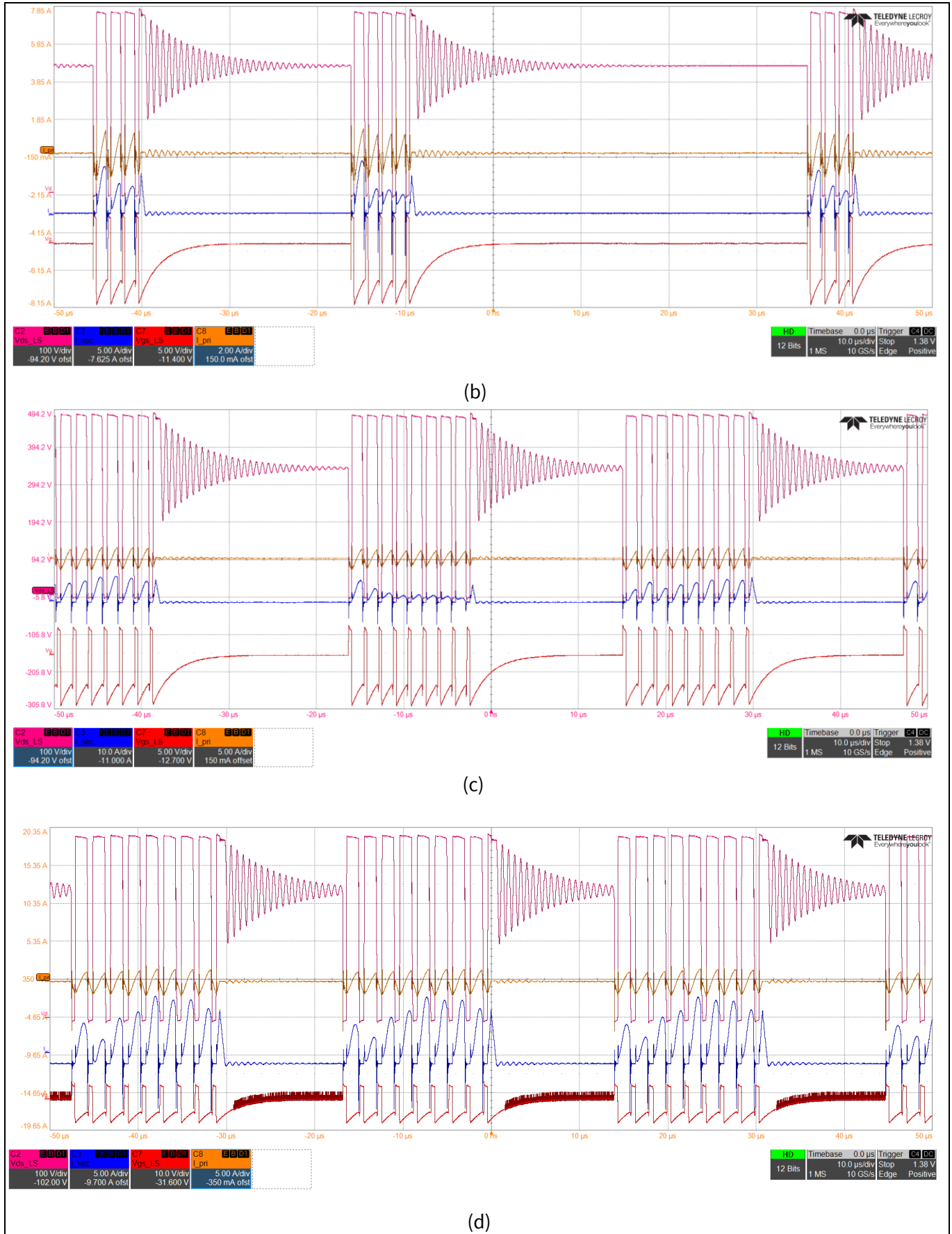

Setup and use

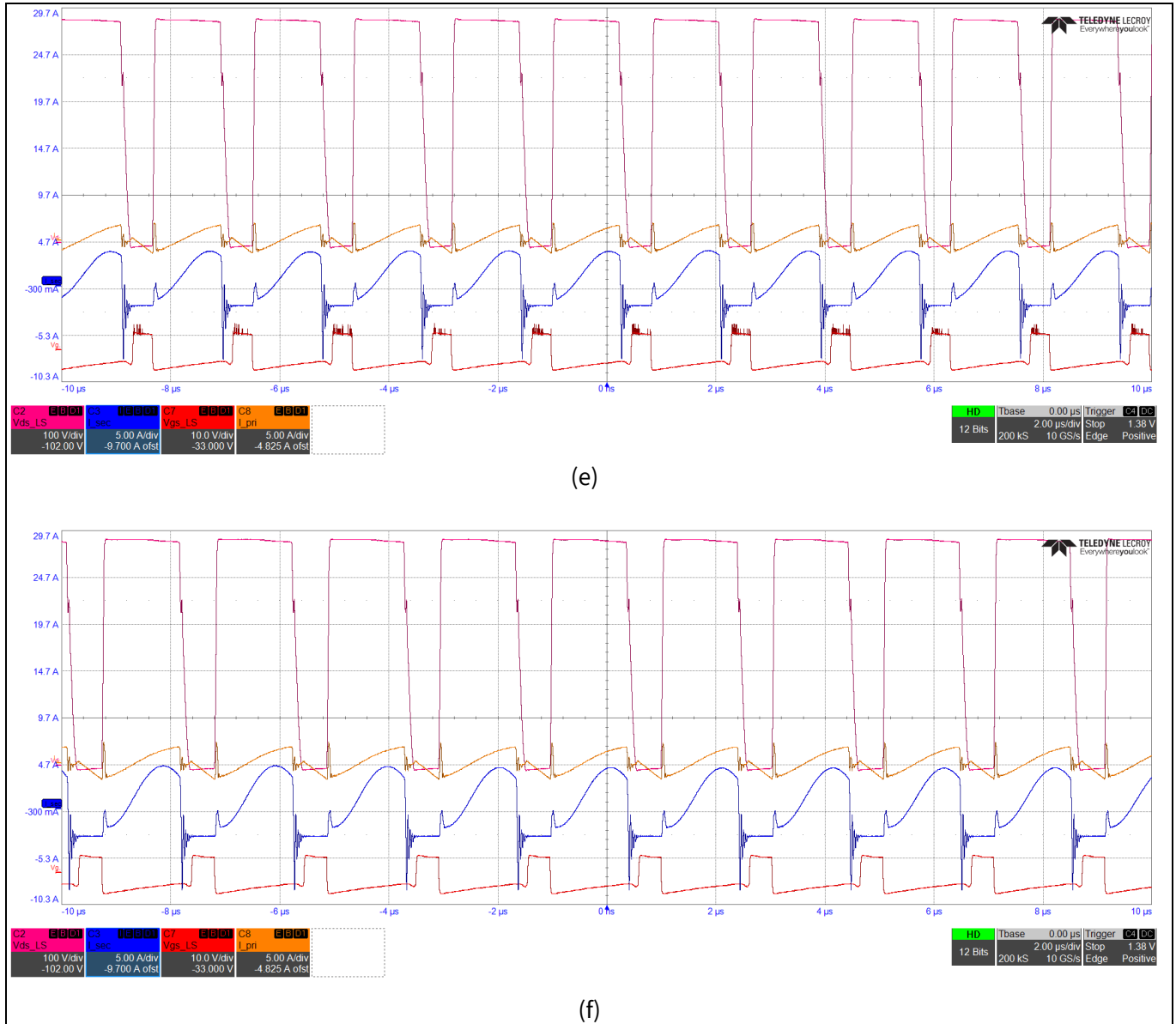

**Figure 13** ACF waveforms operating under 240 V AC input and different load conditions: (a) no load, (b) 10 percent load, (c) 25 percent load, (d) 50 percent load, (e) 75 percent load and (f) 100 percent load (Ch8: transformer primary current , Ch3: transformer secondary current , Ch2/Ch7: low-side GaN  $V_{DS}$ /PWM)

### 3.5 Efficiency performance

Efficiency of the evaluation board is measured with various load and input voltage conditions. [Table 3](#) and [Table 4](#) show the results with 120 V AC and 240 V AC input voltages, respectively. [Figure 14](#) shows the efficiency curves.




Setup and use

**Table 3 Efficiency performance with 120 V AC supply**

V <sub>IN</sub> (AC)	P <sub>OUT</sub> (W)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (%)	Efficiency (%)	Four-point average efficiency	Full-load switching frequency
120	65.246	20.31	3.2125	100	93.182	91.566	350kHz
120	52.81	20.31	2.6	75	92.91		-
120	33.012	20.31	1.6254	50	91.93		-
120	19.814	20.31	0.9756	25	91.143		-
120	6.6231	20.31	0.3261	10	88.663	-	-

**Table 4 Efficiency performance with 240 V AC supply**

V <sub>IN</sub> (AC)	P <sub>OUT</sub> (W)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (%)	Efficiency (%)	Four-point average efficiency	Full-load switching frequency
240	65.496	20.31	3.2248	100	92.312	88.56	477 kHz
240	52.82	20.31	2.6007	75	91.51		-
240	33	20.31	1.6247	50	89.595		-
240	19.804	20.31	0.9751	25	87.244		-
240	6.621	20.31	0.326	10	82.147	-	-

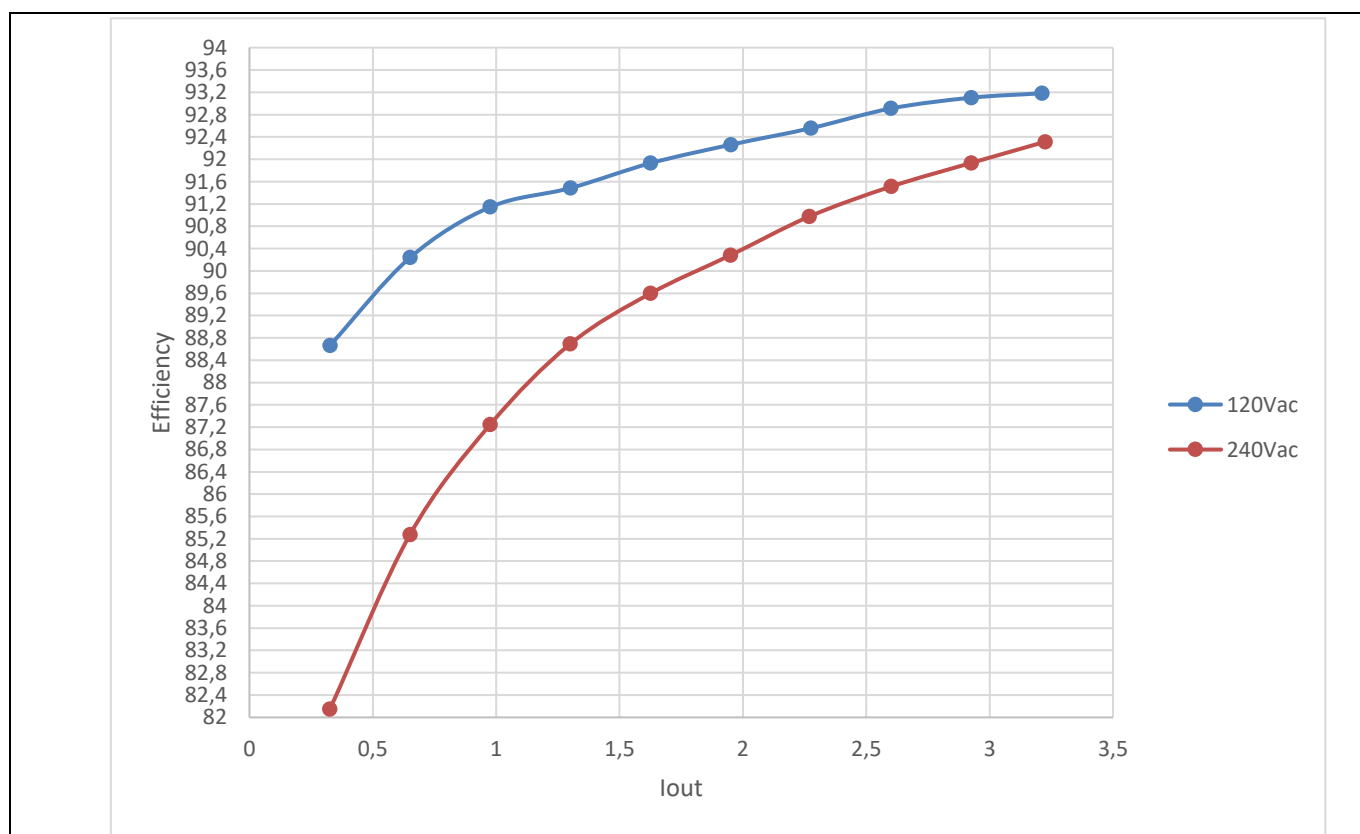

**Figure 14 ACF evaluation board efficiency curve under different input voltage and load conditions**

Setup and use

### 3.6 Thermal performance

Thermal images of this evaluation board are captured operating at full load and different input AC voltages. **Figure 15** shows the thermal image of the unit under test with low-line 90 V AC input and operating at full power. Due to the higher input current at low-line condition, the AC input section (AC rectifier) shows a higher temperature on the hardware. **Figure 16** and **Figure 17** show the thermal images in 120 V AC and 240 V AC input voltages, respectively.

In high-line condition (240 V AC), due to the higher switching frequency, the transformer core loss increases and operates at a high temperature (the transformer has a rated temperature of 120°C). Without any active cooling solution in all cases the CoolGaN™ IPS chipset operates around 70°C. In high-line operating condition (240 V AC) the transformer loss and SR FET loss are high due to the higher switching frequency; meanwhile, in the low-line conditions, the conduction loss in the AC rectifier is dominant.

These thermal images show that all the components run at a safe temperature with a significant safety margin.

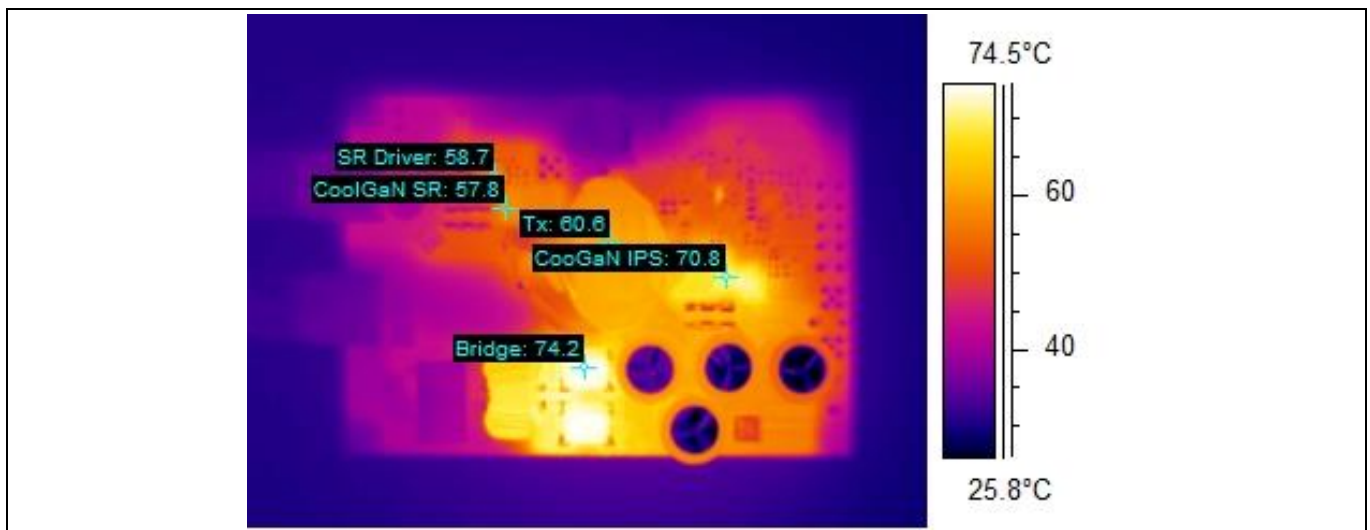


Figure 15 Thermal image of the Full GaN ACF EVB at full power with 90 V AC input voltage

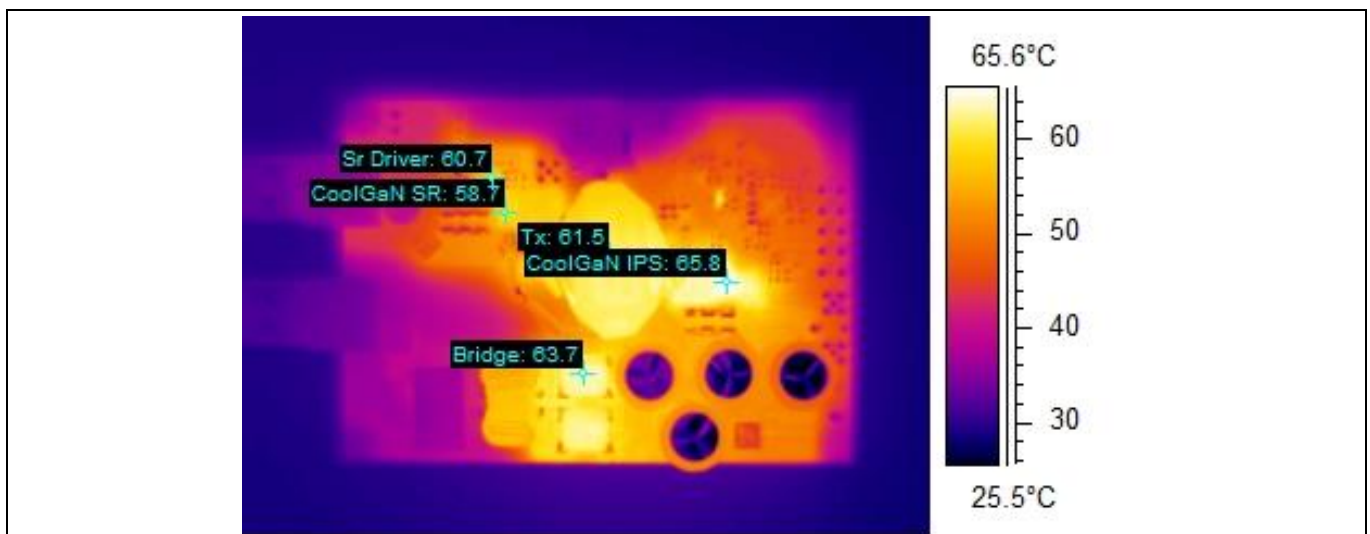


Figure 16 Thermal image of the Full GaN ACF EVB at full power with 120 V AC input voltage

Setup and use

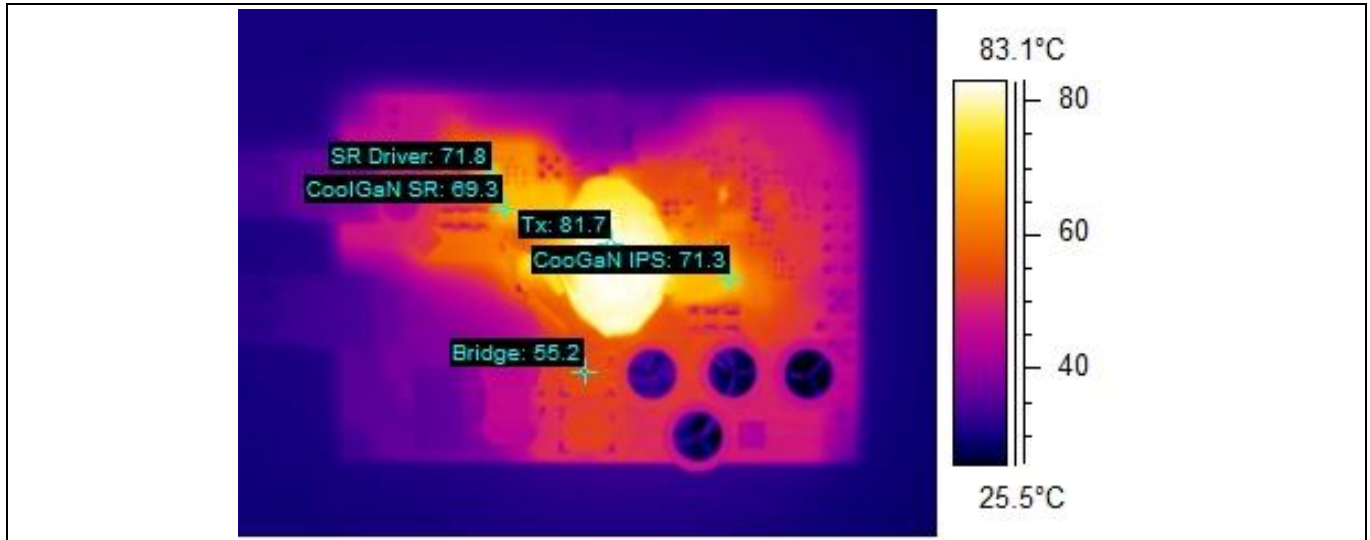


Figure 17 Thermal image of the ACF evaluation board at full power with 240 V AC input voltage

PCB layout

## 4 PCB layout

The evaluation board is 1.0 mm thick, with four layers – 70  $\mu\text{m}$  thick copper on the outer layers, and 35  $\mu\text{m}$  on the middle layers. The layers are shown from [Figure 18](#) to [Figure 21](#).

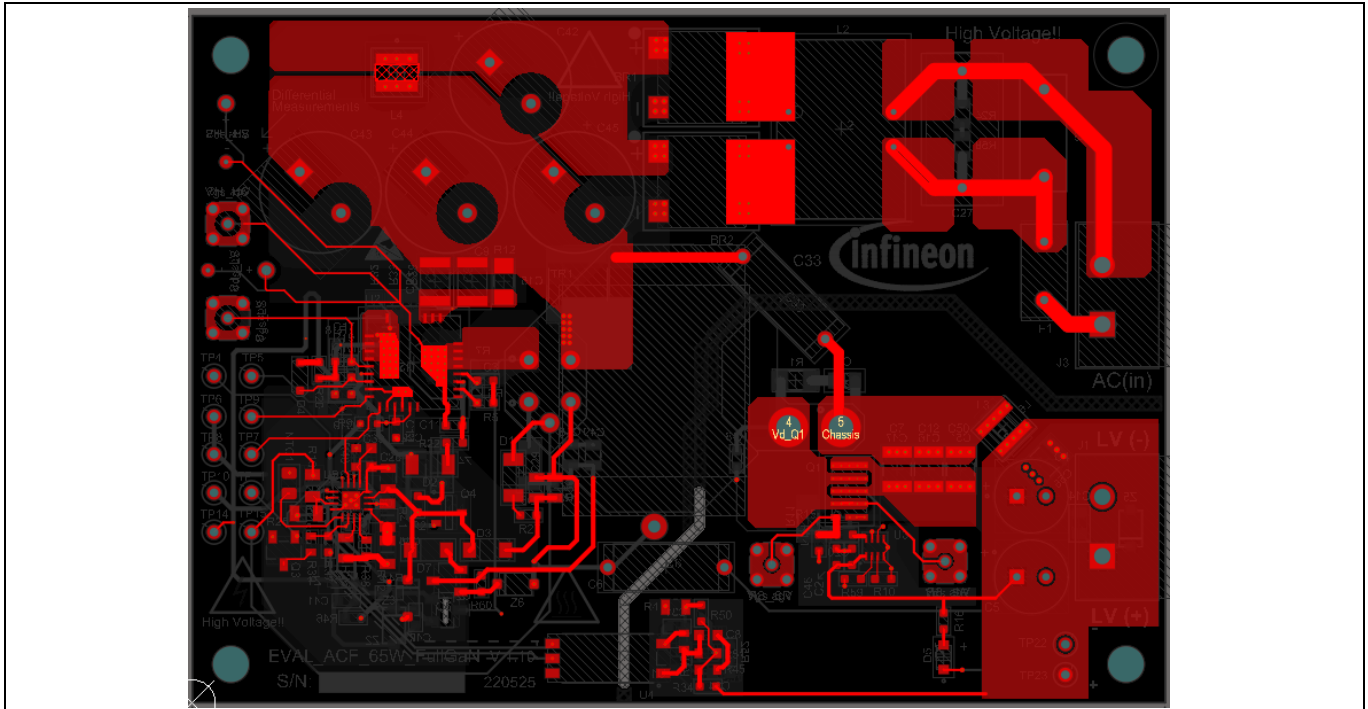


Figure 18 Top copper layer

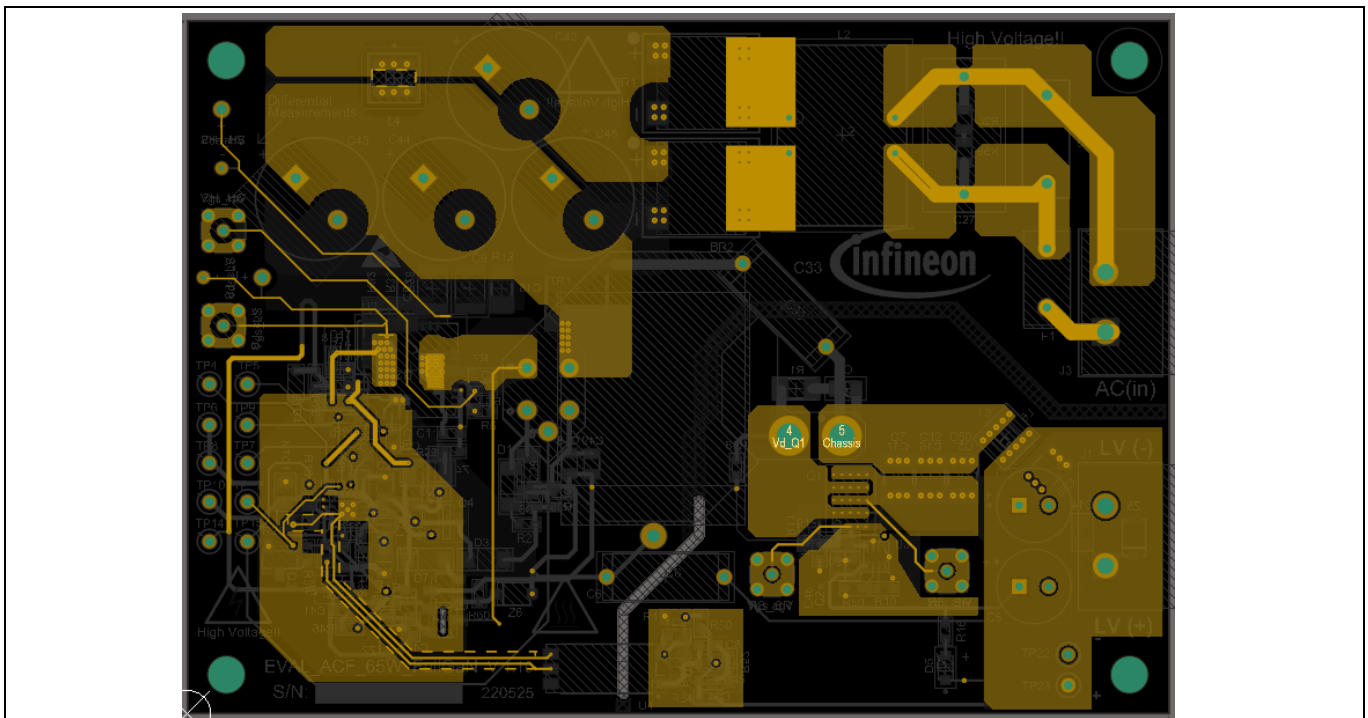


Figure 19 Upper middle copper layer

PCB layout

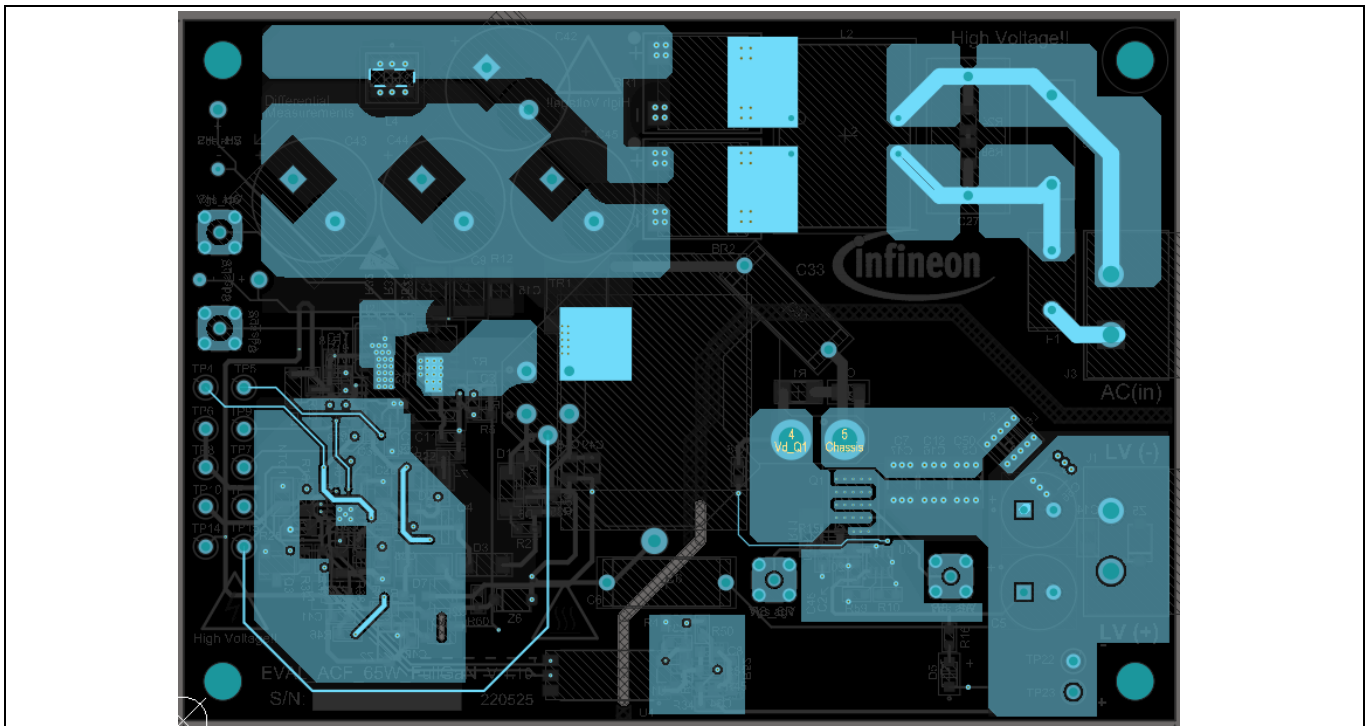


Figure 20 Lower middle copper layer

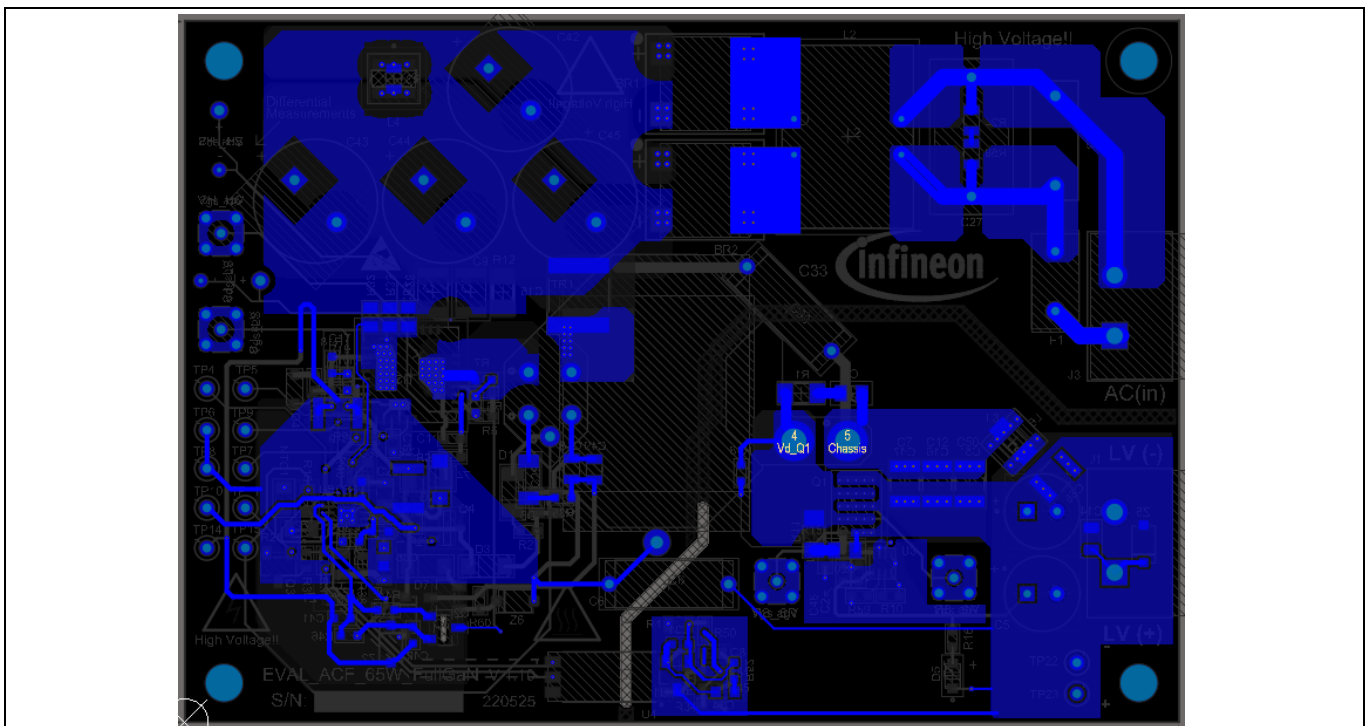


Figure 21 Bottom copper layer



Bill of materials

## 5 Bill of materials

Table 5 describes all of the components on the PCB.

**Table 5 PCB bill of materials**

Designator	Description	Vendor	Quantity
BR1, BR2	YBS bridge rectifier, single-phase 600 V 3 A	YBS3005GTR-ND	2
C1	Ceramic capacitor 220 pF 200 V COG/NPO 0805	GRM21A5C2D221JW01	1
C2, C11, C13, C35, C37	Ceramic capacitor 100 nF 35 V X7R 0603	GMK107B7104KAHT	5
C3, C17	Ceramic capacitor 1.5 nF 25 V COG/NPO 0603	C0603C152J3GAC7867	2
C4	Aishi aluminum solid electrolytic capacitor 470 $\mu$ F 25 V PZ series (6.3x 14mm)	SPZ1EM471E14O00RAXXX	1
C6, C33	Safety capacitors 10x9x4mm 250 V AC 2200 pF	DE1E3RA222MA4BN01F	2
C7, C12, C16, C47, C50, C51, C56	Ceramic capacitor 10 $\mu$ F 50 V X7R 1210	12105C106K4T2A	7
C42, C43, C44, C45	Aishi aluminum capacitor 400 V 27 $\mu$ F	EWH2GM270G200T	4
C8	Ceramic capacitor 33 nF 25 V X7R 0603	GRM188R71E333KA01	1
C9, C23	Ceramic capacitor 220 nF 200 V X7R 1210	GRM32DR72D224KW01	2
C10	Ceramic capacitor 22 nF 16 V X7R 0603	C0603C223K4RACTU	1
C14	Ceramic capacitor 100 nF 50 V X7R 0805	C0805C104K5RACTU	1
C15	Ceramic capacitor 1 $\mu$ F 630 V X7T 2J-Lead	CKG57NX7T2J105M500JH	1
C19, C22	Ceramic capacitor 10 $\mu$ F 50 V X7R 1210	GRM32ER71H106KA12	2
C20	Ceramic capacitor 330 pF 200 V COG/NPO 0805	GRM21A5C2D331JW01	1
C27	Film capacitor 0.22 $\mu$ F 275V Polypropylene Metallized Radial	890324023028	1
C28	Ceramic capacitor 22 $\mu$ F 35 V X5R 0805	C2012X5R1V226M125AC	1
C29, C49	Ceramic capacitor 1 $\mu$ F 35 V X7R 0805	GRM219R7YA105KA12D	2
C30, C48	Ceramic capacitor 22 $\mu$ F 35 V X5R 0805	C2012X5R1V226M125AC	2
C34	Ceramic capacitor 1 nF 25 V X7R 0603	GRM188R71E102JA01	1



# Full GaN 65 W active clamp flyback evaluation board

## EVAL\_ACF\_65W\_FULLGAN



### Bill of materials

C36	Ceramic capacitor 100 pF 25 V COG/NPO 0603	C0603C101K3GACTU	1
C38	Ceramic capacitor 330 pF 50 V X7R 0603	GRM188R71H331KA01	1
C39	Ceramic capacitor 10 pF 50 V COG/NPO 0603	C0603C100K5GACAUTOS	1
C40	Ceramic capacitor 2.2 nF 25 V COG/NPO 0603	C0603C222J3GACTU	1
C41	Ceramic capacitor 22 pF 50 V X7R 0603	C0603C220K5RACTU	1
C46	Ceramic capacitor 1 µF 25 V X7R 0603	GCJ188R71E105KA01D	1
D1, D6	General-purpose diode 600 V 1 A SOD-123H	CSFMT108-HF	2
D2	General-purpose diode 600 V 1 A SMA	ES1JAF	1
D3 , D7	General-purpose diode 200 V 200m A SOD-123	MMSD103T1G	2
D4	Diode Schottky 30V 200mA SOD- 323	BAT54HT1G	1
D5	LED GREEN CLEAR 0805 SMD	150080VS75000	1
F1	Board-mounted fuse 2.5 A 250 V AC radial	39212500000	1
J1, J3	Terminal block HDR two-position 90 degrees 5.08 mm	1748167	2
L2	CMC through-hole 14 mH 94 MΩ	P5320	1
L3	Shielded Molded Inductor 1uH 15 MΩ	74438356010	1
L4	Inductor 4.7uH 3.9A 15 MΩ	74438357047	1
L6	Inductor 680nH 190mA 938 MΩ	LQH31MNR68K03	1
NTC1	Thermistor NTC 50 kΩ 3890k 0805	NTHS0805N01N5002JE	1
Q1	100 V CoolGaN™ SG HEMT	ICQ800NLS	1
Q2	MOSFET N-channel 600 V 0.021 A SOT-23	BSS126H6906XTSA1CT-ND	1
Q3	MOSFET N-channel 60 V 115 mA SOT-23-3	2N7002-FDICT-ND	1
Q4, Q5	Transistor NPN 300 V 0.5 A SOT- 23-3	MMBTA42-FDICT-ND	2
R1, R11	Resistor SMD 10 Ω 5% 1/4 W 1206	ERJ-8GEYJ100V	2
R2	Resistor SMD 120 kΩ 1% 1/10 W 0603	ERJ-3EKF1203V	1
R3	Resistor SMD 10 kΩ 1% 1/8 W 0805	ERJ-6ENF1002V	1
R4	Resistor SMD 21kΩ 1% 1/8 W 0805	ERJ-6ENF2102V	1
R5, R19	Resistor SMD 47Ω 1% 1/10 W 0603	ERJ-3EKF47R0V	2
R6, R17	Resistor SMD 1.5 kΩ 1% 1/10 W 0603	ERJ-3EKF1501V	2
R7, R14, R18, R52	Resistor SMD 22 kΩ 1% 1/10 W 0603	ERJ-3EKF2202V	4

# Full GaN 65 W active clamp flyback evaluation board

## EVAL\_ACF\_65W\_FULLGAN



### Bill of materials

R9	Resistor SMD 820 $\Omega$ 1% 1/10 W 0603	ERJ-3EKF8200V	1
R10, R59	Resistor SMD 0 $\Omega$ 1% 1/10 W 0603	ERJ-3GEY0R00V	2
R12	Resistor SMD 2.2 M $\Omega$ 5% 1/4 W 1206	ERJ-8GEYJ225V	1
R13	Resistor SMD 52.3 k $\Omega$ 1% 1/8 W 0805	ERJ6ENF5232V	1
R15	Resistor SMD 1 $\Omega$ 1% 1/10 W 0603	ERJ-3RQF1R0V	1
R16	Resistor SMD 10 k $\Omega$ 1% 1/10 W 0603	ERJ-3EKF1002V	1
R20	Resistor SMD 3.3 $\Omega$ 1% 1/10 W 0603	ERJ-3RQF3R3V	1
R22 , R27, R35	Resistor SMD 2.2 $\Omega$ 1% 1/10 W 0603	ERJ-3RQF2R2V	3
R23	Varistor 430V 1.2kA Disc 7mm	B72207S0271K101	1
R24, R58	Resistor SMD 1 M $\Omega$ 5% 1/2 W 0805	ERJ-P06J105V	2
R25	Resistor SMD 12.1 k $\Omega$ 1% 1/8 W 0805	CRCW080512K1FK	1
R32, R33	Resistor 0.56 $\Omega$ 1% 1/3 W 0805	RL1220S-R56-F	2
R34	Resistor SMD 0 $\Omega$ 1% 1/10 W 0603	RC0603FR-070RL	1
R36	Resistor SMD 280 k $\Omega$ 1% 1/8 W 0805	ERJ-6ENF2803V	1
R37	Resistor SMD 20 k $\Omega$ 1% 1/10 W 0603	ERJ-3EKF2002V	1
R38	Resistor SMD 56 k $\Omega$ 1% 1/10 W 0603	CRCW060356K0FK	1
R39	Resistor SMD 560 k $\Omega$ 1% 1/10 W 0603	CRCW0603560KFK	1
R40	Resistor SMD 2.2 k $\Omega$ 1% 1/10 W 0603	RC0603FR-072K2L	1
R41	Resistor SMD 560 k $\Omega$ 1% 1/8 W 0805	CRCW0805560KFK	1
R42	Resistor SMD 100 k $\Omega$ 1% 1/8 W 0805	CRCW0805100KFKEA	1
R44	Resistor SMD 120 $\Omega$ 1% 1/10 W 0603	ERJ-3EKF1200V	1
R45	Resistor SMD 75 $\Omega$ 1% 1/10 W 0603	RC0603FR-0775RL	1
R46	Resistor SMD 1 M $\Omega$ 1% 1/10 W 0603	ERJ-3EKF1004V	1
R47	Resistor SMD 6.8 k $\Omega$ 1% 1/10 W 0603	CRCW06036K80FK	1
R48	Resistor SMD 10 $\Omega$ 1% 1/10 W 0603	ERJ-3EKF10R0V	1
R50	Resistor SMD 150 k $\Omega$ 1% 1/10 W 0603	ERJ-3EKF1503V	1
R51	Resistor SMD 1 k $\Omega$ 1% 1/10 W 0603	RC0603FR-071KL	1
R60	Resistor SMD 75 k $\Omega$ 1% 1/10 W 0603	ERJ-3EKF7502V	1
TR1	ACF RM8 65 W transformer 75 $\mu$ H	750841142r00	1

# Full GaN 65 W active clamp flyback evaluation board

## EVAL\_ACF\_65W\_FULLGAN



### Bill of materials

U1	Shunt Voltage Reference IC 2.5V 100mA SOT-23-3	ATL431BQDBZR	1
U2	CoolGaN™ IPS 600 V 200 mΩ	IGI60F2020A1L	1
U4	Vishay TCLT1103 DC input phototransistor output optocoupler SMD five-pin SOP	TCLT1103CT-ND	1
U3	ON Semiconductor NCP43080 SR PWM controller WDFN8 (DRV clamp 4.7 V)	NCP43080AMTTWG	1
U5	Adaptive ZVS Controller UCC28780	UCC28780RTET	1
Z1	TVS Diode Array Series,18V, 45VC	CDSOD323-T18C	1
Z3, Z5	ON Semiconductor SMD Zener diode 25 V 500 mW SOD-123 two- pin	SZMMSZ5253BT1GOSCT-ND	2
Z2	ON Semiconductor Zener diode 22 V 5% 500 mW SMT two-pin SOD-123	SZMMSZ5251BT1GOSCT-ND	1
Z4	Zener Diode 15V 500mW ±5% SOD-123	DDZ9702-7	1
Z6	Zener Diode 15V 500mW ±5% SOD-123	MMSZ4702T1G	1

### References

## References

- [1] Vartanian,R./ Veeredy, D/Medina-Garcia, A: *GaN based Integrated Power Stages (IPS) for Low Power Adapter/Charger Applications*; PCIM Europe digital days 2021; International Exhibition and Conference for Power Electronics, Intelligent Motion, Renewable Energy and Energy Management; 2021, pp. 1–6
- [2] Infineon Technologies AG: *600 V CoolMOS™ PFD7 SJ MOSFET for high power density adapters and motor drive*; [Available online](#)
- [3] Infineon Technologies AG: *ACF 65 W adapter evaluation board with CoolGaN™ IPS half-bridge evaluation board with IGI60F2020A1L*



Revision history

**Revision history**

Document version	Date of release	Description of changes
V 1.0	2023-01-26	Initial release

**Trademarks**

All referenced product or service names and trademarks are the property of their respective owners.

**Edition 2023-01-26**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2023 Infineon Technologies AG.**

**All Rights Reserved.**

**Do you have a question about this document?**

**Email:** [erratum@infineon.com](mailto:erratum@infineon.com)

**Document reference**

**ER\_2201\_PL51\_2204\_105259**

**IMPORTANT NOTICE**

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office ([www.infineon.com](http://www.infineon.com)).

**WARNINGS**

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.