

The Filter Wizard

issue 16: Bruton Charisma: Make those inductors vanish using savvy scaling

Kendall Castor-Perry


I must confess that I just didn't realize how much mess the monkeys would leave in the Monkey House when I let them loose with a few innocent software tools during the development of "[Filter Design Using the Million Monkeys Method](#)". Today's column is the third sequel to that article, which was Filter Wizard #13, and I am still flushing out the little promises that got made in that episode. Maybe those triskaidekaphobics are onto something...

Most recently, you were left hanging by a finger at the end of Filter Wizard #15 ("[Dualling Master: Swap Current and Voltage for Easier Filter Design](#)"). We set out to eliminate the inductors in our LC lowpass filter – and ended up doubling the number! We'll see shortly just how these can be made to disappear in one mathematical stroke. But first, let's talk about impedance scaling. In the text that follows, I'll use w to indicate ω – we'd normally use a lower-case omega but the Web seems to have an aversion to Greek characters in text. I'll also use 2 to mean "squared" – just in case that wasn't obvious...

Our filter uses source and load resistances of 1 ohm. Now, if all the impedances in the network change by the same factor, the voltage transfer function – a dimensionless value which is only ever determined by **ratios** of impedances in a network – is unchanged. So it's easy to scale the filter to make it suit source and load resistances of, for example, 1 kilohm. The impedance of an inductor, $Z=j\omega L$ (I don't have to explain what j is, I hope) is proportional to its inductance, so we just make all the inductor values 1000 times higher. We **reduce** the capacitor values by 1000, because their impedance is **inversely** proportional to their value, $Z=1/(j\omega C)$.

The scaled circuit is shown in figure 1, ready for simulation. The cutoff frequency is unchanged from the original $1/(2\pi)$ Hz; one way of convincing yourself of that is that the **product** of any inductor and capacitor pair is unchanged by the impedance scaling we just did.

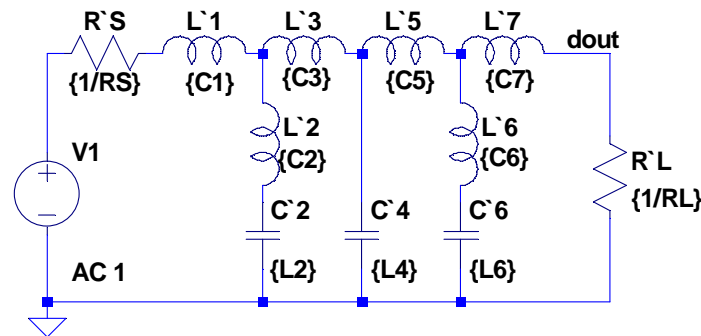The values are even less practical than they were before. We've taken inductor L_3 , for instance, from its previous already-enormous 1.621 H to a rather bizarre 1.621 kH – yes, that's kilo-Henry, not kilo-Hertz with a missing z . I'll forgive those inductor-fearing readers for feeling that things are just getting worse and worse! But just hold on for a moment longer.



```
.param C1 0.760578070494466 * 1k .ac lin 200 1e-6 1
.param C3 1.62145153 * 1k
.param C5 1.510454354 * 1k
.param C7 0.682696105 * 1k
.param L2 1.422990253 / 1k
.param L4 1.967379154 / 1k
.param L6 1.390711149 / 1k
.param C2 0.091512516 * 1k
.param C6 0.163122375 * 1k
.param RS 1 / 1k
.param RL 1 / 1k
```

RS and RL are divided by 1k to make the actual source and load resistors increase by 1000x)

figure 1: as figure 3b from “Dualling Master”, impedance-scaled by 1000x

In 1968, Leonard Bruton, working at the University of Newcastle in the UK, introduced a simple yet beautiful technique to the filter design world. It is sometimes known as the Bruton Transform, though it’s not a functional transform but ‘just’ a scaling. It’s one of the most underrated insights in all of practical network theory. He realized that you could scale the impedance of a component by a factor that’s not just a simple constant, and that interesting things could happen if you chose that factor carefully [reference 1].

Bruton asked: what would happen if I scale the impedance of every element in this network by a factor of $1/(j\omega)$. Let’s investigate. If I multiply a resistor R by an impedance scaling factor $1/(j\omega)$, I get a new impedance of $Z' = R/(j\omega)$. But hang on – that’s just the impedance of a **capacitor** with a value of $C' = 1/R$. By doing this scaling, we’ve made an impedance that can be realized by a physical capacitor. We’ve “turned the resistor into a capacitor”.

What happens when we scale the inductor? Its new impedance is $Z' = j\omega L/(j\omega)$, i.e. $Z = L$. In other words, it’s a real, frequency-independent constant value L . This can be delivered by a resistor of value $R' = L$. We’ve “turned the inductor into a resistor”. Isn’t that just the most wonderful thing? There we were, wondering what we were going to do with these six inductors, and at a stroke we just managed to replace them with six resistors. Result!

Just one more thing to do; let’s scale those capacitors. The new impedance is $Z' = 1/(j\omega C)$ times $1/(j\omega)$, and since we all know that $j*j = -1$, this can be written as $Z' = -1/(C\omega^2)$ and that’s the impedance of an, er, well what, exactly?

Well, we can see that the impedance is real (there's no j there), it's negative, and it depends on frequency. Imaginatively, this new element is sometimes called a Frequency-Dependent Negative Resistor, or FDNR for short. In the golden days of analogue filter theory it was also called a "supercapacitor", but that was before the multi-Farad barrier supercapacitor types used for memory backup were introduced. I like the name "D-element", with a value of D , for which the impedance is $Z = -1/(D\omega^2)$. So we have "turned the capacitor into a D-element" whose value is the same as the original capacitor's.

The commonly-used symbol for the D-element is like a capacitor but with four (occasionally three) bars instead of two, and pretty easy to draw with the symbol editor in your favourite simulator (and if it isn't, then why aren't you using **my** favourite simulator?). Figure 2 shows our original 1 ohm filter on the left, and the Bruton-transformed network on the right. No frequency response plot is needed – they are identical.

It's straightforward to create a suitable D-element subcircuit for simulation from a few controlled sources and impedances, but I've not shown it here. Try working out how to do it yourself. If you get stuck, contact me (filterwizard@cypress.com) or send me a LinkedIn message.

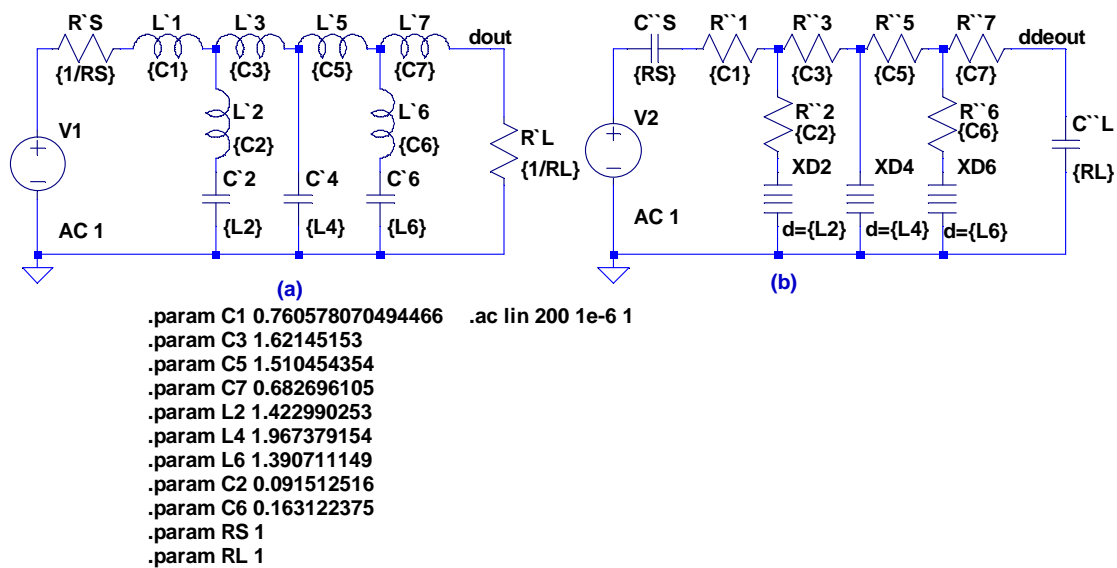


figure 2: our original filter, before and after Brutonization

Now, before you head to the Digi-Key website to order some of these, muttering under your breath that this is another darned class of components to enter into your inventory system, you need to know something. And that is, that **the D-element isn't actually a physically realizable passive component**. It needs a source of energy – can you see why this must be so?

But, although the D-element is not a component as we normally use the term, we can **synthesize** it nicely using regular components – particularly when one end of it is connected to ground. And (though you might think this a bit underwhelming) that’s the main prize we won with all that work in this column and the previous one. We started with three floating inductors that would be a pig to synthesize electronically. We did some dualling and ended up with six still-floating inductors. Then we Brutonized the circuit and ended up back with three D-elements – except they are connected to ground, enabling us to implement them to a high standard.

The same network equations continue to apply to this network, except that the variables now are not voltage and current, but voltage and “Bruton-transformed current”. We’re not transmitting power through this network any more, but this network is ‘similar’ (in the sense of similar triangles) to our original network, at any frequency. So it still has the same fantastic low sensitivity to component tolerance that our original network has.

One more step towards reality for us: let’s design around a more interesting cutoff frequency. How about the very popular 1kHz, sir? Let’s look at how to frequency-scale our CRD network. Well, we want our next filter to ‘do’ the same thing at a frequency f as the last one ‘does’ at $f/(2\pi \cdot 1000)$, or $f/6283$. As before, we arm ourselves with the impedance expressions of the three classes of components. The capacitor, resistor and D-elements have impedances of $1/(j\omega C)$, R and $-1/(D\omega^2)$ respectively. So, by inspection, we can see that we’ll have to **reduce** the capacitor values by a factor of 6283 and **reduce** the D-element values by (6283^2) . We leave the resistor values alone. In figure 3, the calculations are done in the expressions for the capacitor and D-element values. Figure 4 shows the frequency response. The work of the Million Monkeys is now available at a much more useful frequency.

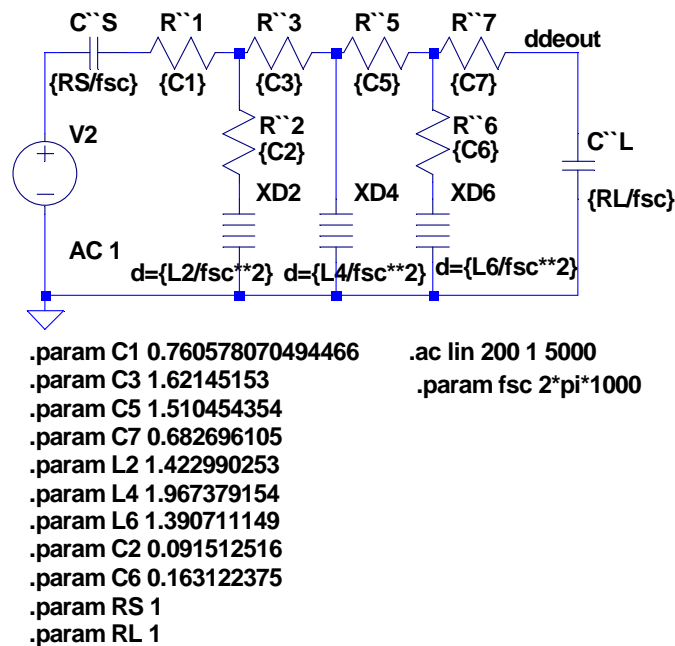


figure 3: frequency scaling, up from $1/(2\pi)$ Hz to 1kHz

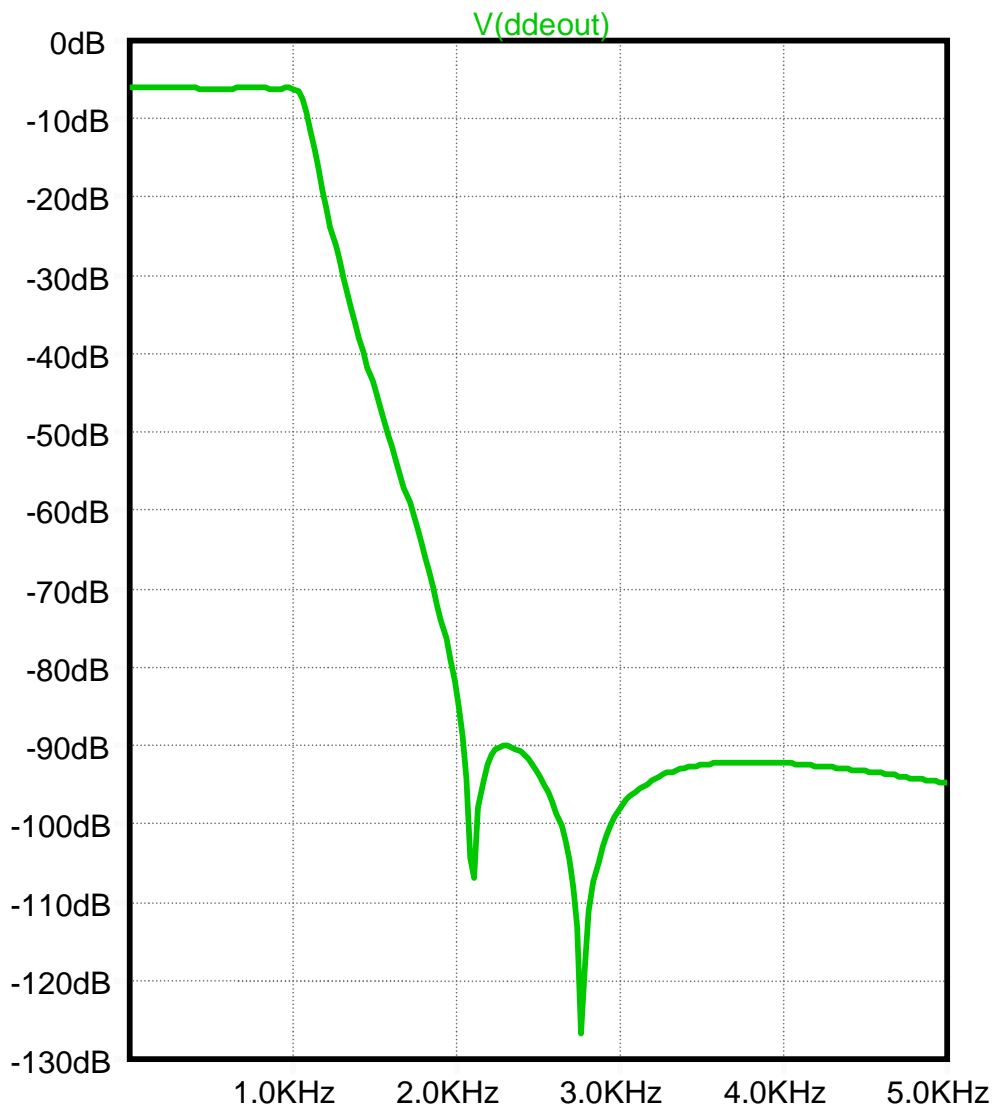


figure 4: frequency response of figure 3's frequency-scaled filter

What do we think of the component values? Calculating out those expressions, capacitors C^S and C^L have a value of $1/6283$ F which is 159.1 μ F. The series value of all the resistors “across the top” is only about 4.5 ohms. That doesn't look easy to drive with standard op-amp circuitry; we'd need an audio power amplifier to push a signal through this. It's not surprising, because we knew that our source and load capacitors were going to have an impedance of 1 ohm at 1kHz (can you see why this is?).

So let's also do some impedance scaling, we know how to do that. To make the circuit opamp-compatible, the resistor values are going to have to go up, and the capacitors will get lower in value to match. What about the D-elements? They are going to go down too, since their impedance is inversely proportional to the D value.

We'd get reasonable impedance values if we scaled by something like 10000, but actually, let's use a value that makes the source and load capacitors a preferred value. 15915 does the trick because it takes those capacitors to 10 nF, which is pretty darned standard.

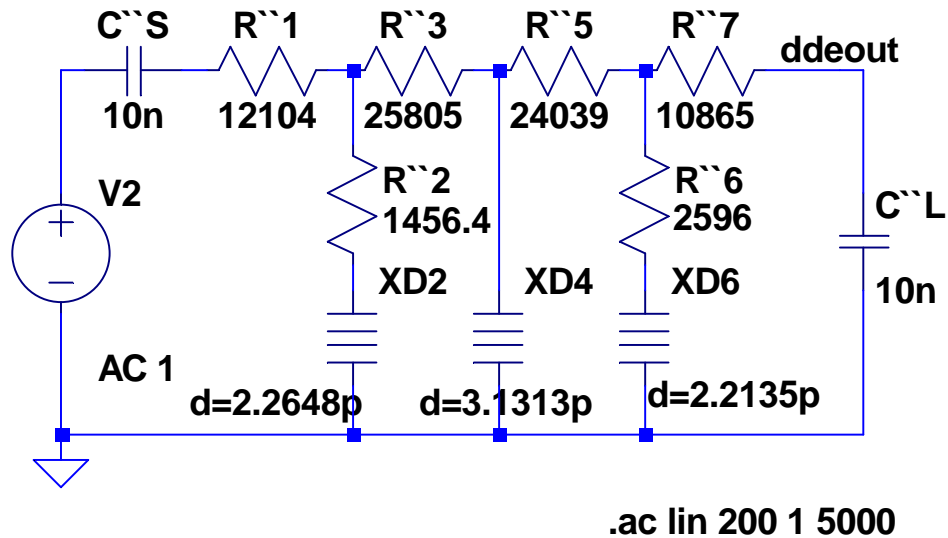


figure 5: as figure 3, impedance scaled to make the caps 10nF

The resulting network, this time with actual values, is shown in figure 5. Trust me, the frequency response plot is indistinguishable from figure 4. And, do you know what? We're out of column space again, and you still haven't seen a single op-amp! Don't worry, I promise I'll rectify that omission soon, when we look at the classic circuit for implementing this filter actively. Meanwhile, happy de-inductoring! – Kendall

[1] L. T. Bruton, "Frequency selectivity using positive impedance converter-type networks". Proc. IEEE (Letters), vol. 56, pp 1378-1379, August 1968