



News

Access to
9,2 Million+
Products
Online



electronics europe News

europe

GaN
EiceDRIVER™

Driving GaN made easy by Infineon



Driving GaN made easy by Infineon

By Dr. Diogo Varajao, Senior System Application Engineer, Infineon Technologies AG
Bernhard Zojer, Principal Concept Engineer, Infineon Technologies Austria AG

CoolGaN™ concept and standard gate drive

Gallium Nitride (GaN) switches on silicon substrates belong to the most promising candidates for next-generation power systems. The combined effort of researchers and manufacturers during the last years has led to mature and reliable devices with some very attractive features when compared with silicon superjunction MOSFETs: zero reverse recovery charge (no intrinsic body diode) and 90 percent lower gate and output charge. This enables operation in hard-switched half-bridge topologies as well as high switching frequency and short dead time. In the high-voltage (600 V) arena, four different GaN switch concepts can be found on the market today. Two of them use the natural, intrinsic GaN/AlGaIn heterojunction transistor with its negative gate threshold voltage, but operate the resulting “normally-on” device in a series connection with a low-voltage silicon MOSFET. In the classic cascode configuration the MOSFET is switched, whereas direct-driven concepts control the GaN gate; this requires a negative gate drive voltage. The alternate approaches use a p-doped GaN gate to shift the threshold voltage to positive values. If this gate is contacted through a Schottky contact, the resulting device is compatible with standard driving, but the gate is highly sensitive to overvoltages, and it is difficult to keep the optimum drive voltage over current and temperature variations. So it is the final concept, combining a pGaN gate with an ohmic contact that Infineon chose for its CoolGaN™ 600 V e-mode HEMTs [1].

In the equivalent circuit of **Figure 1a** and the gate charge curve **Figure 1b** the main differences with respect to a Si MOSFET are highlighted.

- The ohmic pGaN gate can be modeled as a diode between gate and source with a threshold voltage V_F of about 3.5 V. The best way to drive such a gate is by applying a continuous small current of a few mA in the “on”-state.
- The intrinsic transistor lacks a physical body diode and as a consequence, there is zero reverse recovery charge. In reverse operation S and D interchange their functionality and the transistor conducts, if V_{GD} exceeds the threshold voltage. Any negative V_{GS} adds to the “diode” voltage drop V_{SD} .
- Due to the lateral structure, a certain part of the channel resistance ($\sim 20\%$) is located within the gate loop – if driven by a constant voltage, the effective gate voltage would decrease with current and cause an increase in $R_{DS(on)}$. With the proposed current drive, however, the gate voltage adapts itself to the optimum value.
- All CoolGaN™ switches are operated with a Kelvin source connection SK that eliminates the common source inductance, but on the other hand, requires some input-to-output isolation in the gate driver.

Although the total gate charge is very low (~ 5 nC), a gate drive current up to 1 A is required during the switching transients (**Figure 1d**).

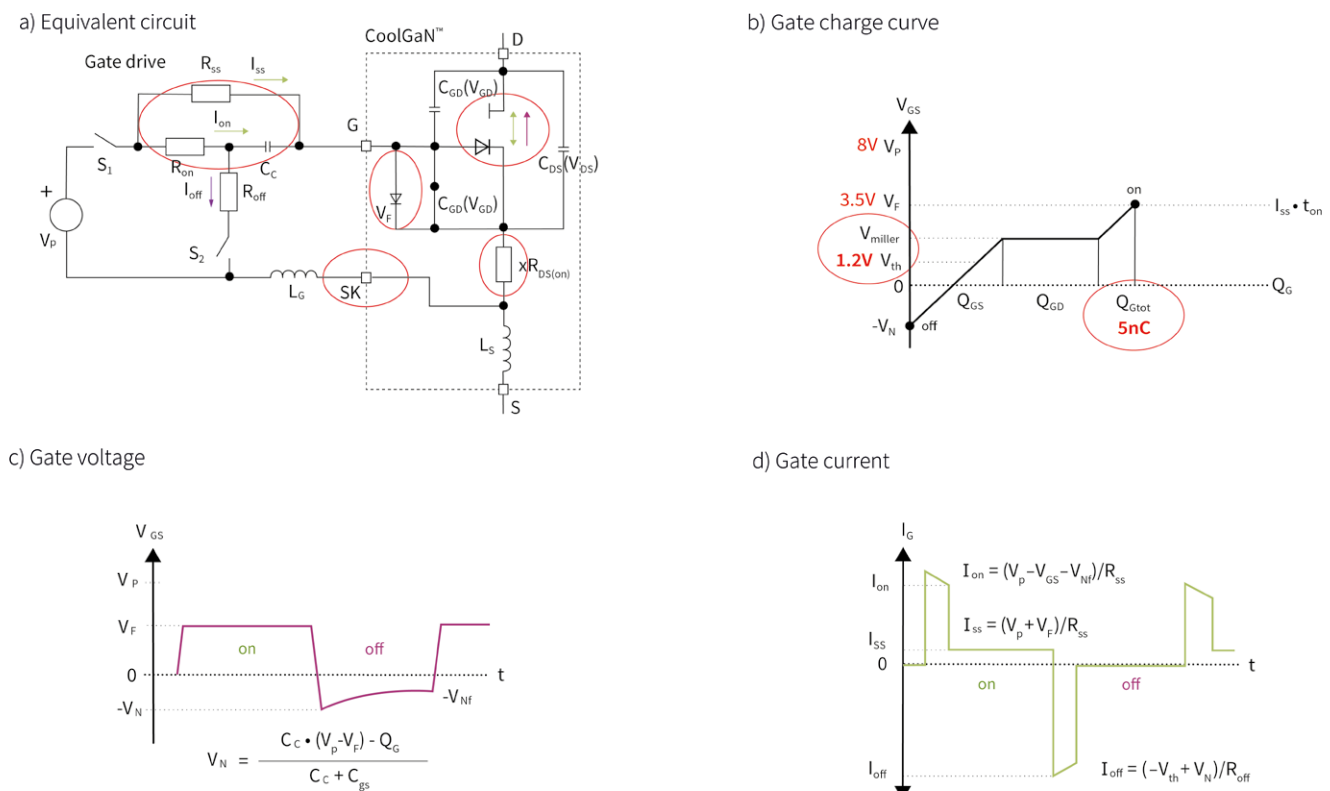


Figure 1 Equivalent circuit of CoolGaN™ and gate drive (a), gate charge curve (b), gate voltage (c) and current waveform (d)

This is why the most simple driving concept depicted in **Figure 1a** consists of a standard gate driver (switches S1, S2) and two parallel gate current paths to provide the high transient currents I_{on}/I_{off} via R_{on}/R_{off} and coupling capacitance C_C , while R_{ss} is used to set the small on-state current I_{ss} . In this context, all gate drivers out of Infineon's EiceDRIVER™ family can be regarded as nearly ideal due to their low output impedance and fast signal propagation. Several possible configurations with isolated (2EDF7275K, 2EDF7275F, 1EDB7275F) and non-isolated (1EDN7550B) drivers are described in [2].

Another typical GaN feature is evident in **Figure 1b** as well. The low V_{th} together with a relatively high Q_{GD}/Q_{GS} ratio in some cases (hard-switched half-bridge) requires the availability of a negative gate drive voltage (V_N) to keep the device safely "off" and avoid unintended turn-on effects. Fortunately, the coupling cap C_C not only provides the high current path but also generates a negative gate voltage V_N after any switching-off event. The reason is that during the preceding "on"-state (S1 closed), C_C has been charged to the difference of driver supply V_P and gate clamp voltage V_F . Thus, when the "off" switch S2 is closed, C_C acts as a charge-pump driving the gate to a negative voltage V_N **Figure 1c**. The resistors define the gate current levels, and with proper dimensioning of the components, all gate drive parameters can be easily adapted to transistor size and application.

This drive concept is simple, versatile, and flexible – but what are the drawbacks?

The most important one is probably the so-called "first-pulse" effect. For a hard-switching transient happening, soon after having switched "off" the passive switch in a half-bridge, the negative V_{GS} will prevent any erroneous turn-on. However, in situations with a much longer dead time, e.g. during start-up, in burst-mode operation, or in case of non-complementary switching, spurious turn-on may happen and increase the voltage/current stress on the switches – in extreme cases, even dangerous oscillations can result. This is why dedicated GaN driver ICs have been developed to address and eliminate the adverse "first-pulse" effects.

Dedicated CoolGaN™ driver: The GaN EiceDRIVER™ family

Figure 2a explains the implemented concept. The output stage consists of two half-bridges, connected to gate and source of the GaN switch, respectively. In normal operation, an external RC network defines the gate drive parameters, very similar to the standard drive. However, by closing switches S1 and S4, a negative gate voltage $-V_P$ can be applied even with completely discharged C_C .

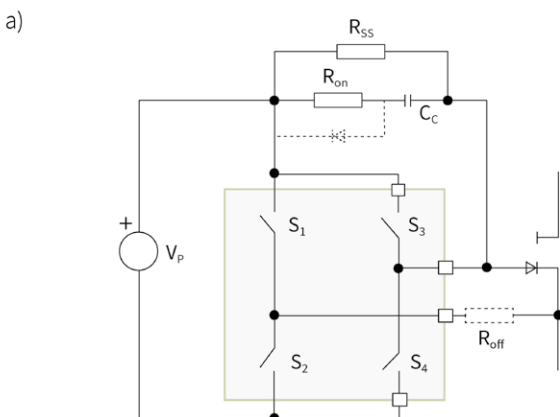


Figure 2b depicts a full switching sequence including a "first-pulse" situation. In normal operation the initial "off"-level V_N is defined by C_C and V_P . However, instead of discharging C_C via R_{ss} , the "off"-voltage is switched back to zero after a programmable fixed time t_1 (typically some 100 ns). This on the one hand means identical conditions for all switch "on" events (independent of "off"-state duration), on the other hand minimizes reverse conduction losses during the dead times. A "first-pulse" situation is assumed if the "off"-state lasts longer than a time t_2 (typically 32μs). Then the "off"-level is switched to $-V_P$, thereby effectively avoiding any unintended turn-on when the opposite switch starts switching again.

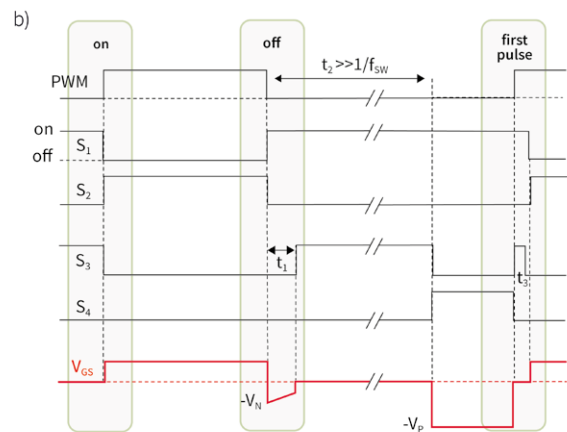


Figure 2 New differential gate drive concept for CoolGaN™ (a) and associated control signals (b)

The GaN EiceDRIVER™ ICs have been developed to optimally drive and protect Infineon's CoolGaN™ 600 V e-mode HEMTs. As depicted in **Figure 3**, these drivers are available in three package versions, enabling an easy adaptation to different requirements in terms of power density, PCB space, and isolation rating [2].



Figure 3 GaN EiceDRIVER™ product family

Table 1 summarizes the main specifications of Infineon's GaN EiceDRIVER™ ICs. The functional isolated 1EDF5673K is available in the LGA-13 5x5 mm² package, whereas the 1EDF5673F comes in a DSO-16 150-mil package. If the PWM control signals have to cross the safe isolation barrier, as in the secondary-side controlled resonant LLC converter, the 1EDS5663H with reinforced isolation is the appropriate choice. In the DSO-16 300-mil package, it is compliant with the safety requirements of the VDE 0884-10 and UL 1577 standards.

Despite the different packages and input-to-output isolation classes, ratings, and certifications, these gate drivers are based on the same rail-to-rail driver output stage. It is realized with complementary MOS transistors that are able to provide a typical 5.4 A sourcing and 9.8 A sinking current. Although these current levels are neither needed nor reached when driving GaN HEMTs (due to their low gate charge of only a few nC), the low on-resistance coming together with the high driving current is

nevertheless beneficial. With an R_{on} of 0.85Ω for the sourcing pMOS and 0.35Ω for the sinking nMOS transistor, the driver can be considered as a nearly ideal switch, enabling cooler operation due to less power dissipation in the IC.

Table 1 GaN EiceDRIVER™ 1EDI-G1 product family specifications

Product	Package	Input-to-output isolation		Peak source / sink output current	CMTI (min.)	Prop. delay	Prop. delay accuracy
		Isolation Class	Rating				
1EDF5673K	LGA-13 5x5 mm ²	functional	$V_{IO} = 1.5 \text{ kV}_{OC}$	5.4 A / -9.8 A	200 V/ns	37 ns	-6 / +7 ns
1EDF5673F	DSO-16 150 mil	functional	$V_{IO} = 1.5 \text{ kV}_{OC}$		200 V/ns	37 ns	-6 / +7 ns
1EDS5663H	DSO-16 300 mil	reinforced	$V_{IOTW} = 8 \text{ kV}_{pk}$ (VDE 0884-10) $V_{SO} = 5.7 \text{ kV}_{rms}$ (UL 1577)		200 V/ns	37 ns	-6 / +7 ns

The common-mode transient immunity (CMTI) is crucial to ensure that no signal corruption occurs during fast transients between the input and output reference potentials (grounds) of the galvanically isolated gate driver IC. Since GaN HEMTs can generate fast voltage transients exceeding 100 V/ns, CMTI is a key parameter to be considered for gate driver selection. The GaN EiceDRIVER™ products feature a minimum 200 V/ns CMTI capability which by far exceeds the requirements for the majority of fast-switching GaN applications, ensuring high robustness and reliability.

The timing performance of the driver is also of particular importance to fully exploit the potential of GaN HEMTs. The low input-to-output propagation delay (37 ns) combined with high accuracy (-6 ns / +7 ns) over both temperature and production variations, allows for usage of a short dead time between the two PWM signals of the half-bridge; this improves efficiency by increasing the effective power transfer period.

The GaN EiceDRIVER™ product family is optimized for high-voltage conversion applications. **Figure 4** shows a typical switched-mode power supply (SMPS) with a totem-pole PFC and a secondary-side controlled resonant LLC converter followed by a full-bridge synchronous rectifier.

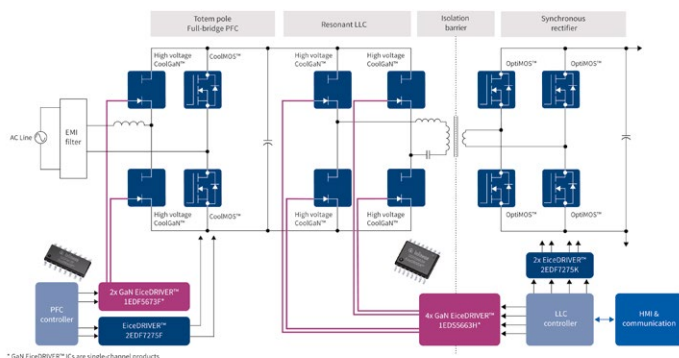


Figure 4 GaN EiceDRIVER™ in typical SMPS application

As the controller is located on the primary side, and functional driver isolation is sufficient, 1EDF5673F or 1EDF5673K gate driver ICs are the best choice in this hard-switching half-bridge application. For driving the low-frequency CoolMOS™ phase rectification half-bridge (switching at 50 Hz or 60 Hz only), the EiceDRIVER™ 2EDF7275F is recommended. However, since the PWM signals have to cross the safe isolation barrier, the DC-DC conversion stage composed of the resonant LLC and full-bridge synchronous rectifier requires a reinforced isolated driver. The 1EDS5663H features 8 mm input-to-output creepage/clearance distances and is compliant with the safety requirements of the VDE 0884-10 and UL 1577 standards. For

driving the OptiMOS™ based full-bridge synchronous rectifier, the EiceDRIVER™ 2EDF7275K is best suited.

Switching CoolGaN™ HEMTs at frequencies above 1 MHz

Thanks to significantly reduced parasitic capacitances, Infineon's CoolGaN™ technology is the ideal choice when switching at frequencies in the MHz range, as required for example in wireless charging applications. For testing CoolGaN™ switches together with the dedicated GaN EiceDRIVER™ ICs, the half-bridge evaluation board EVAL_1EDF_G1_HB_GAN has been designed [3]. The generic topology, a fundamental building block in nearly all converter and inverter applications, can be configured for boost or buck operation, pulse testing, or continuous full-power operation. The power circuit of this evaluation board is composed of two IGOT60R070D1 CoolGaN™ 600 V e-mode HEMTs with 70 mΩ $R_{DS(on)}$, and two 1EDF5673K GaN EiceDRIVER™ ICs. The output and bus voltage of this evaluation platform can range up to 450 V, limited by the capacitor rating. Furthermore, it is able to switch a continuous current of 12 A as well as a peak current up to 35 A, and can be configured for hard- or soft-switching. The switching frequency can go up to several MHz, depending on transistor power dissipation (limited to about 15 W per device with appropriate heatsink and airflow).

Figure 5a shows the top-side view of the GaN EiceDRIVER™ half-bridge evaluation board and the gate-to-Kelvin-source voltages of the two CoolGaN™ transistors. As explained, the V_{GS} voltage is clamped by the intrinsic gate-to-source diode to around 3.5 V. Additionally, the negative voltage after every turn-off is defined by the gate driver supply voltage and the coupling capacitance C_C . Typically 200 ns after turn-off, V_{GS} is actively switched to zero in order to reduce the reverse conduction losses during the subsequent dead time. As can be seen from the measured waveforms in **Figure 5b**, reliable commutation of the CoolGaN™ transistors above 1 MHz can be ensured by the GaN EiceDRIVER™ gate driver ICs.

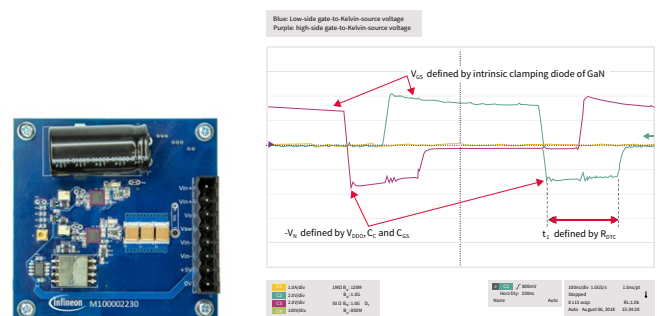


Figure 5 GaN EiceDRIVER™ half-bridge evaluation board (a) and measurement results (b).

References:

- [1] B. Zojer, "Driving 600 V CoolGaN™ high electron mobility transistors", Infineon Technologies AG, Application Note AN_201702_PL52_012, 2018
- [2] D. Varajao and C. M. Matriciano, "Isolated gate driving solutions: increasing power density and robustness with isolated gate driver ICs", Infineon Technologies AG, Application Note AN_1909_PL52_1910_201256, 2020
- [3] E. Persson, Y. Haksoz, "600 V CoolGaN™ half-bridge evaluation platform featuring GaN EiceDRIVER™", Infineon Technologies AG, Application Note AN_1811_PL52_1811_234307, 2019