

Hardware design guide for the TRAVEO™ T2G family

About this document

Scope and purpose

This application note describes how to set up a hardware environment for TRAVEO™ T2G MCU family.

Intended audience

This application note is intended for hardware designers.

Associated part family

TRAVEO™ T2G automotive microcontroller family CYT2B, CYT4B, CYT3D, CYT4D series

Table of contents

About this document.....	1
Table of contents.....	1
1 Introduction	5
2 Package selection	6
2.1 LQFP.....	6
2.2 BGA and PBGA	6
3 Power supply.....	7
3.1 Power domains.....	7
3.2 ADC supply pins.....	7
3.3 Power supply variants.....	7
3.3.1 ADC	7
3.3.2 Debug connection	7
3.4 Power ON/OFF sequence of power supply domains	7
3.4.1 General	8
3.4.2 External core supply.....	8
3.4.3 ADC	8
3.5 Power supply circuit.....	9
3.6 External core supply control.....	9
3.7 Unused power domains	10
4 Clock system	11
4.1 Clock sources.....	11
5 PLL	12
5.1.1 Example	12
6 Reset circuit	13
6.1 Reset pin (XRES)	13
6.2 Power supply monitoring.....	13

Table of contents

6.2.1	Power-on reset (POR).....	13
6.2.2	Brown-out detection (BOD)	13
6.2.3	Low-voltage detection (LVD) and high-voltage detection (HVD)	14
6.2.4	Over-voltage detection (OVD).....	14
6.2.5	Over-current detection (OCD).....	14
6.2.6	Power domain voltage monitoring by the ADC.....	14
6.3	Watchdog reset.....	15
7	Ports and non-power pins	16
7.1	Port input/unused pins: General considerations.....	16
7.1.1	Open pin connection.....	16
7.1.2	Direct connection to GND or power supply.....	16
7.1.3	Internal pull-up/down resistor as termination	16
7.1.4	External pull up/down resistor as termination	16
7.2	Dedicated port pins.....	17
7.3	Port pin configuration in AUTOSAR MCAL	17
7.4	Pins in low-power mode	18
7.5	Latch-up considerations (Switch).....	18
7.5.1	Solution A	20
7.5.2	Solution B (recommended)	21
7.6	5-V-tolerant input pins	22
7.7	Reset behavior of I/O port pins	22
7.8	Glitch filtering.....	22
7.8.1	Analog filter	22
7.8.2	Digital-based filter.....	22
7.9	Mode pin	23
7.10	External interrupt input pins	23
7.11	Clamping structure of I/O pins with shared analog functions.....	24
7.12	External supply for the core voltage.....	24
7.12.1	Requirements	24
7.12.2	Drive output current of “Enable” control pin.....	25
7.13	Audio-DAC.....	25
7.13.1	Implementation and features.....	25
7.13.2	Power domain filter	26
7.13.2.1	Low-pass filter calculation.....	27
7.13.3	Unused audio-DAC	29
7.13.4	Avoiding the pop noise at the speaker output.....	29
8	Flash programming connection	31
9	Debug interface	32
9.1	Legacy 20-pin IDC JTAG connector.....	32
9.2	10-pin Cortex® debug connector	32
9.3	20-pin Cortex® debug + ETM connector.....	33
9.4	Termination resistors.....	33
10	Clock output function	36
10.1	Using the EXT_CLK port pin	36
10.2	Using the alternate function pin	36
11	Layout and electromagnetic compatibility.....	37
11.1	General.....	37
11.2	Power supply pins	37
11.3	Ground and power supply	37

Table of contents

11.4	Power supply decoupling	38
11.4.1	Placement.....	38
11.4.2	I/O domains	40
11.5	Quartz crystal placement and signal routing.....	40
11.5.1	Setup.....	40
11.5.2	PCB design.....	42
11.6	Component placement	43
11.7	Signal routing	43
12	Thermal considerations	44
13	ADC.....	46
13.1	Filter design considerations for analog inputs.....	46
13.1.1	Principle of acquisition	46
13.1.2	Accuracy at sample time	46
13.1.3	Sample time charging process	47
13.1.4	Charge balancing between C_{EXT} and C_{VIN}	48
13.1.5	Charging the analog input by the analog source V_0	49
13.1.6	Filter case: $C_{EXT} > 2^r * C_{VIN}$	50
13.1.7	Discrete RC filter	51
14	Assembly and package-related PCB design	52
15	Video interface.....	53
15.1	FPD-Link.....	53
15.1.1	Signal pin configuration.....	53
15.1.2	Power domain VDD_PLL	53
15.2	RGB interface	53
15.2.1	Signal pin configuration.....	53
16	Summary	55
17	Abbreviations	56
18	Related documents	58
19	Appendix A – Power supply concept	59
19.1	Introduction (key note)	59
19.2	Definitions	59
19.3	CYT2B series	60
19.4	CYT3B/4B series with TEQFP package.....	63
19.5	CYT4B series with BGA package.....	67
19.6	CYT3D series with TEQFP package.....	70
19.7	CYT4D series with BGA package.....	74
20	Appendix B – Analog supply	78
21	Appendix C – Oscillator layout	79
21.1	QFP packages	79
21.2	BGA packages	80
22	Appendix D – Active regulator inrush current	81
23	Appendix E – Unused power domain handling	82
23.1	Introduction.....	82
23.2	CYT2B series	83
23.3	CYT3B/4B series.....	84
23.4	CYT3D Series.....	85
24	Appendix F – Power supply filter characteristics	87



Table of contents

25 Appendix G – Clamping structure of I/O pins with shared analog functions88

Revision history.....90

Introduction

1 Introduction

This document describes how to set up a hardware environment for the TRAVEO™ T2G MCU family.

Design restrictions and recommendations regarding signal wiring and the electrical power system of the MCU are considered. For details on device features and their relevant settings, see the TRAVEO™ T2G architecture technical reference manual (TRM) and the dedicated device datasheet.

This application note answers most of frequent questions. It is not intended to replace the designer's responsibility.

Package selection

2 Package selection

First, decide the package you want to use for your design. Several considerations drive this decision, including number of I/O pins required, PCB and product size, PCB design rules, and thermal and mechanical stresses.

The device families have a very large selection of devices to help match your exact needs in any situation with an efficient and cost-effective solution. Packaging solutions range from the ultra-small wafer scale packages to high-pin-count ball grid array (BGA) packages. Easier to layout on lower layer counts and lower cost PCBs are the leaded quad flat pack (LQFP). LQFP packaging options range from 48-pin devices to 176-pin devices for example.

Some of the package selection criteria are as follows:

2.1 LQFP

- Easier to route signals due to large pitch and the open area below the part
- Less mechanical rigidity for more protection against vibration and mechanical stress
- Disadvantages include larger package size and lower thermal conduction (θ_{JA})

2.2 BGA and PBGA

- Small-scale packages offering high pin counts in larger lead pitches, which significantly reduce the manufacturing complexities for high I/O devices. BGA packages are used in applications requiring:
 - Faster circuitry speed because the terminations are much shorter and therefore less inductive and resistive
 - Better heat dissipation
- Conventional surface mount technology (SMT) production technologies such as stencil printing and component mounting can be used.
- Robust reflow processing, due to higher pitch (1.27 mm, 0.050", typical), better lead rigidity, and self-alignment characteristics. Self-alignment during reflow is beneficial and opens the process window considerably.
- Disadvantage: X-ray is needed for solder joint inspection.

Power supply

3 Power supply

3.1 Power domains

MCU power system is based on separate analog and digital supplies. To define a single supply rail, all power supplies should be connected to voltages between 3.3 V and 5.0 V. If you need to apply different power supply voltages, such as 5 V to the analog system (i.e., $V_{DDA} = V_{REFH}$) and 3.3 V to V_{DDIO} of the MCU port pins, see the operating conditions in the datasheet of the dedicated device.

Devices designed for applications with higher power dissipation require an external core supply source, which is controlled by dedicated MCU pins. See also [Appendix A – Power supply concept](#).

3.2 ADC supply pins

To avoid additional leakage current, connect the ADC supply pins (V_{DDA} , V_{SSA} , V_{REFH} , and optionally V_{REFL}), even if the ADC is not used.

3.3 Power supply variants

Although separate power supplies are provided in the MCU, dependencies between each other must be considered. The power domains are independent of each other.

3.3.1 ADC

The enabled analog inputs belong to dedicated I/O domains, which means that the applied voltage level of an analog sensor is limited to the I/O domain supply level and the protection diode structure. That means, the analog supplies and the I/O domains of the selected analog inputs must have the same voltage supply level.

3.3.2 Debug connection

You must select a power supply on which both the debug HW tool and the MCU can communicate with each other. For more information on the HW connection, see [Debug interface](#).

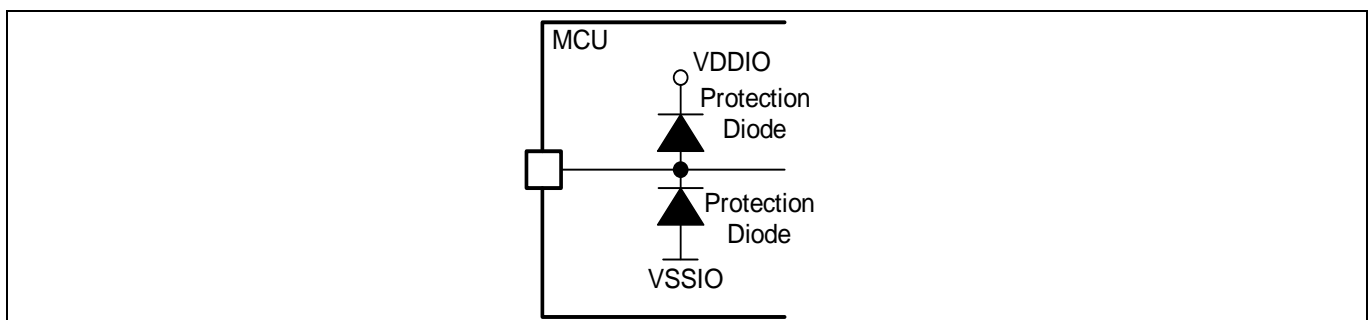


Figure 1 Protection diode structure for all I/O pins

3.4 Power ON/OFF sequence of power supply domains

Different voltage levels can be supplied to the power rails of the MCU. Therefore, power ON/OFF sequence is not required for power supplies of many devices. When there is no supply voltage at V_{DD} , but the analog supply V_{DDA} is powered, a leakage current inside the MCU can occur. However, no port output will be driven. If a device needs a power sequence, see the [device datasheet](#).

Power supply

3.4.1 General

- Disable monitoring features (for example, LVD, BOD, internal supply monitoring via ADC) before disabling related power domains. Otherwise, an unintended reset or fault might occur.
- Disable or tie to low-output pins before disabling the power domains.
- Disable input buffers before disabling the power domains.
- Power sequencing requirements and power domain dependencies can differ between power modes. So, when domains need to be switched OFF to reduce the leakage current in power save modes, carefully consider the transition phase for entering and leaving the modes.
- ECU peripherals must be in proper states during power mode transitions.

3.4.2 External core supply

- Devices running with external core supply have the same power ON/OFF sequence, because the MCU is starting in the internal supply mode and the external core supply must be enabled by the application. In power off transition, the external core supply is disabled by the MCU.

3.4.3 ADC

- In Active mode, leakage current occurs only when $V_{CCD} > V_{DDA_ADC}$.
- Many I/O domains with shared analog/digital inputs can be ramped up after V_{DDA_ADC} , as long as the ADC does not start the sampling operation of these domains.
- When the I/O domain is deployed only for digital signaling, many I/O domains can also have voltage operation range different from that of the ADC. See [Clamping structure of I/O pins with shared analog functions](#).
- Do not address analog multiplexing bus (AMUXBUS) to unpowered domains.

Power supply

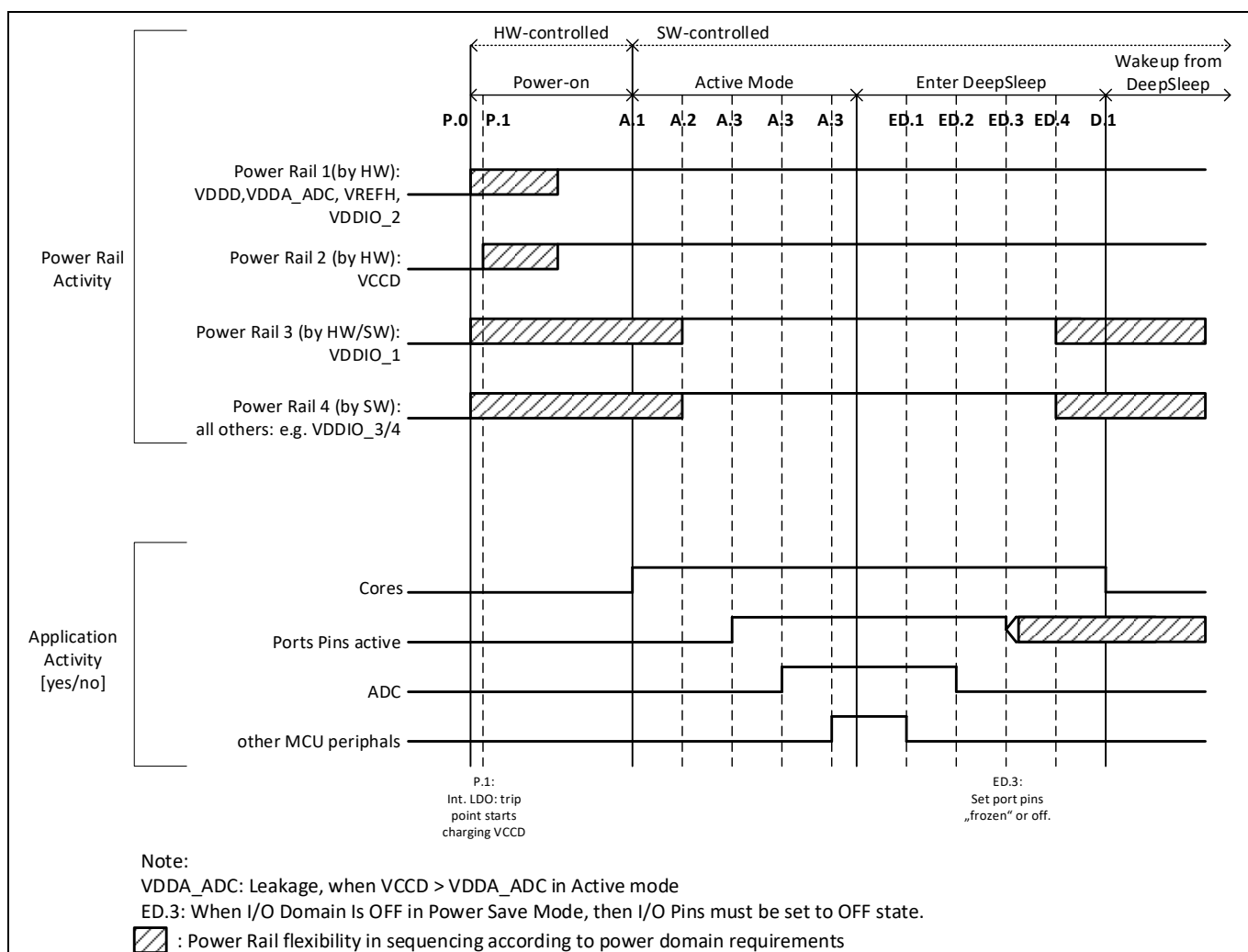


Figure 2 Power sequencing example on CYT4B series

3.5 Power supply circuit

To meet the EMC requirements for the target board, a noise-efficient supply buffering concept is needed. Therefore, the supply should be filtered. To have a minimum noise on the analog supply, it is recommended to use separate analog and digital power supplies.

Power supply concept proposals for different devices are discussed in [Appendix A – Power supply concept](#).

3.6 External core supply control

The power supply concept description is not part of this documentation. See the application note corresponding to your device in [Related documents](#).

Power supply

3.7 Unused power domains

An unused power domain is usually considered as a permanent OFF state related to the power domain in the full application lifecycle. However, a temporary state of an unused domain is also possible, when some not-always-on power domains stay on in power save modes. For details on how to handle the I/O port pins of dedicated domain, see [Port input/unused pins](#).

In general, the following are the main classes of an unused domain:

- Permanent unused domain: Not required in application
- Temporary unused domain: Disabled in power save mode

For details on different devices, see [Appendix E – Unused power domain handling](#).

Note: In principle, you can remove the big bypass capacitors and keep only small decoupling caps (decaps) left on the unused power domains that cannot be grounded. However, you must check if bypass capacitors are also used for other shared power domains in power concept.

If you do not find information on unused power domains in the device datasheet, contact technical support.

Clock system

4 Clock system

The MCU provides several clock sources depending on the system requirements. [Table 1](#) lists the available clock sources for the MCU system and shows how the clock sources are connected to the MCU internal clock system.

4.1 Clock sources

Table 1 Clock sources

Clock source	Oscillator	Int/ Ext	Port pin name (ext. only)	Frequency	Trimmable	Use case
Internal main oscillator (IMO)	Yes	Int	–	8 MHz	Yes	LIN
Internal low-speed oscillator (ILO)	Yes	Int	–	32 kHz	Yes	–
External crystal oscillator (ECO)	Yes	Ext	ECO_IN ECO_OUT	~4 MHz to 33.33 MHz	Yes	CAN communication
Watch crystal oscillator (WCO)	Yes	Ext	WCO_IN WCO_OUT	32.768 kHz	No	Watch
Low-power external crystal oscillator (LPECO) ¹	Yes	Ext	LPECO_IN LPECO_OUT	~4 MHz to 8 MHz	No	Watch
EXT_CLK pin ²	No	Ext	Optional on several pins	Note ³	–	Test
Reference clock for Ethernet PHY and MAC	Yes	Ext	ETHn_REF_CLK	50 MHz	–	Ethernet: RMII
				125 MHz	–	Ethernet: GMII, RGMII

¹ LPECO is available only for CYT4D series.

² This port pin is bidirectional and can be used as an external clock source for the device and as a clock observation mechanism for internal clock signals.

³ See the device datasheet for external clock input specifications.

PLL

5 PLL

With the help of the PLL it is possible to generate higher output frequencies based on the input reference clock (F_{ref}). The principal setup of a PLL is shown in [Figure 3](#). According to application requirements for nominal target frequency and jitter, the PLLs can have different modi⁴:

- Integer
- Fractional
- Spread spectrum clock generation (SSCG)

Depending on the selected mode, the phase detector frequency (F_{pfd}) has a permitted frequency range, which has also an impact to the nominal frequency selection of the external clock source (e.g., crystal quartz).

5.1.1 Example

Several PLLs share an external crystal quartz as the common clock source and following modi are used:

PLL#A: Integer mode: $F_{pfd} = 4\text{--}20\text{ MHz}$

PLL#B: Fractional mode: $F_{pfd} = 8\text{--}20\text{ MHz}$

Result: The crystal quartz must be min. 8 MHz.

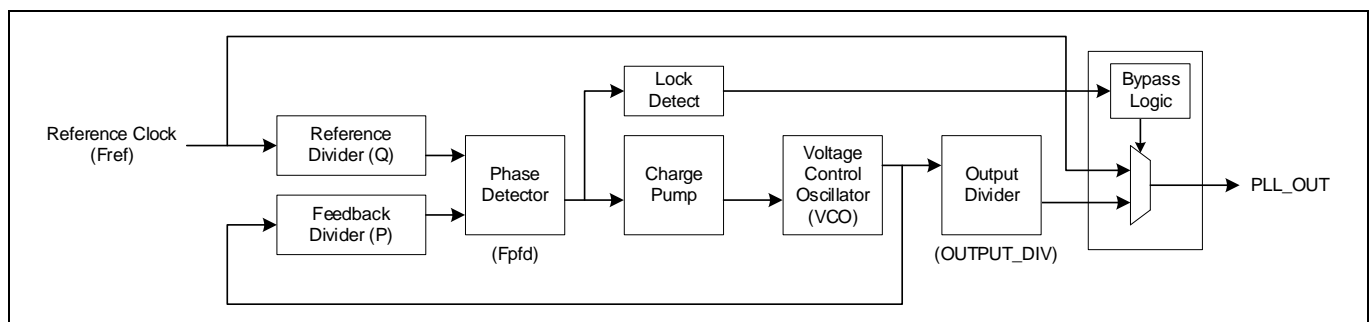


Figure 3 Principle block diagram of PLL

⁴ See the corresponding architecture TRM for details about each configuration.

Reset circuit

6 Reset circuit

To make sure that an MCU operates within specifications, an external reset signal via the reset input pin (XRES pin) or an internal reset signal can be generated. The implementation of the internal reset circuits has several advantages over the hardware design:

- Reduced bill of material (BOM) cost as the external monitoring ICs are removed
- Detection of MCU internal out-of-range operations, which cannot be monitored externally (for example, MCU internal voltage drops)

Note that external monitoring or resetting ICs might still be needed based on the application requirements.

6.1 Reset pin (XRES)

A switch connects the reset input pin to VSSIO (Ground). An internal pull-up resistor and an internal noise filter of minimum 100 ns are available to reduce the BOM cost. If an external capacitor is applied for additional filtering, make sure that the EMC requirements are fulfilled. Otherwise, the ESD test pulses might destroy the ESD protection structure inside the MCU.

For details on the reset pin, see the datasheet.

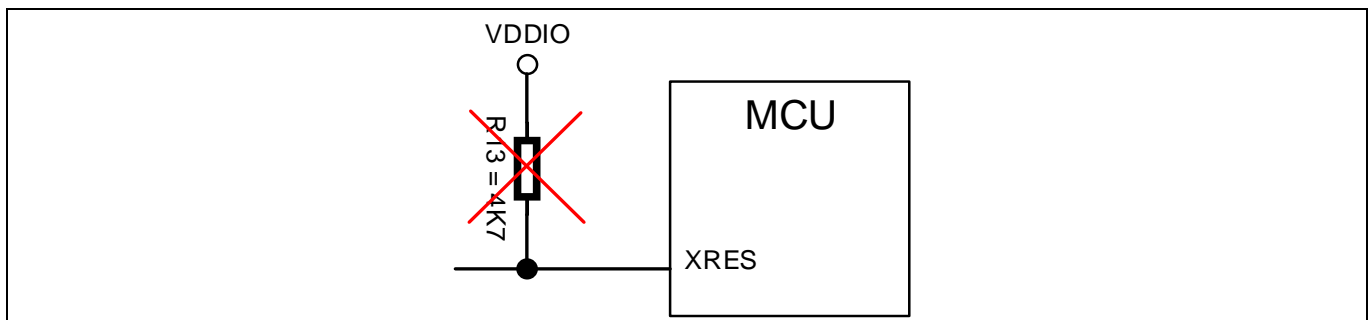


Figure 4 External reset input (XRES)

6.2 Power supply monitoring

To make sure that the MCU is not running beyond operating conditions, a broad range of power monitor circuits is provided by the MCU. See the device architecture TRM and datasheet for details.

6.2.1 Power-on reset (POR)

Power-on reset (POR) circuits provide a reset pulse during the initial power ramp. Here, only the V_{DD} power supply rail is observed.

6.2.2 Brown-out detection (BOD)

The brown-out detection (BOD) circuit protects the operating or retaining logic from possibly unsafe supply conditions by applying a reset to the device. BOD circuits for the VDDD, VDDA, and VCCD power supply rails are provided. A reset is generated when one of the monitored operating ranges is undercut. This circuit is required to detect a sneaking voltage drop of the battery power supply.

Reset circuit

6.2.3 Low-voltage detection (LVD) and high-voltage detection (HVD)

Before the BOD level threshold generates a reset, you might be warned by the configurable circuit for low-voltage detection (LVD) and high-voltage detection (HVD) use case. You can configure the trip point (detection level), which creates an interrupt for possible safety measures. This circuit can oversee faster transitions.

6.2.4 Over-voltage detection (OVD)

Over-voltage detection (OVD) circuit applies a device reset when V_{CCD} , V_{DDD} , or V_{DDA} supply goes above the maximum allowed voltage. This concept is a reverse of the BOD circuit.

6.2.5 Over-current detection (OCD)

The over-current detection circuit monitors the current of the V_{CCD} power supply rail and detects whether the load current of a regulator is higher than expected. If the current is over the regulator limit, the OCD circuit generates a reset to protect the device.

6.2.6 Power domain voltage monitoring by the ADC

The ADC provides the opportunity to monitor several power supply and ground pads. Instead of a reset, only an interrupt is generated by the corresponding ADC unit. To keep the CPU load low, the range detection feature can be enabled to generate only an interrupt when a critical range is entered. The pads can be selected by a complex multiplexer structure as shown in **Figure 5**. For details on this feature, see the *Analog subsystem > SAR ADC > Reference buffer* and *Resources subsystem (SRSS) > Voltage monitoring > Voltage monitoring by ADC* chapters in the **architecture TRM**.

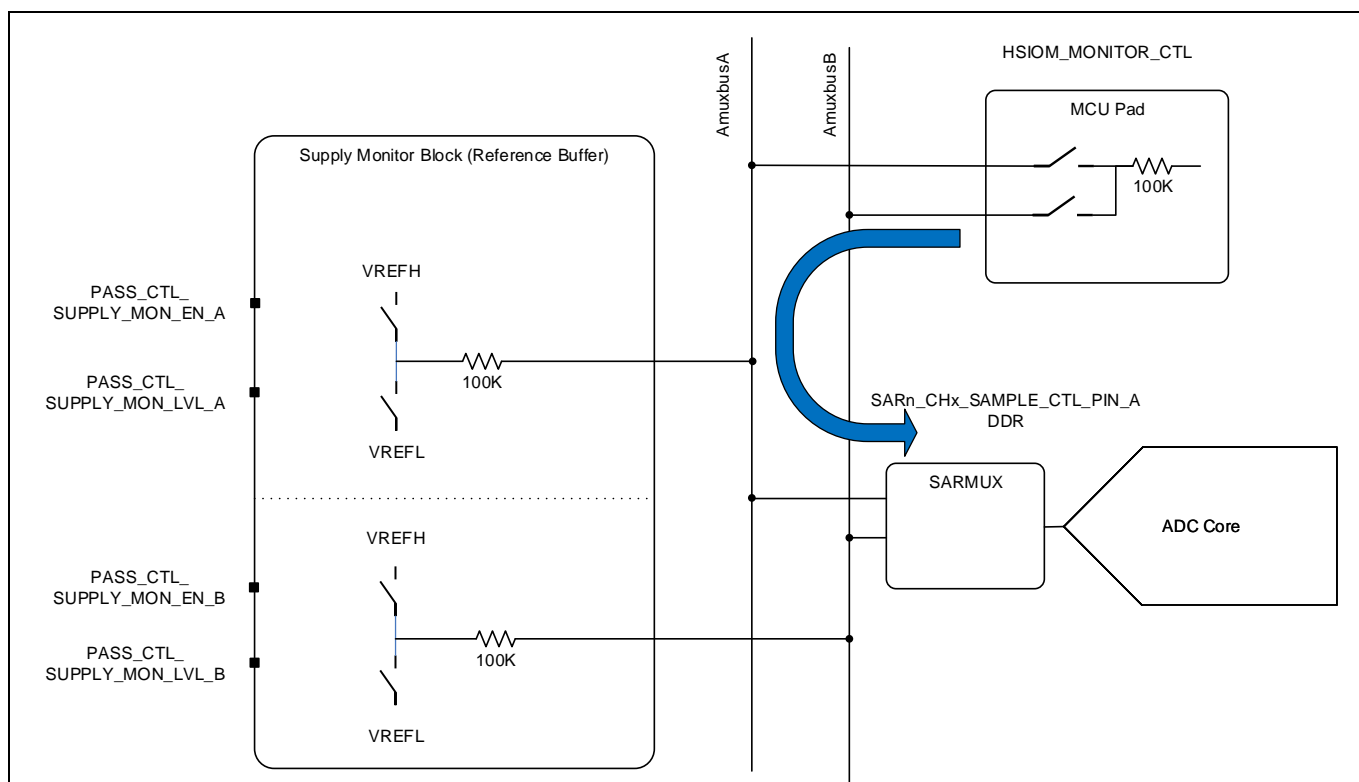


Figure 5 **Block diagram of voltage monitoring by ADC**

Reset circuit

6.3 Watchdog reset

An internal watchdog timer (WDT) within the MCU supports a wide range of capabilities. This WDT circuit can also run in the Hibernate power mode (see “Device power modes” in the [architecture TRM](#)).

Ports and non-power pins

7 Ports and non-power pins

7.1 Port input/unused pins: General considerations

This section explains the different methods to handle unused pins and the advantages and disadvantages with respect to the MCU operation. In general, the risk of unused pins is floating inputs and a latch-up effect within the pin structure.

7.1.1 Open pin connection

During and after POR, by default, the I/O pins are in a high-impedance (High-Z) analog state with disabled input buffers. The advantage of this method is that the current consumption of the MCU is lower when compared to the use of a terminal resistor, and the BOM cost is reduced. The disadvantage is that during an assembly option, a long signal trace is routed to the pin; the signal trace can take effect as an antenna and a captured noise can cause a latch-up at the pin.

7.1.2 Direct connection to GND or power supply

The I/O pins should not be connected directly to GND or to power supply as the power supply traces can take effect as an antenna to the pin and the captured noise can cause a latch-up effect.

7.1.3 Internal pull-up/down resistor as termination

When there is a risk of a latch-up effect at an unused pin due to the board design (long traces of optional features), terminate the input pin using internal pull-up or pull-down resistors.

The advantage is low current consumption and BOM cost reduction compared to using external termination resistors. Disadvantage is that you must configure the port pin state after a reset. Therefore, during a reset caused by any disturbance (supply, clock issues, and so on), the internal termination is not available anymore and the system is again vulnerable against a latch-up effect.

You can choose this method if there are unused pins without a long trace. In general, it must be considered that the pin state (enabled pull-up or pull-down resistor) must be unchanged when a low-power mode is entered. The reason is that for an external resistor, the internal termination must be available all the time.

7.1.4 External pull up/down resistor as termination

An external termination resistor can be placed next to the unused I/O pin instead of using the internal ones. In the case of an open signal line routed to the pin, any injected noise can be safely terminated even during a device reset. A resistor value between 2.2 k Ω and 10 k Ω can be used. However, you should not connect several unused pins to one common termination resistor because if unused I/O pins unintentionally drive different output levels against each other, the I/O pins might be permanently damaged.

Ports and non-power pins

7.2 Dedicated port pins

For dedicated MCU peripherals, the unused I/O handling is explicitly considered. In most of these cases, the entire MCU peripheral including the power domain pins must be considered to avoid the risk of latch-up (LU). For details on power domain pins, see [Unused power domains](#).

Table 2 Handling of unused dedicated I/O pins

MCU peripheral	Power domain	I/O pin	I/O function [IN/OUT]	Pin I/O handling (Connect to ...)
MIPI	VDDA_MIPI	MIPI_DPx x: 0/1/2/3	IN	Open pin connection
	VDDA_MIPI	MIPI_DNx x: 0/1/2/3	IN	Open pin connection
	VDDA_MIPI	REXT	IN	Open pin connection (external 15 kΩ removed)
FPD	VDDA_FPD	FPD_TxP x: A/B/C/D	OUT	Open pin connection
	VDDA_FPD	FPD_TxN x: A/B/C/D	OUT	Open pin connection
Audio-DAC	VDDA_DAC	C_L, C_R	IN	GND
		DAC_L, DAC_R	OUT	(when Mono sound: Open pin connection of the unused part)

7.3 Port pin configuration in AUTOSAR MCAL

Microcontroller abstraction layer (MCAL) of AUTOSAR is a low-level driver for the microcontroller, which is used in the software developed for automotive applications. So, the port pin configuration with the PORT module is part of the MCAL.

The following are the possible risks if there is a wrong port pin setting to the MCU:

- I/O structure being destroyed
- Additional leakage current in power save modes
- Latch-up effect

Therefore, especially with regard to the latch-up risk, keep the SW port pin configuration always compliant with the HW concept for unused I/O pins (see [Port input/unused pins](#)) and unused I/O power domains (see [Unused power domains](#)). This is also relevant for the SW-controlled power sequencing procedure in which unpowered I/O domains must be considered as unused power domains.

In the MCAL PORT module, you can configure port pins depending on different use cases within the corresponding application cycles, each time in a PortContainer. All port pins which are not explicitly configured by the dedicated PortContainer will be implicitly configured according to the PortDefaultContainer. The `Port_Init()` API sets all pins of the derivative device either according to the explicit configuration in PortContainer (if the pin was configured) or the implicit configuration in PortDefaultContainer (if the pin was not configured in PortContainer).

The `PortPinDirection=PORT_PIN_IN` setting sets the pin as an input and enables the input buffer. If a pin is not needed (that is, no output and no input required), the pin should be configured to

`PortPinDirection=PORT_PIN_OUT, PortPinOutputDrive=PORT_PIN_OUT_MODE_HIGHZ`, and

Ports and non-power pins

`PortPinOutputInBufEnable=FALSE`. This is the only recommended setting for `PortDefaultContainer`, but the key is to be compliant with the latch-up HW requirements to I/O pins.

7.4 Pins in low-power mode

To achieve the lowest possible quiescent current in a low-power mode, the current consumption of I/O pins must be considered. Depending on the low-power mode, the configuration state and the last output state are frozen. In the case of input pins, it is forbidden to have floating input levels because the quiescent current of the MCU increases dramatically. When an input pin is used as a wake-up pin, do not change the configuration under the assumption that the pin has an internal or external pull-up or pull-down resistor for termination. When an input pin is not required in a low-power mode, it can be configured as High-Z input with disabled input buffer. For details on different low-power modes, see the architecture TRM and the corresponding application note listed in [Related documents](#).

7.5 Latch-up considerations (Switch)

Pressed switches usually cause a bouncing signal, which can damage the MCU port pin. As a countermeasure, debounce capacitors are deployed. Exercise caution with external switches to V_{CC} or ground together with debounce capacitors connected to port pins.

A usual configuration is shown in [Figure 6](#).

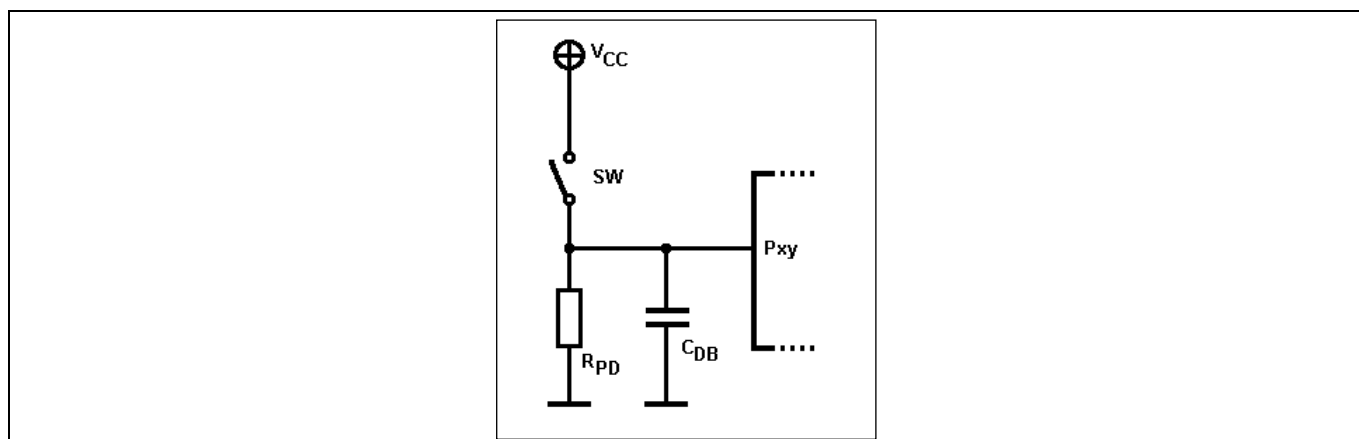


Figure 6 Principle switch circuit

R_{PD} is a pull-down resistor and C_{DB} a debounce capacitor. If the switch SW is open, a “0” is read from the port pin Pxy. When the switch is closed, the input changes to “1”.

From the physical aspect, it needs to be considered that the switch is often placed at a distance from the MCU by cable, wire, or circuit path. The longer the circuit path is, the higher is its inductivity LX (and capacity CX).

An equivalent circuit diagram is shown in [Figure 7](#).

Ports and non-power pins

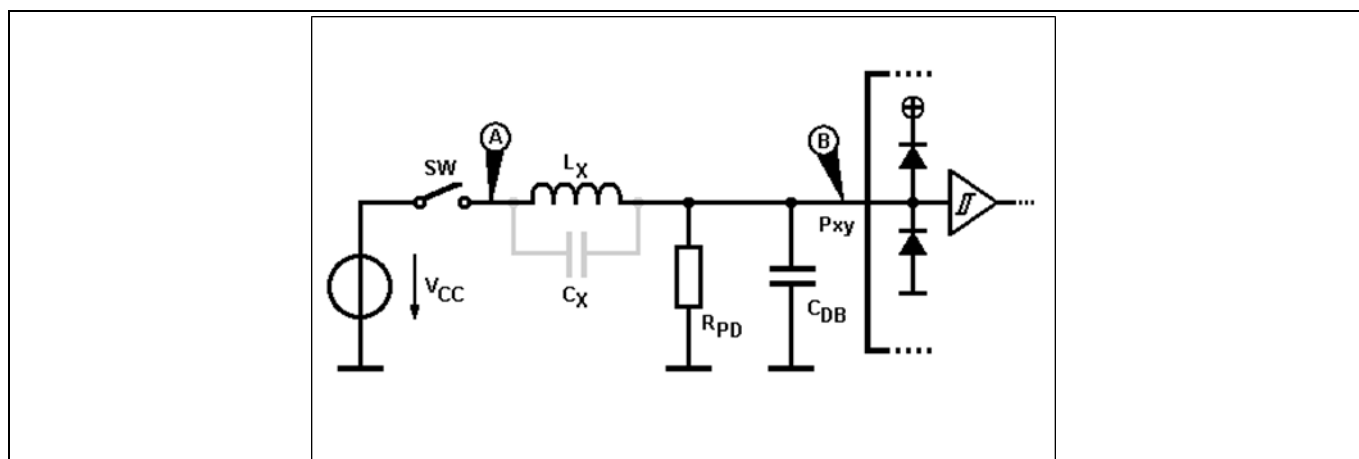


Figure 7 Equivalent circuit of the principle switch circuit

By closing the switch SW at time t_0 , as shown in [Figure 8](#), the voltage can be measured at point (A).

 


Figure 8 Signal rise after closing the switch at Point (A).

However, at the port pin Pxy on Point (B), as shown [Figure 9](#), voltage can be measured.

 


Figure 9 Signal rise after closing the switch at Point (B)

By closing the switch SW, the circuit becomes a parallel oscillator with the wire inductivity L_x , the debounce capacitance C_x , and the damping R_{PD} of the pull-down resistor (It is assumed that it is an ideal power supply, that is, it has no internal resistance).

Ports and non-power pins

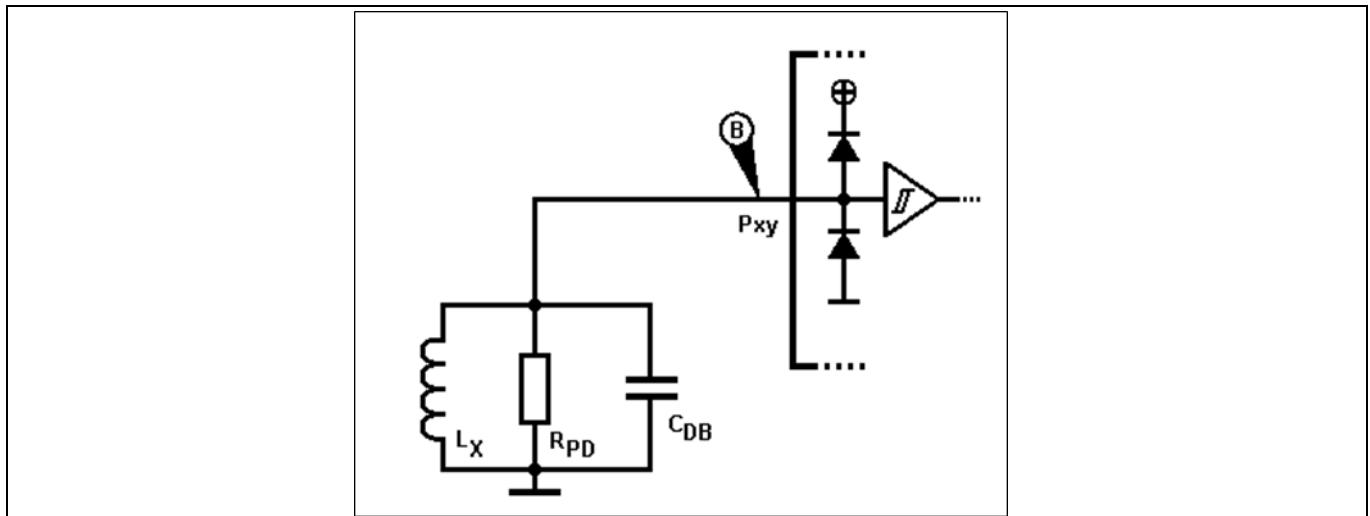


Figure 10 Equivalent circuit during closed switch

R_{PD} is often chosen high ($> 50 \text{ k}\Omega$), and so its damping effect is weak.

This (weakly) attenuated oscillator causes voltage overshoots on the port pin (Point (B)), as shown in red in [Figure 11](#).

 


Figure 11 Signal overshoots on the port pin after closing the switch

These overshoots may cause an internal latch-up on the port pin, as the internal clamping diode connected to internal power supply becomes conductive. Similar is the effect if the switch SW is opened. In this case, there are undershoots on the port pin.

The frequency of the oscillation can be calculated by [Equation 1](#).

$$f_{osc} = \frac{1}{2\pi\sqrt{L_X C_{DB}}} \quad \text{Equation 1}$$

The inductivity (L_X) is an unknown value and depends on the PCB, its routing, and the wire length.

There are two counter measures to prevent a latch-up.

7.5.1 Solution A

Decrease the capacitance of the debounce capacitor. This increases the oscillation frequency, which causes the overall energy of the overshoots to be smaller.

Ports and non-power pins

 


Figure 12 Bounce signal on the pin with a large capacitance

 


Figure 13 Bounce signal on the pin with a small capacitance

This solution has two disadvantages: the debounce effect decreases and there is no guarantee that the latch-up condition is eliminated.

7.5.2 Solution B (recommended)

Use a series resistor (R_S) at the port pin as shown [Figure 14](#).

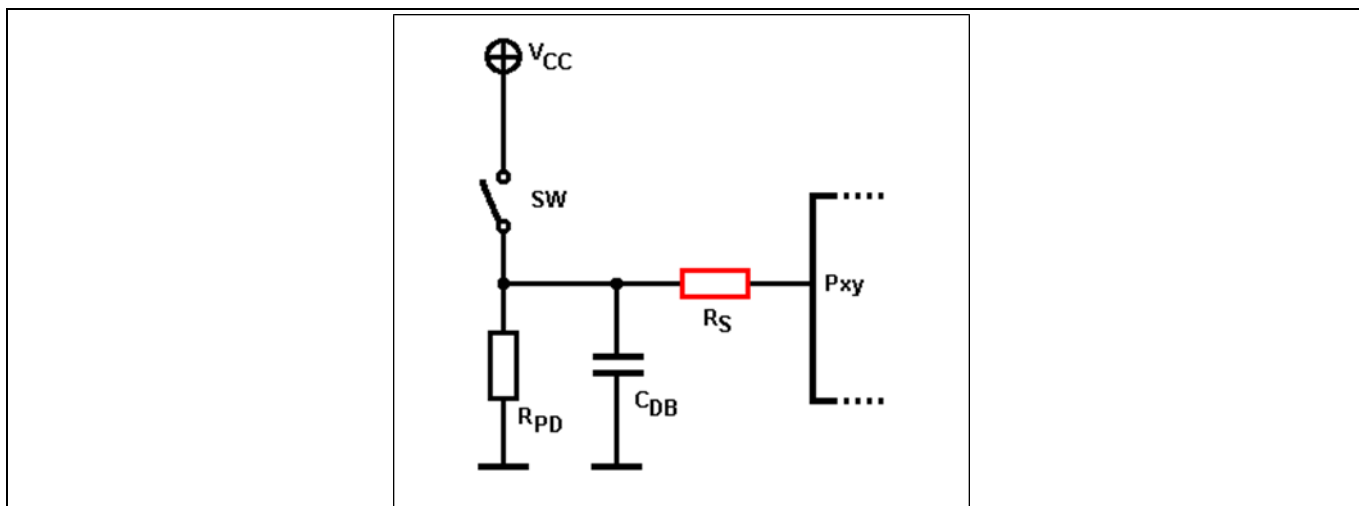


Figure 14 Recommended switch circuit with series resistor

The series resistor R_S reduces the amplitude of the oscillation and decreases the voltage offset at first. Do not choose too high a resistor value. Otherwise, the port pin input voltage (V_P) will be below the high input level threshold of the dedicated port pin (for example, CMOS/TTL/Automotive level).

Ports and non-power pins

 


Figure 15 Reduction of the signal bouncing on the pin due to the series resistor

7.6 5-V-tolerant input pins

The MCU does not have 5-V-tolerant input pins if the corresponding I/O domain has a smaller voltage supply (for example, 3.3 V). In the case of the deployment of an I²C bus system with 5 V, and if V_{DDIO} is supplied with 3.3 V, an external level shifter must be added to avoid the latch-up effect on the MCU pin.

7.7 Reset behavior of I/O port pins

During and after the power-on reset (POR), all GPIOs are in high-impedance analog state and the input buffers are disabled. During runtime, GPIOs can be configured by writing to the associated registers. The Debug Access Port (DAP) connection can be disabled or reconfigured for general-purpose use only after the code execution starts.

7.8 Glitch filtering

The MCU provides the option of internal glitch filtering. As the glitch filters are not available on every port pin, the assignment of wakeup pins must be done with caution. Before assigning wakeup pins, check the number of available glitch filters in the device datasheet.

7.8.1 Analog filter

Every port group has one analog filter, which also works in DeepSleep mode. For details on AC characteristics, see the device datasheet.

7.8.2 Digital-based filter

The smart I/O module in the I/O system can implement one digital-based filter in dedicated ports. In the DeepSleep mode, either the internal low-speed oscillator (ILO) or the external crystal oscillator (ECO) clock can be selected as the clock source (see [Clock system](#)). This means that the minimum filter period is ~30 μ s. Additionally, the current consumption increases because a clock is running. For more information, see smart I/O, I/O system in the architecture technical reference manual (TRM).

See [Latch-up considerations \(Switch\)](#) for the latch-up considerations regarding deployed external filters.

Ports and non-power pins

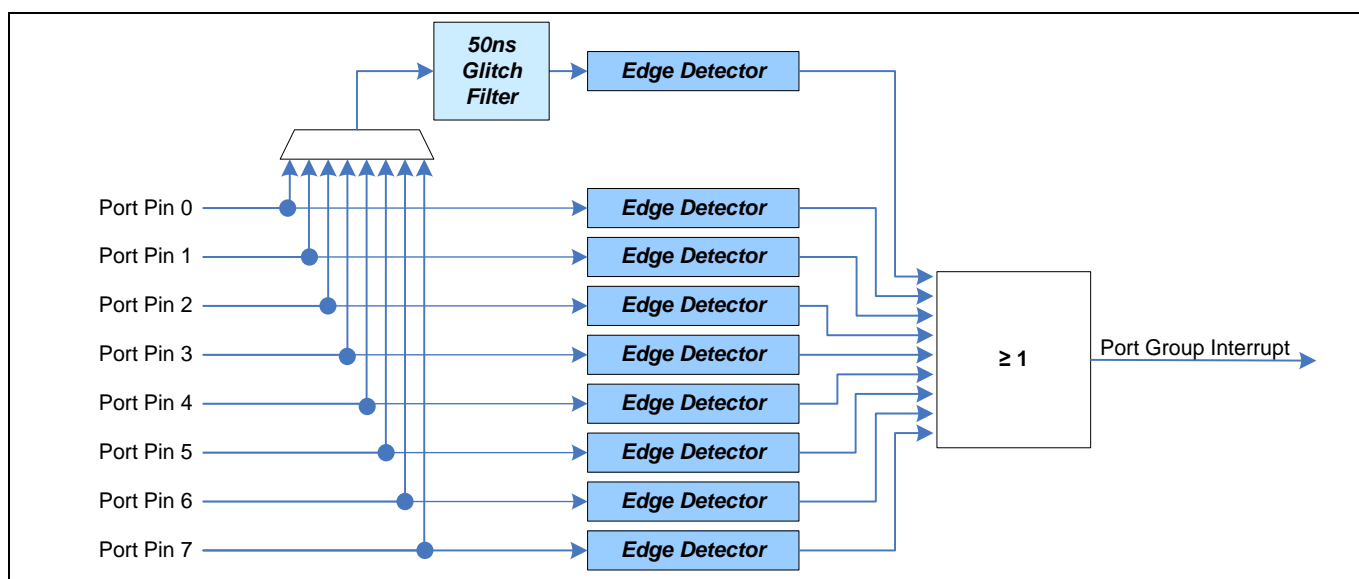


Figure 16 Port glitch filter and interrupt structure

7.9 Mode pin

A dedicated Mode pin is not required to enter the MCU into programming or normal run mode.

7.10 External interrupt input pins

In general, an external interrupt can be captured by edge detection on every general-purpose I/O (GPIO) port pin. See [Glitch filtering](#) to learn how to use glitch filtering.

Table 3 lists the wakeup sources in the different power modes. For more details on the power modes, see the “System resources subsystem (SRSS)” and “Device power modes” sections in the corresponding TRM.

Table 3 External interrupt/wakeup support in power modes

Port pin function	External interrupt/wakeup in power mode			
	Active	Sleep	DeepSleep	Hibernate
GPIO	x	X	x	-
Dedicated peripherals ⁵	x	X	x	x
WAKEUP ⁶	-	-	-	x

⁵ See the architecture TRM, device datasheet, or both.

⁶ The WAKEUP function is supported only on a few pins.

Ports and non-power pins

7.11 Clamping structure of I/O pins with shared analog functions

It is important to identify the power supply domains that must have a common supply level in each application. **Figure 17** and **Appendix G – Clamping structure of I/O pins with shared analog functions** provide the overview of the clamping structure and the consequences when the analog input function is used on dedicated power domains. When any port pin of a dedicated power domain (PD) is applied as an analog input, the domain must have the same or lower voltage level than the analog supply (VDDA_ADC). **Appendix G – Clamping structure of I/O pins with shared analog functions** lists the special use cases.

General

- Usually the I/O domain, PD_1, deployed is also the same as PD_2, but in some cases there are exceptions for PD_2.
- The power domain dependency $PD_1 \leq PD_2$ is especially relevant when PD_1 is a different power domain when compared to PD_2.
- When VDDA_ADC is only on PD_3 and as long as the pin input has not started to operate as an analog input, PD_1 and PD_2 can be greater than VDDA_ADC. See also **Power ON/OFF sequence of power supply domains**.

Note: The implementation of power rail voltage levels for the dedicated I/O domains and the ADC supply must be compliant with the other power sequencing requirements mentioned in the device datasheet.

 


Figure 17 Clamping structure of I/O pins with shared analog functions

See **Appendix G – Clamping structure of I/O pins with shared analog functions** for device-specific information.

7.12 External supply for the core voltage

7.12.1 Requirements

- Applications with < 300 mA core current consumption can run with the MCU-internal LDO.
- Applications with > 300 mA core current consumption need an external supply for the core voltage.

Ports and non-power pins

For the technical requirements of the DC/DC converter and details on how to use it, see AN226698 listed in [Related documents](#).

Note: In AN226698, DC/DC converters are termed as PMIC, although only the core voltage regulation handling is considered.

7.12.2 Drive output current of “Enable” control pin

To control the Enable (EN) input pin of the external DC/DC converter, a dedicated output control pin on the MCU is available. Compared to a standard GPIO pin, the absolute maximum drive current is extremely limited. Therefore, for current limitation, a series resistor is necessary. Otherwise, this MCU control pin might be permanently damaged. For electrical specification, see the device datasheet.

7.13 Audio-DAC

7.13.1 Implementation and features

The audio digital-to-analog converter (DAC) is an analog audio block inside the MCU and supports internal CIC filter, FIR filter, interpolation filter, and delta-sigma modulator for 10-bit resolution. Both OUT signals (DAC_L and DAC_R) are intended to connect with an external audio amplifier with an external output load resistance > 20 k Ω and load capacitance < 100 pF.

The DAC block consists of several internal power domains. The cut-off frequency of the third-order low-pass filter is 90 kHz. The noise-critical circuitry of the DAC is the analog part VDDA. The DC bias output voltage will be by internal voltage divider 131.6k / 131.6k and external smoothing capacitor at the COM pin (C_{COM}), shown in [Figure 18](#).

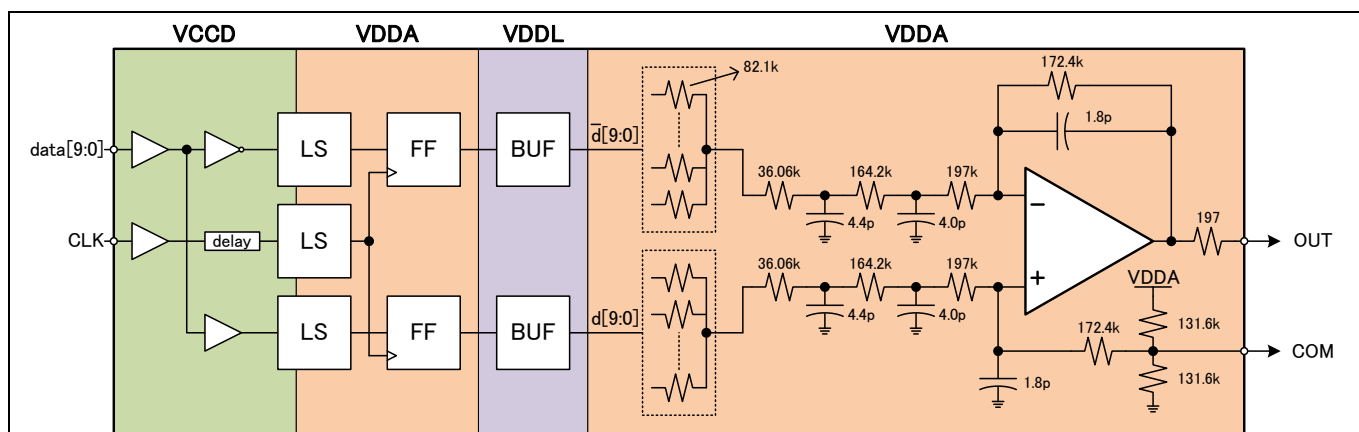


Figure 18 Block diagram of the audio-DAC output

As shown [Figure 19](#), the startup time depends on the selected smoothing capacitor (C_{COM}) value and should be configured with the integrated fast startup timer to 70 ms at 2.2 μ F (low ESR). If a capacitor larger than 2.2 μ F is needed, the timer setting for the *FastRampCount* period and the *CompRampCount* period must be adjusted based on this reference value from the datasheet, as shown in [Figure 19](#).

Ports and non-power pins

 


Figure 19 Audio-DAC startup time

During the audio-DAC startup time, the external amplifier must be either powered down or in mute mode (if mute mode is available). The typical COM capacitor value is 2.2 μF . For the typical case, the fast startup timer must be set to 13 ms to ensure that the audio-DAC is ready in 70 ms. The maximum supported COM capacitor is 10 μF . For this case, the fast startup timer must be set to 60 ms. **Figure 19** shows the relationship between DAC_EN, FAST_RAMP_EN, and how the COM output behaves during startup.

7.13.2 Power domain filter

The analog block of the Audio-DAC, which corresponds to the internal VDDA block in **Figure 18**, is very noise-sensitive. Each noise on its supply can be heard directly on the audio output. Therefore, either of the following possibility is recommended to create a silent supply at the VDDA_DAC/VSSA_DAC power domain pins:

- LDO linear regulator
- Low-pass filter (LPF) for the 3.3-V supply

If using a common 3.3-V supply for digital and analog parts of the application, it is necessary to consider the potential noise sources as listed in **Table 4**. In this case, a power supply filter in **Figure 20** is recommended for the 3V3 audio power domain.

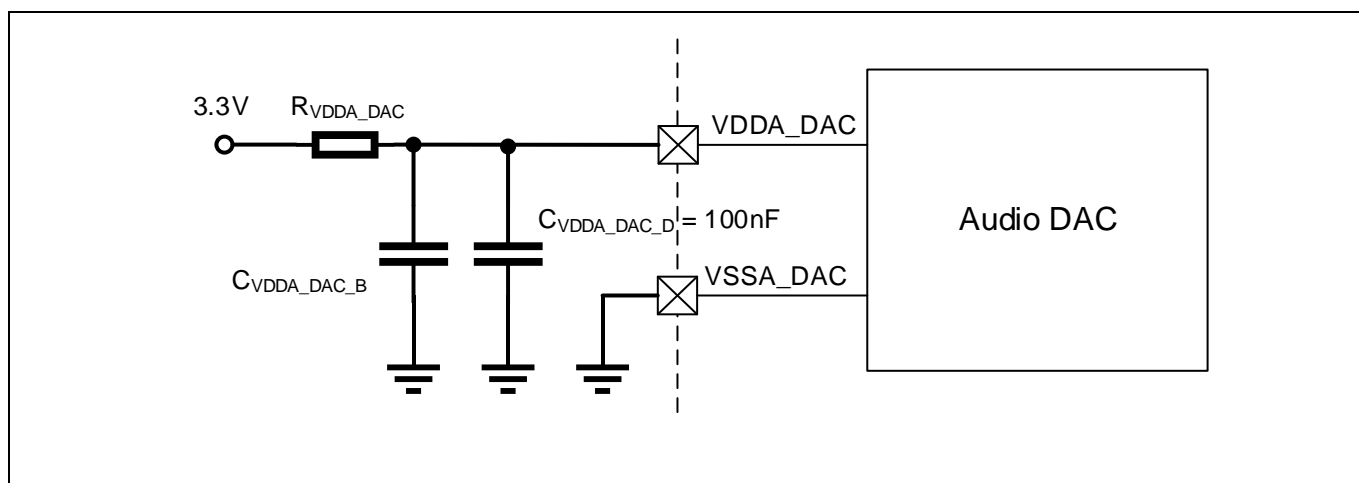


Figure 20 Power supply filter (LPF) for audio-DAC

Ports and non-power pins

Table 4 Potential noise sources on 3V3 audio power domain

Domain	Frequency range	Comment
Audio	100 Hz ... 20 kHz	Audio
DC-DC converter (switching regulator)	300 kHz ... 2.2 MHz	Switching frequency
	< 100 kHz	Response time
FPD-Link (I/O domain)	32 MHz ... 110 MHz	Bus speed; equivalent frequency range of transitions are not considered
Memory interface	50 MHz ... 133 MHz	
Ethernet	50 MHz ... 125 MHz	
Communication interface	1 MHz ... 10 MHz	

7.13.2.1 Low-pass filter calculation

Figure 21 shows a simple RC LPF for the power supply of the audio-DAC, which is the responsibility of the user.

 


Figure 21 RC low-pass filter (RC LPF)

The cut-off frequency of the filter can be calculated by **Equation 2**.

$$a = \frac{V_i}{V_o} = \frac{1}{\sqrt{1 + (2\pi fRC)^2}} \quad \text{Equation 2}$$

$$f_c = \frac{1}{2\pi RC}$$

Note: RC-filter -6 dB per octave corresponds to 20 dB per decade.

Equation 3 shows an example calculation for the RC-low-pass filter.

$$f_c(-3 \text{ dB}) = \frac{1}{2\pi * 10 \Omega * 10 \mu F} = 1.592 \text{ kHz} \quad \text{Equation 3}$$

Table 5 shows the calculated cut-off frequency of LPF. Default values: C = 2.2 uF and R = 10 Ω.

Table 5 LPF cut-off frequency

R[Ω]	10	1	0.3
C[uF]	f3dB[kHz]	f3dB[kHz]	f3dB[kHz]

Ports and non-power pins

R[Ω]	10	1	0.3
10	1.59	15.9	53.1
4.7	3.39	33.9	112.9
2.2	7.2	72.3	241.1
1	15.92	159.2	530.5
0.47	33.96	338.6	1128.8
0.22	72.34	723.4	2411.4
0.1	159.15	1591.5	5305.2

Table 6 LPF DC-power power drop estimation

IDD[mA] (SID1318)	R[Ω]	Vdc[mV]
3.2	10	32
	4.7	15.04
	2.2	7.04
	1	3.2
	0.8	2.56
	0.5	1.6
	0.3	0.96
	0.1	0.32

There is an estimated IR drop on the power domain pin, VDDA DC, as shown in [Table 6](#), due to the series resistor (Rfilter). The reduction of the series resistor (Rfilter) of the LPF impacts the cut-off frequency. As an alternate for the resistor, a ferrite bead with $R_{dc} \leq 300 \text{ m}\Omega$ is recommended. See the example in [Appendix F – Power supply filter characteristics](#).

Note: In the application, to connect to the speakers, small series capacitors are added to the output pins DAC_L/R, as shown in [Figure 23](#). This HW setup is not in contradiction to the parameters R_L and C_L of SID1300 (see [Table 7](#)). These parameters belong to the test circuit as shown in [Figure 22](#).

Note: For the correct values, see the device datasheet.

Table 7 Audio-DAC output load and C_{COM} specification

SID1300	f_{CLKDA0}	System clock frequency	2.048	–	18.432	MHz	All parameters specified $f_S = 44.1 \text{ kHz}$, system clock $256 \times f_S$ and 16-bit data, $R_L = 20 \text{ k}\Omega$, $C_L = 100 \text{ pF}$, unless otherwise noted
SID1301	f_S	Sampling clock	8	–	48	kHz	
SID1302	R_L	Analog output load resistance	20	–	–	kΩ	DAC_L, DAC_R
SID1303	C_L	Analog output load capacitance	–	–	100	pF	DAC_L, DAC_R
SID1304	C_{COM}	Com Capacitance	2.2	–	10	μF	C_L, C_R
SID1305	V_{OUT_MAX}	Analog output single-end output range (±full scale)	$0.655 \times V_{DDA_DAC}$	$0.673 \times V_{DDA_DAC}$	$0.690 \times V_{DDA_DAC}$	V_{P_P}	DAC_L, DAC_R, $R_L = 20 \text{ k}\Omega$, $C_L = 100 \text{ pF}$
SID1306	V_{OUT_ZERO}	Analog output voltage (zero)	$0.49 \times V_{DDA_DAC}$	$0.5 \times V_{DDA_DAC}$	$0.51 \times V_{DDA_DAC}$	V	DAC_L, DAC_R

Ports and non-power pins

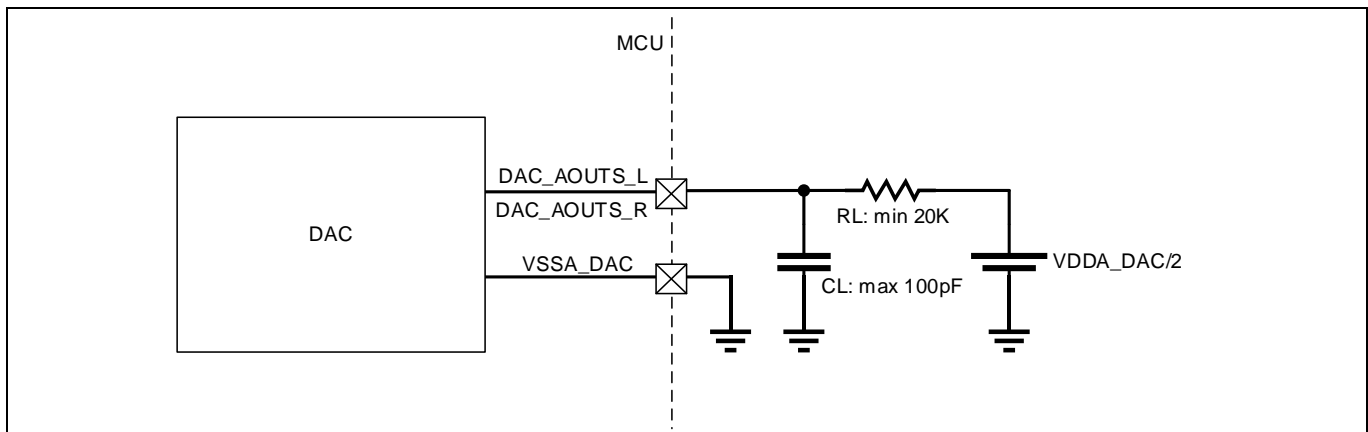


Figure 22 DC coupling connected to VDDA_DAC/2 (test circuit)

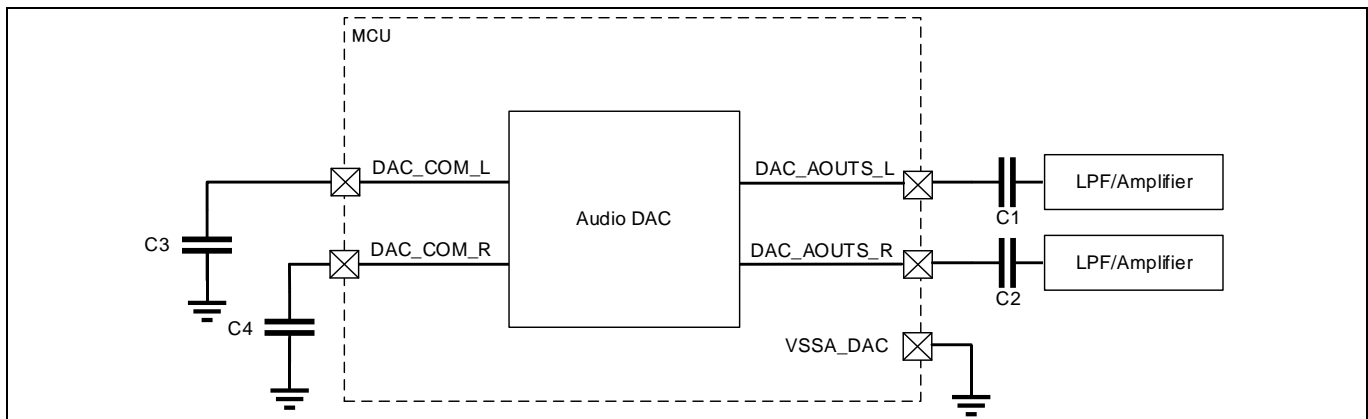


Figure 23 AC coupling connected to LPF and amplifier (application example)

Capacitors:

- C1, C2: 10-nF – 10-μF AC coupling capacitor
- C3, C4: 2.2-μF -10-μF low-ESR capacitors

7.13.3 Unused audio-DAC

When the audio-DAC is not used in the target system or is used only as mono sound output, the related audio-DAC pins are handled as described in [Unused power domains](#) and [Dedicated port pins](#).

7.13.4 Avoiding the pop noise at the speaker output

The audio-DAC and external amplifier will generate a pop noise when a transition from high-to-low or low-to-high occurs on the DAC_EN bit of the DAC0_IF_CTL register during power up or power down.

An external circuitry is recommended, as shown in [Figure 24](#) and [Figure 25](#), to suppress such pop noises if necessary. During audio-DAC start-up, the external amplifier must be either powered down, or in mute mode (if mute mode is available). [Figure 24](#) and [Figure 25](#) show examples for audio-DAC use cases.

Ports and non-power pins

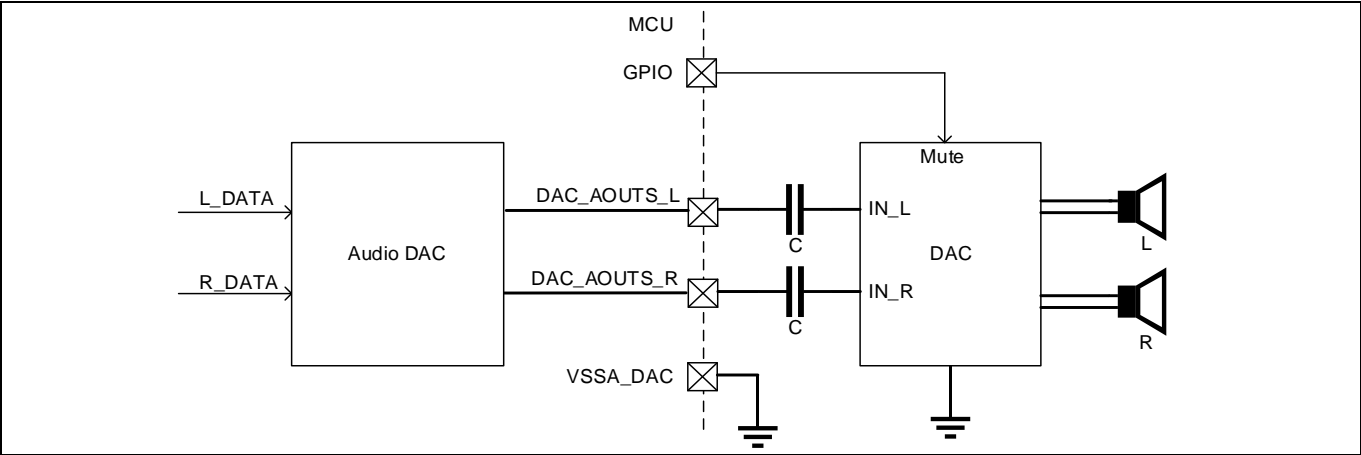


Figure 24 Audio-DAC with single-end mono/stereo output

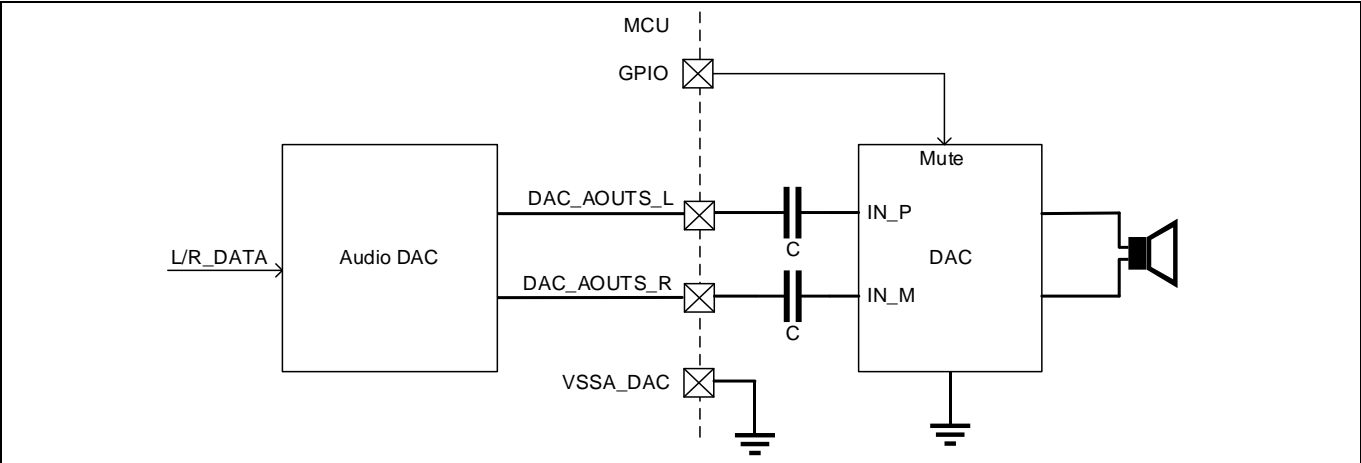


Figure 25 Audio-DAC with differential mono output

Flash programming connection

8 Flash programming connection

Flash programming can be done with the JTAG/SWD connection. Due to this fact, no mode pins are available to switch the device into a programming mode after power-on reset. See [Debug interface](#) for information on the debug connections. There is also the option to use dedicated LIN and the CAN channels for mass production programming.

Debug interface

9 Debug interface

There are several options to connect the debug system to the MCU depending on the debug requirements and the tool chain support. The following are the debug connectors:

- Legacy 20-pin IDC JTAG connector
- 10-pin Cortex® debug connector
- 20-pin Cortex® debug + ETM connector

In all these connectors, the JTAG and SWD signals are shared. The differences are indicated by marking the serial wire debug (SWD) protocol signals in blue. For more information on the interface signals, see Chapter 11 of the [CoreSight Components Technical Reference Manual](#). A short overview is given in [Table 8](#).

Table 8 Overview of SWD and JTAG interfaces

Item	JTAG	SWD
Pin count	4	2
Functionalities	Programming Debugging Boundary scan	Programming Debugging
Topology	Daisy-chained	Star
Extra features	N/A	Print out debug info

9.1 Legacy 20-pin IDC JTAG connector

The legacy JTAG interface is used for flash programming and debugging. The RTCK JTAG signal is not available on the MCU. Additionally, the SWD signals can be shared.

Note: The JTAG interface terminates in a 20-way, 2.54-mm-pitch IDC connector (for example, Hirose HIF3FC-20PA-2.54DSA).

 


Figure 26 Legacy 20-pin IDC JTAG Connector

9.2 10-pin Cortex® debug connector

To use the SWD debug interface, a 10-pin MIPI connector is defined with the minimum number of signals, which are required for debugging. The JTAG interface signals are replaced by the bidirectional data signal (SWDIO) and the clock signal (SWCLK). The freed-up TDO signal can be reused as a system trace data output serial wire output (SWO).

Note:

Debug interface

1. For the SWD debugging a 10-way connector with 1.27-mm pitch is applied (for example, Samtech FTSH-105-01-L-DV-K).
2. Position 7 (KEY) has no pin and serves only as a key to properly orient the connector.

 


Figure 27 10-pin Cortex® debug connector

9.3 20-pin Cortex® debug + ETM connector

Beside JTAG debugging and SWD debugging, this connector is used to connect a signal trace probe for the embedded trace macrocell (ETM) instruction trace operations.

Note:

1. As a connector, a 20-way 1.27-mm-pitch IDC-connector is applied (for example, Samtech FTSH-110-01-L-DV-K).
2. Position 7 (KEY) has no pin and serves only as a key to properly orient the connector.

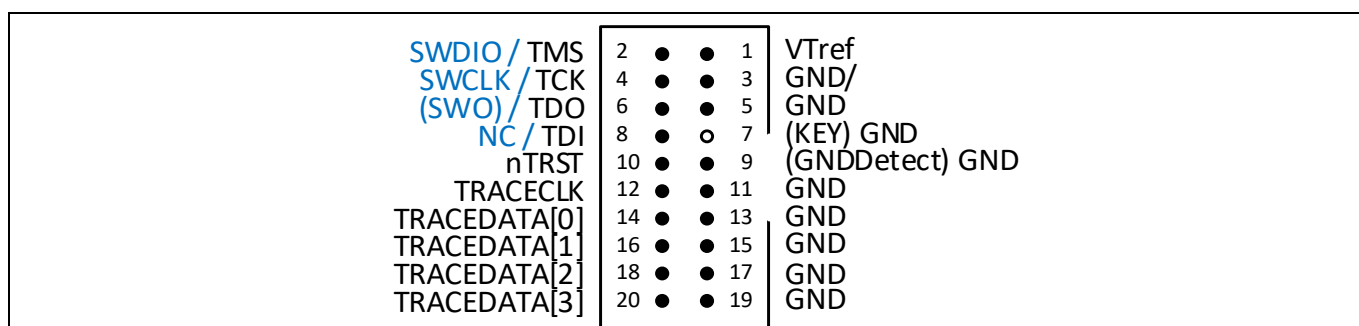


Figure 28 20-pin Cortex® debug + ETM connector

9.4 Termination resistors

In general, the debug connection needs termination resistors for a proper communication. External termination resistors should not be required for this MCU, because after POR, by default, the JTAG interface is enabled in the boot ROM. If externals are applied on the board, each external signal termination must in the same direction as it is done in the device implementation. Although the JTAG interface is enabled by after reset, the SWD mode can be enabled afterward by establishing the SWD connection.

Table 9 Termination resistor for debug interface

JTAG mode	SWD mode	Signal	Required termination resistor (if N/A in the MCU)	MCU implementation
TCK	SWCLK	Clock into debug core	10 k–100 kΩ pull-down resistor to GND	Pull-down resistor
TDI	-	JTAG test data input	10 k–100 kΩ pull-up resistor to V _{DDIO}	Pull-up resistor

Debug interface

JTAG mode	SWD mode	Signal	Required termination resistor (if N/A in the MCU)	MCU implementation
TDO	SWO (optional)	JTAG test data output, SWV trace data output	10 k–100 kΩ pull-up resistor to V_{DDIO}	None. Termination, push-pull driver implemented.
TMS	SWDIO	JTAG test mode select, SWD data in/out	10 k–100 kΩ pull-up resistor to V_{DDIO}	Pull-up resistor
nTRST	–	JTAG TAP reset (active LOW)	10 k–100 kΩ pull-up resistor to V_{DDIO}	Pull-up resistor
GND	GND	Connection to the system ground	–	–

Figure 29 and **Figure 30** show how to connect the debug connector to the MCU. In general, it is recommended to place a series resistor (R16) closer to the connector to avoid reflections and ringing of the debug clock signal. Otherwise, with strong oscillations during level settlement, the debug interface can interpret the wrong data. It must be considered that due to the internal termination resistor, a possible voltage divider in the debug clock signal might be created.

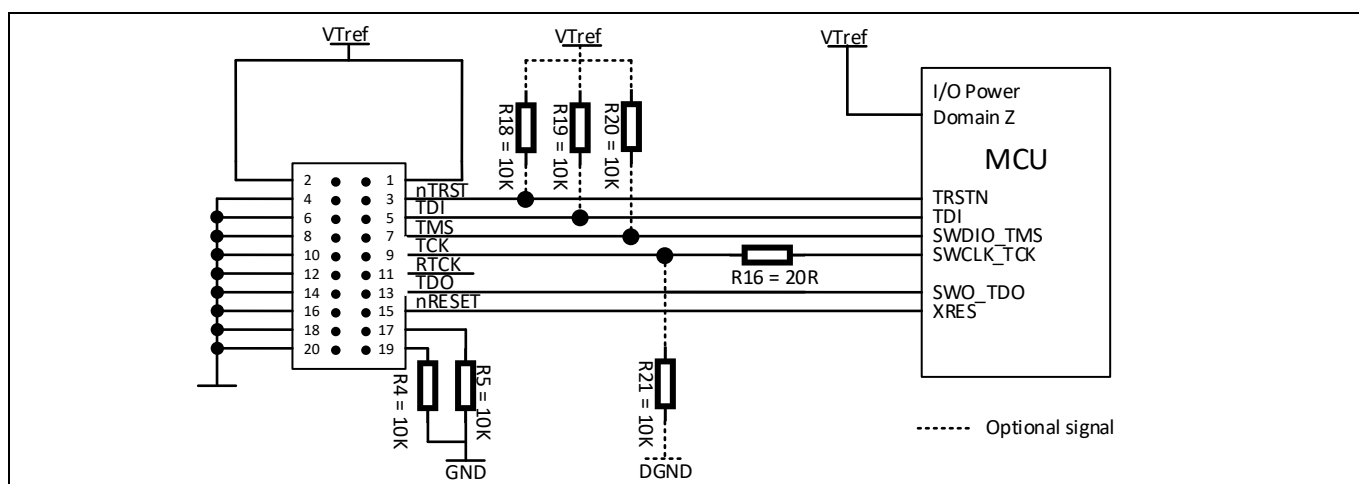


Figure 29 JTAG debug connection to the MCU with 20-pin IDC connector

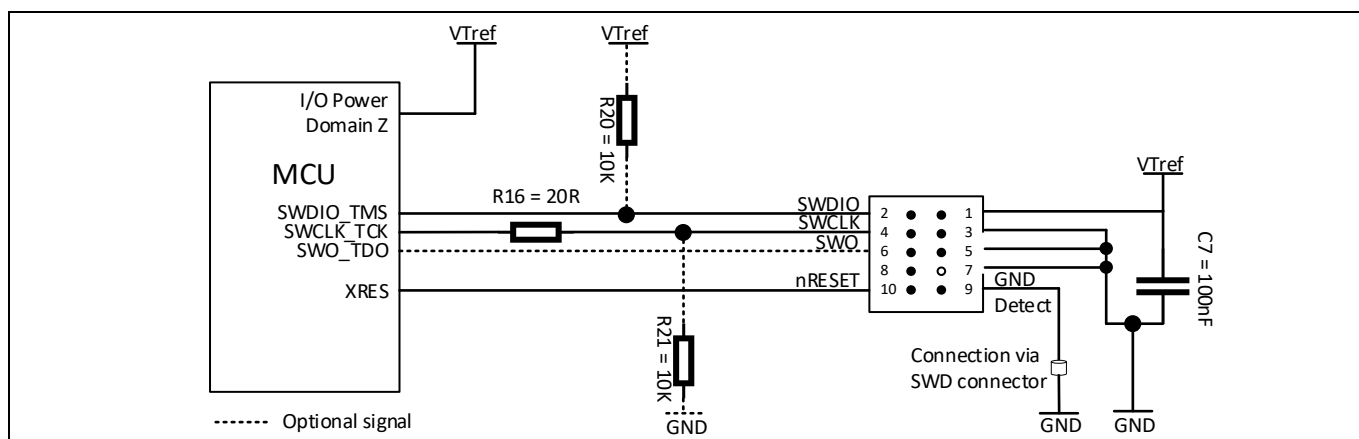


Figure 30 SWD debug connection to the MCU with 10-pin MIPI SWD debug connector

Debug interface

1. *When SWD is used as the debug interface instead of JTAG, there is a time slot after reset and in between boot ROM and user pin configuration in which unused JTAG pins are configured according to JTAG communication. When these unused JTAG pins are used in an application, make sure that the peripherals on the ECU are not negatively affected.*
2. *It is recommended to check the debug connection that is supported by the vendors for flash programming and debugging. Also, check for the target board supply and the supported power supply level of the vendor's hardware. In the case of a power supply mismatch, an adapter is required.*
3. *Boundary-scan is supported only on JTAG interface, not on SWD.*

Clock output function

10 Clock output function

You might need to cross-check the MCU internal clock signals for evaluation purposes. You can cross-check with the following options:

- EXT_CLK port pin
- Alternate output function pin

10.1 Using the EXT_CLK port pin

Internal clocks can be routed through a divider to the alternate function port pin EXT_CLK as the clock output function. It must be taken into consideration that the event generator macro (EVTGEN) and EXT_CLK are driven by the same internal clock signal (CLK_HF1). Therefore, when the divided ECO signal should be observed at the EXT_CLK pin, the EVTGEN macro is also driven with the ECO clock accordingly. This may have an impact on the application. The EXT_CLK pin is a bidirectional pin and can be also used as an external clock source. See [Clock system](#) for more information about this pin.

As the MCU clock output functionality drives the fast digital signal, this signal must be routed far away from the analog input and the analog voltage reference signals.

10.2 Using the alternate function pin

The system clocks can be implicitly observed by using a PWM signal coming from a TCPWM output channel for instance. It must be taken into consideration that each TCPWM channel input clock is derived by a dedicated clock divider of the peripheral clock. See the “Clocking system” chapter in the TRM for details on the clock tree.

11 Layout and electromagnetic compatibility

11.1 General

To avoid ESD problems and noise emission of the system, consider some rules for the layout design.

The most critical point is the VCCD pin, as this is the connection to the internal supply for the MCU core. The required decoupling capacitors (decaps) must be placed as close as possible to this pin. Usually a bigger buffer or bypass capacitor of μF range is added to the dedicated power domain to bypass the period of time until the capacitors are recharged again. Otherwise, decaps and finally the system fall below the power supply operating range.

As the MCU has different digital supply rails, routing of power supply traces must be done carefully. Supply traces should be routed in a star shape or as digital plane in the middle layer. A digital ground plane in the middle layer or on the mounting side just under the MCU is recommended. Decoupling capacitors should be assembled as near as possible to the related pins. If these capacitors are placed too far away, their functionality is diminished.

If possible, all decoupling capacitors should be placed on the same mounting side as the MCU. Alternatively, the decaps could be placed on the bottom layer below the paired power supply pins (for example, VDD/VSS pair).

The analog supply should be decoupled from the digital supply and a common-ground star point should be placed as far as possible from the MCU. In the hardware design, make sure that no latch-up effect between the digital and analog supply or between analog and digital ground can occur. Therefore, the impedance between the different VSS pins and between analog ground and analog reference input must be as low as possible.

11.2 Power supply pins

For proper operation of the MCU decaps and bypass capacitors are needed for the power supply pins. See [General](#) regarding recommendations about the placement of the decaps.

11.3 Ground and power supply

For a multi-layer PCB, the power supply rails and ground should be routed as a plane in the inner layers of the PCB. Considering a layer stack with several power supply planes, these planes should not overlap to avoid noise coupling.

Here are some recommendations for good EMC behavior:

- Use a multi-layer PCB.
- Use power supply planes (ground and power) in the inner-layer of the PCB layer stack.
- Place one or two decoupling capacitors close to each corresponding supply pin pair to reduce possible radiation.
- Use capacitor groups to match the frequency behavior of power supply decoupling. The decoupling capacitors can have values between 1 nF and 10 μF .
- Make sure that only one common star point connects analog and digital ground planes to each other. To have less noise on the analog part, the star point should be placed as far as possible from the MCU and as close as possible to the voltage regulator capacitor with respect to the electronic control unit (ECU) connector.
- Make sure that the digital and analog planes do not overlap and interfere. Furthermore, there should be no signal plane between these planes.

Layout and electromagnetic compatibility

- Shield the analog input signals by the analog ground as much as possible.
- Avoid ground loops.
- Make sure that the supply traces with a layer changeover have at least two vias.

Figure 31 shows an example of a bad PCB layer stack, as there might be crosstalk between different power supply planes. However, **Figure 32** is an example of a well-designed PCB layer stack in which the analog and digital supply planes are separated in the common layer. Thus, the EMC behavior of the board is already improved.

 


Figure 31 Example of a bad PCB layer stack

 


Figure 32 Example of a good PCB layer stack

11.4 Power supply decoupling

11.4.1 Placement

In general, the decaps should be placed as close as possible to the MCU. When a small ceramic capacitor is used together with a large electrolytic capacitor for decoupling, place the ceramic capacitor closer to the MCU power supply rail than the electrolytic capacitor.

Decaps for power supply must be placed within the current flow. If not, they provide no benefit as their function becomes less efficient as shown in **Figure 33**. As the description is valid for generic use, as shown in **Figure 33** to **Figure 35**, the generic naming convention for power supply pins is VCC; for ground pins, it is VSS.

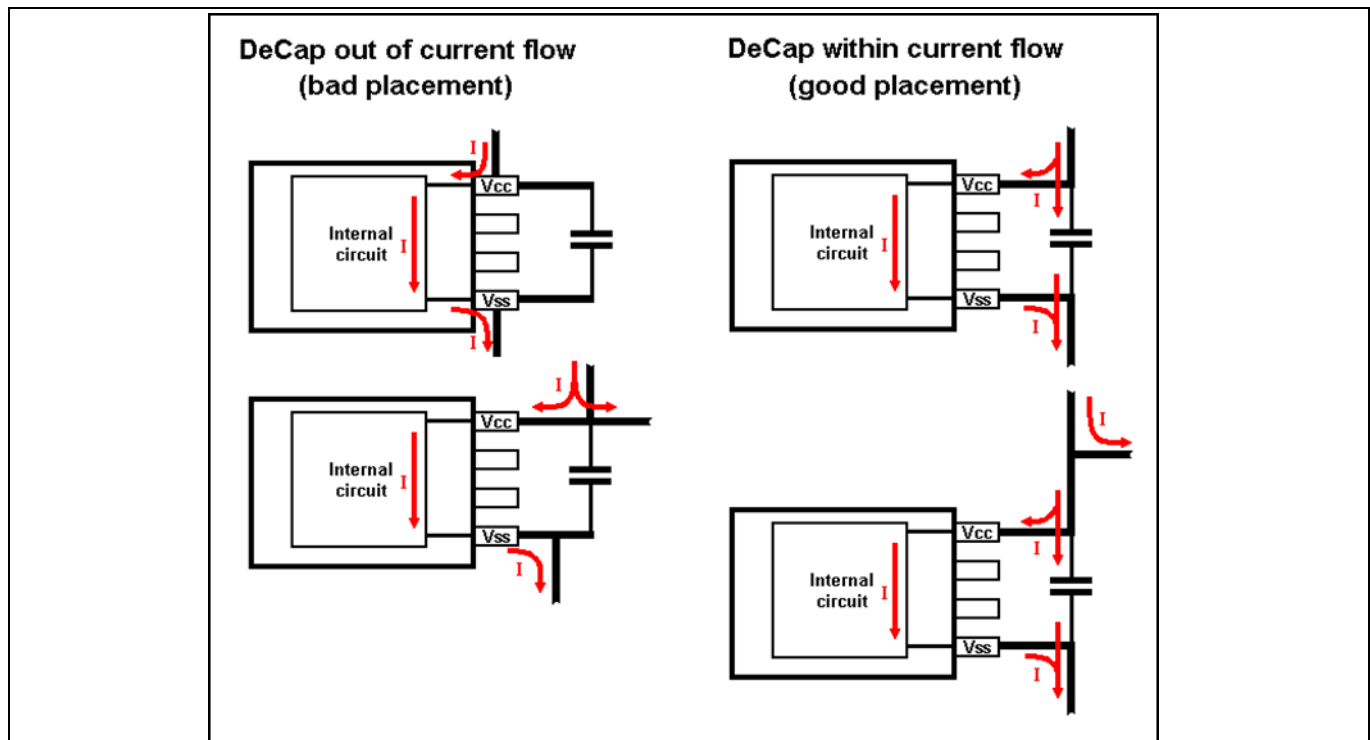


Figure 33 Power supply decoupling capacitor placement

Usually the noise current should flow through the soldering pad of decoupling capacitor CB. [Figure 34](#) shows the recommended routing and placement on the boards.

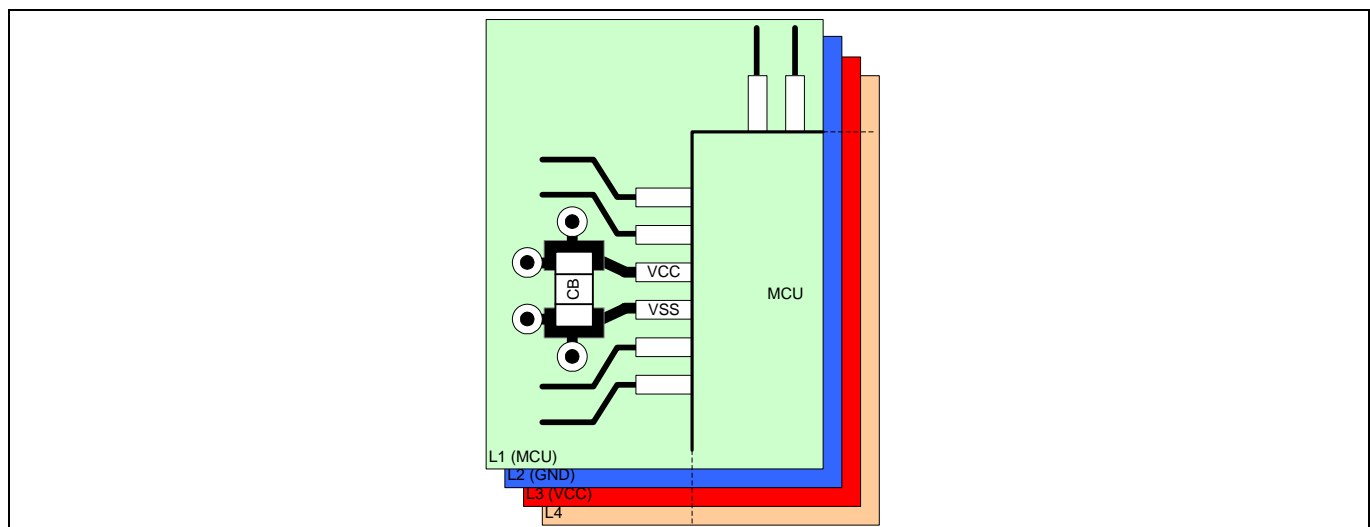


Figure 34 Recommended power supply decoupling on boards

[Figure 35](#) shows an alternate, but not recommended routing and placement. Note that the capacitor is placed on the opposite PCB side like the MCU. This solution works best for high-density board assembly.

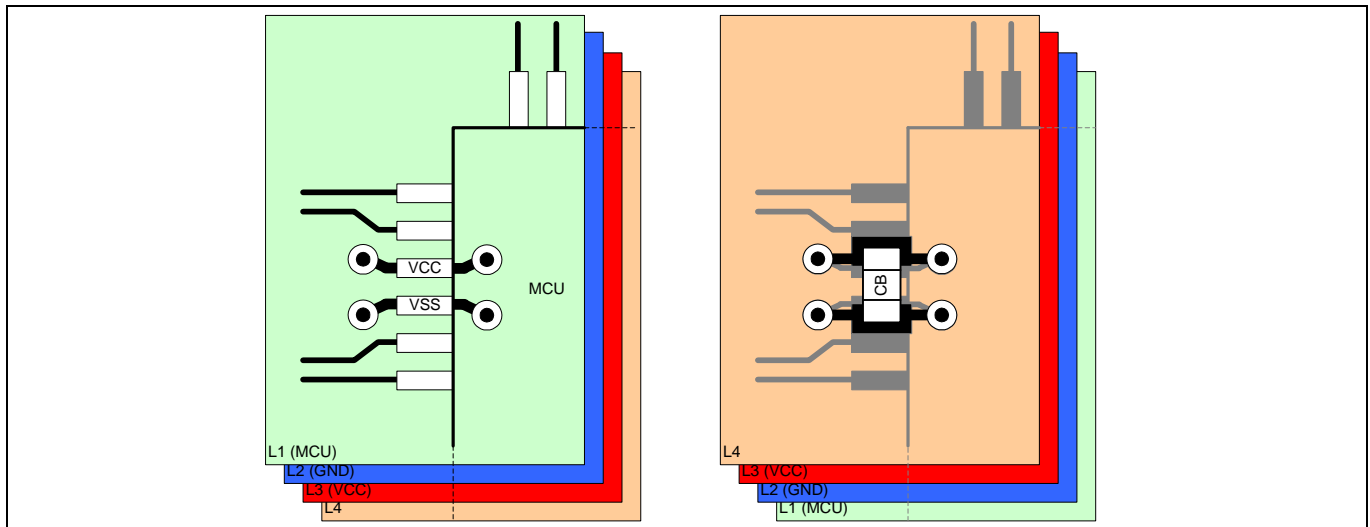


Figure 35 Alternate power supply decoupling on boards

11.4.2 I/O domains

The dimensioning of the decaps and bypass capacitors for the I/O domain is application-specific. The following are some points to be considered while dimensioning:

- How is the switching behavior (periodic or random) of the output stages and what is the transition requirement?
- How many outputs have the same transition at the same time during the running operation or after any wakeup or reset?
- How big is the capacitive load at one output pin?
- Which driver strength configuration is selected?
- Is there any DC current caused by resistors which might be also buffered by a big bypass capacitor?

It is strongly recommended to make either a power distribution network (PDN) analysis with an according model (IBIS or lumped model) or test on the PCB. A simplified consideration about the decoupling is provided in the [SRAM board design guidelines](#).

11.5 Quartz crystal placement and signal routing

The MCU provides two pierce oscillators implementations with an embedded feedback resistor (R_f) for the ECO and external watch oscillator (WCO). You can enable both oscillators by software. It means that the MCU starts the boot process from an internal clock source.

Note: [Figure 36](#) to [Figure 39](#) showing the implementation of oscillators in the MCU family and the trimming features discussed in this application note might differ from the dedicated device architecture TRM. Due to different trimming features, the external BOM cost can be reduced in the ECU design.

11.5.1 Setup

[Figure 36](#) shows the principle of an external oscillator circuit. The feedback resistor (R_f) is required to act is necessary for the inverter to act as amplifier. Optionally, a damping resistor (R_d) is required for drive level (DL) reduction. If the DL is too strong, the crystal can be damaged over the life time. The load capacitance C_L is the

Layout and electromagnetic compatibility

terminal capacitance and is connected to the crystal. Thus, C_L includes the external capacitors C1 and C2 and the stray capacitance C_s . C_s comes from the PCB layout, manufacturing tolerances, and the oscillator MCU pins. As the stray capacitance is usually ~4 pF for each signal line, the value of both load capacitors (C1 and C2) should be determined with a crystal matching test. This test must always be done by the crystal manufacturer when there is any change on the target board affecting the oscillator circuit.

Load capacitance (C_L)

$$C_L = \frac{C1 \times C2}{C1 + C2} + C_s$$

Equation 4

Note:

1. The oscillator pins are shared with standard GPIO pins, which automatically leads to additional load capacitance in the oscillator circuit. This must be considered with regards to external load capacitors.
2. For details on crystal trimming, see AN230194.

 


Figure 36 Principle setup of an external oscillator circuit

The ECO design is optimized for BOM cost reduction (see [Figure 37](#)). This is realized by a scalable DL and an embedded Rf implementation. By trimming features, a broad crystal frequency range can be supported. For details, see the “Clock sources” section in the architecture TRM.

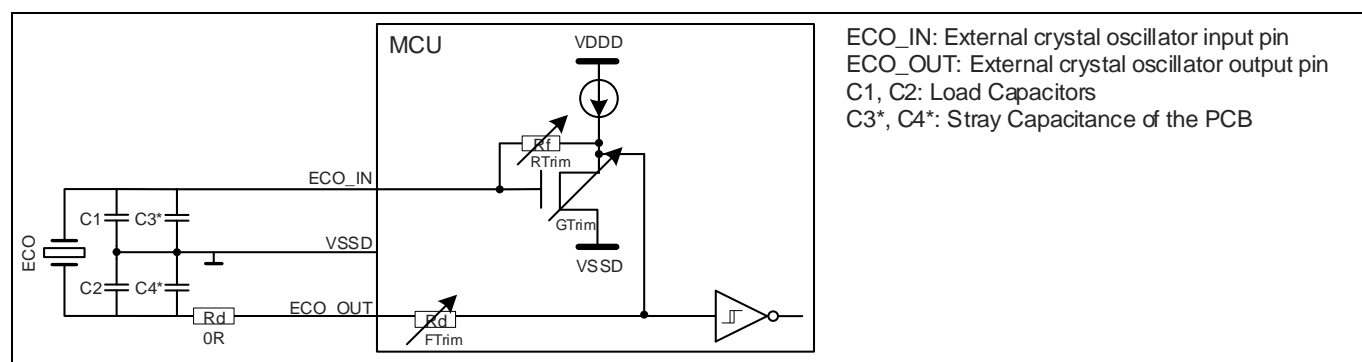


Figure 37 ECO circuit scheme⁷

⁷ Figure might differ from dedicated architecture TRM. Trimming features are not covered 100%.

Layout and electromagnetic compatibility

The WCO implementation scheme is shown in **Figure 38**. Like in the ECO, R_f is embedded to reduce the external BOM cost. An external R_d might be required to avoid damage of the external watch crystal.

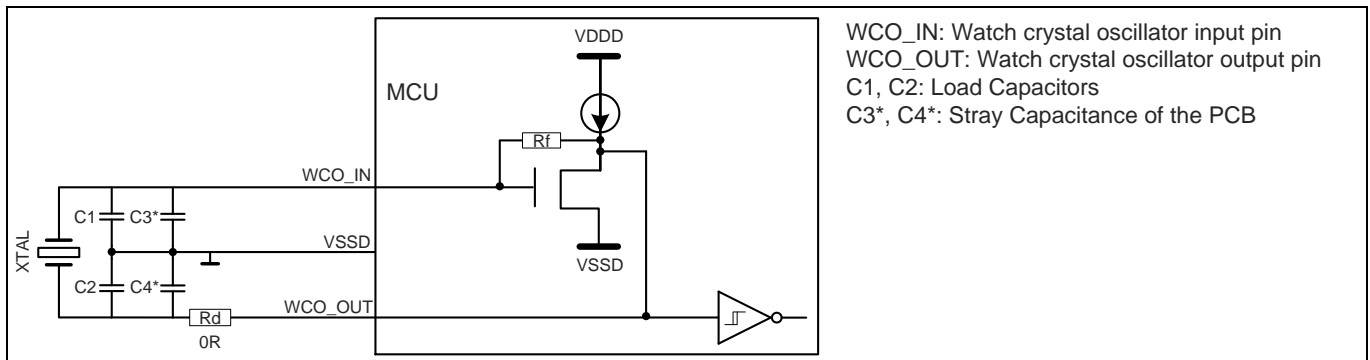


Figure 38 WCO circuit scheme⁷

The LPECO design is optimized for BOM cost reduction (see **Figure 39**). This is realized by a scalable DL and an embedded R_f implementation.

 


Figure 39 LPECO circuit scheme⁷

11.5.2 PCB design

To reduce the impact of EMI, the placement of the external oscillator components and the signal routing must be done carefully. The following should be considered during PCB layouts. Due to design constraints, it might be required to make a tradeoff between the items.

- Stable frequency
 - Place the external oscillator components on the MCU layer.
 - Place the external oscillator components as close as possible to the MCU.
 - Make sure that the connection of load capacitors C1 and C2 to the oscillator ground is in a common star point.
 - Make sure that there is no signal line between both capacitor ground connections.
 - Do not use vias for ground signal routing.
- Noise injection
 - Use a ground layer directly below the MCU.
 - Use a ground shield in the MCU layer and use the neighbor layer as the ground layer.
 - Shield the area of oscillator bonding wires.

Layout and electromagnetic compatibility

- Do not use the ground shield as the oscillator ground signal.
- Avoid ground loops. The oscillator ground signal must be connected at first to VSSD before connecting to the system ground.
- Make sure that the routing of the oscillator ground to VSSD is as short as possible.
- Do not route signals with strong pulses close to the oscillator. This is also valid for the neighbor layer.
- Noise emission
 - Do not route sensitive signals close to the oscillator signals (example: analog sensor signals).

11.6 Component placement

- The placement of analog components should be done in a way that the ground connection is on a common partition area. The same should be also done for digital components. The analog voltage reference regulator should be placed over the analog plane and the digital voltage regulator accordingly over the digital plane.
- Components with a common power supply should be located as centrally as possible to each other.
- The MCU and other mixed signal components should accordingly be placed on the PCB as a bridge between the analog and digital partitions.

11.7 Signal routing

- Digital power and signal traces should be routed over the digital ground planes and analog power and signal traces should be routed over the analog ground plane.
- To isolate analog signals traces, areas around the traces should be filled with copper, which are connected to analog ground plane. Accordingly, the same recommendation is also valid for areas with digital signal traces.
- Do not route traces near to or parallel to other noisy and sensitive traces.
- Keep the trace lengths as short as possible.

Furthermore, when designing an application, the following areas should be closely studied to improve the EMC performance:

- Noisy signals, for example, signals with fast edge times
- Sensitive and high-impedance signals
- Signals that capture events, such as interrupts and strobe signals

Thermal considerations

12 Thermal considerations

Once an indication of the MCU total power requirement is known, it is very important to understand, whether the system design can properly dissipate this power into the ambient air efficiently enough. This determines whether further action or significant heat sinking and PCB design choices is required.

The MCUs cover a wide range of products from devices capable of very low power to MCUs with very fast complex logic requiring higher power needs. Under certain conditions, MCUs may dissipate more than 1 watt of power including the core, peripheral, and I/O currents. With a lot of power in a device, necessary steps must be considered to avoid it from overheating.

Before a design is finalized, a complete thermal review should be done. Items such as the amount of airflow through the system, nearby heat sources, and PCB construction should be reviewed. The examples given below are first steps to determine whether the preliminary design objectives can be met by taking the equation.

Calculation of junction temperature

$$T_J = T_A + \Theta_{JA} \times P_D \quad \text{Equation 5}$$

T_J : Junction temperature

T_A : Ambient temperature

Θ_{JA} : Thermal resistance from junction to ambient

P_D : Power dissipation

For a first-order approximation, first check the datasheet for the thermal resistance from junction to ambient (Θ_{JA}) for the target device package. Θ_{JA} is expressed in units of °C/watt.

For example, the Θ_{JA} for an LQFP 120-pin is 38 °C/watt. For the same device in an LQFP 120-pin package with an exposed pad on the bottom side correctly mounted, the Θ_{JA} is reduced to 18 °C/watt, allowing a much higher total device power usage or a higher ambient operating temperature.

The maximum temperature difference between the device junction and the ambient air surrounding the device is Θ_{JA} times the maximum power, or as in the first case above, 38 °C/watt x 1.0 watt = 38 °C. Because the specified maximum operating junction temperature of the device is 125°C, the maximum allowable ambient air temperature is 125 – 38 = 87 °C. If you use the exposed pad version of package, which has a lower thermal resistance Θ_{JA} of 18°C/watt if implemented with proper PCB to pad design, the maximum allowable ambient air temperature is 125 °C – 18 °C = 107 °C. This allows a 20 °C increase in ambient operating temperature or the possibility to drive more power from the device I/O or core.

Each datasheet for a device series contains a table showing package thermal resistance and maximum permissible power. This allows you to quickly see the amount of power that can practically be consumed by a device in a given package. In the DS, recommended minimal PCB construction might be given. So, for example, a four-layer PCB has a better power dissipation characteristic than a two-layer PCB, because inner plane layers help to dissipate heat.

Note: *The datasheet specifications for Θ_{JA} are typical. The ambient air temperature should be much less than the allowable maximum for the product design.*

Note: *With the above calculation, if the Θ_{JA} or the power dissipated is high, the maximum allowable ambient air temperature could theoretically approach the 125°C junction temperature limit.*

Thermal considerations

However, the product's commercial-range ambient air temperature limit of 85°C or the industrial-range ambient air temperature limit of 105°C still applies. In the example above, the first example would be unacceptable for operating a consumer grade (85°C) device. In the second example, a consumer grade or industrial grade device would be well suited depending on the choice of operating conditions of the final product.

MCUs offered in BGA or QFN packages have a reduced available surface area for thermal conduction due to the small package size; these packages must be thoroughly reviewed for power applications.

Detailed information is provided in the application notes AN72845, AN202751, and AN79938 listed in [Related documents](#).

ADC

13 ADC

This section considers ADC and its analog input (AN) circuit for highly accurate sampling of the analog sensor level and potential other issues.

13.1 Filter design considerations for analog inputs

13.1.1 Principle of acquisition

The full period of sampling the analog value and then the conversion into a digital value is called acquisition time (t_{ACQ}). The voltage level of the analog input is sampled by an internal sample capacitor (C_{VIN}) within a configurable sample time (t_s); the conversion time (t_{CNV}) is implicitly configurable by the ADC clock input.

Figure 40 shows a principle circuit between the sensor, the analog source V_0 , and the analog input.

$$t_{ACQ} = t_s + t_{CNV}$$

Equation 6

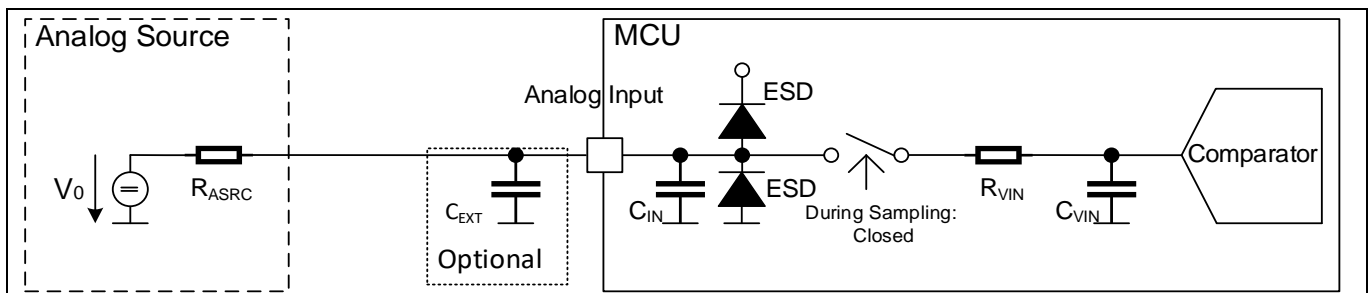


Figure 40 Analog input with optional external buffer capacitor

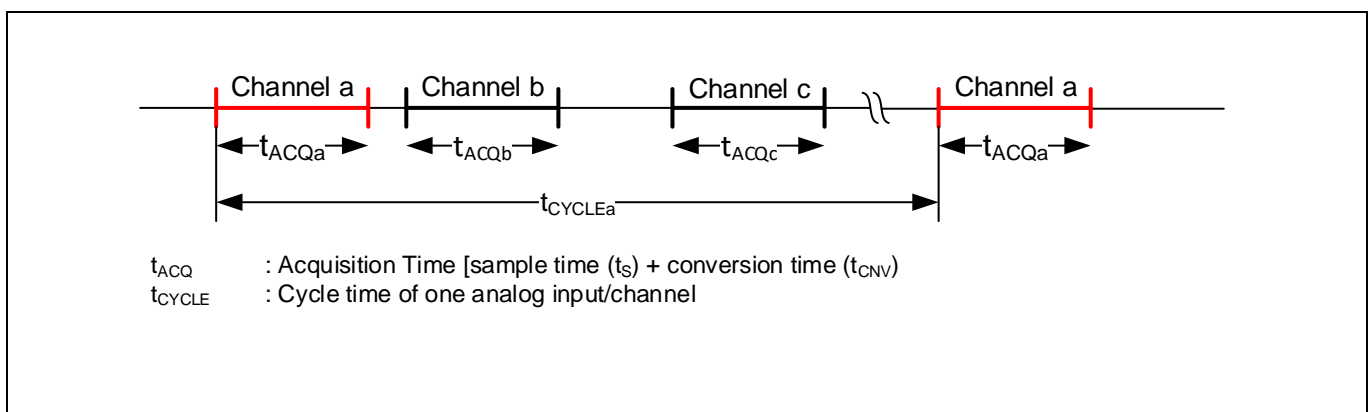


Figure 41 Cycle time of analog channels

13.1.2 Accuracy at sample time

The sample time (t_s) must be long enough for charging C_{VIN} at the same level as the analog source, which means that the internal resistance of the analog source (R_{ASRC}) should be usually small enough. When R_{ASRC} is too high, either the sample time must be longer which has an impact on the total sample rate of all channels or the cycle time (t_{CYCLE}), the period between two acquisitions of a channel, must be longer accordingly (see **Figure 40**). After the cycle time, there should be either no or a neglectable voltage difference between the

ADC

analog source V_0 and the analog input (AN) before the next acquisition. When a channel is sampled twice or more directly one after the other, the following equation must be fulfilled: $t_{\text{CYCLE}} \leq t_{\text{ACQ}}$.

The following are the assumptions to be considered while calculating the cycle time t_{CYCLE} :

- The analog input must be reloaded to a new source level V_0 with a remaining voltage difference V_R depending on the required resolution 2^r . V_R should be smaller than the sampled error.
- The reloading from the external capacitor C_{EXT} to internal sample capacitor C_{VIN} during the sample time extends the cycle time.

$$t_{\text{CYCLE}} = t_S + k \times \tau = t_S + \ln\left(\frac{2^r}{V_{R,\text{LSB}}}\right) \times (R_{\text{ASRC}} \times (C_{\text{EXT}} + C_{\text{IN}})) \quad \text{Equation 7}$$

Example:

Resolution: 12-bit

$$V_{R,\text{LSB}}: 0.25 \text{ LSB} = 0.25 \times (1/2^{12})$$

$$t_{\text{CYCLE}} = t_S + k \times \tau = t_S + \ln\left(\frac{2^{12}}{0.25}\right) \times (R_{\text{ASRC}} \times (C_{\text{EXT}} + C_{\text{IN}})) = t_S + 9.7 \times \tau \quad \text{Equation 8}$$

13.1.3 Sample time charging process

During the sample phase, the sample capacitor C_{VIN} is charged by the external capacitor C_{EXT} until both reach a common voltage (charge balancing). After that, both capacitors are charged to the analog source level V_0 via the source resistance.

So, different time constants must be considered:

- $T_{S,\Delta}$: Time constant at the beginning of the sample time for the charge balancing between C_{EXT} and C_{VIN} .
- $T_{S,\text{REST}}$: Time constant during the sample time, after charge balancing, to charge close to V_0 with an acceptable error.
- T_{CEXT} : Time constant, starting from the conversion time and ending with the next sample phase of the analog input.

 


Figure 42 Charging curve of the analog input during acquisition time

13.1.4 Charge balancing between C_{EXT} and C_{VIN}

Depending on the ADC macro implementation, the sample capacitor can be precharged to a target level ($C_{VIN,PRE}$) before starting the sample phase. If this feature is not deployed, C_{VIN} will have the voltage level of the previous acquisition, which means that in the worst case, the maximum voltage difference ($\Delta V_{C_{VIN},PRE}$) between C_{VIN} and the external capacitor C_{EXT} corresponds to the analog reference voltage V_{REFH} . When the sample switch is closed, charge balancing between the external capacitor C_{EXT} and the sample capacitor C_{VIN} causes a voltage drop at the analog input $V_{AN,D}$.

$$V_{AN,D} = \frac{Q_{VIN}}{(C_{IN} + C_{EXT}) + C_{VIN}} = \frac{C_{VIN} \times (V_0 - V_{VIN,PRE})}{(C_{IN} + C_{EXT}) + C_{VIN}} = \frac{C_{VIN} \times \Delta V_{VIN,PRE}}{(C_{IN} + C_{EXT}) + C_{VIN}} \quad \text{Equation 9}$$

In a simplified consideration of [Equation 9](#), the analog input and the analog source have the same voltage level $V_{AN} = V_0$, resulting in [Equation 10](#).

ADC

$$V_{AN,D} = \frac{Q_{VIN}}{(C_{IN} + C_{EXT}) + C_{VIN}} = \frac{C_{VIN} \times (V_0 - V_{VIN,PRE})}{(C_{IN} + C_{EXT}) + C_{VIN}} \quad \text{Equation 10}$$

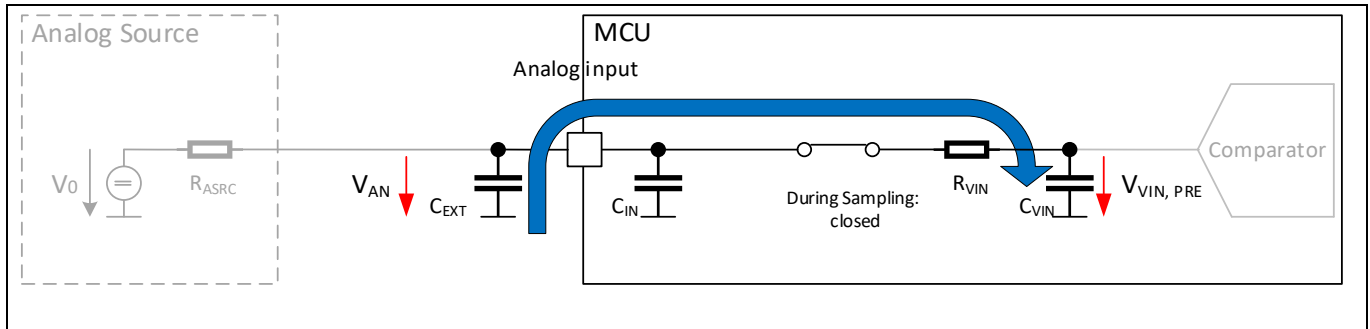


Figure 43 Charge balancing during ADC sample time

While this charge balancing happens, it is assumed that $R_{ASRC} \gg R_{VIN}$, and therefore R_{ASRC} has no impact during that phase. This results in the following time constant $\tau_{s,\Delta}$ for charging the capacitor:

$$\tau_{s,D} = R_{VIN} \times C_{SUM} = R_{VIN} \times \left(\frac{1}{1/(C_{EXT} + C_{IN}) + 1/C_{VIN}} \right) \quad \text{Equation 11}$$

Thus, in the worst-case scenario for the maximum voltage difference between analog input and the sample capacitor after $9.7 \times \tau_{s,D}$, the voltage error of the analog input is less than 0.25 LSB_{12} .

13.1.5 Charging the analog input by the analog source V_0

Depending on the dimensioning of the external capacitor C_{EXT} , charge balancing between C_{EXT} and C_{VIN} causes a huge voltage difference in the analog input in relation to the analog source V_0 . The analog input must be charged by V_0 itself directly. In this case, the analog source resistance R_{ASRC} has a relevant influence for the charging curve.

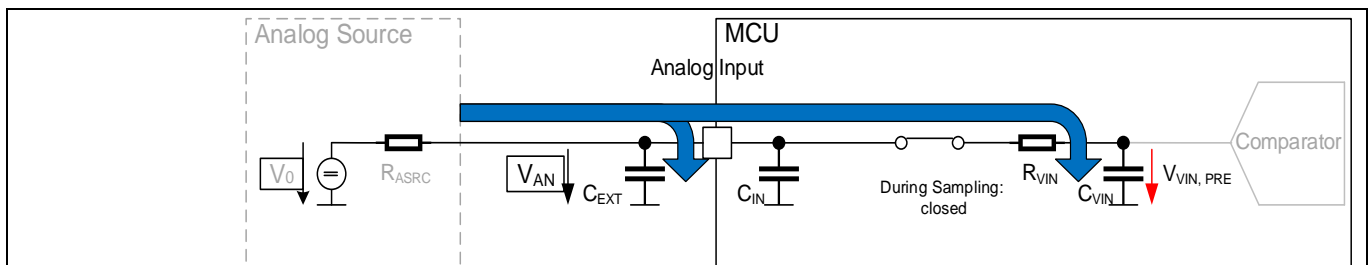


Figure 44 Charging of the analog input during the sample time by the analog source V_0

Thus, for the rest of the sample time, the time constant $\tau_{s,REST}$ is calculated as follows:

ADC

$$\tau_{S,REST} = (R_{VIN} + R_{ARSC}) \times C_{VIN} + R_{ARSC} \times (C_{EXT} + C_{IN})$$

Equation 12

13.1.6 Filter case: $C_{EXT} > 2^r * C_{VIN}$

When the analog source impedance is too high, the sampling period for analog voltages may be insufficient, especially when all analog input needs to be sampled with a common high sample rate (for example, 1 MS/s). If the cyclic sampling of the dedicated analog input, the cycle time (t_{CYCLE}), can be much longer, a big external buffer capacitor C_{EXT} can be deployed. The dimensioning considers the maximal target error at the sampled analog input $Error_{AN}$.

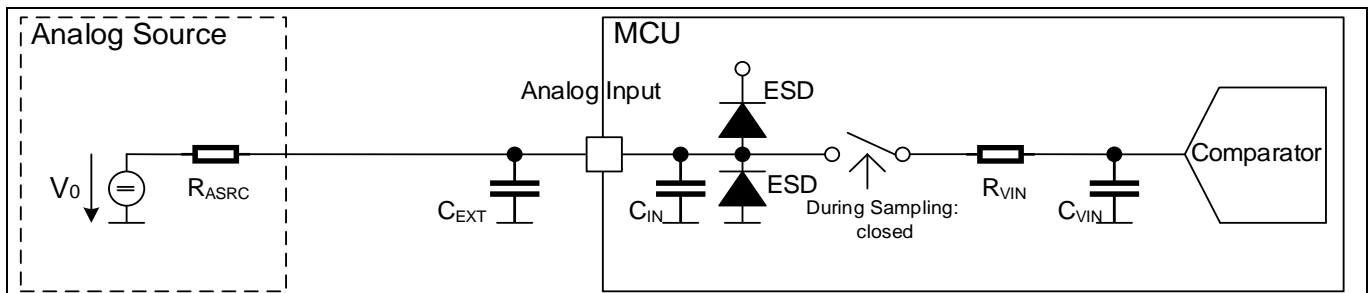


Figure 45 Analog input with decoupling capacitor against internal switching noise

 


Figure 46 Simplified cyclic charge Curve of C_{EXT} for use case $C_{EXT} > 2^r * C_{VIN}$

At first, the maximum permitted error $Error_{AN}$ must be defined as shown in [Equation 13](#).

ADC

$$Error_{AN} = 1/2^E \times LSB_r$$

Equation 13

with:

$r = 12$: 12-bit resolution $E = 0$; $Error_{AN} = 1 \text{ LSB}_r$

$r = 12$: 12-bit resolution $E = 1$; $Error_{AN} = \text{LSBr} / 2$

$r = 12$: 12-bit resolution $E = 2$; $Error_{AN} = \text{LSBr} / 4$

$$C_{EXT} = 2^{r+E} \times C_{VIN}$$

Equation 14

To achieve a sampling error of less than 0.25 LSB ($E = 2$) at 12-bit resolution ($r = 12$), the minimum external filter capacitor C_{EXT} is as shown in [Equation 15](#).

$$C_{EXT,0.25LSB} \geq 2^{r+E} \times C_{VIN} = 2^{12+2} \times C_{VIN}$$

Equation 15

Due to the selection of $C_{EXT} > 2^r \times C_{VIN}$, the sample time t_s can be selected independently of the analog source R_{ASRC} . Nevertheless, R_{ASRC} has a direct impact to the cycle time t_{CYCLE} .

13.1.7 Discrete RC filter

If an extended sample time is insufficient to filter the noise on the analog signal input, you can use an external low-pass filter (RC filter) to the analog input pin (see [Figure 47](#)). Cross-check the possible sample period with the cut-off frequency of the RC filter. Furthermore, the voltage drop at R_{EXT} due to the complete leakage current of the analog input must not be higher than the required accuracy of the measured analog signal.

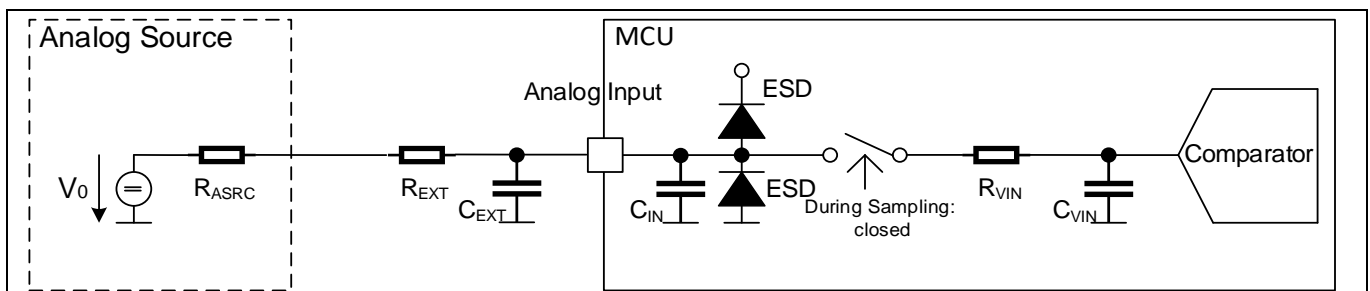


Figure 47 Analog input with low-pass filter

14 Assembly and package-related PCB design

The application notes AN202751 and AN79938 provided guidelines on surface mount assembly for different BGA packages, related PCB design, surface mount process flow, and final joint inspection methods.

Video interface

15 Video interface

15.1 FPD-Link

15.1.1 Signal pin configuration

The FPD differential data output signal pairs FPDx_TyP/N can be freely configured. This provides the advantage of avoiding signal pair crossing by changing the PCB layers for signal routing to the display connector. However, the FPD clock signal pair is on fixed pins.

15.1.2 Power domain VDD_PLL

The PLL power domain, VDD_PLL, of the FPD-Link is very noise sensitive, which can result in erroneous FPD-Link communication due to jitter. Thus, the following countermeasures are required to fulfill a silent power supply input:

- External filter
- Nearby signals that do not cause crosstalk (for example, I/O signals)

Note: In the CYT3DL 216-TEQFP package, when in parallel, FPD-Link and port pins P.16.5 and P16.6 are used. Both pins must be only for noiseless I/O function (for example, a control signal with low driver strength).

15.2 RGB interface

15.2.1 Signal pin configuration

As the pin names of the RGB interface are not 100% clear with regard to the functional assignment, [Figure 48](#) shows the flexibility in functional assignment for the bypass mode, the “standard” GPU display mode. In the following sections, the signal group routing is described.

Pixel clock: The pixel clock is routed directly to the TTL_DSPx_CLOCK pins.

Frame timing signals (HSYNC, VSYNC, DE): Each signal is routed through the signal generator of the GPU to several TTL_DISPx_CONTROL[y] pins. This provides additional flexibility and is the recommended approach for the functional pin assignment.

If instead of 24-bit RGB only 18-bit RGB is in use, it is also possible to map the control signals via the map bit (MB) MUXer to one of the TTL_DISPx_DATA0/1[y] pins. This option is only available, because the MB MUXer is actually responsible for the bit mapping of all RGB signals for FPD-Link, which is not part of this chapter.

RGB color signals: The color signals can be routed freely to TTL_DISPx_DATA0/1[y]. This flexible pin assignment provides the chance to avoid signal crossing on the PCB to the display connector.

Video interface

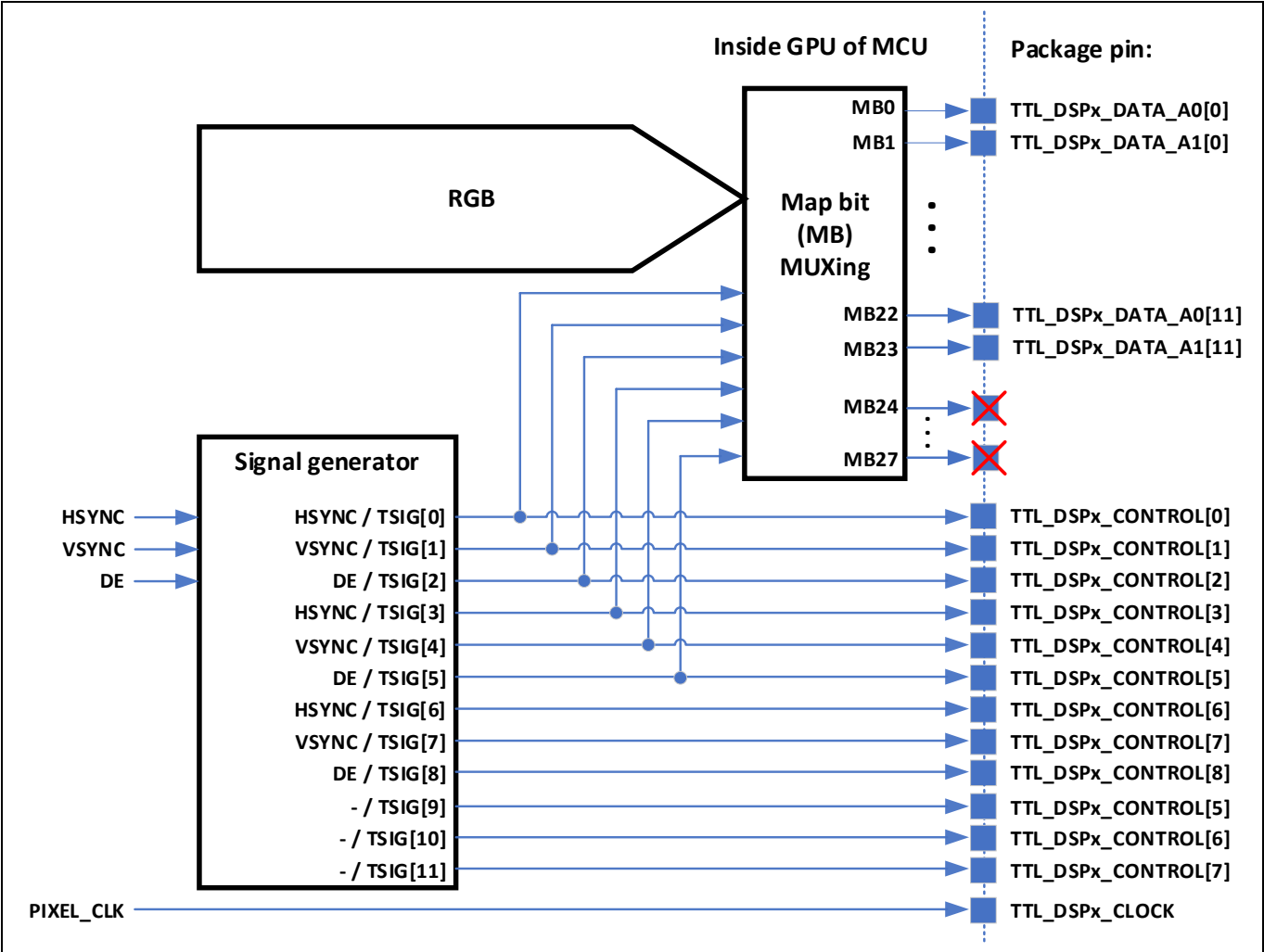


Figure 48 Internal RGB signal routing from GPU to package pins

Summary

16 Summary

The application note described how to set up a minimum MCU system. The application note also provided hints on how to handle different uses cases at MCU pins and how to make a proper PCB layout design.

Abbreviations

17 Abbreviations

Abbreviation	Description
ADC	A/D converter
ALT	alternate
AN	analog input
BOD	brown-out detection
BOM	bill of material
Cap	capacitor
DAP	debug access port
decap	decoupling capacitor
DDR	double data rate. Data sampled twice within a clock cycle. fDATA = fCLK
DE	display enable
DS	datasheet
DUT	device under test
ECU	electronic control unit
ETM	embedded trace macrocell
Ext	external
GND	electrical ground
GPIO	general purpose I/O
HVD	high-voltage detection
HSYNC	horizontal synchronization
IC	integrated circuit
IF	interface
Int	internal
IO	input output
JTAG	Joint Test Action Group is the common name for the IEEE 1149.1 Standard Test Access Port, Boundary-Scan Architecture, and interface for debug tools for on-chip debug inside the target MCU
LDO	low drop-out line regulator
LPF	low-pass filter
LVD	low-voltage detection
LU	latch-up
MAC	media access control. Component independent from communication medium.
MB	map bit
MCU	microcontroller
MCU	microcontroller unit
PDN	power distribution network
PHY	PHYSical layer. Electrical component for data coding and decoding between pure digital and modulated channel
PMIC	power management IC

Abbreviations

Abbreviation	Description
SDR	single data rate. Data sampled only once within a clock cycle. $f_{DATA} = \frac{1}{2} \times f_{CLK}$
S/s	samples per second
NC	not connected
OCD	overcurrent detection
OVD	overvoltage detection
PCB	printed circuit board
POR	power-on reset
Rd	damping resistor
Rf	feedback resistor
STP	shielded twisted pair
SWD	serial wire debug
TRM	technical reference manual
VCC	Generic naming convention for power supply pin
Voltage droop	transient voltage drop
VSS	Generic naming convention for ground pin
VSYNC	vertical synchronization
WDT	watchdog timer

Related documents

18 Related documents

- AN230194 – Setting ECO parameters
- AN224153 – Design and layout guide for SEMPER™ NOR flash memory
- AN233447 – Power filter options for FPD-Link interfaces for the TRAVEO™ T2G family
- [AN79938](#) – Design guidelines for Infineon ball grid array (BGA) packaged devices
- [AN202751](#) – Surface mount assembly recommendations for Infineon FBGA packages
- [AN213250](#) – Power filter options for FPD-Link interfaces
- AN226698 – External power supply design guide for TRAVEO™ T2G family CYT4BF000 series
- AN220118 – Getting started with TRAVEO™ T2G family
- [AN72845](#) – Design guidelines for QFN packaged devices
- [AN89611](#) – PSoC™ 3 and PSoC™ 5LP getting started with chip scale packages
- [AN80994](#) – Design considerations for electrical fast transient (EFT) immunity
- [AN57821](#) – PSoC™ 3, PSoC™ 4, and PSoC™ 5LP mixed signal circuit board layout considerations
- AN220222 – Low-power mode procedure in the TRAVEO™ T2G family
- [ARM_Link_01](#) – CoreSight components technical reference manual (Cortex® debug connector detailed specification in Appendix C)
- [ARM_Link_02](#) – Cortex®-M debug connectors
- [SRAM board design guidelines](#)
- Device datasheet
 - CYT2B7 datasheet 32-bit Arm® Cortex®-M4F microcontroller TRAVEO™ T2G family
 - CYT2B9 datasheet 32-bit Arm® Cortex®-M4F microcontroller TRAVEO™ T2G family
 - CYT4BF datasheet 32-bit Arm® Cortex®-M7 microcontroller TRAVEO™ T2G family
 - CYT4DN datasheet 32-bit Arm® Cortex®-M7 microcontroller TRAVEO™ T2G family
- CYT2B series
 - TRAVEO™ T2G automotive body controller entry family architecture technical reference manual (TRM)
 - TRAVEO™ T2G automotive body controller entry registers technical reference manual (TRM) for CYT2B7
 - TRAVEO™ T2G automotive body controller entry registers technical reference manual (TRM) for CYT2B9
- CYT4B series
 - TRAVEO™ T2G automotive body controller high family architecture technical reference manual (TRM)
 - TRAVEO™ T2G automotive body controller high registers technical reference manual (TRM)
- CYT4D Series
 - TRAVEO™ T2G automotive cluster 2D family architecture technical reference manual (TRM)
 - TRAVEO™ T2G automotive cluster 2D registers technical reference manual (TRM)

Contact [Technical support](#) to obtain TRAVEO™ T2G family series datasheets and technical reference manuals.

Appendix A – Power supply concept

19 Appendix A – Power supply concept

19.1 Introduction (key note)

The appendix provides the MCU-specific proposals for a power supply concept including decoupling capacitors for the MCU power supply.

Note: The deployment of decoupling caps and the bypass capacitors depend on the application and is in full responsibility on the customer side. The bypass capacitors usually do not suffice to cover a PMIC load response. This is especially valid for I/O supplies. For more information, see [I/O domains](#).

Note: By default capacitors with X7R temperature characteristic should be used.

19.2 Definitions

- f_{CLK} : Clock signal frequency
- f_{DATA} : Data signal frequency
- SDR: Single data rate. Data sampled only once within a clock cycle. $f_{DATA} = \frac{1}{2} \times f_{CLK}$
- DDR: Double data rate. Data sampled twice within a clock cycle. $f_{DATA} = f_{CLK}$
- ‘Pin’: Synonym for the original pin name
- Domain: Power domain. One power domain can have one or more power pins (for example, VDDD has several pins)
- Voltage drop: Transient voltage drop

 


Figure 49 Equivalent RLC low-pass filter composition

Appendix A – Power supply concept

19.3 CYT2B series

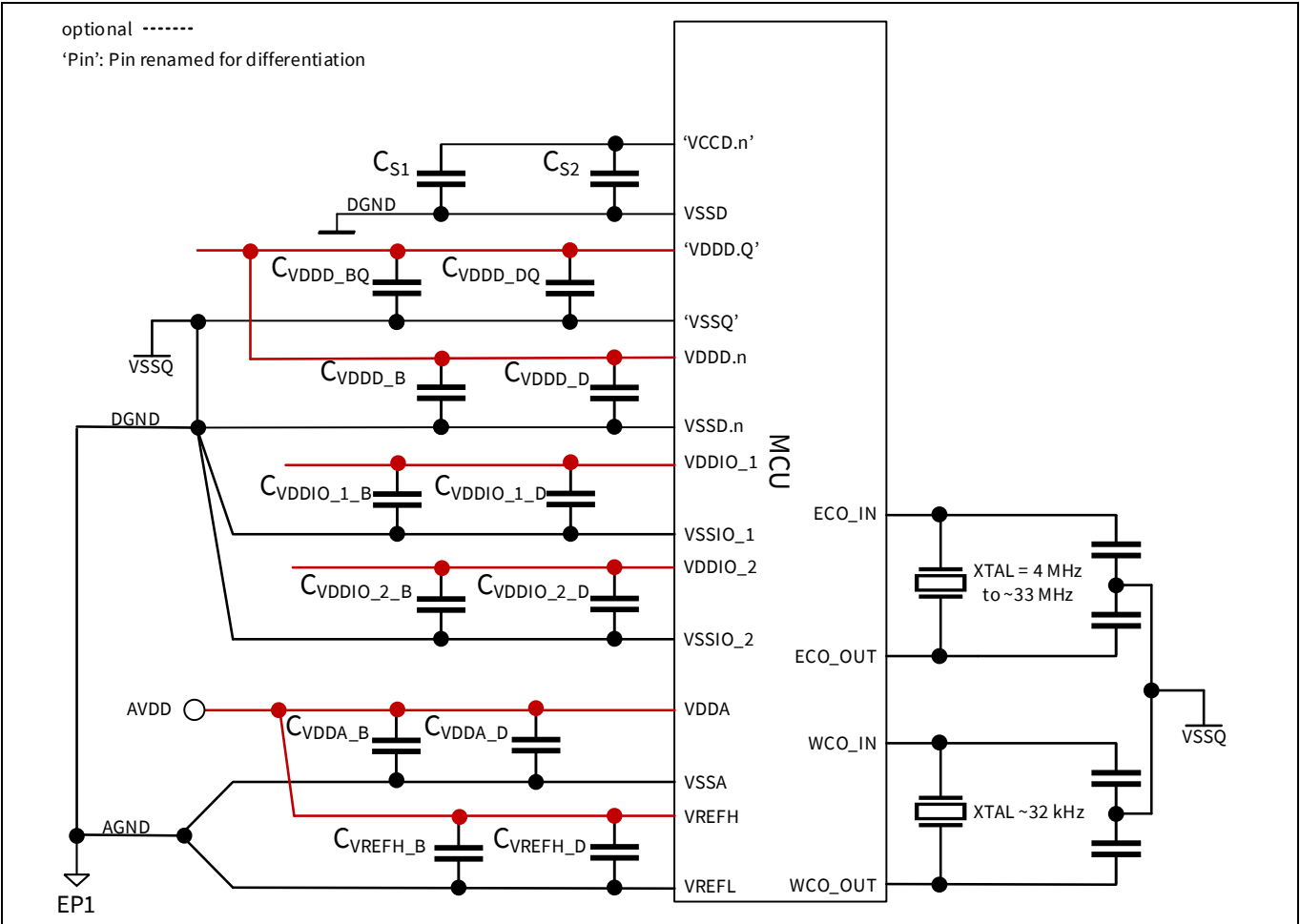


Figure 50 Power supply concept example for CYT2B series

Appendix A – Power supply concept

Table 10 External component integration example for CYT2B series

Symbol	Parameter	Package	
		Value	Remark
C_{S1}	Bypass / smoothing capacitor for core power supply domain VCCD	X7R type	Value in the datasheet. Close to the pin pair according to the device DS specification with respect to 'VCCD.CS1'. 1 capacitor per domain. $ESR \leq 100 \text{ m}\Omega$, $ESL \leq 4 \text{ nH}$ in total per capacitor and including the board track to all VCCD pins with priority on pin 'VCCD.CS1' with $I_{DD}^8 \leq 150 \text{ mA}$ by active regulator. Low impedant plane recommended.
C_{S2}	Decoupling capacitor for core power supply domain VCCD	100 nF X7R ALT: 47 nF X7R	Optional: 1 capacitor on affected power domain pin, having risk of EMC issues due to PCB parasitics between C_{S1} and power domain pin.
C_{VDDD_BQ}	Bypass capacitor for VDDD domain IPs	4.7 uF X7R	Also, used for low-frequency decoupling and MCU inrush current. For PCB-specific capacitor dimensioning, consider the inrush current from active regulator in spec ID SID603 mentioned in the datasheet and Appendix D – Active regulator inrush current . $ESR \leq 100 \text{ m}\Omega$, $ESL \leq 4 \text{ nH}$ including board track.
C_{VDDD_DQ}	Decoupling capacitor for VDDD domain IPs	100 nF X7R	Voltage drop greater than 300 mV must be avoided to keep the stability of the internal LDO and to reset assertion trip points. Pin 'VDDD.Q' (Quiet Supply) not shared with I/O domain, but for oscillator among others.
C_{VDDD_B}	Bypass capacitor for VDDD domain IPs and I/O	-	Required only if C_{VDDD_BQ} is not sufficient for bypassing the power rail supply.
$C_{VDDD_D}^{9,10}$	Decoupling capacitor VDDD domain logic and I/O	100 nF X7R	1 capacitor per domain pin. Decoupling conditions are valid per pin; all toggling groups should toggle asynchronously to each other.

⁸ I_{DD} : input current definition of VDDD in CYT2B datasheet

⁹ VDDD: 5 V, 4% voltage drop, f_{DATA} : 2 MHz, 4x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

¹⁰ VDDD: 5 V, 4% voltage drop, f_{DATA} : 0.1 MHz, 4x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDIO_1_B}$	Bypass capacitor for I/O domain VDDIO_1	TBD	Optional. Depending on the power supply inductance.
$C_{VDDIO_1_D}^{11,12}$	Decoupling capacitor for I/O domain VDDIO_1	100 nF X7R	1 capacitor per domain pin. Decoupling condition is valid for the whole domain.
$C_{VDDIO_2_B}$	Bypass capacitor for I/O domain VDDIO_2	-	-
$C_{VDDIO_2_D}^{13}$	Decoupling capacitor for I/O domain VDDIO_2	100 nF X7R	1 capacitor per domain pin. Decoupling condition is valid for the whole domain. Note: Voltage drop at VDDIO_2 must fulfill the requirement $VDDA - 0.3\text{ V} \leq VDDIO_2 \leq VDDA$
$C_{VDDA_B}^{14}$	Bypass capacitor for ADC VDDA	2.2 μ F X7R	-
C_{VDDA_D}	Decoupling capacitor for ADC VDDA	100 nF X7R	1 capacitor per domain pin
C_{VREFH_B}	Bypass capacitor for ADC VREFH	2.2 μ F X7R	Optional. Required only if a separate analog reference supply is used. Silent supply is required. If the supply is not sufficient, LPF is required.
C_{VREFH_D}	Decoupling capacitor for ADC VREFH	100 nF X7R	-

Table 11 Special power domain pins for CYT2B series

Name	Package pin number (original pin name)					Comment
	64-LQFP	80-LQFP	100-LQFP	144-LQFP	176-LQFP	
VDDD.Q	55 (VDDD)	69 (VDDD)	86 (VDDD)	124 (VDDD)	153 (VDDD)	Quiet Supply. Not shared with the I/O domain.
VSSQ	56 (VSSD)	70 (VSSD)	87 (VSSD)	125 (VSSD)	154 (VSSD)	Quiet Ground for the oscillator

¹¹ VDDIO_1: 5 V, 4% voltage drop, f_{DATA} : 2 MHz, 5x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

¹² VDDIO_1: 5 V, 4% voltage drop, f_{DATA} : 0.1 MHz, 5x parallel transition: 100 ns, C_L /pin: 47 pF, asynchronous to footnote 11, no consideration of device internal impedance

¹³ VDDIO_2: 5 V, 4% voltage drop, f_{CLK} : 2 MHz, SDR, 10 x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

¹⁴ Connection of C_{VDDA_B} to both ADC DeCaps for low-noise environment. Three ADC units run simultaneously, not asynchronously and no use of the precondition feature. Power rails and ground parasitic for the analog supply should not exceed the following values according to [Figure 56](#): $R_{AVDD} \leq 100\text{ m}\Omega$, $L_{AVDD} \leq 15\text{ nH}$, $R_{AGND} \leq 100\text{ m}\Omega$, $L_{AGND} \leq 15\text{ nH}$, $L1 \leq 1\text{ nH}$, $L2 \leq 1\text{ nH}$

Appendix A – Power supply concept

Name	Package pin number (original pin name)					Comment
	64-LQFP	80-LQFP	100-LQFP	144-LQFP	176-LQFP	
VCCD.CS1	58 (VCCD)	72 (VCCD)	89 (VCCD)	127 (VCCD)	156 (VCCD)	

19.4 CYT3B/4B series with TEQFP package

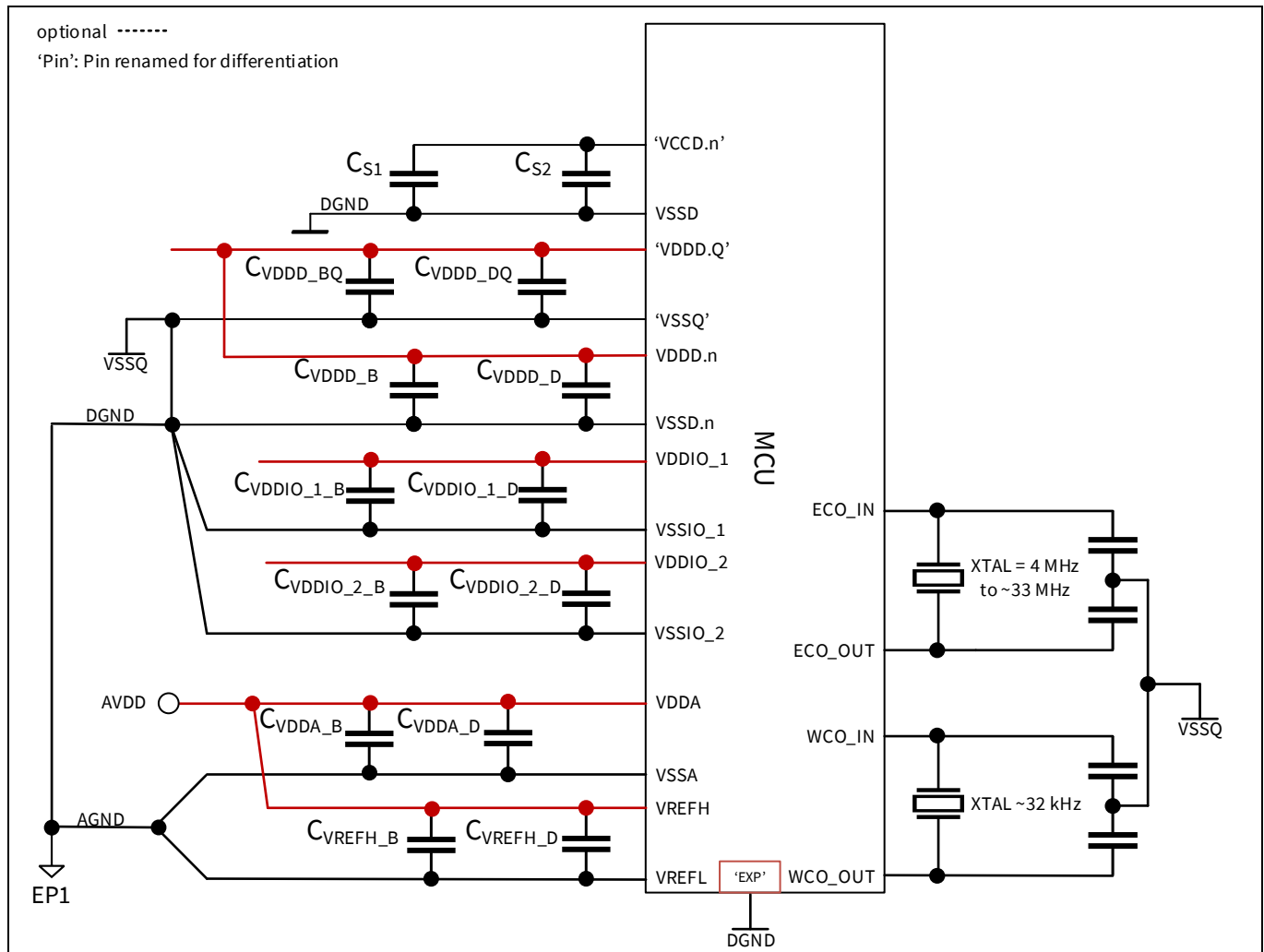


Figure 51 Power supply concept example for CYT4B series with TEQFP package

Appendix A – Power supply concept

Table 12 External component integration example for CYT4B series with TEQFP package

Symbol	Parameter	Package	
		Value	Remark
C_{S1}	Bypass/smoothing capacitor for the core power supply domain VCCD	X7R Type	Value in the datasheet. Close to pin pair according to the device DS specification with respect to 'VCCD.CS1'. 2 capacitors per power domain. $ESR \leq 100 \text{ m}\Omega$, $ESL \leq 4 \text{ nH}$ in total per capacitor including board track to all VCCD pins with priority on pin 'VCCD.CS1' with $I_{DD_VDD}^{15} \leq 150 \text{ mA}$ by the active regulator. Values do not cover higher load transition cases like wakeup from DeepSleep with permanent supply from an external PMIC.
C_{S2}	Decoupling capacitor for core power supply domain VCCD	100 nF X7R ALT: 47 nF X7R	1 capacitor per domain pin group. For VCCD pin group definition, see Table 13 .
C_{VDD_BQ}	Bypass capacitor for VDDD domain IPs	$> 22 \mu\text{F}$ X7R	Also, used for low-frequency decoupling and MCU inrush current. For PCB-specific capacitor dimensioning, consider the inrush current from the active regulator in spec ID SID603 mentioned in the datasheet and Appendix D – Active regulator inrush current . $ESR \leq 50 \text{ m}\Omega$, $ESL \leq 2 \text{ nH}$ in total including board track. In total 2 pcs recommended due to impedance.
C_{VDD_DQ}	Decoupling capacitor for VDDD domain IPs	100 nF X7R	Voltage drop greater than 300 mV must be avoided to keep the stability of the internal LDO and reset assertion trip points. Pin 'VDDD.Q' (Quiet Supply) is not shared with the I/O domain, but with oscillator among others.
C_{VDD_B}	Bypass capacitor for VDDD domain IPs and I/O	-	Only required if C_{VDD_BQ} is not sufficient for bypassing power rail supply

¹⁵ I_{DD_VDD} : input current definition of VDDD in internal supply mode in CYT4B datasheet.

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDD_D}^{16,17}$	Decoupling capacitor VDDD domain logic and I/O	100 nF X7R	1 capacitor per domain pin. Decoupling conditions are valid per pin; all toggling groups should toggle asynchronously with each other.
$C_{VDDIO_1_B}$	Bypass capacitor for I/O domain VDDIO_1	TBD	Optional; depends on the power supply inductance.
$C_{VDDIO_1_D}^{18,19}$	Decoupling capacitor for I/O domain VDDIO_1	100 nF X7R	1 capacitor per domain pin. Decoupling condition is valid for the whole domain.
$C_{VDDIO_2_B}$	Bypass capacitor for I/O domain VDDIO_2	-	-
$C_{VDDIO_2_D}^{20}$	Decoupling capacitor for I/O domain VDDIO_2	100 nF X7R	1 capacitor per domain pin. Decoupling condition is valid for the whole domain. <i>Note:</i> Voltage drop at VDDIO_2 must fulfill the requirement $VDDA - 0.3\text{ V} \leq VDDIO_2 \leq VDDA$
$C_{VDDA_B}^{21}$	Bypass capacitor for ADC VDDA	2.2 μ F X7R	-
C_{VDDA_D}	Decoupling capacitor for ADC VDDA	100 nF X7R	1 capacitor per domain pin
C_{VREFH_B}	Bypass capacitor for ADC VREFH	2.2 μ F X7R	Optional. Required only if a separate analog reference supply is used. Silent supply is required. If the supply is not sufficient, LPF is required.
C_{VREFH_D}	Decoupling capacitor for ADC VREFH	100 nF X7R	-

¹⁶ VDDD: 5 V, 4% voltage drop, f_{DATA} : 2 MHz, 4x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

¹⁷ VDDD: 5 V, 4% voltage drop, f_{DATA} : 0.1 MHz, 4x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

¹⁸ VDDIO_1: 5 V, 4% voltage drop, f_{DATA} : 2 MHz, 5x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

¹⁹ VDDIO_1: 5 V, 4% voltage drop, f_{DATA} : 0.1 MHz, 5x parallel transition: 100 ns, C_L /pin: 47 pF, asynchronous to footnote 18, no consideration of device internal impedance

²⁰ VDDIO_2: 5 V, 4% voltage drop, f_{CLK} : 2 MHz, SDR, 10 x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

²¹ Connection of C_{VDDA_B} to both ADC DeCaps for low-noise environment. Three ADC units run simultaneously, not asynchronously and no use of the precondition feature. Power rails and ground parasitic for the analog supply should not exceed the following values according to [Figure 56](#): $R_{AVDD} \leq 100\text{ m}\Omega$, $L_{AVDD} \leq 15\text{ nH}$, $R_{AGND} \leq 100\text{ m}\Omega$, $L_{AGND} \leq 15\text{ nH}$, $L1 \leq 1\text{ nH}$, $L2 \leq 1\text{ nH}$

Appendix A – Power supply concept

Table 13 Special power domain pins for CYT4B series with TEQFP package

Name	Package pin number (original pin name)					Remark
	64-TEQFP	80-TEQFP	100-TEQFP	144-TEQFP	176-TEQFP	
VDDD.Q	Package(s) not available		86 (VDDD)	124 (VDDD)	153 (VDDD)	Quiet Supply. Not shared with the I/O domain.
VSSQ			87 (VSSD)	125 (VSSD)	154 (VSSD)	Quiet Ground for the oscillator
VCCD.CS2.A			27 (VCCD) 28 (VCCD)	38 (VCCD) 39 (VCCD)	46 (VCCD) 47 (VCCD)	One decap C _{s2} on the pin group
VCCD.CS2.B			64 (VCCD) 65 (VCCD)	92 (VCCD) 93 (VCCD)	111 (VCCD) 112 (VCCD) 113 (VCCD)	One decap C _{s2} on the pin group
VCCD.CS2.C			89 (VCCD)	127 (VCCD)	156 (VCCD)	One decap C _{s2} on the pin group
EXP	N/A	N/A	Yes	Yes	Yes	Exposed pad

Appendix A – Power supply concept

19.5 CYT4B series with BGA package

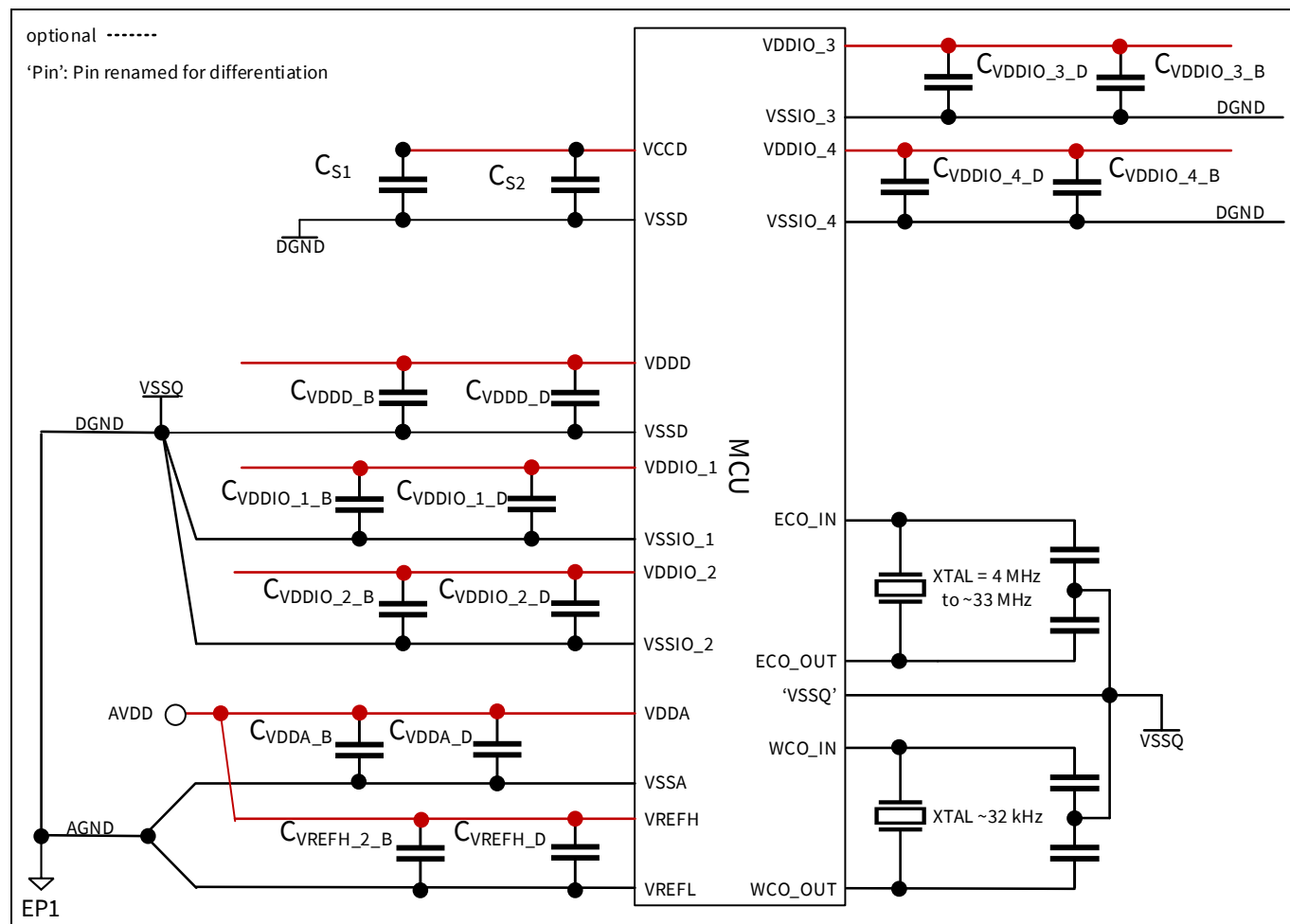


Figure 52 MCU power supply concept example for CYT4B series with BGA package

Table 14 External component integration example for CYT4B series BGA package

Symbol	Parameter	Package	
		Value	Remark
C_{S1}	Bypass/Smoothing capacitor for core power supply domain VCCD	X7R Type	Value in the datasheet. Nominal value for domain. Close to the pin pair according to the device datasheet specification. Check the capacitor value and placement requirements between the MCU and PMIC depending on the core VCCD power rail concept.
C_{S2}	Decoupling capacitor for core power supply domain VCCD	100 nF X7R ALT: 47 nF X7R	1 capacitor per domain pin
C_{VDDD_B}	Bypass capacitor for VDDD domain IPs and I/O	> 22 μ F X7R	Required for internal LDO. For PCB-specific capacitor dimensioning, consider the inrush

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
			current from the active regulator in spec ID SID603 mentioned in the datasheet and Appendix D – Active regulator inrush current . ESR ≤ 50 mΩ, ESL ≤ 2 nH in total including board track. In total 2 pcs recommended due to impedance.
C_{VDD_D}	Decoupling capacitor VDDD domain logic and I/O	100 nF X7R	1 capacitor per domain pin. Voltage drop greater than 300 mV must be avoided due to internal LDO and reset assertion trip points. Number of parallel transitions should be reduced as much as possible.
$C_{VDDIO_1_B}^{22}$	Bypass capacitor for I/O domain VDDIO_1	1 μF X7R	1 capacitor per domain
$C_{VDDIO_1_D}^{20}$	Decoupling capacitor for I/O domain VDDIO_1	100 nF X7R	1 capacitor per domain pin. Minimum two pieces are required.
$C_{VDDIO_2_B}$	Bypass capacitor for I/O domain VDDIO_2	-	
$C_{VDDIO_2_D}^{23}$	Decoupling capacitor for I/O domain VDDIO_2	100 nF X7R	1 capacitor per domain pin <i>Note: Voltage drop at VDDIO_2 must fulfill the requirement $VDDA - 0.3 V \leq VDDIO_2 \leq VDDA$.</i>
$C_{VDDIO_3_B}$	Bypass capacitor for I/O domain VDDIO_3	1 μF X7R	1 capacitor per domain Equivalent power rail inductance: 20 nH
$C_{VDDIO_3_D}^{24}$	Decoupling capacitor for I/O domain VDDIO_3	100 nF X7R 10 nF X7R	1 capacitor for domain 1 capacitor for domain
$C_{VDDIO_4_B}$	Bypass capacitor for I/O domain VDDIO_4	1 μF X7R	1 capacitor per domain Equivalent power rail inductance: 20 nH
$C_{VDDIO_4_D}^{25}$	Decoupling capacitor for I/O domain VDDIO_4	100 nF X7R 10 nF X7R	1 capacitor for domain 1 capacitor for domain

²² VDDIO_1: 3.3 V, 5% voltage drop at capacitors(s), f_{CLK} : 25 MHz, DDR, 9 x parallel transition: 3 ns, C_L /pin: 20 pF, no consideration of device internal impedance

²³ VDDIO_2: 5 V, 4% voltage drop at capacitor(s), f_{DATA} : 2 MHz, 10 x parallel transition: 20 ns, C_L /pin: 47 pF, no consideration of device internal impedance

Conditions:

²⁴ VDDIO_3: 3.3 V, 7% voltage drop at capacitors, f_{CLK} : 100 MHz, DDR, 9 x parallel transition: 1.5 ns, C_L /pin: 15 pF, no consideration of device internal impedance

²⁵ VDDIO_4: 3.3 V, 7% voltage drop at capacitors, f_{CLK} : 125 MHz, SDR, 9 x parallel transition: 0.75 ns, C_L /pin: 10 pF, no consideration of device internal impedance

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDA_B}^{26}$	Bypass capacitor for ADC VDDA	2.2 μ F X7R	-
C_{VDDA_D}	Decoupling capacitor for ADC VDDA	100 nF X7R	1 capacitor per domain pin
$C_{VREFH_2_B}$	Bypass capacitor for ADC VREFH	2.2 μ F X7R	Optional. Required only if a separate analog reference supply is used.
C_{VREFH_D}	Decoupling capacitor for ADC VREFH	100 nF X7R	-

Table 15 Special powerdomain pins for CYT4B series with BGA package

Name	Package pin number (original pin name)		Remark
	272-BGA	320-BGA	
VSSQ	L11 (VSSD_1)	N13 (VSSD_1)	Quiet Ground for the oscillator

²⁶ Connection of C_{VDDA_B} to both ADC DeCaps for low-noise environment. Three ADC units run simultaneously, not asynchronously and no use of the precondition feature. Power rails and ground parasitic for the analog supply should not exceed the following values according to [Figure 56](#): $R_{AVDD} \leq 100$ m Ω , $L_{AVDD} \leq 15$ nH, $R_{AGND} \leq 100$ m Ω , $L_{AGND} \leq 15$ nH, $L1 \leq 1$ nH, $L2 \leq 1$ nH

Appendix A – Power supply concept

Table 16 External component integration example for CYT3D series TEQFP package^{27,28}

Symbol	Parameter	Package	
		Value	Remark
C _{S1}	Bypass/Smoothing capacitor for core power supply domain VCCD	X7R Type	Value in the datasheet. 2 capacitors for domain. Close to the pin pair according to the device datasheet specification. Check capacitor value and placement requirements between the MCU and PMIC depending on the core VCCD power rail concept ²⁹ .
C _{S2}	Decoupling capacitor for core power supply domain VCCD	100 nF X7R	1 capacitor per domain pin
C _{VDDD_B}	Bypass capacitor for VDDD domain IPs and I/O	> 22 µF X7R	Required for internal LDO For PCB-specific capacitor dimensioning, consider the inrush current from active regulator in spec ID SID603 mentioned in the datasheet, Appendix D – Active regulator inrush current , and all bypass capacitors for the core supply. ESR ≤ 50 mΩ, ESL ≤ 2 nH in total including board track. In total 2 pcs recommended due to impedance.
C _{VDDD_D}	Decoupling capacitor VDDD domain logic and I/O	100 nF X7R	1 capacitor per domain pin. Voltage drop greater than 300 mV must be avoided due to internal LDO and reset assertion trip points. Number of parallel transitions should be reduced as much as possible.
C _{VDDIO_GPIO1_B}	Bypass capacitor for I/O domain GPIO	1 µF X7R	1 capacitor for domain
C _{VDDIO_GPIO1_D}	Decoupling capacitor for I/O domain GPIO	100 nF X7R	1 capacitor per domain pin
C _{VDDIO_GPIO2_B}	Bypass capacitor for I/O domain GPIO	1 µF X7R	1 capacitor for domain
C _{VDDIO_GPIO2_D}	Decoupling capacitor for I/O domain GPIO	100 nF X7R	1 capacitor per domain pin
C _{VDDIO_SMC_B}	Bypass capacitor for I/O domain SMC	2.2 µF X7R	1 capacitor per domain. Required only when SMC control is in use.

²⁷ Device internal impedance and resonance frequencies are not considered.

²⁸ Dimensioning of bypass capacitors does not consider slow response time of PMICs in kHz range, especially for fast signal domains.

²⁹ Under clarification, if MIPI and FPD-link filter caps must be considered for total C_{S1} range.

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDIO_SMC_D}$	Decoupling capacitor for I/O domain SMC	100 nF X7R	1 capacitor per 2 domain pins
$C_{VDDIO_HSIO1_B1}$	Bypass capacitor for I/O domain HSIO1	1 μ F X7R	1 capacitor per SMIF ch.
$C_{VDDIO_HSIO1_B2}$	Bypass capacitor for I/O domain HSIO1	470 nF X7R	1 capacitor per ETH ch.
$C_{VDDIO_HSIO1_D}$	Decoupling capacitor for I/O domain HSIO1	100 nF X7R	1 capacitor per 2 domain pins
$C_{VDDA_ADC_B}$	Bypass capacitor for ADC VDDA	4.7 μ F X7R	1 capacitor per domain
$C_{VDDA_ADC_D}$	Decoupling capacitor for ADC VDDA	100 nF X7R	1 capacitor per domain pin
C_{VREFH_B}	Bypass capacitor for ADC VREFH	2.2 μ F X7R	1 capacitor per domain. Optional. Required only if a separate analog reference supply is used. Silent supply required. If not sufficient, a low-pass filter (LPF) required.
C_{VREFH_D}	Decoupling capacitor for ADC VREFH	100 nF X7R	1 capacitor per 2 domain pins
$C_{VDDA_DAC_B}$	Bypass capacitor for DAC VDDA	2.2 μ F X7R	1 capacitor per domain
$C_{VDDA_DAC_D}$	Decoupling capacitor for DAC VDDA	100 nF X7R	1 capacitor per domain
$C_{VDDPLL_FPD_B}$	Bypass capacitor for FPD VDDPLL	10 μ F X7R	1 capacitor per domain
$C_{VDDPLL_FPD_D}$	Decoupling capacitor for FPD VDDPLL	1.5 nF X7R	1 capacitor per 2 domain pins
$F_{BVDDPLL_FPD}$	Ferrite bead for FPD VDDPLL	MPZ1608B471ATA00	1 ferrite bead per domain. Silent supply must be ensured. In total, 2 Ω in series as RLC filter ^{30,31} against the resonance frequency < 100 kHz from the PMIC.
$C_{VDDA_FPD_B}$	Bypass capacitor for FPD VDDA	10 μ F X7R	1 capacitor per domain
$C_{VDDA_FPD_D}$	Decoupling capacitor for FPD VDDA	1.5 nF X7R	4 capacitors per domain
F_{VDDA_FPD}	Ferrite bead for FPD VDDA	MPZ1608B471ATA00	1 ferrite bead per domain. Silent supply must be ensured. In total, 2 Ω DC in series as RLC filter ^{30,31} against the resonance frequency < 100 kHz from the PMIC.

³⁰ Equivalent RLC filter type as shown in [Figure 49](#).

³¹ IR drop comprised in min. operation range.

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDA_MIPI_B}$	Bypass capacitor for MIPI VDDA	10 μ F X7R	1 capacitor for domain
$C_{VDDA_MIPI_D}$	Decoupling capacitor for MIPI VDDA	100 nF X7R, 1nF X7R	1 capacitor per domain, 1 capacitor per domain
F_{VDDA_MIPI}	Ferrite bead for MIPI VDDA	tbd	1 ferrite bead per domain. Silent supply must be ensured. Optional: In total, 2 Ω DC in series as RLC filter ³⁰ against the resonance frequency < 100 kHz from the PMIC.
$C_{VDDHA_FPD_B}$	Bypass capacitor for FPD VDDHA	10 μ F X7R	1 capacitor per domain
$C_{VDDHA_FPD_D}$	Decoupling capacitor for FPD VDDHA	100 nF X7R, 10 nF X7R, 1.5 nF X7R	1 capacitor per domain, 1 capacitor per domain, 1 capacitor per domain
F_{VDDHA_FPD}	Ferrite bead for FPD VDDA	tbd	1 ferrite bead per domain. Silent supply must be ensured.

Table 17 Special power domain pins for CYT3D series with TEQFP packages

Name	Package pin number (original pin name)		Remark
	208-TEQFP	216-TEQFP	
(VSSECO) VSSD	138 (VSSD)	142 (VSSD)	Quiet ground for ECO oscillator shielding shared with other SRSS IPs
(VSSWCO) VSSA_DAC	131 (VSSD_DAC)	135 (VSSD_DAC)	Quiet ground for WCO/LPECO oscillator shielding shared with analog IP
'EXP'	N/A	N/A	Exposed pad

Appendix A – Power supply concept

19.7 CYT4D series with BGA package

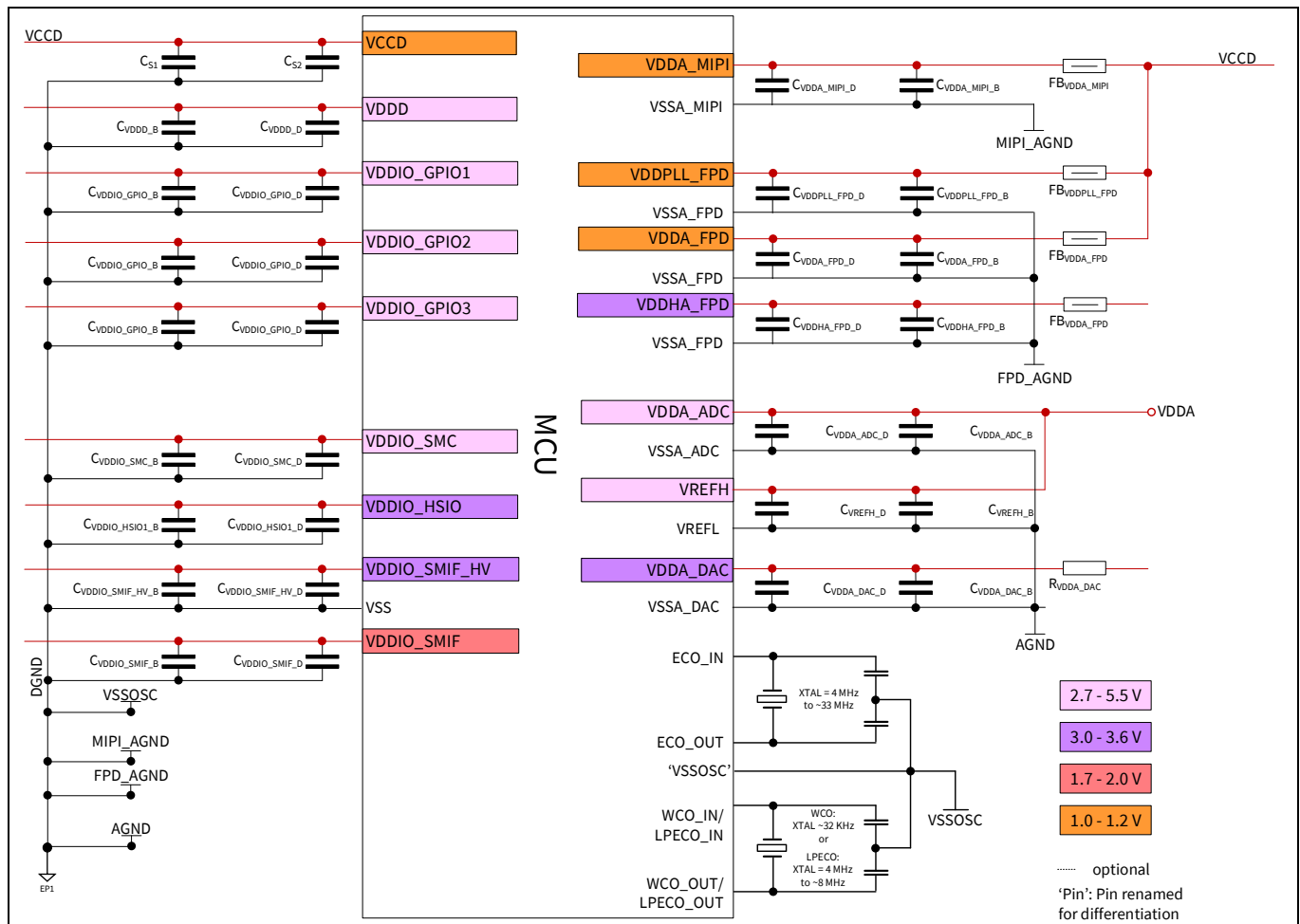


Figure 54 MCU power supply concept example for CYT4D series with BGA package

Appendix A – Power supply concept

Table 18 External component integration example for CYT4D series with BGA package^{32,33}

Symbol	Parameter	Package	
		Value	Remark
C _{S1}	Bypass/Smoothing capacitor for core power supply domain VCCD	X7R type	Value in the datasheet. 2 capacitors for domain. Close to the pin pair according to the device datasheet specification. Check the capacitor value and placement requirements between the MCU and PMIC depending on the core VCCD power rail concept ³⁴ .
C _{S2}	Decoupling capacitor for core power supply domain VCCD	100 nF X7R	1 capacitor per domain pin
C _{VDDD_B}	Bypass capacitor for VDDD domain IPs and I/O	> 22 μ F X7R	Required for internal LDO. For PCB-specific capacitor dimensioning, consider the inrush current from the active regulator in spec ID SID603 mentioned in the datasheet, Appendix D – Active regulator inrush current , and all bypass capacitors for the core supply. ESR \leq 50 m Ω , ESL \leq 2 nH in total including board track. In total 2 pcs recommended due to impedance.
C _{VDDD_D}	Decoupling capacitor VDDD domain logic and I/O	100 nF X7R	1 capacitor per domain pin. Voltage drop greater than 300 mV must be avoided due to internal LDO. Number of parallel transitions should be reduced as much as possible.
C _{VDDIO_GPIO1_B}	Bypass capacitor for I/O domain GPIO	1 μ F X7R	1 capacitor for domain
C _{VDDIO_GPIO1_D}	Decoupling capacitor for I/O domain GPIO	100 nF X7R	1 capacitor per domain pin
C _{VDDIO_GPIO2_B}	Bypass capacitor for I/O domain GPIO	1 μ F X7R	1 capacitor for domain
C _{VDDIO_GPIO2_D}	Decoupling capacitor for I/O domain GPIO	100 nF X7R	1 capacitor per domain pin
C _{VDDIO_GPIO3_B}	Bypass capacitor for I/O domain GPIO	1 μ F X7R	1 capacitor for domain

³² Device internal impedance and resonance frequencies are not considered.

³³ Dimensioning of bypass capacitors does not consider slow response time of PMICs in kHz range, especially for fast signal domains.

³⁴ Under clarification, if MIPI and FPD-link filter caps must be considered for total C_{S1} range.

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDIO_GPIO3_D}$	Decoupling capacitor for I/O domain GPIO	100 nF X7R	1 capacitor per domain pin
$C_{VDDIO_SMC_B}$	Bypass capacitor for I/O domain SMC	2.2 μ F X7R	1 capacitor per domain
$C_{VDDIO_SMC_D}$	Decoupling capacitor for I/O domain SMC	100 nF X7R	1 capacitor per 2 domain pins
$C_{VDDIO_HSIO1_B}$	Bypass capacitor for I/O domain HSIO1	2.2 μ F X7R	1 capacitor per domain
$C_{VDDIO_HSIO1_D}$	Decoupling capacitor for I/O domain HSIO1	100 nF X7R	1 capacitor per 2 domain pins
$C_{VDDIO_SMIF_B}$	Bypass capacitor for I/O domain SMIF	2.2 μ F X7R	1 capacitor per domain
$C_{VDDIO_SMIF_D}$	Decoupling capacitor for I/O domain SMIF	100 nF + 2.2 nF or 2x 100nF	1 capacitor per 2 domain pins
$C_{VDDIO_SMIF_HV_B}$	Bypass capacitor for I/O domain SMIF_HV	-	No capacitor per domain
$C_{VDDIO_SMIF_HV_D}$	Decoupling capacitor for I/O domain SMIF_HV	100 nF	1 capacitor per domain
$C_{VDDA_ADC_B}$	Bypass capacitor for ADC VDDA	4.7 μ F X7R	1 capacitor per domain
$C_{VDDA_ADC_D}$	Decoupling capacitor for ADC VDDA	100 nF X7R	1 capacitor per domain pin
$C_{VDDA_DAC_B}$	Bypass capacitor for DAC VDDA	2.2 μ F X7R	1 capacitor per domain
$C_{VDDA_DAC_D}$	Decoupling capacitor for DAC VDDA	100 nF X7R	1 capacitor per domain
C_{VREFH_B}	Bypass capacitor for ADC VREFH	2.2 μ F X7R	1 capacitor per domain. Optional. Required only if a separate analog reference supply is used.
C_{VREFH_D}	Decoupling capacitor for ADC VREFH	100 nF X7R	1 capacitor per 2 domain pins
$C_{VDDPLL_FPD_B}$	Bypass capacitor for FPD VDDPLL	10 μ F X7R	1 capacitor per domain
$C_{VDDPLL_FPD_D}$	Decoupling capacitor for FPD VDDPLL	1.5 nF X7R	1 capacitor per domain
$F_{BVDDPLL_FPD}$	Ferrite bead for FPD VDDPLL	MPZ1608B471ATA00	1 ferrite bead per domain. Silent supply must be ensured. In total, 2 Ω DC in series as RLC filter ^{35,36} against the resonance frequency < 100 kHz from the PMIC.

³⁵ Equivalent RLC filter type as shown in [Figure 49](#).

³⁶ IR drop comprised in min. operation range.

Appendix A – Power supply concept

Symbol	Parameter	Package	
		Value	Remark
$C_{VDDA_FPD_B}$	Bypass capacitor for FPD VDDA	10 μ F X7R	1 capacitor per domain
$C_{VDDA_FPD_D}$	Decoupling capacitor for FPD VDDA	1.5 nF X7R	1 capacitor per domain
F_{VDDA_FPD}	Ferrite bead for FPD VDDA	MPZ1608B471ATA00	1 ferrite bead per domain. Silent supply must be ensured. Optional: In total, 2 Ω DC in series as RLC filter ^{35,36} against the resonance frequency < 100 kHz from the PMIC.
$C_{VDDA_MIPI_B}$	Bypass capacitor for MIPI VDDA	10 μ F X7R	1 capacitor for domain
$C_{VDDA_MIPI_D}$	Decoupling capacitor for MIPI VDDA	100 nF X7R, 1nF X7R	1 capacitor per domain, 1 capacitor per domain
F_{VDDA_MIPI}	Ferrite bead for MIPI VDDA	MPZ1608B471ATA00	1 ferrite bead per domain. Silent supply must be ensured. In total, 2 Ω DC in series as RLC filter ³⁵ against the resonance frequency < 100 kHz from the PMIC.
$C_{VDDHA_FPD_B}$	Bypass capacitor for FPD VDDHA	10 μ F X7R	1 capacitor per domain
$C_{VDDHA_FPD_D}$	Decoupling capacitor for FPD VDDHA	100 nF X7R, 10 nF X7R, 1.5 nF X7R	1 capacitor per domain, 1 capacitor per domain, 1 capacitor per domain
F_{VDDHA_FPD}	Ferrite bead for FPD VDDA	Tbd	1 ferrite bead per domain. Silent supply must be ensured.

Table 19 Special power domain pins for CYT4B series with BGA packages

Name	Package pin number (original pin name)		Comment
	327-BGA rev. A0	500-BGA rev. A0	
VSSOSC	E20, F19, G20	H25, H26, K25, K26 (VSS)	Quiet ground for oscillator shielding

Appendix B – Analog supply

20 Appendix B – Analog supply

Figure 55 and **Figure 56** show the difference between an ideal analog supply without any parasitic elements and a real analog supply with the parasitic elements in the power rail and in the filter capacitors.

 


Figure 55 Ideal analog power supply

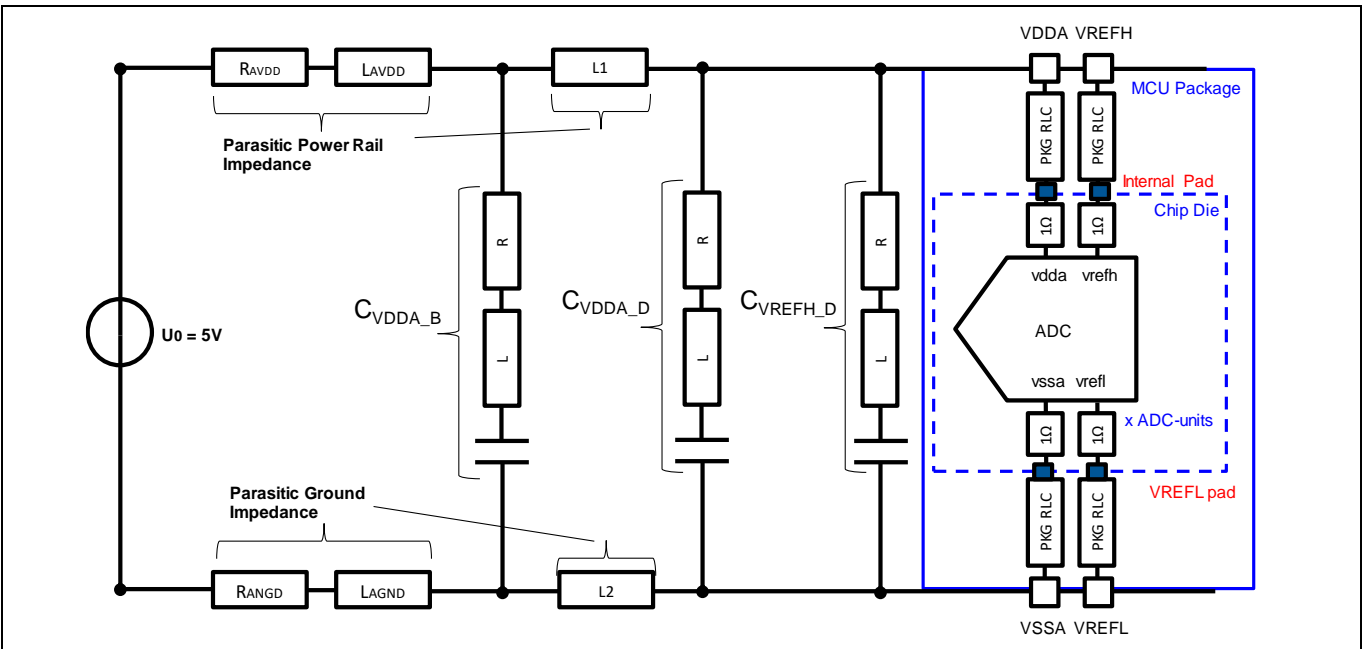


Figure 56 Real analog power supply

Appendix C – Oscillator layout

21 Appendix C – Oscillator layout

Generic oscillator layout proposals are given for several packages.

Note: The recommendations for layout design do not guarantee the correct component ratio or follow any PCB design rules. You may need to make changes for different packages.

21.1 QFP packages

A generic proposal for an oscillator layout with the QFP package is shown in **Figure 57**.

 


Figure 57 Oscillator layout proposal for CYT2B, CYT3B, and CYT4B series QFP packages

Appendix C – Oscillator layout

21.2 BGA packages

Figure 58 shows a recommended oscillator layout with the BGA package.

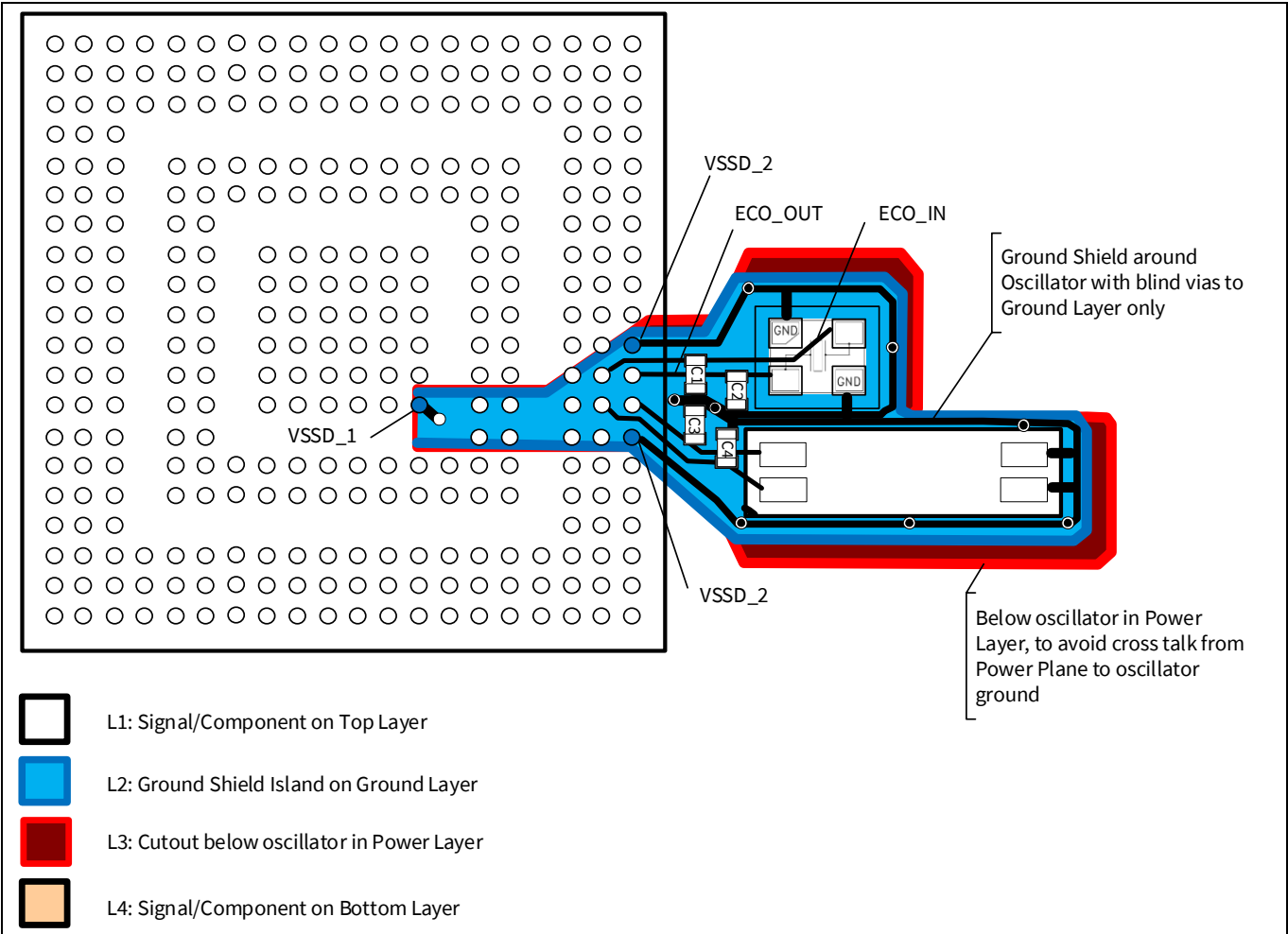


Figure 58 Oscillator layout proposal for BGA packages (based on CYT4B series 320-BGA package)

Appendix D – Active regulator inrush current

22 Appendix D – Active regulator inrush current

As a part of the dimensioning of bypass capacitors at the VDDD domain, the external voltage regulator, the PCB parasitics (ESR and ESL) of that power rail, and the maximum current consumption of the active regulator (internal LDO) must be considered. The fastest inrush current transient into the active regulator is shown for:

- MCUs with a maximum of 150-mA internal LDO operation current (CYT2)
- MCUs with a maximum of 300-mA internal LDO operation current (CYT3/CYT4)

 


Figure 59 CYT2 active regulator inrush current in the worst-case scenario

 


Figure 60 CYT3/CYT4 active regulator inrush current in the worst-case scenario

23 Appendix E – Unused power domain handling

23.1 Introduction

This section explains how to handle unused power domains and their I/O port pins. It does not consider the transition requirements for different power modes, that is, the power ON/OFF sequencing. With regard to I/O port pin handling, make sure that the ECU peripherals are in proper states during power mode transitions. See [Unused power domains](#) to learn how to handle permanently unused power domains that cannot be grounded. See [Port input/unused pins](#) for details on I/O pin handling.

23.2 CYT2B series

Table 20 Unused domain handling of CYT2B series

Power domain	Voltage operation range	Permanent unused domain (active mode)				DeepSleep mode			Hibernate		
		Can be switched OFF? [Yes/No]	Power pin handling ^[37]	I/O pin handling ^[37]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[37]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[37]	Remarks
VDDD (always-on)	2.7 - 5.5 V	No	–	–	–	No	–	–	No	–	–
VCCD	1.09 - 1.21 V	No	–	–	–	No	–	–	–	–	–
VDDA_ADC	2.7 - 5.5 V	No	–	–	–	Yes	–	Disable BOD reset before DeepSleep	Yes	–	–
VDDA_VREFH	2.7 - 5.5 V	Yes	Tie to GND	–	–	Yes	–	–	Yes	–	–
VDDIO_1	2.7 - 5.5 V	No	–	–	–	No	–	–	No	Disable	–
VDDIO_2	2.7 - 5.5 V	No	–	–	–	Yes	Disable	–	Yes	Disable	–

³⁷ Explanation on pin handling (for details on unused I/O port pins, see [Port input/unused pins](#)):

- Tie to GND: Direct connection to GND. Floating levels must be avoided due to Latch-up (LU) risk.
- Open pin: Pin stays open, no wiring. Exception in power save modes.
- Pull Down: External resistor pulled down to GND
- Disable: Disable the input buffer and disable the output.

23.3 CYT3B/4B series

Table 21 Unused domain handling of CYT4B series

Power domain	Voltage operation range	Permanent unused domain (active mode)				DeepSleep mode			Hibernate		
		Can be switched OFF? [Yes/No]	Power pin handling ^[38]	I/O pin handling ^[38]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[38]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[38]	Remarks
VDDD (always-on)	2.7 - 5.5 V	No	–	–	–	No	–	–	No	–	–
VCCD	1.09 - 1.21 V	No	–	–	–	No	–	–	–	–	–
VDDA_ADC	2.7 - 5.5 V	No	–	–	–	Yes	–	Disable BOD reset before DeepSleep	Yes	–	–
VDDA_VREFH	2.7 - 5.5 V	Yes	Tie to GND	–	–	Yes	–	–	Yes	–	–
VDDIO_1	2.7 - 5.5 V	Yes	Tie to GND	Tie to GND, open pin	–	Yes	Disable	–	Yes	Disable	–
VDDIO_2	2.7 - 5.5 V	No	–	–	–	Yes	Disable	–	Yes	Disable	–
VDDIO_3	2.7 - 3.6 V	Yes	Tie to GND	Tie to GND, open pin	–	Yes	Disable	–	Yes	Disable	–
VDDIO_4	2.7 - 3.6 V	Yes	Tie to GND	Tie to GND, open pin	N/A in all packages	Yes	Disable	–	Yes	Disable	–

³⁸ Explanation on pin handling (for details on unused I/O port pins, see [Port input/unused pins](#)):

- Tie to GND: Direct connection to GND. Floating levels must be avoided due to latch-up (LU) risk.
- Open pin: Pin stays open, no wiring. Exception in power save modes.
- Pull Down: External resistor pulled down to GND.
- Disable: Disable the input buffer and disable the output.

23.4 CYT3D Series

Table 22 Unused domain handling of CYT3D series

Power domain	Voltage operation range	Permanent unused domain (active mode)				DeepSleep mode			Hibernate		
		Can be switched OFF? [Yes/No]	Power pin handling ^[39]	I/O pin handling ^[39]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[39]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[39]	Remarks
VDDD (always-on)	2.7 - 5.5 V	No	–	–	–	No	–	–	No	–	–
VCCD	1.09 - 1.21 V	No	–	–	–	No	–	–	–	–	–
VDDA_FPD	1.09 - 1.21 V	No	–	Dedicated port pins	–	No	Disable IP	–	–	Disable IP	–
VDDPLL_FPD	1.09 - 1.21 V	No	–	Dedicated port pins	–	No	Disable IP	–	–	Disable IP	–
VDDA_MIPI	1.09 - 1.21 V	Yes	Tie to GND	Dedicated port pins	–	Yes	Disable IP	–	Yes	Disable IP	–
VDDHA_FPD	3.0 – 3.6 V	No	–	–	–	Yes	Disable IP	–	Yes	Disable IP	–
VDDIO_HSIO	3.0 – 3.6 V	Yes	Tie to GND	Tie to GND, open pin, pull down	–	Yes	Disable	–	Yes	Disable	–
VDDA_DAC	3.0 – 3.6 V	Yes	Tie to GND	Dedicated port pins	–	Yes	Disable IP	–	Yes	Disable IP	–
VDDA_ADC	2.7 - 5.5 V	No	–	–	–	Yes	–	Disable BOD reset before DeepSleep	Yes	–	–

³⁹ Explanation on pin handling (for details on unused I/O port pins, see [Port input/unused pins](#)):

- Tie to GND: Direct connection to GND. Floating levels must be avoided due to latch-up (LU) risk.
- Open pin: Pin stays open, no wiring. Exception in power save modes.
- Pull Down: External resistor pulled down to GND.
- Disable: Disable the input buffer and disable the output.

Appendix E – Unused power domain handling

Power domain	Voltage operation range	Permanent unused domain (active mode)				DeepSleep mode			Hibernate		
		Can be switched OFF? [Yes/No]	Power pin handling ^[39]	I/O pin handling ^[39]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[39]	Remarks	Can be switched OFF? [Yes/No]	I/O pin handling ^[39]	Remarks
VDDA_VREFH	2.7 - 5.5 V	Yes	–	–	–	Yes	–	–	Yes	–	–
VDDIO_1	2.7 - 5.5 V	Yes	Tie to GND	Tie to GND, open pin, pull down	–	Yes	Disable	–	Yes	Disable	–
VDDIO_2	2.7 - 5.5 V	No	Tie to GND	Tie to GND, open pin, pull down	–	Yes	Disable	–	Yes	Disable	–
VDDIO_SMC	2.7 - 5.5 V	No	Tie to GND	Tie to GND, open pin, pull down	–	Yes	Disable	–	Yes	Disable	–

Appendix F – Power supply filter characteristics

24 Appendix F – Power supply filter characteristics

As part of a second-order LPF, a ferrite bead is deployed instead of an inductor. This appendix shows a ferrite bead specification example.

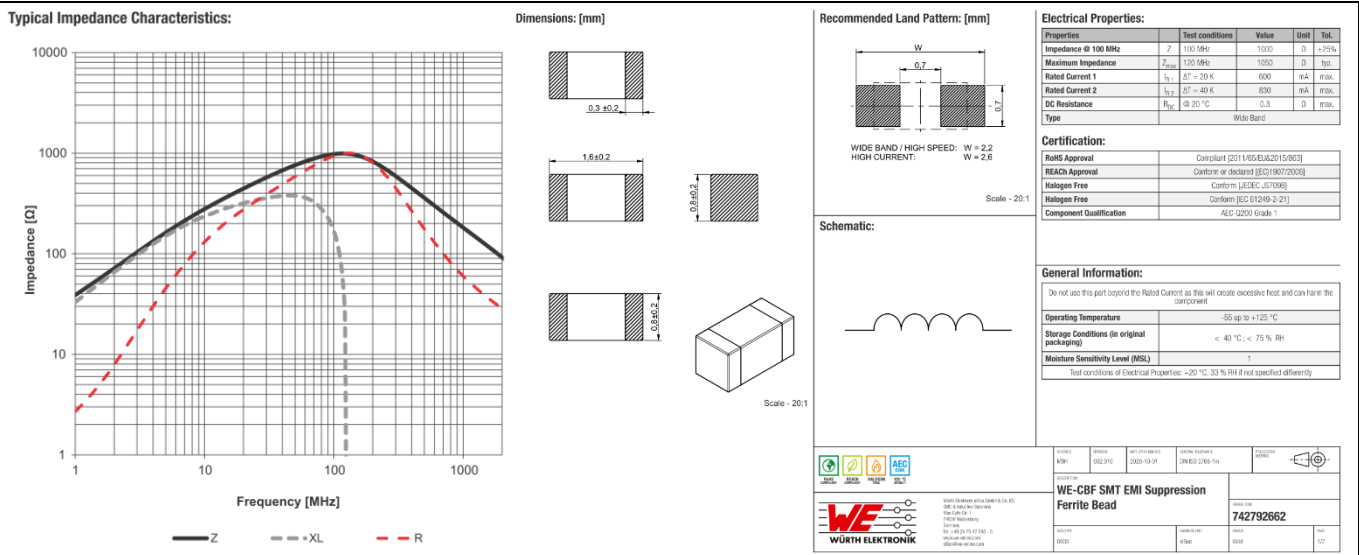


Figure 61 Ferrite bead specification example

Appendix G – Clamping structure of I/O pins with shared analog functions

25 Appendix G – Clamping structure of I/O pins with shared analog functions

As described in [Clamping structure of I/O pins with shared analog functions](#), the clamping structure for different I/O domains with shared analog function are different. Power dependencies and power sequencing are not considered here.

Table 23 Clamping structure of I/O pins with shared analog functions within CYT2B and CYT3B/4B

PD_1 port pins used also as analog inputs	Clamping diode stages			Required voltage level of power domain PD_1/2 ≤ VDDA (same as VDDA) ⁴⁰
	Power domain PD_1 (GPIO stage)	Power domain PD_2 (ADC MUX stage)	Power domain PD_3 (SAR MUX stage)	
No (only digital)	VDDIO_1	VDDIO_1	VDDA	No
Yes	VDDIO_1	VDDIO_1	VDDA	Yes
No. Port P11 is not in use.	VDDIO_2	VDDIO_2	VDDA	No
Yes	VDDIO_2	VDDIO_2	VDDA	No
Not on Port P11, but P11 is in use	VDDIO_2	VDDA	VDDA	Yes
Yes on Port P11, but P11 is in use	VDDIO_2	VDDA	VDDA	Yes
No (digital only)	VDDD	VDDD	VDDA	No
Yes	VDDD	VDDD	VDDA	Yes

Table 24 Clamping structure of I/O pins with shared analog functions within CYT3D

PD_1 port pins used also as analog inputs	Clamping diode stages of I/O domain (= PD 1)			Required voltage level of power domain PD_1/2 ≤ VDDA_ADC (same as VDDA_ADC) ⁴¹
	Power domain PD_1 (GPIO stage)	Power domain PD_2 (ADC MUX stage)	Power domain PD_3 (SAR MUX stage)	
No (digital only)	VDDIO_GPIO1	VDDIO_GPIO1	VDDA	No
Yes	VDDIO_GPIO1	VDDIO_GPIO1	VDDA	Yes
No (digital only)	VDDIO_GPIO2	VDDIO_GPIO1	VDDA	No
Yes	VDDIO_GPIO2	VDDIO_GPIO1	VDDA	Yes
Yes	VDDIO_SMC	VDDIO_SMC	VDDA	Yes

⁴⁰ Implementation of power rail voltage levels for the dedicated I/O domains and the ADC supply must be compliant with the other power sequencing requirements mentioned in the device datasheet.

⁴¹ Implementation of power rail voltage levels for the dedicated I/O domains and the ADC supply must be compliant with the other power sequencing requirements mentioned in the device datasheet.

Appendix G – Clamping structure of I/O pins with shared analog functions

Table 25 Clamping structure of I/O pins with shared analog functions within CYT4D

PD_1 port pins used also as analog inputs	Clamping diode stages of I/O domain (= PD 1)			Required voltage level of power domain PD_1/2 \leq VDDA_ADC (same as VDDA_ADC) ⁴²
	Power domain PD_1 (GPIO stage)	Power domain PD_2 (ADC MUX stage)	Power domain PD_3 (SAR MUX stage)	
No (digital only)	VDDIO_GPIO1	VDDIO_GPIO2	VDDA	No
Yes	VDDIO_GPIO1	VDDIO_GPIO2	VDDA	Yes
No (digital only)	VDDIO_GPIO2	VDDIO_GPIO2	VDDA	No
Yes	VDDIO_GPIO2	VDDIO_GPIO2	VDDA	Yes
Yes	VDDIO_SMC	VDDIO_SMC	VDDA	Yes

⁴² Implementation of power rail voltage levels for the dedicated I/O domains and the ADC supply must be compliant with the other power sequencing requirements mentioned in the device datasheet.

Revision history

Revision history

Version	Date	Description
**	2017-11-27	New application note.
*A	2019-08-19	<ul style="list-style-type: none"> Remove section Minimum System Removed Figure 1 Replaced Figure 23, Figure 24, and Figure 42 Updated section 6.2 Power supply monitoring Changed 19 from Minimum Device System to Power Supply Concept Added 20 and 21 Moved Oscillator Design Proposal to 21 Add CYT4D series Parts Number <ul style="list-style-type: none"> Updated Table 1, Table 2, and Table 3 Updated Figure 27 to Figure 29 Added Figure 30 to Figure 42 Added Table 15 Deleted CYT3B series Parts Number Deleted 6.1 Analog Input Pins
*B	2019-12-18	<ul style="list-style-type: none"> Updated External core supply control, 5-V-tolerant input pins, Related documents Updated Appendix 19.4, A.1 Corrected Table 13 Updated Figure 28 Added section Clamping structure of I/O pins with shared analog functions Added section 13 ADC
*C	2020-05-28	<ul style="list-style-type: none"> Updated Appendix: all “<i>External Component Integration</i>” tables, A.1 New linked documents in Related documents Added section: Assembly and package-related PCB design, Appendix D – Active regulator inrush current, Unused power domains Updated section: Power ON/OFF sequence of power supply domains
*D	2020-12-18	<ul style="list-style-type: none"> Added sections: Unused power domains, Appendix E – Unused power domain handling, FPD-Link Updated sections: Power ON/OFF sequence of power supply domains, Debug interface, Port input/unused pins, Clamping structure of I/O pins with shared analog functions Updated: Figure 20, Figure 21, and Figure 43
*E	2021-04-27	<ul style="list-style-type: none"> Updated to Infineon Template

Revision history

Version	Date	Description
		<ul style="list-style-type: none"> Minor changes: ADC, Charge balancing between CEXT and CVIN, Equation 15 Updated: <ul style="list-style-type: none"> Figure 17, Figure 18, Figure 19, Figure 20 Table 5, Table 12, Table 14 Clamping structure of I/O pins with shared analog functions , Quartz crystal placement and signal routing, Related documents, Appendix D – Active regulator inrush current, Appendix E – Unused power domain handling, Ground and power supply, Clock system Added: Table 4, Audio-DAC, CYT3D series with TEQFP package, FPD-Link, Port pin configuration in AUTOSAR MCAL, Appendix F – Power supply filter characteristics
*F	2021-10-21	<ul style="list-style-type: none"> Minor changes: CYT3B/4B series with TEQFP package, Quartz crystal placement and signal routing, and changed from upper case to lower case in whole document Updated: <ul style="list-style-type: none"> Abbreviations, Appendix A – Power supply concept, Appendix E – Unused power domain handling, Clamping structure of I/O pins with shared analog functions, Clock system, Ground and power supply, Related documents, RGB interface, Power domains Added: Video interface, Appendix G – Clamping structure of I/O pins with shared analog functions

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2021-10-21

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2021 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about this document?

Go to: www.cypress.com/support

Document reference

002-20270 Rev. *F

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.