

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### About this document

#### Scope and purpose

This document summarizes the application of designing an isolated multiple rail buck converter using [TDA38825](#).

#### Intended audience

The intended audience for this document includes FAEs, customers, and application engineers who work on the design and development of power conversion circuits with fast constant on-time (COT) Point of Loads (POLs) products.

## Table of contents

<b>About this document</b> .....	<b>1</b>
<b>Table of contents</b> .....	<b>2</b>
<b>1 Introduction</b> .....	<b>3</b>
1.1 Typical applications: .....	3
<b>2 Overview</b> .....	<b>4</b>
2.1 Specifications .....	4
<b>3 Schematic</b> .....	<b>5</b>
<b>4 ISO buck operation principle</b> .....	<b>6</b>
<b>5 Design of external components</b> .....	<b>8</b>
5.1 Input capacitors .....	8
5.2 Transformer selection .....	8
5.2.1 Selection of primary inductor.....	8
5.3 Schottky diode selection.....	12
5.4 Output capacitor selection .....	12
5.5 Primary output voltage .....	13
5.6 Secondary output voltage .....	13
<b>6 Typical operating waveforms</b> .....	<b>14</b>
6.1 Efficiency.....	14
6.1.1 Efficiency for $V_{out\_pri}$ .....	14
6.1.2 Efficiency for $V_{out\_sec1}$ .....	15
6.1.3 Efficiency for $V_{out\_sec2}$ .....	15
6.2 Load regulation .....	16
6.2.1 $V_{out\_pri}$ regulation vs $I_{out\_pri}$ .....	16
6.2.2 $V_{out\_sec1}$ regulation vs $I_{out\_sec1}$ .....	17
6.2.3 $V_{out\_sec2}$ regulation vs $I_{out\_sec2}$ .....	17
6.2.4 $V_{out\_sec1}$ regulation vs $V_{in}$ .....	18
6.2.5 $V_{out\_sec2}$ regulation vs $V_{in}$ .....	18
6.3 Start-up.....	19
6.4 Shutdown .....	19
6.5 Start-up with load .....	20
6.6 Shutdown with load .....	21
6.7 Current waveform at steady state .....	22
6.8 Current waveform at start-up .....	24
<b>References</b> .....	<b>27</b>
<b>Revision history</b> .....	<b>28</b>
<b>Disclaimer</b> .....	<b>29</b>

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Introduction

## 1 Introduction

Among Infineon's POL product families, the proprietary Fast COT is the most popular loop control. It achieves fast load transient as conventional COT control does, at the same time, maintains high DC accuracy in  $V_{out}$  as voltage mode and current mode control do. See [1] for an introduction of the Fast COT control.

Power supply circuits come in the form of voltage step-up (boost) or the more common step-down (buck) DC-DC converter. Many of today's applications require multiple voltage rails to drive a variety of ICs. These rails can be inverting or non-inverting, with or without isolation. While designers typically use multiple buck converters with single filter inductors, they add cost, footprint, and height. A simpler alternative is to use a single buck converter with coupled inductors or transformers configured in isolated converter topologies. Designers can use the buck converter for inverting or non-inverting voltage rails and configure it for use as an inverting buck-boost converter. Coupled inductors or transformers can also be used with a buck-boost converter to generate multiple inverting or non-inverting outputs with voltage step up/down function.

This application note will discuss about the isolated DC-DC topology and demonstrate how they can be implemented using a synchronous buck converter TDA38825.

### 1.1 Typical applications:

Galvanic isolation and multiple output applications are common in various power electronics applications such as:

- Telecommunications, industrial programmable logic controllers (PLCs)
- Industrial factory automation, isolated communication interfaces (i.e., RS-485, RS-232)
- Bias supplies for gate drives, sensors, op amps, motor drive applications, and any application that requires positive and negative rails

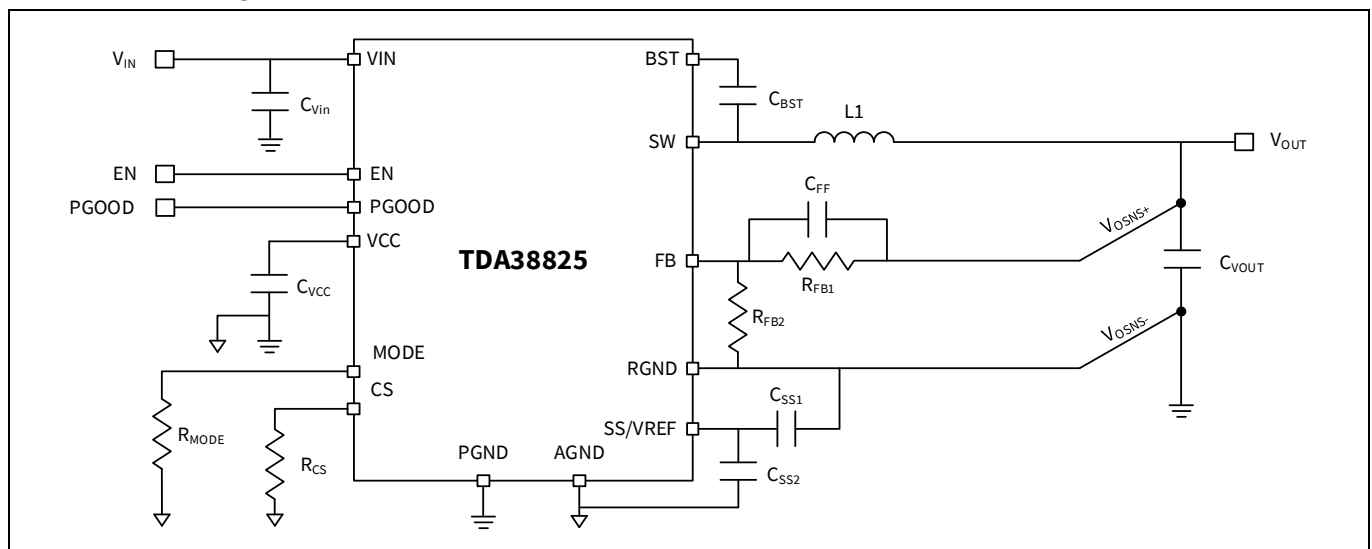


Figure 1 Application diagram of TDA38825

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

---

### Overview

## 2 Overview

The TDA38825 [2] is a 20 A fully integrated and highly efficient DC-DC buck regulator. It uses a fast Constant On-Time (COT) control scheme, which simplifies the design efforts and achieves fast transient response while maintaining excellent line and load regulation. It can operate over a wide range of input voltages (2.7 V to 16 V) using an external bias supply.

TDA38825 is a versatile regulator, offering switching frequency selectable from 600 kHz, 800 kHz, and 1 MHz, programmable current limit, and soft-start time with a minimum of 1 ms, Forced Continuous Conduction Mode (FCCM) and Diode Emulation Mode (DEM) operation. The TDA38825 supports voltage tracking with an external reference input. It also features important protection functions such as pre-bias start-up, thermally compensated current limit, overvoltage and under voltage protection, and thermal shutdown to give a required system level security in the event of fault conditions. The TDA38825 is available in a standard QFN-21 (3 mm x 4 mm) package and can operate over a wide temperature range ( $-40^{\circ}\text{C} < T_j < 125^{\circ}\text{C}$ ).

### 2.1 Specifications

These boards have been configured and optimized for the following operating conditions:


- $V_{IN} = 12\text{ V}$
- $V_{OUT\_PRI} = +3.3\text{ V}$ ,  $I_{MAX\_PRI} = 2\text{ A}$
- $V_{OUT\_SEC1} = +3.3\text{ V}$ ,  $I_{MAX\_SEC1} = 0.5\text{ A}$
- $V_{OUT\_SEC2} = -3.3\text{ V}$ ,  $I_{MAX\_SEC2} = -0.5\text{ A}$
- $F_{sw} = 600\text{ kHz}$

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Schematic

## 3 Schematic

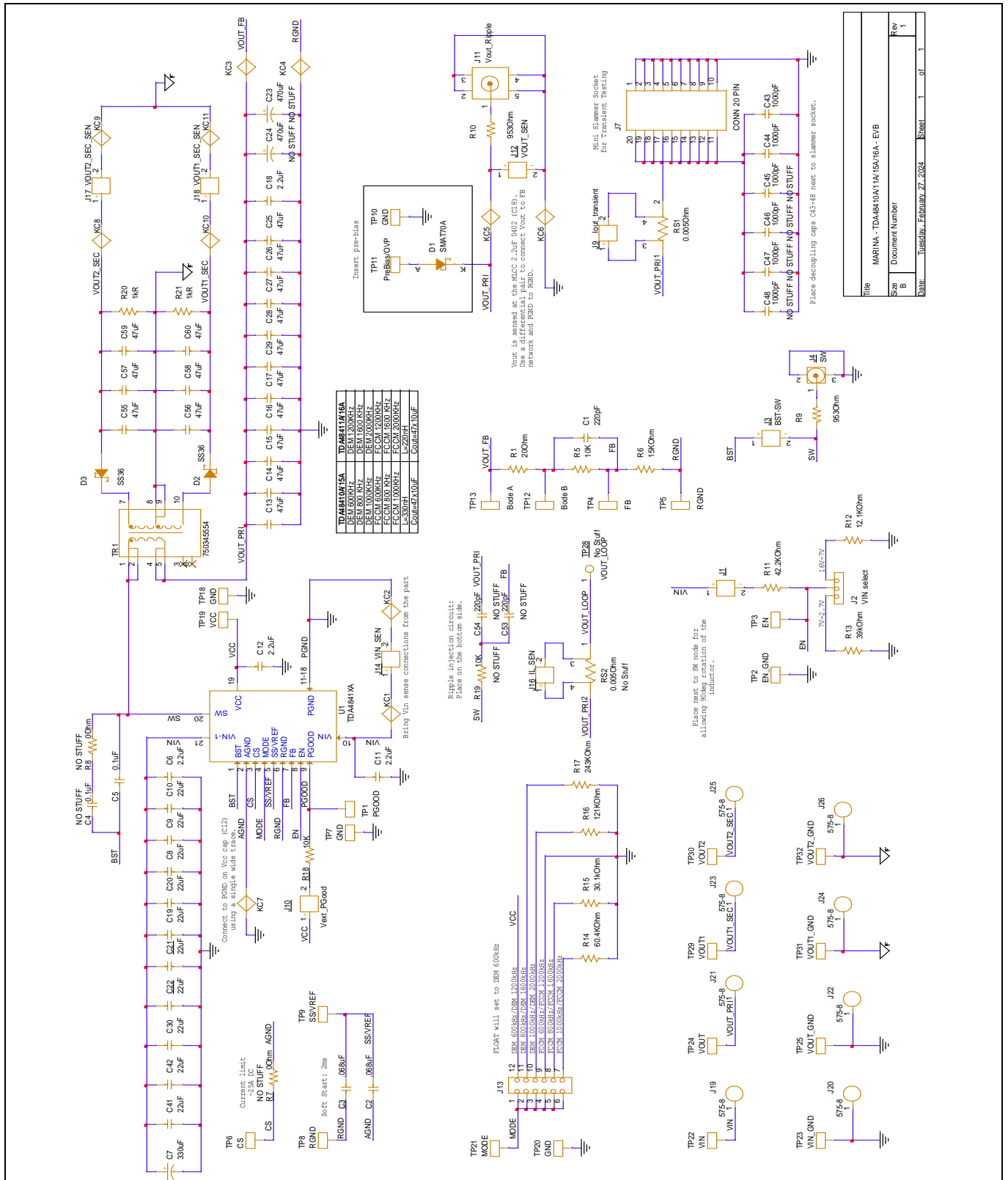


# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### ISO buck operation principle

#### 4 ISO buck operation principle

Figure 3 describes the operation principle of the ISO-buck converter. When the high-side MOSFET is turned on, the current flows through the primary winding of the transformer and charges the primary output capacitor. Considering the dot convention of the transformer, the voltage at the anode of the Schottky diode is negative, hence, the diode is reverse-biased and no current flows in the secondary winding. The load connected to the secondary output is supplied by Cout2. When the low-side MOSFET is turned on, the voltage applied at the transformer windings inverts its polarity. Therefore, the Schottky diode is now forward-biased and allows the current to flow from the secondary winding to Cout and the load. Under this condition the energy transfer from primary to secondary side occurs.

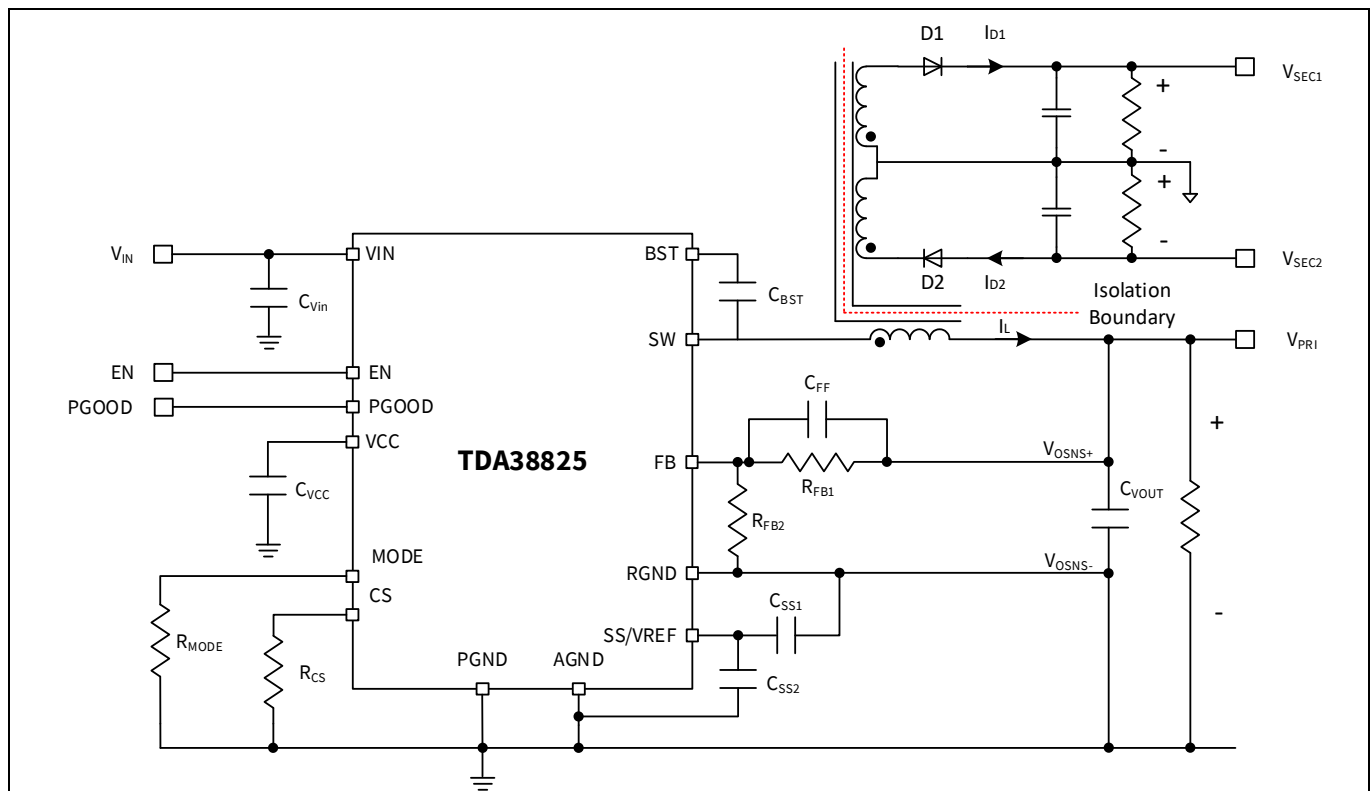

**Figure 3** ISO buck application diagram

For a multiple output configuration, the total current of the various outputs reflected to the primary side must be accounted for to make sure the IC is able to handle the resultant current.

The equations for the above circuit are given as:

$$V_{pri} = D * V_{in}$$

**Equation 1**

$$V_{sec1} = N1 * V_{pri} - V_{diode}$$

**Equation 2**

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### ISO buck operation principle

$$V_{sec2} = -(N2 * V_{pri} - V_{diode})$$

Equation 3

$$\Delta i = (V_{in} - V_{pri}) \frac{D}{L * F_{sw}}$$

Equation 4

$$IDS_{pk} = I_{out_{pri}} + \frac{\Delta i}{2} + \frac{I_{out2}}{N1} + \frac{I_{out3}}{N2}$$

Equation 5

Where  $V_{pri}$  is the primary output and  $V_{sec1}$  and  $V_{sec2}$  are the positive and negative secondary outputs, respectively,  $D$  is the duty cycle,  $N1$  and  $N2$  are the turn ratio of the transformer for  $V_{sec1}$  and  $V_{sec2}$ , respectively.  $V_{diode}$  is the forward voltage drop across the diode.  $I_{OUT1}$ ,  $I_{OUT2}$ , and  $I_{OUT3}$  are the output current drawn from  $V_{pri}$ ,  $V_{sec1}$  and  $V_{sec2}$ , respectively,  $IDS_{pk}$  is the peak current through the top switch and  $\Delta i$  is the triangular portion of the primary inductor ripple current.

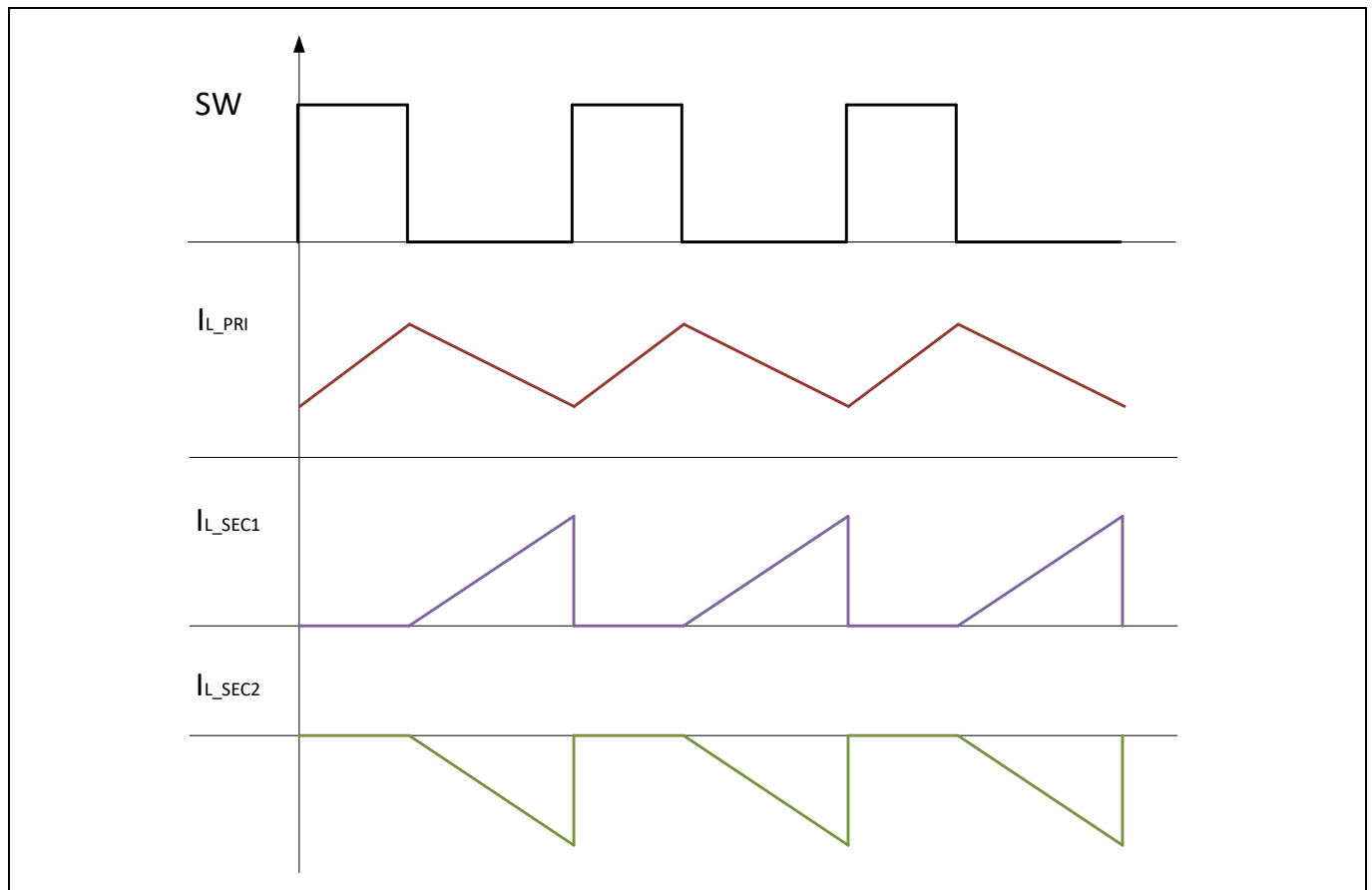


Figure 4 Primary and secondary winding current

## 5 Design of external components

### 5.1 Input capacitors

The input capacitor, just like in a standard buck, should limit the input voltage ripple. Key parameters of the input capacitor are, together with its value, the maximum operating voltage, and the RMS current capability. The input capacitor voltage rating must be higher than the maximum input operating voltage of the application. During the switching activity, a pulsed current flows into the input capacitor and so its RMS current capability must be selected according to the application conditions. Internal losses of the input filter depend on the ESR value so usually low ESR capacitors (like multilayer ceramic capacitors) have higher RMS current capability. On the other hand, given the RMS current value, a lower ESR input filter has lower losses and so contributes to higher conversion efficiency.

The maximum RMS input current flowing through the capacitor can be calculated as:

$$I_{rms} = \left( I_{out_{pri}} + \frac{I_{out2}}{N1} + \frac{I_{out3}}{N2} \right) * \sqrt{\left(1 - \frac{D}{\eta}\right) * \frac{D}{\eta}}$$

**Equation 6**

Typically, CIN is dimensioned to keep the maximum peak-to-peak voltage across the input filter in the order of 5 percent of VINmax.

### 5.2 Transformer selection

The transformer has two essential tasks:

- Providing the isolation between primary and secondary sides in accordance with the application requirements
- Generating the necessary secondary output voltage from the regulated primary voltage with the most suitable turn ratio

The transformer selection implies defining the following parameters:

- Isolation voltage
- Turn ratio
- Primary inductance
- Peak and RMS currents
- Windings resistance
- Leakage inductance
- Parasitic capacitances

#### 5.2.1 Selection of primary inductor

The inductor is selected based on output power, operating frequency, and efficiency requirements. A low inductor value results in a large ripple current, lower efficiency, and high output noise, but helps with size reduction and transient load response. Generally, the desired peak-to-peak ripple current in the inductor ( $\Delta i$ ) is found between 20 percent and 50 percent of the output current.

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Design of external components

The inductor saturation current must be higher than the maximum spec of the OCP limit plus the peak-to-peak inductor ripple current. For some core materials, inductor saturation current may decrease with increasing temperature. It is important to check the inductor saturation current at the maximum operating temperature.

The inductor value for the desired operating ripple current can be determined using the following relations:

$$L = (V_{in} - V_{out\_pri}) \times \frac{D_{min}}{\Delta i_{L(max)} \times F_{sw}}$$

**Equation 7**

$$D_{min} = \frac{V_o}{V_{in(max)}}$$

**Equation 8**

$$I_{sat} \geq OCP_{max} + \Delta i_{L(max)}$$

**Equation 9**

Where: VIN = Maximum input voltage;  $\Delta i_{Lmax}$  = Maximum peak-to-peak inductor ripple current; OCPmax = maximum spec of the OCP limit as defined in TDA38825; and Isat = inductor saturation current.

In this case, select the inductor to achieve  $\Delta i_{Lmax}$  = 20 percent of maximum current of TDA38825, which is 20 A.

$$L = (12 - 3.3) \times \frac{0.275}{4 \times 600 \times 10^3}$$

**Equation 10**

$$L = 1 \mu H$$

**Equation 11**

### Transformer parameters:

The transformer is obtained from Würth Elektronik after customizing it for 1 uH inductance value. [Table 1](#) shows the parameters and [Figure 5](#) shows the footprint and winding structure of the transformer.

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator



### Design of external components


**Table 1 Transformer parameters**

<b>Transformer parameters</b>	<b>Test conditions</b>	<b>Values</b>
DC Resistance (1-5)	Tie (1+2,4+5), at 20°C	15 mohms
DC Resistance (7-8)	Tie (8+9), @20°C	30 mohms
DC Resistance (8-10)	Tie (8+9), @20°C	30 mohms
Inductance (1-5)	Tie (1+2,4+5),10kHz, 100mV, Ls	1 uH +-20%
Saturation Current (1-5)	Tie (1+2,4+5), 30% rolloff from initial	25 A
Leakage Inductance (1-5)	Tie (1+2,4+5,7+8+9+10),100kHz, 100mV, Ls	0.5 uH
DIELECTRIC (1-10)	Tie (1+2,8+9), 1000VAC, 1 second	-
TURNS Ratio	(7-8):(1-5), tie(8+9,1+2,4+5)	1.13:1
TURNS Ratio	(7-8):(8-10), tie(8+9)	1.00:1

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Design of external components

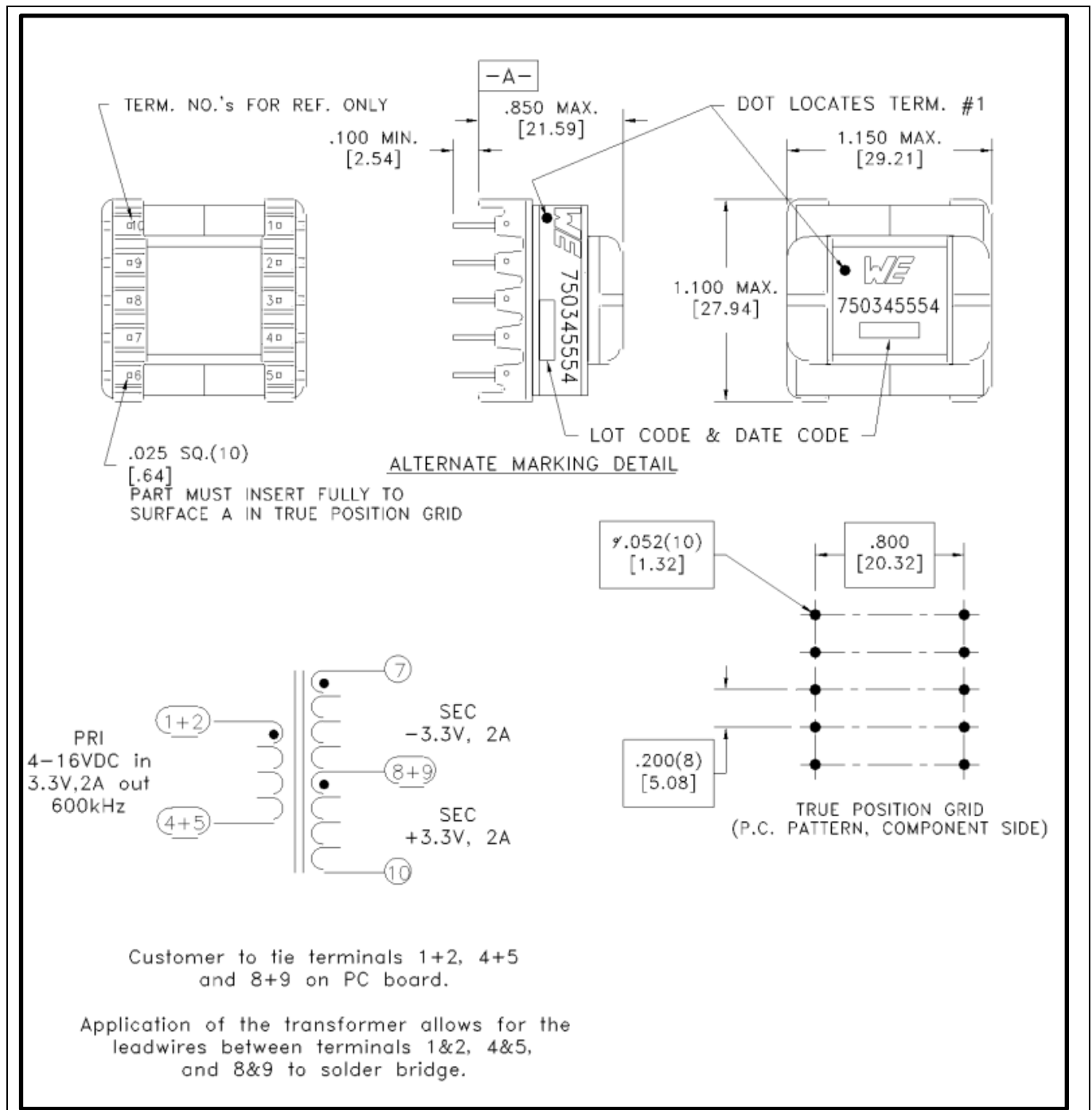

**Figure 5 Transformer package and layout**

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Design of external components

#### 5.3 Schottky diode selection

The selection of the Schottky diode should consider the following parameters:

- Maximum forward current, mainly defined by the secondary output current demand
- Forward voltage drop, which affects the secondary output voltage regulation
- Maximum peak reverse voltage. During the on-phase of the primary side, when in the secondary side no current flows, the diode is reverse biased and must withstand this voltage
- Junction capacitance, which should be as low as possible to reduce the ringing

#### 5.4 Output capacitor selection

##### Primary output capacitor

As in a standard buck converter, the primary output capacitor is involved in:

- Determining the output voltage ripple
- Supporting load transient
- The loop stability, by setting one pole and one zero in the transfer function. Considering the output voltage ripple requirement, the primary output capacitance should be selected according to the following equation

To satisfy the  $V_o$  ripple requirement,  $C_o$  should satisfy the following criterion:

$$C_o > \frac{\Delta i_{Lmax}}{8 \times \Delta V_{or} \times f_{sw}}$$

##### Equation 12

Where  $\Delta V_{or}$  is the desired peak-to-peak output ripple voltage. The ESR and ESL of the output capacitors, as well as the parasitic resistance or inductance due to PCB layout, can also contribute to the output voltage ripple. It is suggested to use multi-layer ceramic capacitor (MLCC) for their low ESR, ESL, and small size.

To meet the transient response requirements, the output capacitors should also meet the following criteria:

$$C_o > \frac{L \times \Delta I_{o(max)}^2}{2 \times \Delta V_{oL} \times V_o}$$

##### Equation 13

Where  $\Delta V_{oL}$  is the allowable  $V_o$  deviation during the load transient.  $\Delta I_{o(max)}$  is the maximum step load current.

##### Secondary output capacitor:

The secondary output capacitor supplies the secondary output load current during the  $t_{ON}$  (when diode D1 is reverse biased) and its value defines the secondary output voltage ripple ( $\Delta V_{OUT2}$ ).

$$C_{o\_sec} > \frac{I_{out2} \times D}{\Delta V_{OUT2} \times f_{sw}}$$

##### Equation 14

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Design of external components

#### 5.5 Primary output voltage

The output voltage can be programmed with an external voltage divider. The FB voltage is compared to an internal reference voltage of 0.6 V. The divider ratio is set to provide 0.6 V at the FB pin when the output is at its desired value. The calculation of the feedback resistor divider is shown below.

$$V_o = V_{ref} \times \left(1 + \frac{R_{FB1}}{R_{FB2}}\right)$$

#### Equation 15

Where  $R_{FB1}$  and  $R_{FB2}$  are the top and bottom feedback resistors, select  $R_{FB1} = 10 \text{ k}\Omega$  and  $R_{FB2} = 10 \text{ k}\Omega$ , to achieve  $V_o = 1.2 \text{ V}$ . The same resistor divider can be used at the VSNS pin to achieve the same voltage scaling factor.

#### 5.6 Secondary output voltage

The secondary output voltage is calculated as:

$$V_{sec1} = N1 * V_{pri} - V_{diode}$$

#### Equation 16

$$V_{sec2} = -(N2 * V_{pri} - V_{diode})$$

#### Equation 17

Where,  $N1 = N2 = 1.13$ ,  $V_{pri} = 3.3 \text{ V}$ ,  $V_{diode} = 0.4 \text{ V}$

$$V_{sec1} = (1.13 * 3.3) - 0.4 = 3.33 \text{ V}$$

Similarly,  $V_{sec2} = -3.33 \text{ V}$

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

## 6 Typical operating waveforms

- $V_{in} = 12\text{ V}$ ,  $L = 1000\text{ nH}$ ,  $F_{sw} = 600\text{ kHz FCCM}$
- $V_{out\_pri} = 3.3\text{ V}$ ,  $I_{out\_pri} = 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}$ ,  $I_{out\_sec1} = 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}$ ,  $I_{out\_sec2} = 0.5\text{ A}$

### 6.1 Efficiency

#### 6.1.1 Efficiency for $V_{out\_pri}$

- $V_{out\_pri} = 3.3\text{ V}$ ,  $I_{out\_pri} = 0\text{--}2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}$ , No Load
- $V_{out\_sec2} = -3.3\text{ V}$ , No Load

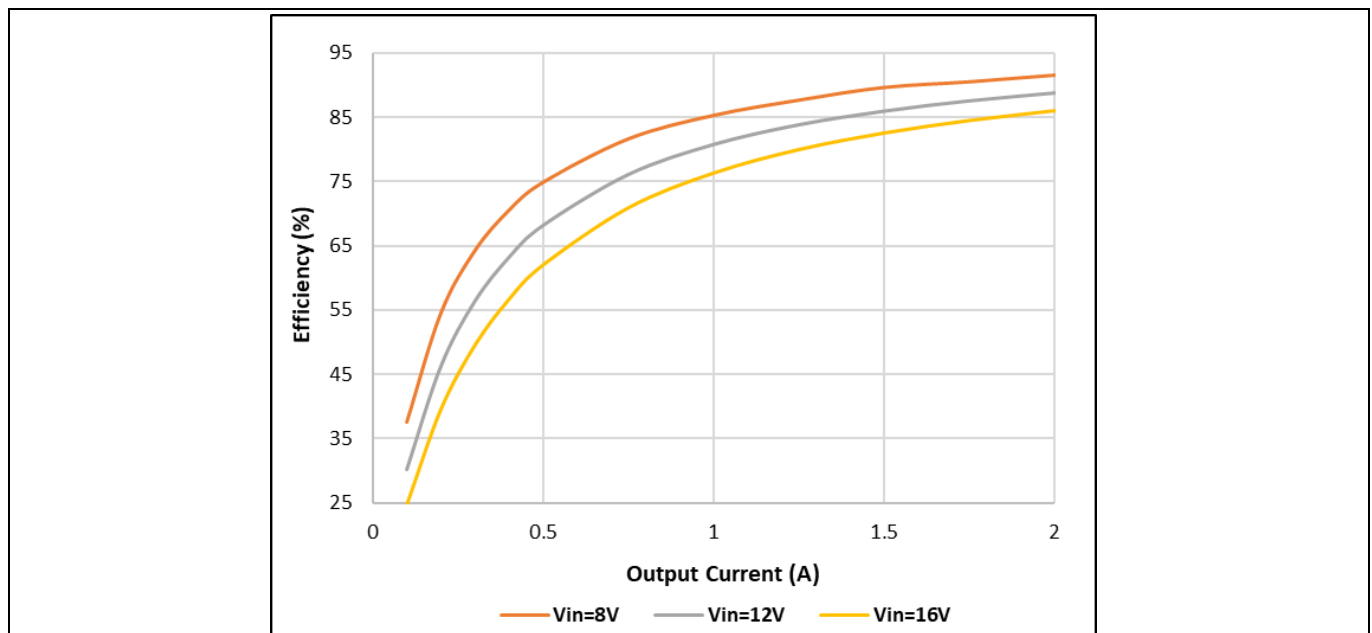


Figure 6 Efficiency for  $V_{out\_pri}$  at different input voltage

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

#### 6.1.2 Efficiency for Vout\_sec1

Vout\_sec1 = 3.3 V, Iout\_sec2 = 0-0.5 A

Vout\_pri = 3.3 V, No Load

Vout\_sec2 = -3.3 V, No Load

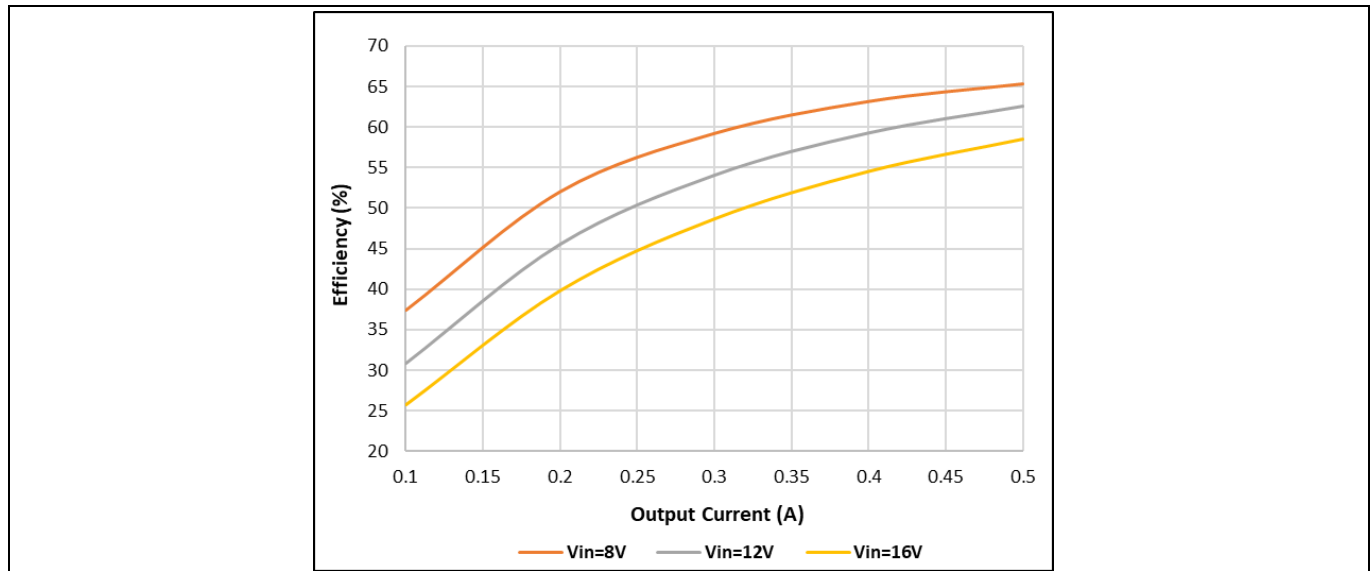


Figure 7 Efficiency for Vout\_sec1 at different input voltage

#### 6.1.3 Efficiency for Vout\_sec2

- Vout\_sec2 = -3.3 V, Iout\_sec2 = 0-0.5 A

- Vout\_pri = 3.3 V, No Load

- Vout\_sec1 = 3.3 V, No Load

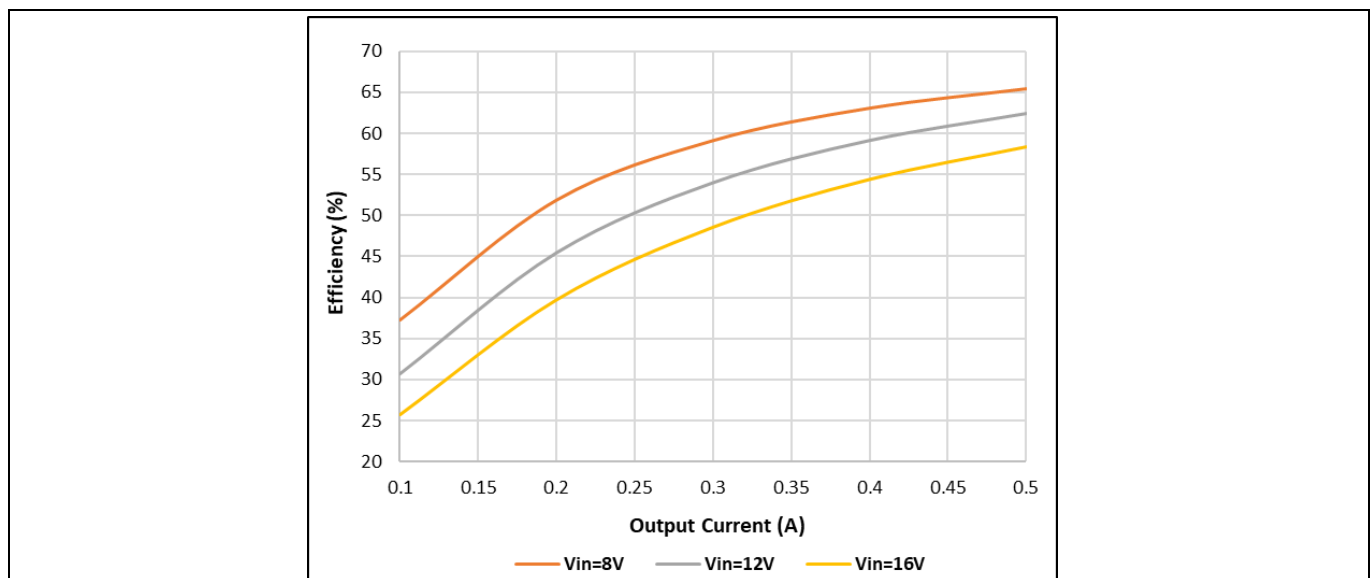


Figure 8 Efficiency for Vout\_sec2 at different input voltage

## 6.2 Load regulation

### 6.2.1 Vout\_pri regulation vs Iout\_pri

- Vout\_pri = 3.3 V, Iout\_pri = 0-2 A
- Vout\_sec1 = 3.3 V, No Load
- Vout\_sec2 = -3.3 V, No Load

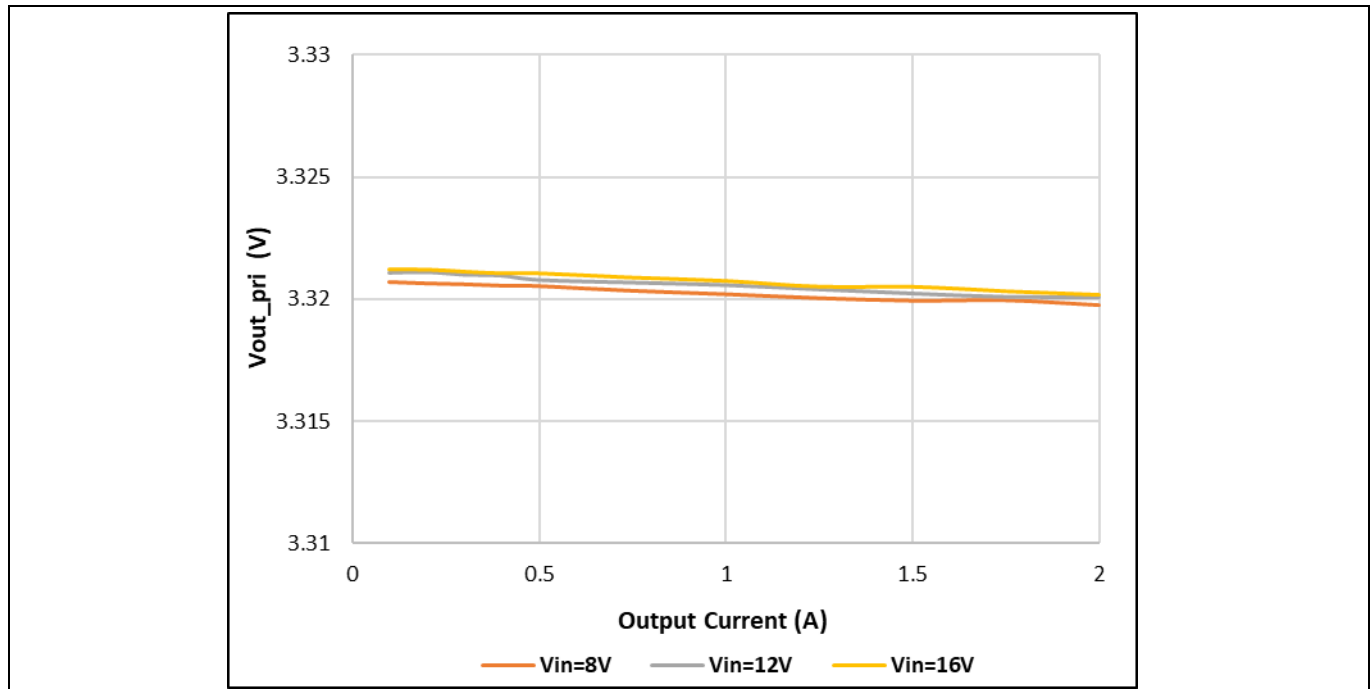


Figure 9 Vout\_pri regulation vs Iout\_pri

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

#### 6.2.2 Vout\_sec1 regulation vs Iout\_sec1

- Vout\_sec1 = 3.8 V, Iout\_sec1 = 0-0.5 A
- Vout\_pri = 3.3 V, No Load
- Vout\_sec2 = -3.3 V, No Load

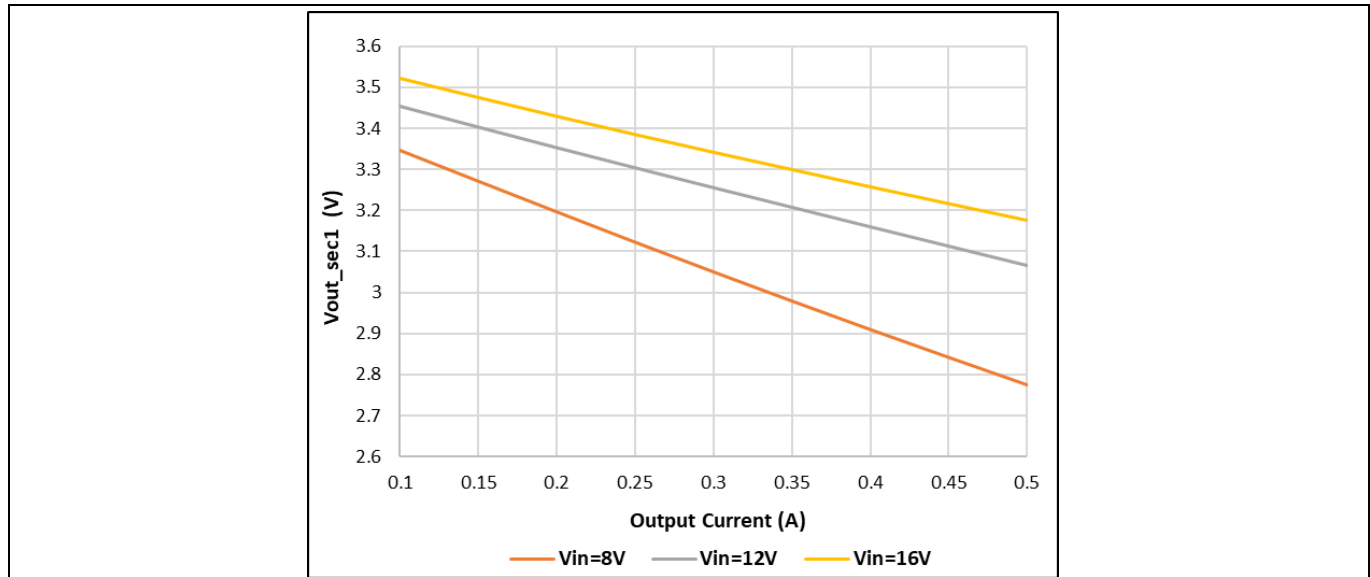


Figure 10 Vout\_sec1 regulation vs Iout\_sec1

#### 6.2.3 Vout\_sec2 regulation vs Iout\_sec2

- Vout\_sec2 = -3.3 V, Iout\_sec2 = 0-0.5 A
- Vout\_pri = 3.3 V, No Load
- Vout\_sec2 = 3.3 V, No Load

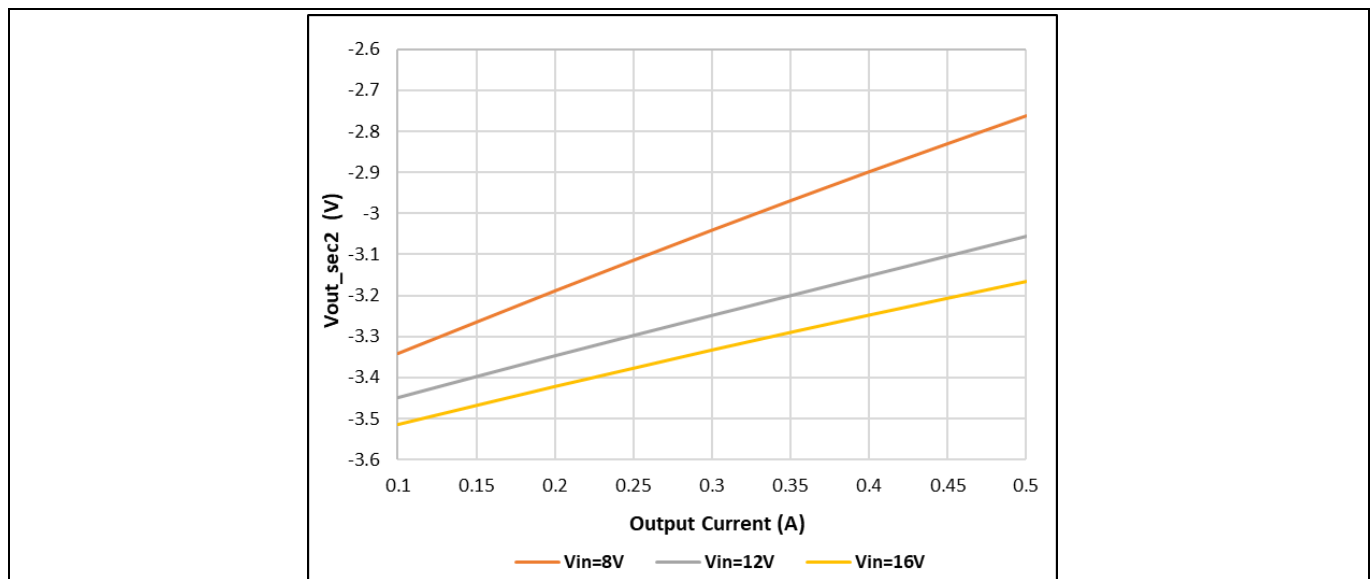


Figure 11 Vout\_sec2 regulation vs Iout\_sec2

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

#### 6.2.4 Vout\_sec1 regulation vs Vin

- Vout\_sec1 = 3.3 V, Iout\_sec1 = 0-0.5 A
- Vout\_pri = 3.3 V, No Load
- Vout\_sec2 = -3.3 V, No Load

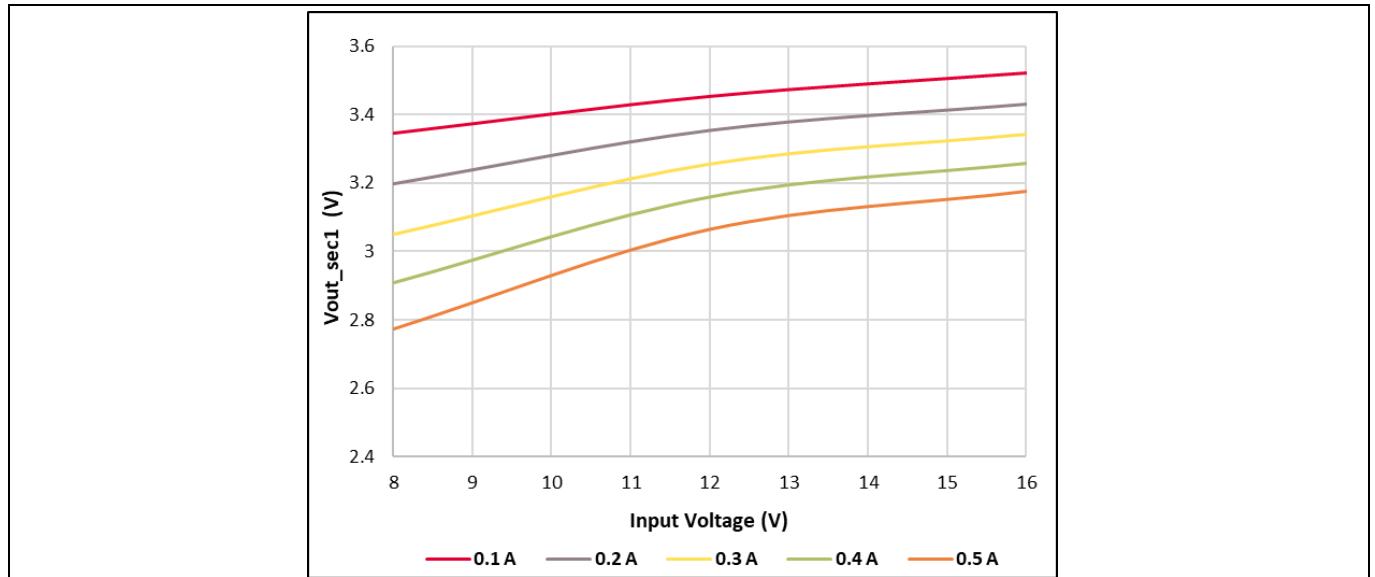


Figure 12 Vout\_sec1 regulation vs Vin

#### 6.2.5 Vout\_sec2 regulation vs Vin

- Vout\_sec2 = -3.3 V, Iout\_sec2 = 0-0.5 A
- Vout\_pri = 3.3 V, No Load
- Vout\_sec2 = 3.3 V, No Load

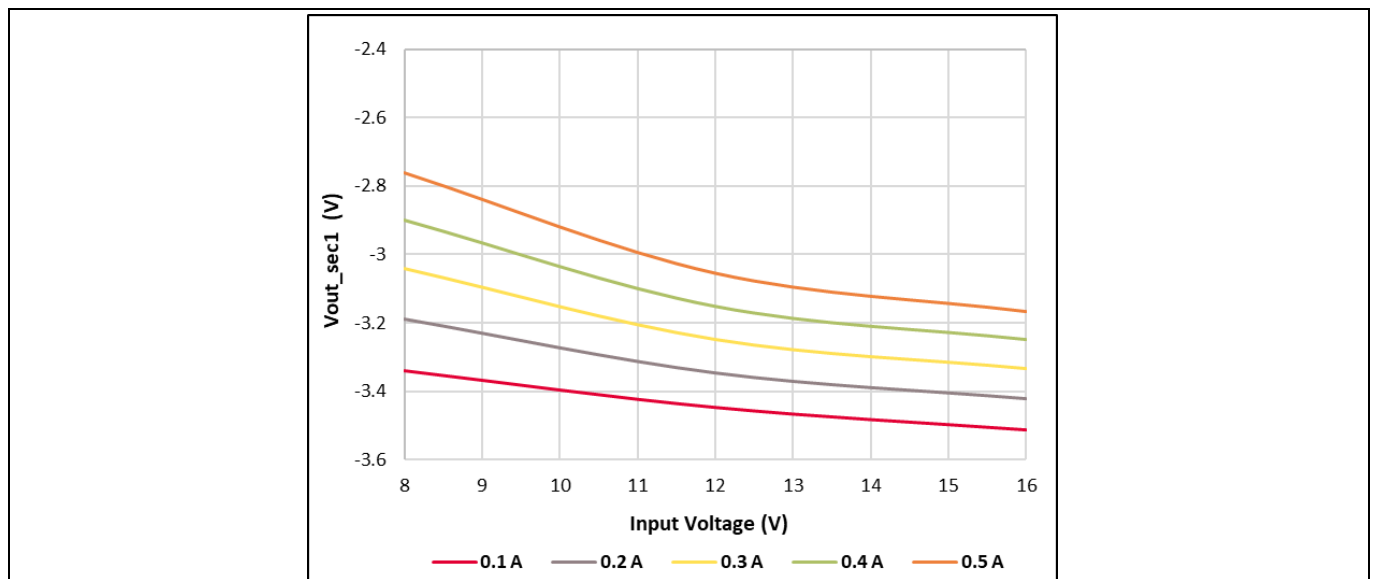


Figure 13 Vout\_sec2 regulation vs Vin

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

### 6.3 Start-up

- Vout\_pri = 3.3 V, No Load
- Vout\_sec1 = 3.3 V, No Load
- Vout\_sec2 = -3.3 V, No Load

#### Oscilloscope:

- Channel 1: Enable
- Channel 2: Vout\_pri
- Channel 3: Vout\_sec1
- Channel 4: Vout\_sec2

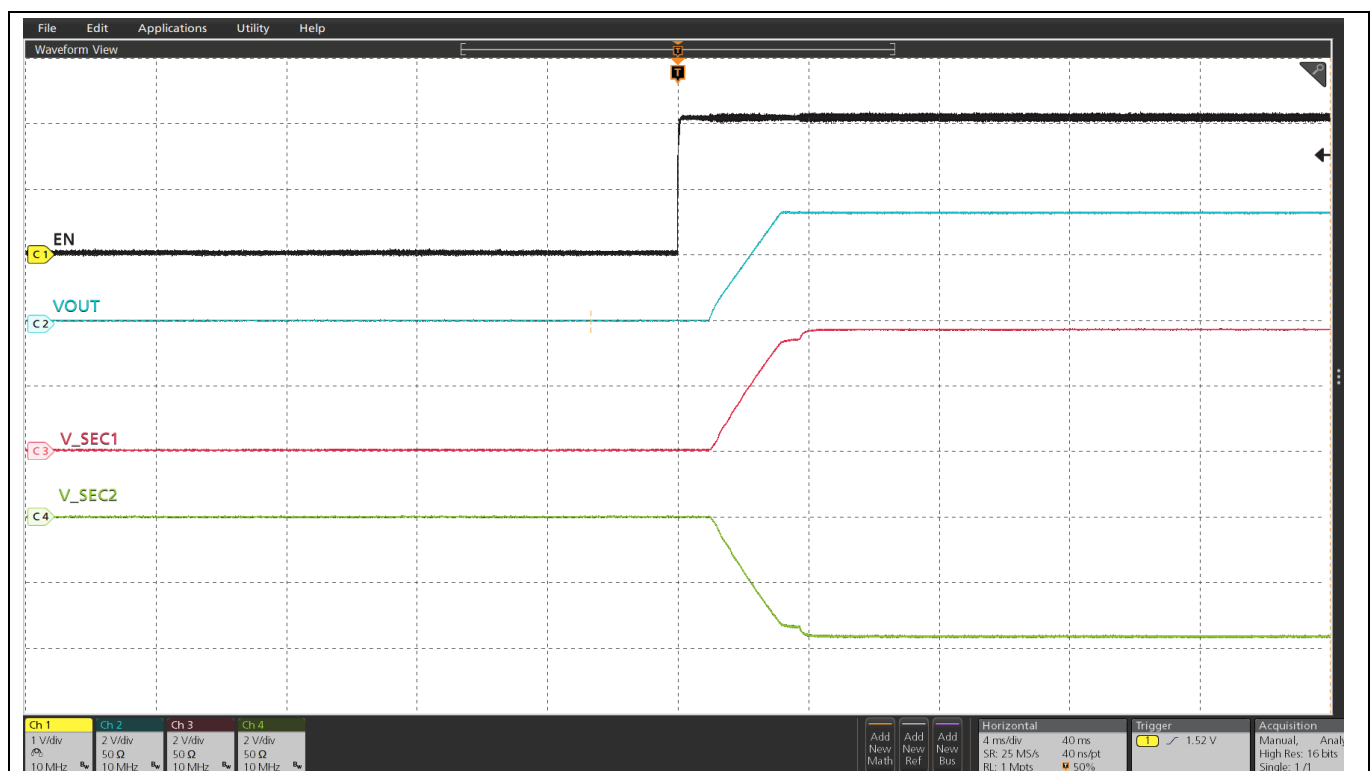


Figure 14 Start-up by enable

### 6.4 Shutdown

- Vout\_pri = 3.3 V, No Load
- Vout\_sec1 = 3.3 V, No Load
- Vout\_sec2 = -3.3 V, No Load

#### Oscilloscope:

- Channel 1: Enable
- Channel 2: Vout\_pri
- Channel 3: Vout\_sec1
- Channel 4: Vout\_sec2

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

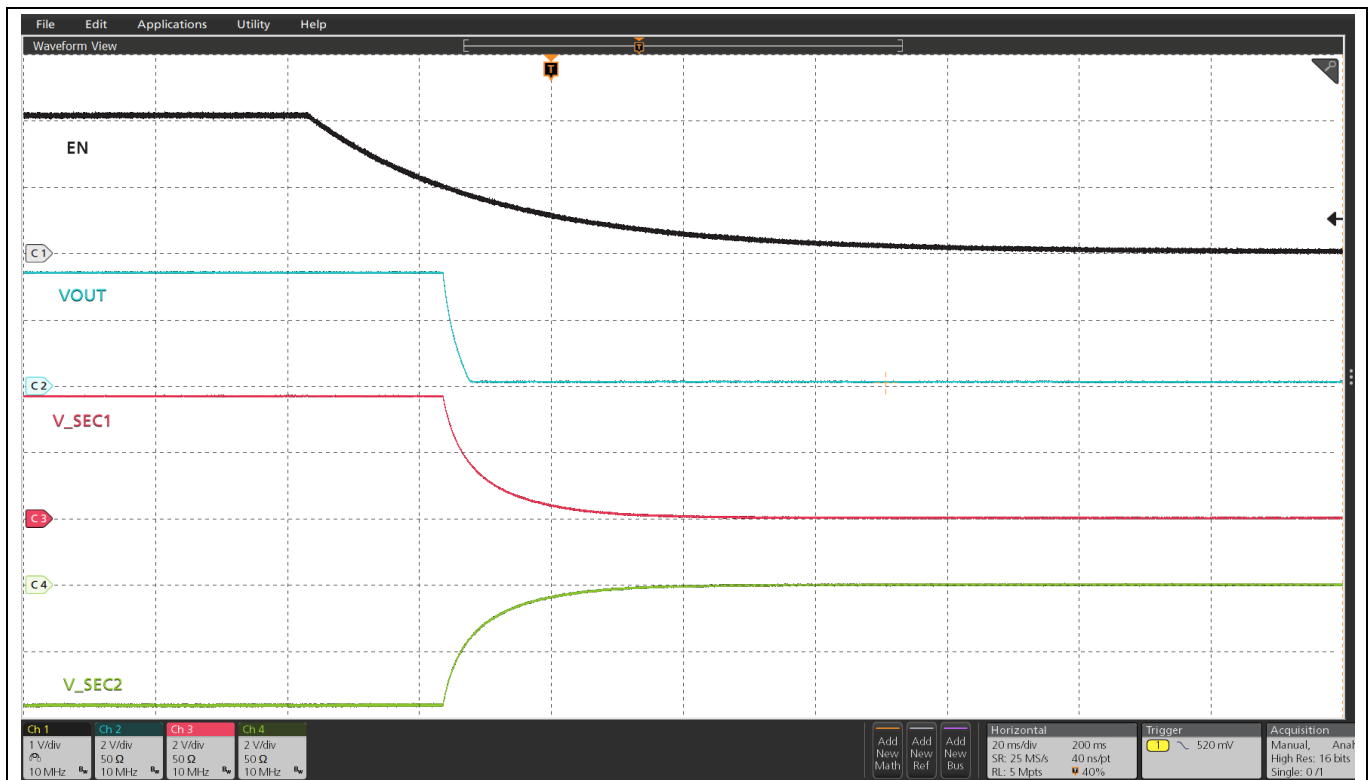


Figure 15 Shutdown by enable

## 6.5 Start-up with load

- $V_{out\_pri} = 3.3\text{ V}, 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}, 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}, 0.5\text{ A}$


### Oscilloscope:

- Channel 1: Enable
- Channel 2:  $V_{out\_pri}$
- Channel 3:  $V_{out\_sec1}$
- Channel 4:  $V_{out\_sec2}$

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

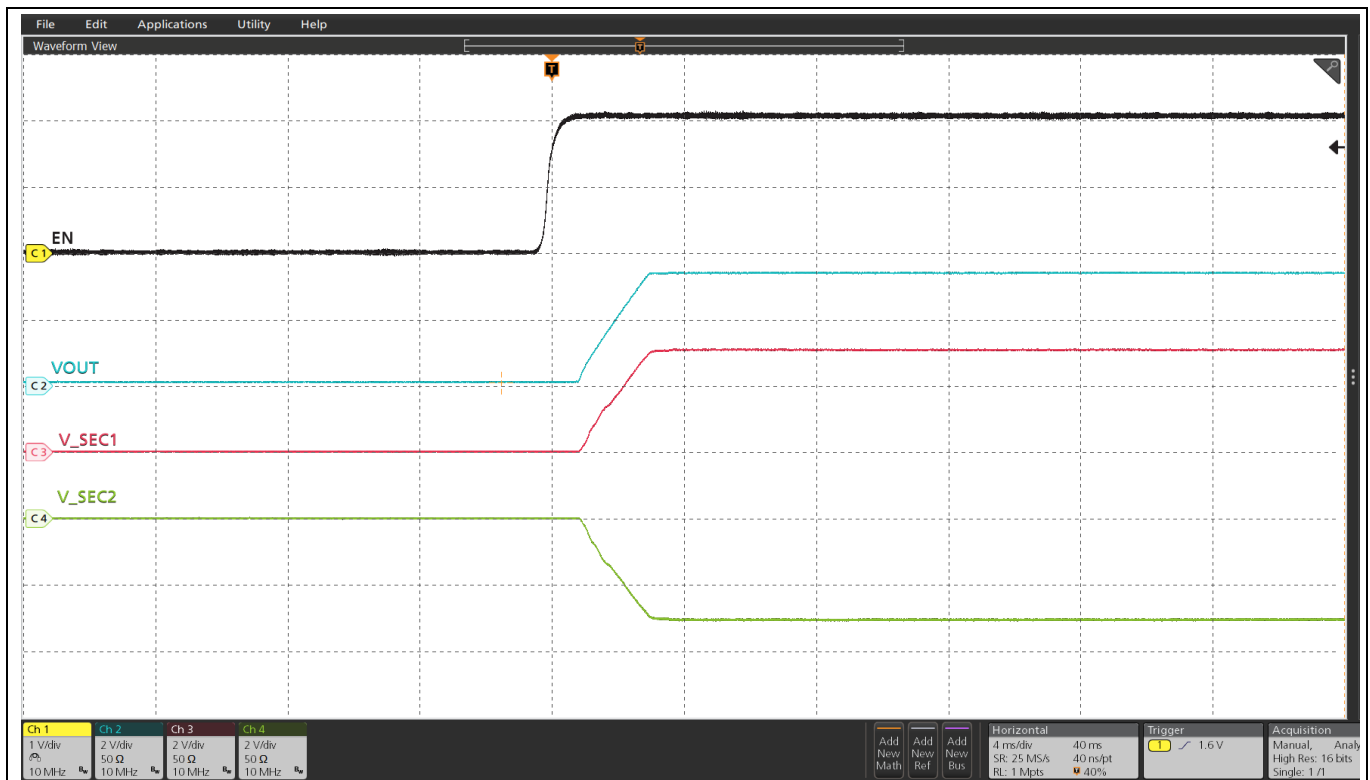

**Figure 16 Start-up by enable**

## 6.6 Shutdown with load

- $V_{out\_pri} = 3.3\text{ V}, 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}, 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}, 0.5\text{ A}$


### Oscilloscope:

- Channel 1: Enable
- Channel 2:  $V_{out\_pri}$
- Channel 3:  $V_{out\_sec1}$
- Channel 4:  $V_{out\_sec2}$

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

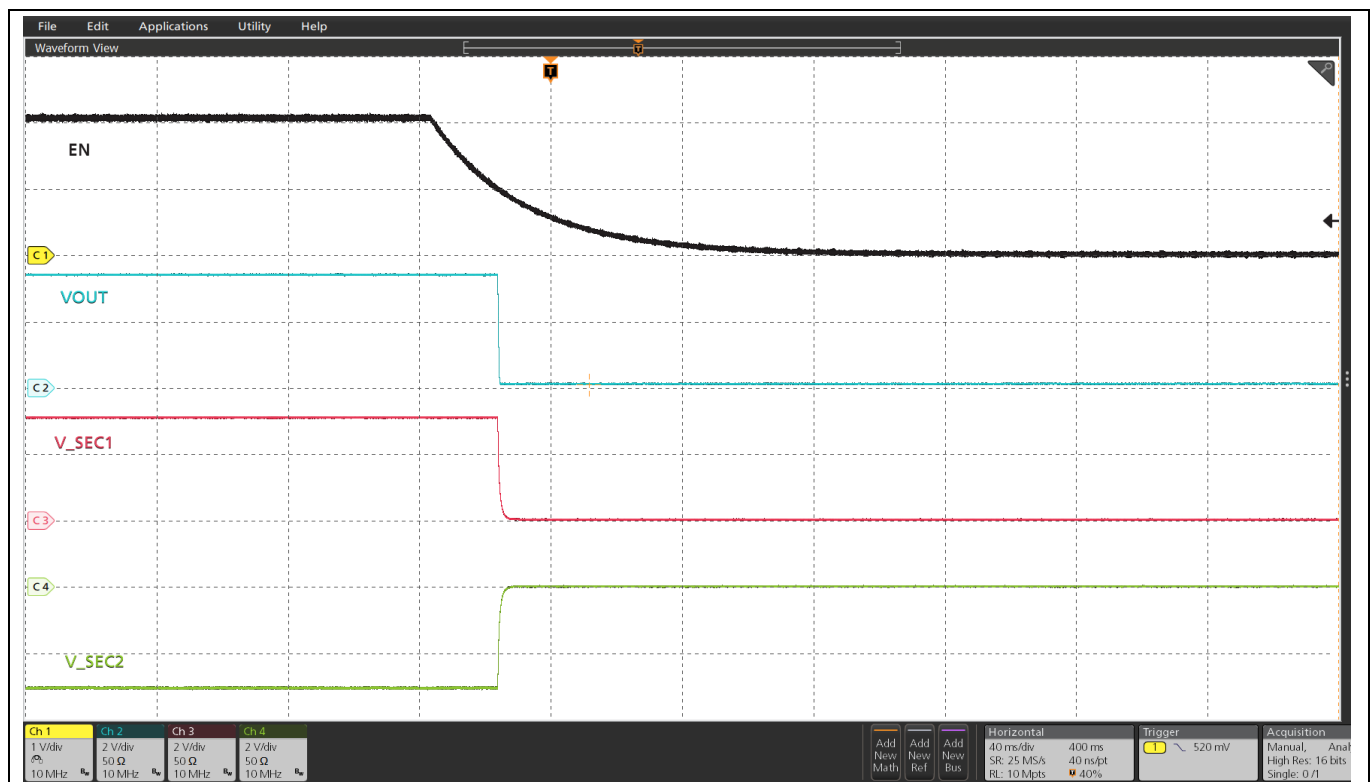

**Figure 17 Shutdown by enable**

## 6.7 Current waveform at steady state

- $V_{out\_pri} = 3.3\text{ V}, 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}, 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}, 0.5\text{ A}$


### Oscilloscope:

- Channel 1:  $V_{out\_pri}$
- Channel 2:  $V_{out\_sec1}$
- Channel 3: Primary inductor current
- Channel 4: Secondary1 inductor current

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

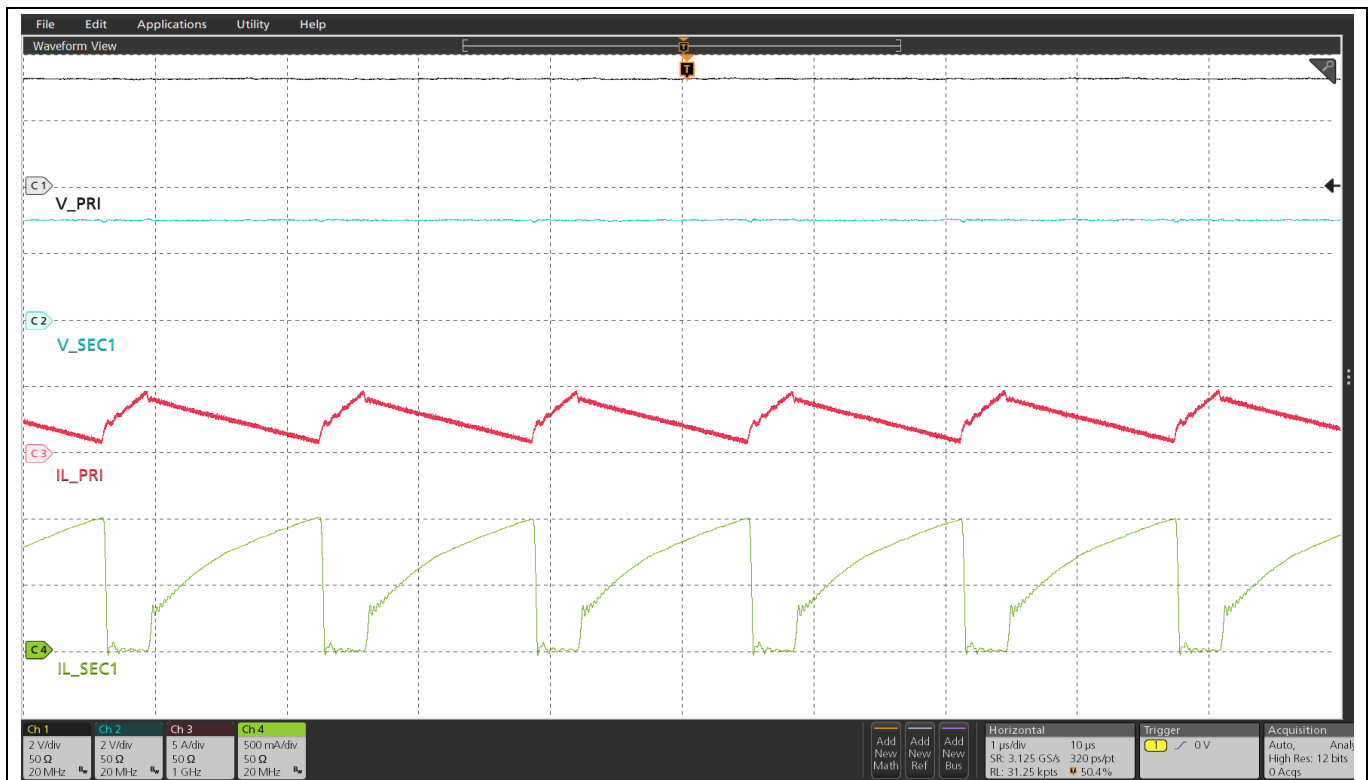

**Figure 18 Primary and secondary1 inductor current and at steady state**

- $V_{out\_pri} = 3.3\text{ V}, 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}, 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}, 0.5\text{ A}$


#### Oscilloscope:

- Channel 1:  $V_{out\_pri}$
- Channel 2:  $V_{out\_sec2}$
- Channel 3: Primary inductor current
- Channel 4: Secondary2 inductor current

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

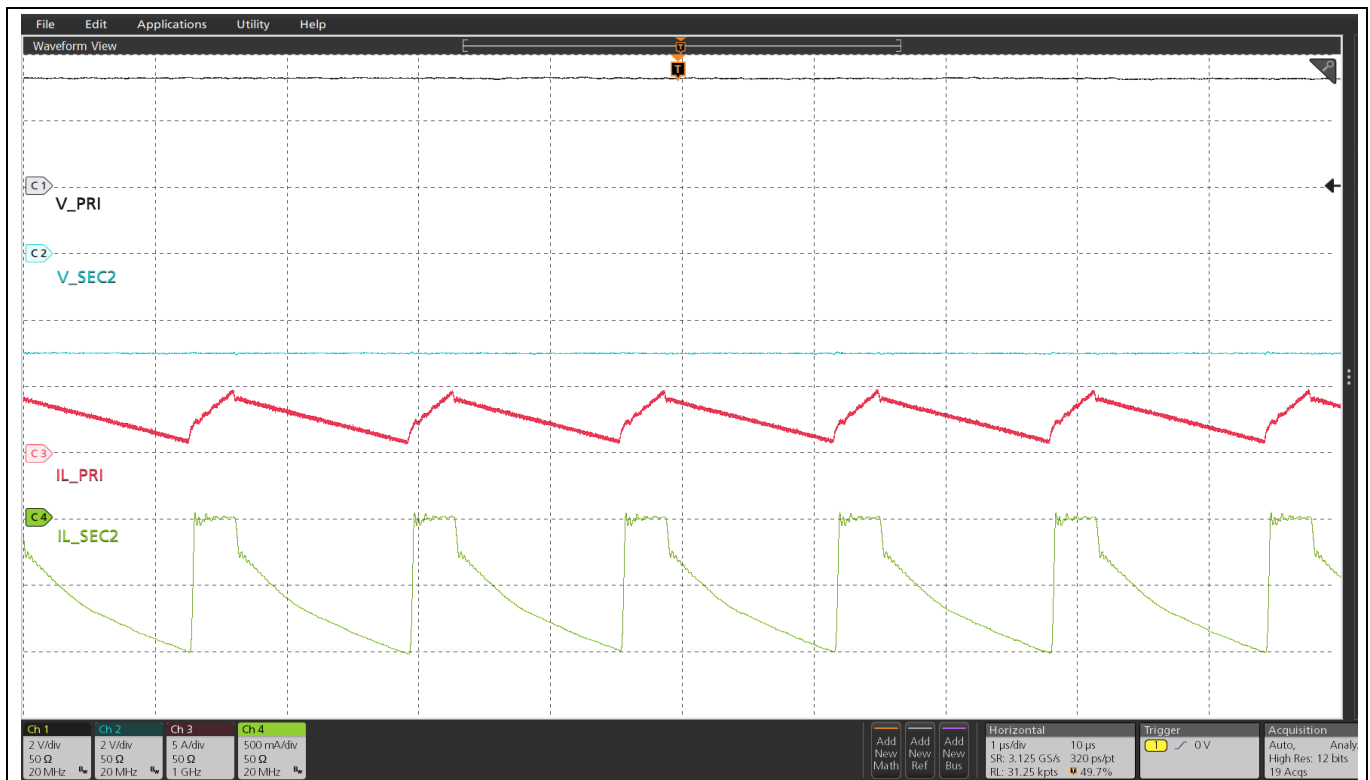

**Figure 19** Primary and secondary2 inductor current at steady state

## 6.8 Current waveform at start-up

- $V_{out\_pri} = 3.3\text{ V}, 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}, 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}, 0.5\text{ A}$


### Oscilloscope:

- Channel 1:  $V_{out\_pri}$
- Channel 2: Primary inductor current
- Channel 3:  $V_{out\_sec1}$
- Channel 4:  $I_{out\_sec1}$

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

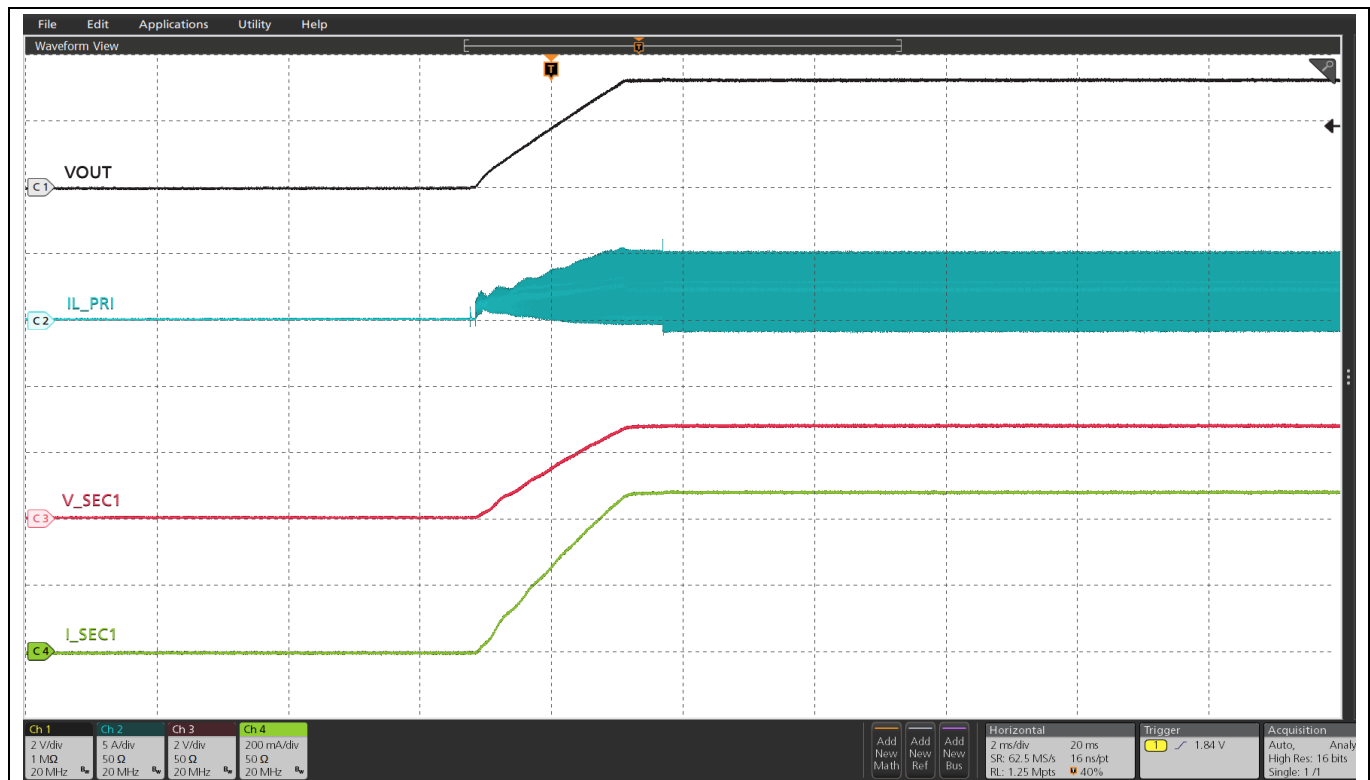

**Figure 20 Primary inductor current and lout\_sec1 waveform at start-up**

- $V_{out\_pri} = 3.3\text{ V}, 2\text{ A}$
- $V_{out\_sec1} = 3.3\text{ V}, 0.5\text{ A}$
- $V_{out\_sec2} = -3.3\text{ V}, 0.5\text{ A}$

#### Oscilloscope:

- Channel 1:  $V_{out\_pri}$
- Channel 2: Primary inductor current
- Channel 3:  $V_{out\_sec2}$
- Channel 4:  $I_{out\_sec2}$

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

### Typical operating waveforms

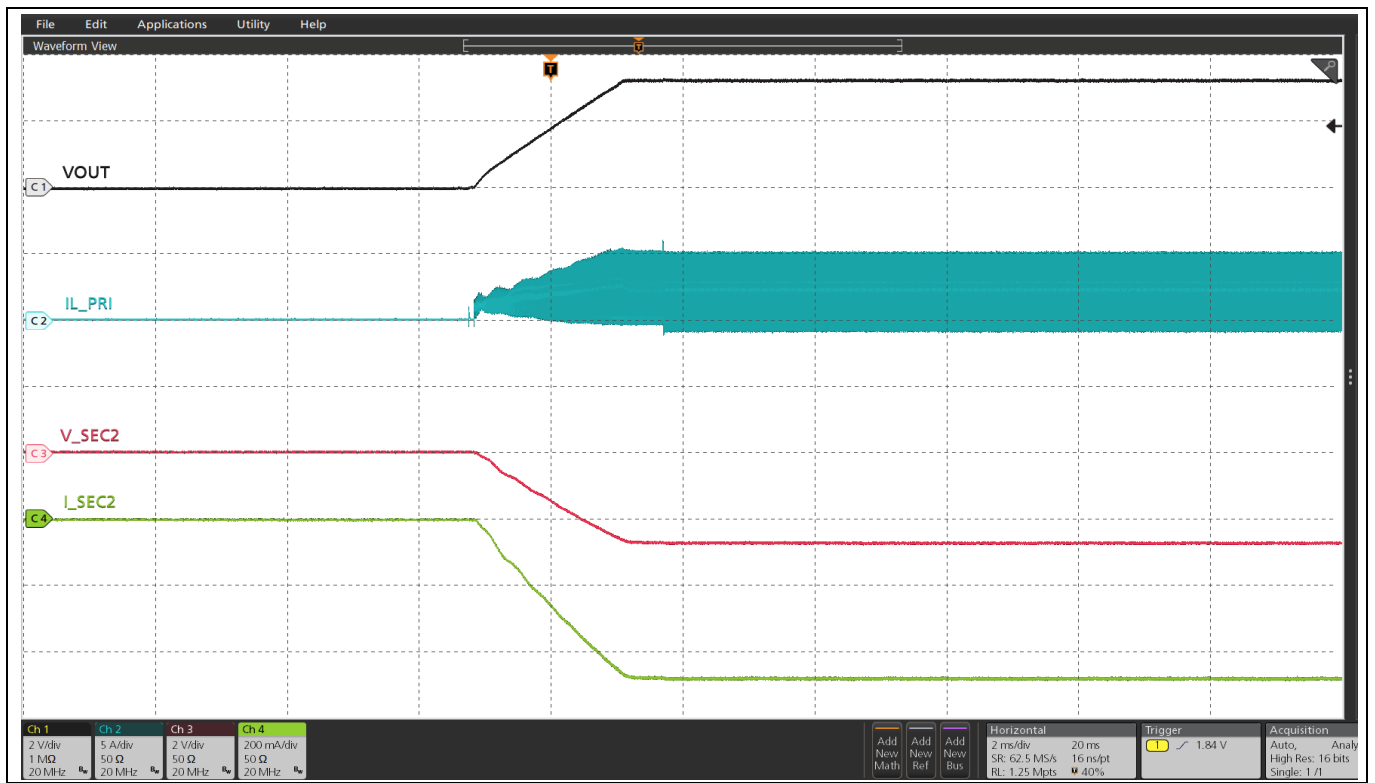


Figure 21 Primary inductor current and I<sub>out\_sec2</sub> waveform at start-up

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator

---



### References

### References

- [1] Infineon Technologies AG: *Introduction of fast COT*; [Available online](#)
- [2] Infineon Technologies AG: *TDA38825 Datasheet*; [Available online](#)

# Isolated multiple rail buck converter using TDA38825

## 20 A buck regulator



### Revision history

---

### Revision history

Document revision	Date	Description of changes
1.0	2024-07-11	Initial release

**Trademarks**

All referenced product or service names and trademarks are the property of their respective owners.

**Edition 2024-07-11**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2024 Infineon Technologies AG.**

**All Rights Reserved.**

**Do you have a question about this document?**

**Email:** [erratum@infineon.com](mailto:erratum@infineon.com)

**Document reference**

**AN085546**

**Important notice**

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

**Warnings**

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.