

30<sup>th</sup> ANNIVERSARY • 1985–2015

**APEC** 2015

**Charlotte, NC**

**March 15-19, 2015**

Applied Power Electronics Conference and Exposition

# Professional Education Seminar **S17**

## Practical Application of 600 V GaN HEMTs in Power Electronics

Monday March 16, 2015 8:30 – 12:00

Eric Persson, GaN Applications

# Seminar Outline

- Limitations of today's 600 V Silicon
- Topologies where superjunction performs well
- Topologies where superjunction application is limited
- GaN HEMT characteristics
  - Depletion-mode, cascode, enhancement-mode
  - GaN applied to hard and soft-switching topologies
- Gate drive considerations for GaN
- PFC Application examples
  - Standard boost, dual boost, totem-pole bridgeless
- LLC converter example
- ZVS phase-shifted full-bridge example
- Motor drive example

# What needs improvement?


For same  $R_{ds(on)}$ , improve all the charge parameters:

- Reduce  $C_{oss}$  nonlinearity
  - Nonlinearity makes timing and  $dv/dt$  control challenging
- Reduce  $Q_{oss}$  (and therefore  $E_{oss}$ ) magnitude
- Reduce  $C_{oss}$  dissipation factor
- Improve body diode dynamic performance
  - Reduce/eliminate  $Q_{rr}$
- Reduce gate charge
- All of the above at affordable cost


# Topologies where superjunction works well

- Unipolar current flow, hard or soft-switched
- Two-transistor forward
  - Hard switched, partial valley switched
- Boost PFC
  - CCM or CrCM
- Flyback
  - Hard switched, partial valley switched
- Why?
  - Superjunction has low  $R_{ds(on)} \cdot E_{oss}$  figure of merit
  - Body diode performance is not important

# 2-Transistor Forward Converter (2TF)

 


# 2TF voltage and current waveforms

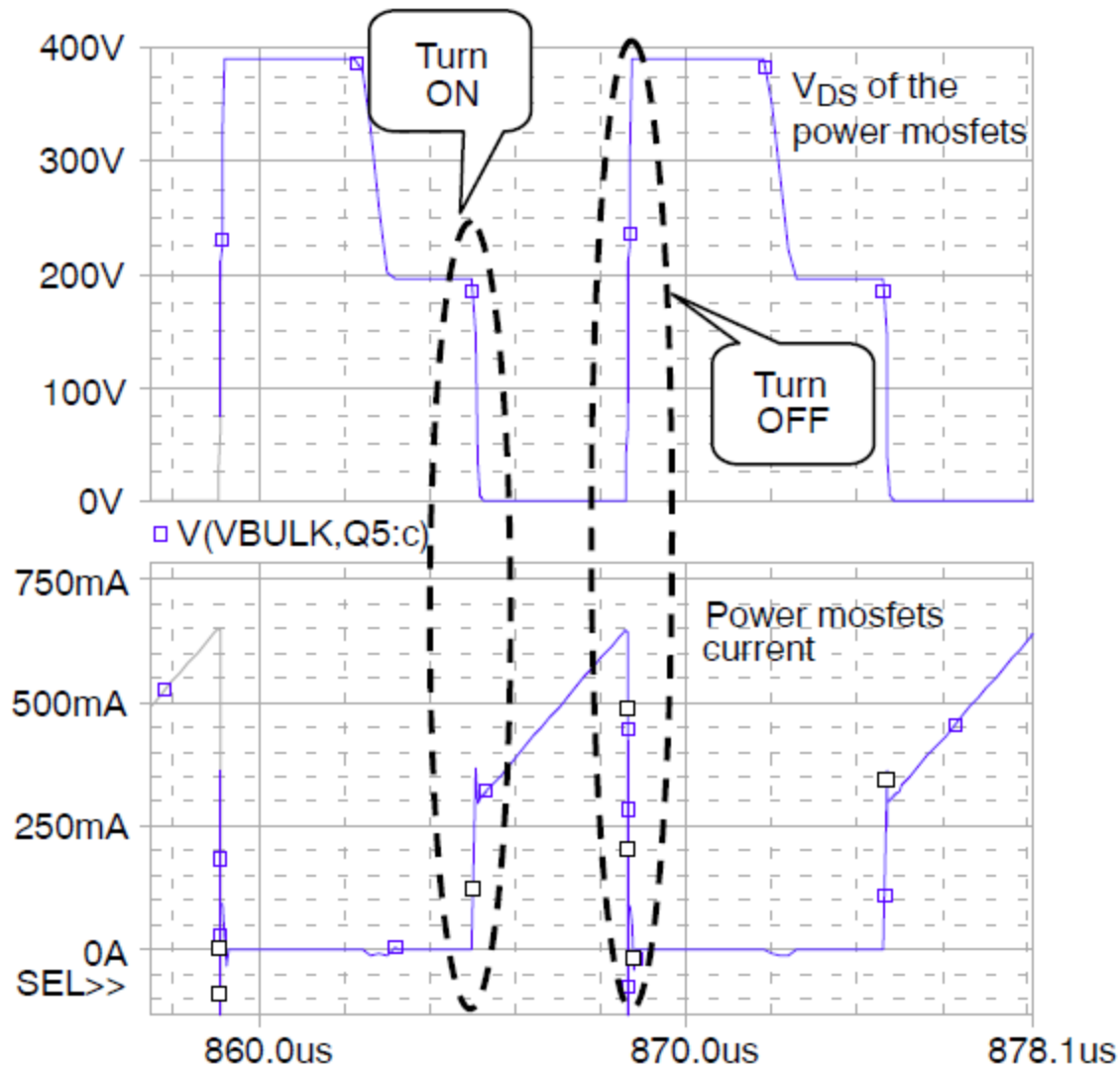

Ref: Thierry Sutto, "2 switch forward current mode converter," ON semi app note AND8373/D


# 2TF FET turn-on loss measurement

 

Ref: Thierry Sutto, "2 switch forward current mode converter," ON semi app note AND8373/D
 
# 2TF FET turn-on loss analysis

- This accounts for the “crossover” loss
  - Where the transistor is supporting simultaneous V and I



$$P_{SW,on} = F_{sw} \int_0^{\Delta t} I_D(t) V_{DS}(t) dt$$

$$= \frac{I_{p\_valley} \frac{V_{bulk}}{2} \Delta t}{6} F_{sw}$$



$$P_{SW,on} = \frac{I_{p\_valley} V_{bulk} \Delta t}{12} F_{sw}$$

- What is missing?
- This suggests that if  $\Delta t$  goes to 0, Turn-on loss = 0

Ref: Thierry Sutto, “2 switch forward current mode converter,” ON semi app note AND8373/D




# What about the Eoss of the FET itself?

 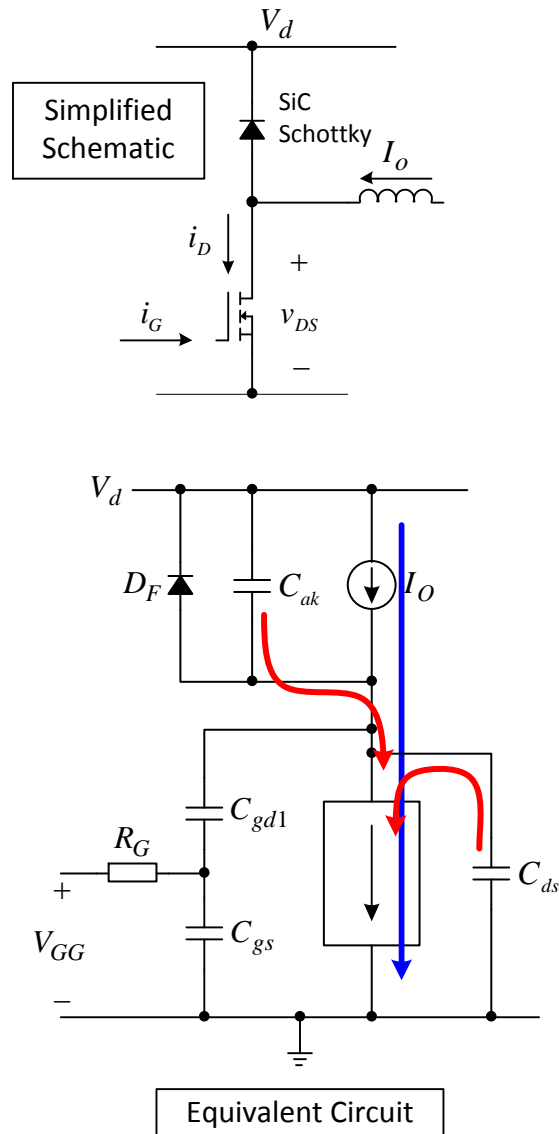
 
# 2TF FET turn-off loss

- Turn-off losses limited entirely by gate drive
  - If you can turn-off the gate extremely fast, get ZVS





Ref: Thierry Sutto, "2 switch forward current mode converter," ON semi app note AND8373/D

## 2 Transistor Forward Summary

- This is a unipolar topology
  - Superjunction already works well
  - Body diode performance is unimportant
- Switch losses are dominated by:
  - Conduction
  - Turn-on speed
  - Eoss
  - Turn-off speed
- Possible switch improvements
  - For a given  $R_{ds(on)}$ :
  - Reduced Eoss (stored energy in device Coss)
  - Reduced Qg to enable faster switching



# Flyback Converter

■ Avalanche risk

  
  
# Flyback turn-on timing is critical

- Eoss dissipated proportional to  $V_{ds}^2$
- Strong dependence on timing turn-on to waveform
  - Turning on at peak versus valley – big difference in Eoss




# Flyback Summary

- This is a unipolar topology
  - Superjunction already works well
  - Body diode performance is unimportant
  - Avalanche or overvoltage capability likely necessary
- Switch losses are dominated by:
  - Conduction
  - Turn-on speed
  - Eoss (valley switching can minimize loss)
  - Turn-off speed
- Possible switch improvements
  - For a given  $R_{ds(on)}$ :
  - Reduced Eoss (stored energy in device  $C_{oss}$ )
  - Reduced  $Q_g$  to enable faster switching
 
# Standard boost PFC

- $S_B$  typically superjunction
- $D_B$  SiC Schottky for lowest loss
- Can achieve >96% efficiency



REF: L. Huber, Y. Jang, M. Jovanovic, "Performance Evaluation of Bridgeless PFC Boost Rectifiers," IEEE TRANSACTIONS ON POWER ELECTRONICS, VOL. 23, NO. 3, MAY 2008

# Standard boost PFC

- Typical operating frequency  $< 70$  kHz
  - Keep fundamental and 2<sup>nd</sup> harmonic below 150 kHz EMI
  - Increasing frequency increases switching loss
- Control mode typically Continuous Conduction Mode
  - CCM balances ripple current losses and switching loss
- Can be operated Discontinuous or Critical mode
  - Much higher ripple current
  - But ZVS or near ZVS possible, much lower switching loss
- Either way, **dominant loss is input bridge rectifier**
  - 1-2% total efficiency loss due to input bridge
  - Even a “perfect” zero loss switch can’t make-up for bridge




# Standard boost PFC summary

- This is a unipolar topology
  - Superjunction already works well
  - Body diode performance is unimportant
- Switch losses are dominated by:
  - Conduction (especially severe for high ripple CrCM and DCM)
  - Turn-on speed
  - Eoss (only for CCM)
  - Turn-off speed
- Possible switch improvements
  - For a given  $R_{ds(on)}$ :
  - Reduced Eoss (stored energy in device  $C_{oss}$ )
  - Reduced  $Q_g$  to enable faster switching
 
# What about bridgeless PFC topologies?

- Dual boost – semi bridgeless
- S1 S2 commonly superjunction, D1 D2 SiC



Ref: A. F. Souza and I. Barbi, "High power factor rectifier with reduced conduction and commutation losses," in *Proc. Int. Telecommunication Energy Conf.*, Jun. 1999, pp. 8.1.1–8.1.5.


# Dual boost PFC summary

- This is a unipolar topology
  - Superjunction already works well
  - Body diode performance is unimportant
- Switch losses are dominated by:
  - Conduction (especially severe for high ripple CrCM and DCM)
  - Turn-on speed
  - Eoss (only for CCM)
  - Turn-off speed
- Possible switch improvements
  - For a given  $R_{ds(on)}$ :
  - Reduced Eoss (stored energy in device  $C_{oss}$ )
  - Reduced  $Q_g$  to enable faster switching

**Tradeoff: eliminate 1 diode drop, add an entire boost stage**


 
# Why not totem-pole PFC with superjunction?

- Hard-switched half-bridge requires good body-diode



REF: J. C. Salmon, "Circuit topologies for PWM boost rectifiers operated from 1-phase and 3-phase ac supplies and using either single or split dc rail voltage outputs," *APEC*, Mar. 1995, pp. 473–479.

# Hard-switched half-bridge

  

# Summary: topologies with limited superjunction use


- Bipolar current flow topologies
  - Anywhere diode recovery is important
- Half-bridge hard-switching
  - Totem-pole bridgeless boost CCM (except line polarity switch)
  - Inverters, motor drives
- Half-bridge soft-switching or resonant? Depends...
  - Limited frequency range
  - Risk of hard-switching
  - Frequency dependent losses in  $Q_{oss}$

# GaN High Electron Mobility Transistor (HEMT)

- Depletion-mode basic HEMT
  - Normally-on is a problem for power electronics
- 2 methods to achieve normally-off
  - Cascode
  - Enhancement-mode
- GaN cascode characteristics
- GaN enhancement-mode characteristics
- GaN application summary
  - Hard-switching
  - Soft-switching & resonant
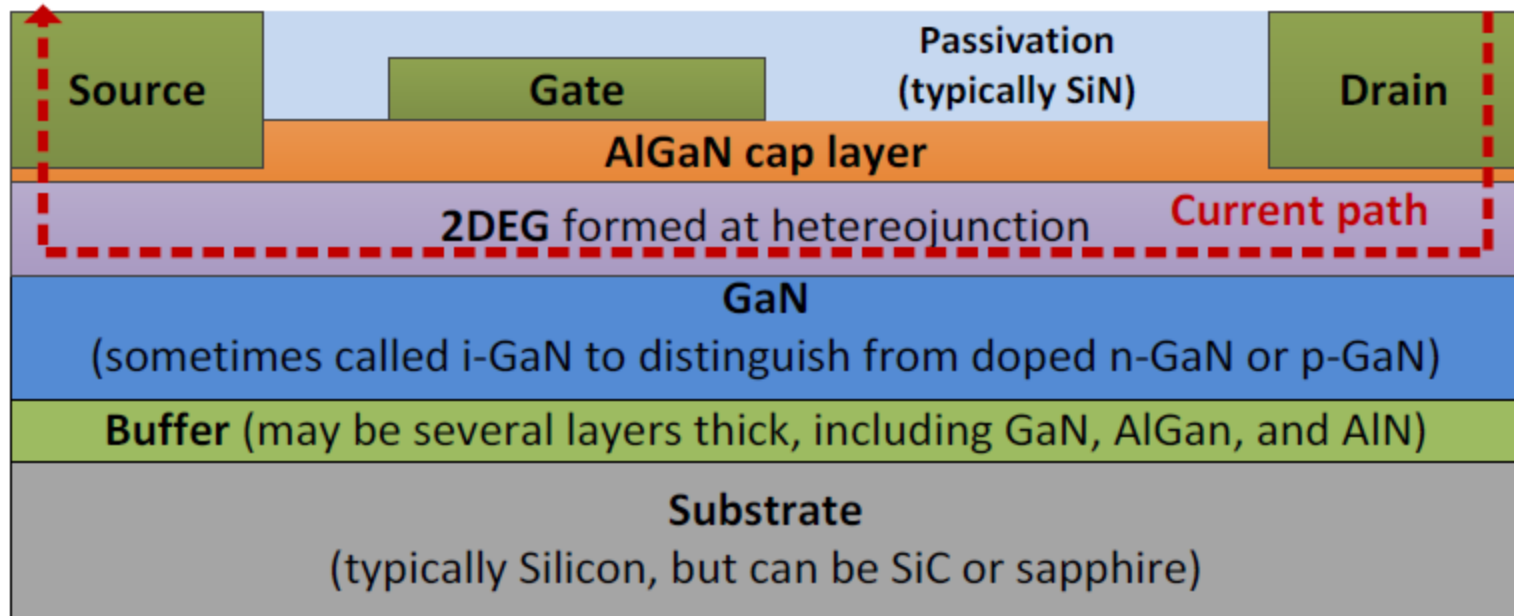
# GaN High Electron Mobility Transistor (HEMT)

- Depletion-mode (normally-on) HEMT
- Si substrate for low cost
- Normally-on potential problem for power electronics



Ref: Jones, E.A.; Wang, F.; Ozpineci, B., "Application-based review of GaN HFETs," Wide Bandgap Power Devices and Applications (WiPDA) 2014, pp.24-29, 13-15 Oct. 2014




# Depletion-mode HEMT

- Normally-on
  - Essentially a resistor that can be turned-off with -gate bias
  - Potential issues with power-up and power-down
  - Requires additional master enable switch
  - Requires negative gate drive
- Low area specific on-resistance
- Bi-directional conduction
  - No intrinsic body diode
- Can be made bi-directional blocking
- Lateral device – monolithic integration possibilities


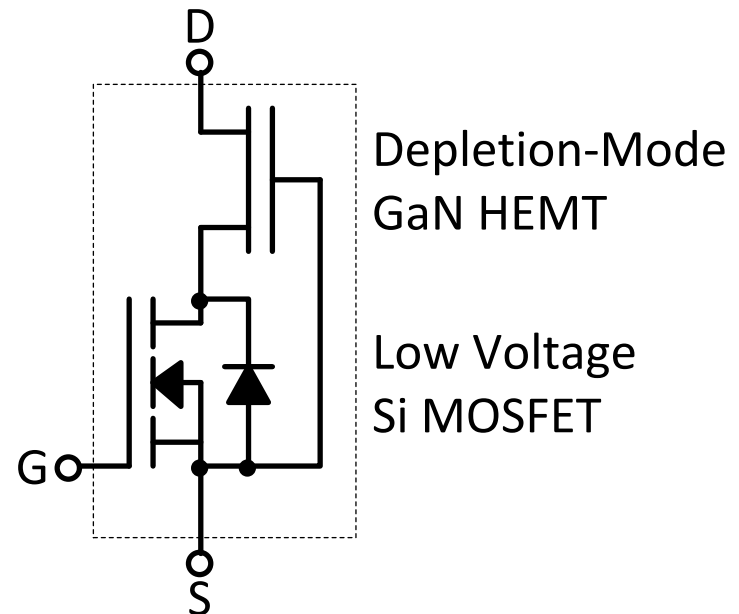
# Cascode Provides Normally-OFF Function

- Native d-mode GaN HEMT + LV Si FET in cascode
  - $R_{ds(on)}$  is compromised to shift threshold positive
- Cascode has easy gate drive
- Cascode includes excellent body diode
- 2-chip solution no more difficult than IGBT
- Almost zero “Miller Effect”
  - C dv/dt immunity
  - Enables turn-off ZVS in almost any topology



Hybrid Semiconductor Device, US Pat. 8,017,978  
Hybrid semiconductor device having a GaN transistor and  
a Silicon MOSFET, US Pat. 8,368,120


# Cascode Conduction Modes

  

Ref: Xiucheng Huang, Fred C. Lee, Qiang Li, "Characterization and Enhancement of 600V Cascode GaN Device," CPES PMC Review, March 11, 2015

# Body diode reverse-recovery

- >100x lower  $Q_{rr}$  for GaN cascode

 


# Comparing GaN cascode to superjunction

## ■ 1<sup>st</sup> Generation GaN cascode

Parameter	GaN cascode	Equivalent SJ	
Package	6x8 mm PQFN	8x8 mm PQFN	GaN 25% smaller package
Vdss	600 V	650 V	
Rdson typ 25°C	135 mΩ	115 mΩ	
Rdson typ 125°C	225 mΩ	230 mΩ	GaN 1.67x; SJ 2x
Qg (10V Vgs, 480V Vds)	8.8 nC	35 nC	GaN ~4X lower than SJ
Qrr (100A/μs, 25°C)	49 nC	6,400 nC	GaN >100X lower than SJ
Coss (400V)	47 pF	53 - 579 pF	Energy vs time equivalent
Rθ J-C (°C/W)	1.65	1.22	Consistent with package

 
# Turn-on waveform, 135 mΩ (typ) cascode

- Hard-switching  $R_g = 2\Omega$ .  $\sim 9 \mu\text{J}$   $E_{\text{ON}}$


 
# GaN HEMT Safe Operating Area



- Measured destruct current >2x higher than calculated thermal limit



- Lines represent calculated thermal limit – points are measured failures
  
# GaN performance interdependent on package

- Two key factors for minimizing losses:
  - Minimize GaN – Si interconnect inductance
  - Eliminate common-source inductance with Kelvin connection




REF: Z. Liu, X. Huang, FC Lee, Q. Li, "Investigation of Package Influence on High Voltage Cascode GaN HEMT with Simulation Model," CPES review 2-13-2013, Milpitas, CA


 
# Die-on-die cascode construction


- Minimizes parasitic impedance between HEMT and FET
  - Faster switching transitions, less ringing and overshoot




US Pat. No. 8,847,408

# E-mode GaN HEMT Structures

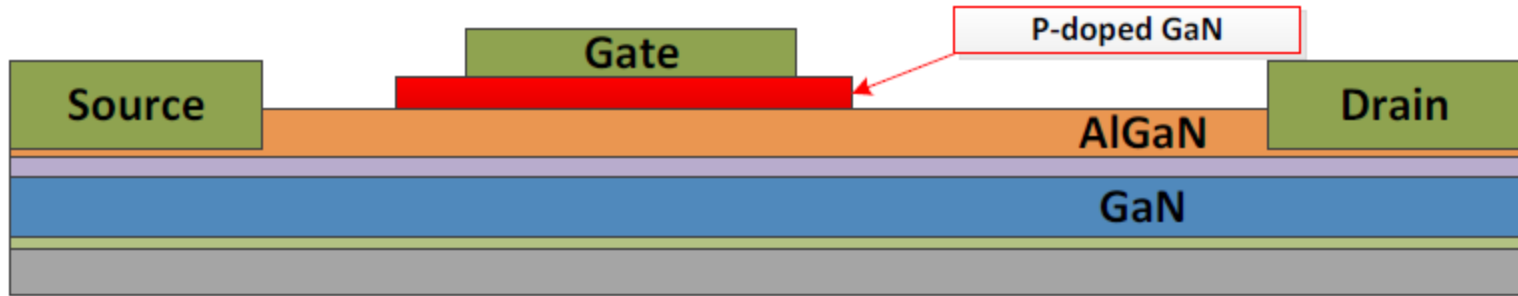- a) P-gate enhancement-mode
- b) P-gate enhancement-mode (gate injection)




(a)

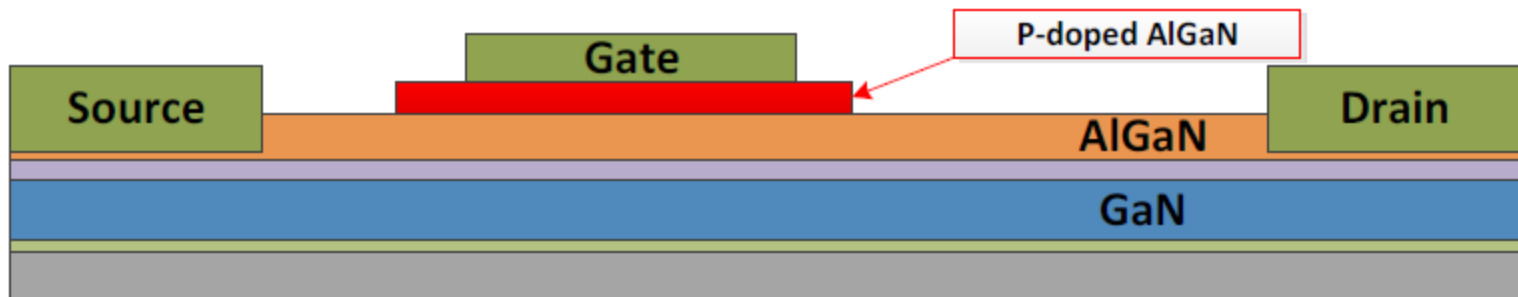


(b)

Ref: Jones, E.A.; Wang, F.; Ozpineci, B., "Application-based review of GaN HFETs," Wide Bandgap Power Devices and Applications (WiPDA) 2014, pp.24-29, 13-15 Oct. 2014

# Enhancement-Mode HEMT (Gate Injection)

 

 $V_g = 0V$   
p-gate potential depletes the channel under the gate  
↓  
No drain current




$V_g > V_f$  of GaN-PN junction  
Hole injection  
↓  
Electron generation  
↓  
Large drain current  
(conductivity modulation)

Ref: [http://www.semicon.panasonic.co.jp/en/news/contents/2013/apec/panel/APEC2013\\_GaN\\_FPD\\_WEB.pdf](http://www.semicon.panasonic.co.jp/en/news/contents/2013/apec/panel/APEC2013_GaN_FPD_WEB.pdf)
 
# Gate Characteristics (Enhancement Mode)


- Typical non-insulated gate characteristic
  - Gate injection uses small DC current (e.g. 10 mA)



Ref: Jones, E.A.; Wang, F.; Ozpineci, B., "Application-based review of GaN HFETs," Wide Bandgap Power Devices and Applications (WiPDA) 2014, pp.24-29, 13-15 Oct. 2014

 
# Output Characteristics (Enhancement Mode)

- HEMT turns back ON when drain goes below G, S





Ref: Jones, E.A.; Wang, F.; Ozpineci, B., "Application-based review of GaN HFETs," Wide Bandgap Power Devices and Applications (WiPDA) 2014, pp.24-29, 13-15 Oct. 2014

# Reverse Bias Diode-Like Behavior

 


Equivalent Circuit  
when  $V_g = 0$

  

$S'$  = drain *acting* as source in reverse bias  
 $D'$  = source *acting* as drain in reverse bias
 
# Forward and Reverse I-V Characteristics


- HEMT eventually saturates at very high current



Ref: [http://www.semicon.panasonic.co.jp/en/news/contents/2013/apec/panel/APEC2013\\_GaN\\_FPD\\_WEB.pdf](http://www.semicon.panasonic.co.jp/en/news/contents/2013/apec/panel/APEC2013_GaN_FPD_WEB.pdf)

 
# GaN, superjunction, (& SiC) transfer curves

- Cascode superjunction and SiC  $\sim 135 \text{ m}\Omega$  typical
- E-mode GaN (non GIT)  $\sim 50 \text{ m}\Omega$  ( $135 \text{ m}\Omega$  @  $150^\circ\text{C}$ )





# Comparing GaN vs SJ Qoss

 

**Fig. 5, Comparison of the charge stored in the output capacitance  $Q_{oss}$  for different CoolMOS devices and potential SiC and GaN devices.**



REF: M. Treu, E. Vecino, M. Pippan, O. Häberlen, G. Curatola, G. Deboy, M. Kutschak, U. Kirchner, "The role of silicon, silicon carbide and gallium nitride in power electronics," IEEE International Electron Devices Meeting, December, 2012

# Comparing Coss, Qoss, Eoss GaN vs SJ

Blue = superjunction

Red = e-mode HEMT

  Both  $\sim 70 \text{ m}\Omega$  max  $R_{ds(on)}$




# Comparing GaN vs superjunction turn-off

- LLC topology looking at low-side switch
  - 400 V bus, 2 A
  - Same  $R_{ds(on)}$

Superjunction

Cascode GaN

 

# Avalanche and overvoltage

- Superjunction has junction with avalanche capability
  - Useful in circuits with unclamped inductive energy (flyback)
- GaN has no junction, no avalanche behavior
  - GaN ultimately breaks down destructively at  $\sim 2\times$  rating
  - Overvoltage spikes are allowed depending on supplier
- GaN is best suited for half-bridge topology
  - Fast body diode helps to mitigate overvoltage spikes
  - Overvoltage spikes are clamped to bus
  - With proper design, no risk of breakdown

# GaN Device Summary


- Both cascode and enhancement mode – compared to superjunction:
- Provides MUCH lower  $Q_{rr}$  (zero for e-mode)
  - Enables use of efficient half-bridge topologies
- Provide smaller, more linear  $Q_{oss}$ 
  - Reduces deadtime in resonant and ZVS circuits
- Provide lower gate charge  $Q_g$ 
  - Lower gate drive power and faster switching speed
- $E_{oss}$  not much difference
- Does not have avalanche behavior
  - Does have overvoltage capability

# Applications of GaN

# Gate Drive

- Cascode – standard Si gate drivers work
  - $V_{gs(th)}$  is potential issue
  - Common Source Inductance is a concern as always
  - $C \, dv/dt$  induced gate currents
  - Kelvin gate-source connections
  - Advantages of floating gate drive


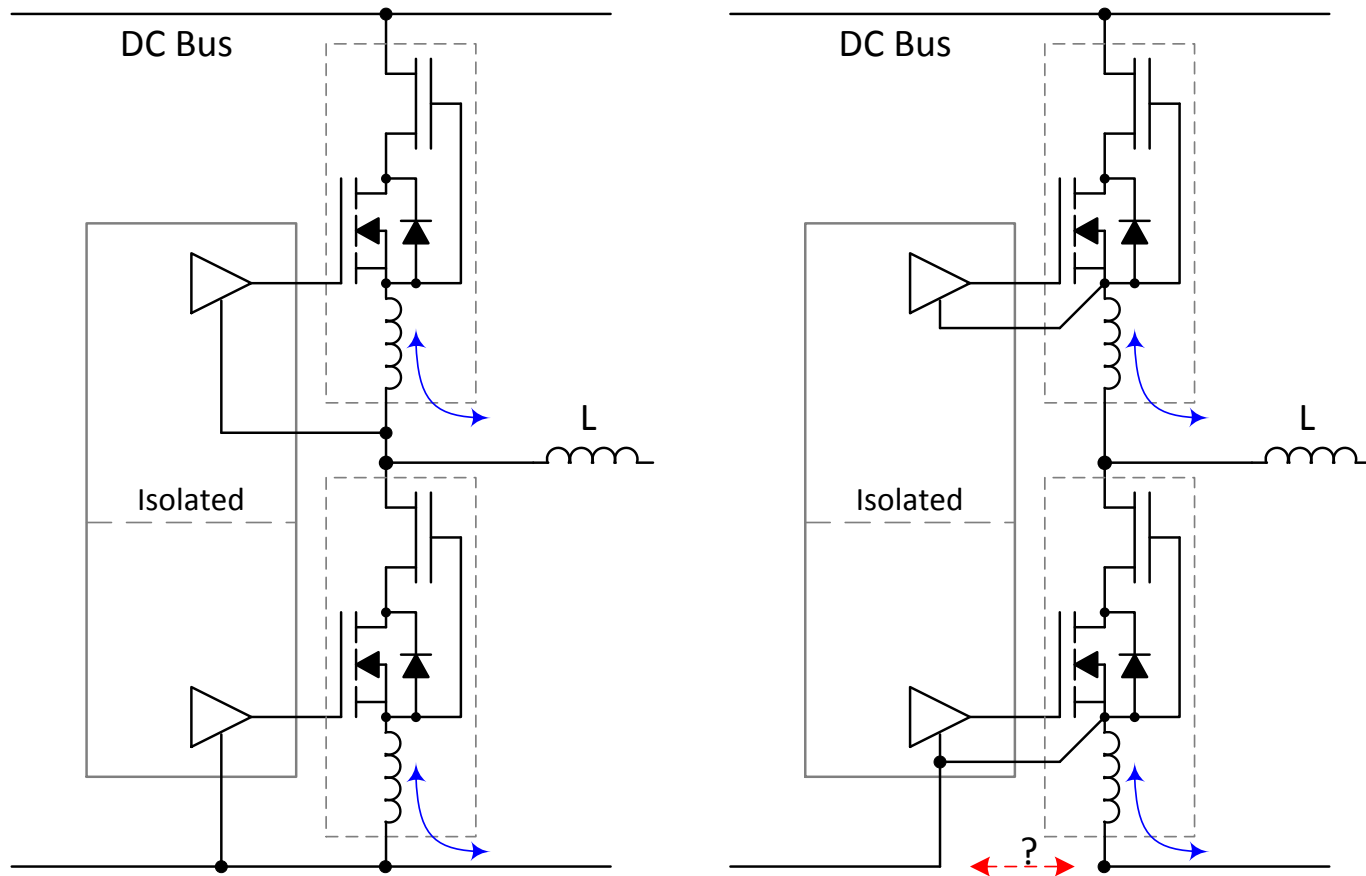
# Gate drive challenges for low threshold devices



- Common Source Inductance distorts  $V_{gs}$
- Kelvin source connection eliminates CSI
- ...BUT can cause system grounding problems for driver




 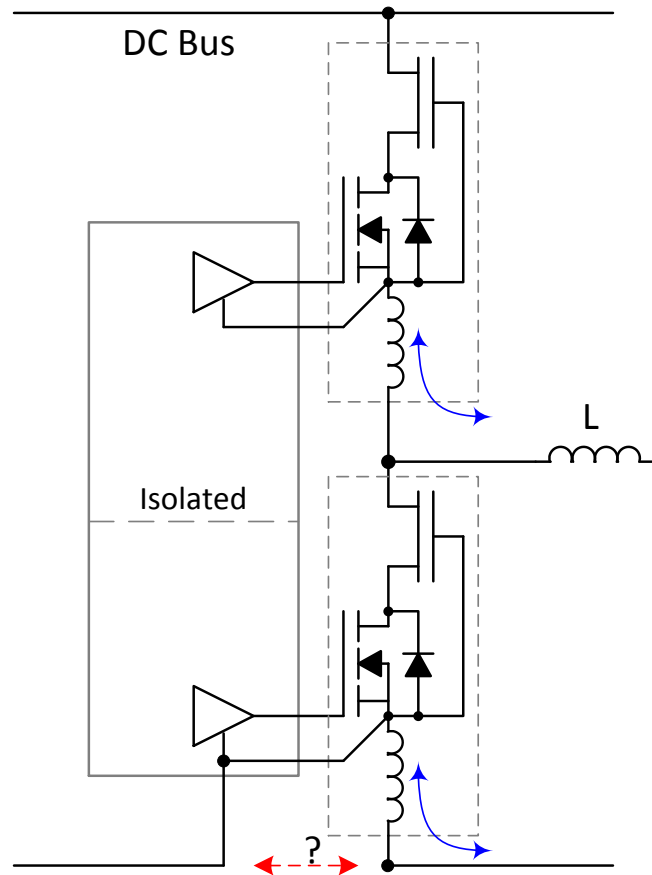
# Isolated gate drive + Kelvin source connection




- Isolating both high and low-side drivers solves system ground bounce issues which can affect current sense and logic ground

# Gate drive for gate injection

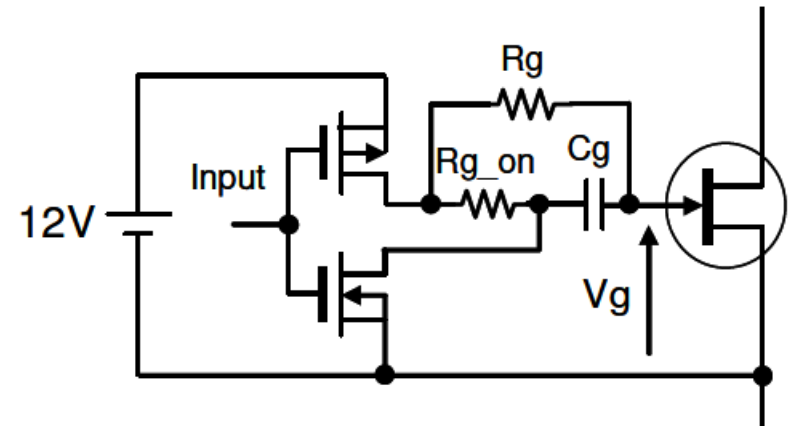 

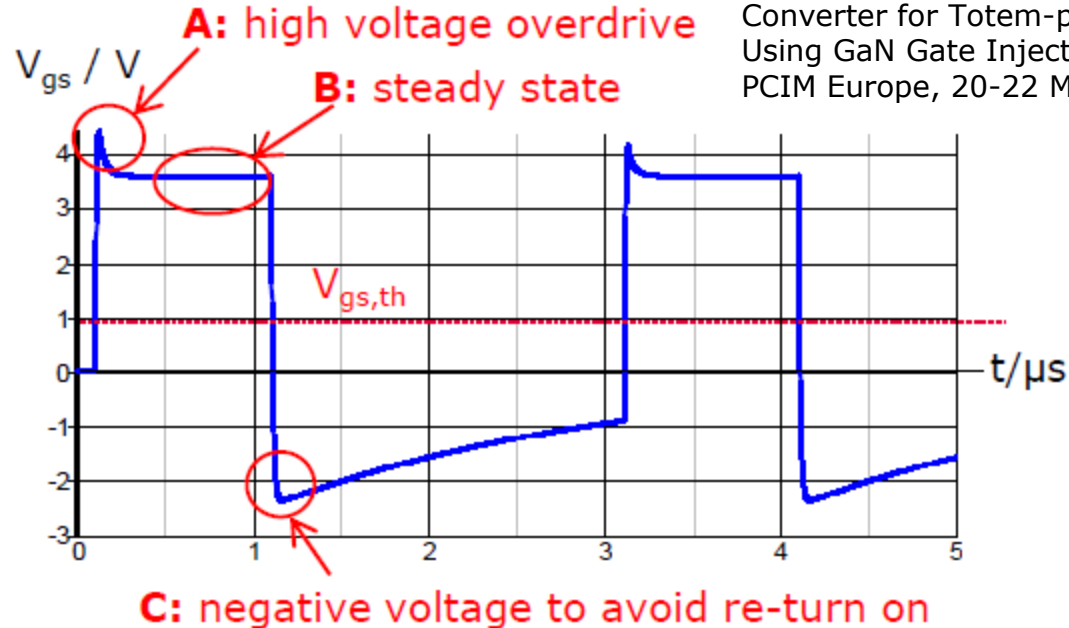
REF: T. Morita, H. Hanada, S Ujita, M Ishida, T. Ueda, "99.3% Efficiency Boost-up Converter for Totem-pole Bridgeless PFC Using GaN Gate Injection Transistors," Proc. PCIM Europe, 20-22 May 2014



# Gate drive summary


- Cascode GaN:
  - Standard FET gate driver compatibility
  - Lower  $Q_g$  for given current-handling capability
  - ZVS turn-off easier to achieve
- Enhancement-mode GaN
  - Low threshold, noise sensitivity, negative drive can help
  - Tighter limits on  $V_{gs}$
  - *Very* low  $Q_g$
  - Kelvin source connection mandatory
  - Floating driver helpful especially at higher power

# Totem-Pole PFC Full-Bridge

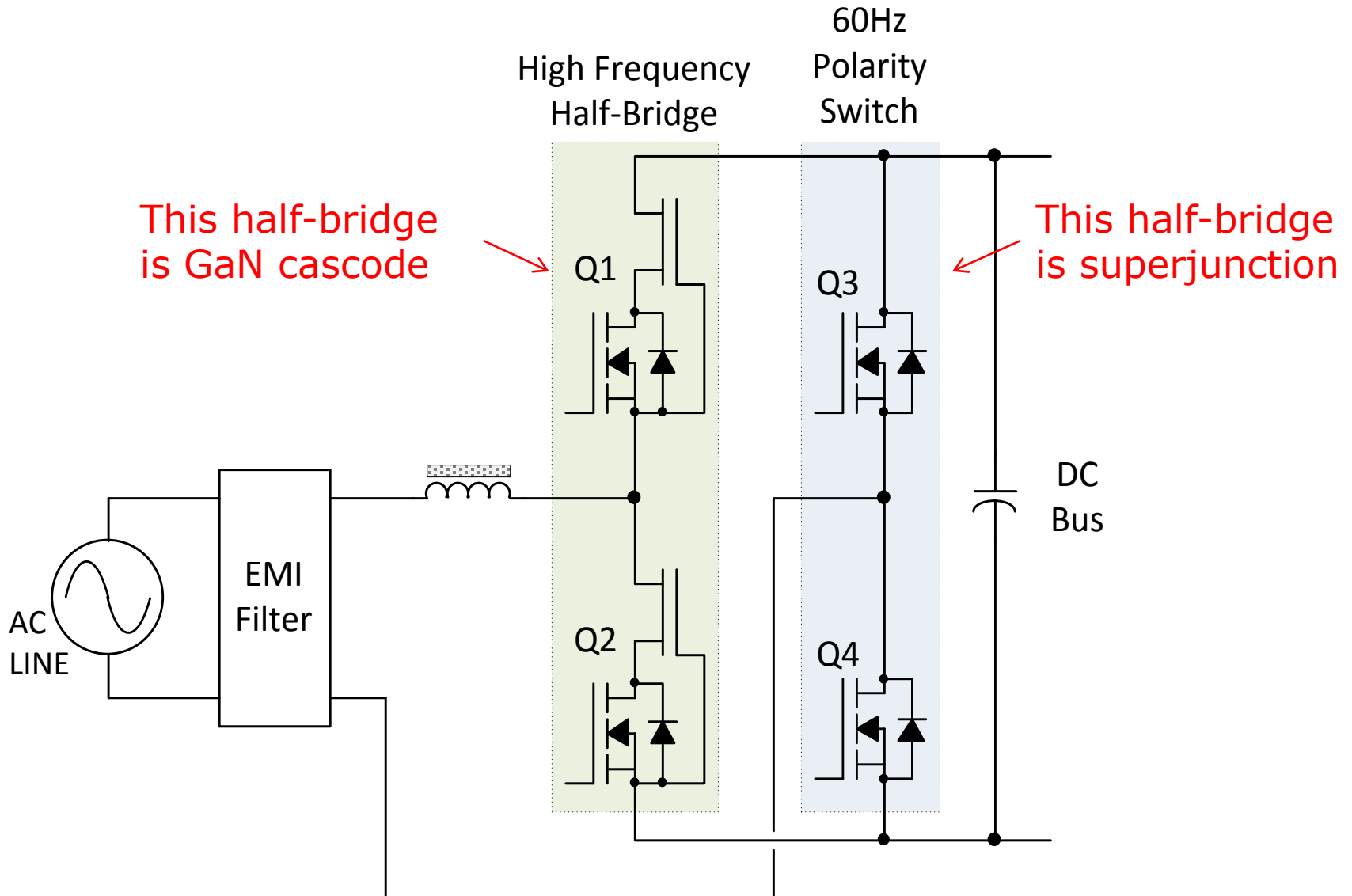


# Totem-Pole PFC Full-Bridge

 - 2.5 kW all SMD power stage proof-of-concept
- GaN boost stage 70 mΩ max enhancement-mode
- superjunction sync line rectifiers




Bottom View of PCB

 

 
# Totem-Pole PFC Full-Bridge

- Input 230 V<sub>AC</sub>
- Output 400 V<sub>DC</sub>, 6.25 A
- CCM 45 to 65 kHz



# Totem-Pole PFC full-bridge performance

- >99% efficiency from 18-70% load

 

Complete Power Stage.  $V_{in}=230$  V,  $T_{amb}=25^{\circ}$  C


# Totem Pole PFC

- No diode drops – only switch conduction voltage
- Very high efficiency possible  $>99\%$
- Lower component count than other bridgeless topologies
- Topology is enabled by GaN HEMT
  - Traditional Si FETs have too much body-diode  $Q_{rr}$   
Large recovery currents and high losses
- Topology is Intrinsically bi-directional power flow
  - Can also be used in inverter/UPS applications


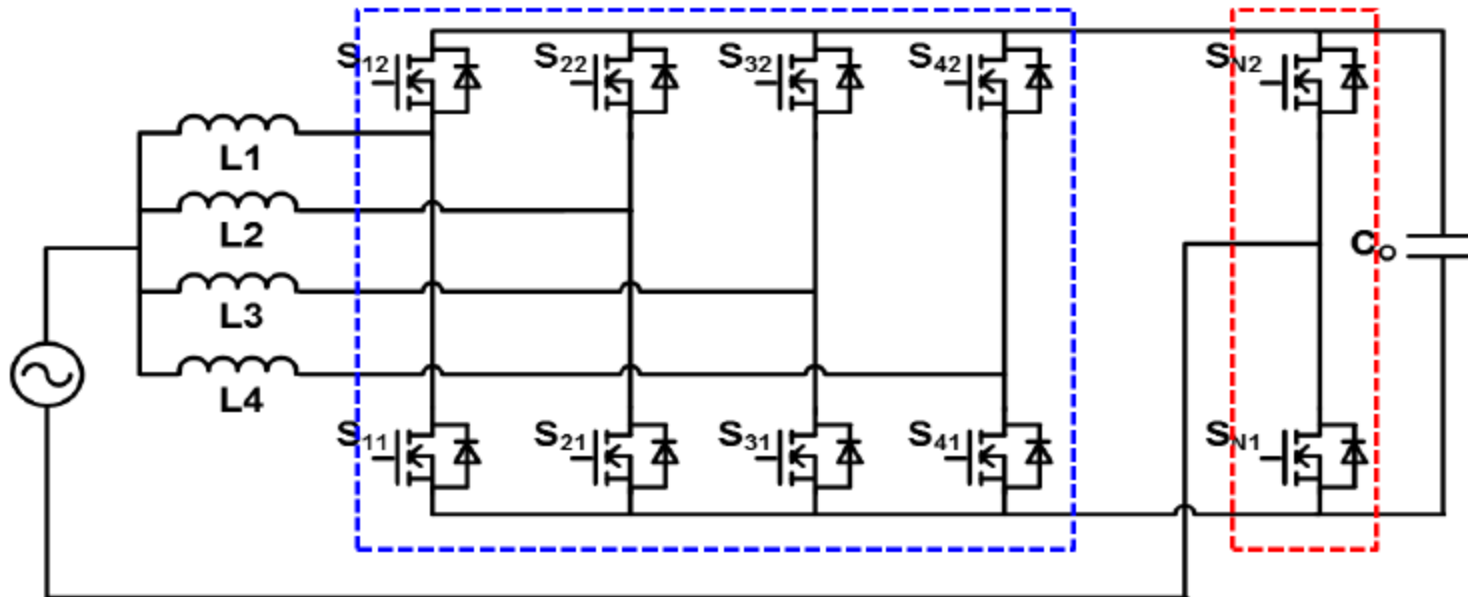
# Totem Pole PFC Future


- MHz ZVS – still achieving 99% efficiency
- Multiphase architectures to minimize ripple
- Digital control to optimize performance & efficiency




Ref: Zhengyang Liu, Fred C. Lee, QiangLi, "Digital Control for MHz Totem-pole PFC Rectifier," CPES PMC Review, Mar.11, 2015
 
# LLC Resonant DC-DC


- Popular topology today using superjunction
- Frequency range <200 kHz typically
- Caution required to prevent hard-switching



# LLC typical waveforms and circuit

 


*Square wave generator*

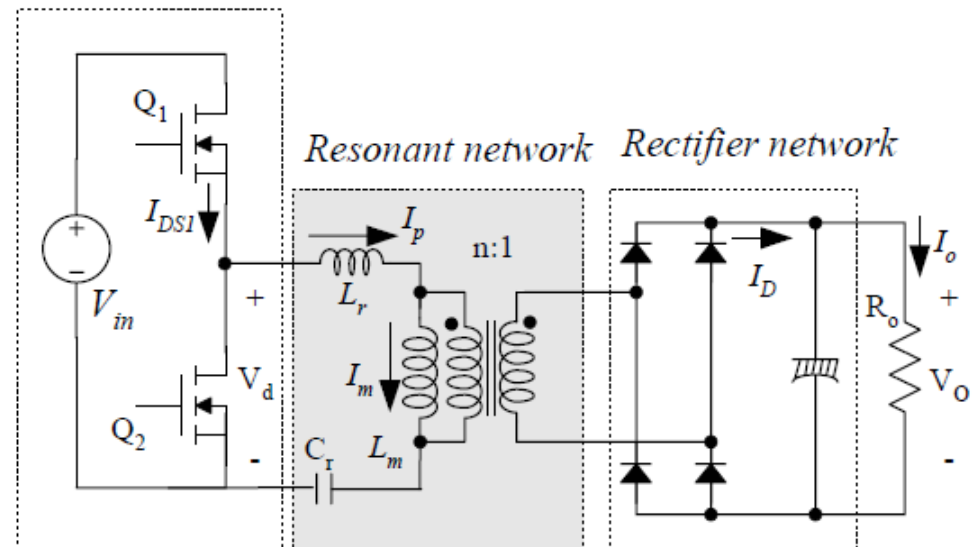


# GaN enables shorter deadtime vs SJ @ 1MHz

## ■ Shorter deadtime lowers rms current

	I <sup>2</sup> Primary	I <sup>2</sup> Secondary	Gate Drive
GaN	3.84A <sup>2</sup>	48.0A <sup>2</sup>	0.24W
Superjunction	4.93A <sup>2</sup>	64.6A <sup>2</sup>	1.88W
Difference	+28.3%	+34.6%	+685%

 


# Nonlinear Qoss Charge Affects Deadtime

 

# Cascode Charge Balance During ZVS Turn-ON


Improper charge balance results in loss of ZVS

- Significant energy loss

 

Properly balanced Cascode achieves full ZVS

- No energy loss

 


Measured Results: IR-Infineon Cascode

X. Huang, W. Du, Z. Liu, F. C. Lee, and Q. Li, "Performance Analysis of Cascode GaN Device," CPES Review, Nov 18, 2013

# Cascode Charge Balance During ZVS Turn-OFF


Improper charge balance results in Si avalanche

- Significant energy loss

 

Properly balanced Cascode no avalanche, full ZVS

- No energy loss

 


Measured Results: IR-Infineon Cascode

X. Huang, W. Du, Z. Liu, F. C. Lee, and Q. Li, "Performance Analysis of Cascode GaN Device," CPES Review, Nov 18, 2013
 
# ZVS phase-shifted full-bridge


- ZVS over most of power range except light-load
- Current-doubler output effective for 12 V and below






 
# ZVS phase-shifted full-bridge

- 1 kW 380 V to 12 V
- 350 kHz
- 120 W/in<sup>3</sup>




# ZVS phase-shifted full-bridge

## ■ Waveforms at 50% load

  


# ZVS phase-shifted full-bridge efficiency

## Efficiency vs Percentage Load

 

# Efficiency vs Frequency at half-load

 
## ■ Comparing GaN cascode vs superjunction





Freq [Khz]	Efficiency_GaN [%]	Efficiency_SJ [%]
100	96.7	96.5
200	96.5	96.2
300	96.4	95.4
350	96.3	95
400	95.9	94
450	95.6	
500	95.4	
 
# Why GaN for Motor Drive Applications?

- Switching speed is not necessarily a key issue for drives:
- Typically want  $dv/dt < 6V/ns$  (GaN can switch  $> 10x$  faster)
  - $I=C dv/dt$  currents in motor windings can result in failures
  - Corona and partial-discharge creates ozone and erodes insulation
  - Common-mode currents forced through bearings, eroding races
- Yet customers still want higher efficiency, increased density
- Compressor drives have even more constraints:
  - Very low leakage current mandates small Y-cap values (EMI)
  - Newer “green” refrigerants have very high permittivity
- Goal is to improve light-load efficiency ( $< 25\%$  of full power)
- EU2013 directive for Energy Saving A+++ Class
- Reducing losses also improves packaging density




# Typical Compressor Drive Today

 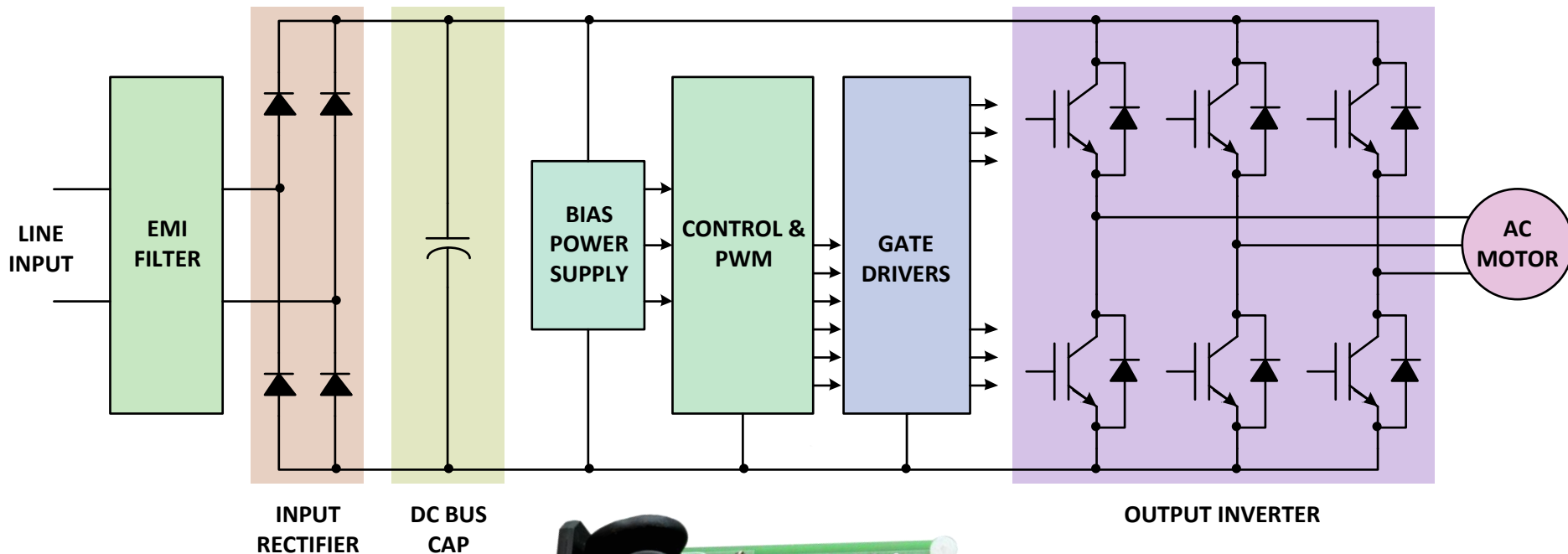

 
# Conduction Voltage for Same Footprint Size

Comparing Conduction voltage of IGBT vs FET (measured data)



# Total Power Loss Summary (per switch)

 




# Cascode GaN dv/dt control via Gate Modulation

2A Turn off


2A Turn on

 

- Dv/dt control possible by modulating cascode gate-drive current
- This places HEMT in linear region increasing switching times and losses
- Unknown if this affects long-term reliability – further study needed
 
# GaN HEMT Short-Circuit Capability

- Initial devices are high-gain – limited SCSOA
  - Typically  $\sim 1 \mu\text{s}$  @ 300V
- Likely tradeoff between gain and SCSOA similar to IGBTs



Ref: Xing Huang; Dong Young Lee; Bondarenko, V.; Baker, A.; Sheridan, D.C.; Huang, A.Q.; Baliga, B.J., "Experimental study of 650V AlGaIn/GaN HEMT short-circuit safe operating area (SCSOA)," Proc. ISPSD pp.273,276, 15-19 June 2014

# Summary

- GaN HEMTs offer performance improvements for power electronic applications
  - Benefits are strongly topology-dependent
  - Just dropping GaN into existing circuit may show little benefit
- Half-bridge topology is good match for GaN
  - Half-bridge requires good dynamic reverse conduction
  - Both cascode and e-mode GaN devices benefit half-bridge
- Higher efficiency at same frequency
  - By use of better topologies i.e. totem-pole PFC
- Higher frequency at high efficiency
  - Lower charge of GaN helps HF performance
  - E.g. LLC example and ZVS full-bridge example

# Questions?

# References

- 1) Alex Lidow, Johan Strydom, Michael de Rooij, David Reusch, "GaN Transistors for Efficient Power Conversion, 2nd Edition," Wiley, ISBN: 978-1-118-84476-2, Sept. 2014
- 2) Fedison, J.B.; Fornage, M.; Harrison, M.J.; Zimmanck, D.R., "Coss related energy loss in power MOSFETs used in zero-voltage-switched applications," *APEC 2014*, pp.150-156, 16-20 March 2014
- 3) Strydom, J.T.; van Wyk, J.D.; Ferreira, J.A., "Capacitor measurements for power electronic applications," *IEEE IAS '99*, vol.4, pp.2435,2440, 1999
- 4) Jones, E.A.; Wang, F.; Ozpineci, B., "Application-based review of GaN HFETs," *Wide Bandgap Power Devices and Applications (WiPDA) 2014*, pp.24-29, 13-15 Oct. 2014
- 5) Zhan Wang; Honea, J.; Yuxiang Shi; Hui Li, "Investigation of driver circuits for GaN HEMTs in leaded packages," *Wide Bandgap Power Devices and Applications (WiPDA) 2014*, pp.81-87, 13-15 Oct. 2014
- 6) Lautner, J.; Piepenbreier, B., "Impact of current measurement on switching characterization of GaN transistors," *Wide Bandgap Power Devices and Applications (WiPDA) 2014*, pp.98-102, 13-15 Oct. 2014
- 7) Chang-Yeol Oh; Yun-Sung Kim; Won-Yong Sung; Nam-Jin Cho; Byoung-Kuk Lee, "Analysis of MOSFET failure modes in bi-directional phase-shift full-bridge converters," *APEC 2014*, pp.43-48, March 2014
- 8) Xiucheng Huang, Fred C. Lee, Qiang Li, "Characterization and Enhancement of 600V Cascode GaN Device," *CPES PMC Review*, March 11, 2015
- 9) Xing Huang; Dong Young Lee; Bondarenko, V.; Baker, A.; Sheridan, D.C.; Huang, A.Q.; Baliga, B.J., "Experimental study of 650V AlGaIn/GaN HEMT short-circuit safe operating area (SCSOA)," *Proc. ISPSD* pp.273,276, 15-19 June 2014