

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1

About this document

Scope and purpose

This document shows a reference board design for a 33 W USB power delivery (PD) charger using the latest Infineon 5th generation quasi-resonant (QR) controller **ICE5QSBG**. The charger is designed with a universal input with a USB type-C output connector to charge USB PD-enabled devices such as smartphones and tablets with multi-output configuration.

Highlights of the 33 W USB PD charger:

- Supports USB PD 3.0 programmable power supply (PPS) up to 33 W continuous output power in a universal input voltage range
- High average efficiency and low standby power to meet the European Union's Code of Conduct (CoC) Version 5 Tier 2 single-voltage external AC-DC power supply basic-voltage/low-voltage requirements
- Comprehensive protection feature, QR controller **ICE5QSBG** in DSO-8 package and a highly integrated USB type-C port controller with synchronous rectifier (SR) function from Cypress PAG1S for secondary side
- Narrow-lead **700 V CoolMOS™ P7** in **TO-220** package and high-frequency switching OptiMOS™ in **SuperSO8** package

Intended audience

This document is intended for power supply design or application engineers, etc. who want to design USB PD chargers that are efficient under light and heavy load conditions, reliable and easy to design.

Table of contents

About this document	1
Table of contents	1
1 System introduction	3
1.1 Fast-charging technologies.....	3
1.2 High average efficiency and low standby power	4
2 Reference board design	5
3 Power supply specifications	6
4 Circuit diagram	7
5 Circuit description	9
5.1 EMI filtering and line rectification.....	9
5.2 Flyback converter power stage.....	9
5.3 Clamper circuit	9
5.4 Control of flyback converter through 5 th generation QR controller ICE5QSBG	9
5.4.1 Fast self-start-up and sustaining of V _{CC}	9
5.4.2 QR switching with valley sensing.....	10

System introduction

5.4.3	Current sensing (CS).....	10
5.4.4	Feedback (FB) and compensation network	10
5.4.5	System robustness and reliability through protection features	10
5.5	Synchronous rectification.....	11
5.6	Output voltage configuration	11
5.7	PCB design tips.....	11
5.8	EMI reduction tips	12
6	PCB layout.....	13
6.1	Main board.....	13
6.2	Daughter board	13
7	Bill of materials (BOM)	14
8	Transformer specification	17
9	Measurement data and graphs.....	18
9.1	Efficiency curves.....	22
9.2	Line and load regulation	22
9.3	PPS compatible mode.....	24
9.4	Surge immunity (EN 61000-4-5)	24
9.5	Conducted emissions (EN 55022 class B)	25
9.6	Thermal measurements.....	26
10	Waveform and oscilloscope plots	27
10.1	Start-up time (5 V output)	27
10.2	Primary MOSFET drain and CS voltage at full load (11 V output)	27
10.3	SR MOSFET drain-to-source voltage at full load (11 V output)	28
10.4	Output ripple voltage	28
10.5	Dynamic load (fixed PDO)	32
10.6	Output voltage transition (fixed PDO)	34
10.7	Entering ABM (5 V output)	36
10.8	During ABM (5 V output)	36
10.9	Leaving ABM (5 V output)	37
10.10	Output OVP (fixed PDO)	38
10.11	Brown-in/-out protection.....	39
10.12	Overcurrent protection (fixed PDO).....	40
10.13	Hold-up time (9 V/3 A)	41
11	Appendix A: Transformer design and spreadsheet	42
12	References	47
	Revision history.....	48

1 System introduction

It's now possible to charge laptops, tablets, smartphones, smartwatches and other wearable and portable gadgets that have rechargeable batteries using a single universal charger solution. Most chargers have fast-charging capabilities, detecting whether the connected device can accept fast-charging, and then configuring their output to the right charging profile. Standards such as USB PD, quickcharge (QC) and supercharge are among the proprietary technologies that enable the fast-charging feature. Charging cables and connectors should be able to support increased output power without compromising safety, for example by resisting overheating. Lightning and USB type-C ports are the most used for these types of applications. Although charging power is increased, the form factor should remain small for portability.

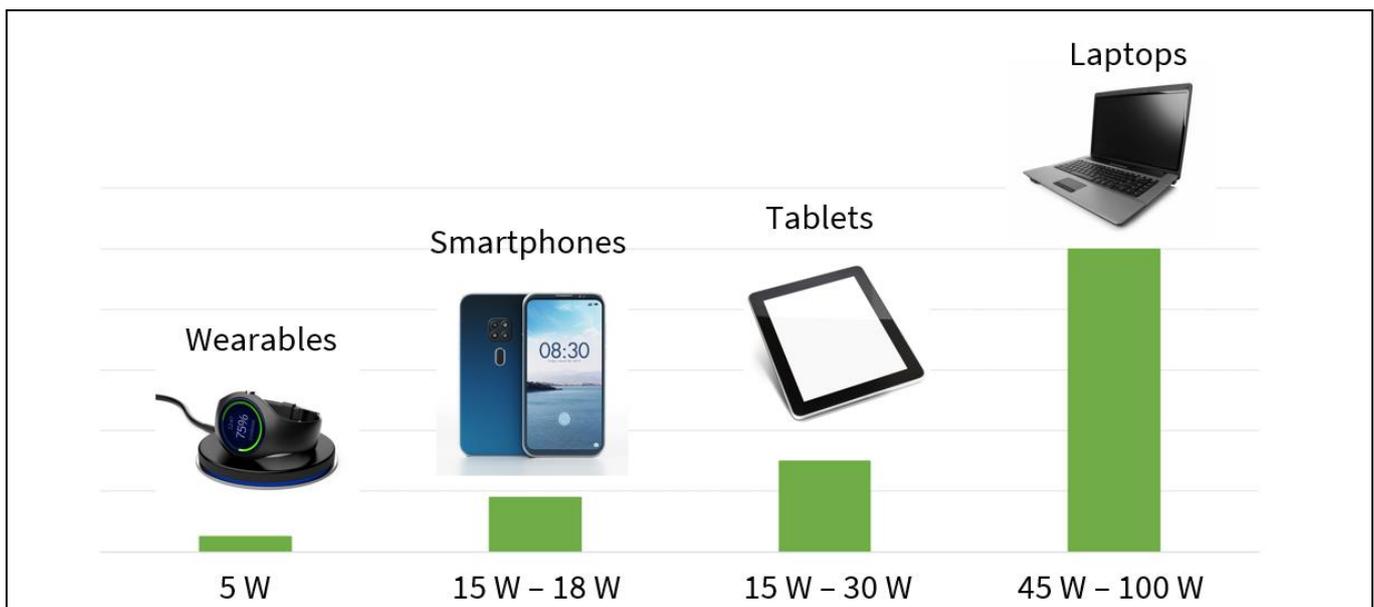


Figure 1 Charging requirements for portable devices

1.1 Fast-charging technologies

There are various fast-charging standard protocols in the market. The most commonly used protocols are QC and USB PD.

QC 4.0+ and USB PD are intercompatible, which means a USB PD charger should support fast-charging a QC 4.0+ device, and a QC 4.0+ charger should support fast-charging a USB PD device.

QC 4.0+ and USB PD are variable-output voltages up to 20 V. With the USB PD 3.0 PPS, which is also compatible and supports QC 4.0+, the output allows small steps in voltage (as low as 20 mV incremental steps) and current (as low as 50 mA incremental steps).

As for the connector ports, the previous version of QC (2.0 and 3.0) can be delivered through USB type-A. QC 4.0+ and USB PD use USB type-C, which can deliver up to 100 W power.

USB PD implements a power rule, recommending four voltage levels at 5 V, 9 V, 15 V and 20 V. Sources supplying more than 15 W offer voltages of 5 V and 9 V, those supplying more than 27 W offer 5 V, 9 V and 15 V, and those supplying more than 45 W offer 5 V, 9 V, 15 V and 20 V. The maximum 100 W power supply is achieved with 20 V and up to 5 A, which requires a higher end cable to support such current, although all of the other voltage modes cap out at 3 A, depending on the required power.

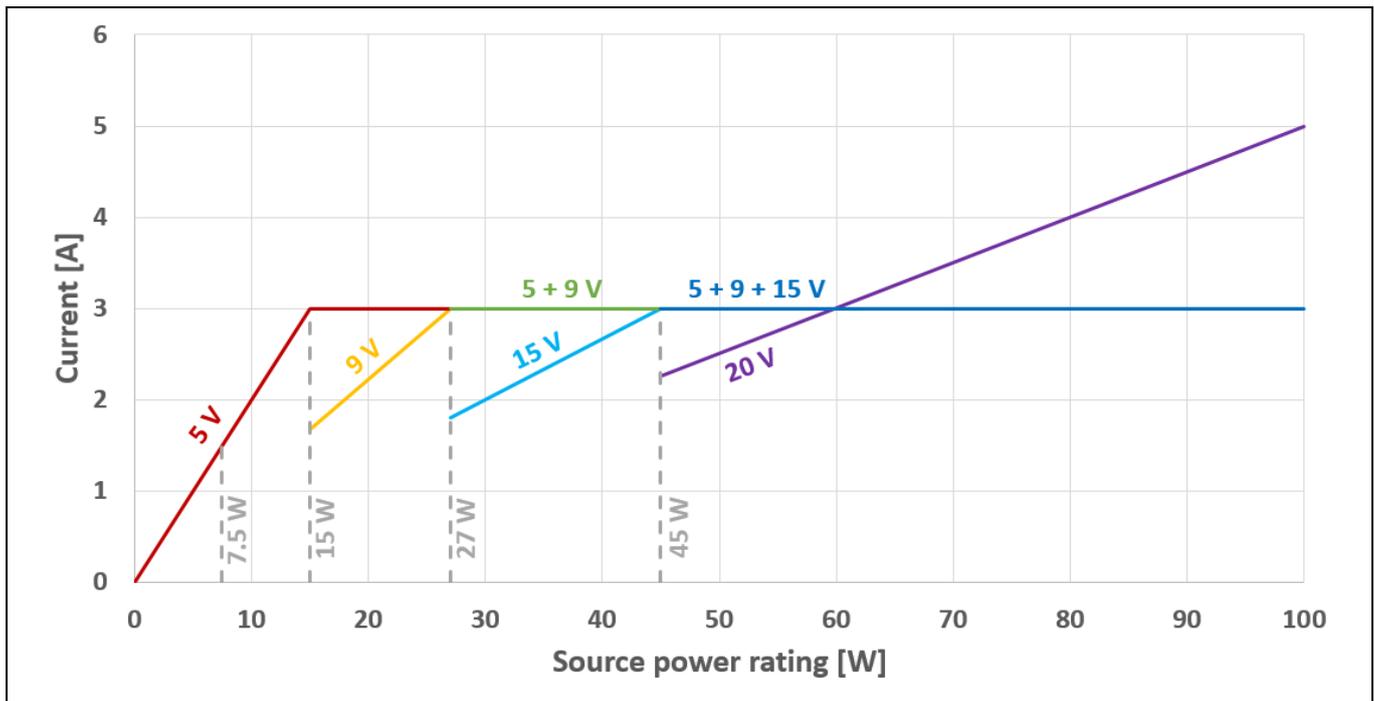


Figure 2 Output current against output power under different output voltages

1.2 High average efficiency and low standby power

In this reference design, **ICE5QSBG** was primarily chosen due to its digital frequency reduction switching scheme and active burst mode (ABM). Compared with a traditional QR flyback, the controller reduces its switching frequency by switching to the next valley (e.g., from first valley to eighth valley for low-line and third valley to tenth valley for high-line), thereby minimizing switching losses. Further reduction in load will trigger the controller to operate in ABM for a more efficient operation.

PAG1S is an integrated SR controller and charging port controller. PAG1S is designed to fit into a traditional primary-controlled flyback system with secondary-side sensing and regulation. PAG1S is targeted toward mobile power adapters, and it fits well into high-efficiency AC-DC flyback designs for USB PD, Qualcomm QC and other standard charging protocols. PAG1S also supports USB PD PPS mode.

In addition, the low switching losses introduced by the latest 700 V CoolMOS™ P7 **IPAN70R600P7S** in **TO-220** narrow-lead package and high-frequency switching OptiMOS™ **BSC070N10NS5** in **SuperSO8** package enable the charger to meet the highest efficiency standards and support high power density.

2 Reference board design

This document provides complete design details including specifications, schematics, bill of materials (BOM), PCB layout, and transformer design and construction information. Performance results pertaining to line/load regulation, efficiency, transient load, thermal conditions, conducted EMI scans and so on are also included.

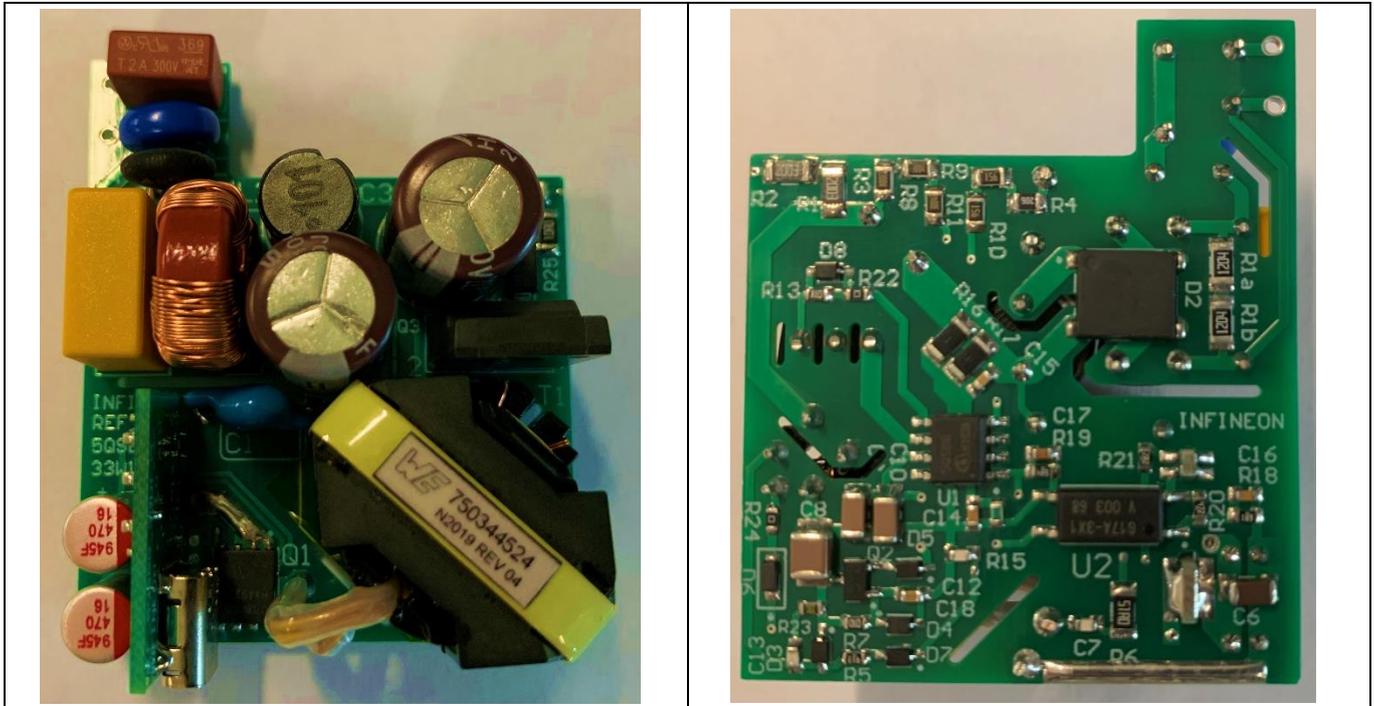


Figure 3 PCB

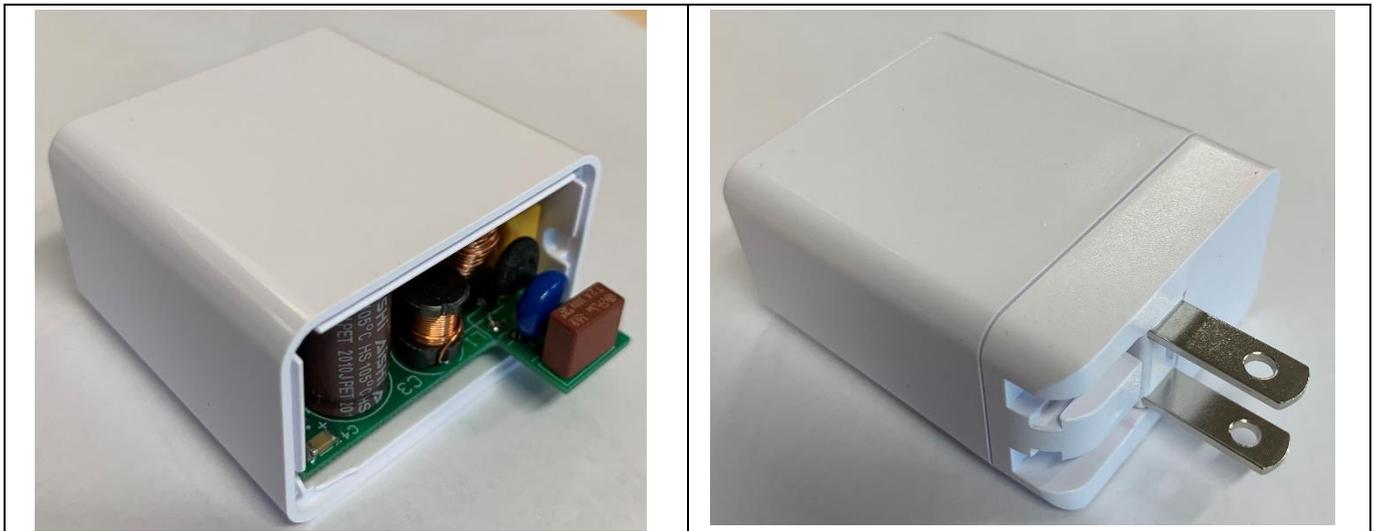


Figure 4 PCBA fitted in a case size of 54 x 45 x 28 mm (L x W x T), with foldable prongs

Power supply specifications

3 Power supply specifications

The table below represents the minimum acceptance performance of the design at 25°C ambient temperature. Actual results are listed in the measurements section.

Table 1 Specifications of REF_5QSBG_33W1

Description		Symbol	Min.	Typ.		Max.	Units	Comments
Input								
Voltage		V_{IN}	90	-		264	V AC	2-wire (no PE) 230 V AC
Frequency		f_{LINE}	47	50/60		63	Hz	
Standby power		P_{stby}	-	-		75	mW	
Output Voltage and current	PD 3.0 mode		-	5/3	9/3	-	V/A	PPS: 3.3 to 5.9 V, 0 to 3 A PPS: 3.3 to 11 V, 0 to 3 A
	PPS mode		3.3/3	-	-	11/3		
	QC 2.0 mode		-	5/3	9/3	12/2.25		
Efficiency		η_{avg}	CoC Tier 2				%	
Output voltage accuracy			Less than $\pm 5\%$ (PD mode)				%	
Constant current accuracy			Less than ± 150 (PPS mode)				mA	
Overcurrent protection (OCP)			Less than 130% of rated current				A	Latch-up
Overvoltage protection (OVP)			Less than 120% of V_{bus_set}				V	Latch-up
Undervoltage protection (UVP)			More than 70% of V_{bus_set}				V	Latch-up
Dynamic load		V_{dy}	Less than $\pm 10\%$ of V_{bus_set}				V	100 Hz, 0.4 A/ μ s
Ripple and noise voltage		V_{pk-pk}	Less than 3% of V_{bus_set} (20 MHz bandwidth)				mV	With 10 μ F E-cap and 0.1 μ F MLCC
Start-up time		t_{start_up}	-	-		500	ms	5 V output
Hold-up time		t_{hold_up}	10	-		-	ms	115 V AC, 27 W
Environmental								
Conducted EMI			6				dB	Margin, CISPR 22 class B EN 61000-4-5
Surge immunity Differential mode (DM)			± 1				kV	
Ambient temperature		T_{amb}	-20	-		50	°C	Free convection, sea level
PCBA form factor			40 × 40 × 18				mm ³	L × W × H

Circuit diagram

4 Circuit diagram

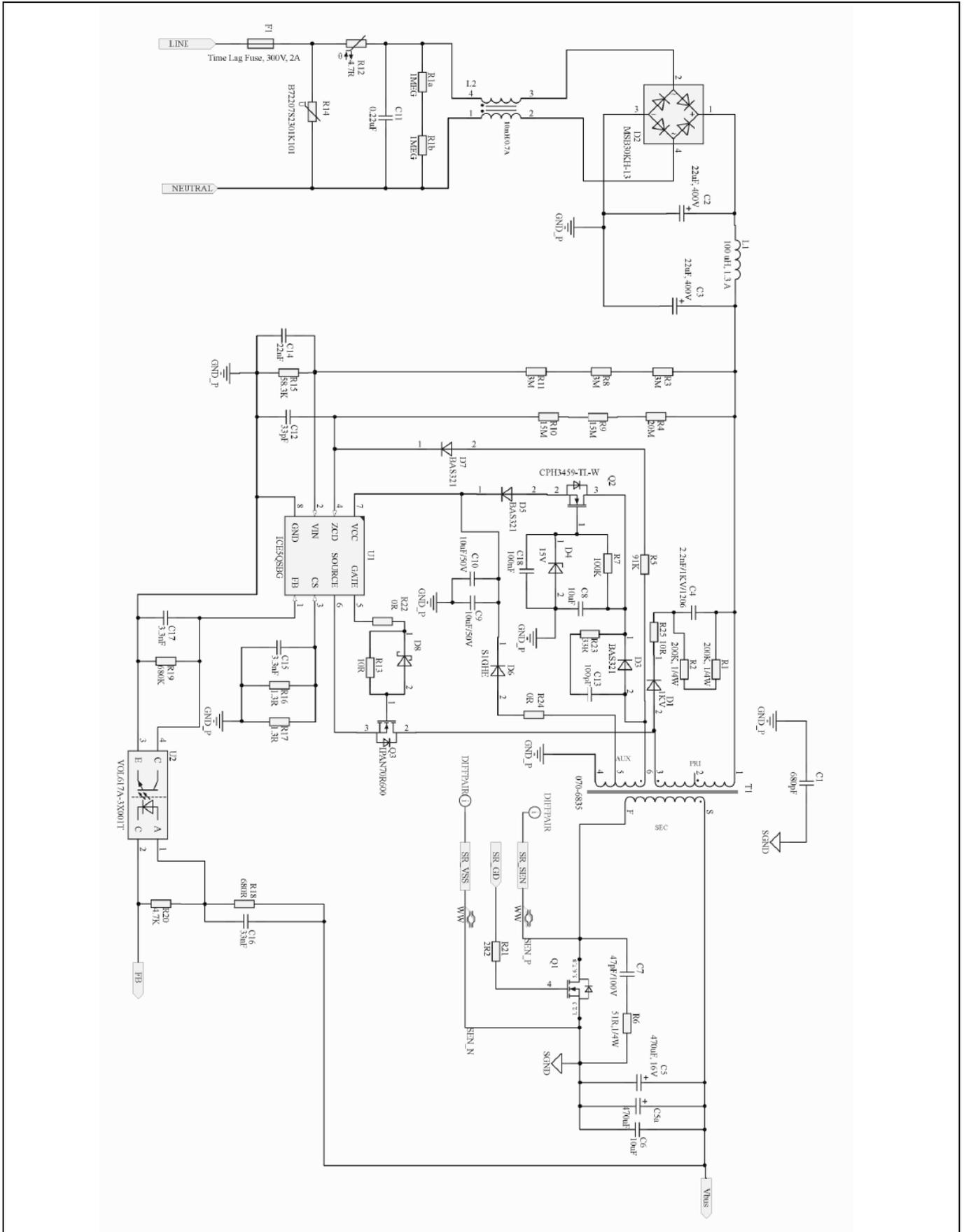


Figure 5 Schematic diagram of REF_5QSBG_33W1_M

Circuit description

5 Circuit description

In this section, the reference design circuit for the USB PD charger will be briefly described by the different functional blocks. For details of the design procedure and component selection for the flyback circuitry, please refer to the IC design guide [4] and calculation tool [5].

5.1 EMI filtering and line rectification

The input of the USB PD charger is taken from the AC power grid, which is in the range of 90 V AC ~ 264 V AC. The fuse F1 is directly connected to the input line to protect the system in case of excess current entering the system circuit due to any fault. Following is the thermistor R12, which is connected in series with F1 to reduce the inrush current, then the varistor R14, which is connected across the input to absorb excess energy during line surge transient. CM choke L2 together with π filter C2, L1 and C3 are filters to attenuate the DM and CM conducted EMI noise. The bridge rectifier D2 rectifies the AC input into DC voltage, filtered by the bulk capacitors C2 and C3.

5.2 Flyback converter power stage

The flyback converter power stage consists of transformer T1, a primary HV MOSFET Q3, secondary SR MOSFET Q1 and secondary output capacitors C5 and C5a.

When the HV MOSFET turns on, energy is stored in the transformer. When it turns off, the stored energy is discharged to the output capacitors and into the output load.

Secondary winding is sandwiched between two layers of primary winding to reduce leakage inductance. This improves efficiency and reduces voltage spikes.

For output rectification, the SR MOSFET is used to improve efficiency. Capacitors C5 and C5a store the energy needed during output load jumps, and help ensure low ESR.

5.3 Clamper circuit

A clamper network consisting of D1, C4, R1, R2 and R25 is used to reduce the switching voltage spikes across the drain pin of the HV MOSFET, which are generated from the leakage inductance of the transformer T1. This is a dissipative circuit, therefore R1, R2 and C4 need to be fine-tuned depending on the voltage derating factor and efficiency requirements.

5.4 Control of flyback converter through 5th generation QR controller ICE5QSBG

The **ICE5QSBG** controller is an eight-pin device in a DSO-8 package. It has been integrated with all necessary features and protections needed for a QR flyback controller.

5.4.1 Fast self-start-up and sustaining of V_{CC}

The IC uses a cascode structure to fast-charge the V_{CC} capacitor. Pull-up resistors R4, R9 and R10 connected to the multifunction zero crossing detection (ZCD) pin (pin 4) is used to initiate the start-up phase. At first, 0.2 mA is used to charge the V_{CC} capacitor from 0 V to 1.1 V. This is a protection which reduces the power dissipation of the power MOSFET during V_{CC} short-to-GND condition. Thereafter, a much higher charging current of 3.2 mA will charge the V_{CC} capacitor until the V_{CC_ON} is reached.

After start-up, the IC V_{CC} supply is sustained by the auxiliary winding of transformer T1, which needs to support the V_{CC} to be above undervoltage lockout (UVLO) voltage (10 V typ.) through two rectifier circuits.

Circuit description

5.4.2 QR switching with valley sensing

ICE5QSBG is a QR flyback controller which turns the HV MOSFET on at the lowest valley point of the drain voltage to minimize the switching losses. The IC senses the valley point through the ZCD pin (pin 4), which monitors auxiliary winding voltage through R5, D7 and C12 together with the internal resistor R_{ZCD} . When the ZCD voltage drops below 100 mV (typ.), the HV MOSFET switches on.

The IC employs digital frequency reduction to avoid the inherent increasing switching frequency of QR operation during load reduction. With **ICE5QSBG**, the HV MOSFET switches on from first to eighth valley for low-line or third to tenth valley for high-line.

5.4.3 Current sensing (CS)

The **ICE5QSBG** is a CM controller. The peak current is controlled cycle-by-cycle through the CS resistors R16 and R17 in the CS pin (pin 3). Transformer saturation can be avoided through peak current control (PCL), making the system better protected and more reliable.

5.4.4 Feedback (FB) and compensation network

V_{OUT} is sensed by PAG1S together with PD protocol integrated to switch between 3 V and 12 V output.

The FB pin of **ICE5QSBG** is a multifunction pin which is used to select the entry/exit burst power level through the resistor at the FB pin (R44) and also the burst-on/burst-off sense input during ABM.

5.4.5 System robustness and reliability through protection features

Protection is one of the major factors in determining whether the system is safe and robust – therefore sufficient protection is necessary. **ICE5QSBG** provides comprehensive protection to ensure the system is operating safely. This includes brown-in/brown-out, V_{IN} overvoltage (OV), V_{OUT} OV, V_{CC} OV and undervoltage (UV), open-loop/overload, overtemperature and V_{CC} short-to-GND. When those faults are found, the system will enter into protection mode. Once the fault is removed, the system resumes normal operation. A list of protections and failure conditions is shown in the table below.

PAG1S also supports configurable output OVP/UVP, and output overcurrent/short-circuit protection.

Table 2 Protection functions of ICE5QSBG

Protection function	Failure condition (typical values)	Protection mode
V_{CC} OV	V_{VCC} more than 25.5 V	Odd-skip auto restart
V_{CC} UV	V_{VCC} less than 10 V	Auto restart
V_{OUT} OV	V_{ZCD} more than 2 V for 10 consecutive pulses	Non-switch auto restart
V_{IN} OV	V_{VIN} more than 2.9 V	Non-switch auto restart
Brown-in/brown-out	V_{VIN_BI} less than 0.66 V/ V_{VIN_BO} less than 0.40 V	Non-switch auto restart
Open-loop/overload	V_{FB} more than 2.75 V and lasts for 30 ms	Odd-skip auto restart
Overtemperature	T_J more than 140°C (40°C hysteresis)	Non-switch auto restart
V_{CC} short-to-GND ($V_{VCC} = 0$ V, start-up = 50 M Ω and $V_{DRAIN} = 90$ V)	V_{VCC} less than 1.1 V, $I_{VCC_Charge1} \approx -0.2$ mA	Cannot start-up

Circuit description

5.5 Synchronous rectification

PAG1S is an integrated SR controller and charging port controller, which is good to drive an N-channel power MOSFET in a secondary output rectifier circuit. The MOSFET gate is switched on and off to bypass its body diode during the conduction period to minimize power dissipation, remaining off during the blocking period. The drain-to-source voltage is accurately sensed to determine the direction and magnitude of the current, allowing the PAG1S to turn the MOSFET on and off at close to zero current.

5.6 Output voltage configuration

The device connected on the output terminal communicates with the protocol IC to set the output voltage of the USB PD charger. The output connector is a USB type-C to support higher PD.

5.7 PCB design tips

For a good PCB design layout, there are several points to note.

- The switching power loop needs to be as small as possible (see [Figure 7](#)). There are two power loops in the reference design: one on the primary side and one on the secondary side. The primary-side loop starts from the bulk capacitor (C2/C3) positive terminal, primary transformer winding, primary MOSFET Q3, QR controller, CS resistors and back to the C4 negative terminal. The secondary-side loop starts at the secondary transformer winding, output capacitor C5/C5a, SR MOSFET Q1 and T1.

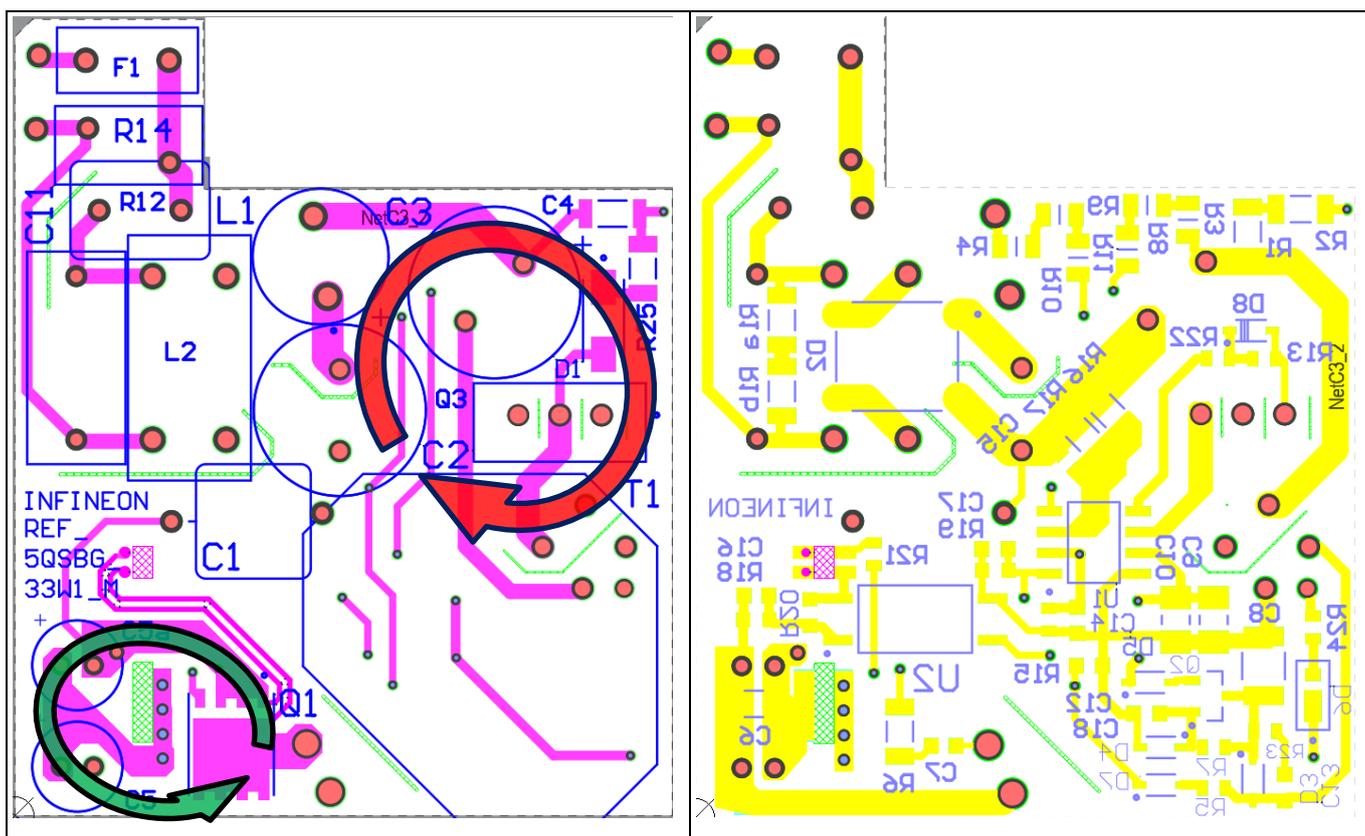


Figure 7 PCB layout tips

Circuit description

- Star-ground connection should be used to reduce HF noise coupling that can affect functional operation. The ground of the small-signal components, e.g., R15, C12, C17, R19, C14, and the emitter of the optocoupler (pin 3 of OPTO1) should connect directly to the IC ground (pin 8 of U1).
- Separating the HV components, e.g., the clamper circuit and the LV components, can reduce the spark-over chance of the high energy surge during ESD or a lightning surge test.
- Make the PCB copper pour on the DRAIN pin of the MOSFETs cover as wide an area as possible to act as a heatsink.

5.8 EMI reduction tips

EMI compliance is always a challenge for the power supply designer. There are several critical points to consider in order to achieve satisfactory EMI performance.

- A proper transformer design can significantly reduce EMI. Low leakage inductance can incur a low switching spike and HF noise. Interlaced winding is the most common technique to reduce leakage inductance. Winding shield, core shield and whole transformer shield are also among the techniques used to reduce EMI.
- Input CMC and X-capacitor greatly reduce EMI, but are costly and impractical, especially for low-power applications.
- Short-switching power-loop design in the PCB (as described in section 5.7) can reduce radiated EMI due to the antenna effect.
- The Y-capacitor CY1 dampens the HF noise generated between the primary and secondary, reducing the EMI noise.
- A secondary SR MOSFET snubber circuit (R6 and C7) can reduce HF noise.
- Ferrite beads can reduce HF noise especially on critical nodes such as the DRAIN pin of MOSFETs and clamper diodes. There is no ferrite bead used in this design, as this can reduce the efficiency due to additional losses, especially on MOSFETs.

Bill of materials (BOM)

7 Bill of materials (BOM)

Table 3 BOM

No.	Designator	Description	Part number	Manufacturer	Qty
1	C1	Safety capacitors 250 V AC 680 pF	DE1B3RA681KN4AN01F	Murata	1
2	C2, C3	Aluminum electrolytic capacitors 22 μ F 400 V 20%	EHS2GM220G160T	AiSHi	2
3	C4	MLCC – SMD/SMT 1206 2200 pF 1000 V X7R 10%	GRM31BR73A222KW01	Murata	1
4	C5, C5a	Aluminum polymer capacitors 470 μ F 16 V 20%	SPF1CM471B11O00RAXXX	AiSHi	2
5	C6	MLCC – SMD/SMT 10.0 μ F 16.0 V	C1206C106J4RAC	Kemet	1
6	C7	MLCC – SMD/SMT 100 V 47 pF 0603 C0G 5%			1
7	C8	MLCC – SMD/SMT 1210 100 V 4.7 μ F X7S 10%	CGA6M3X7S2A475K200AE	TDK Corporation	1
8	C9, C10	MLCC – SMD/SMT 1206 50 V 4.7 μ F X7R 10%	C3216X7R1H106K160AE	TDK Corporation	2
9	C11	Safety capacitors 0.22 μ F 310 V 20% X2	MKP224K310VAC	KYET	1
10	C12	MLCC – SMD/SMT 0603 50 V 33 pF 10%			1
11	C13	MLCC – SMD/SMT 0603 100 V 100 pF 10%			1
12	C14	MLCC – SMD/SMT 0603 50 V 22 nF 10%			1
13	C15	MLCC – SMD/SMT 0603 50 V 3.3 nF 10%			1
14	C16	MLCC – SMD/SMT 0603 50 V 33 nF 10%			1
15	C17	MLCC – SMD/SMT 0603 50 V 4.7 nF 10%			1
16	C18	MLCC – SMD/SMT 50 V 0.1 μ F X7R 0603 10%			1
17	D1	Standard recovery diode 1 kV 1 A, single	S1M	ON Semiconductor	1
18	D2	Bridge rectifier single phase 1 kV 3 A SMD	MSB30M-13	Diodes	1
19	D3, D5, D7, D8	Diode 200 V 250 MA SOD-323	BAS321	Nexperia	4
20	D6	Standard diode 400 V 1 A SMD SOD-323HE	S1GHE	ON Semiconductor	1
21	D4	Zener single diode 15 V SOD-323	BZX384-C15,115	Nexperia	1
22	F1	Time-lag fuse 300 V 2 A	36912000000	Littelfuse	1
23	L1	Radial leaded wire-wound inductor WE-TI size 8095 100 μ H 1.3 A	7447720101	Würth Elektronik	1
24	L2	WE-CMB CM power line choke type XS 10 mH 0.7 A 250 V	744821110	Würth Elektronik	1
25	Q1	MOSFET N-channel 100 V 80 A TDSO8	BSC070N10NS5	Infineon	1

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Bill of materials (BOM)

26	Q2	MOSFET N-channel 200 V 500 mA 2.8 Ω SOT-23	CPH3459-TL-W	ON Semiconductor	1
27	Q3	MOSFET N-channel 700 V 8.5 A TO220-FP	IPAN70R600P7S	Infineon	1
28	R1, R2	Thick-film resistors – SMD 1206 200 k Ω 1%			2
29	R1a, R1b	Thick-film resistors – SMD 1206 1.2 M Ω 5%			2
30	R3, R8, R11	Thick-film resistors – SMD 0805 3 M Ω 5%			3
31	R9, R10	Thick-film resistors – SMD 0805 15 M Ω 5%			2
32	R4	Thick-film resistors – SMD 0805 20 M Ω 5%			1
33	R5	Thick-film resistors – SMD 0603 91 k Ω 1%			1
34	R6	Thick-film resistors – SMD 1206 51 Ω 1%			1
35	R7	Thick-film resistors – SMD 0603 100 k Ω 1%			1
36	R12	NTC 4.7 Ω -20% to +20% radial leaded	B57153S0479M000	TDK Corporation	1
37	R13	Thick-film resistors – SMD 0603 91 Ω 1%			1
38	R14	SIOV metal oxide varistor	B72207S2301K101	Epcos	1
39	R15	Thin-film resistors – SMD 0603 58.3 K Ω 1%			1
40	R16, R17	Thick-film resistors – SMD 1R3 1% 0.25 W 1206			1
41	R18	Thin-film resistors – SMD 0603 680 Ω 1%			1
42	R19	Thin-film resistors – SMD 0603 680 K Ω 1%			1
43	R20	Thin-film resistors – SMD 0603 4700 Ω 1%			1
44	R21	Thick-film resistors – SMD 1/10 W 2.2 Ω 1%			1
45	R23	Thin-film resistors – SMD 0603 33 Ω 1%			1
46	R22, R24	Thick-film resistors – SMD 0 R 0.1 W 0603			2
47	R25	Thick-film resistors – SMD 1206 10 Ω 1%			1
48	T1	Transformer THT vertical RM-style bobbins RM8		Würth Elektronik	1
49	U1	QR PWM controller	ICE5QSBG	Infineon	1
50	U2	Optocoupler	VOL617A-3X001T	Vishay	1

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Bill of materials (BOM)

Table 4 Daughter board list

No.	Designator	Description	Part number	Manufacturer	Qty
1	C1	MLCC – SMD/SMT 0603 16 V DC 10 μ F X5R 10%			1
2	C2, C3, C6	MLCC – SMD/SMT 16 V 0.1 μ F X7R 0402 10%			3
3	C4, C5	MLCC – SMD/SMT 0603 25 V DC 4.7 μ F X5R 10%			2
4	C7	MLCC – SMD/SMT 0402 25 V DC 2.2 μ F 10% X5R			1
5	C8, C9	MLCC – SMD/SMT 390 pF 50 V C0G 5% 0402			2
6	C11	MLCC – SMD/SMT 100 pF 50 V C0G 5% 0402			1
7	C12	MLCC – SMD/SMT 150 pF 50 V C0G 5% 0402			1
8	C13	MLCC – SMD/SMT 0402 25 V DC 2.2 nF 10% X5R			1
9	C14	MLCC – SMD/SMT 0402 25 V DC 47 nF 10% X5R			1
10	J1	USB connectors USB type-C recep. R/A top-mounted	105450-0101	Molex	1
11	Q1	OptiMOS™ power – N-channel 40 A 40 V 2 m Ω	BSZ025N04LS	Infineon	1
12	R1	Thick-film resistors – SMD 0402 2.2 Ω 5%			1
13	R2	Resistors – SMD 1/4 W 0.005 Ω 1%		Vishay	1
14	R3, R4, R6, R11	Thick-film resistors – SMD 0402 0 Ω			4
15	R5	Thick-film resistors – SMD 0402 4.99 k Ω 1%			1
16	R8, R9	Thick-film resistors – SMD 100 k Ω 1% 1/16 W			2
17	R10, R12	Thermistors 0402 100 k Ω 1% NTC			2
18	R13	Thin-film resistors – SMD 68 k Ω 1% 0402			1
19	R14	Thick-film resistors – SMD 1/16 W 5.23 k Ω 1%			1
20	U1	USB PD power adapter SR controller	CYPD3184A1-24LQXQ	Cypress	1

Transformer specification

8 Transformer specification

Core: RM8, TP4A

Bobbin: 10-terminal EXT, THT, vertical

Primary inductance: $L_p = 400 \mu\text{H}$ (± 10 percent), measured between pin 1 and pin 3

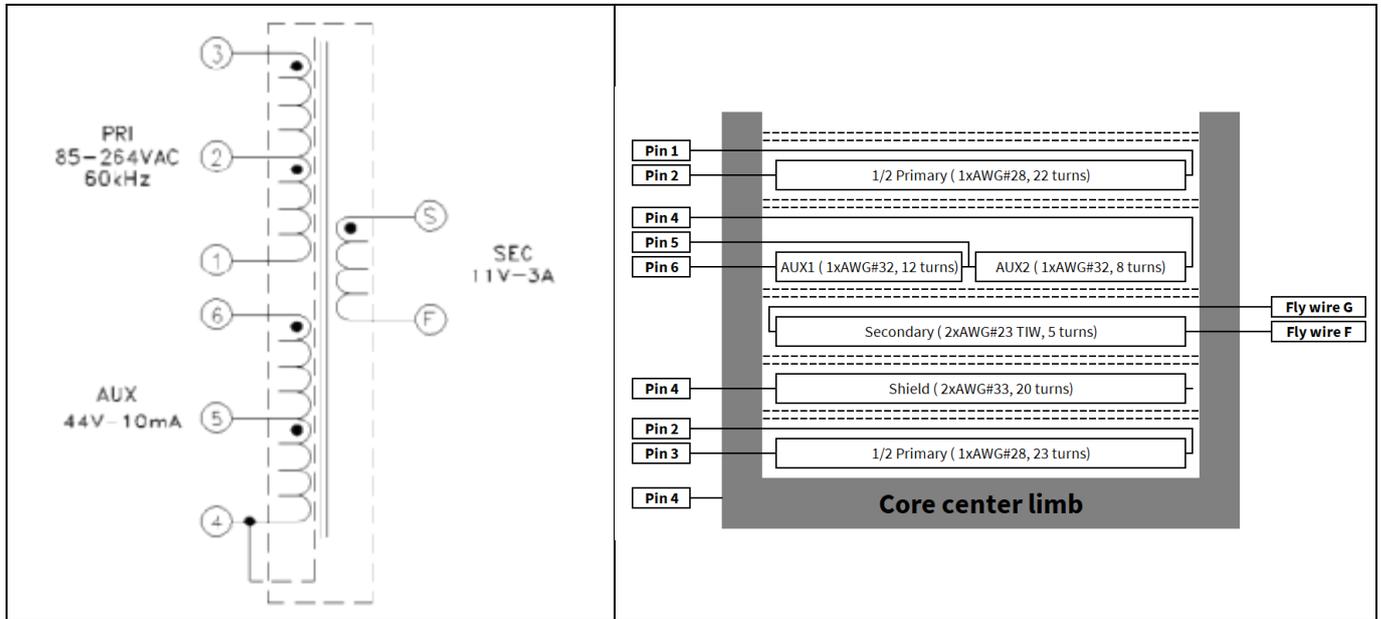


Figure 10 Transformer structure

Measurement data and graphs

9 Measurement data and graphs

All measurements are tested at 25°C room temperature and taken at the PCB end. ArteZ USB PD tester is used to configure the output voltage. Standby power is measured by a Yokogawa power meter WT210 with integrated testing of one minute.

Table 5 Standby power measurements

Input (V AC/Hz)	Loading	P _{IN} (mW)	Criteria	Remark
115 V AC/60 Hz	0% load	35	Less than 75 mW	No USB sink attached
230 V AC/50 Hz	0% load	53	Less than 75 mW	

Table 6 3.3 V output electrical measurements

Input (V AC/Hz)	Loading	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	P _{OUT} (W)	Efficiency (%)	Average efficiency (%)
90 V AC/ 60 Hz	10% load	1.178	3.300	0.2981	0.98	83.51%	86.89%
	25% load	2.869	3.296	0.7498	2.47	86.13%	
	50% load	5.644	3.290	1.4950	4.92	87.15%	
	75% load	8.461	3.283	2.2465	7.38	87.17%	
	100% load	11.270	3.277	2.9956	9.82	87.10%	
115 V AC/ 60 Hz	10% load	1.148	3.300	0.2943	0.97	84.57%	87.56%
	25% load	2.829	3.296	0.7453	2.46	86.84%	
	50% load	5.568	3.290	1.4950	4.92	88.34%	
	75% load	8.383	3.283	2.2465	7.38	87.98%	
	100% load	11.270	3.277	2.9956	9.82	87.10%	
230 V AC/ 50 Hz	10% load	1.230	3.300	0.2994	0.99	80.33%	86.25%
	25% load	2.906	3.296	0.7453	2.46	84.52%	
	50% load	5.650	3.290	1.4950	4.92	87.06%	
	75% load	8.516	3.283	2.2500	7.39	86.74%	
	100% load	11.278	3.277	2.9827	9.77	86.67%	
264 V AC/ 50 Hz	10% load	1.250	3.300	0.2994	0.99	79.04%	85.20%
	25% load	2.990	3.296	0.7453	2.46	82.16%	
	50% load	5.702	3.290	1.4950	4.92	86.26%	
	75% load	8.595	3.283	2.2500	7.39	85.94%	
	100% load	11.310	3.277	2.9827	9.77	86.42%	

Measurement data and graphs

Table 7 5 V output electrical measurements

Input (V AC/Hz)	Loading	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	P _{OUT} (W)	Efficiency (%)	Average efficiency (%)
90 V AC/ 60 Hz	10% load	1.720	5.096	0.2944	1.50	87.22%	88.43%
	25% load	4.316	5.092	0.7456	3.80	87.97%	
	50% load	8.562	5.086	1.4950	7.60	88.81%	
	75% load	12.876	5.080	2.2465	11.41	88.63%	
	100% load	17.210	5.073	2.9956	15.20	88.30%	
115 V AC/ 60 Hz	10% load	1.726	5.096	0.2944	1.50	86.94%	88.78%
	25% load	4.335	5.092	0.7456	3.80	87.58%	
	50% load	8.520	5.086	1.4950	7.60	89.24%	
	75% load	12.790	5.080	2.2465	11.41	89.23%	
	100% load	17.056	5.072	2.9956	15.19	89.08%	
230 V AC/ 50 Hz	10% load	1.812	5.096	0.2944	1.50	82.80%	87.14%
	25% load	4.547	5.092	0.7456	3.80	83.50%	
	50% load	8.655	5.086	1.4950	7.60	87.85%	
	75% load	12.910	5.080	2.2465	11.41	88.40%	
	100% load	17.105	5.072	2.9956	15.19	88.83%	
264 V AC/ 50 Hz	10% load	1.844	5.096	0.2944	1.50	81.36%	86.68%
	25% load	4.520	5.092	0.7456	3.80	84.00%	
	50% load	8.747	5.086	1.4950	7.60	86.93%	
	75% load	13.001	5.080	2.2465	11.41	87.78%	
	100% load	17.263	5.072	2.9956	15.19	88.01%	

Table 8 9 V output electrical measurements

Input (V AC/Hz)	Loading	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	P _{OUT} (W)	Efficiency (%)	Average efficiency (%)
90 V AC/ 60 Hz	10% load	3.078	9.054	0.2943	2.66	86.57%	88.75%
	25% load	7.605	9.050	0.7457	6.75	88.74%	
	50% load	15.209	9.043	1.4956	13.52	88.93%	
	75% load	22.846	9.037	2.2465	20.30	88.86%	
	100% load	30.580	9.030	2.9956	27.05	88.46%	
115 V AC/ 60 Hz	10% load	3.070	9.054	0.2943	2.66	86.79%	89.70%
	25% load	7.577	9.050	0.7457	6.75	89.07%	
	50% load	15.032	9.043	1.4950	13.52	89.94%	
	75% load	22.555	9.037	2.2465	20.30	90.01%	
	100% load	30.127	9.030	2.9956	27.05	89.79%	
230 V AC/ 50 Hz	10% load	3.180	9.054	0.2943	2.66	83.79%	89.33%
	25% load	7.770	9.050	0.7457	6.75	86.85%	

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Measurement data and graphs

Input (V AC/Hz)	Loading	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	P _{OUT} (W)	Efficiency (%)	Average efficiency (%)
	50% load	15.053	9.043	1.4956	13.52	89.85%	
	75% load	22.500	9.037	2.2465	20.30	90.23%	
	100% load	29.932	9.030	2.9956	27.05	90.37%	
264 V AC/ 50 Hz	10% load	3.220	9.054	0.2943	2.66	82.75%	88.75%
	25% load	7.877	9.050	0.7457	6.75	85.68%	
	50% load	15.144	9.043	1.4956	13.52	89.31%	
	75% load	22.580	9.037	2.2465	20.30	89.91%	
	100% load	30.020	9.030	2.9956	27.05	90.11%	

Table 9 11 V output electrical measurements

Input (V AC/Hz)	Loading	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	P _{OUT} (W)	Efficiency (%)	Average efficiency (%)
90 V AC/ 60 Hz	10% load	3.794	10.960	0.2950	3.23	85.21%	88.78%
	25% load	9.204	10.960	0.7456	8.17	88.79%	
	50% load	18.344	10.950	1.4950	16.37	89.24%	
	75% load	27.600	10.940	2.2465	24.58	89.05%	
	100% load	37.212	10.940	2.9953	32.77	88.06%	
115 V AC/ 60 Hz	10% load	3.791	10.960	0.2950	3.23	85.29%	89.82%
	25% load	9.163	10.960	0.7456	8.17	89.18%	
	50% load	18.169	10.950	1.4953	16.37	90.12%	
	75% load	27.289	10.940	2.2465	24.58	90.06%	
	100% load	36.444	10.940	2.9956	32.77	89.92%	
230 V AC/ 50 Hz	10% load	3.869	10.960	0.2945	3.23	83.43%	89.47%
	25% load	9.336	10.960	0.7456	8.17	87.53%	
	50% load	18.304	10.950	1.4953	16.37	89.46%	
	75% load	27.252	10.940	2.2465	24.58	90.18%	
	100% load	36.120	10.940	2.9956	32.77	90.73%	
264 V AC/ 50 Hz	10% load	3.950	10.960	0.2950	3.23	81.84%	88.88%
	25% load	9.452	10.960	0.7456	8.17	86.45%	
	50% load	18.394	10.950	1.4950	16.37	89.00%	
	75% load	27.438	10.944	2.2465	24.59	89.60%	
	100% load	36.234	10.940	2.9956	32.77	90.45%	

Measurement data and graphs

Table 10 12 V output electrical measurements

Input (V AC/Hz)	Loading	P _{IN} (W)	V _{OUT} (V)	I _{OUT} (A)	P _{OUT} (W)	Efficiency (%)	Average efficiency (%)
90 V AC/ 60 Hz	10% load	3.050	12.063	0.2128	2.57	84.16%	88.69%
	25% load	7.700	12.060	0.5606	6.76	87.80%	
	50% load	15.108	12.054	1.1146	13.44	88.93%	
	75% load	22.679	12.050	1.6768	20.21	89.09%	
	100% load	30.419	12.044	2.2465	27.06	88.95%	
115 V AC/ 60 Hz	10% load	3.098	12.063	0.2128	2.57	82.86%	89.46%
	25% load	7.684	12.060	0.5606	6.76	87.99%	
	50% load	14.982	12.054	1.1146	13.44	89.68%	
	75% load	22.447	12.050	1.6768	20.21	90.01%	
	100% load	30.010	12.044	2.2465	27.06	90.16%	
230 V AC/ 50 Hz	10% load	3.154	12.063	0.2128	2.57	81.40%	88.97%
	25% load	7.880	12.060	0.5606	6.76	85.80%	
	50% load	15.025	12.054	1.1146	13.44	89.42%	
	75% load	22.386	12.050	1.6768	20.21	90.26%	
	100% load	29.927	12.044	2.2465	27.06	90.41%	
264 V AC/ 50 Hz	10% load	3.180	12.063	0.2128	2.57	80.72%	88.19%
	25% load	7.970	12.060	0.5606	6.76	84.83%	
	50% load	15.188	12.054	1.1146	13.44	88.46%	
	75% load	22.600	12.050	1.6768	20.21	89.40%	
	100% load	30.040	12.044	2.2465	27.06	90.07%	

Table 11 Efficiency summary

Parameter	Test condition	Criteria	Test result	
		Minimum	115 V AC/60 Hz	230 V AC/50 Hz
CoC Version 5 Tier 2 four-point average efficiency (average of 25%, 50%, 75%, 100% load)	V _{OUT} = 3.3 V DC, I _{OUT} = 3 A	78.19%	87.56%	86.25%
	V _{OUT} = 5 V DC, I _{OUT} = 3 A	81.76%	88.78%	87.14%
	V _{OUT} = 9 V DC, I _{OUT} = 3 A	87.30%	89.70%	89.33%
	V _{OUT} = 11 V DC, I _{OUT} = 3 A	88.03%	89.82%	89.47%
	V _{OUT} = 12 V DC, I _{OUT} = 2.25 A	87.30%	89.46%	88.97%
CoC Version 5 Tier 2 10% load efficiency	V _{OUT} = 3.3 V DC, I _{OUT} = 0.3 A	68.98%	84.57%	80.33%
	V _{OUT} = 5 V DC, I _{OUT} = 0.3 A	72.48%	86.94%	82.80%
	V _{OUT} = 9 V DC, I _{OUT} = 0.3 A	77.30%	86.79%	83.79%
	V _{OUT} = 11 V DC, I _{OUT} = 0.3 A	78.03%	85.29%	83.43%
	V _{OUT} = 12 V DC, I _{OUT} = 0.225 A	77.30%	82.86 %	80.72%

Measurement data and graphs

9.1 Efficiency curves

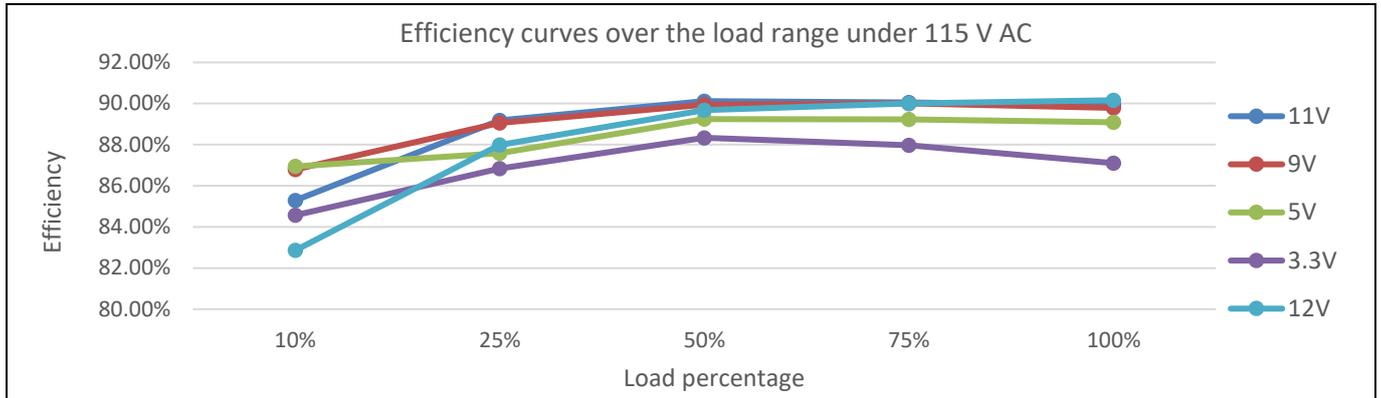


Figure 11 Efficiency curves over the load range under 115 V AC

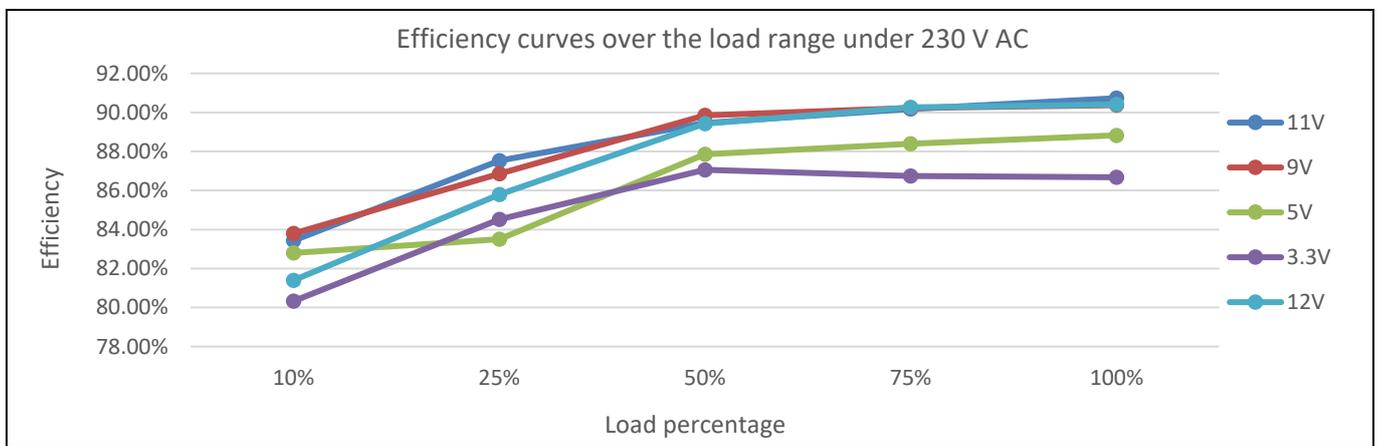


Figure 12 Efficiency curves over the load range under 230 V AC

9.2 Line and load regulation

The steady-state output regulation is verified under various loadings and different input voltages, which passes ± 5 percent specification.

Measurement data and graphs

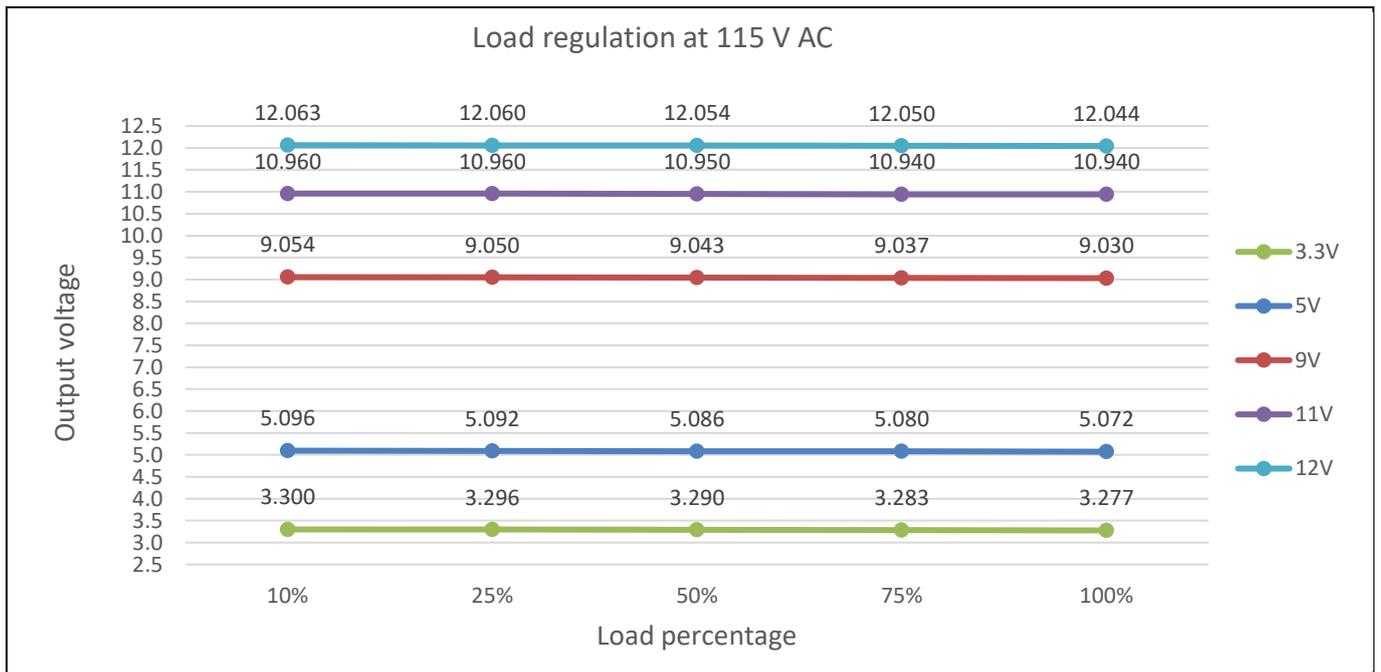


Figure 13 Load regulation at 115 V AC line input voltage

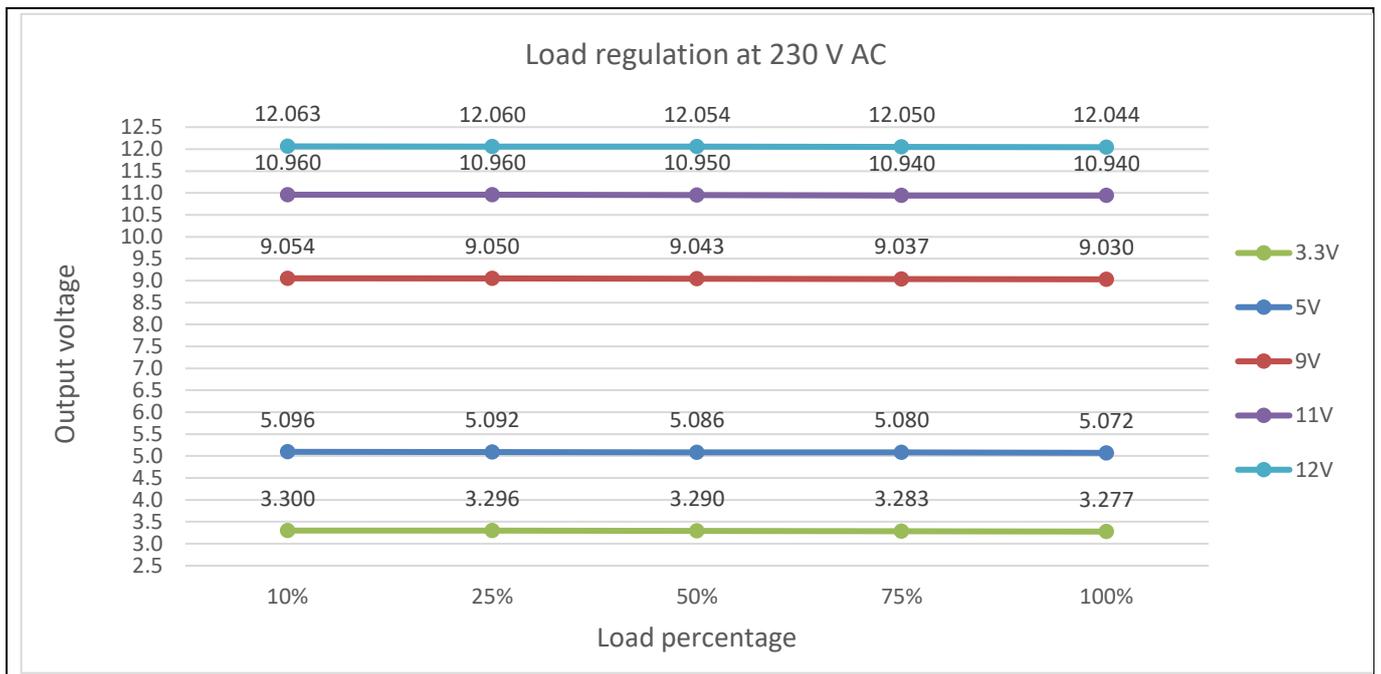


Figure 14 Load regulation at 230 V AC line input voltage

Measurement data and graphs

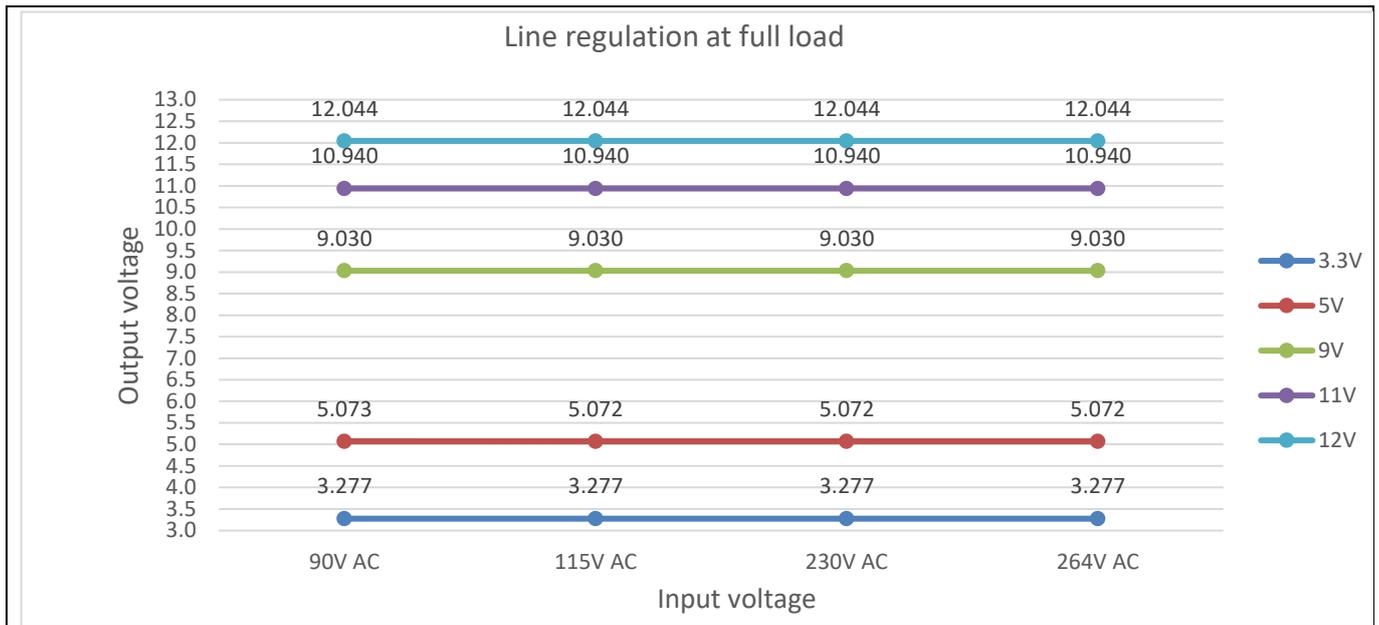


Figure 15 Line regulation at 100 percent load

9.3 PPS compatible mode

Constant current (CC) mode current limitation function is tested by E-load under CR mode; set device under test (DUT) to PPS mode and then increase current (by reducing R) to verify CC-CV curve.

Table 12 PPS mode constant current

Mode	V _{OUT} (V)	V _{IN,AC} (V/Hz)	I _{OUT,CC} (A)	Requirement (A)
PPS	3.3	90/60	3.021	2.85 ~ 3.15 (less than ±150 mA of rated output current)
		264/50	3.022	
	5.9	90/60	3.022	
		264/50	3.021	
	11	90/60	3.022	
		264/50	3.021	

9.4 Surge immunity (EN 61000-4-5)

The reference board was subjected to a surge immunity test (±1 kV DM) according to EN 61000-4-5. It was tested at 11 V full load (33 W) using resistive load (3.6 Ω) at an input voltage of 230 V AC. Output GND was connected to PE during testing. A test failure was defined as a non-recoverable and/or system auto restart.

Table 13 System surge immunity test results

Description	Test	Level		Number of strikes				Test result
				0°	90°	180°	270°	
230 V AC, 33 W (3.6 Ω R _{LOAD})	DM	+1 kV	L → N	3	3	3	3	Pass
		-1 kV	L → N	3	3	3	3	Pass

Measurement data and graphs

9.5 Conducted emissions (EN 55022 class B)

The conducted EMI (CEMI) was measured by Schaffner (SMR4503) and followed the test standard of EN 55022 (CISPR 22) class B. The reference board was tested at 11 V full load using resistive load at an input voltage of 115 V AC and 230 V AC with more than 6 dB margin.

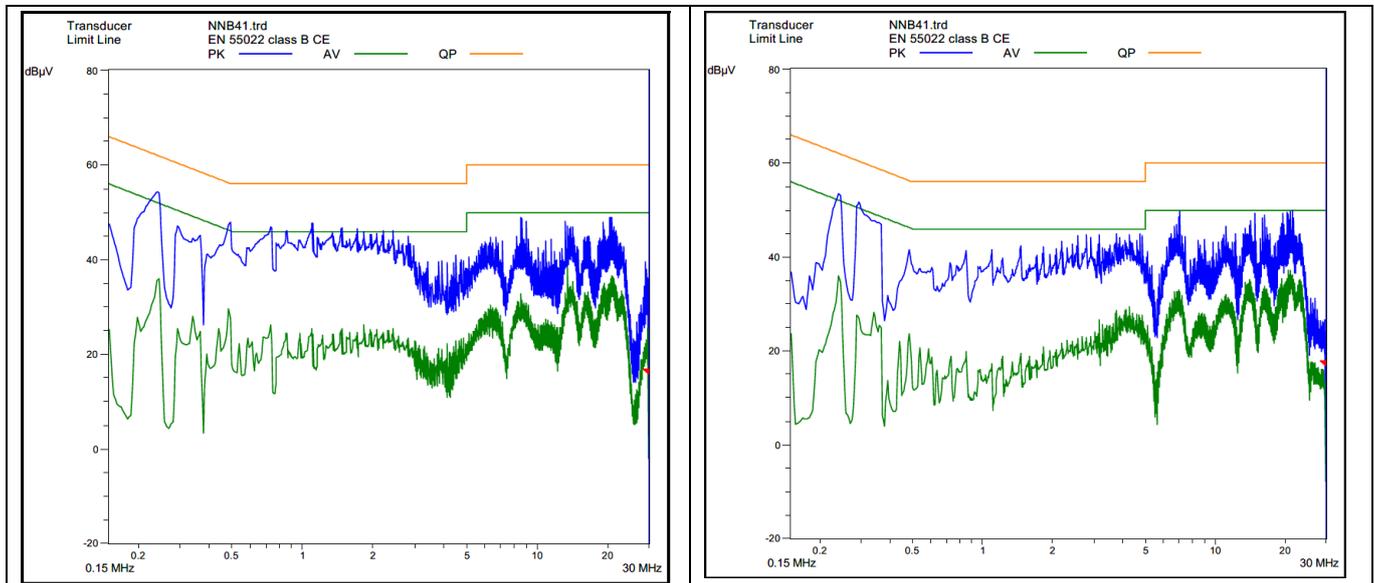


Figure 16 Conducted emissions on line (left) and neutral (right) at 115 V AC and full load

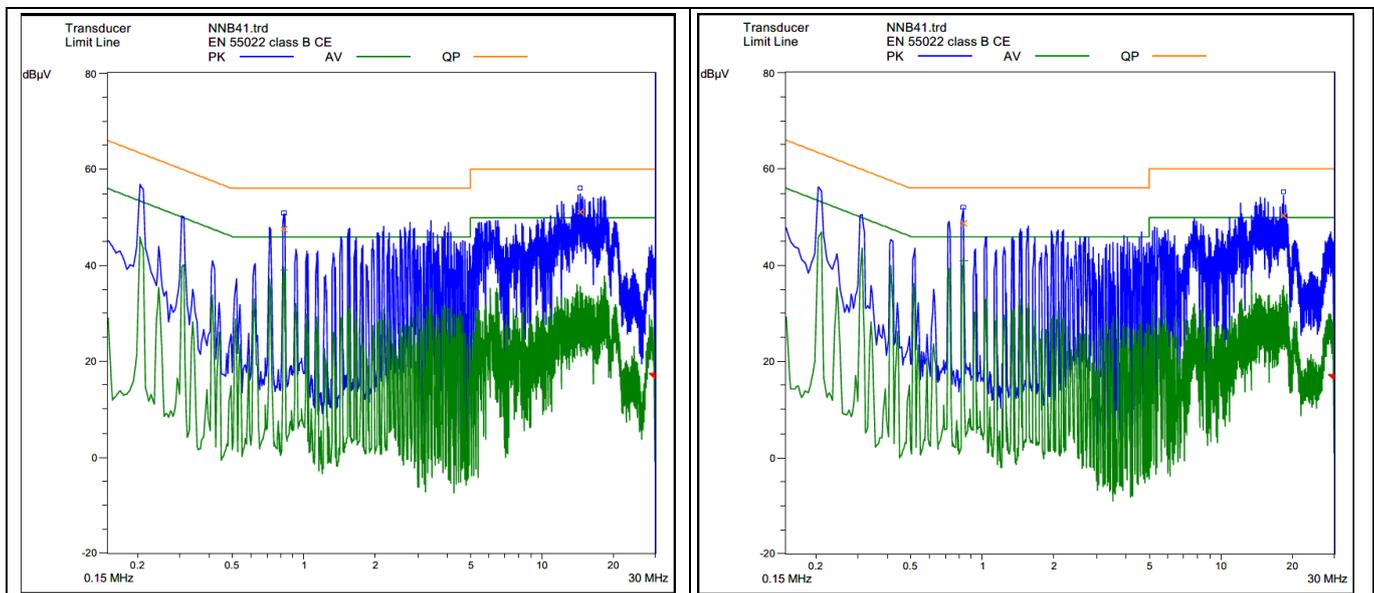


Figure 17 Conducted emissions on line (left) and neutral (right) at 230 V AC and full load

Measurement data and graphs

9.6 Thermal measurements

Thermal measurements were taken using an infrared thermography camera (FLIR-T62101) at an ambient temperature of 25°C, after one hour running at full load, 33 W. The component temperatures were taken in an open-frame setup.

Table 14 11 V output thermal measurements on components (open-frame)

No.	Components	Temperature at 90 V AC (°C)	Temperature at 264 V AC (°C)
1	Q1 (SR MOSFET)	83.6	81.9
2	T1 (transformer)	78.4	76.2
3	U1 (ICE5QSBG)	85.2	64.8
4	Q3 (primary MOSFET)	83.6	78.9
5	D2 (diode bridge)	95.5	64.9

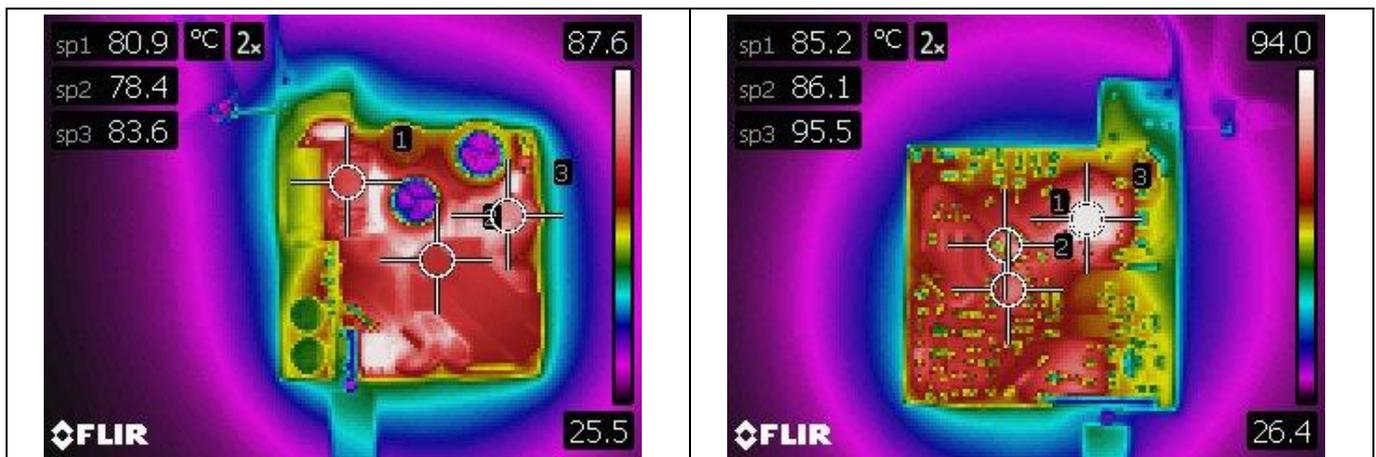


Figure 18 Top layer (left) and bottom layer (right) thermal image at 90 V AC input voltage

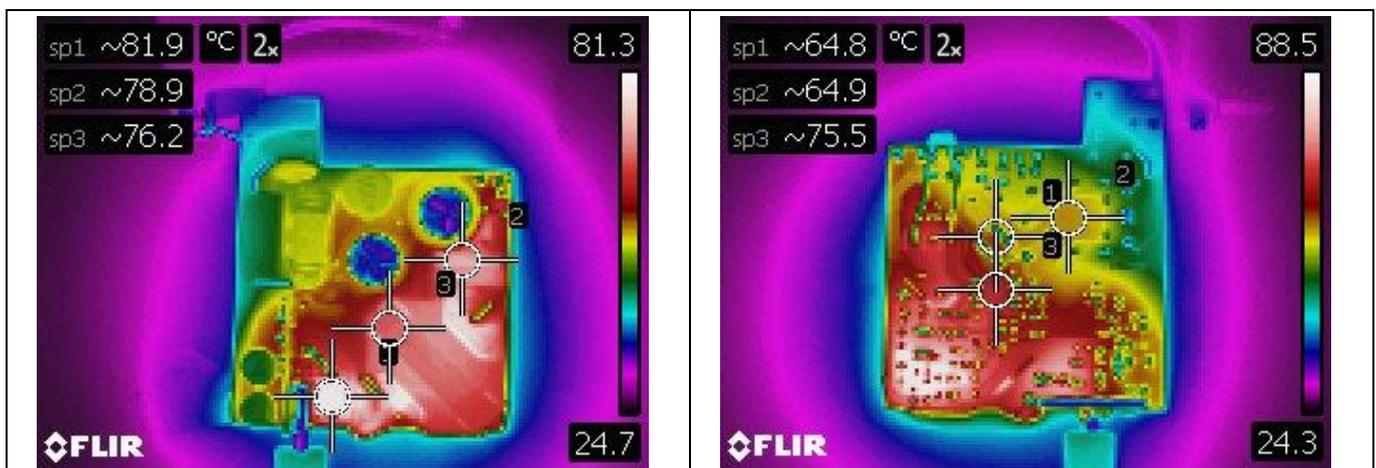


Figure 19 Top layer (left) and bottom layer (right) thermal image at 264 V AC input voltage

Waveform and oscilloscope plots

10 Waveform and oscilloscope plots

All waveforms and scope plots were recorded with a Teledyne LeCroy WaveRunner 40xi oscilloscope.

10.1 Start-up time (5 V output)

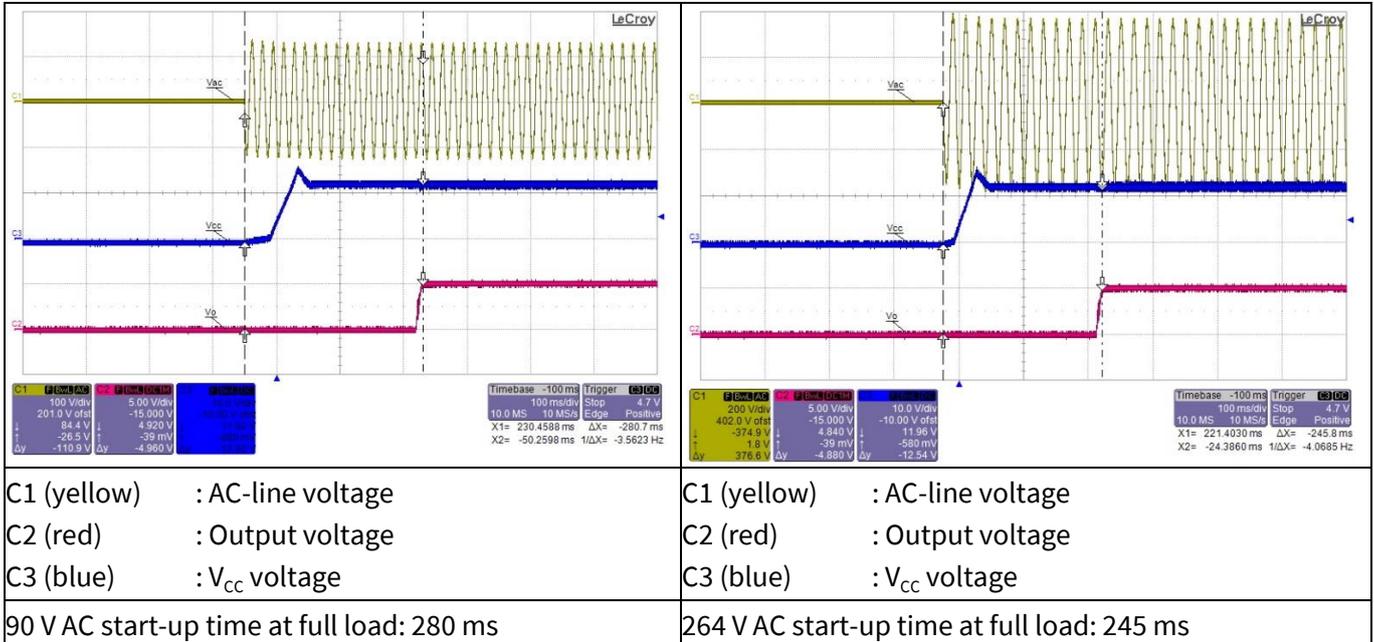


Figure 20 Start-up time

10.2 Primary MOSFET drain and CS voltage at full load (11 V output)

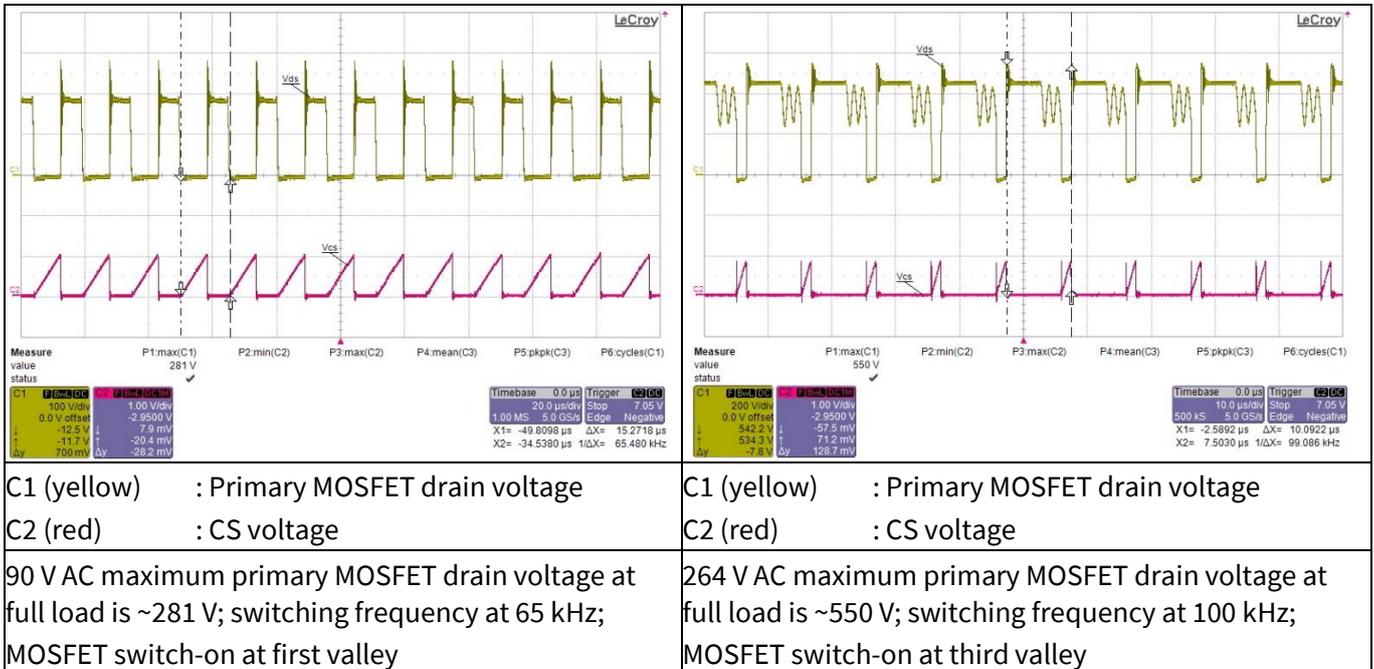


Figure 21 Primary MOSFET drain and CS voltage

Waveform and oscilloscope plots

10.3 SR MOSFET drain-to-source voltage at full load (11 V output)

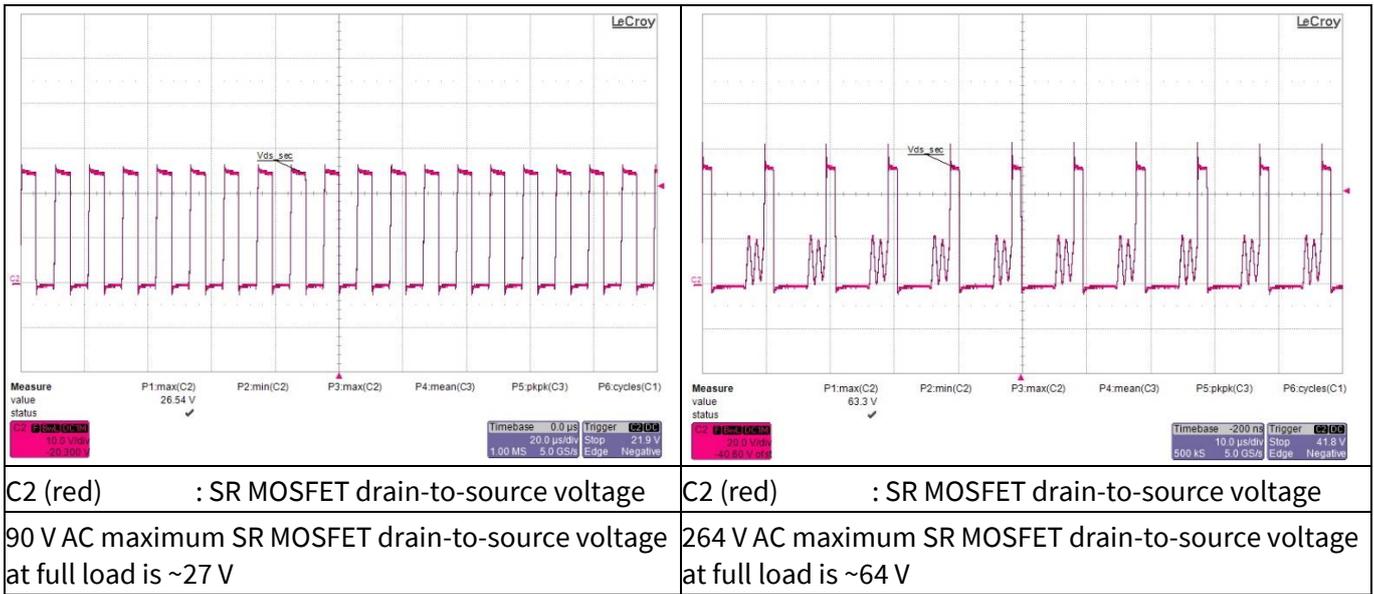


Figure 22 SR MOSFET drain-to-source voltage

10.4 Output ripple voltage

Output ripple is measured at the PCB end with no load or full load. Probe terminals are decoupled with a 10 μ F electrolytic capacitor and a 0.1 μ F ceramic capacitor. Oscilloscope bandwidth is limited to 20 MHz.


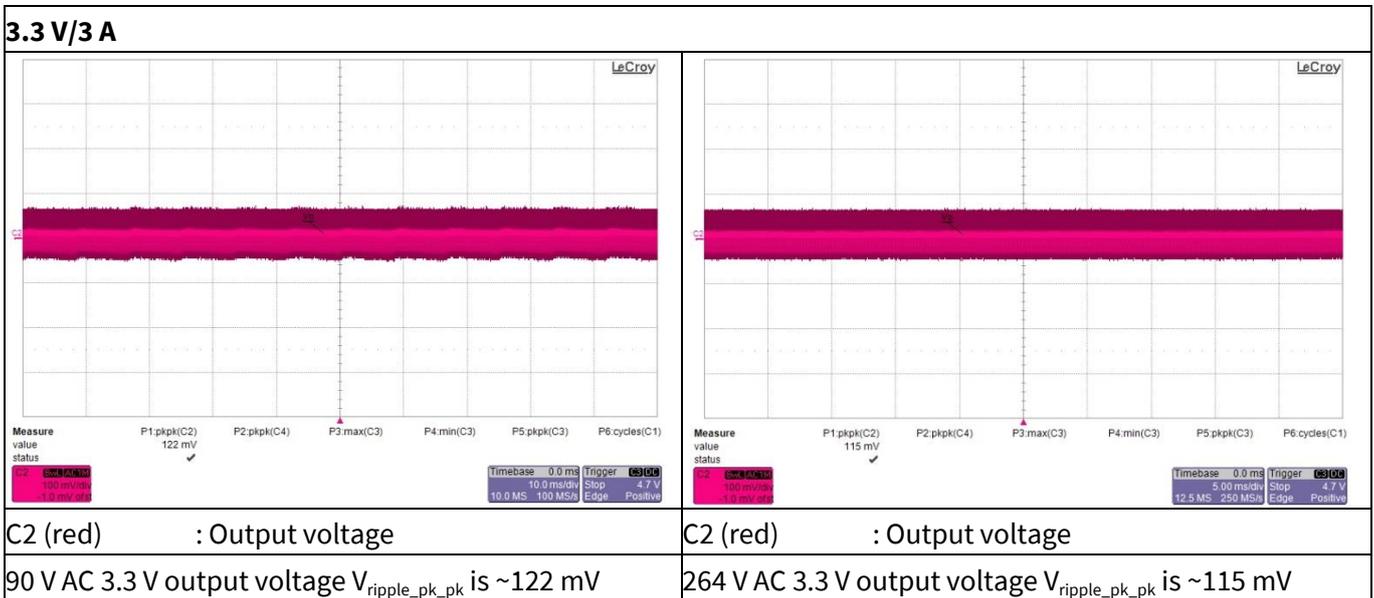


Figure 23 3.3 V output ripple voltage

Waveform and oscilloscope plots

5 V/3 A

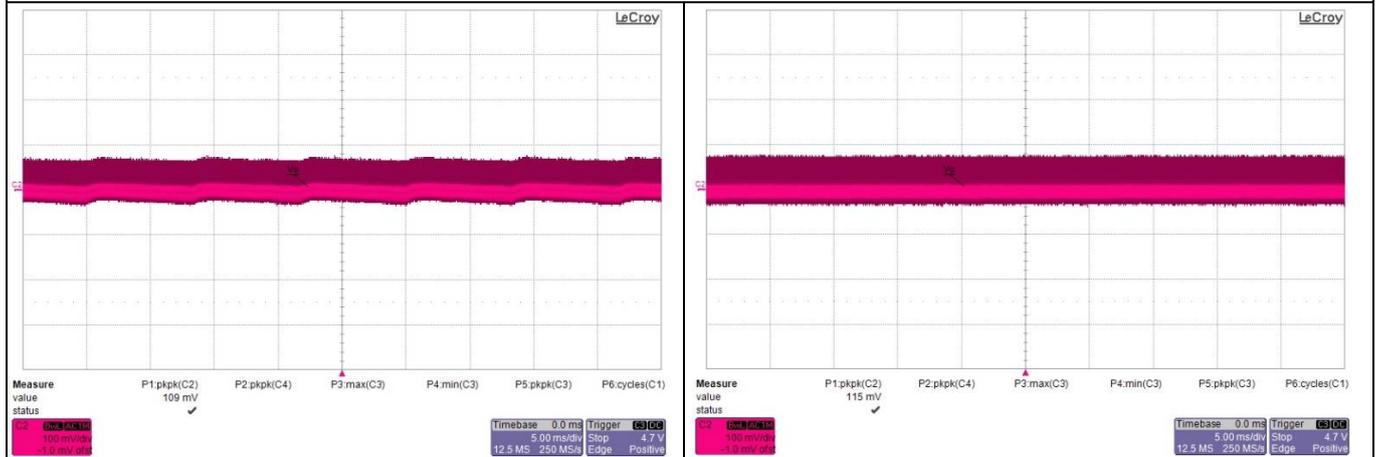

C2 (red) : Output voltage


90 V AC 5 V output voltage $V_{ripple_pk_pk}$ is ~109 mV

C2 (red) : Output voltage

264 V AC 5 V output voltage $V_{ripple_pk_pk}$ is ~115 mV

Figure 24 5 V output ripple voltage

9 V/3 A

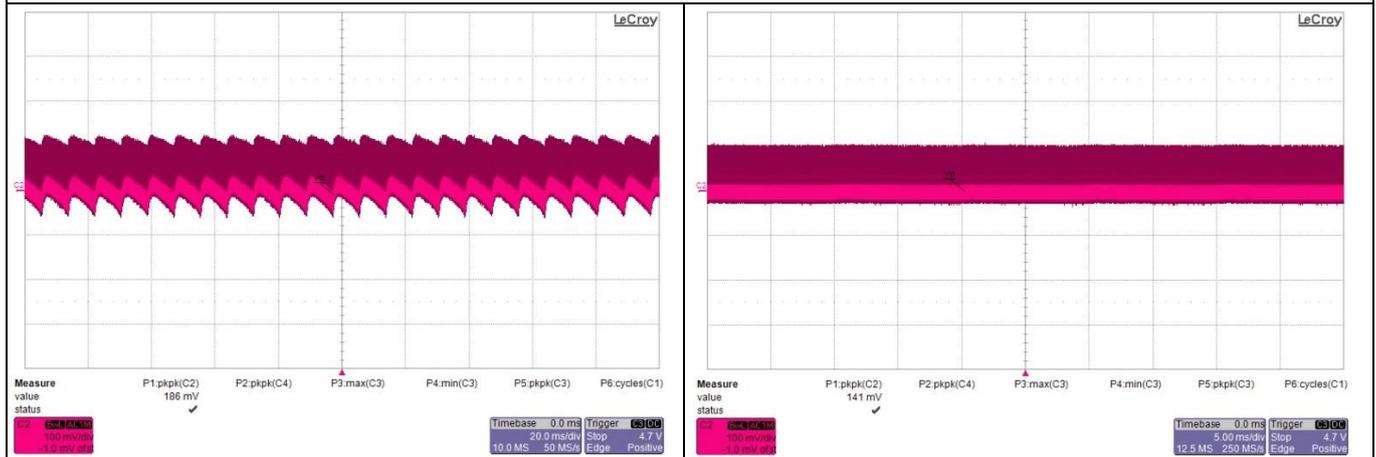

C2 (red) : Output voltage

90 V AC 9 V output voltage $V_{ripple_pk_pk}$ is ~186 mV

C2 (red) : Output voltage

264 V AC 9 V output voltage $V_{ripple_pk_pk}$ is ~141 mV

Figure 25 9 V output ripple voltage

Waveform and oscilloscope plots

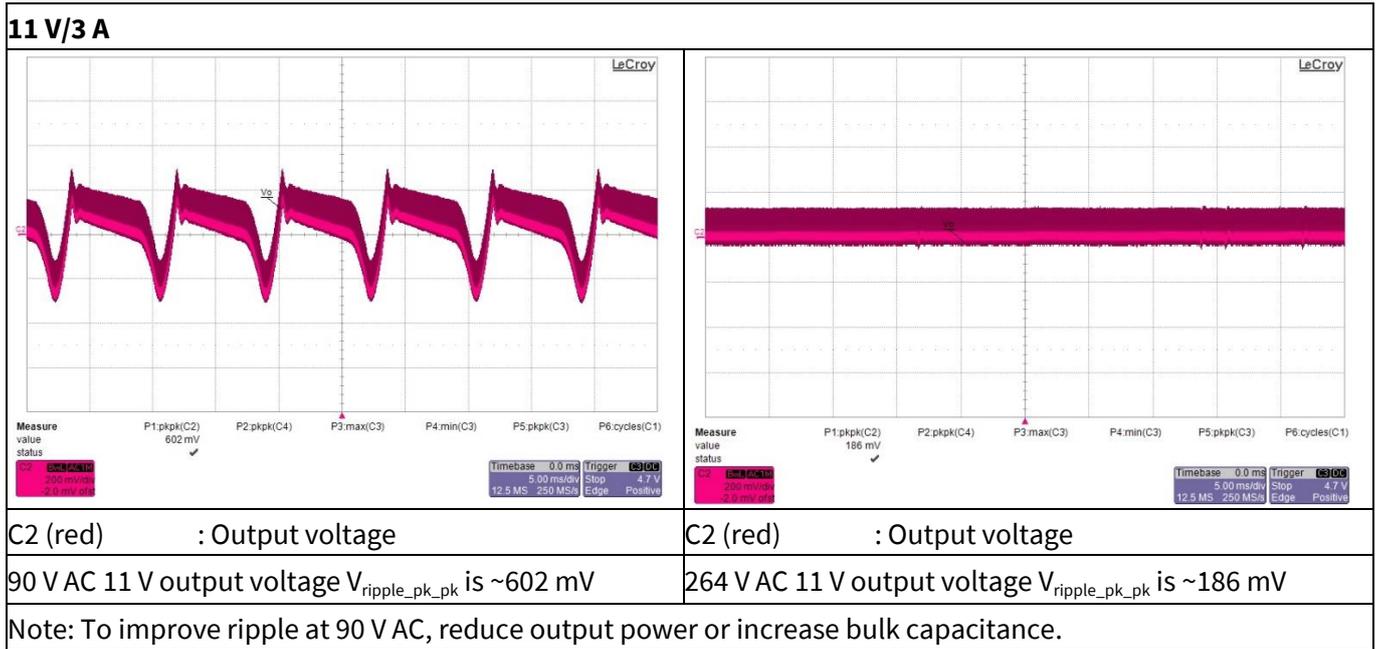


Figure 26 11 V output ripple voltage

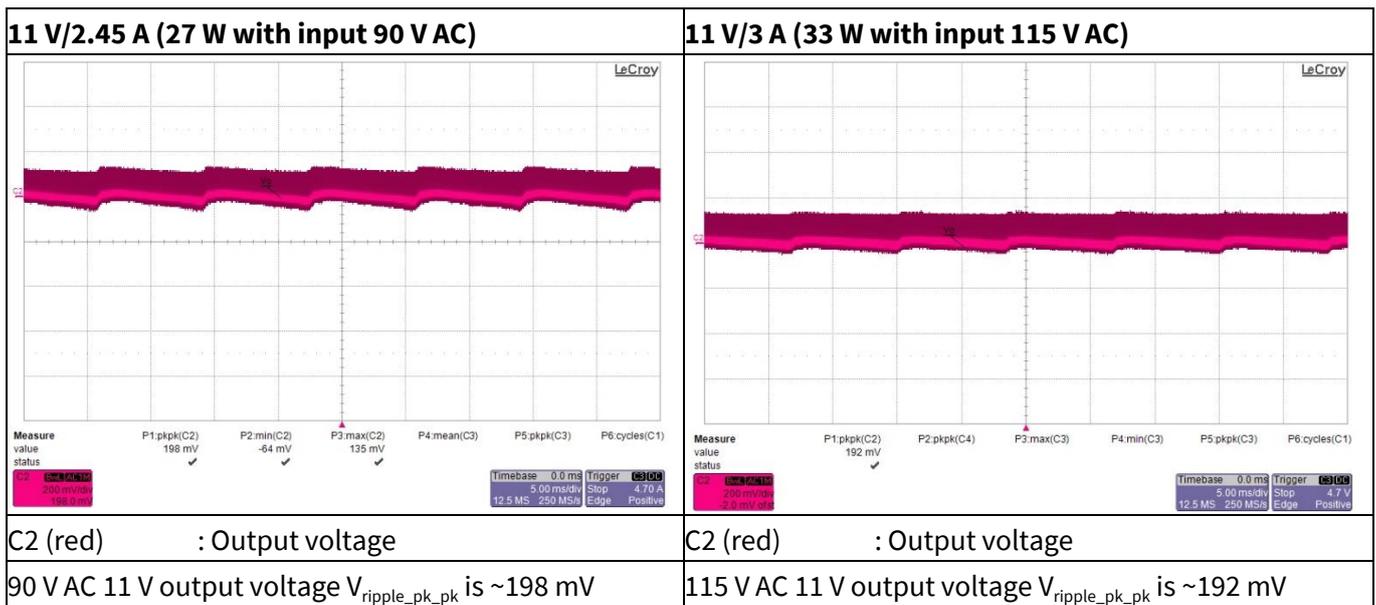


Figure 27 11 V output ripple voltage with 27 W load at 90 V AC and with 33 W load at input 115 V AC

Waveform and oscilloscope plots

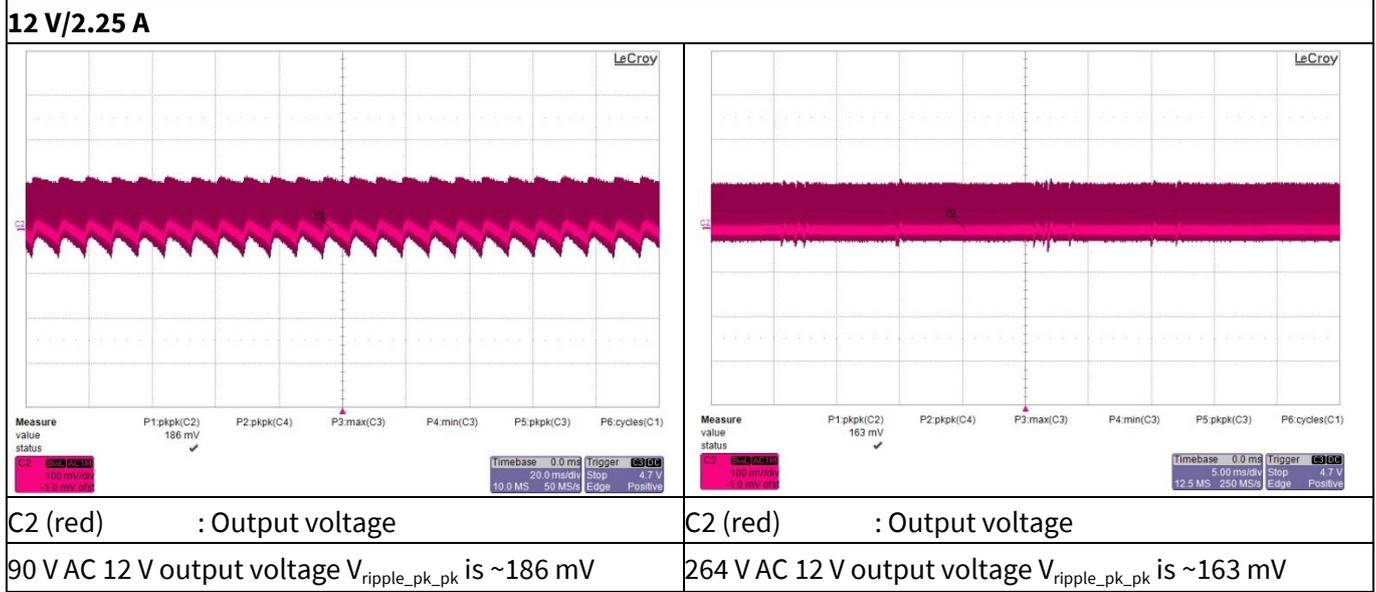


Figure 28 12 V output ripple voltage

Waveform and oscilloscope plots

10.5 Dynamic load (fixed PDO)

5 V (PD 3.0)	
<p>C2 (red) : Output voltage C4 (green) : Output current</p>	<p>C2 (red) : Output voltage C4 (green) : Output current</p>
90 V AC 5 V output voltage $V_{ripple_pk_pk}$ is ~ 588 mV	264 V AC 5 V output voltage $V_{ripple_pk_pk}$ is ~653 mV
Requirement: 4.5 V less than V_{OUT} less than 5.5 V	
9 V (PD 3.0)	
<p>C2 (red) : Output voltage C4 (green) : Output current</p>	<p>C2 (red) : Output voltage C4 (green) : Output current</p>
90 V AC 9 V output voltage $V_{ripple_pk_pk}$ is ~659 mV	264 V AC 9 V output voltage $V_{ripple_pk_pk}$ is ~742 mV
Requirement: 8.1 V less than V_{OUT} less than 9.9 V	
12 V (QC 2.0)	

Waveform and oscilloscope plots

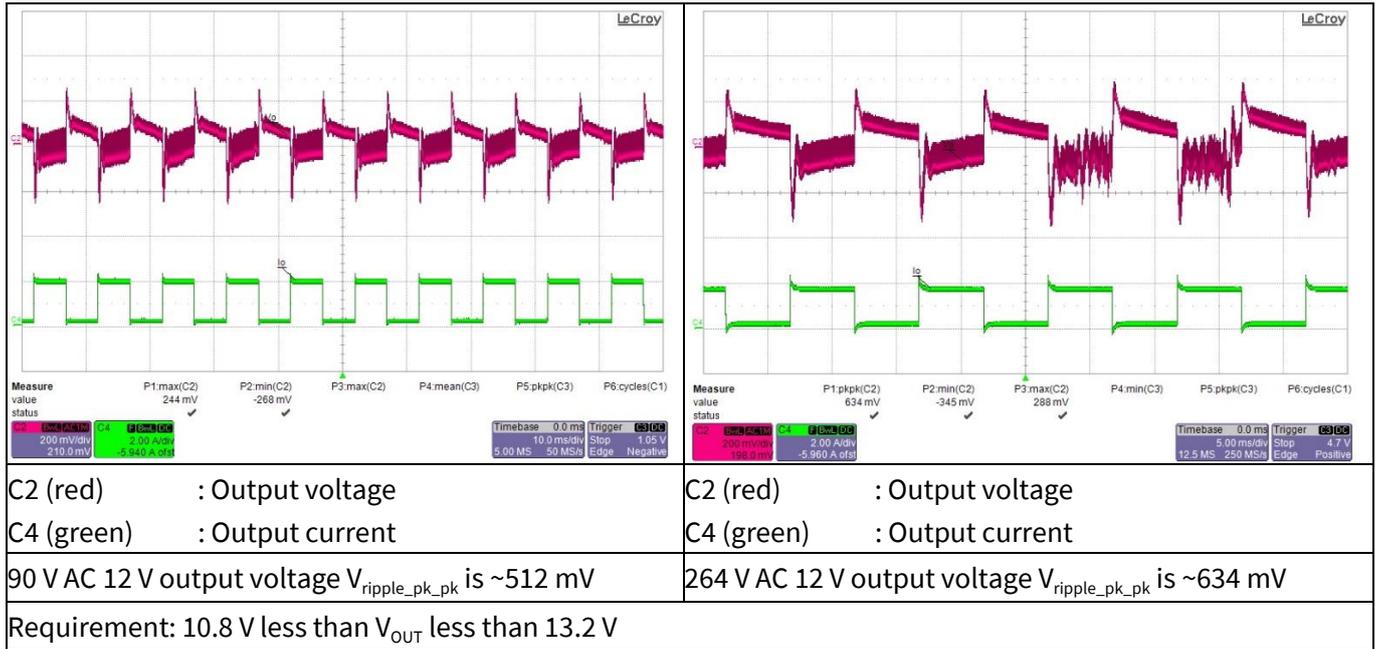


Figure 29 Load-transient response with output load change from 10 percent to 100 percent at 0.4 A/ μ s slew rate, 100 Hz. Probe terminals are connected on the PCB end and decoupled with a 1 μ F electrolytic capacitor and a 0.1 μ F ceramic capacitor. Oscilloscope is bandwidth filter limited to 20 MHz.

Waveform and oscilloscope plots


10.6 Output voltage transition (fixed PDO)

Input voltage: 115 V AC/60 Hz

Output current: No load and full load


Requirement: Less than 200 ms

5 V ↔ 9 V

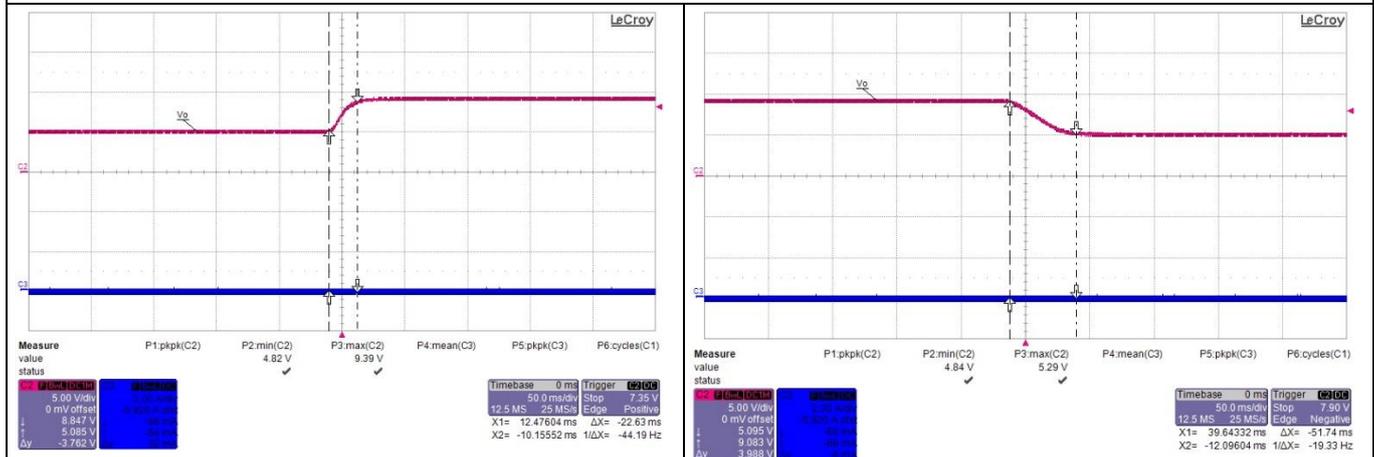

Transition time without load: 22.63 ms


Transition time with full load: 51.74 ms

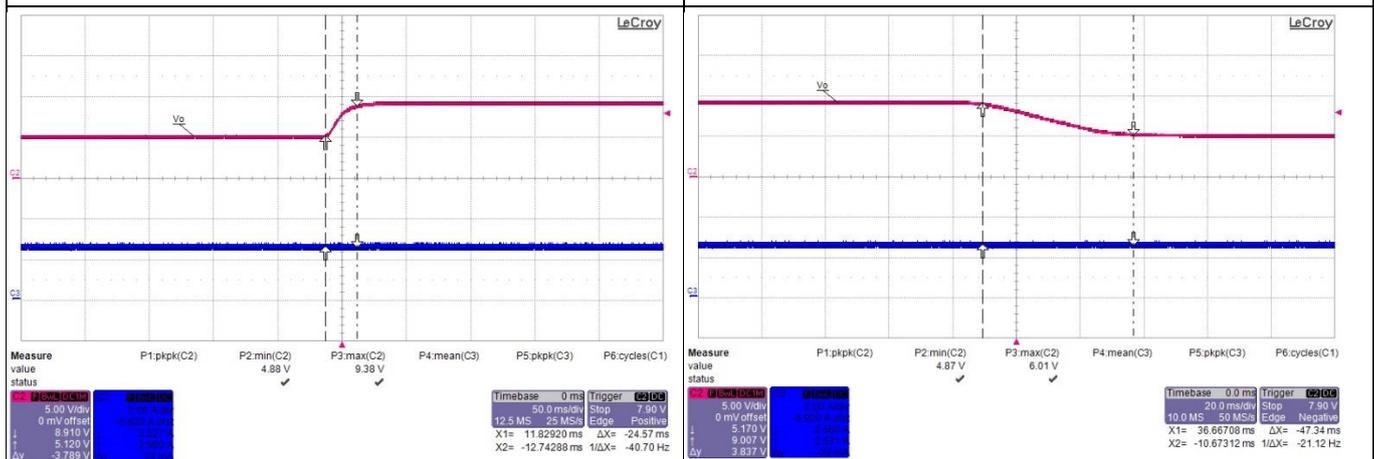

Transition time with full load: 24.57 ms

Transition time without load: 47.34 ms

5 V ↔ 12 V

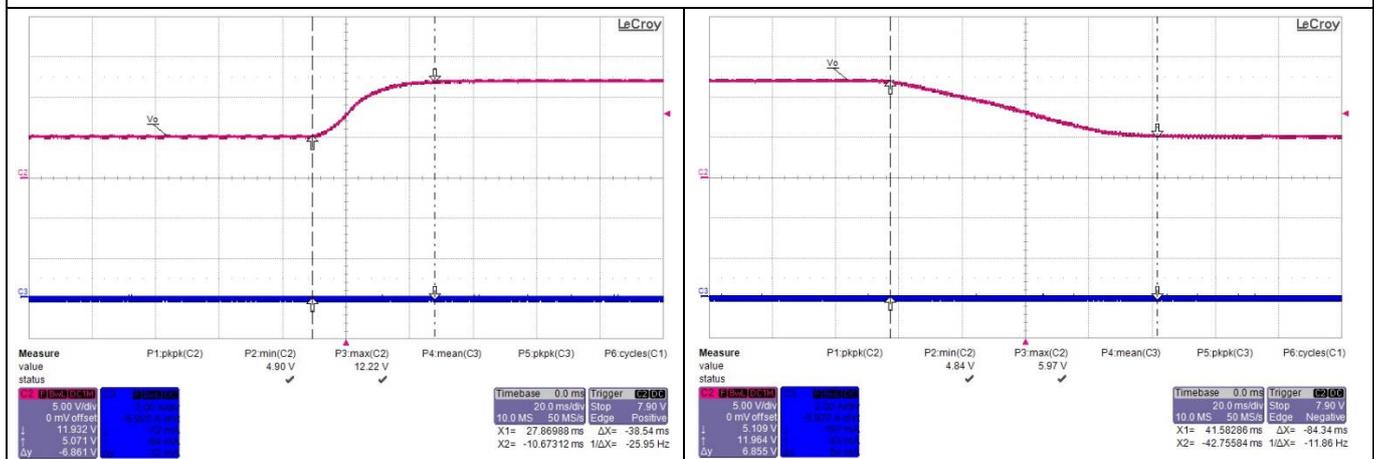

Transition time without load: 38.54 ms

Transition time with full load: 84.34 ms

Waveform and oscilloscope plots

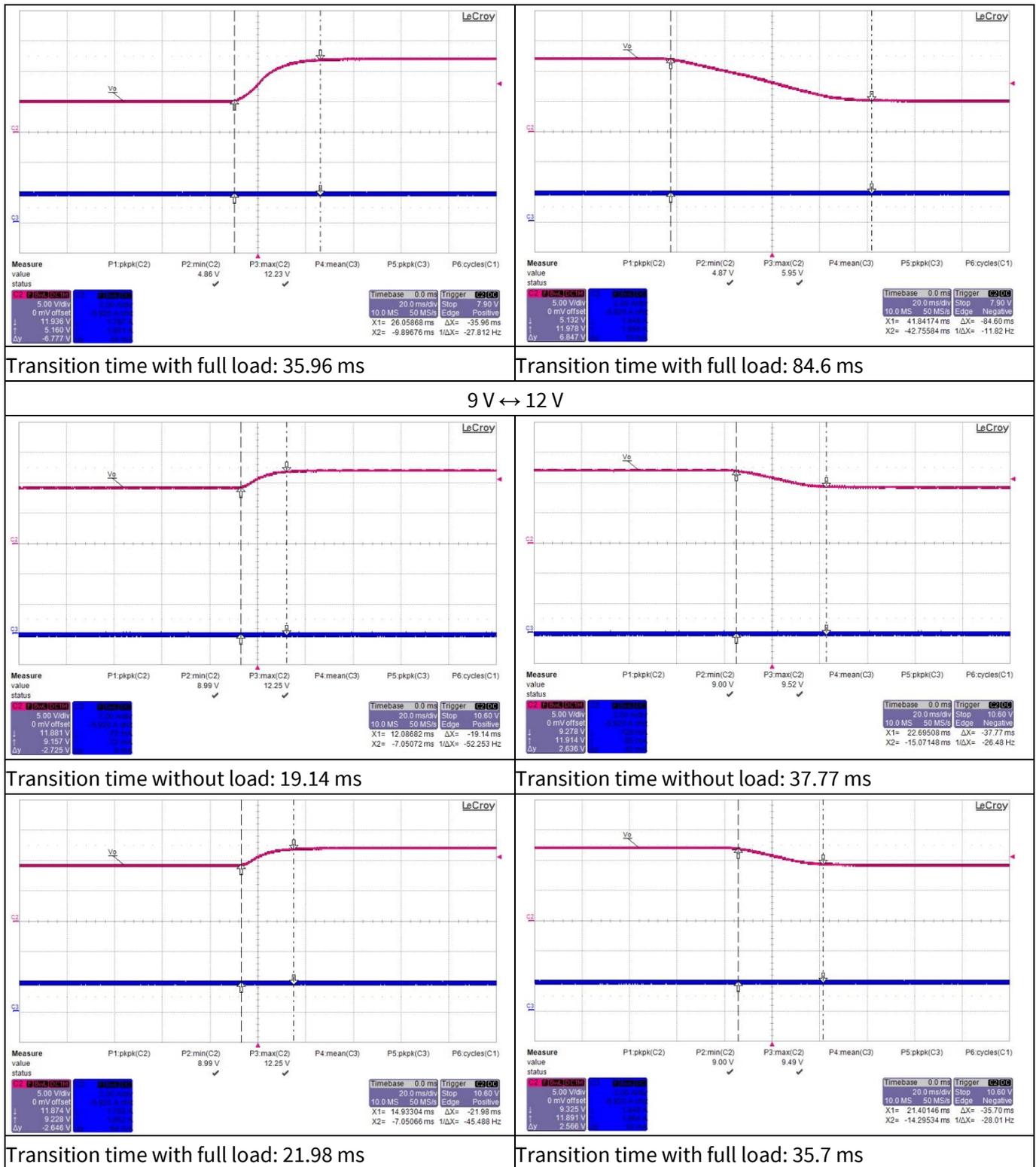


Figure 30 Output voltage transition

Waveform and oscilloscope plots

10.7 Entering ABM (5 V output)

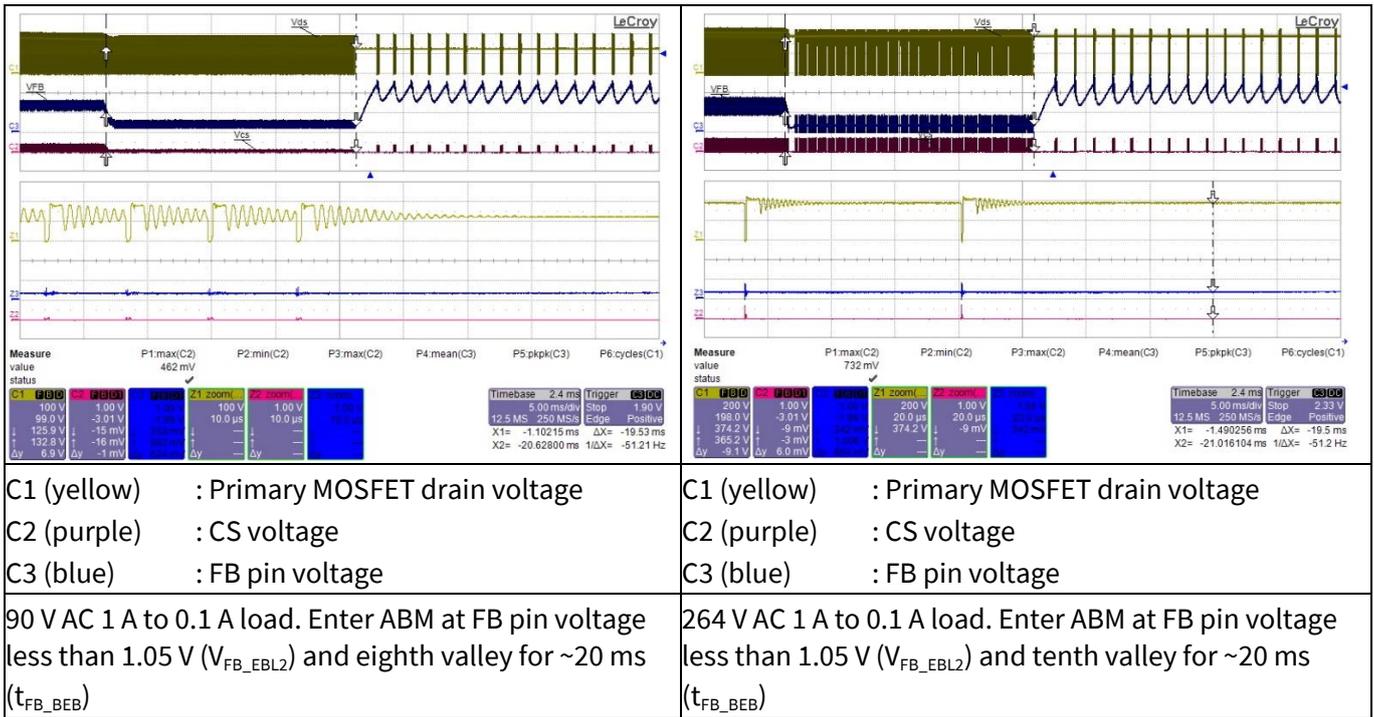


Figure 31 Entering ABM; output at 1 A to 100 mA load

10.8 During ABM (5 V output)

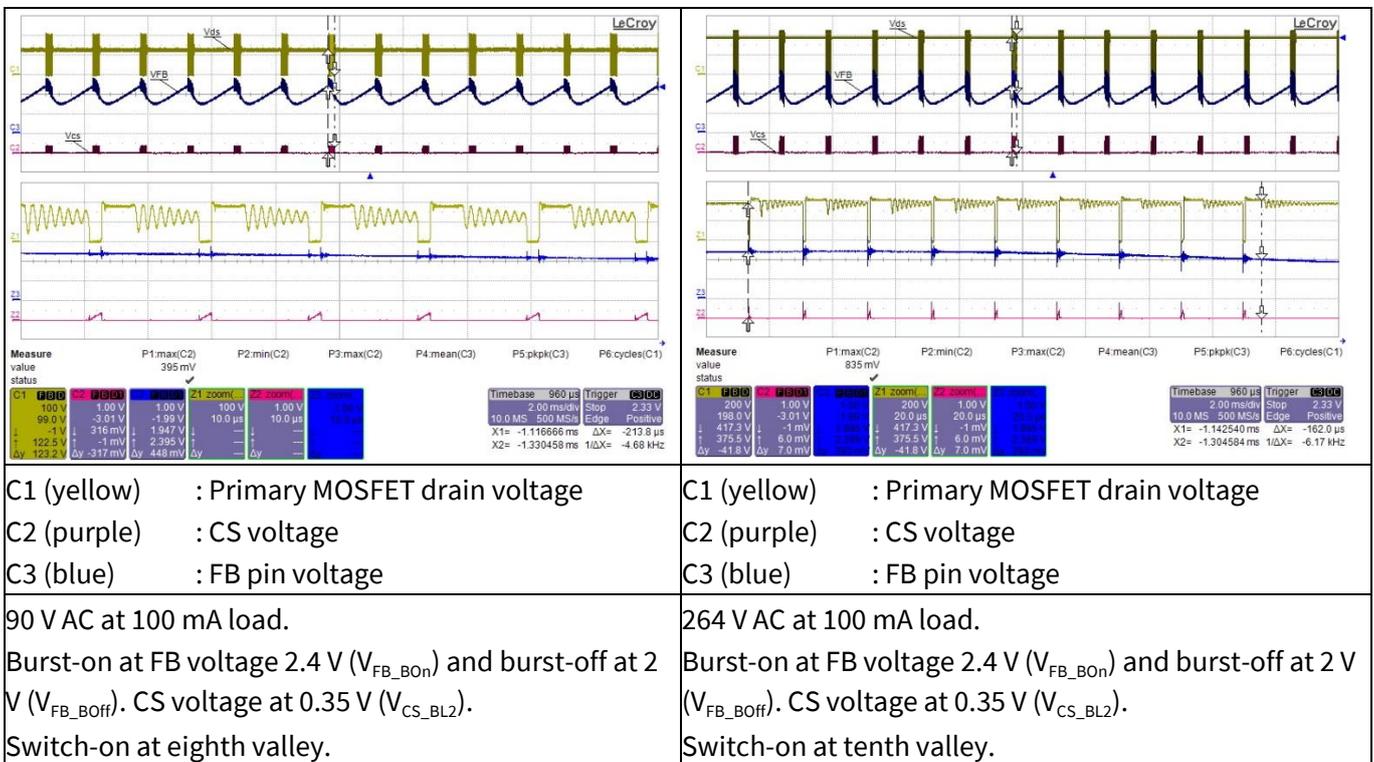


Figure 32 During ABM; output at 100 mA load

Waveform and oscilloscope plots

10.9 Leaving ABM (5 V output)

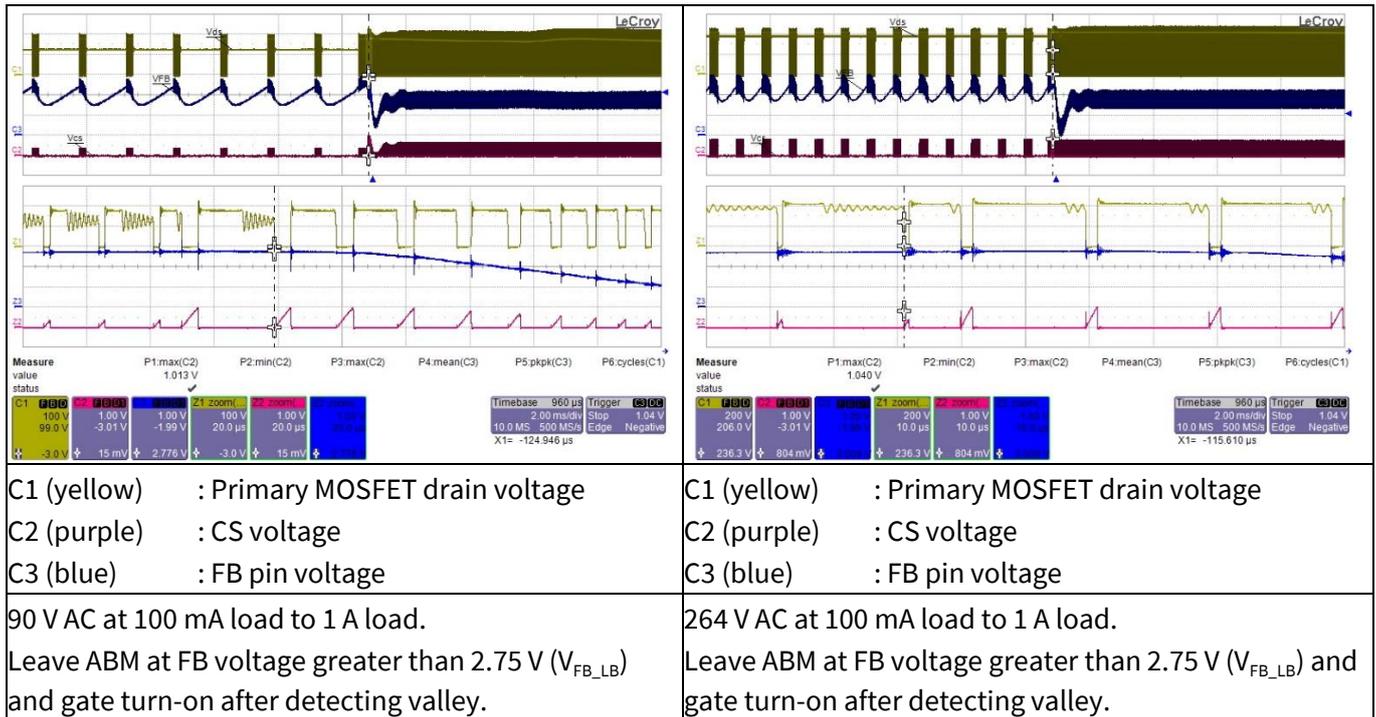


Figure 33 Leaving ABM; output at 10 mA load to 1 A load

Waveform and oscilloscope plots

10.10 Output OVP (fixed PDO)


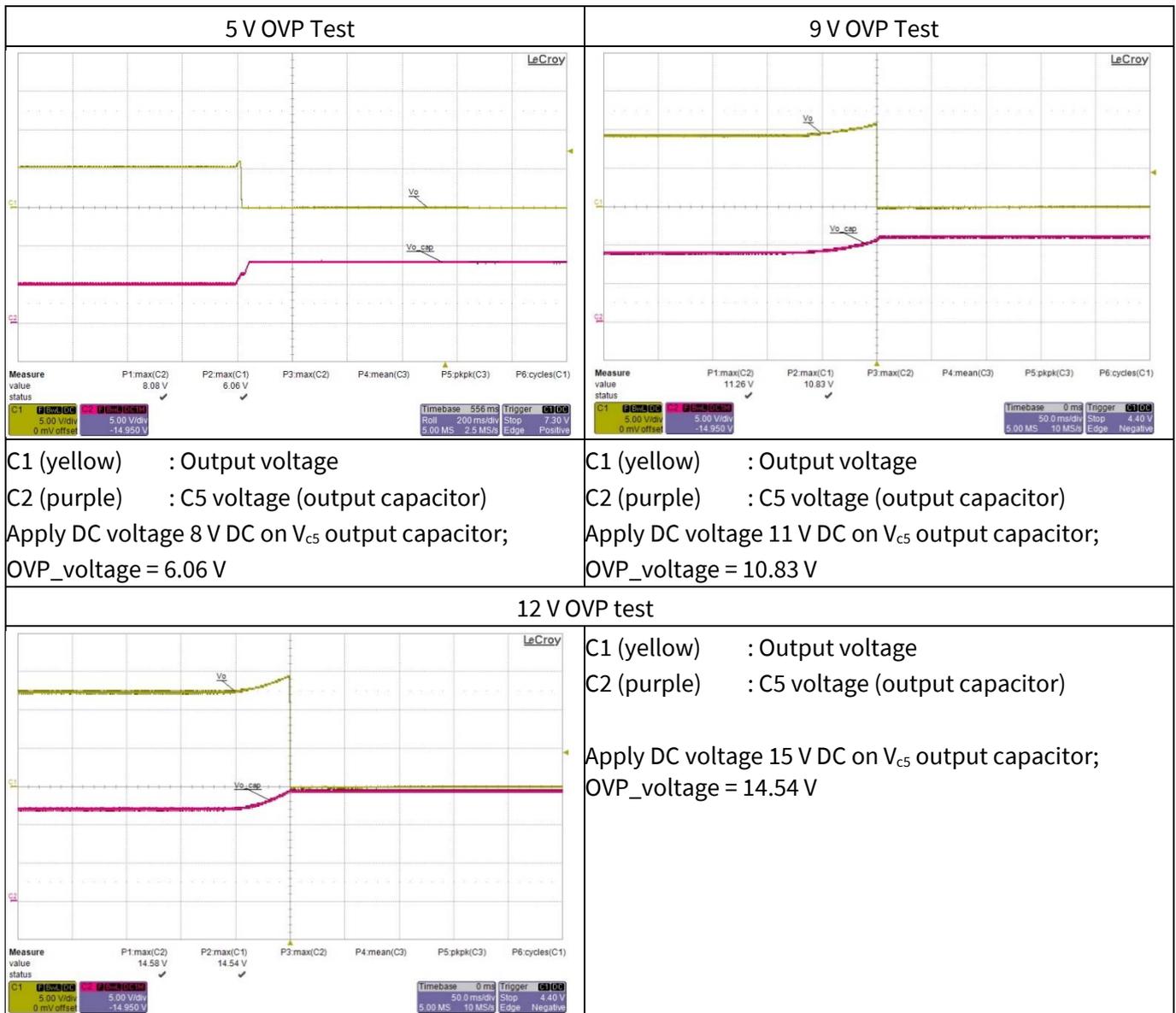


Figure 34 Output OVP at no load

Waveform and oscilloscope plots

10.11 Brown-in/-out protection

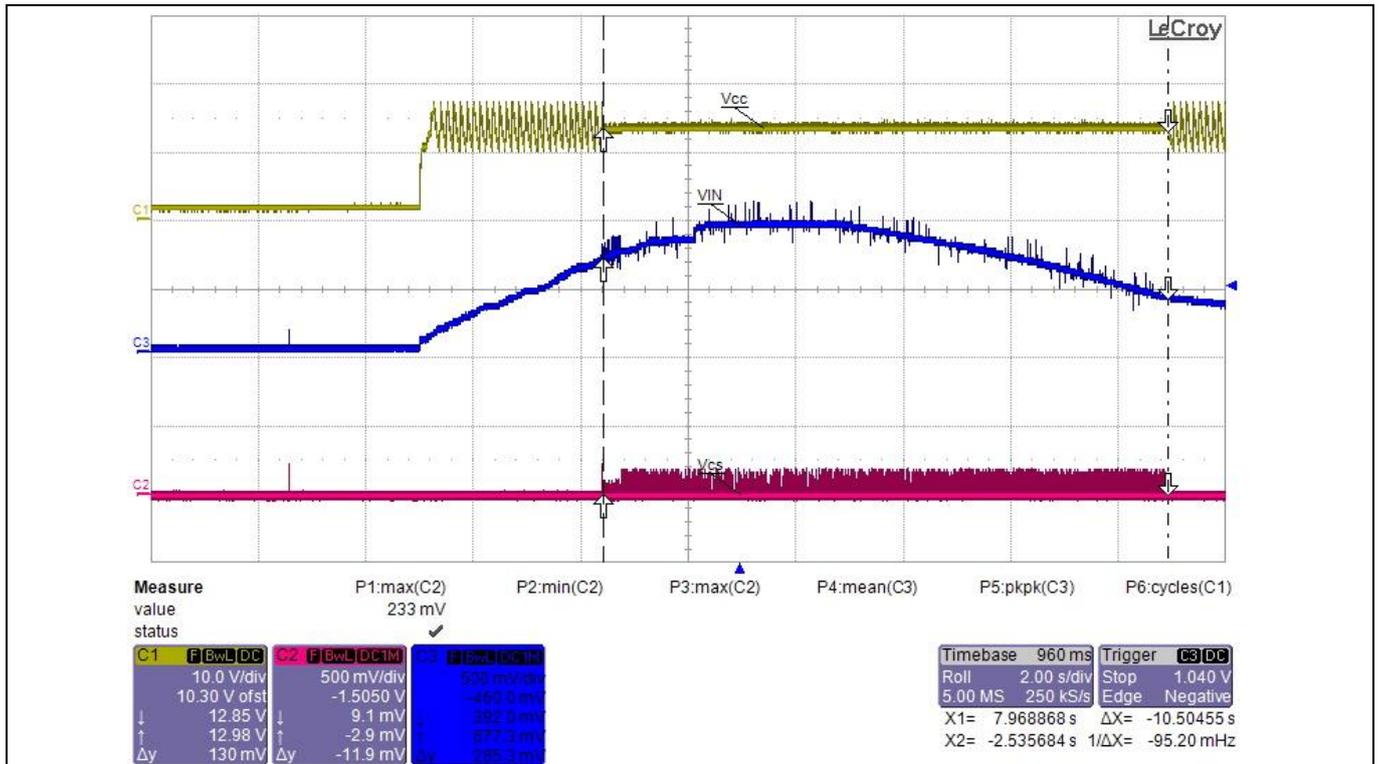

C1 (yellow) : Primary MOSFET drain voltage
 C2 (purple) : CS voltage
 C3 (blue) : VIN pin voltage

1. Gradually increase input voltage at no load. Brown-in at V_{VIN} voltage greater than 0.66 V (V_{VIN_BI}).
 2. Gradually decrease input voltage at no load. Trigger brown-out protection at V_{VIN} voltage less than 0.40 V (V_{VIN_BO}).
- Non-switch auto restart mode.

Figure 35 Brown-in/-out protection at no load. Brown-in at ~80 V AC and brown-out at ~48 V AC. The expected line OVP is at ~350 V AC.

Waveform and oscilloscope plots

10.12 Overcurrent protection (fixed PDO)

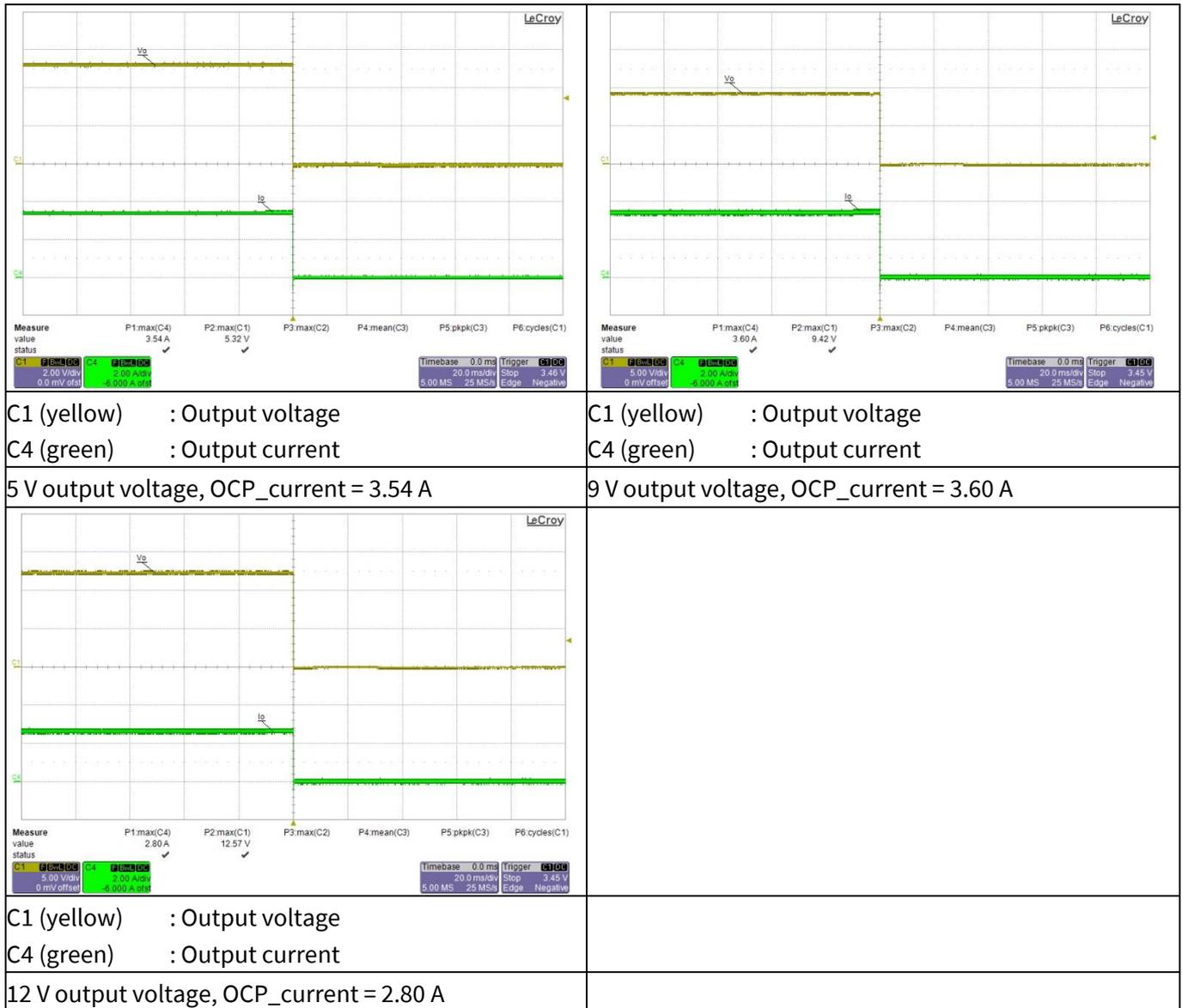


Figure 36 Overcurrent protection

Waveform and oscilloscope plots

10.13 Hold-up time (9 V/3 A)

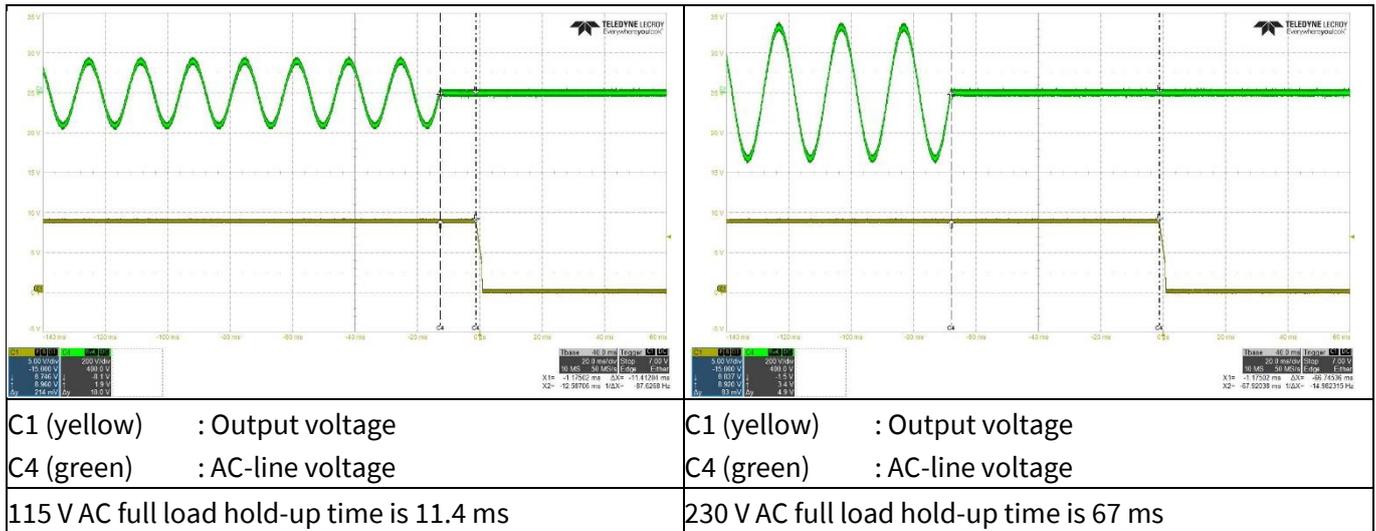


Figure 37 Hold-up time at full load

11 Appendix A: Transformer design and spreadsheet

Design procedure for QR flyback converter using Q5 CoolSET™ 5QRxxxxAx (Version 1.1)


Project	33 W USB PD charger using ICE5QSBG
Application	90 ~ 264 V AC, 11 V/3 A single-output single FB
Controller	ICE5QSBG
Date	
Version	1.0

Enter design variables in yellow colored cells

Read design results in green colored cells

Equation numbers are according to the application note

			Unit	Value
Input	Minimum AC input voltage	$V_{AC\ Min}$	[V]	90
Input	Maximum AC input voltage	$V_{AC\ Max}$	[V]	264
Input	Line frequency	f_{AC}	[Hz]	60
Input	Bus capacitor (C13) DC ripple voltage	$V_{DC\ Ripple}$	[V]	48
Input	Output voltage 1	V_{Out1}	[V]	11
Input	Output current 1	I_{Out1}	[A]	3.00
Input	Forward voltage of output diode (D21)	$V_{F\ Out1}$	[V]	0.1
Input	Output ripple voltage	$V_{Out\ Ripple}$	[V]	0.24
Input	Maximum output power for start-up, transient response and over-load protection	$P_{Out\ Max}$	[W]	33
Result	Nominal output power	$P_{Out\ Nor}$	[W]	33.00
Input	Minimum output power	$P_{Out\ Min}$	[W]	3
Input	Efficiency	η		0.88
Result	Drain-to-source capacitance of MOSFET (including $C_{o(er)}$ of MOSFET)	$C_{DS+C_{o(er)}}$	[pF]	10.00

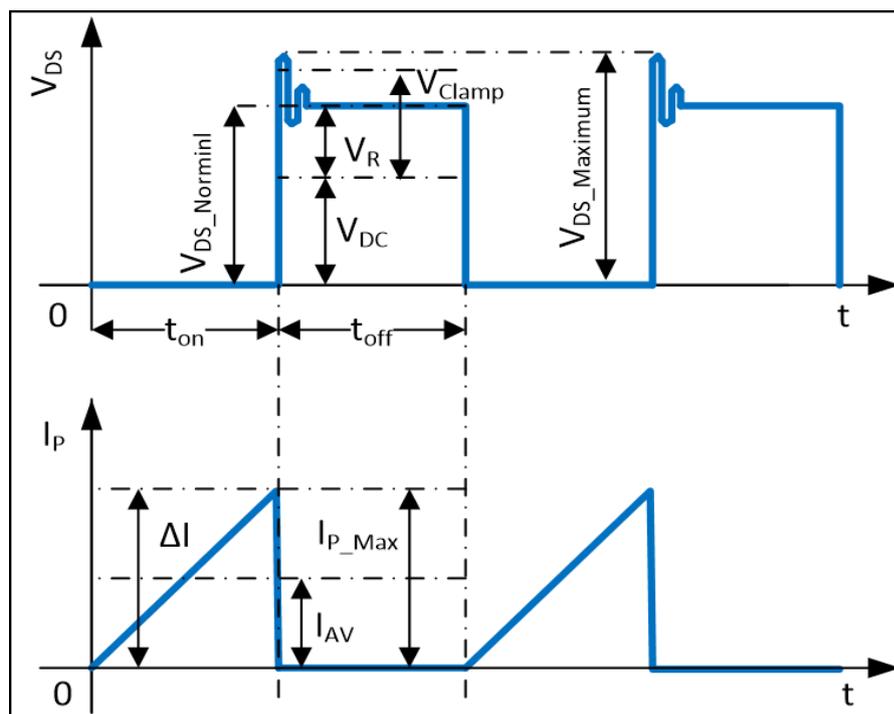

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Appendix A: Transformer design and spreadsheet

Input	Reflection voltage	V_R	[V]	99.9
Input	V_{CC} voltage	V_{VCC}	[V]	18
Input	Forward voltage of V_{CC} diode (D12)	$V_{F VCC}$	[V]	0.6
<i>Result</i>	Fifth-generation QR flyback PWM controller	CoolSET™ -Q5		ICE5QSBG
Input	Low-line min. switching frequency	f_s	[Hz]	62000
Input	Targeted max. drain-to-source voltage	$V_{DS Max}$	[V]	700
Input	Max. ambient temperature	T_a	[°C]	50

Diode bridge (BR1)

<i>Result</i>	Eq 1	$P_{In Max}$	[W]	37.5
<i>Result</i>	Eq 2	$I_{AC RMS}$	[A]	0.694
<i>Result</i>	Eq 3	$V_{DC Max Pk}$	[V]	373.35
<i>Result</i>	Eq 4	$V_{DC Min Pk}$	[V]	127.28
<i>Result</i>	Eq 10	$V_{DC Min}$	[V]	77.83
<i>Result</i>	Eq 6	T_D	[ms]	5.95
<i>Result</i>	Eq 7	W_{In}	[Ws]	0.22
<i>Result</i>	Eq 11	D_{Max}		0.5621

Input capacitor (C13)

<i>Result</i>	Eq 8	C_{in} (C13)	[μF]	45.01
Input	Select input capacitor	C_{in} (C13)	[μF]	44

Transformer (TR1)

<i>Result</i>	Eq 12	L_P	[H]	4.015E-04
<i>Result</i>	Eq 13	I_{AV}	[A]	0.86
<i>Result</i>	Eq 14	ΔI	[A]	1.758
<i>Result</i>	Eq 15	$I_{P Max}$	[A]	1.74
<i>Result</i>	Eq 16	I_{valley}	[A]	0.0
<i>Result</i>	Eq 17	$I_{P RMS}$	[A]	0.75

Select core type

Input	Select core type			10
		Core type		RM8
		Core material		TP4A
	Maximum flux density	B_{Max}	[T]	0.35
	Effective magnetic cross-section	A_e	[mm ²]	52
	Bobbin width	BW	[mm]	9.14
	Winding cross-section	A_N	[mm ²]	31.35
	Average length of turn	l_N	[mm]	44.6

Winding calculation

<i>Result</i>	Eq 18	N_P	Turns	38.29
Input	Choose number of primary turns	N_P	Turns	45
<i>Result</i>	Eq 19	N_{S1}	Turns	5.00
Input	Choose number of secondary turns	N_{S1}	Turns	5
<i>Result</i>	Eq 20	N_{VCC}	Turns	8.38
5Input	Choose number of auxiliary turns	N_{VCC}	Turns	20
<i>Result</i>	Auxiliary supply voltage (Eq 21)	V_{VCC}	[V]	43.80

Post calculation

<i>Result</i>	Eq 23	V_R	[V]	99.9
<i>Result</i>	Eq 24	D_{Max}		0.56
<i>Result</i>	Eq 25	D_{Max}'		0.44
<i>Result</i>	Eq 26	B_{Max}	[T]	0.298

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Appendix A: Transformer design and spreadsheet

CS resistor (R14)

Input	CS threshold value from datasheet	V_{csth}	[V]	1
Result	Eq 21	R _{Sense}	[Ω]	0.58
Result	Eq 22	P _{SR}	[W]	0.32
Input	PWM-OP gain from datasheet	A_v		2.05
Result	Eq 94	Z _{PWM}	[V/A]	1.2

Transformer winding design

Input	Margin according to safety standard	M	[mm]	0
Input	Copper space factor	f_{cu}		0.4

Primary

Input	Insulation thickness	INS	[mm]	0.01
Result	Eq 32	A _p (area of primary wire)	[mm ²]	0.14
Result	Eq 36	d (diameter of primary wire)	[mm]	0.42
Result	Eq 35	AWG		26
Input	Selected wire size	AWG		27
Input	Number of parallel wires	np		1
Result	Eq 37	D (diameter of primary wire)	[mm]	0.36
Result	Eq 38	(Effective copper area of primary)	[mm ²]	0.1034
Result	Eq 39	S _p (primary current density)	[A/mm ²]	7.22
Result	Eq 30	BW _e (effective bobbin width)	[mm]	9.1
Result	Eq 40	Od _p (diameter of primary wire including insulation)	[mm]	0.38
Result	Eq 41	NL _p (max. primary turns/layer)	Turns/layer	23
Result	Eq 42	Ln _p (primary layers)	Layers	2

Secondary

Input	Insulation thickness	INS	[mm]	0.02
Result	Eq 33	A _s (area of secondary wire)	[mm ²]	1.13
Result	Eq 36	d (diameter of secondary wire)	[mm]	1.20
Result	Eq 35	AWG		17
Input	Selected wire size	AWG		22
Input	Number of parallel wires	np		2
Result	Eq 37	dia (diameter of secondary wire)	[mm]	0.65
Result	Eq 38	(Effective copper area of secondary)	[mm ²]	0.6564
Result	Eq 39	S _s (secondary current density)	[A/mm ²]	9.04
Result	Eq 30	BW _E (effective bobbin width)	[mm]	9.1
Result	Eq 40	Od _s (diameter of secondary wire including insulation)	[mm]	0.69
Result	Eq 41	NL _s (max. secondary turns/layer)	Turns/layer	6
Result	Eq 42	Ln _s (secondary layers)	Layers	1

Leakage Inductance

Input		Leakage inductance in % of L_p	[%]	1
Result	Eq 45	L _{LK}	[H]	4.01E-06

RCD clamper circuit (D11,R11 and C15)

Result	Eq 44	V _{clamp}	[V]	226.75
Result	Eq 46	C _{clamp} (C15)	[nF]	0.2
Input	Selected C_{clamp} capacitor value	C_{clamp} (C15)	[nF]	1
Result	Eq 47	R _{clamp} (R11)	[kΩ]	257.9
Input	Selected R_{clamp} value	R_{clamp} (R11)	[kΩ]	440

Output and V_{cc} diode (D21, D22 and D12)

Result	Eq 27	K _{L1} (load factor)		1.00
--------	-------	-------------------------------	--	------

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Appendix A: Transformer design and spreadsheet

Result	Eq 43a	$V_{RDiode1}$ (for output MOSFET)	[V]	52.48
Result	Eq 28	$I_{S\ Max1}$	[A]	15.62
Result	Eq 29	$I_{S\ RMS1}$	[A]	5.93
Result	Eq 43b	V_{RDiode} (for V_{CC} diode)	[V]	183.93

Output capacitor (C22 and C23)

Input	Max. voltage overshoot at output capacitor (C22, C23)	ΔV_{Out}	[V]	0.5
Input	Number of clock periods	n_{cp}		10
Result	Eq 49	I_{Ripple}	[A]	5.11
Result	Eq 50	C_{Out}	[μ F]	968

Soft-start time

Input	Chosen soft-start time from datasheet	$t_{softstart}$	[ms]	12
-------	---------------------------------------	-----------------	------	----

V_{CC} capacitor (C16) and start-up time

Input	Chosen $I_{VCC,Charge3}$ from datasheet	$I_{VCC,Charge3}$	[mA]	3
Input	Chosen $V_{VCC,hys}$ from datasheet	$V_{VCC,hys}$	[V]	6
Result	Eq 56A	C_{VCC}	[μ F]	6.00
Input	Select V_{CC} capacitor	C_{VCC} (C16)	[μ F]	20
Input	Select $V_{VCC,STG}$ from datasheet	$V_{VCC,STG}$	[V]	1.1
Input	Select $I_{VCC,Charge1}$ from datasheet	$I_{VCC,Charge1}$	[mA]	0.2
Input	Select $V_{VCC,ON}$ from datasheet	$V_{VCC,ON}$	[V]	16
Result	Eq 56B	$t_{StartUp}$	[ms]	216.67

Calculation of losses

Input diode bridge

Result	Eq 57 ($V_f = 1.1\text{ V}$)	P_{DIN}	[W]	1.53
--------	--------------------------------	-----------	-----	------

Transformer copper losses

Result	Eq 58	R_{PCu}	[m Ω]	333.74
Result	Eq 58	R_{SCu}	[m Ω]	5.84
Result	Eq 59	P_{PCu}	[mW]	186.13
Result	Eq 60	P_{SCu}	[mW]	205.64
Result	Eq 61	P_{Cu}	[W]	0.3918

Output SR

Result	Eq 62 ($R_{DS(on)} = 9\text{ m}\Omega$)	$P_{Out\ SR}$	[W]	0.05
--------	---	---------------	-----	------

RCD clamper circuit

Result	Eq 63	$P_{Clamper}$	[W]	0.54
--------	-------	---------------	-----	------

MOSFET

Input	$R_{DS(on)}$ from datasheet	$R_{DS(on)} @ T_A=125^\circ\text{C}$	[Ω]	1.03
Input	$C_{o(er)}$ from datasheet	$C_{o(er)}$	[pF]	17
Input	External drain-to-source capacitance of MOSFET	C_{ds}	[pF]	0

MOSFET losses at $V_{ACmin} + P_{max}$

Result	Eq 65	P_{SON}	[W]	0.000256704
Result	Eq 66	P_{cond}	[W]	0.5744
Result	Eq 67	MOSFET losses	[W]	0.5747

MOSFET losses at $V_{ACmax} + P_{max}$

Result	Eq 68	P_{SON}	[W]	0.0512
Result	Eq 69	P_{cond}	[W]	0.1557
Result	Eq 70	MOSFET losses	[W]	0.2069

Temperature calculation

Input	Enter MOSFET losses	MOSFET losses	[W]	0.5747
Input	Enter thermal resistance junction - ambient	R_{th}	[$^\circ\text{K/W}$]	80
Result	Eq 74	ΔT	[$^\circ\text{K}$]	46

33 W USB power delivery charger using ICE5QSBG

REF_5QSBG_33W1



Appendix A: Transformer design and spreadsheet

Result	Eq 75	T_{jmax}	°C	96
--------	-------	------------	----	----

Controller

Result	$I_{VCC,Normal} \times V_{VCC}$	Controller losses	[W]	0.0258
--------	---------------------------------	-------------------	-----	--------

Choke losses and thermistor loss

Result	$I_{AC,RMS} \times R_{DCR}$	P_{Choke}	[W]	0.6389
--------	-----------------------------	-------------	-----	--------

Result	$I_{AC,RMS} \times R_{NTC}$	P_{NTC}	[W]	0.1069
--------	-----------------------------	-----------	-----	--------

Sum of losses

Result	Eq 77	P_{Losses}	[W]	3.85
--------	-------	--------------	-----	------

Efficiency after losses

Result	Eq 78	η_L		0.8855
--------	-------	----------	--	--------

ZCD and output OVP calculation

Input	Designed V_{OUT_OVP}	V_{OUT_OVP}	[V]	15
-------	-------------------------	----------------	-----	----

Input	$V_{ZC_OVP_MIN}$ from datasheet	$V_{ZC_OVP_MIN}$	[V]	1.9
-------	-----------------------------------	--------------------	-----	-----

Input	R_{ZCD_MIN} from datasheet	R_{ZCD}	[kΩ]	3
-------	-------------------------------	-----------	------	---

Result	Eq 103	R_{ZC} (R15)	[kΩ]	92.37
--------	--------	----------------	------	-------

Input	Selected value of R15	R_{ZC} (R15)	[kΩ]	91
-------	-----------------------	----------------	------	----

Input	f_{OSC2} by measurement	f_{OSC2}	[kHz]	820
-------	---------------------------	------------	-------	-----

Result	Eq 104	C_{ZC} (C19)	[pF]	118
--------	--------	----------------	------	-----

Input	Selected value of C_{ZC} (C19)	C_{ZC} (C19)	[pF]	33
-------	----------------------------------	----------------	------	----

Line OVP is the first priority and its associated brown-out, brown-in and line selection

Input		R_{I1} (R18)	[Ω]	9,000,000
-------	--	----------------	-----	-----------

Input		Line over voltage (V_{OVP_AC})	[V AC]	320
-------	--	-------------------------------------	--------	-----

Input		V_{DC} Ripple	[V]	48
-------	--	-----------------	-----	----

Result	Eq 105A	R_{I2} (R19)	[Ω]	58,045
--------	---------	----------------	-----	--------

Input	Selected value of R19 (R_{I2})	R_{I2} (R19)	[Ω]	58,300
-------	------------------------------------	----------------	-----	--------

Result	Eq 106	Brown-in voltage ($V_{Brownin_AC}$)	[V AC]	73
--------	--------	--	--------	----

Result	Eq 107	Brown-out voltage for full load which considers $V_{DCRIPPLE}$ ($V_{Brownout_AC}$)	[V AC]	78
--------	--------	---	--------	----

Result	Eq 107	Brown-out voltage for light load which neglects $V_{DCRIPPLE}$ ($V_{Brownout_AC}$)	[V AC]	44
--------	--------	---	--------	----

Result	Eq 108	Line selection threshold with $V_{DCRIPPLE}$ ($V_{VIN} = 1.52$ V)	[V AC]	201
--------	--------	--	--------	-----

Result	Eq 108	Line selection threshold without $V_{DCRIPPLE}$ ($V_{VIN} = 1.52$ V)	[V AC]	167
--------	--------	---	--------	-----

Brown-out is the first priority and its associated line OVP and line selection

Input		R_{I1} (R18)	[Ω]	9,000,000
-------	--	----------------	-----	-----------

Input		Brown-in voltage (V_{OVP_AC})	[V AC]	73
-------	--	------------------------------------	--------	----

Input		$V_{DCRIPPLE}$	[V]	48
-------	--	----------------	-----	----

Result	Eq 105B	R_{I2} (R19)	[Ω]	57,907
--------	---------	----------------	-----	--------

Input	Selected value of R19 (R_{I2})	R_{I2} (R19)	[Ω]	58,300
-------	------------------------------------	----------------	-----	--------

Result	Eq 107	Brown-out voltage for full load which considers $V_{DCRIPPLE}$ ($V_{Brownout_AC}$)	[V AC]	78
--------	--------	---	--------	----

Result	Eq 107	Brown-out voltage for light load which neglects $V_{DCRIPPLE}$ ($V_{Brownout_AC}$)	[V AC]	44
--------	--------	---	--------	----

Result	Eq 114	Line over voltage (V_{OVP_AC})	[V AC]	319
--------	--------	-------------------------------------	--------	-----

Result	Eq 108	Line selection threshold with $V_{DCRIPPLE}$ ($V_{VIN} = 1.52$ V)	[V AC]	201
--------	--------	--	--------	-----

Result	Eq 108	Line selection threshold without $V_{DCRIPPLE}$ ($V_{VIN} = 1.52$ V)	[V AC]	167
--------	--------	---	--------	-----

References

12 References

- [1] [ICE5QSBG datasheet, Infineon Technologies AG](#)
- [2] [PAG1S – CYPAS111 datasheet, Cypress Semiconductor Corporation](#)
- [3] [IPAN70R600P7S datasheet, Infineon Technologies AG](#)
- [4] [AN-201609_PL83_026 – 5th Generation QR Design Guide](#)
- [5] [Calculation Tool Quasi Resonant CoolSET™ Generation 5](#)

Revision history

Revision history

Document version	Date of release	Description of changes
V 1.0	2020-09-07	First release

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2020-09-07

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2020 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference

AN_2007_PL83_2007_093226

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.