

TLE 472x – Family Stepper Motor Drivers

Current Control Method and Accuracy

by Frank Heinrichs

Automotive Power



Never stop thinking.

1. Abstract

This Application Note is intended to provide detailed technical information about the current control method that is used in Infineons stepper motor driver family TLE 472x. Special attention is paid on accuracy considerations.

2. Introduction

The TLE 472x stepper motor drivers are intended to be used for bipolar, two-phase, current-controlled stepper motors (see figure 1).

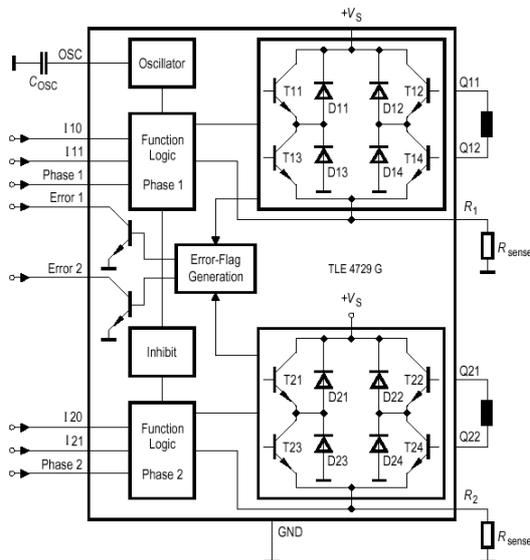


Figure1: TLE 4729 block-diagram

3. Current Control Method

In general, three different methods are used to control the current in the coil of a stepper motor:

3.1. Peak current control with fixed off-time

With this control method, the H-bridge is switched into freewheel-condition as soon as the output current reaches the desired value I_{target} . The bridge remains in off-state for a fixed time t_{off} and is switched on again automatically after t_{off} (see figure 2). As a result, the peak value of the output current equals the desired value.

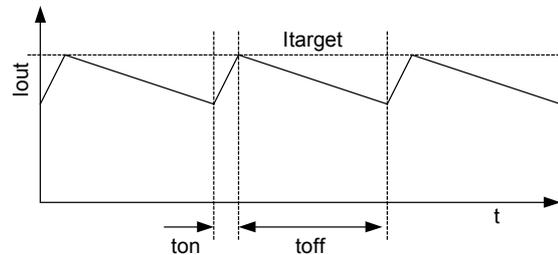


Figure 2: peak current control with constant off-time

3.2. Peak current control with fixed frequency

With this control method, the H-bridge is switched into freewheel-condition as soon as the output current reaches the desired value I_{target} . In contrast to the previous method, the off-time is not fixed, but the bridge is switched ON after every time interval $1/f$, f being the chopper frequency as shown in figure 3. This has the advantage that the chopper frequency is fixed, i.e. independent of the load characteristics and the supply voltage (in other words: independent of the off-time t_{off}). **This control method is used in the TLE 472x driver family.**

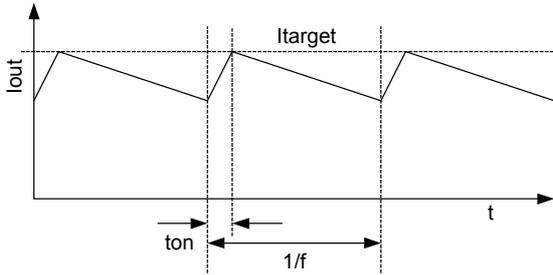


Figure 3: peak current control with fixed frequency

3.3. Mean-value current control (current-mode control).

The control methods described so far have the disadvantage that the effective, mean output current is always smaller than the desired current. By using suitable filters and comparators, it is also possible to control the current in such a manner that the mean value of the output current is equal to the desired value Itarget, as shown in figure 4.

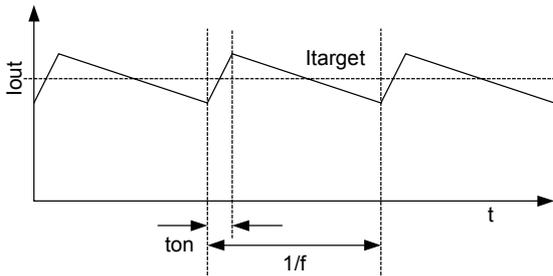


Figure 4: current-mode control

However, for this method it is necessary to adapt the filtering elements to the load characteristics, so a fully integrated IC solution is not possible. For that reason, current mode control is not implemented in the TLE 472x family.

4. Implementation

As just described, fixed frequency peak-current control is used in the TLE 472x stepper motor driver family. As simplified schematic of the implementation is shown in figure 5.

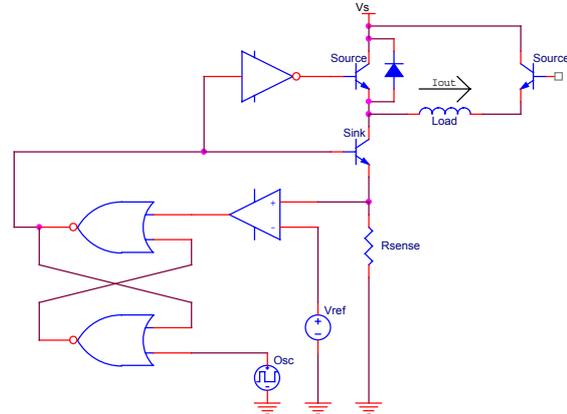


Figure 5: simplified schematic of current control implementation

The oscillator sets the NOR-latch output to high with the oscillator frequency fosc. By this, the sink-transistor is turned ON every period 1/f.

According to the input signals IXX, a reference voltage Vref is generated:

IX0	IX1	Symb.	min	typ	max	unit
H	L	Vch	40	70	100	mV
L	H	Vcs	410	450	510	mV
H	H	Vca	630	700	800	mV

This reference Voltage is compared to the drop across the sense resistor Rsense. As soon as Iout * Rsense equals Vref, the NOR-latch is set to low. This turns OFF the sink transistor, setting the H-bridge to freewheel (freewheel in source transistors).

This means that the desired output current is:

$$I_{target} = V_{ref} / R_{sense}$$

5. Accuracy Considerations

The accuracy of the actual output current value depends on the accuracy of :

- the internal comparator reference voltage Vref
- the external sense resistor
- the current ripple

5.1. Accuracy of Vref and Rsense

The accuracy of Vref is given in the datasheet and in above table. For Example, the Setpoint

current has a nominal value of 450mV and a variation of -9% and +13%. As the output current depends linearly on Vref, the same accuracy has to be expected for the output current.

The same is true for the sense resistor. The accuracy of Rsense contributes linearly to the accuracy of Iout.

5.2. Current ripple

As explained earlier, the control method leads to an average current smaller than the desired current Itarget because the peak current is limited to Itarget. If DI is the current ripple, the average current is

$$I_{out,mean} = I_{target} - DI/2$$


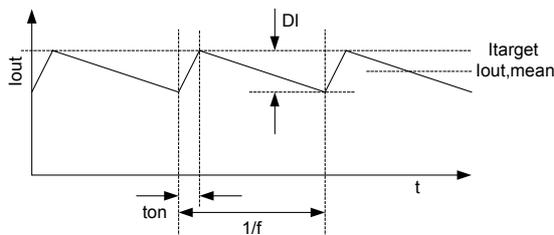


Figure 6: Current ripple, peak- and mean current

To determine, the current ripple, we have to calculate the voltage drop across the load inductivity.

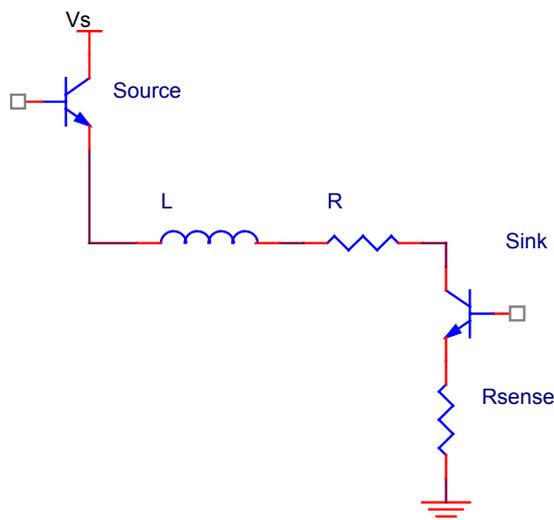5.2.1. (di/dt)charge

For the rising current slope (charging the inductivity), we have:



$$V_s = V_{satuC} + U_L + R \cdot I_{out} + V_{satl} + R_{sense} \cdot I_{out}$$

The parameter we are interested in is the current slew rate:

$$\left(\frac{di}{dt}\right)_c = \frac{U_L}{L} = \frac{(V_s - V_{satuC} - V_{satl} - I_{out}(R + R_{sense}))}{L}$$

Lets look at an example to carry out the calculation:

Vs	=	12V
Rsense	=	1.3Ohm
Iout	=	315mA
R	=	8Ohm
L = 4mH		

From the datasheet, we have (using the values at Iout = 450mA):

VsatuC	=	1V
Vsatl = 0.3V		

This leads to :

$$\left(\frac{di}{dt}\right)_c = (12 - 1 - 0.3 - 2.92)V / 4mH = 1.95 A/ms$$

5.2.2. (di/dt)discharge

The same has now to be done for the falling current slope (discharging of the inductivity, freewheeling):



We have


$$-U_L = R \cdot I_{out} + V_{Fu} + V_{satuD}, \quad \left(\frac{di}{dt}\right)_d = (R \cdot I_{out} + V_{Fu} + V_{satuD}) / L$$

For our example, this leads to:

$$\left(\frac{di}{dt}\right)_d = \frac{U_L}{L} = - (2.52 + 1 + 0.3)V / 4mH = -0.96A/ms$$

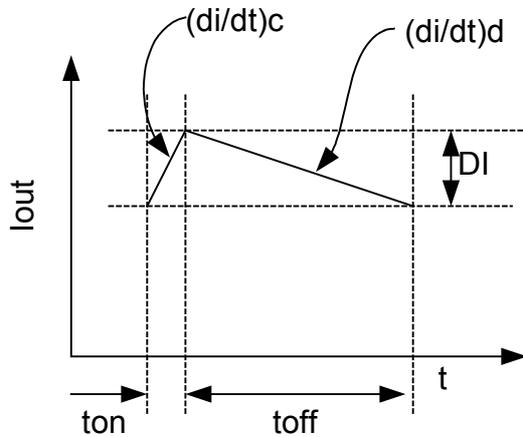5.2.3. ton, toff and Ripple

Now, we can approximate toff and ton by making the approximation of constant di/dt:



$$t_{on} + t_{off} = 1/f_{osc},$$

$$(di/dt)_c * t_{on} = (di/dt)_d * t_{off} = DI$$

This leads to:

$$t_{on} = (1/f_{osc}) / \left[\frac{(di/dt)_c}{(di/dt)_d} + 1 \right],$$

$$t_{off} = 1/f_{osc} - t_{on},$$

$$DI = (di/dt)_c * t_{on}$$

For our example with $f_{osc} = 25\text{kHz}$, this leads to:

$$t_{on} = 40\mu\text{s} / \left[\frac{1.95}{0.96} + 1 \right] = 13.2\mu\text{s}$$

$$t_{off} = 40\mu\text{s} - t_{on} = 26.8\mu\text{s}$$

We see that the ON-time is much shorter than the OFF-time. The reason is that the (higher) supply-voltage is used to charge the coil, while during freewheeling only the (smaller) drops across load resistance and power transistors contribute to the di/dt .

This finally gives us the current ripple:

$$DI = (di/dt)_c * t_{on} = 25.7\text{mA}$$

6. Conclusion

The general method to control the output current that is used in the TLE 472x stepper motor driver family was explained. An approximative formula to determine the current ripple and thus the difference between mean output current and desired current is derived and carried out for a representative example

7. Disclaimer

Edition 2000-07-14

**Published by Infineon Technologies AG,
St.-Martin-Strasse 53,
D-81541 München, Germany**

**© Infineon Technologies AG 8/d/yy.
All Rights Reserved.**

Attention please!

The information herein is given to describe certain components and shall not be considered as warranted characteristics.

Terms of delivery and rights to technical change reserved.

We hereby disclaim any and all warranties, including but not limited to warranties of non-infringement, regarding circuits, descriptions and charts stated herein.

Infineon Technologies is an approved CECC manufacturer.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office in Germany or our Infineon Technologies Representatives worldwide (see address list).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

<http://www.infineon.com>

Published by Infineon Technologies AG

8. Infineon goes business Excellence

“Business excellence means intelligent approaches and clearly defined processes, which are both constantly under review and ultimately lead to good operating results.

Better operating results and business excellence mean less idleness and wastefulness for all of us, more professional success, more accurate information, a better overview and, thereby, less frustration and more satisfaction.”

Dr. Ulrich Schuhmacher