

Application Note AN-1134

Production-Friendly Trimming Example of IR2520D

By Peter Bredemeier

Table of Contents

	Page
Introduction	2
Typical Application Diagram.....	2
IR2520D Datasheet Information.....	3
Proposed Technique	4
Implementation on PCB	5
Summary.....	5


Introduction

In ballast designs, IC trimming techniques can be applied to reduce wide parameter tolerances improving the quality and reliability of the end product. The tolerances often specified on an IC's datasheet depict the expected performance range across many IC production lots while the tolerance for a given parameter within one lot is normally much tighter.

One approach to trimming, the trial and error replacement of resistors in production, leads to bottlenecks in production and problems with logistics.

This Application Note will suggest an alternative trimming technique involving IR's IR2520D CFL ballast IC which, through the addition of two resistors used to set the minimum running frequency (RFMIN), reduces the running frequency tolerance to one third of that specified in the data sheet and minimizes production issues.

Typical Application Diagram

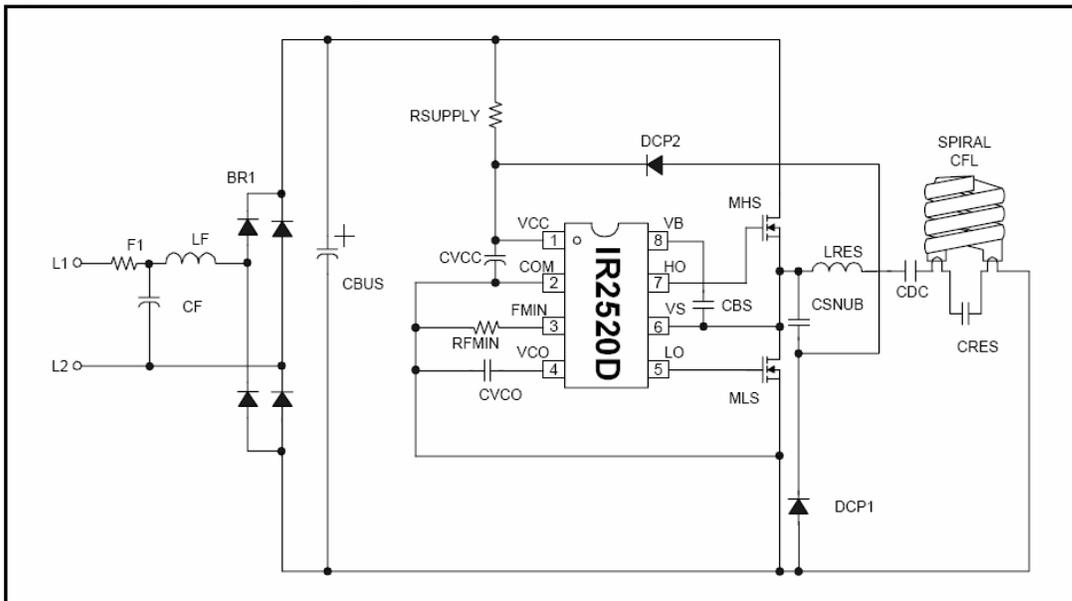

IR2520D Datasheet Information

Looking at the IR2520D datasheet, the expected frequency tolerances for $R_{FMIN} = 82\text{ k}\Omega$ is $34\text{ kHz} \pm 12\%$.

Electrical Characteristics

$V_{CC} = V_{BS} = V_{BIAS} = 14\text{ V} \pm 0.25\text{ V}$, $C_{LO} = C_{HO} = 1000\text{ pF}$, $R_{FMIN} = 82\text{ k}\Omega$ and $T_A = 25^\circ\text{C}$ unless otherwise specified.

Symbol	Definition	Min.	Typ.	Max.	Units	Test Conditions
--------	------------	------	------	------	-------	-----------------

Oscillator I/O Characteristics

Symbol	Definition	Min.	Typ.	Max.	Units	Test Conditions
$f_{(min)}$	Minimum oscillator frequency (Note 4)	29.6	34	38.2	kHz	$V_{VCO} = 6\text{V}$
$f_{(max)}$	Maximum oscillator frequency (Note 4)	67	86	96		$V_{VCO} = 0\text{V}$

Figure 14 of IR2520D datasheet provides the information needed to reduce the frequency tolerance. Note that below 60 kHz, temperature variation does not have a significant impact on the frequency.


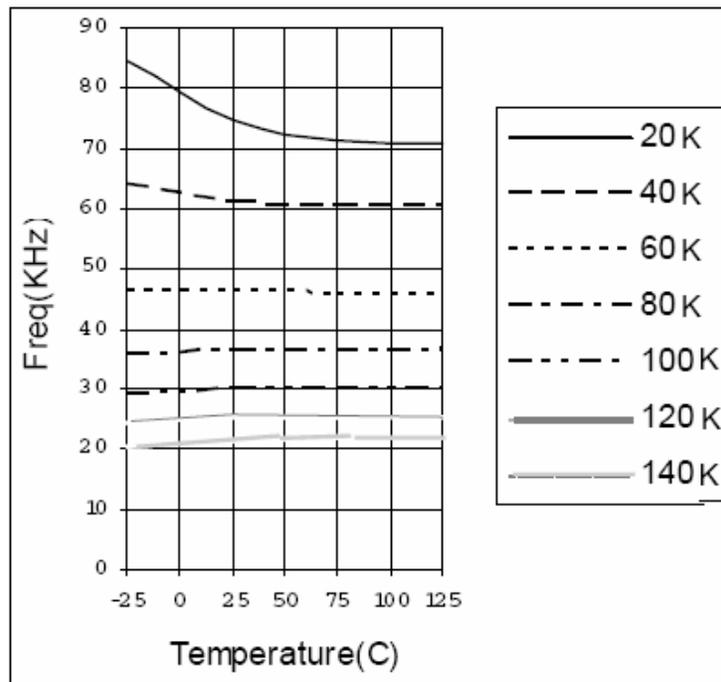


Fig. 14 Frequency vs R_{FMIN} vs TEMP
V_{VCO}=6V

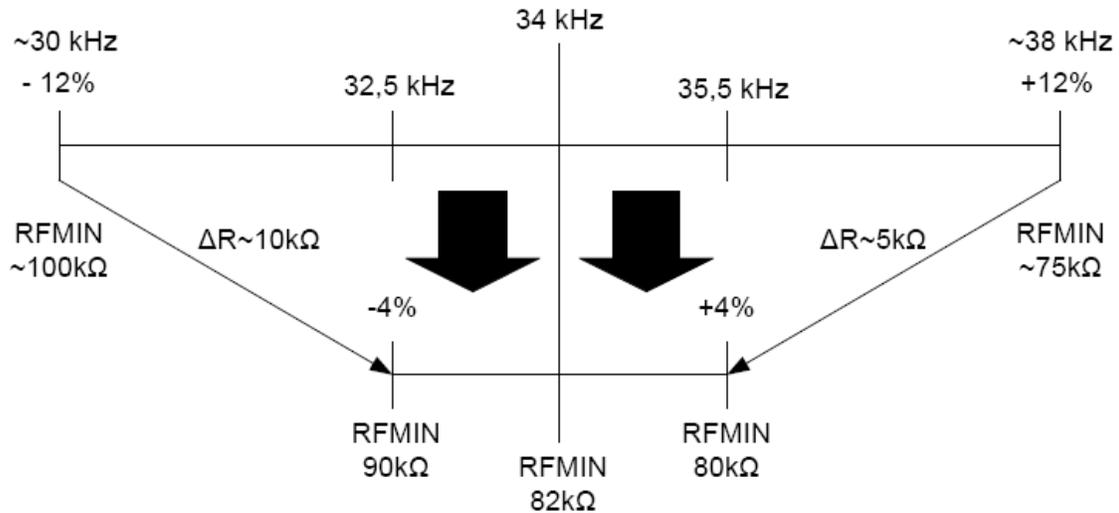Information extracted from Figure 14 of the IR2520D datasheet can be graphically summarised in this way:



If the mean frequency of an IR2520D lot is between 30 and 32.5 kHz, decreasing RFMIN by 10 kΩ will bring the frequency back into the 34 kHz $\pm 4\%$ range.

On the other side, if the mean frequency of an IR2520D lot is between 35.5 and 38 kHz, increasing RFMIN by 5 kΩ will bring the frequency back into the 34 kHz $\pm 4\%$ range.

As already stated, variations in tolerances across one lot of ballast ICs are typically small and, as a result, production variances within one lot will be minimal. If using ballast ICs from multiple lots, the frequency for each lot will need to be measured and the resistance value for RFMIN adjusted.

Proposed Technique

With two additional resistors, the frequency tolerance can be reduced to within a window of $\pm 4\%$.

With 2 solder bumps on the PCB to eventually connect the additional resistors, the resulting resistance for RFMIN can be adapted to the parameters of the ballast.

