Application Note No. 034

Carrier Lifetime and Forward Resistance in RF PIN-Diodes

RF & Protection Devices

Never stop thinking

Edition 2006-10-20

Published by
Infineon Technologies AG
81726 München, Germany

© Infineon Technologies AG 2009.
All Rights Reserved.

LEGAL DISCLAIMER

THE INFORMATION GIVEN IN THIS APPLICATION NOTE IS GIVEN AS A HINT FOR THE IMPLEMENTATION OF THE INFINEON TECHNOLOGIES COMPONENT ONLY AND SHALL NOT BE REGARDED AS ANY DESCRIPTION OR WARRANTY OF A CERTAIN FUNCTIONALITY, CONDITION OR QUALITY OF THE INFINEON TECHNOLOGIES COMPONENT. THE RECIPIENT OF THIS APPLICATION NOTE MUST VERIFY ANY FUNCTION DESCRIBED HEREIN IN THE REAL APPLICATION. INFINEON TECHNOLOGIES HEREBY DISCLAIMS ANY AND ALL WARRANTIES AND LIABILITIES OF ANY KIND (INCLUDING WITHOUT LIMITATION WARRANTIES OF NON-INFRINGEMENT OF INTELLECTUAL PROPERTY RIGHTS OF ANY THIRD PARTY) WITH RESPECT TO ANY AND ALL INFORMATION GIVEN IN THIS APPLICATION NOTE.

Information

For further information on technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies Office (**www.infineon.com**).

Warnings

Due to technical requirements components may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies Office.

Infineon Technologies Components may only be used in life-support devices or systems with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system, or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body, or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

Carrier Lifetime and Forward Resistance in RF PIN-Diodes
Revision History: 2006-10-20, Rev. 2.0

Previous Version: 2000-07-28

Page	Subjects (major changes since last revision)
All	Document layout change

1 Carrier Lifetime and Forward Resistance in RF PIN-Diodes

This abstract summarizes the fundamentals of RF PIN Diode physics. General design considerations of PIN Diodes are discussed and a measuring method for the carrier lifetime is introduced.

PIN diodes are used as switches or controlled resistors for signals at radio and microwave frequencies. **Figure 1** shows a theoretical sketch of a PIN diode.

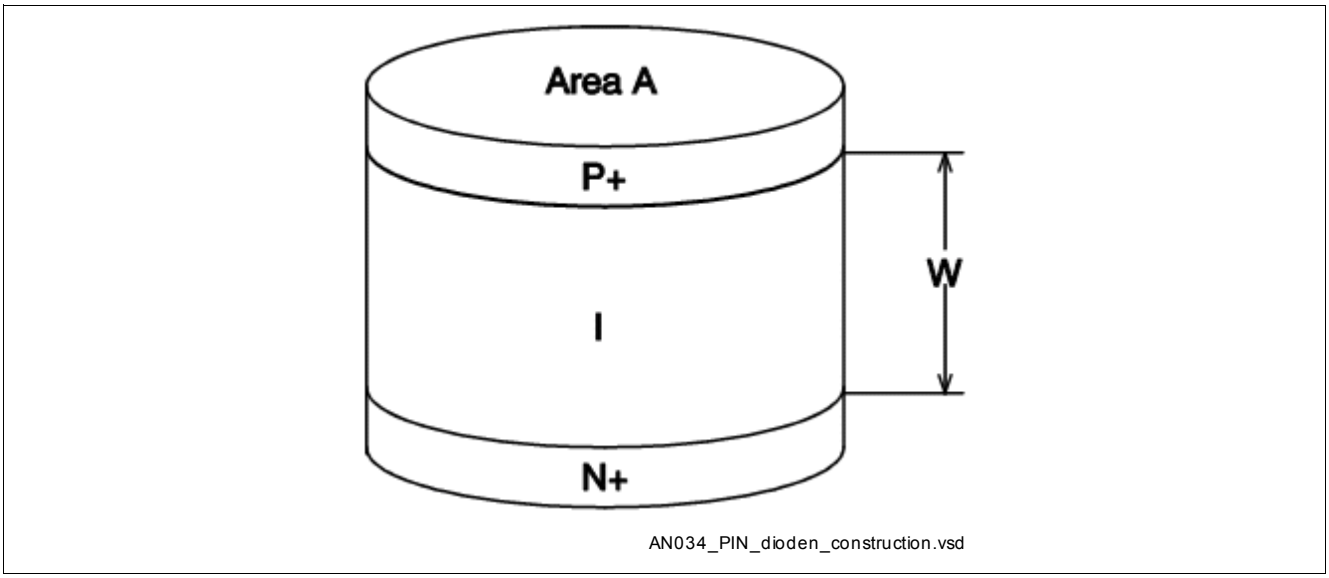


Figure 1 PIN Diode construction

A lightly doped I-region (intrinsic) separates the heavily doped P+ and N+ regions. This forms a capacitor at zero bias:

(1)

$$C_0 = \frac{\varepsilon A}{W}$$

Where:

C_0: capacitance at zero bias

ε: dielectric constant of I-zone material

The intrinsic region has a high resistance which can be calculated at zero bias by the following equation:

(2)

$$r_0 = \frac{\sigma W}{A}$$

Where:

r_0: resistance at zero bias

σ: specific resistance of I-region (dependant on the doping concentration)

In forward bias the injection of carriers from the P+ and N+ region reduces the specific resistance to a level below that obtained from doping alone. The carrier concentration is determined by both injection and recombination processes; recombination is quantified by the term ‘carrier lifetime‘. The resulting resistance for radio frequencies can be approximated by the following equation:

(3)

$$r_f = \frac{W^2}{(\mu_n + \mu_p) \cdot \tau I_f}$$

Where:

r_f: forward resistance for radio frequencies

I_f: forward current

μ_n: electron mobility

μ_p: hole mobility

τ: carrier lifetime

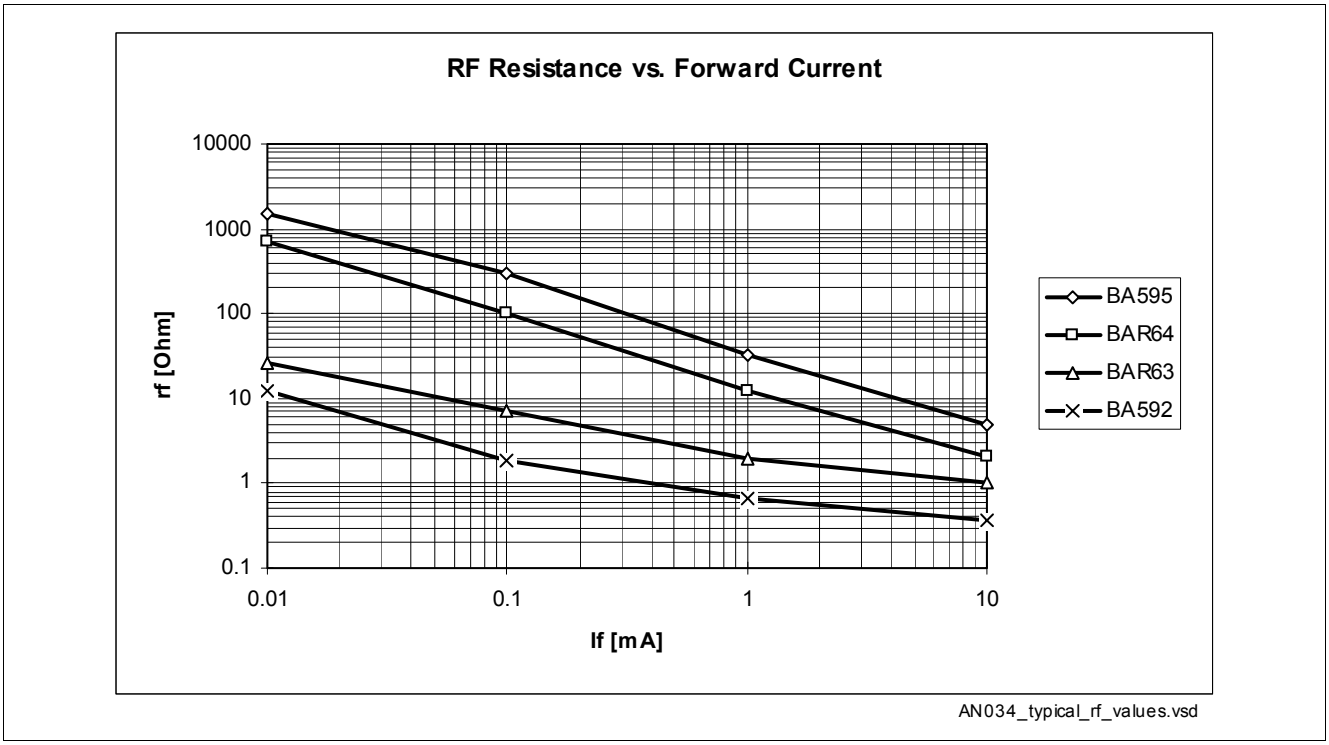


Figure 2 Typical values

To make things more complicated τ is not constant- it decreases with higher I_f - because recombination is facilitated when more carriers are available. Additionally τ is reduced by ‘traps‘(e.g. fold atoms) and border effects around the active I-zone. Refer to **Figure 2** for a typical values of r_f resistances.

Table 1 Overview of diode parameters

	A	W	τ	r_f	C_0
BA595	Medium	High	1600 ns	High	230 fF
BAR64	High	Medium	1400 ns	Medium	300 fF
BAR63	Low	Low	80 ns	Low	300 fF
BA592	Medium	Very low	120 ns	Very low	1200 fF

As a rule of thumb PIN diodes should be operated at frequencies considerably higher than the reciprocal of τ:

(4)

$$f \geq \frac{10}{\tau}$$

This avoids non-linear intermodulation and harmonics effects by preventing modulation of the charge carrier concentration.

How can you actually measure the electrical characteristics of a diode? r_f and C_t under bias condition can be obtained by using an impedance analyzer e.g. HP4291. Another test setup gives us the carrier lifetime (**Figure 3**).

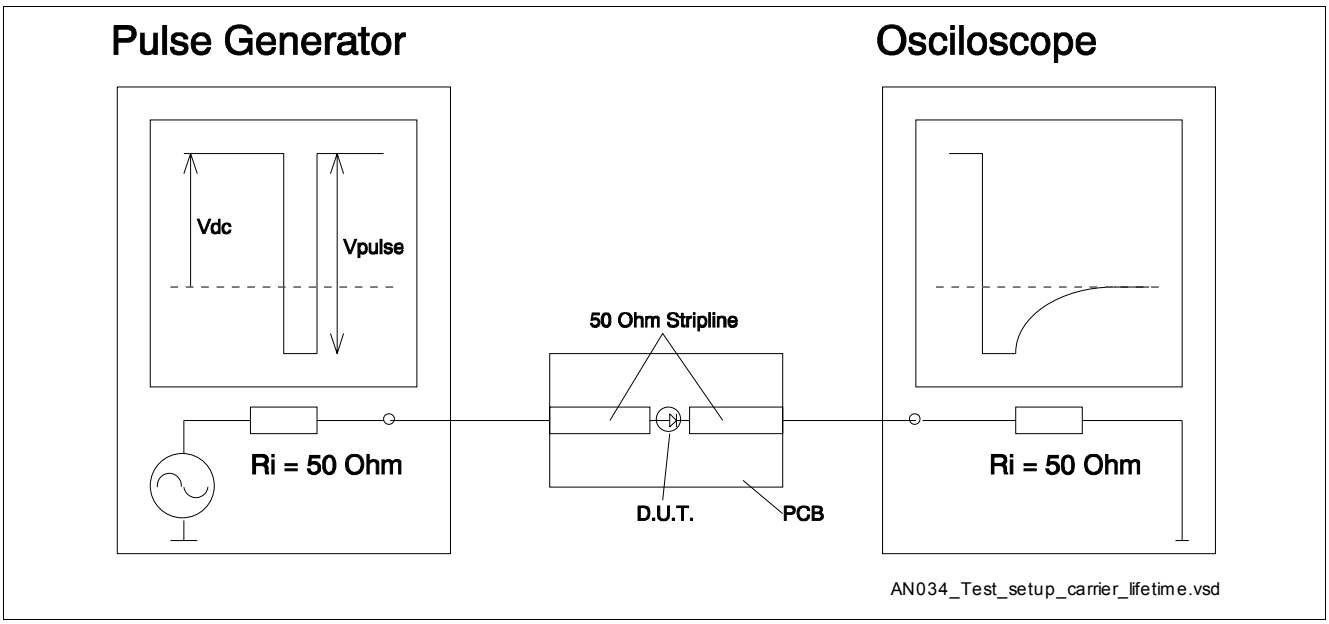


Figure 3 Test setup for measuring the carrier lifetime

The pulse width of the negative pulse from the generator must exceed the expected carrier lifetime. The DC conditions and pulse amplitude should be adjusted to obtain the oscilloscope trace shown in **Figure 4**: in this example I_f = 10 mA (0.5 V across 50 Ω) in forward bias, I_r = 6 mA in reverse bias. The time τ_{rr} (reverse recovery time) measured from the falling slope of the pulse to the time where it reaches 3 mA reverse bias given an estimate for τ, which is due to the following relationship between τ_{rr} and τ:

(5)

$$\tau_{rr} = \tau \ln \cdot \left(1 + \frac{I_f}{I_r}\right)$$

For chosen I_f and I_r the natural logarithm in the equation reduces to 1.

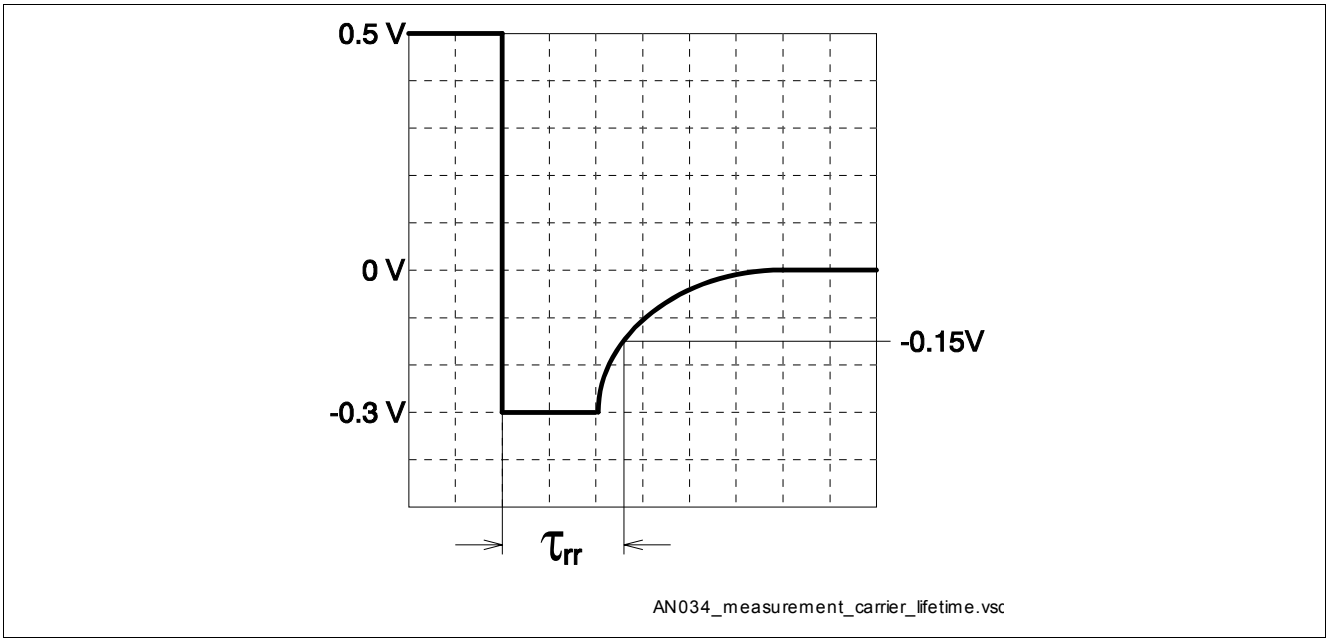


Figure 4 Oscilloscope trace showing the measurement of carrier lifetime